

NAVSHIPS 0967-000-0120

**ELECTRONICS
INSTALLATION
AND
MAINTENANCE BOOK**

ELECTRONIC CIRCUITS

**DEPARTMENT OF THE NAVY
NAVAL SHIP ENGINEERING CENTER**

PUBLISHED: DECEMBER 1972

The designation "FOR OFFICIAL USE ONLY" signifies that this document may not be further released to the public or to sources outside the U. S. Government without the permission of the Commander, Naval Ship Systems Command.

FOR OFFICIAL USE ONLY

**BOX SCORE
ELECTRONIC CIRCUITS HANDBOOK
NAVSHIPS 0967-000-0120**

EDITION	PUBLICATION DATE	STOCK NUMBER
Basic	December 1972	0967-000-0120

LIST OF EFFECTIVE PAGES

Page Number	Change In Effect	Page Number	Change In Effect
FRONT MATTER		SECTION 11 - MIXING, HETERODYNING, AND AUTOMATIC CONTROL CIRCUITS	
Title Page/ii iii thru xii A/B	Original Original Original	11-1 thru 11-74	Original
SECTION 1 - INTRODUCTION		SECTION 12 - MODULATORS	
1-1 thru 1-5	Original	12-1 thru 12-109	Original
SECTION 2 - POWER SUPPLIES		SECTION 13 - SPECIAL CIRCUITS	
2-1 thru 2-142	Original	13-1 thru 13-102	Original
SECTION 3 - VOLTAGE REGULATORS		SECTION 14 - SYNCHROS AND SERVOS	
3-1 thru 3-60	Original	14-1 thru 14-20	Original
SECTION 4 - FILTERS		SECTION 15 - COUNTERS	
4-1 thru 4-45	Original	15-1 thru 15-13	Original
SECTION 5 - AMPLIFIERS		SECTION 16 - LOGIC CIRCUITS	
5-1 thru 5-318	Original	16-1 thru 16-117	Original
SECTION 6 - OSCILLATORS			
6-1 thru 6-165	Original		
SECTION 7 - MULTIVIBRATORS			
7-1 thru 7-64	Original		
SECTION 8 - SWEEP GENERATORS			
8-1 thru 8-22	Original		
SECTION 9 - CRT CIRCUITS			
9-1 thru 9-50	Original		
SECTION 10 - DETECTORS			
10-1 thru 10-87	Original		

TABLE OF CONTENTS

Part	Page	Part	Page
SECTION 1 - INTRODUCTION			
Purpose	1-1	2-5 SILICON-CONTROLLED RECTIFIERS	2-102
Use	1-1	Single-Phase, Full-Wave SCR	2-102
Scope	1-2	Three-Phase, Full-Wave SCR	2-104
Handbook Changes	1-3	Bridge-Connected SCR	2-108
Definitions of Letter Symbols Used	1-3	SCR Inverter (DC to AC)	2-110
		SCR Regulator	2-113
SECTION 2 - POWER SUPPLIES			
2-0 INTRODUCTION	2-1	2-6 ELECTROMECHANICAL POWER SUPPLIES	2-117
Electron Tube Diode Principles	2-1	Dynamotor	2-117
Electron Tube Diode Ratings	2-1	Inverter	2-120
Semiconductor Diode Principles	2-1	Nonsynchronous Vibrator Supply	2-129
Silicon Controlled Rectifiers	2-7	Synchronous Vibrator Supply	2-136
Rectifiers	2-10	SECTION 3 - VOLTAGE REGULATORS	
Basic Power Supplies	2-10	3-0 INTRODUCTION	3-1
Multiphase Power Supplies	2-11	Voltage Regulation Circuits	3-1
Voltage Multiplier Power Supplies	2-12	Electronic Regulators	3-1
DC-to-DC Converters	2-12	Electromechanical Regulators	3-4
Rotating Electromechanical Systems	2-12	Electromagnetic Regulators	3-9
Vibration Type Power Supplies	2-13	3-1 ELECTRONIC VOLTAGE REGULATORS	3-16
2-1 BASIC POWER SUPPLY CIRCUITS	2-15	Gas-Tube Regulator	3-16
Single-Phase, Half-Wave Rectifier (Electron Tube)	2-15	Breakdown Diode Shunt-Type Regulator	3-19
Single-Phase, Half-Wave Rectifier (Semiconductor)	2-18	Shunt Transistor Regulator	3-22
Single-Phase, Full-Wave Rectifier (Electron Tube)	2-21	Series Transistor Regulator	3-23
Single-Phase, Full-Wave Rectifier (Semiconductor)	2-25	DC Regulator Using Pentode Amplifier	3-25
Single-Phase, Full-Wave Bridge Rectifier (Electron Tube)	2-27	DC Regulator Using Cascode Twin-Triode Amplifier	3-30
Single-Phase, Full-Wave Bridge Rectifier (Semiconductor)	2-33	DC Regulator Using Cascade Twin-Triode Amplifier	3-33
2-2 MULTIPHASE POWER SUPPLIES	2-37	DC Regulator Using Twin-Triode and Pentode (Balanced Input)	3-37
Three-Phase, Half-Wave (Single "Y" Secondary) Rectifier (Electron Tube)	2-37	DC Regulator Using Twin-Triode and Pentode (Balanced Output)	3-45
Three-Phase, Half-Wave (Single "Y" Secondary) Rectifier (Semiconductor)	2-41	Base-Controlled Regulator (Semiconductor)	3-51
Three-Phase, Full-Wave (Single "Y" Secondary) Rectifier (Electron Tube)	2-43	Emitter-Follower Regulator (Semiconductor)	3-53
Three-Phase, Full-Wave (Single "Y" Secondary) Rectifier (Semiconductor)	2-53	Constant-Current Regulator (Semiconductor)	3-55
Three-Phase, Half-Wave (Double "Y" Secondary) Rectifier (Electron Tube)	2-58	Current-Limited Series Voltage Regulator (Semiconductor)	3-56
Three-Phase, Half-Wave (Double "Y" Secondary) Rectifier (Semiconductor)	2-62	High-Voltage Series Stack Regulator (Semiconductor)	3-58
2-3 VOLTAGE MULTIPLIERS	2-65	SECTION 4 - FILTERS	
Half-Wave Voltage Doubler (Electron Tube)	2-65	4-1 POWER SUPPLY	4-1
Half-Wave Voltage Doubler (Semiconductor)	2-67	Power Supply Filters (General)	4-1
Full-Wave Voltage Doubler (Electron Tube)	2-69	Shunt-Capacitor Filter	4-9
Full-Wave Voltage Doubler (Semiconductor)	2-72	R-C Capacitor-Input Filter	4-12
Voltage Tripler (Electron Tube)	2-75	L-C Capacitor-Input Filter	4-15
Voltage Tripler (Semiconductor)	2-78	L-C Choke-Input Filter	4-18
Voltage Quadrupler (Electron Tube)	2-81	Resonant Filter	4-23
Voltage Quadrupler (Semiconductor)	2-84	4-2 SIGNAL	4-26
2-4 DC-to-DC CONVERTERS	2-87	High-Pass Filters	4-26
DC-to-DC Converter, Audio Oscillator Type (Electron Tube)	2-87	Low-Pass Filters	4-31
DC-to-DC Converter, Square-Wave (Audio) Oscillator Type (Semiconductor)	2-90	Band-Pass Filters	4-38
DC-to-DC Converter, R-F Oscillator Type (Electron Tube)	2-95	Band-Rejection Filters	4-41
Dosimeter Charger (DC-to-DC Converter) (Semiconductor)	2-98	SECTION 5 - AMPLIFIERS	
		5-0 INTRODUCTION	5-1
		Biasing Methods (Electron Tube)	5-1
		Biasing Methods (Semiconductor)	5-6
		Triode Common-Base Circuits	5-6
		Triode Common-Emitter Circuits	5-10
		Diode Stabilization Circuits	5-17
		Classes of Amplifier Operation (Electron Tube)	5-24
		Classes of Amplifier Operation (Semiconductor)	5-27

TABLE OF CONTENTS

Part		Page	Part		Page
5-0	INTRODUCTION (Continued)		5-4	CATHODE FOLLOWERS	5-154
	Coupling Methods (Electron Tube)	5-30		Basic Cathode Followers (Electron Tube)	5-154
	Coupling Methods (Semiconductor)	5-34		Low-Level Video Cathode Follower (Electron Tube)	5-159
	Time Constants	5-38		Pulse Cathode Follower (Electron Tube)	5-161
5-1	DC AMPLIFIERS	5-43	5-5	VIDEO	5-163
	Direct-Coupled (DC) Amplifier (Electron Tube)	5-43		Video Amplifiers (General)	5-163
	Direct-Coupled (DC) Amplifier (Semiconductor)	5-46		Triode Video Amplifier (Electron Tube)	5-164
	Push-Pull Direct-Coupled (DC) Amplifier (Electron Tube)	5-53		Pentode Video Amplifier	5-170
	DC Chopper Amplifier (Electron Tube)	5-57		Triode Video Driver Amplifier (Electron Tube)	5-173
	DC Chopper Amplifier (Semiconductor)	5-61		Beam-Power Video Driver Amplifier	5-176
5-2	AUDIO AMPLIFIERS	5-66		Chain (Mixer, Amplifier, and Driver)	
	Audio Amplifiers (General)	5-66		Video Amplifier (Electron Tube)	5-179
	R-C Coupled Triode Audio Amplifier (Electron Tube)	5-70		Cathode-Coupled (In-Phase) Video Amplifier	5-182
	R-C Coupled Triode Audio Amplifier (Semiconductor)	5-72		Wide-Band Video Amplifier (Semiconductor)	5-184
	R-C Coupled Pentode Audio Amplifier	5-76	5-6	R-F	5-189
	Impedance-Coupled Audio Amplifier (Electron Tube)	5-78		R-F Amplifiers (General)	5-189
	Impedance-Coupled Audio Amplifier (Semiconductor)	5-82		Triode Grounded-Grid R-F Amplifier	5-193
	Transformer-Coupled Audio Amplifier (Electron Tube)	5-85		Pentode R-F Voltage Amplifier	5-197
	Transformer-Coupled Audio Amplifier (Semiconductor)	5-89		Cascade R-F Amplifier (Electron Tube)	5-200
	Single-Ended, R-C Coupled, Triode Audio Power Amplifier (Electron Tube)	5-93		Cascode R-F Amplifier (Electron Tube)	5-203
	Single-Ended, R-C Coupled Pentode Audio Power Amplifier	5-97		Tuned Interstage (I-F) Amplifier (Electron Tube)	5-208
	Push-Pull Audio Power Amplifier (Electron Tube)(Class A, AB, & B)	5-101		Tuned Interstage (I-F) Amplifier (Semiconductor)	5-213
	Push-Pull Audio Power Amplifier (Semiconductor)(Class A, AB, & B)	5-109		Triode R-F Buffer Amplifier (Electron Tube)	5-217
	Push-Pull, Single-Ended Complementary Symmetry Audio Power Amplifier (Semiconductor)	5-115		Pentode R-F Buffer Amplifier (Electron Tube)	5-221
	Push-Pull, Single-Ended, Series-Connected Audio Power Amplifier (Semiconductor)	5-119		Tuned Common-Base R-F Amplifier	5-225
	Push-Pull, Capacitance-Diode Coupled Audio Power Amplifier (Semiconductor)	5-121		Tuned Common-Emitter R-F Amplifier	5-229
	Compound-Connected Audio Power Amplifier (Semiconductor)	5-123		Single-Ended R-F Amplifier (Electron Tube) (Class B or C)	5-233
	Bridge-Connected Audio Power Amplifier (Semiconductor)	5-127		Push-Pull R-F Amplifier (Class B or C)	5-242
	Feedback Amplifiers	5-129		Traveling-Wave Tube R-F Amplifier	5-247
	Positive Feed Amplifier (Direct, Regenerative)(Electron Tube)	5-130		Multicavity Klystron R-F Amplifier	5-251
	Negative Feedback Amplifier (Inverse, Degenerative)(Electron Tube)	5-133	5-7	RF FREQUENCY MULTIPLIERS	5-257
5-3	PHASE INVERTERS	5-136		RF Frequency Multipliers (General)	5-257
	Transformer Type Phase Inverter (Electron Tube)	5-136		Pentode RF Frequency Multiplier	5-257
	Single-Stage Paraphase Inverter (Electron Tube)	5-137		Push-Push RF Frequency Multiplier (Electron Tube)	5-261
	Single-Stage Paraphase Inverter (Semiconductor)	5-139	5-8	DEFLECTION	5-265
	Two-Stage Paraphase Inverter (Electron Tube)	5-141		Deflection Amplifiers (General)	5-265
	Two-Stage Paraphase Inverter (Semiconductor)	5-145		Basic Deflection Amplifier (Electron Tube)	5-266
	Paraphase, Cathode-Coupled Inverter (Electron Tube)	5-148		Voltage Deflection Amplifier (For Electro-static CRT)(Electron Tube)	5-268
	Differential Paraphase Inverter (Electron Tube)	5-150		Current Deflection Amplifier (For Electro-magnetic CRT)(Electron Tube)	5-273
			5-9	OPERATIONAL AMPLIFIERS	5-279
				Operational Amplifiers (General)	5-279
				Combining Amplifier (Electron Tube)	5-279
				Combining Amplifier (Semiconductor)	5-281
				Coincidence Amplifier (Electron Tube)	5-283
				Derivative Amplifier (Electron Tube)	5-285
				Derivative Amplifier (Semiconductor)	5-286
				Differential Amplifier (Electron Tube)	5-288
				Differential Amplifier (Semiconductor)	5-290
				Balanced Differential Amplifier (Semiconductor)	5-292
				Single-Ended Output Differential Amplifier (Semiconductor)	5-293
				Balanced Super-Alpha Differential Amplifier (Semiconductor)	5-295

TABLE OF CONTENTS

Part		Page	Part		Page
5-9	OPERATIONAL AMPLIFIERS (Continued)		6-4	BLOCKING AND SHOCK EXCITED	6-134
	Direct-Coupled Cascaded Differential Amplifier (Semiconductor)	5-297		Free-Running PRF Generator (Electron Tube)	6-134
	Direct-Coupled Cascaded, Complementary-Symmetry Differential Amplifier (Semiconductor)	5-300		Free-Running PRF Generator (Semiconductor)	6-137
	Exponential Amplifier (Electron Tube)	5-302		Parallel-Triggered Blocking Oscillator (Electron Tube)	6-141
	Exponential Amplifier (Semiconductor)	5-304		Series-Triggered Blocking Oscillator (Electron Tube)	6-144
	Integrating Amplifier (Electron Tube)	5-306		Triggered Block Oscillator (Semiconductor)	6-147
	Integrating Amplifier (Semiconductor)	5-308		Fast-Recovery Blocking Oscillator (Electron Tube)	6-149
	Logarithmic Amplifier (Electron Tube)	5-309		Nonsaturating Diode-Clamped Blocking Oscillator (Semiconductor)	6-152
	Logarithmic Amplifier (Semiconductor)	5-311		Pulse-Frequency Divider (Electron Tube)	6-154
	Summing Amplifier (Electron Tube)	5-313		Distance-Mark Divider (Electron Tube)	6-157
	Summing Amplifier (Semiconductor)	5-315		Shock-Excited Ringing Oscillator (Electron Tube)	6-160
	Ring-Bridge Amplifier (Semiconductor)	5-316		Shock-Excited Peaking Oscillator (Electron Tube)	6-163
	SECTION 6 - OSCILLATORS			SECTION 7 - MULTIVIBRATORS	
6-1	ELECTRONIC	6-1	7-1	ASTABLE	7-1
	Armstrong (Tickler-Coil) Oscillator (Electron Tube)	6-1		Astable (Free-Running) Multivibrators (General)	7-1
	Armstrong (Tickler-Coil) Oscillator (Semiconductor)	6-7		Basic Astable (Free-Running) Multivibrator (Electron Tube)	7-1
	Hartley Oscillator (Electron Tube)	6-11		Basic Astable (Free-Running) Multivibrator (Semiconductor)	7-5
	Hartley Oscillator (Semiconductor)	6-14		Pentode Electron-Coupled Astable Multivibrator	7-10
	Colpitts Oscillator (Electron Tube)	6-18		Triode Cathode-Coupled Astable Multivibrator	7-12
	Colpitts Oscillator (Semiconductor)	6-22	7-2	BISTABLE	7-20
	Clapp Oscillator (Electron Tube)	6-25		Bistable (Start-Stop) Multivibrators (General)	7-20
	Clapp Oscillator (Semiconductor)	6-27		Basic Flip-Flop (Eccles-Jordan) Multivibrator (Electron Tube)	7-21
	Tuned-Plate Tuned-Grid Oscillator	6-29		Basic Flip-Flop Multivibrator (Semiconductor)	7-24
	Electron-Coupled Oscillator (Electron Tube)	6-33		Pentode Flip-Flop (Eccles-Jordan) Multivibrator	7-28
	Utraudion Oscillator (Electron Tube)	6-37		Direct-Coupled (or Binary) Multivibrator (Semiconductor)	7-32
	R-C Phase-Shift Oscillator (Electron Tube)	6-40		Squaring Multivibrator (Semiconductor)	7-35
	R-C Phase-Shift Oscillator (Semiconductor)	6-42		Saturating Multivibrator (Semiconductor)	7-38
	Wien-Bridge Oscillator (Electron Tube)	6-44		Nonsaturating Multivibrator (Semiconductor)	7-41
	Wien-Bridge Oscillator (Semiconductor)	6-47		Relay Control Multivibrator (Semiconductor)	7-45
	Magnetostriction Oscillators	6-49	7-3	MONOSTABLE	7-47
	Negative Resistance Oscillators (General)	6-51		Monostable (One-Shot) Multivibrators (General)	7-47
	Dynatron Oscillator	6-53		Triode Plate-to-Grid-Coupled Monostable Multivibrator	7-48
	Transistor (Negative GM) Oscillator	6-56		Triode Common-Cathode-Resistor Coupled Monostable Multivibrator	7-51
	Kallitron (Push-Pull) Oscillator (Electron Tube)	6-59		Basic One-Shot Transistor Multivibrator	7-56
6-2	CRYSTAL	6-61		Phantastron Multivibrator	7-58
	Crystal Oscillator (General)	6-61			
	Grid-Cathode (Miller) Crystal Oscillator (Electron Tube)	6-67			
	Grid-Plate (Pierce) Crystal Oscillator (Electron Tube)	6-72			
	Electron-Coupled Crystal Oscillator (Electron Tube)	6-79			
	Overtone Cathode-Coupled (Butler) Crystal Oscillator (Electron Tube)	6-82			
	Overtone Crystal Oscillator (Semiconductor)	6-86			
	Tickler-Coil Feedback Crystal Oscillator (Semiconductor)	6-90			
	Colpitts Crystal Oscillator (Semiconductor)	6-94			
6-3	TUNED LINE	6-101			
	Tuned-Line (General)	6-101			
	Lighthouse-Tube Oscillator	6-103			
	Lecher-Wire Oscillator	6-106			
	Magnetron Oscillator	6-109			
	Reflex Klystron Oscillator	6-124			
	Backward Wave (Carcinotron) Oscillator	6-131			

TABLE OF CONTENTS

Part		Page	Part		Page
	SECTION 8 - SWEEP GENERATORS				
8-1	SAWTOOTH	8-1	10-2	FM (Continued)	
	Sawtooth Wave, Gas-Tube Sweep Generator Circuits (General)	8-1		Ratio Detector (Electron Tube)	10-47
	Triode Sawtooth-Wave Sweep Generator Circuits (General)	8-1		Ratio Detector (Semiconductor)	10-52
	Semiconductor Sawtooth Wave Circuits (General)	8-1	10-3	Travis Discriminator (Electron Tube)	10-56
	Neon Gas-Tube Sweep Generator	8-2		Gated-Beam Detector	10-59
	Thyratron Sweep Generator	8-3		VIDEO	10-64
	Unijunction (Double-Base Diode) Sawtooth Generator	8-5		Video Detectors (General)	10-64
	Four-Layer Diode Sawtooth Generator	8-7		Basic Video Detector (Electron Tube)	10-64
	Basic Triode Sawtooth Sweep Generator (Electron Tube)	8-13	10-4	Basic Video Detector (Semiconductor)	10-66
	Bootstrap Sweep Generator (Electron Tube)	8-15		BALANCED	10-67
	Triode Trapezoidal-Wave Sweep Generator (Electron Tube)	8-17		Balanced Detectors (General)	10-67
		8-20		Basic Diode Balanced Detector (Electron Tube)	10-68
	SECTION 9 - CRT CIRCUITS			Basic Transistor Balanced Detector	10-70
9-1	ELECTROSTATIC	9-1		Lattice Type Diode Balanced Detector (Semiconductor)	10-73
	Electrostatic Cathode-Ray Tube Circuits (General)	9-1		Ring-Type Diode Detector (Electron Tube)	10-75
	Basic Electrostatic Oscilloscope Circuits	9-1		Balanced Bridge Detector (Electron Tube)	10-77
	Synchroscope	9-9		Triode, Push-Pull Output Balanced Detector (Electron Tube)	10-79
	CRT Display Circuits	9-16		Triode, Parallel Output Balanced Detector (Electron Tube)	10-82
9-2	ELECTROMAGNETIC	9-23		Pentagrid Balanced Detector	10-85
	Electromagnetic Cathode-Ray Tube Circuits (General)	9-23	11-1	SECTION 11 - MIXING, HETERODYNING, AND AUTOMATIC CONTROL CIRCUITS	
	Plan Position Indicator (PPI)	9-24		MIXER CIRCUITS	11-1
	Other Types of Electromagnetic Scans	9-34		Audio Mixers (General)	11-1
9-3	ANCILLARY CIRCUITS	9-45		Common Plate-Load Audio Mixer	11-1
	Blanking Circuits	9-45		Separate Plate-Load Audio Mixer	11-5
	RC Restorer	9-46		Video Mixers (General)	11-7
	Damper and Flyback Circuits	9-48		Common-Cathode Video Mixer	11-8
				Common-Plate Video Mixer	11-13
	SECTION 10 - DETECTORS		11-2	HETERODYNING CIRCUITS	11-17
10-1	AM	10-1		Mixers (General)	11-17
	AM Detectors (General)	10-1		Diode Mixer (Electron Tube)	11-19
	Diode Detectors (Electron Tube)	10-2		Diode Mixer (Semiconductor)	11-21
	Voltage Output Diode Detector (Semiconductor)	10-6		Microwave Diode Mixer (Semiconductor)	11-25
	Current Output, Diode Detector (Semiconductor)	10-8		Triode Mixer (Electron Tube)	11-27
	Diode Detector with AVC (Electron Tube)	10-9	11-3	Triode Mixer (Semiconductor)	11-29
	Diode Detector with Noise Limiter (Electron Tube)	10-11		Autodyne Converter (Semiconductor)	11-32
	Grid-Leak Detector	10-13		Pentode Mixer	11-34
	Plate Detector	10-17		Balanced Mixer (Electron Tube)	11-36
	Common-Emitter Detector	10-21		Pentagrid Mixer	11-39
	Common-Base Detector	10-23		Pentagrid Converter	11-41
	Infinite Impedance Detector (Electron Tube)	10-24		AGC CIRCUITS	11-46
	Regenerative Detector (Electron Tube)	10-27		AGC (AVC) Circuits (General)	11-46
	Super-Regenerative Detector (Electron Tube)	10-31		Simple AGC Circuit (Electron Tube)	11-53
	Product Detector (Electron Tube)	10-35		Emitter-Current Control AGC	11-55
	Coherent (Synchronous Detector (Electron Tube))	10-37		Auxiliary Diode Control Circuit (Semiconductor)	11-58
10-2	FM	10-40	11-4	Collector Voltage Control Circuit (Semiconductor)	11-60
	FM (or PM) Detectors (General)	10-40		AGC-Controlled Audio Amplifier (Electron Tube)	11-62
	Foster-Seeley Discriminator (Electron Tube)	10-41		AFC CIRCUITS	11-64
	Foster-Seeley Discriminator (Semiconductor)	10-45		AFC Circuits (General)	11-64
				Phantastron AFC Circuit	11-66
				Thyratron AFC Circuit	11-68
				Reactance Tube AFC Circuit	11-70
				DC Amplifier AFC System (Electron Tube)	11-72

TABLE OF CONTENTS

Part		Page	Part		Page
	SECTION 12 - MODULATORS				
12-1	AM	12-1	13-2	LIMITERS (Continued)	
	Amplitude Modulation (Electron Tube)	12-1		Two-Diode, Positive and Negative	
	(General)	12-1		Lobe Diode Limiter (Semiconductor)	13-28
	Amplitude Modulation (Semiconductor)	12-4		Triode Grid Limiter	13-29
	(General)	12-4		Triode Saturation Limiter (Electron	
	Choke (Heising) Modulator (Electron	12-4		Tube)	13-33
	Tube)	12-4		Triode Cutoff Limiter (Electron	
	Plate Modulator	12-8		Tube)	13-35
	Collector-Injection Modulator	12-22		Triode Overdriven Amplifier Limiter	13-43
	Control Grid Modulator	12-24		Video Limiter (Electron Tube)	13-44
	Base-Injection Modulator	12-28		R-F Pentode Limiter (Electron Tube)	13-47
	Cathode Modulator	12-33	13-3	CLAMPERS	13-50
	Emitter-Injection Modulator	12-40		Diode Clamper (Electron Tube)	13-50
	Suppressor-Grid Modulator	12-43		Diode Clamper (Semiconductor)	13-53
	Screen Grid Modulator	12-50		Biased Diode Clamper (Electron Tube)	13-56
	Plate and Screen Modulator	12-56		Biased Diode Clamper (Semiconductor)	13-59
	Series Modulator (Electron Tube)	12-63		Triode Clamper (Electron Tube)	13-61
	Double Sideband Modulator (Electron	12-65		Triode, Basic Common-Base Clamper	13-63
	Tube)	12-65		Synchronized Triode Clamper (Elec-	
12-2	SINGLE SIDEBAND	12-70		tron Tube)	13-65
	Single Sideband Modulation (SSB)	12-70	13-4	WAVESHAPING CIRCUITS	13-67
	(General)	12-70		R-C Differentiator	13-67
	Balanced (Push-Pull Carrier Input)	12-72		R-L Differentiator	13-69
	Modulator (Electron Tube)	12-72		R-C Integrator	13-72
	Balanced (Parallel Carrier Input)	12-75		R-L Integrator	13-74
	Modulator (Electron Tube)	12-75		Saturable-Core Reactor Peaking	
	Balanced (Parallel Carrier Input)	12-78		Circuit	13-76
	Modulator (Semiconductor)	12-78		Semiconductor Pulse Shaper	13-77
	Balanced Complementary Symmetry	12-81	13-5	TIME DELAY CIRCUITS	13-80
	Modulator (Semiconductor)	12-81		Basic Phantastron Circuits	13-80
	Balanced Bridge Modulator (Electron	12-84		Fast-Recovery Phantestron Circuit	13-86
	Tube)	12-84		Electromechanical (Acoustic) Delay	
	Product Modulator (Electron Tube)	12-87		Lines	13-91
12-3	FM	12-89		Electromagnetic Delay Lines	13-93
	Frequency Modulation (FM)(General)	12-89		SECTION 14 - SYNCHROS AND SERVOS	
	Basic Reactance Modulator (Electron	12-90	14-1	SERVOMECHANISMS	14-1
	Tube)	12-90		Servomechanism Circuits (General)	14-1
	Basic Reactance Modulator (Semicon-	12-93		Synchro Control Systems	14-2
	ductor)	12-93		Servo Motor-Controller Circuit	14-11
	Balanced Reactance Modulator (Elec-	12-95		Resolver-Driver Circuit	14-14
	tron Tube)	12-95		Phase Sensitive Null Detector	
12-4	PHASE	12-98		Circuit	14-17
	Phase Modulation (PM)(General)	12-98		SECTION 15 - COUNTERS	
	Basic Phase Modulator (Electron	12-99	15-1	DIODE	15-1
	Tube)	12-99		Positive Diode Counter (Electron	
	Phasitron Modulator (Electron Tube)	12-102		Tube)	15-1
12-5	PULSE	12-104		Positive Diode Counter (Semicon-	
	Pulse Modulation (General)	12-104		ductor)	15-3
	Spark Gap Modulator (Electron Tube)	12-104		Negative Diode Counter (Electron	
	Thyratron (Gas-Tube) Modulator	12-106		Tube)	15-5
	Hard-Tube Modulator	12-108		Negative Diode Counter (Semicon-	
				ductor)	15-7
	SECTION 13 - SPECIAL CIRCUITS			Step-By-Step Counter (Electron Tube)	15-10
13-1	SPECIAL PURPOSE TRANSISTORS & CIRCUITS	13-1		Step-By-Step Counter (Semiconductor)	15-12
	Tetrode, Power, and Special Purpose	13-1		SECTION 16 - LOGIC CIRCUITS	
	Transistors and Circuits	13-1			
13-2	LIMITERS	13-13	16-0	INTRODUCTION	16-1
	Series, Positive or Negative Lobe	13-13		Logic Polarity	16-1
	Diode Limiter (Electron Tube)	13-13		Gating Circuits	16-2
	Series, Positive or Negative Lobe	13-16		Logic Computation	16-3
	Diode Limiter (Semiconductor)	13-16		Input Signals	16-4
	Parallel, Positive or Negative Lobe	13-18		Failure Analysis	16-4
	Diode Limiter (Electron Tube)	13-18			
	Parallel, Positive or Negative Lobe	13-23	16-1	SWITCH LOGIC	16-5
	Diode Limiter (Semiconductor)	13-23		Switch Logic (General)	16-5
	Two-Diode, Positive and Negative	13-26		OR Circuits	16-7
	Lobe Diode Limiter (Electron Tube)	13-26		AND Circuits	16-10

TABLE OF CONTENTS

Part		Page	Part		Page
16-1	SWITCH LOGIC (Continued)		16-4	COUNTERS	16-85
	Flip-Flop Circuits	16-11		Logic Counters (General)	16-85
	Two-Way and Three-Way Circuits	16-13		Operational Counter	16-85
	Simplification Principles	16-15		Ring Counter	16-87
				Decimal Counter	16-90
16-2	DIODE LOGIC	16-18	16-5	REGISTERS	16-95
	Diode Logic (General)	16-18		Logic Registers (General)	16-95
	OR Gate	16-18		Clear Register	16-95
	AND Gate	16-20		Shift Register	16-97
	Rectangular Matrices	16-23		Complement Register	16-98
	Encoding Matrices	16-26		Double-Line Transfer Register	16-101
	Decoding Matrices	16-28		Circulating Register	16-102
	Two-Level AND-OR Gate	16-31		Accumulator Register	16-103
	Half-Adder Circuits	16-32			
	Full Adder	16-34	16-6	MEMORY DEVICES	16-106
16-3	TRANSISTOR LOGIC	16-40		Memory Devices (General)	16-106
	Transistor Logic (General)	16-40		Magnetic Core Memory	16-106
	OR Gate	16-40		Memory Driver Circuit	16-108
	AND Gate	16-42		Data Memory Circuit	16-110
	NOT Gate	16-43		Magnetic Drum Memory	16-112
	NOR Gate	16-45		Magnetic Disk Memory	16-114
	NAND Gate	16-46		Magnetic Tape Memory	16-116
	Inhibit Gate	16-47			
	Dual Type (AND-OR) Gate	16-48			
	Flip-Flop Circuit	16-51			
	Resistor-Transistor Logic Flip-Flop	16-53			
	Inverter	16-54			
	Emitter-Follower Circuits	16-55			
	Lamp Drivers and Relay Pullers	16-58			
	Parallel Adder	16-60			
	Series Adder	16-63			
	Series-Parallel Adder	16-68			
	Half Subtractor	16-70			
	Full Subtractor	16-74			
	Retiming and Reshaping Circuit	16-77			
	Current Steering Gate	16-78			
	Diode-Transistor Matrix Switch	16-80			
	Diode-Transistor Flip-Flop	16-82			

PREFACE

POLICY AND PURPOSE

The Electronics Installation and Maintenance Book (EIMB) was established as the medium for collecting, publishing, and distributing, in one convenient source document, those subordinate maintenance and repair policies, installation practices, and overall electronic equipment and material-handling procedures required to implement the major policies set forth in Chapter 9670 of the Naval Ships Technical Manual. All data contained within the EIMB derive their authority from Chapter 9670 of the Naval Ships Technical Manual, as established in accordance with Article 1201, U. S. Navy Regulations.

Since its inception the EIMB has been expanded to include selected information of general interest to electronic installation and maintenance personnel. These items are such as would generally be contained in textbooks, periodicals, or technical papers, and form (along with the information cited above) a comprehensive reference document. In application, the EIMB is to be used for information and guidance by all military and civilian personnel involved in the installation, maintenance, and repair of electronic equipment under cognizance, or technical control, of the Naval Ship Systems Command (NAVSHIPS). The information, instructions, and procedures, in the EIMB supplement instructions and data supplied in equipment technical manuals and other approved maintenance publications.

ORGANIZATION

The EIMB is organized into a series of handbooks to afford maximum flexibility and ease in handling. The handbooks are stocked and issued as separate items so that individual handbooks may be obtained as needed.

The handbooks fall within two categories: general information handbooks, and equipment-oriented handbooks. The general information handbooks contain data which are of interest to all personnel involved in installation and maintenance, regardless of their equipment specialty. The titles of the various general information handbooks give an overall idea of their data content; the General Handbook includes more complete descriptions of each handbook.

The equipment handbooks are devoted to information about particular classes of equipment. They include general test procedures, adjustments, general servicing information, and field change identification data.

All handbooks of the series are listed below with their NAVSHIPS numbers. The NAVSHIPS numbers serve also as the stock numbers to be used on any requisitions submitted.

HANDBOOK TITLE	NAVSHIPS NUMBER
General Information Handbooks	
General	0967-000-0100
Installation Standards	0967-000-0110
Electronics Circuits	0967-000-0120
Test Methods and Practices	0967-000-0130
Reference Data	0967-000-0140
EMI Reduction	0967-000-0150
General Maintenance	0967-000-0160
Equipment Oriented Handbooks	
Communications	0967-000-0010
Radar	0967-000-0020
Sonar	0967-000-0030
Test Equipment	0967-000-0040
Radiac	0967-000-0050
Countermeasures	0967-000-0070
Miscellaneous	
EIMB Series (Includes all Handbooks, Changes, Binders & Dividers)	0967-000-C000
Binder, 1 Inch	0967-000-0001
Binder, 2 Inch	0967-000-0002
Binders, 2 Inch (set of 5)	0967-000-0007
Binders, 1 Inch (set of 8)	0967-000-0008
EIMB Section Dividers	0967-000-0009

PREFACE

INFORMATION SOURCES

Periodic revisions are made to provide the best current data in the EIMB and keep abreast of new developments. In doing this, many source documents are researched to obtain pertinent information. Some of these sources include the Electronics Information Bulletin (EIB), the Naval Ship Systems Command Technical News, electronics and other textbooks, industry magazines and periodicals, and various military installation and maintenance-related publications. In certain cases, NAVSHIPS publications have been incorporated into the EIMB in their entirety and, as a result, have been cancelled. A list of the documents which have been superseded by the EIMB and are no longer available is given in Section 1 of the General Handbook.

SUGGESTIONS

NAVSHIPS recognizes that users of the EIMB will have occasion to offer comments or suggestions. To encourage more active participation, a pre-addressed comment sheet is frequently provided in the back of each handbook change. Complete information should be given when preparing suggestions. Suggestors are encouraged to include their names and addresses so that clarifying correspondence can be initiated when necessary. Such correspondence will be by letter directly to the individual concerned.

If a comment sheet is not available, or if correspondence is lengthy, suggestions should be directed to the following:

Commander, Naval Ship Engineering Center
Department of the Navy
Hyattsville, Maryland 20782
Attn: Technical Data and Publications
Section (SEC 6181C)

CORRECTIONS

Report all inaccuracies and deficiencies noted in all NAVSHIPS technical publications (including this manual, ship information books, equipment manuals, drawings, and such) by a "Planned Maintenance System (PMS) Feedback Report, OPNAV 4700/7 (REV. 8-66)" or superseding form. If PMS is not yet installed in your ship, report technical publications deficiencies by any convenient means.

DISTRIBUTION

The Electronics Installation and Maintenance Book is transmitted to using activities through automatic distribution procedures. Activities not already on the EIMB distribution list and those requiring changes to the list should submit correspondence to the following:

Commander, Naval Ship Engineering Center
Department of the Navy
Hyattsville, Maryland 20782
Attn: Technical Data and Publications
Section (SEC 6181C)

Activities desiring extra copies of EIMB handbooks or binders should submit requisitions directly to Naval Publications and Forms Center, Philadelphia, Pa. Complete instructions for ordering publications are given in the Navy Stock List of Forms and Publications, NAVSUP Publication 2002.

RECORD OF CORRECTIONS MADE

CHANGE NO	DATE	CHANGES MADE	SIGNATURE

SECTION 1 INTRODUCTION

PURPOSE

The purpose of the Handbook of Electronic Circuits is to provide Naval personnel with an informative reference which describes basic electronic circuits employed in all types of electronic equipment. In addition, this handbook is used to support circuit descriptions contained in equipment technical manuals.

USE

The Handbook of Electronic Circuits will find use as a convenient reference for personnel in three general categories, as follows:

a. Experienced Technician

The experienced technician will have no great difficulty in coping with maintenance problems because of previous experience and developed maintenance skills. This individual will use the handbook as reference or review material and to increase his knowledge of electronics as new circuits are added to the handbook.

b. Technician Out-of-School

This category of technician is represented by the individual who has completed Navy training courses and has been in the fleet for some time, but his experience is limited to equipments covered in training courses and to equipment types serviced and maintained during his tour of duty with the fleet. The handbook should prove extremely valuable to this individual, especially when confronted with newer equipments, because the circuit descriptions in the handbook will help familiarize him with circuits employed in the newer equipment. Furthermore, it is likely that the technical manuals accompanying newer type equipments will refer the reader to the Handbook of Electronic Circuits for information on basic functional circuits, rather than discussing the circuits in detail.

c. Trainee or Student In-School

The trainee or student should find the information contained in the handbook useful as reference material while in training and later as review and

reference material while on duty with the fleet. As a training aid, the individual circuit descriptions may be used as suggested material for reading assignments.

The reader of the Handbook of Electronic Circuits may readily locate the circuit of interest by consulting the Table of Contents. Each circuit description includes information on the circuit application, its important characteristics, an analysis of circuit theory and operation, and a failure analysis based upon signal output indications. Since only basic circuits are presented and described, some variations in design will be found in production equipments because of one or more of the following factors: distributed inductance, capacitance, and resistance; mechanical and physical layout of component parts; circuit deviations necessitated by peculiarities in design and licensing agreements; modifications to enable operation under environmental extremes; etc. However, if the reader thoroughly understands the operation of a basic circuit presented in the handbook, he can reason out the circuit variations without too much difficulty.

The semiconductor device has become one of the outstanding scientific achievements in the electronics field in recent years. As a result, new techniques of circuit design, miniaturization, reliability, and maintenance concepts are being developed. These advances mean that the electronics technician must be prepared to maintain electronic equipments in which semiconductors are employed. To ensure that he will have the circuit information available for attaining proficiency in the maintenance of semiconductor equipment, this handbook includes semiconductor equivalents of the electron-tube circuits, whenever such equivalents exist, and in addition, includes some semiconductor circuits for which there are no electron-tube equivalents.

The Handbook of Electronic Circuits is used as supporting information for technical manuals covering electronic equipment. Technical manuals written and produced in accordance with recent publication specifications do not require a detailed theory treatment of so-called "standard" circuits,

but instead may refer to the Handbook of Electronic Circuits for a discussion of a particular functional circuit. Since the Handbook of Electronic Circuits describes a basic functional circuit and may not describe a circuit identical with the circuit employed in the equipment, the equipment technical manual discusses the circuit differences which are unique and peculiar to the equipment, or differences which represent changes or modifications to the basic functional circuit described in the handbook. Thus, the handbook will describe a basic circuit which is typical and performs a given function. If necessary, the equipment technical manual will treat only circuit differences in detail, building upon the discussion given in the Handbook of Electronic Circuits.

SCOPE

Preliminary studies made by the National Bureau of Standards leading toward electronic circuit standardization indicate that a large percentage of circuit functions could be standardized without adverse effect on equipment performance. Further, many circuits already in use for several years represent designs which have proven to be extremely reliable and have undergone only minor improvements since their initial use. Today there exists a large number of commercial and military equipments employing similar circuits to perform identical electrical functions. Thus, many similar electronic circuits can be reduced to a "common-denominator" circuit representing a basic circuit from which others performing an identical electronic function have been derived either through modification or other engineering improvements. As a result, the technician is frequently confronted by new equipments introduced to the fleet which contain circuits reflecting design improvements.

Frequently, it is up to the individual to familiarize himself with new equipment by means of the technical manual supplied with the equipment. Furthermore, circuits may be incorporated which are totally unfamiliar to the individual. In this case the use of the Handbook of Electronic Circuits should prove extremely valuable, since the circuit or group of circuits in question can likely be reduced to one or more "common-denominator" circuits. When these basic circuits, described in the handbook, are understood by the

individual, similar circuits employed in new equipment, together with their modifications or differences, can be more readily understood by the individual.

The Handbook of Electronic Circuits has been divided into sections based upon the circuit function, rather than being classified according to use as communications, radar, or sonar equipment. Several sections are devoted to general circuit information applicable to either electron-tube or semiconductor circuits. When an electron-tube circuit is described, generally the most common or likely tube type (triode, pentode) is utilized in the handbook description. Where the basic electronic theory is the same for either electron-tube or semiconductor circuits, the basic theory is discussed within the description of the electron-tube circuit and referenced from the semiconductor circuit description; thus, repetition of text is reduced.

Each description of an electronic circuit employing an electron tube or semiconductor is divided into four main parts: application, characteristics, circuit analysis, and failure analysis.

a. Application

This part of the circuit description states briefly how the circuit is employed, its common uses, and the types of equipments employing the circuit.

b. Characteristics

This part of the circuit description consists of short statements concerning technical data and other useful information to assist in circuit identification.

c. Circuit Analysis

The circuit analysis section of the description is written to outline in general terms the circuit function and to name the component parts of the circuit, to describe critical elements or component parts in detail, and to present the theory of operation of the circuit. A schematic with reference designations is used to illustrate the circuit; the associated text utilizes the reference designations when discussing the circuit. Actual values of parts do not normally appear in the text or on the schematic. Additional illustrations, such as

idealized waveforms and simplified diagrams, are provided where deemed necessary to supplement the text.

d. Failure Analysis

This portion of the circuit description is written from an output-indication standpoint based upon possible degradation of performance, changing values of components, etc. The critical circuit components affecting amplitude, time (or frequency), and waveshape are treated in the circuit analysis section. These critical components are again mentioned in the failure analysis discussion, but in this instance from the standpoint of the output signal observed.

The failure analysis discussion is intended to assist the reader in the development of a logical approach to trouble shooting. The failure analysis, as written for an individual circuit, does not pinpoint (or name) parts which "could be" defective but, in effect, encourages the reader to think logically and determine defective or deteriorating parts from the output indications noted. The text, therefore, discusses in broad terms the various troubles that might logically be suspected as the cause of an abnormal (output) indication.

Abnormal output indications observed in equipments are actually symptoms which can be elaborated upon to further localize trouble with a functional circuit. Output indications as discussed in the text elaborate on the circuit analysis text to assist the reader in analyzing a failure; thus, an arbitrary conclusion as to the source of trouble or failure is discouraged and logical reasoning is stimulated. Typical indications discussed are: no output, distorted output, low output, and incorrect output frequency. In these discussions, the reader's attention is called to the improper function within the electronic circuit. Furthermore, so-called "critical" parts (or components) were discussed in the circuit analysis portion of the circuit description from the theoretical and operational standpoint; thus, a complete story is given for the circuit. Logical thinking, therefore, can be applied to the problem of localizing the failure within the circuit after the reader has studied the entire circuit description given in the handbook.

HANDBOOK CHANGES

The handbook, as sectionalized, permits the future addition of circuits to keep the handbook

abreast of electronic developments. Also, the layout of the handbook is designed to permit the addition of new electron-tube or semiconductor circuits, as well as to permit the revision of the existing circuits.

Changes to this handbook will be publicized in the Electronic Information Bulletin (EIB), NAVSHIPS 0967-001-3000 and automatically distributed to holders of the EIMB series. Recommendations for changes and corrections to the handbook should be addressed to:

Commander, Naval Ship Engineering Center
Technical Support Branch
Technical Data and Publications Section
(SEC 6181C)

Department of the Navy
Prince George's Center
Hyattsville, Maryland 20782

DEFINITIONS OF LETTER SYMBOLS USED

Throughout this technical manual a number of letter symbols are used to indicate components, sources of voltage and current, and to differentiate between points not at the same power and voltage levels. Since the technician must be able to read, speak, and understand the jargon of the trade, he should also learn to recognize the letter symbols used as a form of shorthand notation in technical discussions and on engineering drawings and schematic diagrams. To avoid any conflict or confusion, standard letter symbols are used where available. Since definitions and usage change from time to time, an alphabetical listing of symbols used throughout this manual is included for reference (they need not be memorized).

While the basic symbol such as the capital letters E and I always indicate voltage and current, the lower case and subscript letters (or numbers) are assigned as described in the following list of symbols. Therefore, it is recommended that the user of this manual refer to this list to determine the correct meanings of the letter symbols used in the circuits in this technical manual.

a. Construction of Symbols

The letter symbols are made up of single letters with subscripts or superscripts in accordance with the following conventions:

1. Maximum, average, and root-mean-square values are represented by capital (upper case) letters; for example: I, E, P.

2. Where needed to distinguish between values in item a above, the maximum value may be represented by the subscript "m"; for example: E_m , I_m , P_m .

3. Average values may be represented by the subscript "av"; for example: E_{av} , I_{av} , P_{av} .

NOTE

When items 2 and 3 above are used, then item 1 indicates rms, or effective, values.

4. Instantaneous values of current, voltage, and power which vary with time are represented by the lower case (small) letter of the proper symbol; for example: i , e , p .

5. External resistance, impedance, etc, in the circuit external to a vacuum-tube electrode may be represented by the upper case symbol with the proper electrode subscripts; for example: R_g , R_{sc} , Z_g , Z_{sc} .

6. Values of resistance, impedance, etc, inherent within the electron tube are represented by the lower case symbol with the proper electrode subscripts; for example: r_g , Z_g , r_p , Z_p , C_{gp} .

7. The symbols "g" and "p" are used as subscripts to identify instantaneous (ac) values of electrode currents and voltages; for example: e_g , e_p , i_g , i_p .

8. The total instantaneous values of electrode currents and voltages (dc plus ac components) are indicated by the lower case symbol and the subscripts "b" for plate and "c" for grid; for example: i_b , e_c , i_c , e_b .

9. No-signal or static currents and voltages are indicated by upper case symbol and lower case subscripts "b" for plate and "c" for grid; for example: E_c , I_b , E_b , I_c .

10. RMS and maximum values of a varying component are indicated by the upper case letter and the subscripts "g" and "p"; for example: E_g , I_p , E_p , I_g .

11. Average values of current and voltage for the with-signal condition are indicated by adding the subscript "s" to the proper symbol and subscript; for example: I_{bs} , E_{bs} .

12. Supply voltages are indicated by the upper case symbol and double subscript "bb" for plate, "cc" for grid, "ff" for filament; for example: E_{ff} , E_{cc} , E_{bb} .

b. List of Symbols

Since the rules above are somewhat complex, an alphabetical list of the commonly used symbols is presented below.

Symbols	Definitions
C	Capacitor, capacitance
C_c	Coupling capacitor
C_d	Distributed circuit capacitance
C_g	Grid-leak or grid capacitor
C_{gk}	Grid-cathode capacitance
C_{gp}	Grid-plate capacitance
C_k	Cathode capacitor
C_n	Neutralizing capacitor
C_p	Plate capacitor
C_{pk}	Plate-cathode capacitance
C_{sc}	Screen capacitor
C_{sup}	Suppressor capacitor
E, V	Voltage
E_a	Applied voltage
E_{av}	Average voltage
E_b	Plate voltage, static dc value
E_{bb}	Plate voltage source (supply voltage)
E_C	Capacitor voltage
E_c	Grid voltage, static dc (bias) value
E_{car}	DC voltage applied to produce carrier
E_{cc}	Grid bias supply voltage
E_{cc1}	Control grid supply
E_{cc2}	Screen grid supply
E_{cc3}	Suppressor grid supply
E_{co}	Negative tube cutoff voltage
E_f	Filament voltage
E_{ff}	Filament supply voltage
E_g	Root-mean-square value of grid voltage
E_{gm}	Maximum value of varying grid voltage component
E_{in} , E_i	Input voltage
E_L	Reactive voltage drop
E_m , E_{max}	Maximum voltage
E_{min}	Minimum voltage
E_o , E_{out}	Output voltage, pack
E_p	Plate voltage rms value
E_{peak} , E_{pk}	Peak voltage
E_R	Resistive voltage drop
E_{rms}	rms voltage value
E_{sc}	Screen voltage, dc value

e	Instantaneous voltage	i_p	Instantaneous ac component of plate current
e_b	Instantaneous plate voltage	i_t	Current per instant of time
e_c	Instantaneous grid voltage	i_Z	Instantaneous current through impedance
e_{car}	Instantaneous carrier voltage	L	Inductance, inductor
e_g	Instantaneous ac component of grid voltage	P	Power
E_1	Instantaneous voltage on element 1	P_g	Grid dissipation power
e_m	Maximum instantaneous voltage	P_i	Input power
e_o	AC component of output voltage	P_o	Output power
e_p	Instantaneous ac component of plate voltage	P_p	Plate dissipation power
e_{pri}	Instantaneous ac component of secondary voltage	P_q	Reactive power
e_r	Instantaneous resistive voltage drop	P_s	Apparent power
e_{sc}	Instantaneous screen voltage	Q	Figure of merit
e_{sec}	Instantaneous ac component of primary voltage	R	Resistance, resistor
e_{sig}	Instantaneous signal voltage	R_G	Generator internal resistance
e_{su}	Instantaneous suppressor voltage	R_g	Grid resistance
f	Frequency	R_L	Load resistance
f_o, f_r	Resonant frequency	R_k	Cathode resistance
g_m	Transconductance	R_p	Plate resistance, dc
I	Current	R_S	Series resistance
I_{av}	Average current	R_{sc}	Screen resistance
I_b, I_o	Static dc plate current	r_L	AC load resistance
I_C	Capacitive current	r_p	Plate resistance, ac
I_c	Static dc grid current	SWR	Standing-wave ratio
I_f	Filament current	t	Time
I_g	Grid current, rms value	t_d	Deionization time
I_L	Inductive current	t_f	Pulse fall time
I_m, I_{max}	Maximum current	t_k	Cathode heating time
I_{min}	Minimum current	t_p	Pulse duration time
I_p	D-C plate current, rms value	t_r	Pulse rise time
I_R	Current in resistor	T	Transformer
I_{rk}	Cathode current	TC	Time constant
I_{rms}	rms current value	V, v, E	Voltage, volts
I_T	Total current	W	Watts
I_t	Current for time interval (usually used with subscripts, as t_1, t_2 , etc)	X	Reactance
i_b	Instantaneous plate current	X_C	Capacitive reactance
i_c	Instantaneous grid current	X_L	Inductive reactance
i_g	Instantaneous ac component of grid current	Y	Admittance
i_L	Instantaneous inductive current	Z	Impedance
		Z_{in}	Input impedance
		Z_L	Load impedance
		Z_o	Characteristic impedance, surge impedance
		Z_{out}	Output impedance




SECTION 2 POWER SUPPLIES

PART 2-0. INTRODUCTION


ELECTRON TUBE DIODE PRINCIPLES

General.

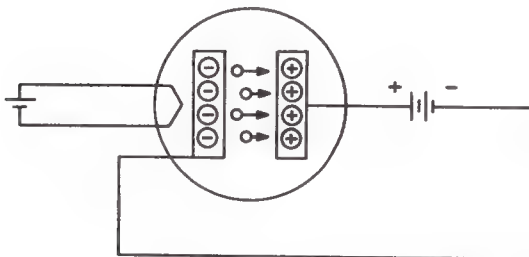A diode electron tube consists basically of only two elements: a cathode (or filament) and a plate. The cathode is responsible for the primary emission of electrons, while the plate collects the electrons emitted by the cathode. The general arrangement of the elements within a diode electron tube is shown in the figure below. This is also the basis of operation for all types of electron tubes.



A. Electron Flow When Plate is Positive

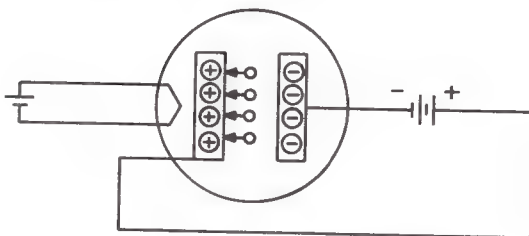

B. Electron Flow When Plate is Negative

When heat is applied to the cathode circuit by the filament, the cathode emits electrons into the space surrounding it (the *Edison Effect*). With no voltages applied to the cathode or plate, this *space charge* will move randomly between the two elements, and no current will flow in the tube circuit.

When the positive side of the battery is connected to the plate of the diode and the negative side of the battery is connected to the cathode (refer to part A

of the figure), the electrons emitted from the cathode will move toward the plate, since unlike charges attract each other, and current flow results in the tube circuit. If the connections are reversed as shown in part B of the figure so that the cathode is positive with respect to the plate, the electrons in the space charge will instead be attracted toward the cathode. Additionally, the negative charge of the plate further repels these electrons toward the cathode, and no current flow results in the tube circuit. Thus, in a diode tube circuit, it can be seen that electron flow can only exist if the plate is positive with respect to the cathode.

ELECTRON TUBE DIODE RATINGS

General.

Three important ratings used in connection with diode electron tubes are discussed in the following paragraphs.

Peak Forward Anode Voltage. This voltage is the maximum instantaneous anode (plate) voltage that can be applied to the tube without damage to the tube structure.

Peak Inverse Anode Voltage. This voltage is the maximum (reverse) instantaneous voltage that can be applied to the anode (plate) during non-conducting periods. When the diode is used in power supply circuits for rectification, the alternating voltage applied to the diode plate will go highly negative with respect to the cathode. If the maximum peak inverse voltage is exceeded, the plate can become so negative with respect to the cathode that the tube can arc from the negative plate to the positive cathode. When this happens, the tube is generally permanently damaged.

Peak Anode Current. This current rating is the maximum instantaneous plate current that can be conducted by the diode without tube damage.

SEMICONDUCTOR DIODE PRINCIPLES

General.

Semiconductor diodes are employed for rectification and detection similarly to electron-tube diodes;


in addition, they have special properties that make them particularly useful for bias and voltage stabilization. Since junction diodes can be made of the same material as the transistor and have the same temperature coefficient and resistance, they will *track* better over the same temperature range, providing nearly ideal thermal compensation. Likewise, application of the avalanche breakdown phenomena provides a special voltage-stabilizing (Zener) diode.

Junction Diode Theory. When P-type and N-type germanium are combined in manufacture, the result is a P-N junction diode, which has characteristics similar to that of the electron-tube diode. If properly biased, the junction diode will conduct heavily in one direction and very lightly or practically not at all in the other direction. The P and N sections of the diode are analogous to the plate and cathode of the electron-tube diode. The direction of heavy current flow is in the forward, or easy current, direction; the flow of light current (back current) is in the reverse direction. To produce a forward current flow, it is necessary to bias the junction diode properly. Proper bias connections for forward and reverse currents are illustrated below. The triangle in the graphical symbol (sometimes called an arrowhead) points against the direction of electron current flow. It is evident that the polarities and electron current flow of the junction diode are identical with those of the vacuum-tube diode and the crystal semiconductor (point-contact) diode. Because of the reverse (back) current flow

(which is not present in any appreciable amount in a vacuum-tube) and the resistivity of the semiconductor, the operation and theory of a junction diode differ somewhat from that of the electron tube diode.


A discussion of the operation of the PN (and the NP) junction and its application to the transistor is included at this point, since an understanding of current flow through the junction and how it varies with external applied bias is essential to circuit operation in later discussions. In semiconductor theory two types of current carriers are encountered, namely, electrons and holes. At room temperature heat energy imparted to a semiconductor causes some electrons to be released from their valence bands with sufficient energy to place them in the conduction band. The resultant vacancy created in the valence band possesses a positive charge and is called a *hole*. When holes are present in the *valence* band, electrons can change their energy state, and conduction is possible by *hole* movement. Likewise, electrons in the *conduction* band can change their state, and conduction is possible by *electron* movement. Thus, conduction within the semiconductor is caused by the movement of positive (hole) and negative (electron) carriers. Although the movement of holes is the result of the movement of electrons, the charge which moves is positive; therefore, it is common to speak of hole movement in the valence band rather than electron movement. In contrast, in a pure conductor such as copper the conduction band and valence bands overlap and are not separated by a forbidden region; thus there is an excess of electrons available, and conduction is spoken of only in terms of electron movement.

An intrinsic semiconductor is one to which no impurities have been added, and in which an equal number of electron and hole carriers exist. An extrinsic semiconductor is one to which an impurity has been added, and in which conduction takes place primarily by one type of carrier. Although the amount of impurity is extremely small (on the order of one part in one million or less), the effect upon the conductivity of the semiconductor is profound. The addition of an impurity which creates a majority of electron carriers is known as a *donor* (because it donates electrons), and the extrinsic semiconductor which results is called N-type. Likewise, the addition of an impurity which creates a majority of hole carriers produces a P-type semiconductor, and is referred to as an *acceptor* impurity (because it will accept electrons).

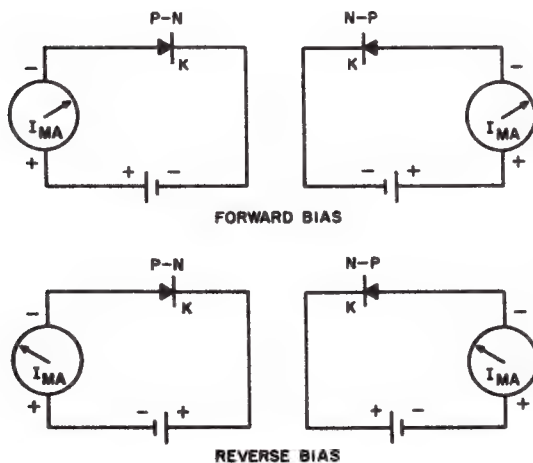

Diode Biasing Circuits

A PN junction is a single crystal consisting of P and N types of semiconductors formed by an alloying or growing process. To facilitate an understanding of its operation, it is assumed that if the P and N materials are brought together externally the junction will function normally, although actually it will not. Each type of material is considered to be electrically neutral. When the P and N materials are brought into contact to form the PN junction, a concentration gradient exists for electrons and holes. Holes diffuse from the P material into the N material, and electrons diffuse from the N material into the P material. This process continues until the donor and acceptor sites near the junction barrier lose their compensating carriers and a potential gradient is built up which opposes the tendency for further diffusion. Eventually a condition of balance is reached where the current across the junction becomes zero. The relationships across the junction and the final charge dipole which results from the diffusion process is graphically illustrated below.


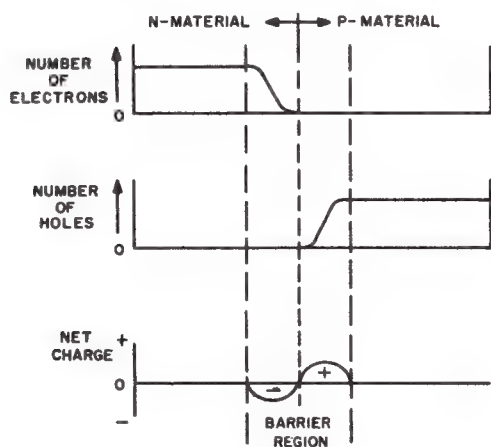


Electric Field Relationships

The region containing the uncompensated donor (negative) and acceptor (positive) ions is commonly referred to as the *depletion region*. (Since the acceptor and donor ions are fixed and are charged electrically, the depletion region is sometime called the *space charge region*.) The electric field between the acceptor (positive) and donor (negative) ions is called a *barrier*, and the effect of the barrier is considered to

be represented by a space-charge equivalent battery (commonly called a *potential hill battery*). In the absence of an external field, the magnitude of the difference in potential across the space-charge *equivalent battery* (this potential is not available for external use as a battery) is on the order of tenths of a volt.

When the negative terminal of an external battery is connected to the P material and the positive terminal is connected to the N material, the junction is said to be reverse-biased. In this condition, the external battery polarity is the same as that of the potential-hill battery as shown below. Therefore, the bias battery aids the potential-hill battery, and very little or no forward current passes across the junction. This action occurs because the holes are attracted to the negative terminal of the external battery and away from the junction. Similarly, the electrons are attracted to the positive terminal of the battery and away from the junction. Thus, the depletion area is effectively widened, and the potential across the junction is effectively increased, making it more difficult

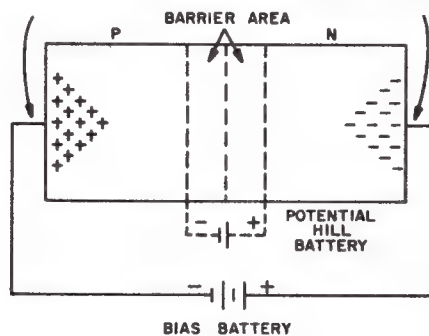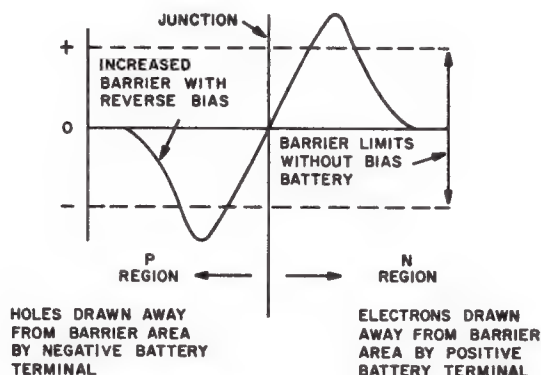



Reverse Bias Conditions

for normal current to flow. With the majority carriers effectively blocked, the only current that can flow is that caused by the minority carriers, and it is in the opposite (or reverse current) direction. This reverse current is called *back current*, and is substantially independent of reverse-bias values until a certain voltage level is reached. At this voltage the covalent bond structure begins to break down, and a sharp rise in reverse current occurs because of *avalanche* breakdown. The breakdown voltage is popularly called the *Zener voltage*, although there is some doubt as to the manner in which it occurs. Once the crystal breaks down, there is a heavy reverse (back) current flow, which, if not controlled, can overheat the crystal and cause permanent damage. If the current is kept at a safe value, the crystal will return to normal operation when the reverse bias is again reduced to the proper value. The construction of the junction determines the type of back current flow. A crystal with more N-type material than P-type material will have a back current due to electron flow; conversely, a crystal with predominantly P-type material will have a back current due to hole flow.

Back current exists solely because the depletion area, although depleted of majority carriers, is never entirely free of minority carriers, and, since they are effectively polarized opposite to the majority carriers, the external reverse-bias polarity is actually a forward bias for the minority carriers.

When the external bias battery is connected so that it is oppositely polarized to the potential-hill battery (positive to P region and negative to N region), the barrier voltage is reduced, and a heavy forward current flows; this bias condition is called *forward bias*. Forward current flow is heavy because the electrons of the N region are repelled from the negative battery terminal and driven toward the junction, and the holes in the P region are forced toward the junction by the positive terminal. Depending upon the battery potential, a number of electrons and holes cross the barrier region of the junction and combine. Simultaneously, two other actions take place. Near the positive terminal of the P material the covalent bonds of the atoms are broken, and electrons are freed, to enter the positive terminal. Each free electron which enters the positive terminal produces a new hole, and the new hole is attracted toward the N material (toward the junction). At the same time an electron enters the negative terminal of the N material and moves toward the junction, heading for the

positive terminal of the P material. This action reduces the effective value of the potential hill so that it no longer prohibits the flow of current across the barrier, or junction, as shown by the upper portion of the illustration below. Internal current flow occurs in the P region by holes (the majority carriers) and in the N region by electrons (also majority carriers). Externally, the current consists of electron flow and is dependent upon the bias battery potential.

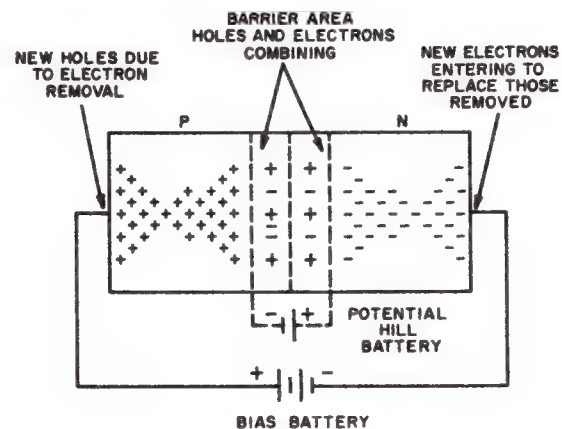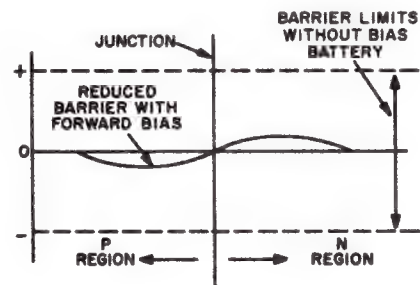


Forward-Bias Conditions

If the forward bias is increased, the current through the junction likewise increases, and causes a reduced barrier potential. If the forward bias were increased sufficiently to reduce the barrier potential to zero, a very heavy forward current would flow and possibly damage the junction because of heating effects. Therefore, the forward bias is usually kept at a low value. Although the initial junction barrier

potential is on the order of tenths of a volt, the material comprising the junction is a semiconductor and has resistance. Thus the applied bias must be sufficient to overcome the resistive drop in the semiconductor; as a rule, one or two volts is usually required to produce a satisfactory current flow.

Even though the depletion region is less depleted with forward bias, the minority carriers still exist. The flow of reverse leakage current is practically negligible, however, because the forward bias is in effect a reverse bias to the minority carriers and reduces the back current practically to zero.

The dynamic transfer characteristic curve of the junction diode, illustrated below, shows how the conduction varies with the applied voltage. Observe that as the reverse bias is increased, a point is reached where the back current suddenly starts to increase. If the reverse bias is increased still further, avalanche breakdown occurs and a heavy reverse current flows as a result of crystal breakdown (sometimes called the *Zener effect*). The minimum breakdown voltage of the junction diode corresponds to the maximum inverse peak voltage of an electron-tube diode.

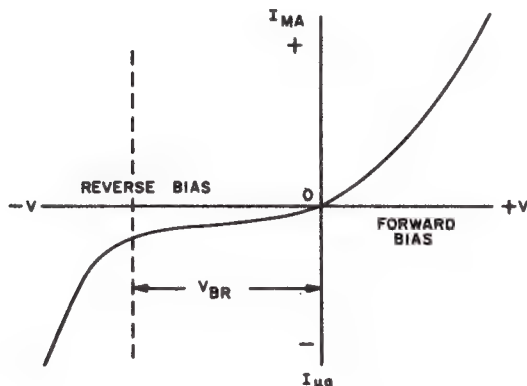

Diode Transfer Characteristic Curve

Application.


The application of semiconductor rectifiers in the design of power supplies for electronic equipment is increasing. The characteristics which have caused this increase are: no requirement for filament (cathode) power, immediate operation without need for warm-up time, low internal voltage drop substantially

independent of load current, low operating temperature, and generally small physical size.

Formerly, metallic or dry-disc rectifiers, such as copper-oxide, copper-sulfide, and selenium rectifiers, were used primarily in low-voltage applications and were limited in use to the lower frequencies (25 to 800 Hz). Additional design improvements have allowed these rectifiers to be used with higher input voltages, and today they are widely used as power rectifiers. The newer silicon-type rectifier is now used in many power-supply circuits where other types were formerly used. The small physical size of semiconductor rectifiers, especially the silicon types, makes it practical to place these units in series to handle the higher input voltages.

The semiconductor rectifier is utilized as a diode in power-supply circuits in much the same manner as the electron-tube diode. A semiconductor rectifier can be substituted for each electron-tube diode in almost every basic power supply circuit given in this handbook; furthermore, many power-supply circuits which were originally designed to use tubes and were formerly considered impracticable can now be used to advantage by incorporating semiconductor rectifiers in lieu of electron-tube diodes. For example, a voltage-multiplier circuit with many stages to obtain an extremely high-voltage output becomes practicable when semiconductor-type rectifiers are used because the need for an independent filament-voltage source for each stage (to operate directly-heated diodes) is eliminated.

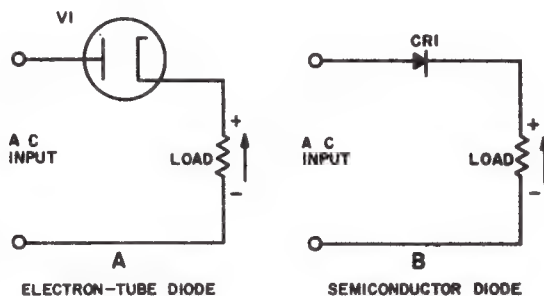Semiconductor rectifiers are particularly well-adapted for use in the power supplies of portable and small electronic equipment where weight and space are important considerations. Many of these smaller



Equivalent Rectifier Circuits

power supplies use very practical bridge and voltage-doubler circuits which require a transformer having only a single high-voltage secondary winding; thus, there is no requirement for a large, expensive transformer which has a center-tapped secondary winding (or an extremely high-voltage secondary winding).

Semiconductor Diode Symbol. The rectifying action of semiconductor diodes is essentially the same as that for electron-tube diodes. The accompanying illustration shows two equivalent rectifier circuits for the purpose of comparison and to establish the correct use of the semiconductor-diode symbol. (The small arrow adjacent to the load resistance indicates the direction of electron flow in the circuit.)

The terminal of the semiconductor diode (CR1), shown in part B, which corresponds to the cathode (or filament) of the electron-tube diode (V1), shown in part A, is usually identified by a colored dot or band, or by a plus (+) sign, the letter "K", the schematic symbol, or other similar means of identification stencilled on the rectifier itself. The power supply circuits described in this section of the handbook and their associated schematics will use the semiconductor-diode symbol in the same manner as shown in the circuit (part B) above.

Rectifier Ratings. The use of one or a combination of several particular type semiconductor rectifiers in any given circuit is based upon the voltage and current requirements of the circuit. All semiconductor rectifiers are subject to certain voltage breakdown and current limitations; for these reasons the rectifier is usually rated in accordance with its ability to withstand a given peak-inverse voltage, its ability to conduct in terms of a maximum dc load current, or its working rms (applied ac input) voltage.

The semiconductor rectifier has an extremely low forward resistance, and precautions are generally taken in the circuit design to ensure that the peak-current rating of the rectifier is not exceeded, especially if the rectifier is used with a capacitance-input filter. For this reason, a small value resistor, called a *surge resistor*, is frequently placed in series with the rectifier to limit the peak current through the rectifier; however, if there is sufficient resistance in the transformer winding (or the ac source), the series resistor is usually omitted. The series resistor, if used, can also be made to act as a fuse in the circuit. Typical values for the series resistor range from approximately 5 ohms for high-current rectifiers (200 milliamperes or greater) to approximately 50 ohms for

low-current rectifiers (50 milliamperes or less). The series resistor is normally not necessary when the rectifier is used with a choke-input filter.

An ideal rectifier would have no (zero) resistance in the forward direction and infinite resistance in the reverse direction. (The electron tube approaches an ideal diode.) In commercially available semiconductor rectifiers, the forward resistance is very small and almost constant, but the reverse resistance is not as great as that of an electron-tube diode; however, the reverse resistance of the semiconductor rectifier can normally be neglected because it is generally so much greater than the associated load resistance. Under normal operating conditions, as long as the rectifier is not subjected to severe overload or otherwise abused, the rectifying action is very stable. The only effect of long use is a gradual increase in the forward resistance with age and, depending upon the rectifier type, a gradual increase in the amount of heat developed. An individual rectifier cell (or element) can withstand only a given peak-inverse voltage without breakdown or rupture of the cell; therefore, if higher peak-inverse voltages are to be sustained, a number of cells must be connected in series. Therefore, it is common practice to place many individual cells in series, or to "stack" several complete rectifier units, to obtain the desired characteristics and ratings necessary to withstand the peak-inverse voltage of the circuit without breakdown.

When rectifiers are placed in series (or stacked) to meet the voltage requirements of the circuit, the total forward resistance is increased accordingly. It is normal for this forward resistance to develop some heat; for this reason, many types of rectifiers are equipped with cooling fins or are mounted on "heat sinks" to dissipate the heat. These rectifiers are cooled by convection air currents or by forced-air. In some special applications, a large number of rectifiers may be incased in an oil-filled container to help dissipate heat. Similarly, just as rectifiers are placed in series to meet certain voltage requirements, they may also be placed in parallel to meet power (current) requirements; however, when rectifiers are operated in parallel to provide for an increased current output, precautions are usually taken to ensure that the parallel rectifiers have reasonably similar electrical characteristics.

Semiconductor Rectifier Circuit Analysis. As mentioned before, the rectifying action of a semiconductor diode is the same as that of an electron-tube

diode; for this reason, the various power-supply circuits in this part of the handbook are described only briefly, especially where the basic circuit is the counterpart of the electron-tube circuit. Since many of the power-supply circuits are similar, much of the detailed theory of circuit operation can be omitted for the semiconductor version, because the rectifier action is identical with that given for the corresponding electron-tube circuit.

Semiconductor Rectifier Failure Analysis. Depending upon the semiconductor type, materials, and construction, a visual check of rectifier appearance may or may not reveal a defective rectifier. Since rectifier failure is not always accompanied by a change in physical appearance, an ohmmeter check or an electrical test may be necessary to determine whether the rectifier is damaged or defective. Improper rectifier operation may result from a change in the rectifier characteristics; that is, the rectifier can be open or shorted, its forward resistance can increase, or its reverse resistance can decrease.

An ohmmeter can be used to make a quick, relative check of rectifier condition. To make this check, disconnect one of the rectifier terminals from the circuit wiring, and make resistance measurements across the terminals of the rectifier. The resistance measurements obtained depend upon the test-lead polarity of the ohmmeter; therefore, two measurements must be made, with the test leads reversed at the rectifier terminals for one of the measurements. The larger resistance value is assumed to be the reverse resistance of the rectifier, and the smaller resistance value is assumed to be the forward resistance. Measurements can be made for comparison purposes using another identical-type rectifier, known to be good, as a standard. Two high-value resistance measurements indicate that the rectifier is open or has a high forward resistance; two low-value resistance measurements indicate that the rectifier is shorted or has a low reverse resistance. An apparently normal set of measurements, with one high value and one low value, does not necessarily indicate satisfactory or efficient rectifier operation, but merely shows that the rectifier is capable of rectification. The rectifier efficiency is determined by how low the forward resistance is as compared with the reverse resistance; that is, it is desirable to have as great a ratio as possible between the reverse and forward resistance measurements. However, the only valid check of rectifier condition is

a dynamic electrical test which determines the rectifier forward current (resistance) and reverse current (resistance) parameters.

SILICON-CONTROLLED RECTIFIERS


General.

The silicon-controlled rectifier is considered to be a PNP device operating as a controlled switch. It has a low resistance in the forward direction when triggered, and a high resistance in the reverse direction. Once triggered, the amount of conduction is limited only by the impedance of the external circuit. In addition, it requires only a small amount of trigger current to initiate conduction. For example, a small current of 50 milliamperes, or less, can control currents from a few milliamperes up to hundreds of amperes. While the silicon-controlled rectifier is normally triggered by a current gate, it may also be turned on by exceeding the forward breakdown voltage. When the forward voltage is increased, the forward leakage current does not increase, or change, until the triggering point is reached. Once triggered, the controlled rectifier continues to conduct until the forward voltage is removed, reversed in polarity, or the holding current is reduced to a value which will no longer sustain conduction. There is also a value of reverse voltage which, when exceeded, will produce avalanche breakdown. Normally, the reverse breakdown voltage is high because of the inherent construction of the device, and is much greater than that of a conventional semiconductor diode.

Generally speaking, the silicon-controlled rectifier is the solid-state counterpart of the electron tube gas-filled thyatron rectifier. In this respect, the forward holding current corresponds to the minimum firing potential of the thyatron. It is important to note, that while the thyatron tube requires a grid firing voltage to cause conduction, the controlled rectifier requires current triggering to initiate conduction. Like most solid-state devices, the controlled rectifier is much smaller in size than a similarly rated thyatron tube.

Controlled Rectifier Symbol. The rectifying action of the controlled rectifier diode, when gated, is essentially the same as that discussed for the semiconductor diode discussed earlier in this section. The two equivalent rectifier circuits are shown in the accompanying illustration for the purpose of comparison, and to establish the correct use of the controlled

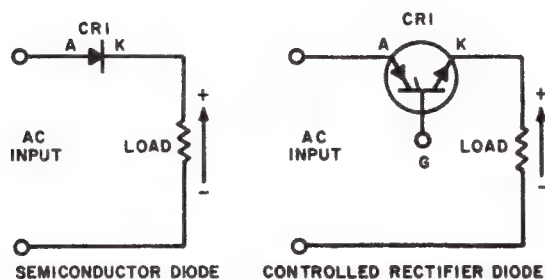rectifier symbol. The small arrow, adjacent to the load resistance, indicates the direction of electron current flow in the circuit.



Equivalent Rectifier Circuits


Silicon-controlled rectifiers are manufactured in many sizes, from small lead-mounted types to large stud-mounted units. They may be obtained in positive or negative polarities (PNPN or NPNP). The positive type usually has the stud connected to the cathode and the braided heavy lead is connected to the anode. The negative type is connected inversely, with the stud connected to the anode, and the heavy braided lead to the cathode. The gate connection is always the smaller and thinner lead which protrudes from the stud. In lead-mounted types the cathode and anode pins are usually diametrically opposite, with the gate lead between them offset to the left. When installing or replacing units, connect them in accordance with the manufacturers' instruction sheets to avoid accidental reversal of connections.

Rectifier Ratings. The use of one, or a combination of several particular types of controlled rectifiers, in any given circuit is based upon the voltage and current requirements of the circuit. All controlled rectifiers are subject to specific voltage breakdown and current limitations. The rectifier is rated in accordance with its ability to withstand a maximum repetitive peak reverse voltage, which corresponds to the peak inverse voltage rating applied to transistors and diodes. It is also rated for maximum permissible dc load current, and for maximum working rms (applied ac input) voltage. In addition, the controlled rectifier is also rated for a maximum value of peak forward blocking voltage, which will prevent the unit from conducting unless gated. The higher the blocking voltage permitted, the higher the permissible con-

trolled voltage. It is also necessary to exceed a certain minimum gate trigger voltage and current to make the rectifier conduct. There is a minimum holding current rating below which forward conduction ceases and blocking again occurs. It is usually necessary to apply the gating current for a short period (from approximately 5 to 15 microseconds) before conduction starts. That is, both the turn-on and turn-off operation are not instantaneous, but take finite intervals, depending upon the size and rating of the rectifier. Maximum turn-off time is approximately 50 microseconds. For example, in some types of rectifiers, without any gate applied, the turn-off current may have ceased for as much as 40 microseconds until the application of forward voltage again causes a flow of forward current. Once the maximum forward turn-off delay time is exceeded, a normal gate or a higher than rated forward blocking voltage is necessary to turn on the controlled rectifier.

When the peak working voltage of the supply is greater than the rectifier rating, it is permissible to connect (stack) a number of controlled rectifiers in series, provided proper equalizing arrangements are made. The simplest arrangements are a series of equalizing resistors placed in shunt with the controlled rectifier. The more elaborate arrangements include series resistor-capacitor combinations, with the resistor shunted by a semiconductor diode. This combination eliminates transients and excessive starting current because of slight differences in ratings between similarly controlled rectifier units. Likewise, when the current-carrying capability of a single control rectifier is insufficient, it is also possible to connect a group of controlled rectifiers in parallel. Compensation must be provided for any differences in forward resistance (or for current ratings and characteristics encountered as a result of production variations). Because of the number of current ratings available, it is seldom that more than two controlled rectifiers are paralleled. Cooling fins or heat sinks are available to ensure that the controlled rectifier is held within temperature ratings by means of convection cooling. Use of the stud-type unit for currents above approximately 5 amperes enables the entire chassis to be used as a permanent low-cost heat sink.

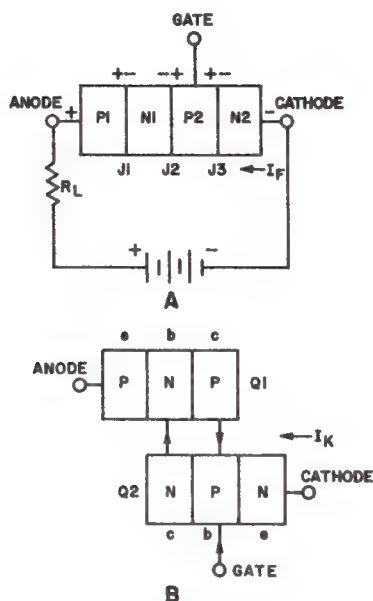Circuit Operation. Operation of a PNPN semiconductor arrangement as used in the controlled rectifier is best visualized by connecting a pair of PNP and NPN transistors to form a regenerative feedback pair as shown in part B of the accompanying illustration.



Transistor Analog of Controlled Rectifier


When a positive voltage is applied to the anode, junctions J1 and J3 (part A of the figure) are forward-biased, but since J2 is reverse-biased, current flow is blocked. Likewise, when a negative voltage is applied to the anode, junctions J1 and J3 are reverse-biased, and although junction J2 is forward biased, current flow is also blocked. The biasing of J2 may be controlled by applying a positive voltage to the gate electrode. Let us assume now that a positive gate current is injected into the P2 layer shown in part A of the figure. In the two-transistor analog shown in part B of the figure, the increase in gate current causes an increase in the base current of transistor Q2. An increase in the base current of Q2 causes the emitter current of Q2 to increase. When the emitter current increases, the collector current of Q2 also increases. Since the collector of Q2 is connected to the base of Q1, an increase of collector current in Q2 causes an increase in the base current of Q1. The increased base current of Q1 now increases the emitter current and also the collector current of Q1. Since the collector of Q1 is shown connected back to the base of Q2, an increase of Q1 collector current feeds back an increased base, or gate current, thus causing the base

current of Q2 to increase further. The feedback around this closed loop rapidly increases and is regenerative, so that even when the external gate is removed, both transistors are still driven rapidly into saturation. Thus, junction J2 is effectively forward-biased by the insertion of the gate current. With all three junctions forward-biased, there is a high electron current flow from cathode to anode of the controlled rectifier and an extremely low forward resistance.

Once triggered, anode current will continue until the current falls below the holding current value. As the current falls below the holding value, the electrons and their positive counterparts called "holes" which were induced as charge carriers during the turn-on process decrease through recombination; the positive feedback ceases and the unit returns to its normally blocked state. At power frequencies, this relatively slow process is no problem. Particularly, since in ac circuits, the turnoff process is further assisted by the reverse half-cycle of voltage which helps sweep out the left-over carriers before blocking the next half-cycle. (When an SCR is used as a switch in dc circuits, for example as an inverter, some means must be provided to turn off the unit.) This is usually accomplished by reversing the voltage and causing the electrons and holes stored in the inner regions to diffuse toward J1 and J3. Thus a reverse current is produced in the external circuit. The voltage across the unit remains at about +0.7 volt until the reverse current ceases and junctions J1 and J3 enter the blocking state. Complete recovery, however, does not occur until the carriers remaining near the center junction, J2, are entirely removed by recombination; this takes a somewhat longer time. If sufficient J2 carriers are not combined, junctions J1 and J3 will conduct when forward-biased by the voltage applied during the forward blocking cycle, and cause false firing.

The accompanying figure shows the voltage and current characteristics of a typical silicon-controlled rectifier.

As shown on the figure, only a small reverse current flows over the reverse blocking region when a negative anode voltage is applied. When the reverse avalanche voltage is exceeded, a heavy reverse current flows. Over the gated region, a heavy forward current flows that is greater than the holding current. Over the forward blocking region, only a small (leakage) current flows; this does not change until the forward

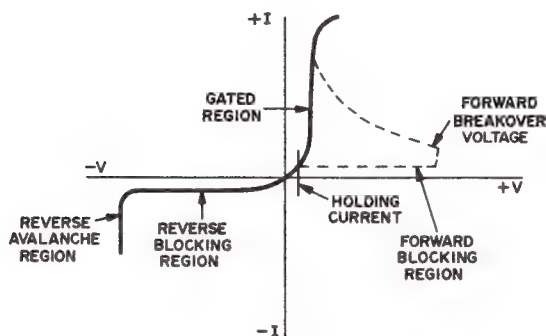

Controlled Rectifier V/I Characteristics

breakover voltage is reached, whereupon the SCR fires and a heavy forward current flows.

Failure Analysis. Since the silicon-controlled rectifier has a high resistance in both the forward and reverse directions until gated, the conventional forward-reverse-resistance diode check, usually made with an ohmmeter, will not give any indication of the condition of the controlled rectifier. Normally, the controlled rectifier will be either open or shorted. If the unit (when not gated) indicates a low forward resistance when checked with an ohmmeter, it definitely is defective. A high resistance reading in the reverse direction, preferably in the megohm region usually indicates low leakage current. However, this is only a relative test, since leakage current varies with different types of controlled rectifiers. The standard tube or diode tester cannot be used to test an SCR. However, there are a number of types of SCR testers available, ranging from precise laboratory types to practical portable types similar in size to a volt-ohmmeter. To determine the condition of an SCR, it is necessary to check the gate firing voltage and gate current, and to determine the anode to cathode leakage. It is also important to know the anode to gate leakage current, since excessive anode-gate leakage can cause self-triggering when the full anode to cathode voltage is applied during operation.

Although most electronic parts exhibit visible evidence of trouble, such as burned or discolored areas, the rugged construction of the silicon-controlled rectifier, to a large extent, makes the possibility of determining failure by visual inspection rather remote. In the absence of a suitable SCR tester, an oscilloscope can be used to determine that the proper firing waveform exists at the gate, and whether or not it is of sufficient amplitude. Usually the SCR will either fire normally, continuously, or erratically, or not at all. Any of these conditions may be caused by a defective SCR, a faulty gate or gate circuit, or poor connections. Isolation of the trouble usually is reduced to making gate voltage and current measurements to determine that proper gating occurs.

RECTIFIERS

General.


Rectifiers are used to convert an alternating current to a direct current to provide power required for operation of electrical and electronic equipment. Several types of rectifiers exist, and selection is based upon the requirements of the equipment it will supply; whether the equipment requires low or high voltage, low or high current, etc.

The dc output of a power supply can be either positive or negative, depending upon the circuit design, but it will always be a pulsating dc voltage (commonly referred to as *ripple voltage*). Filtering circuits are generally required at the rectifier output to reduce these pulsations to a pure or near-pure dc. These filter circuits are described in detail in the Filter section of this handbook. The different types of power supplies in use today are described briefly below.

BASIC POWER SUPPLIES

Half-Wave Rectifiers.

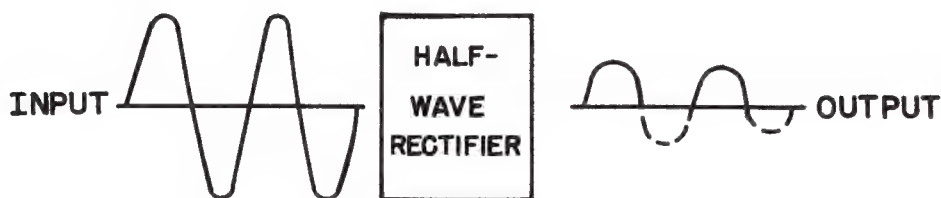A half-wave rectifier power supply allows current to flow in the output only during the positive or negative half cycle of the input, as shown below:




In this example, the half-wave rectifier limits the negative half cycle of the input, as represented by the dashed lines in the output waveform.

The half-wave rectifier is the simplest in design and lowest in cost of all rectifiers. However, because of the low ripple frequency (same frequency as the input), the filtering required at the output must be of high quality. Additionally, the average output voltage is relatively low when compared to the input voltage;

only half the applied power is passed to the load. This factor limits the half-wave rectifier to applications where the power required by the load is very low.

Full-Wave Rectifiers.

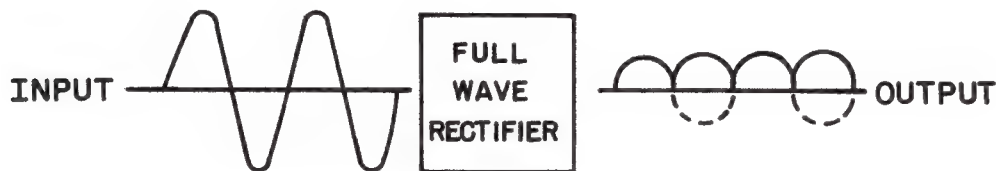The full-wave rectifier power supply allows current to flow in the output during both the positive and negative half cycles of the input, as shown in the illustration below:



In this case, the output ripple voltage is positive; the negative half cycles of the input appear in the output as positive pulses. The output polarity can be reversed to produce negative pulsations by variations in circuit design.

Since the ripple frequency is twice the frequency of the input voltage, it is much easier to filter than the output of a half-wave rectifier. Also, since the frequency of the applied voltage is doubled, the average output voltage is much higher than the half-wave rectifier (given the same input signal) because much more of the applied power is passed to the load.

Full-Wave Bridge Rectifier.


The full-wave bridge rectifier passes the positive and negative halves of the applied voltage, just as the previously described full-wave rectifier. By utilizing

the full secondary voltage of the input transformer instead of using a center tap, a full-wave bridge rectifier acquires the advantage of being able to deliver about twice the voltage of the full-wave rectifier.

MULTIPHASE POWER SUPPLIES

Multiphase Rectifiers.

Multiphase rectifiers are used in most applications where a power requirement of greater than 1 kilowatt exists. The multiphase rectifier (sometimes called *polyphase*) uses a multiphase input, and rectifies each phase independently. The result is a single output voltage with a much smoother ripple (a higher ripple frequency) than the previously described rectifier circuits. The illustration below shows the input and output waveforms of a multiphase rectifier circuit.

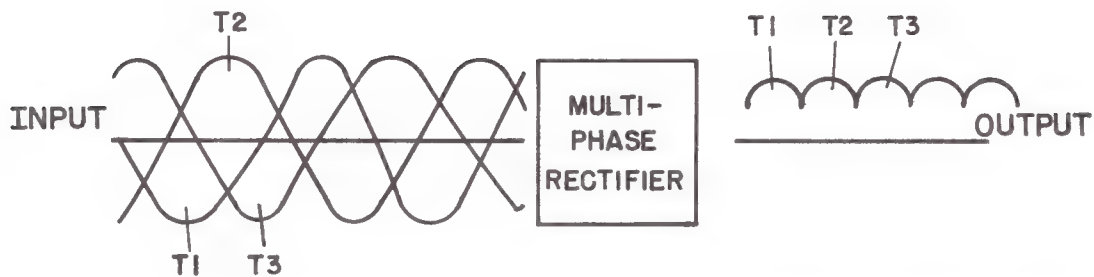

VOLTAGE MULTIPLIER POWER SUPPLIES

Voltage Multipliers.

Voltage multipliers are used to produce an output that is some multiple of the peak input line voltage. Voltage multipliers can be used for high voltage applications but the current delivering capability is very low. The voltage multiplier can produce any of a number of multiples of the input voltage; however, voltage regulation is generally poor. The greater is the multiplying factor, the poorer is the regulation, and the lower the proportion of current available to the load. The output voltage, as the previously discussed rectifier circuits requires filter circuits to smooth the pulsating dc output. These filter circuits are discussed in detail in the Filter section of this handbook.

DC-TO-DC CONVERTERS

General.

The dc-to-dc converter is used to convert a low-level dc voltage to a higher level dc voltage. They are especially useful in applications where the equipment, operates from a dc supply or a battery, or where extremely high dc voltage with low current is required. Basically, the low-level dc voltage is applied to an oscillator circuit which converts it to an ac voltage. This ac voltage is then stepped up through transformer action and applied to a rectifier or voltage multiplier circuit where it is converted back to a pulsating dc voltage that is a higher level than the input. The pulsating dc is then applied to a filtering circuit to smooth the dc pulsations to a constant dc voltage. These filter circuits are discussed in the Filter Section of this handbook.

ROTATING ELECTROMECHANICAL SYSTEMS

General.

The primary electrical power source in many small boats and aircraft is a 12- or 24-volt storage battery; the battery is kept in a charged condition by means of an engine-driven generator. The battery supplies the voltage for the engine ignition system, navigation lights, and other electrical loads. When communications or similar electronic equipment is a part of the electrical load, an electromechanical-type power supply is frequently employed to supply high voltage for operation of the electronic equipment. In such cases, a rotating electromechanical device called a *dynamo* is used to obtain high-voltage dc for operation of the electronic equipment, although a transistorized dc-to-dc converter or a vibrator-type power supply could also be used for the same purpose.

In some instances where the primary electrical power source is ac, an electromechanical device called a *rotary converter* is used to convert ac to dc. By definition, a rotary converter is a machine that changes electrical energy of one form to electrical energy of another form. A rotary converter can convert alternating current to direct current, or it can convert direct current to alternating current. It can also be used to change frequency and phase. In the normal sense, the rotary converter is a machine used to convert ac to dc; when it is used to convert dc to ac it is called an *inverter*, and is occasionally referred to as an *inverted converter*. When ac is available as the primary electrical power source, it is usually more efficient to use a power transformer and rectifier combination to obtain high-voltage dc than to use a rotary converter; for this reason, the application of

rotary converters is limited. However, the rotary converter in another more common form, that of an inverter, is frequently used to convert dc to ac.

In naval aircraft, a source of alternating current is frequently required to power some of the instruments, electronic equipment, fluorescent lighting, etc. If the aircraft does not have an engine-driven ac primary power source (single-phase or polyphase), it is necessary to provide a means of changing the primary dc source to ac for use by the electrical load. In this application an inverter (one form of rotary converter) is used to change the dc to ac; the output of the inverter may be either single- or three-phase dc at a frequency which is normally 400 or 800 hertz.

From the brief discussion above, it can be seen that the dynamotor, rotary converter, and inverter are merely specialized combinations of motors and generators (or alternators). The detailed theory of operation and the construction of ac and dc motors, generators, and alternators are covered in Navy publications on basic electricity, and, therefore, will not be treated in this handbook. Only the basic principles will be discussed in this section of the handbook, as required, to provide a better understanding of the application and the failure analysis of the electro-mechanical devices discussed.

VIBRATOR-TYPE POWER SUPPLIES

General.

The primary electrical power source in many portable and mobile (small boats, light aircraft, and ground vehicles) electronic equipments is a storage battery. Vibrator-type power supplies are used to convert direct current from the storage battery to alternating current which can be rectified to furnish high-voltage for the operation of the equipment. Vibrator-type power supplies are designed for operation with specific input voltages; storage batteries having voltage values of 6, 12, or 24 volts are commonly used to operate this type of supply.

The main differences between a conventional power supply operating from an ac source and a vibrator power supply are the vibrating device used to convert the low dc voltage to high ac voltage and the special step-up power transformer used in conjunction with the vibrator. The vibrator itself is essentially a high-speed reversing switch that alternately opens and closes sets of contacts in the primary circuit of

the power transformer. The rising and falling magnetic field caused by the current pulses in the transformer primary induces an alternating square wave in the secondary circuit. The vibrator is designed to operate at a given frequency, usually between 60 and 250 hertz, although in some applications higher frequencies are employed.

Two basic vibrators are widely used in power supplies of this type; one is called the *nonsynchronous* (or *interrupter*) vibrator, and the other is called the *synchronous* (or *self-rectifying*) vibrator. The primary function of either type of vibrator is to cause the dc input current to flow in pulses through alternate halves of the transformer primary. The nonsynchronous vibrator requires the use of some form of high-voltage rectifier circuit to produce dc output from the supply. The synchronous vibrator does not require a separate rectifier circuit since, as the name *synchronous* (or *self-rectifying*) implies, the vibrator itself performs the additional function of rectifying the high-voltage ac it produces by synchronous switching of the transformer secondary winding; the resultant output voltage is essentially dc.

Occasionally, vibrator power supplies are designed to operate on more than one value of input voltage; this is accomplished by providing a number of taps on the transformer primary, and appropriate switching or terminal points to accommodate the different battery voltages.

Several types of vibrator power supplies are capable of operation from both a low-voltage dc source and a conventional 60-hertz ac source. A combination power supply of this type is usually equipped with a transformer having an additional primary winding for ac operation; the primary winding used for vibrator operation is tapped, and is used as the filament winding for the electron tubes when operating on ac. This type of power supply uses a non-synchronous vibrator and a separate rectifier circuit, since the same high-voltage secondary is used for both ac and dc operation.

Another combination ac and vibrator power-supply design uses two separate power transformers, with independent rectifiers in the vibrator circuit and in the ac input circuit. These two independent power-supply circuits share a common filter circuit to filter their respective dc outputs; either of the two input circuits is selected by a switching arrangement, depending upon whether dc input or ac input operation is desired.

Although there are other circuit arrangements for providing operation from both ac and dc input sources, the examples given above are typical. One other combination vibrator supply which is occasionally employed makes use of two vibrator supplies operating from a common dc input but with two or more output voltages. The outputs of the combined supplies can be either positive or negative, or both, and of different voltage values.

Any of the conventional electron-tube or semiconductor rectifier circuits, such as the half-wave, full-wave, bridge, and voltage doubler, can be used in nonsynchronous vibrator power supplies. The use of semiconductor rectifiers simplifies the design of nonsynchronous vibrator-type power supplies, since no filament voltage is required for the rectifier(s).

PART 2-1. BASIC POWER SUPPLY CIRCUITS

SINGLE-PHASE, HALF-WAVE RECTIFIER (ELECTRON TUBE)

Application.

The single-phase, half-wave rectifier is used in all types of electronic equipment for applications requiring high-voltage dc at a low load current. The rectifier circuit can be arranged to furnish negative or positive high-voltage output to the load.

Characteristics.

Input to circuit is ac; output is pulsating dc.

Uses high-vacuum or gas-filled electron-tube diode as rectifier.

Output requires filtering; dc output ripple frequency is equal to primary line-voltage frequency.

Has poor regulation characteristics.

Circuit provides either positive- or negative-polarity output voltage.


Circuit Analysis.

General. The single-phase, half-wave rectifier is one of the simplest types of rectifier circuits. The circuit consists of a rectifier (diode) in series with the alternating source and the load. Since the rectifier conducts in only one direction, electrons flow through the load and through the rectifier once during each complete cycle of the impressed voltage. Rectifier conduction occurs only during the interval of time the plate is positive with respect to the filament (cathode). Thus, the electrons flow through the load in pulses, one pulse for each positive half cycle of the impressed voltage.

Circuit Operation. In the accompanying circuit schematic, parts A and B illustrate an electron-tube diode, V1, used in a basic single-phase, half-wave rectifier circuit. The circuit given in part A uses a single transformer, T1, to step up the alternating-source voltage to a high value in the secondary. The filament of the tube, V1, is operated from a low-voltage secondary winding located on the same core and connected to the high-voltage winding. The circuit given in part B is shown with two separate transformers; T1 is a step-up transformer to obtain high voltage, and T2 is a step-down transformer to obtain the correct filament voltage for the operation of V1. Although separate transformers are shown in part B, the low-

voltage secondary of T2 could just as well be wound on the core of transformer T1. However, the high- and low-voltage secondary windings must be adequately insulated from one another to allow the simultaneous application of plate and filament voltages to the tube.

In the two circuits illustrated, either terminal of the load may be placed at ground potential, depending upon whether a positive or negative dc output is desired. The circuit illustrated in part A is commonly used as a negative high-voltage supply with the positive terminal of the load connected to ground (chassis); the circuit illustrated in part B is commonly used as a positive high-voltage supply with the negative terminal of the load connected to ground.

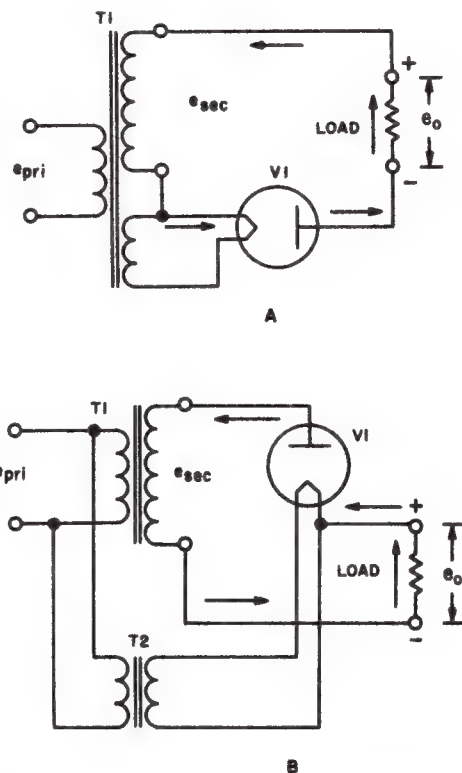

Basic Single-Phase, Half-Wave Rectifier Circuits


The operation of a half-wave rectifier circuit can be understood from the waveforms given in the accompanying illustration.

In part A, the E_p/I_p characteristic curve for the rectifier is given. When high-voltage ac is applied to the rectifier circuit, electrons flow through the tube and the load whenever the plate is positive with respect to the filament or cathode; the amount of current is determined by the characteristic curve of the tube. Part A of the illustration shows that for each positive half cycle of the applied voltage, a current pulse passes through the rectifier, the load, and the secondary winding of the transformer, T1. For each negative half cycle of the applied voltage, the plate is negative with respect to the filament or cathode and no current pulse is obtained. Thus, the electrons flow through the load circuit in pulses, to

produce a pulsating current waveform as shown in part A of the illustration.

In part B of the illustration, voltage waveforms for the half-wave rectifier circuit are given. The primary winding of transformer T1 is connected to an ac source, represented as waveform e_{pri} . The transformer, T1, increases the primary voltage to a higher value in the secondary winding by step-up transformer action. The purpose of the small secondary winding of T1 (or T2) is to supply voltage to the filament of rectifier tube V1. The alternations of the ac source, e_{pri} , are applied to the primary of the transformer and induce a voltage, e_{sec} , in the secondary winding of the transformer. The waveform illustration shows a 180-degree change in phase between the primary (e_{pri}) and secondary (e_{sec}) voltages because of transformer action and the fact that the secondary-output voltage is an induced voltage. Since the transformer is a step-up transformer, the amplitude of the secondary voltage, e_{sec} , is greater than the applied primary voltage, e_{pri} . The induced secondary voltage, e_{sec} , is applied across the rectifier and the load. On positive half cycles of e_{sec} , current passes through the rectifier and the load resistance, producing an output voltage, e_o , across the load resistance. The output voltage e_o , has a pulsating waveform which results in an irregularly shaped ripple voltage; the frequency of the ripple voltage is the same as the frequency of the ac source. Because the output voltage and current are not continuous, the half-wave rectifier circuit requires considerable filtering to smooth out the ripple and produce a steady dc voltage.

The half-wave rectifier utilizes transformer T1 during only one half of the cycle; therefore, for a given transformer less power can be developed in the load than could be developed if the transformer were utilized for both halves of the cycle. Thus, if a considerable amount of power is to be developed in the load, the half-wave transformer must be relatively large compared with a transformer in which both halves of the cycle are utilized. This disadvantage limits the use of the transformer-type half-wave rectifier circuit to applications which require a relatively small load current. Since the dc load current passes through the secondary winding in only one direction, the laminated-iron core of the transformer tends to become magnetized. This effect is called *dc core saturation* and reduces the effective inductance of the transformer. The net effect inductance with the dc

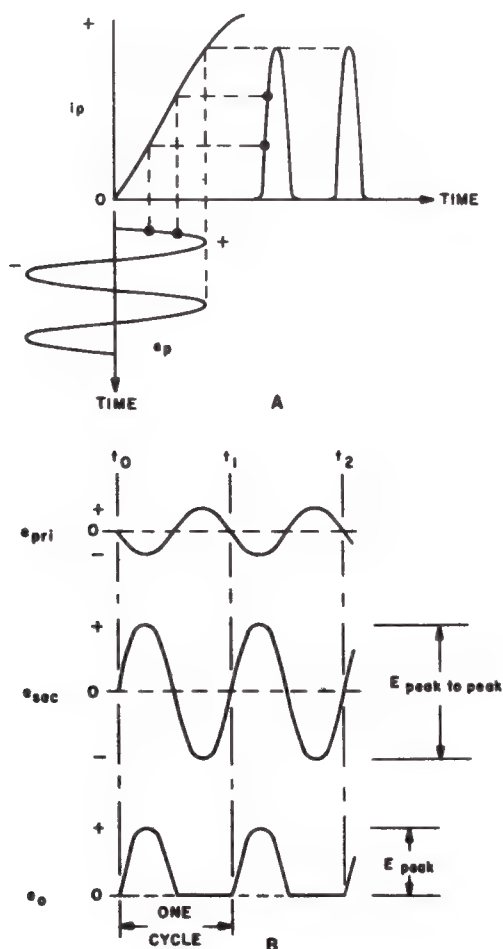

Waveforms for Half-Wave Rectifier Circuit

core saturation effect present is known as *transformer incremental inductance*. Thus, transformer incremental inductance is reduced as the dc load current is increased. The resultant effect is to decrease the primary counter emf to a greater degree and thereby increase the load component of primary current. Therefore, the efficiency of the transformer is reduced, and the regulation of the circuit is impaired.

The half-wave rectifier, assuming half sine waves as the waveform for the output voltage, e_o (unfiltered), produces the following root-mean-square voltage:

$$E_{rms} = \frac{E_{max} \times 0.707}{2}$$

where: E_{max} = maximum instantaneous voltage.
The corresponding average output voltage is:

$$E_{av} = 0.45 E_{rms}$$

Similarly, the root-mean-square and average output currents can be expressed as:

$$I_{rms} = \frac{I_{max} \times 0.707}{2}$$

and: $I_{av} = 0.45 I_{rms}$

The *peak inverse voltage* of a rectifier tube is defined as the maximum instantaneous voltage in the direction opposite to that in which the rectifier is designed to pass current. The peak inverse voltage across the rectifier in a half-wave rectifier circuit during the period of time that the tube is nonconducting is approximately 2.83 times the rms value of the transformer secondary voltage. The peak inverse voltage can be expressed as:

$$E_{inv} = 2.83 E_{rms}$$

where: E_{rms} = transformer secondary
(or applied) voltage

The output of the rectifier circuit is connected to a suitable filter circuit, to smooth the pulsating direct current for use in the load circuit. (Filter circuits are discussed in the Filter Section of this handbook.)

Failure Analysis.

No Output. In the half-wave rectifier circuit, the no-output condition is likely to be limited to one of three possible causes: a defective rectifier tube (open filament), the lack of applied ac voltage, or a shorted load circuit (including shorted filter-circuit components).

A visual check of a glass envelope rectifier tube can be made to determine whether the filament is lit; if the filament is not lit, it may be open or the filament voltage may not be applied. The tube filament should be checked for continuity; also, the presence of correct filament voltage at the tube socket should be determined by measurement.

The ac secondary voltage, e_{sec} , should be measured at the terminals of transformer T1 to determine whether the voltage is present and of correct value. If necessary, measure the applied primary voltage, e_{pri} , to determine whether it is present and of the correct value. With the primary voltage removed from the circuit, continuity (resistance) measurements of the primary and secondary windings should be made to determine whether one of the windings is open, since an open (discontinuity) in either winding will cause a lack of secondary voltage. Also, continuity measurements should be made between each transformer secondary terminal and the corresponding tube socket or load terminal to determine whether either one of these two leads is open.

With the primary voltage removed from the circuit, resistance measurements can be made at the output terminals of the rectifier circuit (across load) to determine whether the load circuit, including the filter, is shorted. If the filter circuit incorporates an electrolytic capacitor, the resistance measurements made across the output of the rectifier circuit may vary depending upon the test-lead polarity of the ohmmeter. Therefore, two measurements must be made, with the test leads reversed at the circuit test points for one of the measurements, to determine the larger of the two resistance measurements. The larger resistance value is then accepted as the measured value. A short in the components of the filter circuit or in the load will cause an excessive load current to flow. If the rectifier tube is a high-vacuum type, the heavy load current will cause the plate to become heated and emit a reddish glow when the plate dissipation is exceeded and, if allowed to continue, may

result in permanent damage to the tube. If a gas-filled rectifier is used in the circuit, a heavy current overload will likely result in damage to the tube, because gas-filled rectifiers are more susceptible to damage from current overload than are high-vacuum rectifiers.

Low Output. The rectifier tube should be checked to determine whether the cause of low output is low filament emission. The load current should be checked to make sure that it is not excessive, because the half-wave rectifier circuit has relatively poor regulation and a decrease in output voltage can be caused by an increase in load current (decrease in load resistance). Also, the ac secondary voltage, e_{sec} , and the primary voltage, e_{pri} , should be measured at terminals of transformer T1 to determine whether these voltages are present and of the correct value. Shorted turns in either the primary or secondary windings will cause the secondary voltage to measure below normal. Shorted turns are not easily detected by resistance measurement; a voltage measurement is a more reliable indication. If the transformer losses (due to shorted turns) are excessive, the transformer may also become overheated. Another check to determine whether the transformer is defective is to disconnect the secondary load(s) and measure the primary current with the transformer unloaded; excessive primary current is an indication of shorted turns. Still another check is to disconnect all primary and secondary leads from the transformer terminals and make measurements between the individual windings and the core, using an ohmmeter or a Megger (insulation tester), to determine whether any of the windings are shorted to the core or to the Faraday shield (noise-reduction shield between primary and secondary).

SINGLE-PHASE, HALF-WAVE RECTIFIER (SEMICONDUCTOR)

Application.

The single-phase, half-wave rectifier is sometimes used in electronic equipment for applications requiring a dc output voltage from an ac source. It is frequently used in "transformerless" circuits where the load current is small and voltage regulation is not critical and also where small space, light weight, high efficiency, ruggedness, and long life are important considerations. The circuit is often employed as the

power supply in small receivers and audio amplifiers. It is also used in low-voltage battery chargers and in some equipment applications, as a bias supply. The rectifier circuit can be arranged to furnish either negative or positive dc output to the load.

Characteristics.

Same characteristics as electron tube version, with following exceptions:

Uses semiconductor diode instead of electron tube.


Depending upon application, it may be used with or without a power or isolation transformer.

Circuit Analysis.

General. The single-phase, half-wave rectifier is the simplest type of rectifier circuit. It consists of a semiconductor rectifier (diode) in series with the alternating source and the load. Since the rectifier conducts in only one direction, electrons flow through the load and through the rectifier once during each complete cycle of the impressed voltage. Thus, the electrons flow through the load in pulses, one pulse for every other half cycle of the impressed voltage.

Circuit Operation. In the accompanying circuit schematic, parts A and B illustrate a semiconductor diode, CR1, used in two variations of a basic single-phase, half-wave rectifier circuit. These two circuit variations use a transformer, T1, as an isolation transformer or to step up the alternating-source voltage to a higher value in the secondary. The use of a transformer in this circuit permits either dc output terminal to be placed at ground (chassis) potential. The two circuit variations shown in parts C and D do not use a transformer, but operate directly from the ac source. Both circuits shown in parts C and D place one side of the ac source at a dc potential, and thus restricts the output of the supply to either a positive dc potential (part C) or a negative dc potential (part D).

In the four circuits illustrated, the function of semiconductor diode CR1 is the same for each circuit. However, because of the manner in which the diode is placed in the circuit, electrons flow through the load in the direction indicated by the arrow adjacent to the load resistance. The dc output polarity for each circuit is indicated by the signs associated with the load resistance. The triangle in the graphic symbol for diode CR1 points in the direction of current flow

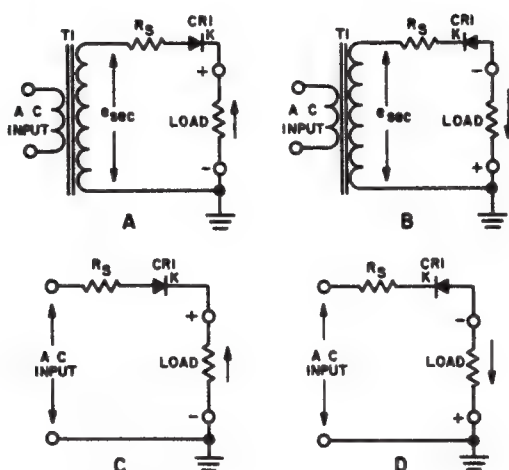


Basic Half-Wave Rectifier Circuits

according to conventional (positive-to-negative) current theory; electron flow is in the opposite direction. The letter "K" assigned to one terminal of the graphic symbol for CR1 indicates that this terminal corresponds to the cathode (filament) of an electron-tube diode. Therefore, the terminal represented by the solid-arrow portion of the graphic symbol corresponds to the plate of an electron-tube diode.

Each of the four circuits shows a resistor, R_S , in series with the semiconductor diode. This resistor, called the *surge resistor*, limits the peak current through the rectifier to a safe value. The value of resistor R_S is influenced by the circuit design; determination of its value includes the consideration of several other factors, such as the applied ac voltage, the resistance of the load circuit, the filter-circuit input capacitance, and the peak current rating of the semiconductor diode. If there is sufficient resistance in the secondary winding of transformer T1 (shown in parts A and B) or in the ac source (parts C and D), the resistor may be omitted; also, if the load circuit of the supply includes a choke-input filter, the resistor may be omitted.

The operation of the half-wave rectifier circuit can be understood from the simplified circuits, parts A and B, and the waveforms, part C, shown in the accompanying illustration.

Assume that the ac voltage applied to the input terminals of the rectifier circuit during the initial

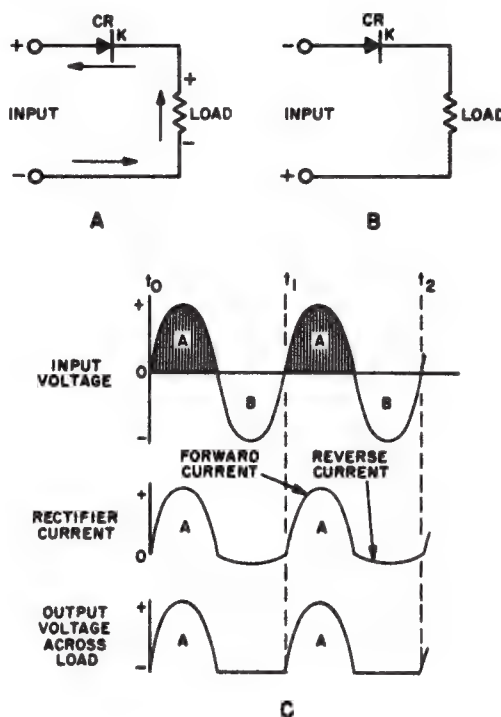Typical Half-Wave Rectifier Circuit
Operation and Waveforms

half-cycle has the polarity indicated in part A of the illustration. Electrons flow in the direction indicated by the small arrows from the lower (negative) input terminal, through the load, through rectifier CR, and to the upper (positive) input terminal. Thus, during the initial half-cycle, rectifier CR passes maximum current in the forward direction, and an output voltage is developed across the load resistance. In other words, when the rectifier conducts, electrons pass through the load to develop a corresponding output-voltage pulse, as shown in part C of the illustration.

During the next half-cycle, the polarity of the applied ac input is as indicated in part B of the illustration. Except for possibly a very small value of reverse current, the rectifier does not conduct, the reverse resistance remains high, and the small current which flows can be neglected. (Normally, the reverse resistance of the rectifier is extremely high as compared with the circuit load resistance.) Thus, during the second half-cycle, no voltage is developed across

the load resistance. In other words, because the rectifier is nonconducting and no electrons pass through the load, there is no output from the circuit.

The waveforms given in part C show that, on positive half cycles of the applied voltage, current passes through the rectifier and the load resistance, producing an output voltage across the load resistance. The output voltage has a pulsating waveform, which results in an irregularly shaped ripple voltage; the frequency of the ripple voltage is the same as the frequency of the ac source. Since the output voltage and current are not continuous, the half-wave rectifier circuit requires considerable filtering to smooth out the ripple and produce a steady dc voltage.

The peak *inverse voltage* of the semiconductor rectifier is defined as the maximum instantaneous voltage in the direction opposite to that in which the rectifier is designed to pass current. Assuming the output of the supply to be filtered, the peak inverse voltage across the rectifier in a half-wave rectifier circuit during the period of time the rectifier is nonconducting is approximately 2.83 times the rms value of the applied (or transformer secondary) voltage.

The output of the half-wave rectifier circuit is connected to a suitable filter circuit, to smooth the pulsating direct current for use in the load circuit. (Filter circuits are discussed in the Filter Section of this handbook.) Because of the very low forward resistance of the semiconductor rectifier and its associated low internal-voltage drop which is practically independent of load current, the half-wave power supply (including filter and load) using a semiconductor diode will have somewhat better regulation characteristics than the equivalent electron-tube circuit; however, the regulation is still considered to be relatively poor.

Failure Analysis.

No Output. In the half-wave rectifier circuit, the no-output condition is likely to be limited to one of several possible causes: the lack of applied ac voltage (including the possibility of an open series resistor R_s or a defective transformer), a defective rectifier, or a shorted load circuit (including shorted filter-circuit components).

The ac supply voltage should be measured at the input of the circuit to determine whether the voltage

is present and is the correct value. If the circuit uses a step-up (or isolation) transformer, measure the voltage at the secondary terminals to determine whether it is present and is the correct value. If necessary, the primary voltage should be removed from the transformer and continuity measurements of the primary and secondary windings made to determine whether one of the windings is open, since an open circuit in either winding will cause a lack of secondary voltage.

If the circuit includes a series resistor (R_s), a resistance measurement can be made to determine whether the resistor is open. However, if the resistor is found to be open, the rectifier and load circuit should be checked further to determine whether excessive load current or a defective rectifier has caused the resistor to act as a fuse and to open.

With the ac supply voltage removed from the input of the circuit and with the load disconnected from the rectifier, resistance measurements can be made across the load to determine whether the load circuit (including filter components) is shorted.

Although physical appearance is not a positive indication of condition, the rectifier may be given a visual check for a change in physical appearance which can indicate rectifier failure. A relative check of the rectifier condition can be made using an ohmmeter, as outlined in a previous paragraph of this section. However, failure of the rectifier may be the result of other causes; therefore, additional tests of the filter and load circuit are necessary.

Low Output. The rectifier should be checked to determine whether the low output is due to normal rectifier aging. A relative check of the rectifier condition can be made using an ohmmeter, as outlined in a previous paragraph of this section. If the forward resistance of the rectifier increases, the output voltage will decrease. Also, if the reverse resistance decreases, the output voltage will decrease, and the amplitude of the ripple voltage will become excessive.

The load current should be checked to make sure that it is not excessive, because the circuit has relatively poor regulation and an appreciable increase in load current (decrease in load resistance) can cause a decrease in output voltage. Also, the filter circuit components should be suspected as a possible cause of low output.

SINGLE-PHASE, FULL-WAVE RECTIFIER (ELECTRON TUBE)

Application.

The single-phase, full-wave rectifier is commonly used in all types of electronic equipment for applications requiring high-voltage dc at a relatively high load current. The rectifier circuit can be arranged to furnish negative or positive high-voltage output to the load.

Characteristics.

Input to circuit is ac; output is pulsating dc.

Uses two high-vacuum or gas-filled electron-tube diodes as rectifiers, or one twin-diode rectifier.

Output requires filtering; dc output ripple frequency is twice the primary line-voltage frequency.

Has good regulation characteristics.

Circuit provides either positive- or negative-polarity output voltage.



Uses power transformer with center-tapped, high-voltage secondary winding.

Circuit Analysis.

General. The single-phase, full-wave rectifier is the most common type of rectifier circuit used in electronic equipment. The circuit consists of a high-voltage transformer with a center-tapped secondary winding. One plate of the rectifier tube (s) is connected to one end of the transformer secondary, and the other plate is connected to the other end. The load is connected between the center-tap of the secondary winding and the filament (cathode) of the rectifiers (s). Since the secondary winding is center-tapped, the voltage developed in each half of the secondary winding is in series with the other half; therefore, only one rectifier plate is positive at any instant. As a result, electrons flow through one half of the secondary winding, the load, and a rectifier diode on each half cycle of the impressed voltage, with first one diode conducting then the other. Thus, the electrons flow through the load in pulses, one pulse for each half cycle of the impressed voltage.

Circuit Operation. In the accompanying circuit schematic, part A illustrates a "full-wave" twin-diode rectifier, V1, used in a basic single-phase, full-wave rectifier circuit. The rectifier circuit uses a single transformer, T1, to step up the alternating-source voltage to a high value in each half of the secondary

winding. The filament of tube V1 is operated from a low-voltage secondary winding located on the same transformer core with the high-voltage secondary. The low-voltage secondary winding is center-tapped and is the mid-point of the filament (cathode) circuit to which the load is connected. The circuit given in part A is typical of plate-voltage and bias supplies designed to meet medium power requirements such as those found in communication receivers and transmitters, audio amplifiers, radar sets, etc.

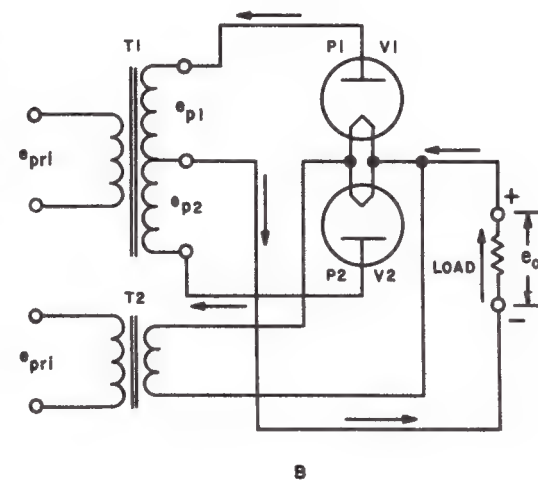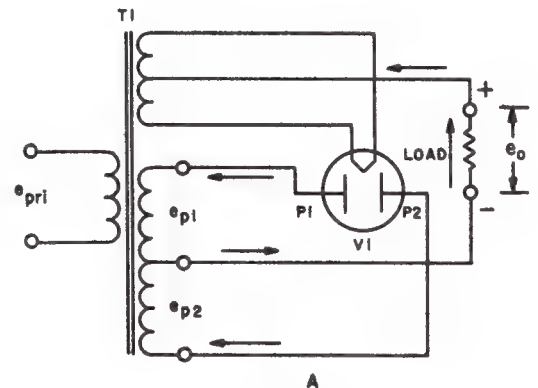

Basic Single-Phase, Full-Wave Rectifier Circuits

The rectifier circuit given in part B is shown with two separate transformers; T1 is a step-up transformer to obtain high voltage in each half of the secondary winding, and T2 is a step-down transformer to


obtain the correct filament voltage for the operation of the two rectifiers, V1 and V2. The circuit is fundamentally the same as that given in part A. The separate transformer arrangement permits the primary voltage to be applied to transformer T2 independent of, the prior to, the application of primary voltage to T1 so that the rectifier filaments may be heated to the normal operating temperature before the plate voltage is applied. Although provision for a time delay in the application of plate voltage is not too important in the case of high-vacuum rectifiers, a time interval to permit preheating of the filament is usually necessary for gas-filled rectifiers. The circuit arrangement given in part B is typical of high-voltage, dc supplies designed for use in radar sets and communication transmitters.

In the two circuits illustrated, either terminal of the load may be placed at ground potential, depending upon whether a positive or negative dc output is desired.

The operation of a full-wave rectifier circuit can be understood from the simplified circuit schematics (parts A and B) and the waveforms (part C) given in the accompanying illustration.

This circuit requires two rectifier diodes and a transformer with a center-tapped secondary winding. Each end terminal of the secondary winding (terminals A and C) is connected to a rectifier plate, as shown in the simplified circuit schematic. Since only one half of the secondary winding is in use at any one time, the total secondary voltage (e_{sec}) must be twice the voltage that would be required for use with a half-wave rectifier circuit (previously described).

The part of the secondary winding between terminals A and B, (e_{p1}) shown in the schematic of part A, may be considered a voltage source that produces a voltage of the polarity given in the illustration. This voltage is applied in series with the load resistance between the plate and cathode of the rectifier, V1. During one half cycle, time interval *a* (part C of the illustration), the plate of V1 is positive with respect to its cathode; therefore, electrons flow in the direction indicated by the arrows on the schematic of part A. Thus, during the time interval *a*, an output voltage is developed across the load resistance. Also during this half cycle, the voltage produced across the part of the secondary winding between terminals B and C (e_{p2}) is negative; therefore, the plate of V2 is negative with respect to its cathode, and V2 is non-conducting.

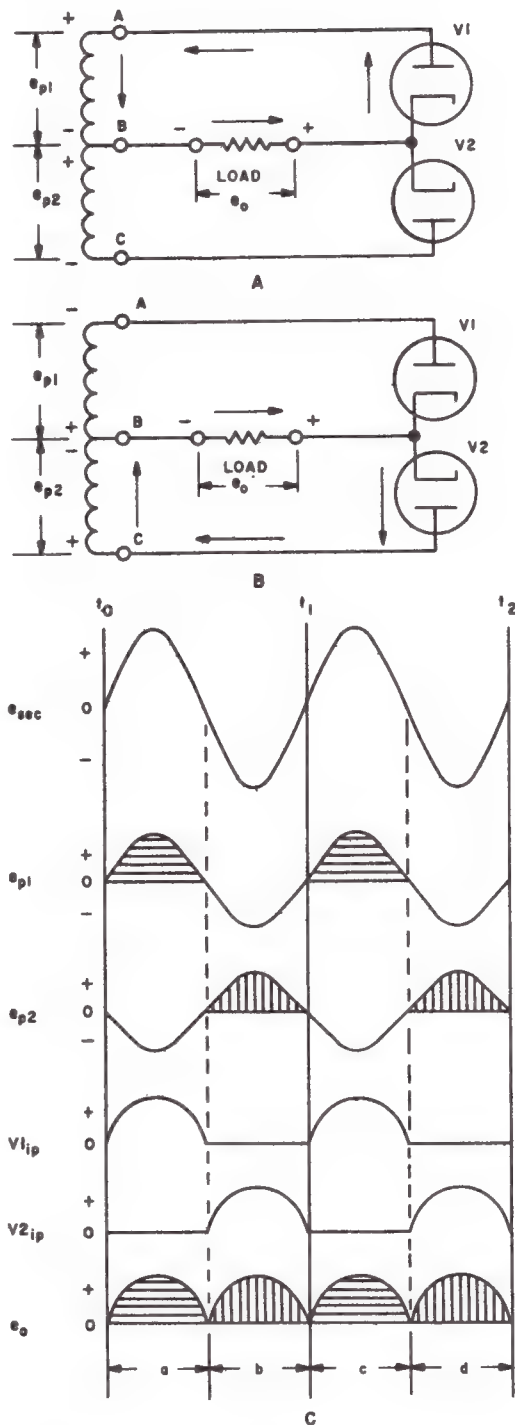

Simplified Full-Wave Rectifier Circuit and Waveforms

During the next half cycle, time interval *b* (part C of the illustration), the polarity of the voltage is reversed. The part of the secondary between terminals B and C (e_{p2}), shown in the schematic of part B, produces a voltage of the polarity given in the illustration. This voltage is applied in series with the load resistance between the plate and cathode of the rectifier, V2. During time interval *b* (part C of the illustration), the plate of V2 is positive with respect to its cathode, and electrons flow in the direction indicated by the arrows on the schematic of part B. Thus, during time interval *b*, an output voltage is developed across the load resistance. Also, during this half cycle, the voltage produced across the part of the secondary winding between terminals A and B (e_{p1}) is negative and, therefore V1 is nonconducting. From the waveforms given in part C, it can be seen that only one rectifier conducts at any instant of time; thus, on alternate half cycles, electrons flow through the load resistance to produce a pulsating output voltage, e_o . This output voltage has a pulsating waveform which results in an irregularly shaped ripple voltage because the output voltage and current are not continuous; the frequency of the ripple voltage is twice the frequency of the ac source. The full-wave rectifier circuit requires filtering to smooth out the ripple and produce a steady dc voltage.

The full-wave rectifier circuit utilizes the transformer (T1) for a greater percentage of the input cycle than the half-wave rectifier, because there are two pulsations of current in the output for each complete cycle of the applied alternating voltage. Therefore, the full-wave rectifier circuit is more efficient, has less output ripple amplitude, and has better voltage regulation than the half-wave rectifier circuit. The dc load current passes through each half of the secondary winding on alternate half cycles, flowing in opposite directions in each half of the winding. Since the windings are electrically equal (ampere turns) to one another, the current passes first in one direction for one half of the secondary winding and then in the other direction for the other half; thus, there is no tendency for the transformer core to become permanently magnetized. Furthermore, since little dc core saturation occurs, the effective inductance of the transformer remains relatively high. As a result, the transformer has much higher efficiency than the transformer used in a half-wave rectifier circuit.

The full-wave rectifier, assuming a series of half sine waves as the waveform for the output voltage e_o

(unfiltered), produces the following root-mean-square voltage:

$$E_{rms} = E_{max} \times 0.707$$

where: E_{max} = maximum instantaneous voltage
The corresponding average output voltage is:

$$E_{av} = 0.9 E_{rms}$$

Similarly, the root-mean-square and average output currents can be expressed as:

$$I_{rms} = I_{max} \times 0.707$$

and:

$$I_{av} = 0.45 I_{rms}$$

The *peak inverse voltage* across a rectifier in a full-wave rectifier circuit during the period of time the tube is nonconducting is approximately 2.83 times the rms voltage across half of the transformer secondary, or 1.41 times the rms voltage across the entire secondary. The peak inverse voltage can be expressed as:

$$E_{inv} = 2.83 E_{rms}$$

where: E_{rms} = rms voltage across half of transformer secondary

or,

$$E_{inv} = 1.41 E_{rms}$$

where: E_{rms} = rms voltage across entire transformer secondary

The output of the full-wave rectifier circuit is connected to a suitable filter circuit to smooth the pulsating direct current for use in the load circuit. (Filter circuits are discussed in part D of this section.)

Failure Analysis.

No Output. In the full-wave rectifier circuit the no-output condition is likely to be limited to one of three possible causes: defective rectifier tube or tubes (open filaments), the lack of applied ac voltage, or a shorted load circuit (including shorted filter-circuit components).

A visual check of glass-envelope rectifier tube (s) can be made to determine whether the filament is lit; if the filament is not lit, the filament of the tube is likely to be open or the filament voltage may not be applied. The tube filament(s) should be checked for continuity; the presence of correct filament voltage at the tube socket should be determined by measurement.

The ac secondary voltage applied to each rectifier plate should be measured between the secondary center-tap and each rectifier plate to determine whether voltage is present and of the correct value. If necessary, measure the applied primary voltage to determine whether it is present and of the correct value. With the primary voltage removed from the circuit, continuity (resistance) measurements of the primary winding should be made to determine whether the winding is open, since an open (discontinuity) in the primary winding will cause a lack of secondary voltage.

With the primary voltage removed from the circuit, resistance measurements can be made at the output terminals of the rectifier circuit (across load) to determine whether the load circuit, including filter, is shorted. If the filter circuit incorporates an electrolytic capacitor, the resistance measurements made across the output of the rectifier circuit may vary depending upon the test-lead polarity of the ohmmeter. Therefore, two measurements must be made, with the test leads reversed at the circuit test points for one of the measurements, to determine the larger of the two resistance measurements. The larger resistance value is then accepted as the measured value. A short in the components of the filter circuit or in the load will cause an excessive load current to flow; if the rectifier-tube type is a high-vacuum type, the heavy load current will cause the plate to become heated and emit a reddish glow when the plate dissipation is exceeded, and, if allowed to continue, may result in permanent damage to the tube. If a gas-filled rectifier is used in the circuit, excessive load current will likely result in damage to the tube because gas-filled rectifiers are more susceptible to damage from current overload than are high-vacuum rectifiers.

Low Output. The rectifier tube(s) should be checked to determine whether the cause of low output is low filament emission. Also, since the full-wave rectifier circuit normally supplies current to the load on each half cycle, failure of either rectifier or an

open in either half of the secondary winding will allow the circuit to act as a half-wave rectifier circuit, and the output voltage will be reduced accordingly. Furthermore, whenever this occurs, the ripple amplitude will also increase, and the ripple frequency will be that of the ac source (instead of twice the source frequency). In the case of two separate rectifier tubes, if one tube is lit and the other is not, the trouble is obviously associated with the tube that is not lit.

With the primary voltage removed from the circuit, resistance measurements can be made to check the continuity between the center-tap and each rectifier plate; this will determine whether one of the windings or plate leads is open. As an alternative, the ac secondary voltage applied to each rectifier plate can be measured between the secondary center-tap and each rectifier plate to determine whether both voltages are present and are of the correct value.

The primary voltage should be measured to determine whether it is of the correct value, since a low applied primary voltage can result in a low secondary voltage. Also, shorted turns in either the primary or secondary windings will cause the secondary voltage to measure below normal. Shorted turns are not easily detected by resistance measurement; a voltage measurement is a more reliable indication. If the transformer losses (due to shorted turns) are excessive, the transformer may also become overheated. Another check to determine whether the transformer is defective is to disconnect the secondary load(s) and measure the primary current with the transformer unloaded; excessive primary current is an indication of shorted turns. Still another check is to disconnect all primary and secondary leads from the transformer and make measurements between the individual windings and the core, using an ohmmeter or a Megger (insulation tester), to determine whether any of the windings are shorted to the core or to the Faraday shield (noise-reduction shield between primary and secondary).

The rectifier-output current (to the filter circuit and to the load) should be checked to make sure that it is within tolerance and is not excessive. A low-output condition due to a decrease in load resistance would cause an increase in load current; for example, excessive leakage in the capacitors of the filter circuit would result in increased load current.

SINGLE-PHASE, FULL-WAVE RECTIFIER (SEMICONDUCTOR)

Application.

The single-phase, full-wave rectifier is commonly used in all types of electronic equipment for applications requiring high- or low-voltage dc at a relatively high load current. The rectifier circuit can be arranged to furnish negative or positive output to the load.



Characteristics.

Same characteristics as electron tube version, except it uses two semiconductor rectifiers instead of electron tubes.

Circuit Analysis.

General. The single-phase, full-wave rectifier is one of the most common types of rectifier circuits used in electronic equipment. It may be used as a low-voltage dc supply for operation of relays, motors, electron-tube filaments, telephone and teletype circuits, and semiconductor circuits, or as a high-voltage dc supply for operation of electron-tube circuits. The full-wave rectifier circuit consists of a transformer with a center-tapped secondary winding. At least two semiconductor diodes are used in the circuit; one diode is connected to one end of the transformer secondary, and the other diode is connected to the other end. The load is connected between the center tap of the secondary winding and the common junction of the two semiconductor diodes. Since the secondary winding is center-tapped, the voltages developed in the two halves of the secondary winding are in series with each other; therefore, only one rectifier is conducting at any instant. As a result, electrons flow through one half of the secondary winding, the load, and a rectifier on each half cycle of the impressed voltage, with first one diode conducting and then the other. Thus, the electrons flow through the load in pulses, one pulse for each half cycle of the impressed voltage.

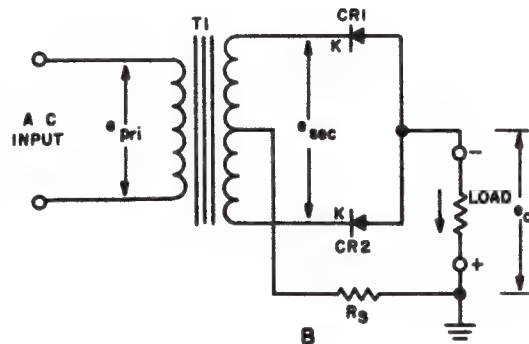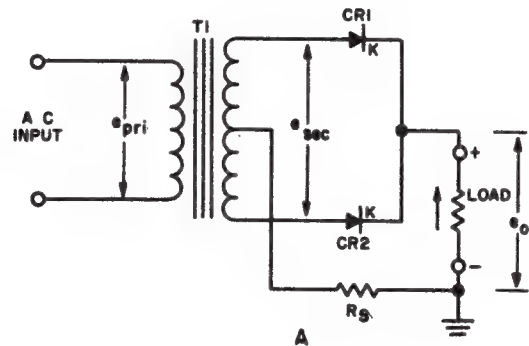Circuit Operation. In parts A and B of the accompanying circuit schematic, two semiconductor diodes, CR1 and CR2, are used in a basic single-phase, full-wave rectifier circuit. Although the schematic shows only two diodes in the circuit, in some instances for high-voltage operation each diode symbol represents two or more diodes in series to obtain the necessary peak-inverse characteristics.



Basic Single-Phase, Full-Wave Rectifier Circuits

The circuit uses a single transformer, T1, either to step up the alternating-source voltage to a higher value in each half of the secondary winding or to step down the voltage to a lower value. The circuit application and the values of the input and output voltages determine whether a step-up or step-down transformer is used.

The series, or surge, resistor (R_s) is generally required only in high-voltage supplies. Its function is to limit the peak current that can flow through the semiconductor rectifiers. When power is applied to the circuit, the input capacitor (in the filter circuit) is in a discharged condition. A very heavy current flows initially to establish the charge on this capacitor. The limiting action of R_s prevents any damage to the rectifiers, which would otherwise occur from the large surge of charging current. For 380-volt (peak inverse) rectifiers, the value of R_s is between 1 and 50 ohms, depending on the peak current rating of the unit. The

resistor is common to both rectifiers since it is placed in the circuit between the transformer center tap and the load. A variation of this design practice uses two resistors, one resistor in series with each rectifier.

The circuit arrangement given in part A is typical of many plate- and low-voltage (positive) supplies. The circuit given in part B is typical for bias supply applications requiring a negative voltage. In the basic circuits illustrated, either terminal of the load may be placed at ground potential, depending upon whether a positive or negative dc output is desired. When the dc output terminal associated with the transformer center tap is grounded, the secondary-to-core insulation need not be as great as it would be if the secondary winding were above ground by the amount of the dc output voltage. For this reason, the two circuits shown in parts A and B are the commonly used circuits, and do not require that special design consideration be given to the secondary-winding insulation.

In parts A and B of the accompanying illustration, the voltage induced in each half of the secondary of transformer T1 causes each diode to conduct on alternate half-cycles of the input voltage. Two dc pulses are thus produced during each complete cycle of ac input voltage. Hence, the output has a frequency which is twice the input frequency. Because of this, the full-wave circuit is more efficient, has better voltage regulation, and has an output which is easier to filter (with a higher average value than that of the half-wave circuit).

As an example of the peak and average voltages obtained from the full-wave rectifier circuit, assume that transformer T1 in part A of the illustration has a step-up ratio of 1 to 6. Then, with an applied input voltage of 115 volts, 690 volts will appear across the secondary winding, and 345 volts will be applied to each diode. Since only one-half of the secondary is used at a time, the peak voltage is found by using half of the voltage across the winding, or 345 volts. From the peak voltage formula:

$$\begin{aligned} E_{\text{peak}} &= 1.414 \times E_{\text{rms}} \\ &= 1.414 \times 345 \\ &= 488 \text{ volts (approx)} \end{aligned}$$

This is the peak value of the output voltage for half-wave (single-phase) rectification. Since two pulses are

produced for every cycle of ac input voltage in full-wave rectification, the average value of the dc output voltage will be greater than that for half-wave rectification; thus:

$$\begin{aligned} E_{\text{av}} &= E_{\text{peak}} \times \frac{2}{\pi} \\ &= 488 \times \frac{2}{3.14} \\ &= 310 \text{ volts (approx)} \end{aligned}$$

In a full-wave rectifier circuit designed to furnish high-voltage dc to the load, the peak-inverse voltage rating of the semiconductor rectifier is an important consideration.

The peak-inverse voltage across a semiconductor rectifier in a full-wave circuit during the period of time it is nonconducting is approximately 2.83 times the rms voltage across half of the transformer secondary ($e_{\text{sec}}/2$), or approximately 1.41 times the rms voltage across the entire secondary (e_{sec}). For high-voltage applications, several identical-type rectifiers may be placed in series or stacked to withstand the peak-inverse voltage and avoid the possibility of rectifier breakdown. Generally, whenever a single rectifier unit is used in the full-wave circuit, it is chosen to have a peak-inverse voltage rating which is conservative and thus provide a safety factor.

Because of the very low forward resistance of the semiconductor rectifier and its low internal-voltage drop which is practically independent of load current, the full-wave power supply using semiconductor diodes has regulation characteristics which approach or equal those of the equivalent electron-tube circuit using mercury-vapor rectifiers. Hence, its regulation characteristics are somewhat better than those of the electron-tube circuit which uses high-vacuum rectifiers.

Failure Analysis.

No Output. In the full-wave rectifier circuit, the no-output condition is likely to be limited to one of several possible causes: the lack of applied ac voltage (including the possibility of a defective transformer), defective rectifiers, or a shorted load circuit (including shorted filter-circuit components).

The ac voltage applied to each rectifier should be measured between the secondary center tap and each rectifier to determine whether voltage is present and of the correct value. If the circuit includes a series resistor (R_s), an additional measurement should be made between the load connection at the resistor and the rectifier to determine whether the resistor is open. (With primary voltage removed from the input, a resistance measurement can be made to determine whether the resistor is open.)

If necessary, measure the applied primary voltage to determine whether it is present and of the correct value. With the primary voltage removed from the circuit, a continuity measurement of the primary winding should be made to determine whether the winding is open, since an open winding will cause lack of secondary voltage.

If the circuit includes a series (surge) resistor common to both rectifiers and the resistor is found to be open, each rectifier and the load circuit should be checked further to determine whether excessive load current or a defective rectifier(s) has caused the resistor to act as a fuse and to open. With the ac supply voltage removed from the input of the circuit and with the load disconnected from the rectifiers, resistance measurements can be made across the load to determine whether the load circuit (including filter components) is shorted.

Although physical appearance is not a positive indication of condition, the rectifier may be given a visual check for a change in physical appearance which can indicate rectifier failure. A relative check of the rectifier condition can be made using an ohmmeter, as outlined in a previous paragraph of this section. However, failure of the rectifier(s) may be the result of other causes; therefore, additional tests of the filter and load circuit are necessary.

Low Output. Each rectifier should be checked to determine whether the low output is due to normal rectifier aging or to one or more defective rectifiers. A relative check of rectifier condition can be made using an ohmmeter, as outlined in a previous paragraph of this section. (A comparison can be made by checking one rectifier against the other to determine whether they have similar characteristics.) If the forward resistance of the rectifier increases, the output voltage will decrease. Also, if the reverse resistance decreases, the output voltage will decrease, and the amplitude of the ripple voltage will become excessive.

Since the full-wave rectifier circuit normally supplies current to the load on each half cycle, failure of either rectifier (or associated series resistor, if used) or an open in either half of the secondary winding will allow the circuit to act as a half-wave rectifier circuit, and the output voltage will be reduced accordingly. Furthermore, whenever this occurs, the ripple amplitude will also increase, and the ripple frequency will be that of the ac source (instead of twice the source frequency). If one rectifier of the full-wave circuit is found to be defective, rather than replace the defective rectifier only, it is good practice to replace both rectifiers at the same time and to make certain that the replacement rectifiers have like, or matched, characteristics.

With the primary voltage removed from the circuit, resistance measurements can be made to check the continuity between the center tap and each rectifier terminal; this will determine whether one of the windings is open. As an alternative, the ac secondary voltage applied to each rectifier can be measured between the center tap and each rectifier to determine whether both voltages are present and are of the correct value.

The primary voltage should be measured to determine whether it is of the correct value, since a low applied primary voltage can result in a low secondary voltage. Also, shorted turns in either the primary or secondary windings will cause the secondary voltage to measure below normal. (A check for shorted turns was outlined in the failure analysis described for the electron-tube full-wave rectifier circuit, given earlier in this section of the handbook).

The load current (to the filter circuit and to the load) should be checked to make sure that it is within tolerance and is not excessive. A low-output condition due to a decrease in load resistance would cause an increase in load current; for example, excessive leakage in the capacitors of the filter circuit would result in increased load current.

SINGLE-PHASE, FULL-WAVE BRIDGE RECTIFIER (ELECTRON TUBE)

Application.

The single-phase, full-wave bridge rectifier is used in electronic equipment for applications requiring high-voltage dc at a high load current. The rectifier

circuit can be arranged to furnish negative or positive high-voltage output to the load, although the circuit is commonly used as a positive high-voltage power supply in most applications.

Characteristics.

Input to circuit is ac; output is pulsating dc.

Uses four high-vacuum or gas-filled electron-tube diodes as rectifiers, or two diodes and one twin-diode as rectifiers.

Output requires filtering; dc output ripple frequency is twice the primary line-voltage frequency.

Has good regulation characteristics.

Circuit provides either positive- or negative-polarity output voltage.

Requires three separate filament transformers or separate filament windings for rectifier tubes.

Uses power transformer with single high-voltage secondary winding; modified circuit to supply two output voltages simultaneously uses transformer with center-tapped, high-voltage secondary winding.

Circuit Analysis.


General. The single-phase, full-wave bridge rectifier circuit uses two half-wave rectifier tubes in series on each side of a single transformer high-voltage secondary winding (the transformer secondary winding does not require a center tap); a total of four rectifiers are used in the bridge circuit. During each half cycle of the impressed ac voltage, two rectifiers, one at each end of the secondary, conduct in series to produce an

electron flow through the load. Thus, electrons flow through the load in pulses, one pulse for each half cycle of the impressed voltage. Since two dc output pulses are therefore produced for each complete input cycle, full-wave rectification is obtained and the output is similar to that of the conventional full-wave rectifier circuit.

One advantage of the bridge rectifier circuit over a conventional full-wave rectifier is that for a given transformer total-secondary voltage the bridge circuit produces an output voltage which is nearly twice that of the full-wave circuit. Another advantage is that the peak inverse voltage across an individual rectifier tube, during the period of time the tube is nonconducting, is approximately half the peak inverse voltage across a tube in a conventional full-wave rectifier circuit designed to produce the same output voltage. One disadvantage of the bridge rectifier circuit, however, is that at least three filament transformers (or three separate windings) are required for the rectifier tubes.

In many power-supply applications, it is desirable to provide two voltages simultaneously—one voltage for high-power stages and the other voltage for low-power stages. For these applications the single-phase, full-wave bridge rectifier circuit can be modified to supply an additional output voltage which is equal to one half of the voltage provided by the full-wave bridge rectifier circuit.

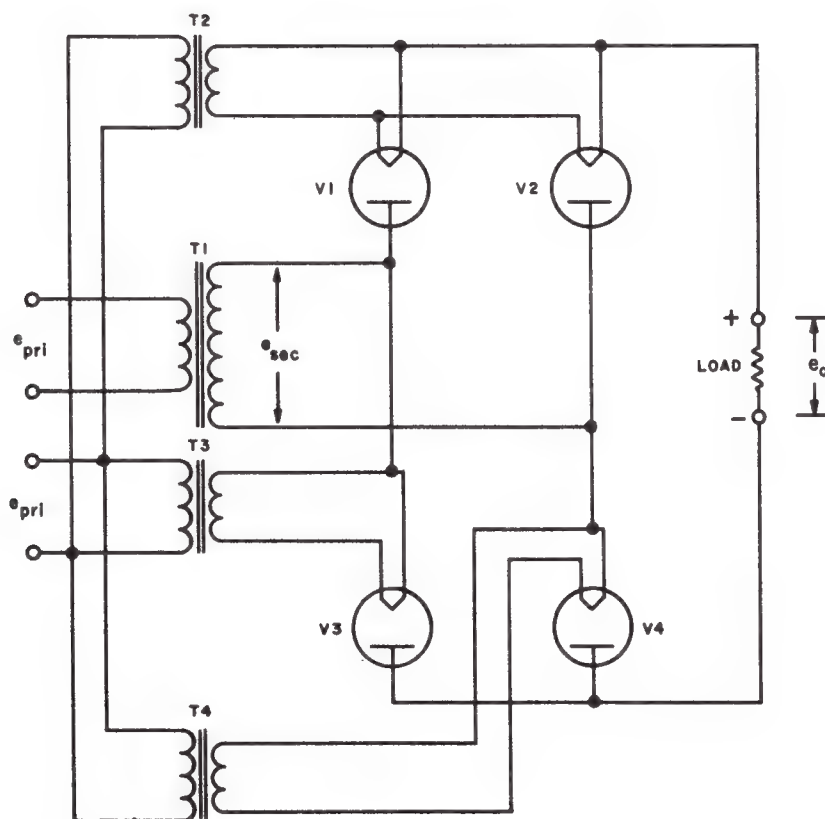Circuit Operation. A single-phase, full-wave bridge rectifier is shown in the accompanying circuit schematic.



**Basic Single-Phase, Full-Wave
Bridge Rectifier Circuit**

Four identical-type electron-tube diodes, V1, V2, V3, and V4, are connected in a bridge circuit across the secondary winding of transformer T1. Each tube forms one arm of the bridge circuit; the load is connected between the junction points of the balanced arms of the bridge. Transformer T1 is a step-up transformer to provide high voltage for the bridge rectifiers. The circuit given shows three separate filament transformers, T2, T3, and T4. A single filament transformer may be used, provided that it incorporates three separate filament secondary windings that are well insulated from each other and from ground (chassis). Note that the filaments of V1 and V2 are at the same potential with respect to each other,

whereas the filaments of V3 and V4 are not. The filaments of V3 and V4 are connected to opposite ends of the high-voltage secondary and therefore operate at the full potential difference that exists across the secondary of T1; thus, if the filaments of V3 and V4 were supplied by a single transformer winding, the common connection would place a short across the high-voltage secondary winding. The filaments of V3 and V4 must, therefore, be insulated from each other and must also be well insulated from ground. In either case, whether three separate filament transformers or a single filament transformer with multiple secondary windings is used, the filament primary voltage is applied independent of, and




prior to, the primary voltage to T1. This arrangement permits the rectifier filaments to be preheated to the normal operating temperature before the high voltage is applied to the bridge-rectifier circuit.

The circuit arrangement given in the illustration permits either terminal of the load to be placed at ground potential, depending upon whether a positive or negative dc output is desired. The circuit is typical of high-voltage, dc supplies designed for use in radar sets and communication transmitters.

The operation of the full-wave bridge rectifier circuit can be understood from the simplified circuit schematic (parts A and B) and the waveforms (part C) shown in the accompanying illustration. The basic bridge rectifier schematic, given earlier in this discussion, has been simplified and redrawn in the form of a simple bridge circuit; the rectifier tube reference designations used correspond to those assigned in the basic bridge rectifier schematic. The bridge circuit uses four identical-type rectifiers. The end terminals of the transformer high-voltage secondary winding are connected to opposite cathode-plate junction points of the rectifiers comprising the arms of the bridge circuit, as shown. The load is connected between the remaining two cathode-plate junction points of the bridge circuit.

During the first half cycle, the transformer secondary winding (terminals A and B), shown in the schematic of part A, may be considered a voltage source that produces a voltage of the polarity given in the illustration. During time interval *a*, terminal A is positive with respect to terminal B; as a result, electrons will flow in the direction indicated by the arrows through the series circuit composed of rectifier V4, the load, and rectifier V1. This electron flow produces an output pulse of the polarity indicated across the load resistance. Also, during this period (time interval *a*), V2 and V3 are nonconducting.

During the next half cycle, time interval *b*, a secondary voltage is produced of the polarity given in part B of the illustration. Terminal B is positive with respect to terminal A; as a result, electrons will flow in the direction indicated by the arrows through the series circuit composed of rectifier V3, the load, and rectifier V2. The electrons flowing in the series circuit once again produce an output pulse of the same polarity as before across the load resistance. During this period (time interval *b*), V1 and V4 are nonconducting.

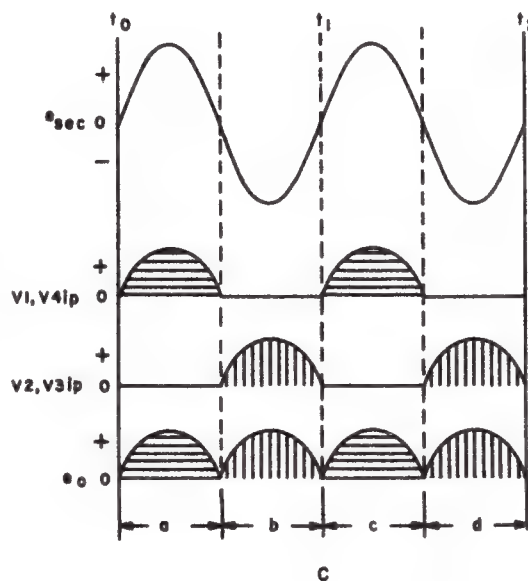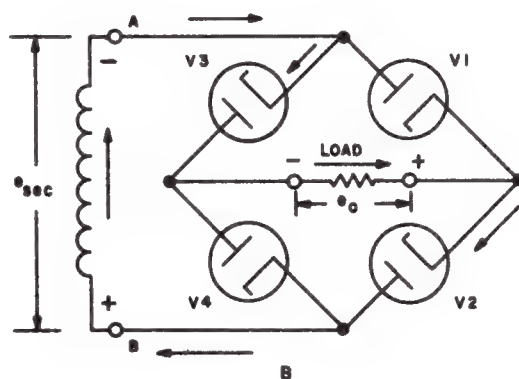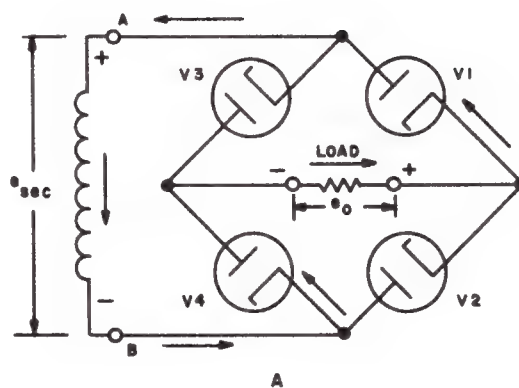

Simplified Full-Wave Bridge Rectifier
Circuit and Waveforms

From the waveforms given in part C, it can be seen that two rectifiers conduct at any instant of time; thus, on alternate half cycles, electrons flow through the load resistance to produce a pulsating output voltage; e_o . This output voltage has a pulsating waveform, which results in an irregularly shaped ripple voltage because the output voltage and current are not continuous; the frequency of the ripple voltage is twice the frequency of the ac source. The full-wave bridge rectifier circuit requires filtering to smooth out the ripple and produce a steady dc voltage.

The full-wave bridge rectifier circuit makes continuous use of the transformer secondary; therefore, there are two pulsations of current in the output for each complete cycle of the applied ac voltage. The dc load current passes through the entire secondary winding, flowing in one direction for one half cycle of the applied voltage, and in the opposite direction for the other half cycle; thus, there is no tendency for the transformer core to become permanently magnetized. Since little dc core saturation occurs, the effective inductance of the transformer, and therefore the efficiency, is relatively high.

The full-wave bridge rectifier, assuming a series of half sine waves as the waveform for the output voltage, e_o (unfiltered), produce the following root-mean-square voltage:

$$E_{rms} = E_{max} \times 0.707$$

where: E_{max} = maximum instantaneous voltage

The corresponding average output voltage is:

$$E_{av} = 0.9 E_{rms}$$

Similarly, the root-mean-square and average output currents can be expressed as:

$$I_{rms} = I_{max} \times 0.707$$

and: $I_{av} = 0.9 I_{rms}$

The peak inverse voltage across an individual rectifier in a full-wave bridge rectifier circuit during the period of time the tube is nonconducting is approximately 1.41 times the ms voltage across the secondary winding. The secondary voltage, e_{sec} , is applied to two rectifier tubes in series; therefore, since less peak inverse voltage (approximately one half) appears across each tube, the bridge circuit can be used to obtain a higher output voltage than can be


obtained from a conventional full-wave rectifier circuit using equivalent rectifier tubes. The peak inverse voltage *per tube* can be expressed as:

$$E_{inv} \text{ (per tube)} = 1.41 E_{rms}$$

where: E_{rms} = ms voltage across entire secondary

The output of the full-wave bridge rectifier is similar to that of the conventional full-wave rectifier circuit. The bridge rectifier provides twice the output voltage for the same total transformer secondary voltage and dc output current as does the full-wave rectifier circuit using a center-tapped secondary. The output of the bridge rectifier circuit is connected to a suitable filter circuit to smooth the pulsating direct current for use in the load circuit. (Filter circuits are discussed in the latter part of this section.)

A variation of the full-wave bridge rectifier circuit uses a transformer with a center-tapped secondary winding to supply two output voltages simultaneously to two separate loads. The circuit is fundamentally the same as that given earlier; for this reason the accompanying circuit schematic has been simplified and redrawn to eliminate the filament transformers and associated filament circuitry. The reference designations previously assigned remain unchanged.

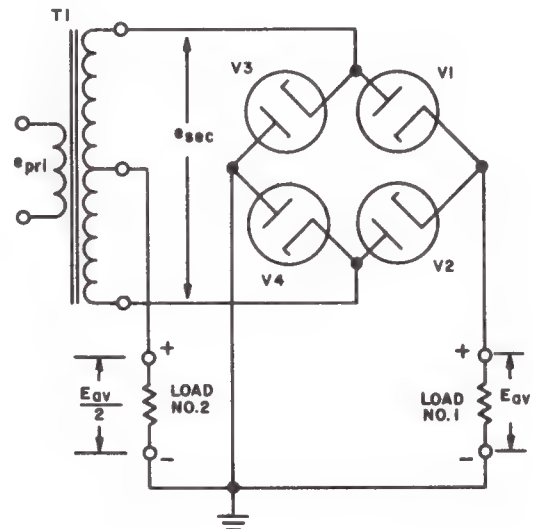

Simplified Full-Wave Center-Tap and Full-Wave Bridge Rectifier Circuit

One advantage of the circuit is that two voltages may be supplied from the same set of rectifiers. One output voltage (E_{av}) is obtained from the output of the bridge circuit; the second output voltage ($E_{av}/2$), which is equal to one half of the bridge output voltage, is obtained by using two rectifiers, V3 and V4 of the bridge, and the center tap of the secondary winding as a conventional full-wave rectifier circuit. (The operation of the full-wave rectifier circuit was previously described in this section.) Although this circuit variation can supply two output voltages simultaneously to two separate loads, there is a limitation on the total current which can be carried by the rectifiers, V3 and V4.

Failure Analysis.

No Output. In the full-wave bridge rectifier circuit, the no-output condition is likely to be limited to one of several possible causes: an open filament supply circuit, defective rectifier tubes, the lack of applied ac voltage, or a shorted load circuit (including shorted filter-circuit components).

A visual check of glass-envelope rectifier tubes can be made to determine whether the filaments are lit. If the filaments are not all lit, the primary voltage may not be applied to the filament transformers (T2, T3, and T4 of Basic Single-Phase, Full-Wave Bridge Rectifier Circuit). If only the filaments of V1 and V2 are not lit, there will be no dc output from the rectifier circuit, and transformer T2 or both tubes may be defective. The tube filaments should be checked for continuity; the presence of correct filament voltage at the tube sockets (V1 and V2) should be determined by measurement. If necessary, the primary and secondary voltages should be checked at the terminals of transformer T2 to determine whether the transformer is defective.

The ac secondary voltage, e_{sec} , should be measured at the terminals of transformer T1 to determine whether the voltage is present and of correct value. If necessary, measure the applied primary voltage, e_{pri} , to determine whether it is present and of the correct value. With the primary voltage removed from the circuit, continuity measurements of the primary and secondary windings should be made to determine whether one of the windings is open, since an open (discontinuity) in either winding will cause a lack of secondary voltage.

With the primary voltage removed from the circuit, resistance measurements can be made at the output terminals of the rectifier circuit (across load) to

determine whether the load circuit, including filter, is shorted. A short in the components of the filter circuit or in the load will cause an excessive load current to flow. If the rectifiers are of the high-vacuum type, the heavy load current will cause the plates of the rectifiers to become heated and emit a reddish glow when the plate dissipation is exceeded and, if allowed to continue, may result in permanent damage to the tubes. The high-voltage bridge circuit normally employs gas-filled rectifiers; an excessive load current will very likely result in permanent damage to the tubes because they are susceptible to damage from current overload. Therefore, once the difficulty in the load circuit has been located and corrected, the gas-filled rectifiers may require replacement as a result of the overload condition.

Low Output. The rectifier tubes should be checked to determine whether the filaments are lit; one or more defective rectifiers in the bridge can cause the low-output condition. Also, failure of only one rectifier in the bridge will allow the circuit to act as a half-wave rectifier with current supplied to the load on alternate half cycles only, and the output voltage will be reduced accordingly. If rectifier tube V1 or V2 is not lit, the trouble is obviously associated with the tube that is not lit; however, if V3 or V4 is not lit, then the trouble may be either the tube (V3 or V4) or its associated filament transformer (T3 or T4). The tube filament should be checked for continuity; the presence of correct filament voltage at the tube socket should be determined by measurement. If necessary, the primary and secondary voltages should be checked at the terminals of the filament transformer (T3 or T4) to determine whether the transformer is defective.

The load current should be checked to make sure that it is not excessive, because a decrease in output voltage can be caused by an increase in load current (decrease in load resistance); for example, excessive leakage in the capacitors of the filter circuit would result in increased load current. Also, the ac secondary voltage, e_{sec} , and the primary voltage, e_{pri} , should be measured at the terminals of transformer T1 to determine whether these voltages are of the correct value. Shorted turns in either the primary or secondary windings will cause the secondary voltage to measure below normal. Shorted turns are not easily detected by resistance measurement; a voltage measurement is a more reliable indication. If the transformer losses (due to shorted turns) are excessive, the

transformer may also become overheated. Another check to determine whether the transformer is defective is to disconnect the secondary load (s) and measure the primary current with the transformer unloaded; excessive primary current is an indication of shorted turns. Still another check is to disconnect all primary and secondary leads from the transformer and make measurements between the individual windings and the core, using an ohmmeter or a Megger (insulation tester), to determine whether any of the windings are shorted to the core or to the Faraday shield (noise-reduction shield between primary and secondary).

SINGLE-PHASE, FULL-WAVE BRIDGE RECTIFIER (SEMICONDUCTOR)

Application.

The single-phase, full-wave bridge rectifier is used in electronic equipment for applications requiring high- or low-voltage dc at a relatively high load current. The circuit can be arranged to furnish negative or positive voltage to the load. A variation of the basic bridge circuit can supply two output voltages simultaneously to separate loads.

Characteristics.

Same characteristics as electron tube version, except that it uses four semiconductor rectifiers (single, multiple, or stacked units) instead of electron tubes.

Circuit Analysis.

General. The single-phase, full-wave bridge rectifier circuit uses two semiconductor rectifiers in series on each side of a single transformer secondary winding (the secondary winding does not require a center tap); four rectifiers are used in the bridge circuit, one in each arm of the bridge. During each half cycle of the impressed ac voltage, two rectifiers, one at each end of the secondary, conduct in series to produce an electron flow through the load. Thus, electrons flow through the load in pulses, one pulse for each half cycle of the impressed voltage. Since two dc output


pulses are produced for each complete input cycle, full-wave rectification is obtained, and the output is similar to that of the conventional full-wave rectifier circuit.

One advantage of the bridge rectifier circuit over a conventional full-wave rectifier is that for a given transformer total-secondary voltage the bridge circuit produces an output voltage which is nearly twice that of the full-wave circuit. Another advantage is that the peak-inverse voltage across an individual rectifier, during the period of time it is nonconducting, is approximately half the peak-inverse voltage across a rectifier in a conventional full-wave circuit designed to produce the same output voltage.

In many power-supply applications, it is desirable to provide two voltages simultaneously—one voltage for high-power stages and the other for low-power stages. For these applications the single-phase, full-wave bridge rectifier circuit can be modified to supply an additional output voltage which is equal to one half of the voltage provided by the full-wave bridge rectifier circuit.



Circuit Operation. A single-phase, full-wave bridge rectifier using semiconductor diodes is shown in the accompanying circuit schematic. Four identical-type semiconductor rectifiers, CR1, CR2, CR3 and CR4, are connected in a bridge circuit across the secondary winding of transformer T1. Each rectifier forms one arm of the bridge circuit; the load is connected between the junction points of the balanced arms of the bridge. The circuit uses a single transformer, T1, either to step up the alternating-source voltage to a higher value in the secondary winding or to step down the voltage to a low value. The circuit application and the values of the input and output voltages determine whether a step-up or step-down transformer is used. The series, or surge, resistor (Rs) is generally used only in high-voltage supplies and is not normally required in low-voltage supplies. The resistor is common to all rectifiers since it is placed in series with the load and filter circuit.

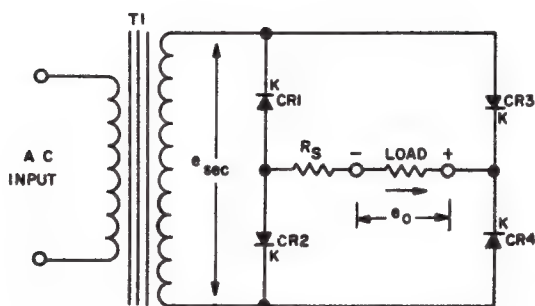The circuit arrangement given in the illustration permits either terminal of the load to be placed at ground potential, depending upon whether a positive or negative dc output is desired.



Basic Single-Phase, Full-Wave Bridge Rectifier Circuit

The operation of the full-wave bridge rectifier circuit can be understood from the simplified circuit schematic (parts A and B) and the waveforms (part C) shown in the accompanying illustration and by reference to the explanation given for the equivalent electron-tube bridge circuit. The basic bridge rectifier schematic, given previously in this discussion, has been simplified and redrawn to show the action which occurs on alternate half-cycles of the applied voltage. The rectifier reference designations used correspond to those assigned in the basic bridge schematic.

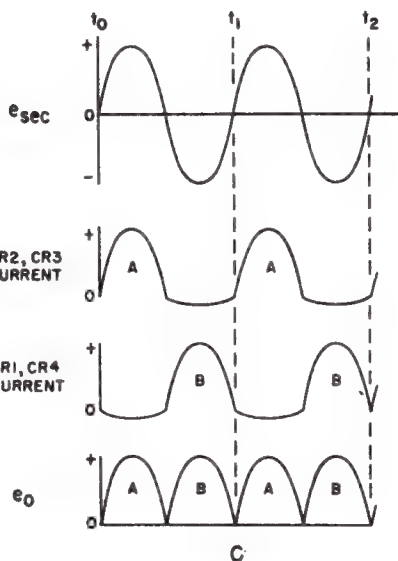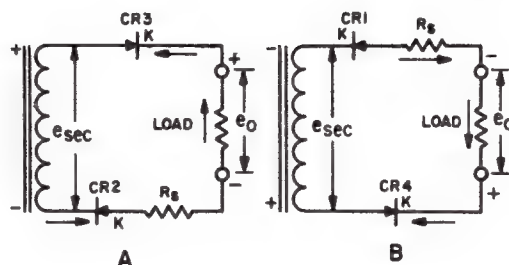

Simplified Full-Wave Bridge Rectifier Circuit and Waveforms

During the first half-cycle the transformer secondary winding may be considered as a voltage source of the polarity given in part A of the illustration. As a result, electrons flow, in the direction indicated by the arrows, through the series circuit composed of rectifier CR2, resistor R_s , the load, and rectifier CR3. This electron flow produces an output pulse of the polarity indicated across the load resistance. Also, during this period, rectifiers CR1 and CR4 are non-conducting.

During the next half-cycle, a secondary voltage is produced of the polarity given in part B of the illustration. As a result, electrons flow, in the direction indicated by the arrows, through the series circuit

composed of rectifier CR1, resistor R_s , the load, and rectifier CR4. The electrons flowing in the series circuit once again produce an output of the same polarity as before across the load resistance. During this period, rectifiers CR2 and CR3 are nonconducting.

From the waveforms given in part C, it can be seen that two rectifiers in series conduct at any instant of time; thus, on alternate half-cycles, electrons flow through the load resistance to produce a pulsating output voltage, e_o . This pulsating waveform results in an irregularly shaped ripple voltage because the output voltage and current are not continuous; the frequency of the ripple voltage is twice the frequency of the ac source. The output of the full-wave bridge rectifier circuit requires filtering to smooth out the ripple and produce a steady dc voltage.

The full-wave bridge rectifier circuit makes continuous use of the transformer secondary; therefore, there are two pulsations of current in the output for each complete cycle of the applied ac voltage. The dc load current phases through the entire secondary winding, flowing in one direction for one half-cycle of the applied voltage, and in the opposite direction for the other half-cycle; thus, there is no tendency for the transformer core to become permanently magnetized. Since little dc core saturation occurs, the effective inductance of the transformer, and therefore the efficiency, is relatively high.

The peak-inverse voltage across an individual rectifier in a full-wave bridge rectifier circuit during the period of time the rectifier is nonconducting is approximately 1.41 times the rms voltage across the secondary winding. Since the secondary voltage, e_{sec} , is applied to two rectifiers in series, less peak-inverse voltage appears across each rectifier. Thus, the bridge circuit can be used to obtain a higher output voltage than can be obtained from a conventional full-wave rectifier circuit using identical rectifiers.


In bridge circuits designed to furnish high-voltage dc to the load, the peak-inverse voltage rating of the semiconductor rectifier is an important consideration. For such applications, several identical-type rectifiers may be placed in series or stacked to withstand the peak-inverse voltage and avoid the possibility of rectifier breakdown.

The output of the full-wave bridge rectifier is similar to that of the conventional full-wave rectifier circuit. For the same total transformer secondary voltage and dc output current, the bridge rectifier

provides twice as much output voltage as does the full-wave rectifiers circuit using a center-tapped secondary.

The output of the bridge rectifier circuit is connected to a suitable filter circuit to smooth out the pulsating direct current for use in the load circuit. (Filter circuits are discussed in the latter part of this handbook.)

A variation of the full-wave bridge rectifier circuit is shown below; it uses a transformer with a center-tapped secondary winding to supply two output voltages simultaneously to two separate loads. The circuit is fundamentally the same as that given earlier; therefore, the reference designations previously assigned to the basic circuit remain unchanged. This modified circuit uses two series (surge) resistors which are common to both the full-wave center-tap rectifier circuit and the full-wave bridge rectifier circuit.

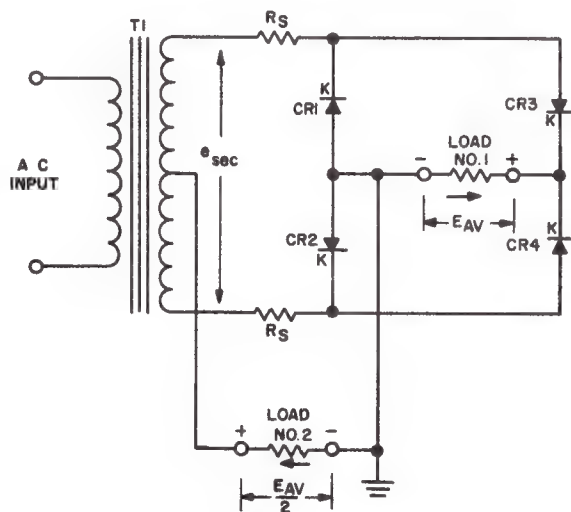

Full-Wave Center-Tap and Full-Wave Bridge Rectifier Circuit

One advantage of this circuit is that two voltages may be supplied from the same set of rectifiers. One output voltage (E_{av}) is obtained from the output of the bridge circuit; the other output voltage ($E_{av}/2$), which is equal to one half of the bridge output voltage, is obtained by using two rectifiers, CR1 and CR2 of the bridge, and the center tap of the secondary winding as a conventional full-wave rectifier circuit.

Although this circuit can supply two output voltages simultaneously to two separate loads, there is a limitation on the total current which can be safely carried by rectifiers CR1 and CR2.

Failure Analysis.

No Output. In the full-wave bridge rectifier circuit, the no-output condition is likely to be limited to one of several possible causes: the lack of applied ac voltage (including the possibility of a defective transformer), a shorted load circuit (including shorted filter-circuit components), or defective rectifiers.

The ac secondary voltage, e_{sec} , should be measured at the transformer terminals to determine whether the voltage is present and of the correct value. If necessary, measure the applied primary voltage to determine whether it is present and of the correct value. With the input voltage removed from the circuit, continuity measurements of the windings can be made to determine whether one of the windings is open, since an open winding will cause a lack of secondary voltage.

If the circuit includes one or more series resistors (R_s), continuity measurements can be made to determine whether the resistors are open. When a series resistor is found to be open, the associated rectifiers and load circuit (including filter-circuit components) should be checked to determine whether excessive load current or defective rectifiers have caused the resistor to act as a fuse and to open.

With the ac supply voltage removed from the input of the circuit and with the load disconnected from the rectifiers, resistance measurements can be made across the load to determine whether the load circuit (including filter components) is shorted.

Although physical appearance is not a positive indication of condition, the rectifiers may be given a visual check for a change in physical appearance which can indicate rectifier failure. A relative check of the rectifier condition can be made using an ohmmeter, as outlined in a previous paragraph of this section. However, failure of the rectifiers may be the result of other causes; for this reason, tests of the filter and load circuit are necessary.

Low Output. Each rectifier should be checked to determine whether the low output is due to normal rectifier aging or to one or more defective rectifiers. A relative check of rectifier condition can be made using an ohmmeter, as outlined in a previous paragraph of this section. A comparison can be made by

checking all rectifiers and noting the results obtained to determine whether the rectifiers have similar characteristics. If the forward resistance of the rectifier increases, the output voltage will decrease. Also, if the reverse resistance decreases, the output voltage will decrease and the amplitude of the ripple will become excessive.

Complete failure of only one rectifier in the bridge will allow the circuit to act as a half-wave rectifier with current supplied to the load on alternate half-cycles only, and the output voltage will be reduced accordingly. Furthermore, whenever this occurs, the ripple amplitude will also increase, and the ripple frequency will be that of the ac source (instead of twice the source frequency).

The load current should be checked to make sure that it is not excessive, because a decrease in output voltage can be caused by an increase in load current (decrease in load resistance); for example, excessive leakage in the capacitors of the filter circuit would result in increased load current. Also, the ac secondary voltage, e_{sec} , and the input (primary) voltage should be measured at the terminals of transformer T1 to determine whether these voltages are of the correct value. Shorted turns in either the primary or secondary windings will cause the secondary voltage to measure below normal. (A check for shorted turns is outlined in the failure analysis described for the electron-tube full-wave bridge rectifier circuit given earlier in this section of the handbook.)

In the modified full-wave center-tap and full-wave bridge circuit, it is possible to have two definite conditions of low voltage caused by defective rectifiers: the output voltage (E_{av}) to load No. 1 can be low and the output voltage (E_{av})/2 to load No. 2 normal, or both output voltages can be below normal. If the load currents are not excessive and the filter components have been checked as satisfactory the defective rectifiers in the first case are assumed to be CR3 and CR4 of the bridge circuit, and those in the second case are assumed to be CR1 and CR2, which are common to both the full-wave center-tap and the bridge circuits. In a practical full-wave center-tap and full-wave bridge circuit, the two rectifiers designated in the schematic as CR1 and CR2 may have higher current ratings than the rectifiers designated as CR3 and CR4, because CR1 and CR2 must carry the combined currents of both output loads. For this reason, rectifiers CR1 and CR2 may not be directly interchangeable with rectifiers CR3 and CR4 of the bridge circuit.

PART 2-2. MULTIPHASE POWER SUPPLIES

THREE-PHASE HALF-WAVE (SINGLE "Y" SECONDARY) RECTIFIER (ELECTRON TUBE)

Application.

The three-phase, (single "y" secondary) or "Half-Wave Star" rectifier is used in electronic equipment for applications where the primary ac source is three-phase and the dc power requirements exceed 1 kilowatt. The rectifier circuit can be arranged to furnish negative or positive high-voltage output to the load.

Characteristics.

Input to circuit is three-phase ac; output is dc with amplitude of ripple voltage less than that for a single-phase rectifier.

Uses three high-vacuum or gas-filled electron-tube diodes as rectifiers.

Output is relatively easy to filter; dc output ripple frequency is equal to three times the primary line-voltage frequency.

Has good regulation characteristics.

Circuit provides either positive- or negative-polarity output voltage.


Uses multiphase power transformer with star- or wye-connected secondary windings; primary windings may be either delta- or wye-connected.

Circuit Analysis.

General. The three-phase, half-wave (single "y" secondary) rectifier is the simplest type of three-phase rectifier circuit. The term *three-phase* refers to

the primary ac source, which is the equivalent of three single-phase sources, each source supplying a sine-wave voltage 120 degrees out of phase with the others. Fundamentally, this rectifier circuit resembles three single-phase, half-wave rectifier circuits, each rectifier circuit operating from one phase of a three-phase source and sharing a common load. The voltages included in the transformer secondary windings differ in phase by 120 degrees; thus, each half-wave rectifier conducts for 120 degrees of the complete input cycle and contributes one third of the dc current supplied to the load. Electrons flow through the load in pulses, one pulse for each positive half cycle of the impressed voltage in each of the three phases; therefore, the output voltage has a ripple frequency which is three times the frequency of the ac source.


Circuit Operation. A basic three-phase, half-wave rectifier is illustrated in the circuit schematic below. The circuit uses a three-phase transformer, T1, to step up the alternating source voltage to a high value in the star- or wye-connected secondaries. The primary windings of transformer T1 are shown delta-connected, although in some instances the primary windings may be wye-connected (as for a three- or four-wire system). The plate of each rectifier tube, V1, V2, and V3, is connected to a high-voltage secondary winding. One filament transformer, T2, is used to supply the filament voltage to all three rectifiers since the filaments of the rectifiers are all at the same potential. The primary of transformer T2 is connected to one phase of the three-phase source. The load is connected between the junction point of the wye-connected secondary windings and the filament circuit of the rectifier tubes.

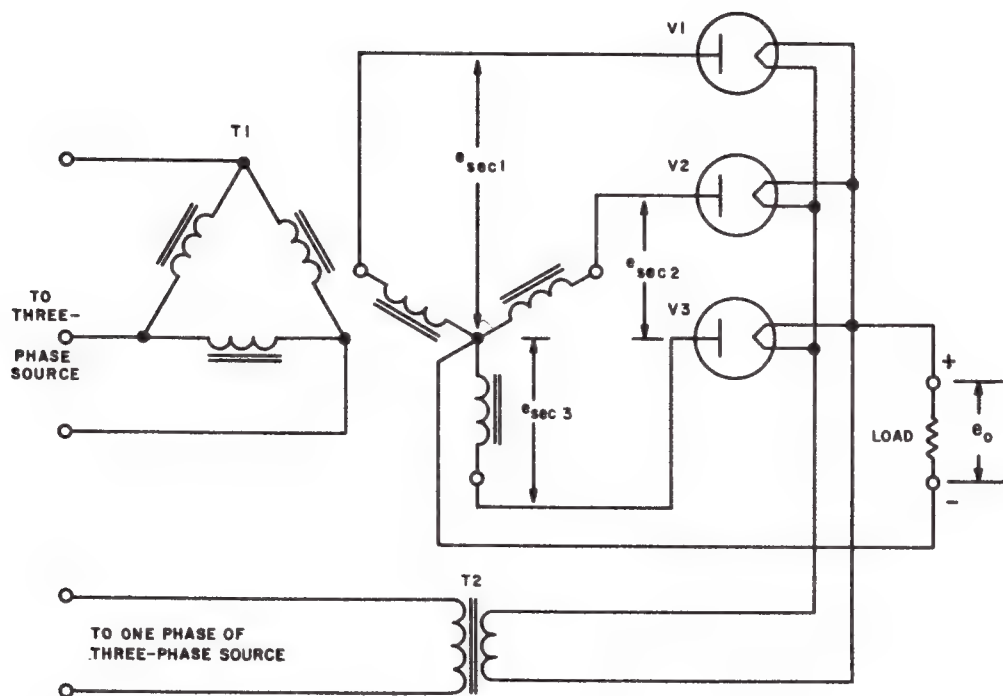

Basic Three-Phase, Half-Wave (Single "y" Secondary)
Rectifier Circuit

In the circuit illustrated, either terminal of the load may be placed at ground potential, depending upon whether a positive or negative dc output is desired.

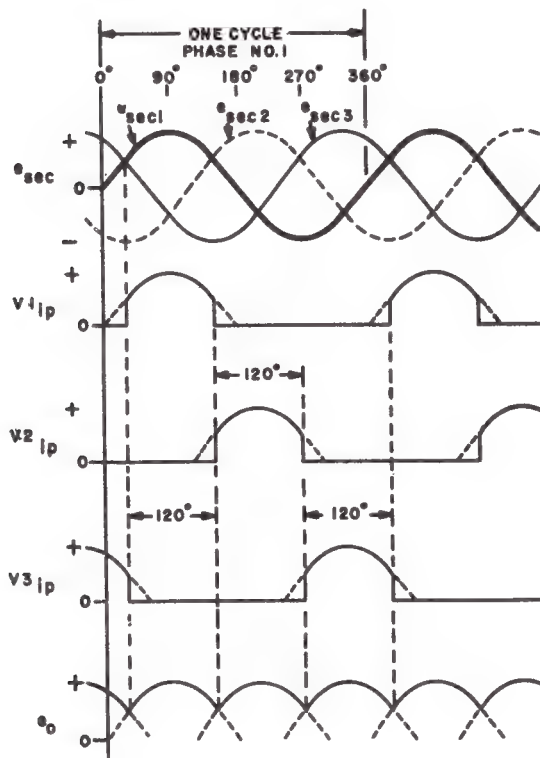The operation of the three-phase, half-wave rectifier circuit can be understood from the circuit schematic previously given and from the waveforms shown in the accompanying illustration.



Three-Phase, Half-Wave Rectifier Waveforms

Each phase of the three-phase secondary voltage is applied across a rectifier and the common load. The secondary voltage of phase No. 1 (e_{sec1}) is applied to rectifier V1, the secondary voltage of phase No. 2 (e_{sec2}) is applied to rectifier V2, and the secondary voltage of phase No. 3 (e_{sec3}) is applied to rectifier V3. The waveform given in the accompanying illustration as e_{sec} shows each of the three secondary voltages displaced 120 degrees from each other. On positive half cycles of e_{sec1} , electrons flow through the

load and rectifier V1; the pulse of plate current for rectifier V1 is identified in the illustration as the waveform, $V1 i_p$. On positive half cycle of e_{sec2} , electrons flow through the load and rectifier V2; the pulse of plate current for V2 is identified as $V2 i_p$. On positive half cycles of e_{sec3} , electrons flow through the load and rectifier V3; the pulse of plate current for V3 is identified as $V3 i_p$. From the three individual plate-current waveforms it can be seen that the start of a conduction period for any rectifier occurs 120 electrical degrees from the start of a conduction period for another rectifier in the circuit. The output voltage, e_o , across the load resistance is determined by the instantaneous currents flowing through the load; therefore, the output voltage has a pulsating waveform which never drops to zero because of the nature of the rectifier conduction periods.

If it were not for the overlapping of applied three-phase secondary voltages, the rectifiers would each conduct for 180 degrees of the cycle; however, during the first 30 degrees of a half cycle, the plate of the rectifier is negative with respect to its positive filament (cathode), and it will not conduct until the positive voltage applied to the plate exceeds the dc output voltage pulsations present across the load and at the filament circuit. Also, during the last 30 degrees of a half cycle, the plate is again negative with respect to the filament, and rectifier conduction ceases because the rectifier of another phase has started to conduct and produce a positive voltage across the load. In other words, each rectifier tube conducts for only one-third cycle, and this results in a series of dc output voltage pulsations with an irregularly shape ripple voltage; the frequency of the ripple voltage is equal to three times the frequency of the ac source. Because the ripple frequency is higher than that of a single-phase rectifier circuit, the three-phase, half-wave rectifier circuit requires less filtering to smooth out the ripple and produce a steady dc voltage.

In order to keep dc core saturation to a minimum (because of current flowing in one direction only in the secondary windings) and to keep the efficiency relatively high, it is necessary to use a single three-phase transformer in this circuit, rather than three separate single-phase transformers.

The three-phase, half-wave rectifier produces across the load a pulsating (unfiltered) dc output voltage, E_{av} , as follows:

where: $E_{av} = 1.17 E_{rms}$
 E_{rms} = rms voltage across one
 secondary winding of
 three-phase transformer

The *peak inverse voltage* across an individual rectifier in the three-phase, half-wave rectifier circuit during the period of time the tube is nonconducting is approximately 2.45 times the rms voltage across the secondary winding of one phase. Some pulsating dc voltage is always present across the load, and this voltage is in series with the ac voltage applied to the plate; therefore, the sum of the instantaneous value of pulsating dc voltage across the load and the instantaneous peak voltage across the secondary represent the value of peak inverse voltage across the rectifier tube. The peak inverse voltage *per tube* can be expressed as:

where: $E_{inv} \text{ (per tube)} = 2.45 E_{rms}$
 E_{rms} = rms voltage across one
 secondary winding of the
 three-phase transformer

The output of the three-phase, half-wave rectifier circuit is connected to a suitable filter circuit to smooth the pulsating direct current for use in the load circuit. (Filter circuits are discussed in the Filter Section of this handbook.

Failure Analysis.

No Output. In the three-phase, half-wave rectifier circuit, the no-output condition is likely to be limited to one of several possible causes: the lack of ac filament supply, the lack of applied ac high voltage, of a shorted load circuit (including shorted filter components).

A visual check of the glass-envelop rectifier tubes can easily be made to determine whether all filaments are lit; if they are not lit, the filament voltage should be measured at the secondary terminals of transformer T2. If necessary, measure the applied primary voltage to determine whether it is present and of the correct value. With the primary voltage removed from the circuit, continuity (resistance) measurements of the primary and secondary windings should be made to determine whether one winding is open, since an open winding (primary or secondary) will cause a lack of filament voltage.

With the primary voltage removed from the circuit, continuity (resistance) measurements should be made of the secondary and primary windings, to determine whether one or more windings are open and whether the common terminal (s) of the wye-connected secondaries is connected to the load circuit. If necessary, the ac secondary voltage applied to the rectifier plates may be measured between the common terminal of the wye-connected secondaries and the plate of one or more rectifiers, to determine whether voltage is present and of the correct value. Also, if necessary, measure the applied three-phase primary voltage to determine whether it is present and of the correct value.

With the primary voltage removed from the circuit, resistance measurements can be made at the output terminals of the rectifier circuit (across load) to determine whether the load circuit, including filter, is shorted. A short in the components of the filter circuit or in the load circuit will cause an excessive load current to flow; if the rectifier tube is of the high-vacuum type, the heavy load current will cause the plate of the rectifiers to become heated and emit a reddish glow when the plate dissipation is exceeded and, if allowed to continue, may result in permanent damage to the tubes. If gas-filled rectifiers are used in the circuit, excessive load current will result in permanent damage to the tubes because gas-filled rectifiers are very susceptible to damage from current overload. Therefore, once the difficulty in the load circuit has been located and corrected, the gas-filled rectifiers will require replacement as a result of the overload condition.

Low Output. If only one or two phases of the three-phase, half-wave rectifier circuit are operating normally the output voltage will be lower than normal. For example, if only one secondary winding and associated rectifier is in operation, the effect is the same as though it were a single-phase, half-wave rectifier circuit and, as a result, the output voltage is much lower than normal. When two phases are operating, the output voltage is somewhat higher and, when all three phases are operating, the output is normal. Thus, the low-output condition can be due to the fact that one or more secondary-phase circuits are not functioning normally.

The rectifier tubes should be checked first to determine whether all filaments are lit. All rectifier filaments are in parallel; therefore, if one filament is

not lit, the trouble is obviously associated with this particular tube. The tube filament should be checked for continuity; the presence of correct filament voltage at the tube socket should be determined by measurement.

With the three-phase primary voltage removed from the circuit, continuity measurements should be made of the secondary and primary windings, to determine whether one (or more) of the windings is open. If necessary, the ac secondary voltage applied to each rectifier plate may be measured between the common terminal of the secondary wye connection and the plate of each rectifier, to determine whether voltage is present and of the correct value. Also, if necessary, measure the applied three-phase primary voltage at each of the phases, to determine whether each voltage is present and of the correct value, since a low applied primary voltage can result in a low secondary voltage.

Shorted turns in either the primary or secondary windings will cause the secondary voltage to measure below normal. Disconnect all secondary leads from the transformer, T1, and measure the primary current in each leg of the three-phase primary with the transformer unloaded; excessive primary current is an indication of shorted turns. A secondary winding which is shorted to the core can cause a low-output voltage indication; all leads should be disconnected from the transformer and measurements made between the individual windings and the core, using an ohmmeter or a Megger (insulation tester), to determine whether any of the windings are shorted to the core.

The rectifier-output current (to the filter circuit and to the load) should be checked to make sure that it is within tolerance and is not excessive. A low-output condition due to a decrease in load resistance would cause an increase in load current; for example, excessive leakage in the capacitors of the filter circuit would result in increased load current.

THREE-PHASE, HALF-WAVE (SINGLE "Y" SECONDARY) RECTIFIER (SEMICONDUCTOR)

Application.

Same as electron tube version.


Characteristics.

Same characteristics as electron tube version, except it uses three semiconductor rectifiers (single, multiple, or stacked units) instead of electron tubes.

Circuit Analysis.

General. The three-phase, half-wave, (single "Y" secondary) rectifier is the simplest type of three-phase rectifier circuit. Fundamentally, this rectifier circuit is three single-phase half-wave rectifier circuits, each rectifier operating from one phase of a three-phase source and sharing a common load. The voltages induced in the transformer secondary windings differ in phase by 120 degrees; thus, each half-wave rectifier conducts for 120 degrees of the complete input cycle, and contributes one-third of the dc current supplied to the load. Electrons flow through the load in pulses, one pulse for every other half-cycle of the impressed voltage in each of the three phases; therefore, the output voltage has a ripple frequency which is three times the frequency of the ac source.

Circuit Operation. A basic three-phase, half-wave rectifier is illustrated in the accompanying circuit schematic. The circuit uses a three-phase transformer, T1, to step up the alternating source voltage to a high value in the wye-connected secondaries. The primary windings of transformer T1 are shown delta-connected, although in some instances the primary windings may be wye-connected (as for a three- or four-wire system). Each rectifier, CR1, CR2, and CR3, is connected to a high-voltage secondary winding. The load is connected between the junction point of the wye-connected secondary windings and the common connection of the three rectifiers.

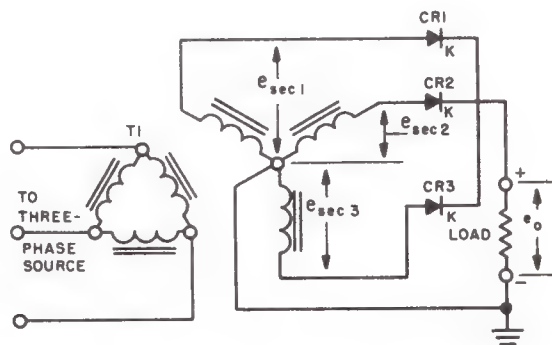

Basic Three-Phase, Half-Wave (Single "Y" Secondary) Rectifier Circuit

In the circuit illustrated, either terminal of the load can be placed at ground potential, depending upon whether a positive or negative dc output is desired. However, it is good design practice for the dc output terminal associated with the junction of the wye-connected secondaries to be grounded, in this case, the secondary-to-core insulation need not be as great as it would be if the secondary windings were above ground by the amount of the dc output voltage. When a negative high-voltage dc supply is required, it is common practice to keep the junction of the wye-connected secondaries at ground (chassis) potential and to reverse the connections to the rectifiers (CR1, CR2, and CR3); in this case, the output polarity across the load will be opposite that shown on the schematic.

The semiconductor rectifiers, CR1, CR2, and CR3, are made up of several rectifiers in series to safely withstand the peak inverse voltage of the circuit and to prevent rectifier breakdown. Since each individual rectifier cell in the series-connected arrangement (multiple or stacked units) has a maximum reverse-voltage rating, it is necessary for the series combination of rectifiers in any secondary leg to have a total reverse-voltage rating in excess of the maximum peak inverse voltage encountered in the circuit configuration. Although the voltage ratings for the commercially available silicon rectifiers are generally higher than for the selenium rectifiers, both selenium and silicon rectifiers are commonly used in high-voltage power supplies. Because a choke-input filter system is commonly employed with this circuit, series, or surge, resistors are not normally used, and for this reason are not shown in the schematic.

The operation of the three-phase, half-wave rectifier circuit can be readily understood from a study of the equivalent electron-tube circuit description and the associated waveforms given previously in this section of the handbook. For this reason, an explanation of circuit operation is not given here.

The action of the semiconductor rectifiers in this circuit is essentially the same as that described for the equivalent electron-tube circuit. The rectifier in each secondary leg conducts for only one-third cycle, and this results in a series of dc output voltage pulsations. The output voltage, e_o , across the load resistance is determined by the instantaneous currents flowing through the load; therefore, the output voltage never drops to zero because of the overlapping of applied three-phase secondary voltages and the resulting rec-

tifier conduction in each secondary leg. Because the ripple voltage is equal to three times the frequency of the ac source, the circuit requires less filtering to smooth out the ripple and produce a steady dc voltage than does a single-phase rectifier circuit.

The peak inverse voltage across the rectifier (multiple or stacked units) in one secondary leg of the three-phase, half-wave circuit during the period of time the rectifier is nonconducting is approximately 2.45 times the rms voltage (e_{sec}) across the secondary winding of one phase.

The regulation of the circuit is considered to be very good, and is better than that of a single-phase rectifier circuit having equivalent power-output rating; the semiconductor rectifier characteristics and the three-phase input contribute greatly to the improved regulation characteristic of the supply. The output of the three-phase, half-wave rectifier circuit is connected to a suitable filter circuit, to smooth the pulsating direct current for use in the load circuit. (Filter circuits are discussed in the Filter Section of this handbook.)

Failure Analysis.

No Output. In the three-phase, half-wave rectifier circuit, the no-output condition is likely to be limited to one of three possible causes: the lack of applied ac voltage, a shorted load circuit (including shorted filter capacitors), or an open filter choke.

NOTE

Most filter circuits used in Navy equipment employ two-section choke-input filters; thus, an open choke in either section will cause no output.

Measure the applied three-phase primary voltage to determine whether it is present and of the correct value. With the primary voltage removed from the circuit, continuity measurements should be made of the secondary and primary windings, to determine whether one or more than one winding is open and whether the common terminal(s) of the wye-connected secondaries is connected to the load circuit. If necessary, the ac secondary voltage applied to the rectifiers may be measured between the common terminal(s) of the wye-connected secondaries and one or more rectifiers, to determine whether voltage is present and of the correct value.

With the primary voltage removed from the circuit, resistance measurements can be made at the output terminals of the rectifiers circuit (across load) to

determine whether the load circuit, including the filter, is shorted. (As explained in the preceding note, an open choke in the filter circuit will also cause no output.) A short in the load circuit (including components in the filter circuit) will cause an excessive load current to flow and may result in permanent damage to the rectifiers. Therefore, once the difficulty in the load (including filter) circuit has been located and corrected, the rectifiers should be checked to determine whether they have been damaged as a result of the overload condition.

Low Output. If only one or two phases of the three-phase, half-wave rectifier circuit are operating normally, the output voltage will be lower than normal. For example, if only one secondary winding and associated rectifier is in operation, the effect is the same as though it were a single-phase, half-wave rectifier circuit; as a result, the output voltage is much lower than normal. When two phases are operating, the output voltage is somewhat higher, and when all three phases are operating, the output is normal. (Also, the percentage of ripple voltage will change for each of the conditions mentioned.) Thus, the low-output condition can be due to the fact that one (or more) of the secondary-phase circuits (including rectifiers) is not functioning normally.

The rectifiers should be checked to determine whether the low output is due to normal rectifier aging, or to one or more defective rectifiers. A relative check of rectifier condition can be made by using an ohmmeter, as outlined in a previous paragraph of this section. (A comparison can be made by checking one rectifier against each of the others to determine whether they have similar characteristics.) If the forward resistance of a rectifier increases, the output voltage will decrease. Also, if the reverse resistance decreases, the output voltage will decrease, and the amplitude of the ripple voltage will increase.

With the three-phase primary voltage removed from the circuit, continuity measurements should be made of the secondary and primary windings, to determine whether one (or more) of the windings is open. If necessary, the ac secondary voltage (e_{sec}) applied to each rectifier may be measured between the common terminal of the secondary wye connection and each rectifier, to determine whether voltage is present and of the correct value. Also, if necessary, measure the applied three-phase voltage at each of the phases, to determine whether each voltage is present and of the correct value, since low applied primary

voltages can result in low secondary voltages.

Shorted turns in either the primary or secondary windings will cause the secondary voltage to measure below normal. (A check for shorted turns is outlined in the failure analysis described for the electron-tube three-phase, half-wave rectifier circuit discussed earlier in this section of the handbook.)

The load current should be checked to make sure that it is not excessive, because a decrease in output voltage can be caused by an increase in load current (decrease in load resistance); for example, excessive leakage in the capacitors of the filter circuit will result in increased load current.

THREE-PHASE, FULL-WAVE (SINGLE "Y" SECONDARY) RECTIFIER (ELECTRON TUBE)

Application.

The three-phase, full-wave rectifier with single-wye secondary is used in electronic equipment for applications where the primary ac source is three-phase and the dc output requirements are relatively high. The rectifier circuit can be arranged to furnish either negative or positive high-voltage output to the load.

Characteristics.

Input to circuit is three-phase ac; output is dc with amplitude of ripple voltage less than that for a single-phase rectifier.

Uses six high-vacuum or gas-filled electron-tube diodes as rectifiers.

Output requires very little filtering; dc output ripple frequency is equal to six times the primary line-voltage frequency.

Has good regulation characteristics.

Circuit provides either positive- or negative-polarity output voltage.

Requires separate filament transformers or separate filament windings for rectifier tubes.

Uses multiphase power transformer with wye-connected secondary windings; primary windings may be either delta- or wye-connected.

Circuit Analysis.


General. The three-phase, full wave (single-wye-connected secondary) rectifier is extensively used where a large amount of power is required by the load, such as for large shipboard or shore electronic installations. The term *three-phase* refers to the primary ac source, which is the equivalent of three single-phase sources, each source supplying a sine-wave voltage 120 degrees out of phase with the

others. Because of the three-phase transformer secondary configuration, the circuit is sometimes referred to as a *bridge* or *six-phase* rectifier circuit.

In many power-supply applications, it is desirable to provide two voltages simultaneously—one voltage for high-power stages and the other voltage for low-power stages. For these applications the three-phase, full-wave rectifier circuit can be modified to supply an additional output voltage, which is equal to one half of the voltage provided by the full-wave rectifier circuit.

Circuit Operation. The basic three-phase, full-wave rectifier circuit is illustrated in the accompanying

circuit schematic. The circuit uses a conventional three-phase power transformer, T1, to step up the alternating source voltage to a high value in the wye-connected secondaries. The primary windings of transformer T1 are shown delta-connected, although in some instances the primary windings may be wye-connected (as for a three- or four-wire system). The plate of rectifier V1 and the filament (cathode) of rectifier V6 are connected to secondary terminal No. 1 of transformer T1; the plate of rectifier V2 and the filament of rectifier V4 are connected to secondary terminal No. 2; the plate of rectifier V3 and the filament of rectifier V5 are connected to secondary terminal No. 3.

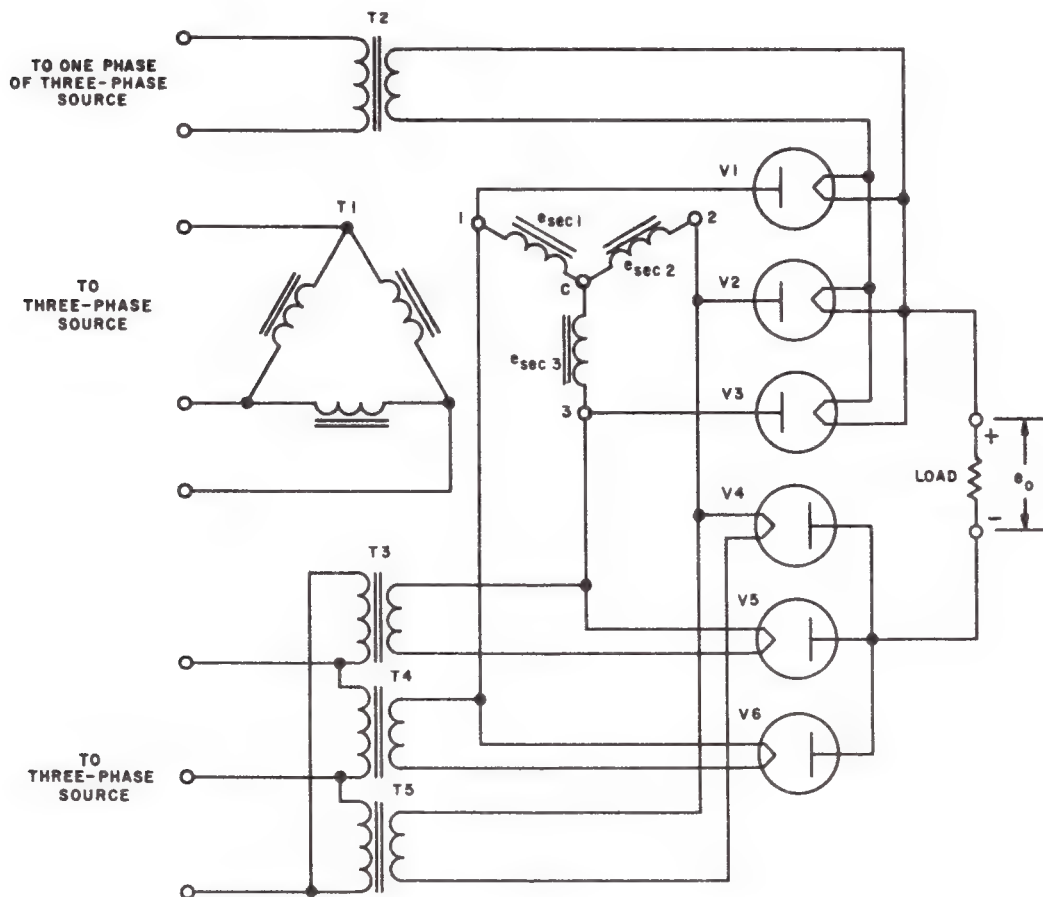

Basic Three-Phase, Full-Wave (Single "Y" Secondary) Rectifier Circuit

One filament transformer, T2, is used to supply the filament voltage to rectifiers V1, V2, and V3, since the filaments of these rectifiers are all at the same potential. However, since the filaments of rectifiers V4, V5, and V6 have a high potential difference existing between them, three separate filament transformers (T3, T4, and T5) are used. A single filament transformer may be used for this purpose, provided that it incorporates three separate filament windings that are well insulated from each other and grounded (chassis). The primary windings of filament transformers T3, T4, and T5 are connected to different phases of the three-phase source. The ac voltage for the primaries of the filament transformers is applied independent of, and prior to, the primary voltage to the three-phase power transformer, T1. A time-delay arrangement, either manually operated or automatic, normally permits the rectifier filaments to be preheated to the normal operating temperature before the high-voltage ac can be applied to the rectifier circuit.

The circuit arrangement given in the illustration permits either terminal of the load to be placed at ground potential, depending upon whether a positive or negative dc output is desired; however, the circuit is commonly arranged for a positive dc output, with the negative output terminal at ground (chassis). The circuit is typical of high-voltage dc supplies designed for use in radar sets, communication transmitters, or other equipment for which the dc power requirement is several kilowatts or more.



The operation of the three-phase, full-wave rectifier circuit can be understood from the simplified circuit schematics (parts A through F) and the waveforms given in the accompanying illustration. The basic three-phase, full-wave rectifier schematic, given earlier in this discussion, has been simplified to show the circuit action throughout the electrical cycle; the reference designations used correspond to those assigned in the basic circuit schematic.

The voltages developed across the secondary windings of transformer T1 are 120 degrees out of phase with relation to each other and are constantly changing in polarity. The polarities indicated for the secondary windings in the simplified circuit sche-

matics (parts A through F) of the accompanying illustration represent the instantaneous polarity of the induced voltages in the secondary. The arrows on the schematics are used to indicate the directions of electron flow in the circuit.

The plates of rectifiers V1, V2, and V3 are connected to secondary windings No. 1, No. 2, and No. 3, respectively; the filaments (cathode) of rectifiers V6, V4, and V5, are connected to secondary windings No. 1, No. 2, and No. 3, respectively. When the plates of V1, V2, and V3 are positive with respect to their filaments, the tubes will conduct; when the filaments of V4, V5, and V6 are negative with respect to their plates, there tubes will conduct. At any given instant of time in the three-phase, full-wave rectifier circuit, a rectifier, the load, and a second rectifier are in series across two of the wye-connected transformer secondaries and, therefore, two rectifiers are conducting. Each of the six rectifiers conducts for 120 degrees of an electrical cycle; however, there is an over-lap of conduction periods, and the rectifiers conduct in a sequence which is determined by the phasing of the instantaneous secondary voltages of the power transformer. In the circuit described, two rectifiers are conducting at any instant of time, with rectifier conduction occurring in the following order: V1 and V4, V1 and V5, V2 and V5, V2 and V6, V3 and V6, V3 and V4, V1 and V4, etc.

Refer to the secondary-voltage waveform, e_{sec} , shown in the accompanying illustration. Assume that the ac voltage induced in secondary No. 1 (between 30 and 90 electrical degrees, phase No. 1) is approaching its maximum positive value (at 90 degrees); also, the voltage induced in secondary No. 2 has reached its maximum negative value (at 30 degrees) and is decreasing. (Secondary No. 3, although positive at 30 degrees, is decreasing to zero.) This condition is shown by the simplified schematic of part A in the accompanying illustration. The plate of rectifier V1 becomes positive with respect to its filament (cathode), and the filament of rectifier V4 is negative with respect to its plate; therefore, both tubes conduct, and the electrons flow through V4, the load, and V1 for 60 degrees of the electrical cycle.

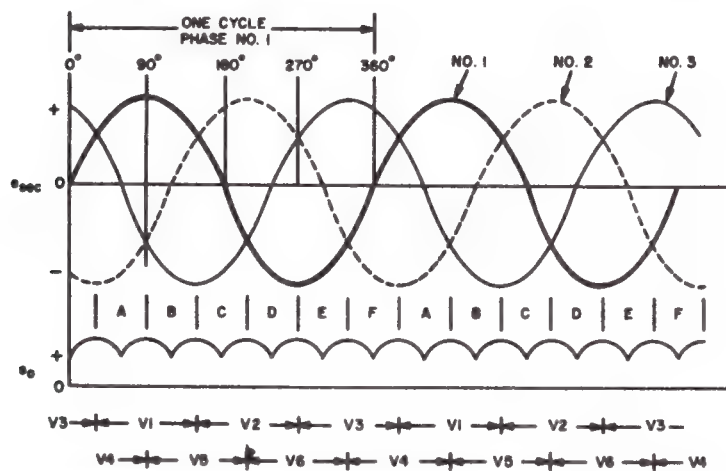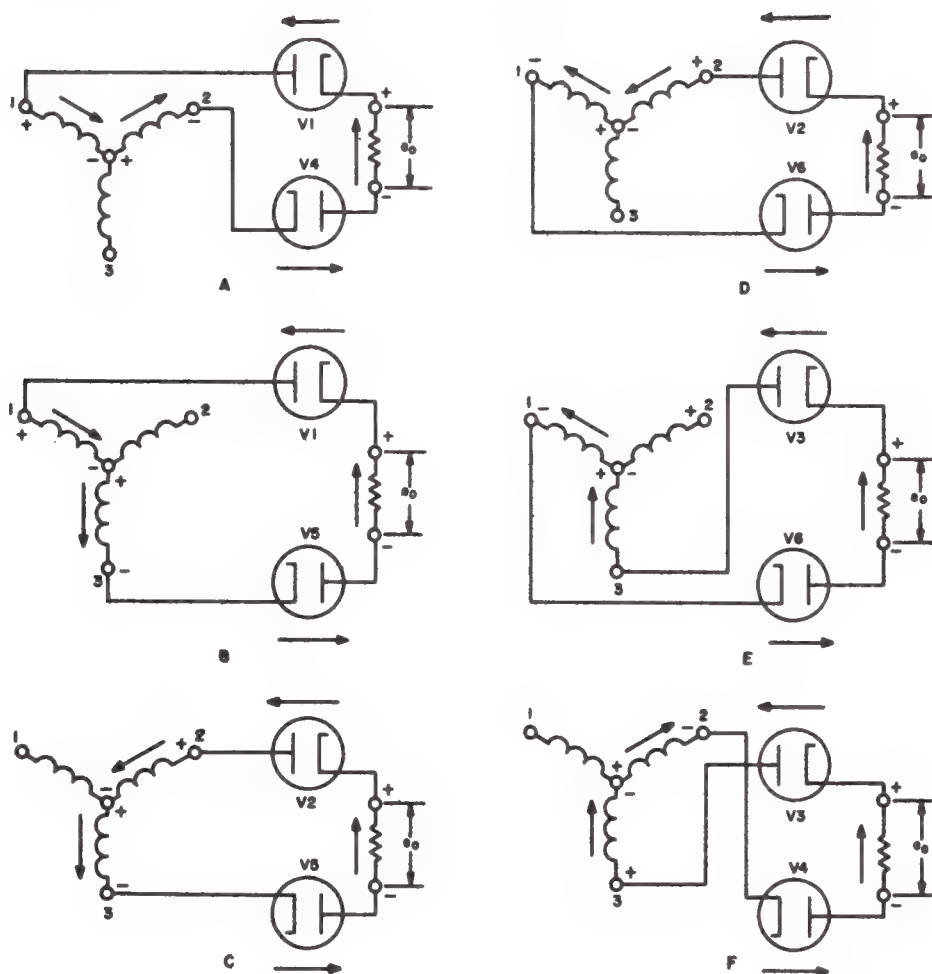

Simplified Circuit Schematics and Waveforms for
Three-Phase, Full-Wave Rectifier

In part B, the ac voltage induced in secondary No. 1 reaches its maximum positive value (at 90 degrees) and starts to decrease during the next 60 degrees of the cycle; the voltage induced in secondary No. 3 is approaching its maximum negative value. The plate of V1 remains positive with respect to its filament, and the filament of V5 becomes negative with respect to its plate; therefore, V1 continues to conduct and V5 takes over conduction from V4, with V1 and V5 conducting in series with the load. Electrons flow through V5, the load, and V1 for another 60 degrees of the cycle.

In part C, the ac voltage induced in secondary No. 3 reaches its maximum negative value and the positive voltage in secondary No. 2 is increasing. The filament of V5 remains negative with respect to its plate, and the plate of V2 becomes positive with respect to its filament; therefore, V5 continues to conduct and V2 takes over conduction from V1, with V2 and V5 conducting in series with the load. Electrons flow through V5, the load, and V2 for another 60 degrees of the cycle.

In part D, the ac voltage induced in secondary No. 2 reaches its maximum positive value and starts to decrease; the voltage induced in secondary No. 1 is approaching its maximum negative value. The plate of V2 remains positive with respect to its filament, and the filament of V6 becomes negative with respect to its plate; therefore, V2 continues to conduct and V6 takes over conduction from V5, with V2 and V6 conducting in series with the load. Electrons flow through V6, the load, and V2 for another 60 degrees of the cycle.

In part E, the ac voltage induced in secondary No. 3 is approaching its maximum positive value, and the negative voltage in secondary No. 1 is decreasing. The filament of V6 remains negative with respect to its plate, and the plate of V3 becomes positive with respect to its filament; therefore, V6 continues to conduct and V3 takes over conduction from V2, with V3 and V6 conducting in series with the load. Electrons flow through V6, the load, and V3 for another 60 degrees of the cycle.

In part F, the ac voltage induced in secondary No. 2 is approaching its maximum negative value, and the positive voltage in secondary No. 3 is decreasing. The plate of V3 remains positive with respect to its filament, and the filament of V4 becomes negative with respect to its plate; therefore, V3 continues to conduct and V4 takes over conduction from V6, with V3

and V4 conducting in series with the load. Electrons flow through V4, the load, and V3 for another 60 degrees of the cycle.

The cycle of operation is repeated, as shown in part A, when the dc voltage induced in secondary No. 2 reaches its maximum negative value and the positive voltage in secondary No. 1 is increasing. The filament of V4 remains negative with respect to its plate, and the plate of V1 becomes positive with respect to its filament; therefore, V4 continues to conduct and V1 takes over conduction from V3, with V1 and V4 conducting in series with the load. Electrons flow through V4, the load, and V1, to initiate another complete cycle.

Thus, from the action described above, it can be seen that each positive and negative peak in each of the three phases produces a current pulse in the load. Because of the nature of the rectifier conduction periods, each rectifier tube conducts for 120 degrees of the cycle and carries one third of the total load current. The output voltage, e_o , produced across the load resistance is determined by the instantaneous currents flowing through the load; therefore, the output voltage has a pulsating waveform, which results in an irregularly shaped ripple voltage, because the output current and voltage are not continuous. The frequency of the ripple voltage is six times the frequency of the ac source. Since this ripple frequency is higher than the ripple frequency of a single-phase, full-wave rectifier circuit or a three-phase, half-wave rectifier circuit, relatively little filtering is required to smooth out the ripple and produce a steady dc voltage.

The three-phase, full-wave rectifier circuit makes continuous use of the transformer secondaries, with the dc load current passing through a secondary winding first in one direction and then in the other; thus, there is no tendency for the transformer core to become permanently magnetized. Since little dc core saturation occurs, the effective inductance of the transformer, and therefore the efficiency, is relatively high.

The three-phase, full-wave rectifier produces across the load a pulsating (unfiltered) dc output voltage, E_{av} , as follows:

$$E_{av} = 2.34 E_{rms}$$

where: E_{rms} = rms voltage across one secondary winding of three-phase transformer


The *peak inverse voltage* across an individual rectifier in the three-phase, full-wave rectifier circuit during the period of time the tube is nonconducting is approximately 2.45 times the rms voltage across the secondary winding of one phase. Some pulsating dc voltage is always present across the load, and this voltage is in series with the applied ac secondary voltage; therefore, the sum of the instantaneous pulsation dc load voltage and the instantaneous peak secondary voltage represents the peak inverse voltage across the rectifier tube. The peak inverse voltage *per tube* can be expressed as:

$$E_{inv} \text{ (per tube)} = 2.45 E_{rms}$$

where: E_{rms} = rms voltage across one secondary winding of three-phase transformer

The output of the three-phase, full-wave rectifier circuit is connected to a suitable filter circuit to smooth the pulsating direct current for use in the load circuit. (Filter circuits are discussed in the Filter Section of this handbook.

A variation of the three-phase, full-wave rectifier circuit uses the common terminal of the wye-connected secondaries and rectifiers V4, V5, and V6 to form a three-phase, half-wave rectifier circuit. The circuit is fundamentally the same as that given earlier; for this reason the accompanying circuit schematic has been simplified and redrawn to eliminate the filament transformers and associated filament circuitry. The reference designations previously assigned remain unchanged.

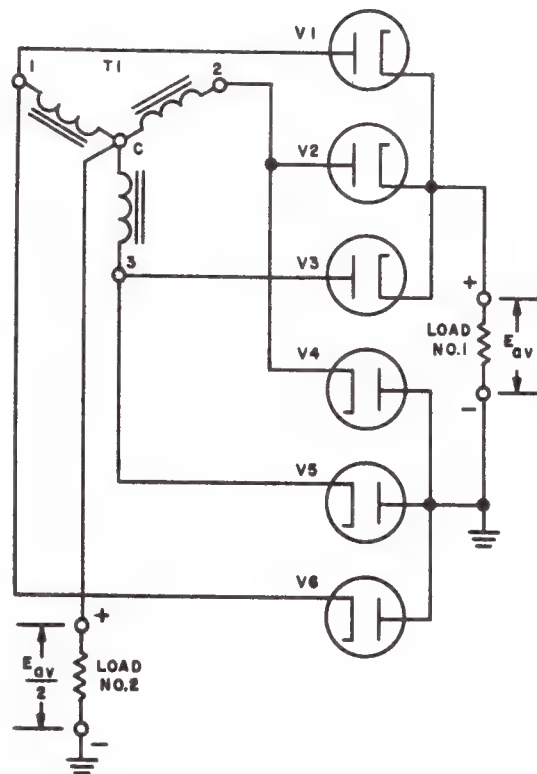


Simplified Three-Phase, Half-Wave and Three-Phase, Full-Wave Rectifier Circuit

One advantage of the circuit is that two voltages may be supplied from the same transformer and rectifier combination. One output voltage (E_{out}) is obtained from the full-wave circuit; the other voltage $E_{out}/2$, which is equal to one half of the full-wave output voltage, is obtained by using rectifiers V4, V5, and V6 and the common terminal of the wye-connected secondaries as a conventional three-phase, half-wave rectifier circuit. (The operation of the three-phase, half-wave rectifier circuit was previously described in this section.) Although this circuit variation can supply two output voltages simultaneously to two separate loads, there is a limitation on the total current which can be carried by the rectifiers (V4, V5, and V6).


Another variation of the three-phase, full-wave rectifier circuit uses a delta-connected secondary for T1. Each secondary winding is connected to the other in proper phase relationship so that the currents through the windings are balanced. Damage can result to the transformer windings if improperly connected; for this reason, the windings are usually connected internally in the proper phase to prevent the possibility of making wrong connections, and only the three secondary terminals are brought out of the case.

A schematic diagram showing this circuit variation is shown below.

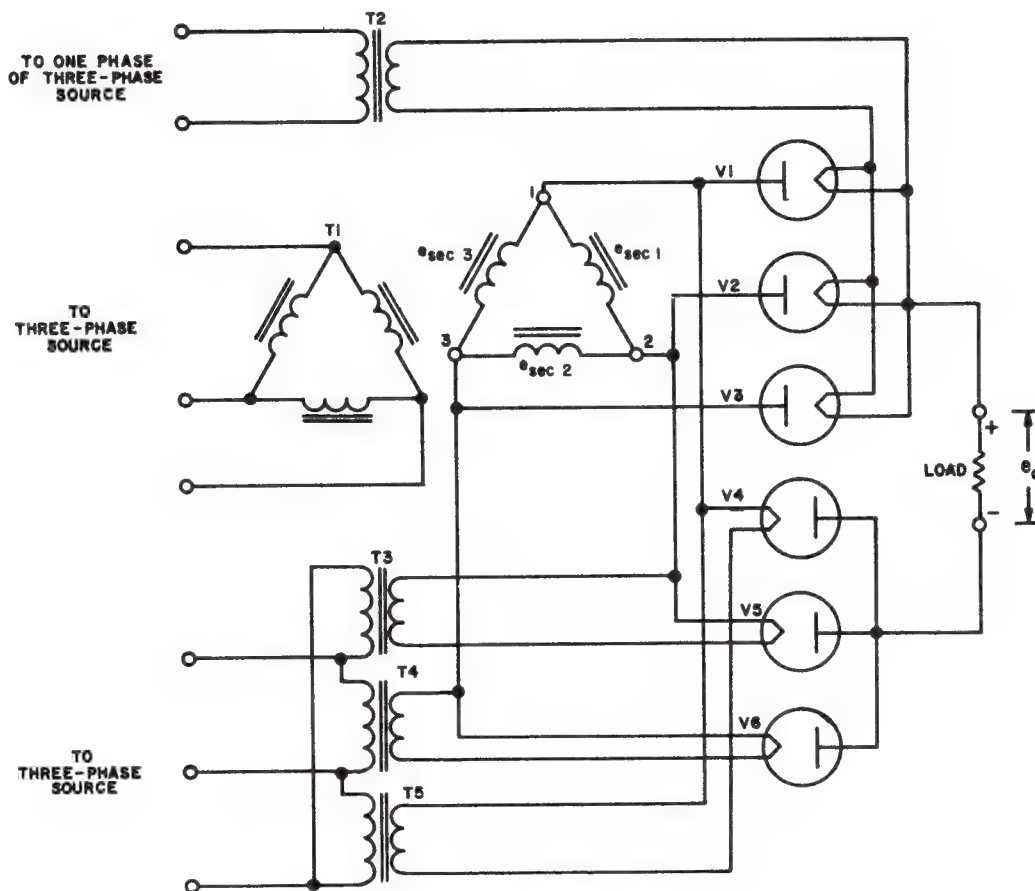The operation of the circuit can be easier understood from the simplified circuit schematics (parts A through F) and the waveforms given in the following illustrations.



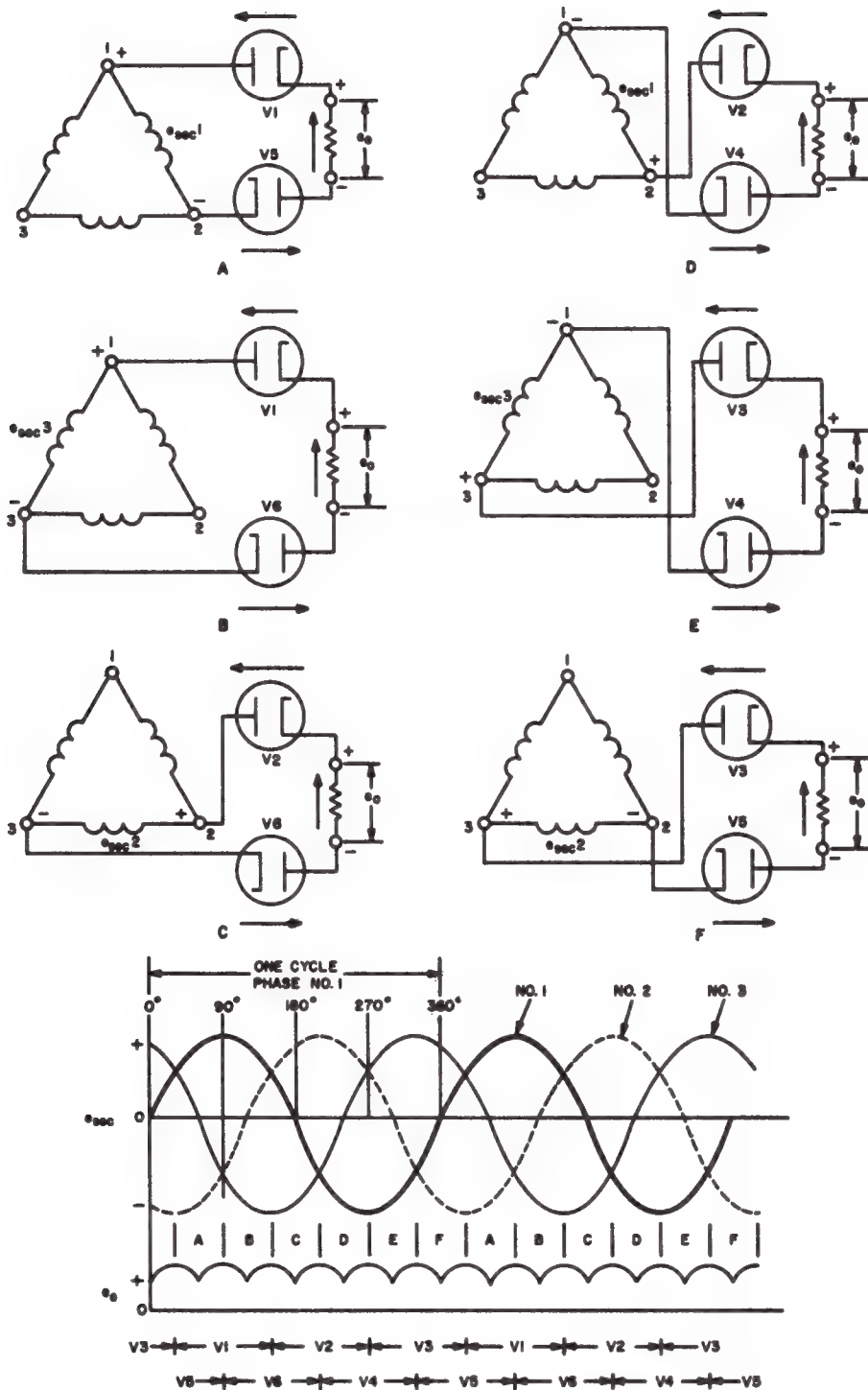Basic Three-Phase, Full-Wave (Delta Secondary)
Rectifier Circuit



Simplified Circuit Schematics and Waveforms for
Three-Phase, Full-Wave Rectifier

The operation of the delta-secondary rectifier circuit is similar to that of the wye-secondary rectifier circuit (previously described); however, the ac voltage across an individual delta-connected secondary winding is $0.742 E_{av}$, whereas the voltage across an individual wye-connected secondary winding is $0.428 E_{av}$ (E_{av} is the unfiltered ac output across the load). The voltages developed across the secondary windings of transformer T1 are 120 degrees out of phase with relation to each other and are constantly changing in polarity. In the delta-connected secondary, at any given instant the voltage in one phase is equal to the vector sum of the voltages in the other two phases. The polarities indicated for the secondary windings in the simplified circuit schematics (parts A through F) of the accompanying illustration represent the instantaneous polarity of the induced voltage in the secondary. Although the instantaneous polarity shown in the schematic is given for only one secondary winding, the sum of the instantaneous voltages in the other two windings is equal to the voltage of the first winding. The arrows on the schematics are used to indicate the directions of electron flow in the circuit.

The plates of rectifiers V1, V2, and V3 are connected to secondary terminals No. 1, No. 2, and No. 3, respectively; the filaments (cathode) of rectifiers V4, V5, and V6 are connected to secondary terminals No. 1, No. 2, and No. 3, respectively. When the plates of V1, V2, and V3 are positive with respect to their filaments, the tubes will conduct; when the filaments of V4, V5, and V6 are negative with respect to their plates, these tubes will conduct.

At any given instant of time in the three-phase, full-wave rectifier circuit, a rectifier, the load, and a second rectifier are in series across two terminals of the delta-connected secondaries and, therefore, two rectifiers are conducting. Each of the six rectifiers conducts for 120 degrees of an electrical cycle; however, there is an overlap of conduction periods, and the rectifiers conduct in a sequence which is determined by the phasing of the instantaneous secondary voltages of the power transformer. In the circuit described, two rectifiers are conducting at any instant of time, with the rectifier conduction periods occurring in the following order: V1 and V6, V6 and V2, V2 and V4, V4 and V3, V3 and V5, V5 and V1, V1 and V6, etc.

Refer to the secondary-voltage waveform, e_{sec} , shown in the accompanying illustration. Assume that

the ac voltage induced in secondary No. 1, transformer terminals No. 1 and No. 2, is approaching its maximum positive value (at 90 degrees); also, the voltage induced in secondary No. 2, transformer secondary terminals No. 2 and No. 3, has reached its maximum negative value (at 30 degrees) and is decreasing. (The voltage induced in secondary No. 3, terminals No. 1 and No. 3, is passing through zero.) This condition is shown by the simplified schematic of part A in the accompanying illustration. The plate of rectifier V1 is positive with respect to its filament (cathode), and the filament of rectifier V5 is negative with respect to its plate; therefore, both tubes conduct, and electrons flow through V5, the load, and V1 for 60 degrees of the electrical cycle.

In part B, the ac voltage induced in secondary No. 1 has reached its maximum positive value (at 90 degrees) and starts to decrease during the next 60 degrees of the cycle; the voltage induced in secondary No. 3 is approaching its maximum negative value. The plate of V1 remains positive with respect to its filament, and the filament of V6 becomes negative with respect to its plate; therefore, V1 continues to conduct and V6 takes over conduction from V5, with V1 and V6 conducting in series with the load. Electrons flow through V6, the load, and V1 for another 60 degrees of the cycle.

In part C, the ac voltage induced in secondary No. 3 has reached its maximum negative value and starts to decrease; the voltage induced in secondary No. 2 is approaching its maximum positive value. The filament of V6 remains negative with respect to its plate, and the plate of V2 becomes positive with respect to its filament; therefore, V6 continues to conduct and V2 takes over conduction from V1, with V2 and V6 conducting in series with the load. Electrons flow through V6, the load, and V2 for another 60 degrees of the cycle.

In part D, the ac voltage induced in secondary No. 2 has reached its maximum positive value and starts to decrease; the voltage induced in secondary No. 1 is approaching its maximum negative value. The plate of V2 remains positive with respect to its filament, and the filament of V4 becomes negative with respect to its plate; therefore, V2 continues to conduct and V4 takes over conduction from V6, with V2 and V4 conducting in series with the load. Electrons flow through V4, the load, and V2 for another 60 degrees of the cycle.

In part E, the dc voltage induced in secondary No. 3 approaches its maximum positive value, and the negative voltage in secondary No. 1 is decreasing. The filament of V4 remains negative with respect to its plate, and the plate of V3 becomes positive with respect to its filament; therefore, V4 continues to conduct and V3 takes over conduction from V2 with V3 and V4 conducting in series with the load. Electrons flow through V4, the load, and V3 for another 60 degrees of the cycle.

In part F, the ac voltage induced in secondary No. 2 approaches its maximum negative value, and the positive voltage in secondary No. 3 is decreasing. The plate of V3 remains positive with respect to its filament, and the filament of V5 becomes negative with respect to its plate; therefore, V3 continues to conduct and V5 takes over conduction from V4, with V3 and V5 conducting in series with the load. Electrons flow through V5, the load, and V3 for another 60 degrees of the cycle.

The cycle of operation is represented, as shown in part A, when the ac voltage induced in secondary No. 2 has reached its maximum negative value and the positive voltage in secondary No. 1 is increasing. The filament of V5 remains negative with respect to its plate, and the plate of V1 becomes positive with respect to its filament; therefore, V5 continues to conduct and V1 takes over conduction from V3, with V1 and V5 conducting in series with the load. Electrons flow through V5, the load, and V1, to initiate another complete cycle. The three-phase, full-wave rectifier with delta-connected secondaries produces across the load a pulsating (unfiltered) dc output voltage, E_{av} , as follows:

$$E_{av} = 1.35 E_{rms}$$

where: E_{rms} = rms voltage across one
secondary winding of
three-phase delta-
connected transformer

The *peak inverse voltage* across an individual rectifier in the three-phase, full-wave circuit during the period of time the tube is nonconducting is approximately 1.42 times the rms voltage across the secondary winding of one phase. Some pulsating dc voltage is always present across the load, and this voltage is in series with the applied ac secondary voltage; therefore, the sum of the instantaneous pulsating dc load voltage and the instantaneous peak to peak

secondary voltage represents the peak inverse voltage across the rectifier tube. The peak inverse voltage *per tube* can be expressed as:

$$E_{inv} \text{ (per tube)} = 1.42 E_{rms}$$

where: E_{rms} = rms voltage across one
secondary winding of
three-phase delta-
connected transformer

Failure Analysis

No Output. In the three-phase, full-wave rectifier circuit, the no-output condition is likely to be limited to the following possible causes: the lack of ac filament or filament-transformer primary supply voltage, the lack of applied ac high voltage, or a shorted load circuit (including shorted filter components).

A visual check of the glass-envelope rectifier tubes can easily be made to determine whether all filaments are lit. The filaments of V1, V2, and V3 should be observed first, because if these rectifiers are not lit there can be no dc output. If the filaments of V1, V2, and V3 are not lit, the filament voltage should be measured at the secondary of transformer T2 to determine whether it is present; if necessary, check the primary voltage of T2 to determine whether it is present and of the correct value. If none of the rectifier filaments are lit, the primary voltage source for the operation of transformers T2, T3, T4, and T5 should be checked for the presence of voltage.

With the primary voltage removed from the circuit, continuity (resistance) measurements should be made of the secondary and primary windings to determine whether one or more windings are open. Since the three windings of the delta-secondary circuit are sometimes connected internally and only three terminals are brought out of the case, voltage and resistance measurements are made between the terminals of the delta-connected secondaries. When making measurements (voltage or resistance) of the secondary circuit, it should be remembered that the windings form a delta configuration, with two windings in series and this combination in parallel with the winding under measurement. In other instances, the secondary windings are connected to six individual terminals, and these terminals are connected together to form a delta configuration. Thus, in this instance, the terminal connections may be removed to enable measurements to be made on individual secondary windings independent of other windings.

If necessary, the ac secondary voltage at each of the three high-voltage secondaries may be measured between the terminals of the delta-connected secondaries, to determine whether voltage is present and of the correct value. Also, if necessary, measure the applied three-phase primary voltage to determine whether it is present and of the correct value.

With primary voltage removed from the rectifier circuit, resistance measurements can be made at the output terminals of the rectifier circuit (across load) to determine whether the load circuit, including the filter, is shorted. A short in the components of the filter circuit or in the load circuit will cause an excessive load current to flow. If the rectifier tubes are of the high-vacuum type, the heavy load current will cause the plate of the rectifiers to become heated and emit a reddish glow when the plate dissipation is exceeded and, if allowed to continue, may result in permanent damage to the tubes. If gas-filled rectifiers are used in the circuit, excessive load current will result in permanent damage to the tubes because gas-filled rectifiers are very susceptible to damage from current overload. Therefore, once the difficulty in the load circuit has been located and corrected, the gas-filled rectifiers will require replacement as a result of the overload condition.

Low Output. The rectifier tubes should be checked to determine whether the filaments are lit. Because of the normal overlap in rectifier conduction periods and the conduction of tubes in series to obtain full-wave output, one or more defective rectifiers in the three-phase, full-wave rectifier circuit can cause the low-output condition. Failure of only one rectifier in the circuit will cause a loss of rectifier conduction and no delivery of current to the load for approximately 120 degrees of the electrical cycle, and the output voltage will be reduced accordingly. If rectifier tube V1, V2, or V3 is not lit, the trouble is obviously associated with the tube that is not lit since the filaments of these tubes are in parallel; however, if V4, V5, or V6 is not lit, then the trouble may be either the tube or its associated filament supply (T3, T4, or T5). The tube filament should be checked for continuity; the presence of correct filament voltage at the tube socket should be determined by measurement. If necessary, the primary and secondary voltages should be checked at the terminals of the filament transformer (T3, T4, or T5) to determine whether the transformer is defective.

With the three-phase primary voltage removed from the circuit, continuity measurements should be made of the primary (and secondary) windings, to determine whether one (or more) of the windings is open. In the case of the delta-connected secondary, refer to the paragraph above explaining the "no-output" condition for procedures to be used when making voltage and resistance measurements of the secondary windings. If necessary, the ac voltage of each secondary winding may be measured between the common terminal of the wye connection and the individual secondary terminal or the corresponding rectifier plate, to determine whether voltage is present and of the correct value. Also, if necessary, measure the applied three-phase primary voltage at each of the phases, to determine whether each voltage is present and of the correct value, since a low applied primary voltage can result in a low secondary voltage.

Shorted turns in either the primary or secondary windings will cause the secondary voltage to measure below normal. Disconnect all secondary leads from the transformer, T1, and measure the current in each leg of the three-phase primary with the transformer unloaded; excessive primary current is an indication of shorted turns. A secondary winding which is shorted to the core can cause a low output voltage indication; to determine whether a winding is shorted to the core, all leads should be disconnected from the transformer and a measurement made between each individual winding and the core, using an ohmmeter or a Megger (insulation tester).

Since a decrease in load resistance can cause an increase in load current and possibly result in a low-output condition, the rectifier-output current (to the filter circuit and to the load) should be checked to make sure that it is within tolerance and not excessive.

THREE-PHASE, FULL-WAVE (SINGLE "Y" SECONDARY) RECTIFIER (SEMICONDUCTOR)

Application.

Same application as electron tube version.

Characteristics.


Same characteristics as electron tube version except that it uses six semiconductor rectifiers (multiple or stacked units) instead of electron tubes, and it does not require filament transformers.

Circuit Analysis.

General. The three-phase, full-wave (single-wye secondary) rectifier is extensively used where a large amount of power is required by the load, such as for large shipboard or shore electronic installations. The rectifiers used in this circuit are generally forced-air-cooled or oil-cooled to dissipate heat developed during normal operation.

In many power-supply applications, it is desirable to provide two voltages simultaneously—one voltage for high-power stages and the other voltage for low-power stages. For these applications the three-phase, full-wave rectifier circuit can be modified to supply an additional output voltage, which is equal to one-half the voltage provided by the full-wave rectifier circuit.

Circuit Operation. The basic three-phase, full-wave rectifier circuit is illustrated in the accompanying circuit schematic. The circuit uses a conventional three-phase power transformer, T1, to step up the alternating source voltage to a high value in the wye-connected secondaries. The primary windings of T1 are shown delta-connected, although in some instances the primary windings may be wye-connected (as for a three-or four-wire system).

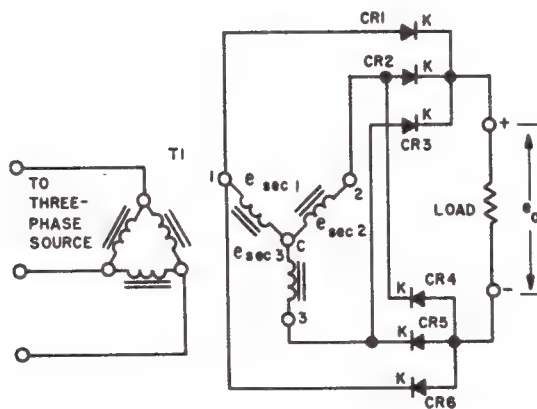

Basic Three-Phase, Full-Wave (Single "Y" Secondary) Rectifier Circuit

Semiconductor rectifiers CR1 and CR6 are connected to secondary terminal No. 1 of transformer T1; rectifiers CR2 and CR4 are connected to secondary terminal No. 2; rectifiers CR3 and CR5 are connected to secondary terminal No. 3. The rectifiers are

identical-type semiconductor rectifiers. Although the schematic shows only six individual rectifiers in the circuit, each graphic diode symbol represents two or more diodes in series to obtain the necessary peak-inverse characteristics for high-voltage operation.

The circuit arrangement shown in the illustration permits either terminal of the load to be placed at ground potential, depending upon whether a positive or negative dc output is desired; however, the circuit is commonly arranged for a positive dc output, with the negative output terminal at ground (chassis). Also, a choke-input filter system is commonly used with this circuit; therefore, series, or surge, resistors are not normally used.

The operation of the three-phase, full-wave rectifier circuit can be readily understood from a study of the equivalent electron-tube circuit description and the associated waveforms given previously in this section of the handbook. The reference designations used for semiconductor rectifiers CR1 through CR6 correspond directly to the reference designations used in the electron-tube circuit for rectifiers V1 through V6. Since the rectifier action which takes place in both circuits is the same, an explanation of circuit operation is not given here.


The voltages developed across the secondary windings of transformer T1 are 120 degrees out of phase with relation to each other, and are constantly changing in polarity. At any given instant of time in the three-phase, full-wave rectifier circuit, a rectifier, the load, and a second rectifier are in series across two of the wye-connected transformer secondaries. Each of the six rectifiers conducts for 120 degrees of an electrical cycle; however, there is an overlap of conduction periods, and the rectifiers conduct in a sequence which is determined by the phasing of the instantaneous secondary voltages. In the circuit given here (and in the electron-tube equivalent circuit), two rectifiers are conducting at any instant of time, with rectifier conduction occurring in the following order: CR1 and CR4, CR1 and CR5, CR2 and CR5, CR2 and CR6, CR3 and CR6, CR3 and CR4, CR1 and CR4, etc.

Each positive and negative peak in each of the three phases produces a current pulse in the load. Because of the nature of the rectifier conduction periods, each rectifier conducts for 120 degrees of the cycle, and carries one third of the total load current. The output voltage, e_o , produced across the load resistance is determined by the instantaneous currents

flowing through the load; therefore, the output voltage has a pulsating waveform, which results in a ripple voltage, because the output current and voltage are not continuous. The frequency of the ripple voltage is six times the frequency of the ac source. Since this ripple frequency is higher than the ripple frequency of a single-phase, full-wave rectifier circuit or a three-phase, half-wave rectifier circuit, relatively little filtering is required to smooth out the ripple and produce a steady dc voltage.

The peak inverse voltage across an individual rectifier (multiple or stacked units) in the three-phase, full-wave rectifier circuit during the period of time the rectifier is nonconducting is approximately 2.45 times the rms voltage across the secondary winding of one phase.

The regulation of the circuit is considered to be very good, and is better than that of a single-phase rectifier or of a three-phase, half-wave rectifier circuit having equivalent power-output rating. The output of the three-phase, full-wave rectifier circuit is connected to a suitable filter circuit to smooth the pulsating direct current for use in the load circuit. (Filter circuits are discussed in the Filter Section of this handbook.)

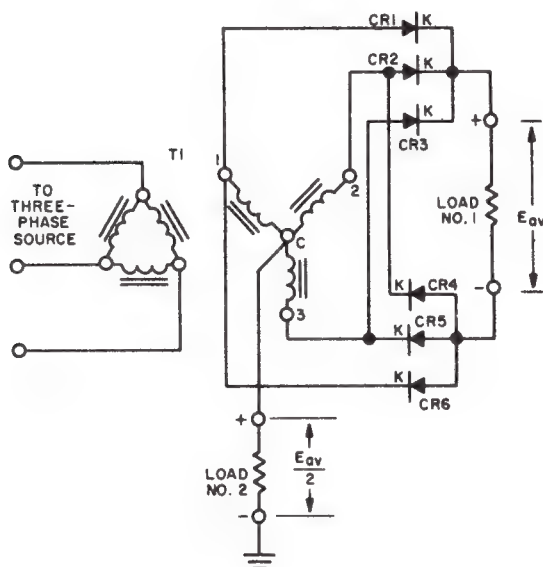


Three-Phase, Half-Wave and Three-Phase, Full-Wave Rectifier Circuit

A variation of the three-phase, full-wave rectifier circuit uses the common terminal of the wye-connected secondaries and rectifiers CR4, CR5, and CR6 to form a three-phase, half-wave rectifier circuit. The circuit is fundamentally the same as that discussed earlier; therefore, the reference designations previously assigned to the basic circuit remain unchanged.

One advantage of this circuit variation is that two voltages may be supplied from the same transformer and rectifier combination. One output voltage (E_{av}) is obtained from the full-wave circuit; the other voltage ($E_{av}/2$), which is equal to one-half the full-wave output voltage, is obtained by using rectifiers CR4, CR5, and CR6 and the common terminal of the wye-connected secondaries as a conventional three-phase, half-wave rectifier circuit. Although this circuit can supply two output voltages simultaneously to two separate loads, there is a limitation on the total current which can be safely carried by the rectifiers (CR4, CR5, and CR6).

Another variation of the three-phase, full-wave rectifier circuit uses a delta-connected secondary for T1. Each secondary winding is connected to the other in proper phase relationship so that the currents through the windings are balanced. Damage can result to the transformer windings if they are improperly connected; for this reason, the windings are usually connected internally in the proper phase to prevent the possibility of making wrong connections, and only three secondary terminals are brought out of the transformer case.

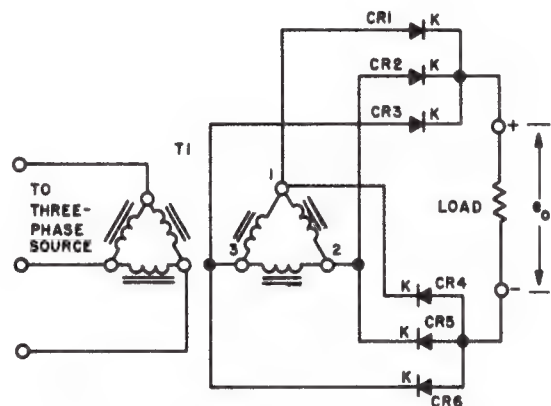

Basic Three-Phase, Full-Wave (Delta Secondary) Rectifier Circuit

The primary windings of transformer T1 are shown delta-connected, although in some instances they may be wye-connected (as for a three- or four-wire system).

Semiconductor rectifiers CR1 and CR4 are connected to secondary terminal No. 1 of transformer T1; rectifiers CR2 and CR5 are connected to secondary terminal No. 2; rectifiers CR3 and CR6 are connected to secondary terminal No. 3. The rectifiers are identical-type semiconductor rectifiers. Although the schematic shows only six individual rectifiers in the circuit, each graphic symbol represents two or more diodes in series to obtain the necessary peak-inverse characteristics for high-voltage operation.

The circuit arrangement shown in the illustration permits either terminal of the load to be placed at ground potential, depending upon whether a positive or negative dc output is desired; however, the circuit is commonly arranged for a positive dc output, with the negative output terminal at ground (chassis). Also, a choke-input filter system is commonly used with this circuit.

The operation of the three-phase, full-wave (delta secondary) rectifier circuit can be readily understood from a study of the equivalent electron-tube circuit description and the associated waveforms given previously in this section of the handbook. The reference designations used for semiconductor rectifiers CR1 through CR6 correspond directly to the reference designations used in the electron-tube circuit for rectifiers V1 through V6. Since the rectifier action which takes place in both circuits is the same, an explanation of circuit operation is not given here.

The operation of the delta-secondary rectifier circuit is similar to that of the wye-secondary rectifier circuit (previously described); however, the ac voltage across an individual delta-connected secondary winding is approximately 1.73 times greater than the voltage across an individual wye-connected secondary winding for equal dc output voltages from the two circuits. The voltages developed across the secondary windings of transformer T1 are 120 degrees out of phase with relation to one another, and are constantly changing in polarity. In the delta-connected secondary, at any given instant the voltage in one phase is equal to the vector sum of the voltages in the other two phases. At any given instant of time in the three-phase, full-wave rectifier circuit, a rectifier, the load, and a second rectifier are in series across two terminals of the delta-connected secondaries. Each of

the six rectifiers conducts for 120 degrees of an electrical cycle; however, there is an overlap of conduction periods, and the rectifiers conduct in a sequence which is determined by the phasing of the instantaneous secondary voltages of the power transformer. In the circuit given here (and in the electron-tube equivalent circuit), two rectifiers are conducting at any instant of time, with rectifier conduction occurring in the following order: CR1 and CR6, CR6 and CR2, CR2 and CR4, CR4 and CR3, CR3 and CR5, CR5 and CR1, CR1 and CR6, etc.

Each positive and negative peak in each of the three phases produces a current pulse in the load. Because of the nature of the rectifier conduction periods, each rectifier conducts for 120 degrees of the cycle, and carries one third of the total load current. The output voltage, e_o , produced across the load resistance is determined by the instantaneous current flowing through the load; therefore, the output voltage has a pulsating waveform, which results in a ripple voltage, because the output current and voltage are not continuous. The frequency of the ripple voltage is six times the frequency of the ac source. Since this ripple frequency is higher than the ripple frequency of a single-phase, full-wave rectifier circuit or a three-phase, half-wave rectifier circuit, relatively little filtering is required to smooth out the ripple and produce a steady dc voltage.

The peak inverse voltage across an individual rectifier (multiple or stacked units) in the three-phase, full-wave (delta secondary) rectifier circuit during the period of time the rectifier is nonconducting is approximately 1.42 times the rms voltage across the secondary winding of one phase.

The regulation of the circuit is considered to be very good, and is better than that of a single-phase rectifier or of a three-phase, half-wave rectifier circuit having equivalent power-output rating. The output of the three-phase, full-wave rectifier circuit is connected to a suitable filter circuit to smooth the pulsating direct current for use in the load circuit. (Filter circuits are discussed in the Filter Section of this handbook.)

Failure Analysis.

No Output. In the three-phase, full-wave rectifier circuit, the no-output condition is likely to be limited to one of three possible causes: the lack of applied ac voltage, a shorted load circuit (including shorted filter capacitors), or an open filter choke.

NOTE

Most filter circuits used in Navy equipment employ two-section choke-input filters; thus, an open choke in either section will cause no output.

Measure the applied three-phase primary voltage to determine whether it is present and of the correct value. With the primary voltage removed from the circuit, continuity measurements should be made of the secondary and primary windings, to determine whether one or more than one winding is open and whether the common terminal(s) of the wye-connected secondaries is connected to the load circuit. If necessary, the ac secondary voltage applied to the rectifiers may be measured between the common terminal(s) of the wye-connected secondaries and one or more rectifiers to determine whether voltage is present and of the correct value.

Since the three windings of the delta-secondary circuit are sometimes connected internally and only three terminals are brought out of the case, voltage and resistance measurements are made between the terminals of the delta-connected secondaries. When making measurements (voltage or resistance) of the secondary circuit, it should be remembered that the windings form a delta configuration, with two windings in series, and this combination in parallel with the winding under measurement. In other instances, the secondary windings are connected to six individual terminals, and these terminals are connected together to form a delta configuration. Thus, in this instance, the terminal connections may be removed to enable measurements to be made on individual secondary windings, independent of other windings. If necessary, the ac voltage at each of the three high-voltage secondaries may be measured between the terminals of the delta-connected secondaries, to determine whether voltage is present and of the correct value. Also, if necessary, measure the applied three-phase primary voltage to determine whether it is present and of the correct value.

With the primary voltage removed from the circuit, resistance measurements can be made at the output terminals of the rectifier circuit (across load) to determine whether the load circuit, including the filter, is shorted. (An open choke in the filter circuit will also cause no output. See note above.) A short in the load circuit (including components in the filter circuit) will cause an excessive load current to flow

and may result in permanent damage to the rectifiers. Therefore, once the difficulty in the load (including filter) circuit has been located and corrected, the rectifiers should be checked to determine whether they have been damaged as a result of the overload condition.

Low Output. Failure of only one rectifier to conduct will cause a loss of current delivered to the load for approximately 120 degrees of the electrical cycle, and the output voltage will be reduced accordingly. (Also, breakdown of a rectifier will cause a shorting effect upon the windings of the transformer and subject other rectifiers to overload.) Furthermore, when one rectifier fails to conduct, the ripple amplitude will increase. Therefore, each rectifier should be checked to determine whether the low output is due to normal rectifier aging, or to one or more defective rectifiers. A relative check of rectifier condition can be made by using an ohmmeter, as outlined in a previous paragraph of this section. A comparison can be made by checking one rectifier against each of the others to determine whether the rectifiers have similar characteristics. If the forward resistance of the rectifier increases, the output voltage will decrease. Also, if the reverse resistance decreases, the output voltage will decrease, and the amplitude of the ripple voltage will increase.

The load current should be checked to make sure that it is not excessive, because a decrease in output voltage can be caused by an increase in load current (decrease in load resistance); for example, excessive leakage in the capacitors of the filter circuit will result in increased load current. Also, the ac secondary voltage and the input (primary) voltage should be measured at the terminals of the transformer to determine whether these voltages are of the correct value. If necessary, and with the primary voltage removed from the circuit, continuity measurements should be made of the secondary and primary windings, to determine whether one (or more) of the windings is open. (Refer to the paragraph above for information concerning procedures to be used when making voltage and resistance measurements on delta-connected secondary windings.)

Shorted turns in either the primary or secondary windings will cause the secondary voltage to measure below normal. (A check for shorted turns is outlined in the failure analysis described for the electron-tube equivalent circuit given earlier in this section of the handbook.)

In the modified three-phase, half-wave and three-phase, full-wave rectifier circuit, it is possible to have two definite conditions of low voltage caused by one or more defective rectifiers; the output voltage (E_{av}) to load No. 1 can be low and the output voltage (E_{av})/2 to load No. 2 normal, or both output voltages can be below normal. If the load currents are not excessive and the filter components have been checked as satisfactory, the defective rectifier(s) in the first case is assumed to be CR1, CR2, or CR3, and in the second case, CR4, CR5, or CR6. When the modified circuit is used, rectifiers CR4, CR5, and CR6 will usually have higher current ratings than the other rectifiers (CR1, CR2, and CR3) because of the requirement to handle the combined currents of both output loads.

THREE-PHASE, HALF-WAVE (DOUBLE "Y" SECONDARY) RECTIFIER (ELECTRON TUBE)

Application.

The three-phase, half-wave rectifier with double-wye secondary and interphase reactor is used in electronic equipment for applications where the primary ac source is three-phase and the dc output power requirements are relatively high. The rectifier circuit can be arranged to furnish either negative or positive high-voltage output to the load.

Characteristics.

Input to circuit is three-phase ac; output is dc with amplitude of ripple voltage less than that for a single-phase rectifier.

Uses six high-vacuum or gas-filled electron-tube diodes as rectifiers.

Output requires very little filtering; dc output ripple frequency is equal to six times the primary line-voltage frequency.

Has good regulation characteristics.

Circuit provides either positive- or negative-polarity output voltage.

Requires only one filament-voltage supply.

Uses multiphase power transformer with two parallel sets of wye-connected secondaries operating 180 degrees out of phase with each other. The center points of the wye-connected secondaries are connected through an interphase reactor or balance coil to the load. The primary windings are generally delta-connected.

Circuit Analysis.

General. Fundamentally, this rectifier circuit resembles two half-wave (single-"y" secondary) recti-

fiers in parallel, each rectifier circuit operating from a common delta-connected primary, and sharing a common load through an interphase reactor or balance coi. (The three-phase, half-wave rectifier circuit was previously described in this section.) The three-phase, half-wave (double-wye secondary) rectifier circuit uses a power transformer with two sets of wye-connected secondaries, the windings of one set being connected 180 degrees out of phase with respect to the corresponding windings of the other set. For this reason, the circuit is sometimes referred to as a *six-phase* rectifier. The junction point of each wye-connected secondary is, in turn, connected to a center-tapped inductance, called an *interphase reactor* or *balance coil*. The center tap of the interphase reactor is the common negative terminal for the load.

Circuit Operation. The three-phase, half-wave (double-wye secondary) rectifier circuit is illustrated in the accompanying circuit schematic. The circuit used a three-phase power transformer, T1, to step up the alternating source voltage to a high value in the wye-connected secondaries. The primary windings of transformer T1 are shown delta-connected; the delta primary is common to both wye-connected secondaries. The plates of rectifiers V1, V2, and V3 are connected to one set of secondary ("A") windings at terminals 1A, 2A, and 3A, respectively. The plates of rectifiers V4, V5, and V6 are connected to the other set of secondary ("B") windings at terminals 3B, 1B, and 2B, respectively.

One filament transformer, T2, is used to supply the filament voltage to all rectifiers, since the filament of the rectifiers are all at the same potential. Although a single filament transformer is shown on the schematic, as many as three identical filament transformers are sometimes used as the filament supply, with each filament transformer supplying two (or more) rectifier tubes; in this case the primary of each single-phase filament transformer is connected to a different phase of the three-phase source. Voltage is applied to the primaries of the filament transformers before it is applied to the primary of the three-phase power transformer T1. A time-delay arrangement, either manually operated or automatic, normally permits the rectifier filaments to be preheated to the normal operating temperature before the high-voltage ac can be applied to the rectifier circuit.


The center-tapped inductance, L1, is an interphase reactor or balance coil. The common terminal of each wye-connected secondary is connected to one end of

L1; the center tap of the interphase reactor is connected to the load. Thus, the output-load current of each three-phase, half-wave rectifier circuit passes through one half of the interphase reactor, and these two currents are then combined in the load. For satisfactory operation, interphase reactor L1 must have sufficient inductance to maintain continuous current flow through each half of the coil. In effect, this reactor constitutes a choke-input filter arrangement, and exhibits the regulation characteristics of such a filter.

The circuit arrangement given in the illustration permits either terminal of the load to be placed at ground potential, depending upon whether a positive or negative dc output is desired; however, the circuit is commonly arranged for a positive dc output, with the negative output terminal at ground (chassis). The

circuit is typical of high-voltage dc supplies designed for use in large communication transmitters or other equipment for which the dc power requirement is several kilowatts or more.


The operation of the three-phase, half-wave (double-wye secondary) rectifier circuit can be understood by reference to the circuit schematic and the waveforms given in the accompanying illustration. The operation of each individual half-wave rectifier is the same as that given for the three-phase, half-wave (three-phase star) rectifier circuit previously described in this section. Although the voltages induced in the three transformer secondary windings differ in phase by 120 degrees, the voltages induced in corresponding windings of the two sets of wye-connected secondaries ("A" and "B") are 180 degrees out of phase with respect to each other.

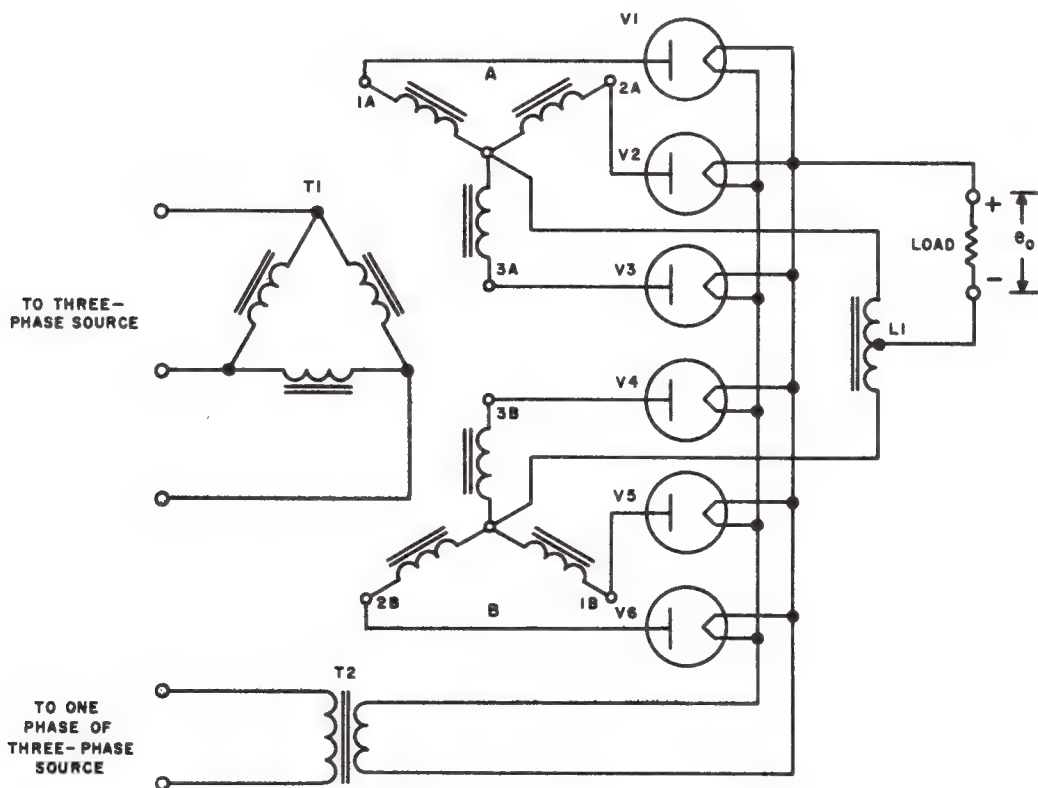

Basic Three-Phase, Half-Wave (Double "Y" Secondary)
Rectifier Circuit

The output resulting from the conduction of rectifiers V1, V2, and V3 in conjunction with secondary "A" is shown on the accompanying illustration; the output resulting from the conduction of rectifiers V4, V5, and V6 in conjunction with secondary "B", the resulting combined dc output voltage, e_o , and the corresponding rectifier conduction periods are also given.

At any instant of time, two rectifier tubes are conducting to deliver current to the load, but their currents are not in phase and an overlap in conduction periods of the six rectifiers occurs. Each rectifier conducts for 120 degrees of the input cycle and contributes one sixth of the total dc current supplied to the load. In the circuit described, two rectifiers are conducting at any instant of time, with the rectifier conduction periods occurring in the following order: V6 and V1, V1 and V4, V4 and V2, V2 and V5, V5 and V3, V3 and V6, V6 and V1, etc.

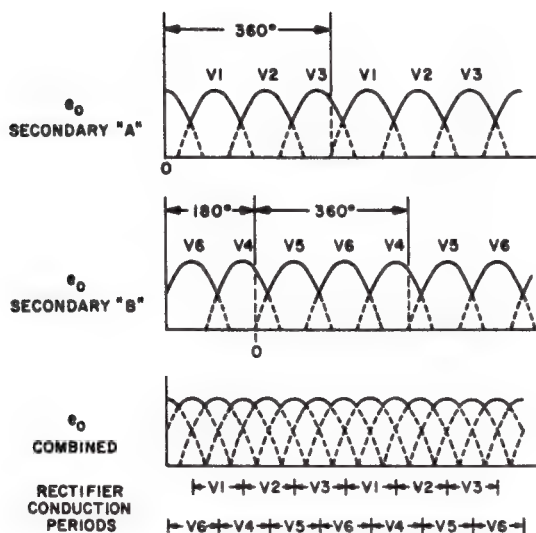

Waveforms for Three-Phase, Half-Wave
(Double "Y" Secondary)
Rectifier Circuit

The main component of the ripple frequency present across the interphase reactor is three times the frequency of the ac source. Electrons flow through the load in pulses, one pulse for each positive half cycle of the impressed voltage in each of the three phases of the two sets of secondaries. As men-

tioned previously, the secondaries are 180 degrees out of phase with respect to each other; therefore, the output voltage has a ripple frequency which is six times the frequency of the ac source. Since this ripple frequency is higher than that of a single-phase, full-wave rectifier circuit or a single three-phase, half-wave rectifier circuit, relatively little filtering is required to smooth out the ripple and produce a steady dc voltage.

In order to keep dc core saturation to a minimum (because of current flowing in one direction only in each secondary winding) and to keep the efficiency relatively high, it is necessary to use a single three-phase transformer with multiple secondaries, rather than six individual single-phase transformers.

The three-phase, half-wave (double-wye secondary) rectifier circuit produces across the load a pulsating (unfiltered) dc output voltage, E_{av} , as follows:

$$E_{av} = 1.17 E_{rms}$$

where: E_{rms} = rms voltage across one secondary winding of the three-phase transformer

The *peak inverse voltage* across an individual rectifier in the three-phase, half-wave rectifier circuit during the period of time the tube is nonconducting is approximately 2.45 times the rms voltage across the secondary winding of one phase. The peak inverse voltage *per tube* can be expressed as:

$$E_{inv} \text{ (per tube)} = 2.45 E_{rms}$$

where: E_{rms} = rms voltage across one secondary winding of the three-phase transformer

The output of the three-phase, half-wave (double-wye secondary) rectifier is connected to a suitable filter circuit, to smooth the pulsating direct current for use in the load circuit. (Filter circuits are discussed in the latter part of this section.)

A variation of the three-phase, half-wave (double-wye secondary) rectifier circuit omits the use of an interphase reactor or balance coil. If the interphase reactor (L1) is not used in the circuit and the common terminal of each wye-connected secondary is connected to the negative terminal of the load, the circuit is classified as a *six-phase star*. However, the six-phase star, half-wave rectifier circuit is considered less desirable than the three-phase, half-wave (double-wye secondary) rectifier circuit, because it

requires the use of tubes with higher peak current ratings and a transformer with a higher KVA rating to obtain an equivalent dc output. Therefore, the circuit is seldom used.

Failure Analysis.

No Output. In the three-phase, half-wave (double-ye secondary) rectifier circuit, the no-output condition is likely to be limited to the following possible causes: the lack of ac filament or filament-transformer primary supply voltage, the lack of applied ac high voltage, or a shorted load circuit (including shorted filter components).

A visual check of the glass-envelope rectifier tubes can easily be made to determine whether the filaments are lit; if they are not lit, there can be no dc output. The filament voltage should be measured at the secondary terminals of transformer T2 to determine whether it is present; if necessary, check the primary voltage to T2 to determine whether it is present and of the correct value. When the circuit employs more than one filament transformer (for example, three transformers each operating from one phase of the three-phase source), if none of the rectifier filaments are lit the primary voltage source for the filament transformers should be checked for the presence of voltage.

With the primary voltage removed from the circuit, continuity (resistance) measurements should be made of the secondary and primary windings, to determine whether one or more windings are open and whether the common terminals of the wye-connected secondaries are connected to the load circuit through the interphase reactor or balance coil. If necessary, the secondary voltage may be measured at one (or more) of the high-voltage secondaries between the common terminal of the wye-connected secondaries and a secondary terminal or corresponding rectifier plate, to determine whether voltage is present and of the correct value. Also, if necessary, measure the applied three-phase primary voltage to determine whether it is present and of the correct value.

With primary voltage removed from the rectifier circuit, resistance measurements can be made at the output terminals of the rectifier circuit (across load) to determine whether the load circuit, including the filter, is shorted. A short in the components of the filter circuit or in the load circuit will cause an excessive load current to flow, and the full output voltage will be developed across each half of the interphase reactor, L1. If the rectifier tubes are of the high-

vacuum type, the heavy load current will cause the plates of the rectifiers to become heated and emit a reddish glow when the plate dissipation is exceeded and, if allowed to continue, may result in permanent damage to the tubes. If gas-filled rectifiers are used in the circuit, excessive load current will result in permanent damage to the tubes because gas-filled rectifiers are very susceptible to damage from current overload. Therefore, once the difficulty in the load circuit has been located and corrected, the gas-filled rectifiers will require replacement as a result of the overload condition.

Low Output. The rectifier tubes should be checked to determine whether all filaments are lit; however, because of the normal overlap in rectifier conduction periods, the failure of one or two rectifiers in the circuit will not greatly affect the output voltage but may increase the ripple amplitude. If only one rectifier is not lit, the tube filament should be checked for continuity. If the circuit employs more than one filament transformer and one or more tubes are not lit, the corresponding filament transformer(s) should be checked. Measure the secondary voltage to determine whether the correct filament voltage is present; the primary voltage should be measured at the transformer terminals, to determine whether voltage is applied and of the correct value. If necessary, continuity measurements of the transformer windings should be made to determine whether the transformer is defective.

The continuity of each half of the interphase reactor, L1, should be measured to determine whether one half of the winding is open. An open circuit in one half of this reactor will disconnect its associated three-phase, wye-connected secondary; the output voltage will decrease as a result, and the rectifier circuit will continue to operate as a three-phase, half-wave rectifier with single-ye secondary.

With the three-phase primary voltage removed from the circuit, continuity measurements should be made of the primary (and secondary) windings, to determine whether one (or more) of the windings is open. If necessary, the ac voltage of each secondary winding in each set of secondaries may be measured between the common terminal of the wye connection and the individual secondary terminal or the corresponding rectifier plate, to determine whether voltage is present and of the correct value. Also, if necessary, measure the applied three-phase primary voltage at each phase, to determine whether voltage is present

and of the correct value, since a low applied primary voltage can result in a low secondary voltage.

Shorted turns in either the primary or secondary windings will cause the secondary voltage to measure below normal. Disconnect all secondary leads from the transformer, and measure the current in each leg of the three-phase primary with the transformer unloaded; excessive primary current is an indication of shorted turns. A secondary winding which is shorted to the core can also cause a low output voltage indication; to determine whether a winding is shorted to the core, all leads should be disconnected from the transformer and a measurement made between each winding and the core, using an ohmmeter or a Megger (insulation tester).

Since a decrease in load resistance can cause an increase in load current and possible result in a low-output condition, the rectifier-output current (to the filter circuit and to the load) should be checked, to make sure that it is within tolerance and is not excessive.

THREE-PHASE, HALF-WAVE (DOUBLE "Y" SECONDARY) RECTIFIER (SEMICONDUCTOR)

Application.

Same as electron tube version.

Characteristics.


Same characteristics as electron tube version, except that it uses six semiconductor rectifiers (multiple or stacked units) instead of electron tubes, and therefore does not require a filament voltage supply.

Circuit Analysis.

General. Fundamentally, this rectifier circuit resembles two half-wave (single "Y" secondary) rectifiers in parallel, each rectifier circuit operating from a common delta-connected primary, and sharing a common load through an interphase reactor or balance coil. (The three-phase, half-wave rectifier circuit was previously described in this section.) The three-phase, half-wave (double-wye secondary) rectifier circuit uses a power transformer with two sets of wye-connected secondaries, the winding of one set being connected 180 degrees out of phase with respect to the corresponding windings of the other set. For this reason, the circuit is sometimes referred to as a *six-phase, half-wave* or a *delta-double-wye-with valance*

coil rectifier circuit. The junction point of each wye-connected secondary is, in turn, connected to a center-tapped inductance, called an *Interphase reactor* or *balance coil*. The center tap of the interphase reactor is the common output terminal for the load.

Circuit Operation. The three-phase, half-wave (double-wye secondary) rectifier circuit is illustrated in the accompanying schematic. The circuit uses a three-phase power transformer, T1, to step up the alternating source voltage to a high value in the wye-connected secondaries. The primary windings of the transformer are shown delta-connected; the delta primary is common to both wye-connected secondaries.

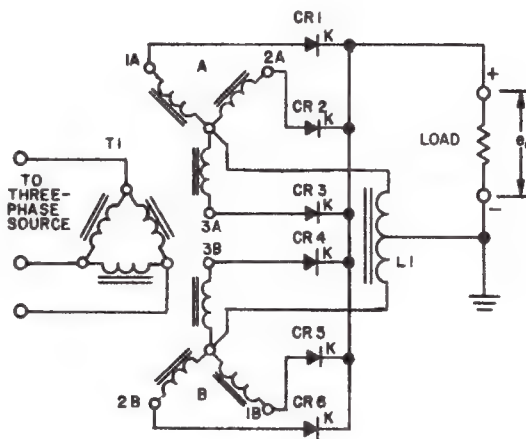

Basic Three-Phase, Half-Wave (Double "Y" Secondary) Rectifier Circuit

Semiconductor rectifiers CR1, CR2, and CR3 are connected to secondary terminals 1A, 2A, and 3A, respectively. Rectifiers CR4, CR5, and CR6 are connected to secondary terminals 3B, 1B, and 2B, respectively. The rectifiers are identical-type semiconductor rectifiers. Although the schematic shows only six individual rectifiers in the circuit, each graphic symbol represents two or more diodes in series to obtain the necessary peak-inverse characteristics for high-voltage operation.

The center-tapped inductance, L1, is an interphase reactor or balance coil. The common terminal of each wye-connected secondary is connected to one end of L1; the center tap of the interphase reactor is connected to the load. Thus, the output-load current of each three-phase, half-wave rectifier circuit passes through one half of the interphase reactor, and these

two currents are then combined in the load. For satisfactory operation, interphase reactor L1 must have sufficient inductance to maintain continuous current flow through each half of the coil. In effect, this reactor constitutes a choke-input filter arrangement, and exhibits the regulation characteristics of such a filter.

The circuit arrangement shown in the illustration permits either terminal of the load to be placed at ground potential, depending upon whether a positive or negative dc output is desired; however, the circuit is commonly arranged for a positive dc output, with the negative output terminal at ground (chassis). It is good design practice for the dc output terminal associated with the center tap of the inductance, L1, to be grounded; therefore, the secondary-to-core insulation of transformer T1 need not be as great as it would be if the secondary windings were above ground by the amount of the ac output voltage. When a negative high-voltage dc supply is required, it is common practice to keep the center tap of inductor L1 at ground (chassis) potential and to reverse the rectifiers (CR1 through CR6); thus, the output polarity across the load will be opposite that shown in the schematic.

The operation of the three-phase, half-wave (double-wye secondary) rectifier circuit can be readily understood from a study of the equivalent electron-tube circuit description and the associated waveforms given previously in this section of the handbook. The reference designations used for semiconductor rectifiers CR1 through CR6 correspond directly to the reference designations used in the electron-tube circuit for rectifiers V1 through V6. Since the rectifier action which takes place in both circuits is the same, as explanation of circuit operation is not given here.

The operation of each half-wave rectifier circuit associated with a three-phase secondary ("A" or "B") is the same as that given for the three-phase, half-wave (single "Y" secondary) rectifier circuit previously described in this section. Although the voltages induced in the three secondary windings differ in phase by 120 degrees, the voltages induced in corresponding windings of the two sets of wye-connected secondaries ("A" and "B") are 180 degrees out of phase with respect to each other.

At any instant of time, two rectifiers are conducting to deliver current to the load, but their cur-

rents are not in phase and an overlap in conduction periods of the six rectifiers occurs. Each rectifier conducts for 120 degrees of the input cycle and contributes one sixth of the total current supplied to the load. In this circuit, two rectifiers are conducting at any instant of time, with the rectifier conduction periods occurring in the following order: CR1 and CR4, CR4 and CR2, CR2 and CR5, CR5 and CR3, CR3 and CR6, CR6 and CR1, CR1 and CR4, etc.

The main component of the ripple frequency present across the interphase reactor (L1) is three times the frequency of the ac source. Electrons flow through the load in pulses, one pulse for each positive half-cycle of the impressed voltage in each of the three phases of the two sets of secondaries. As mentioned previously, the secondaries are 180 degrees out of phase with respect to each other; therefore, the output voltage has a ripple frequency which is six times the frequency of the ac source. Since this ripple frequency is higher than that of a single-phase, full-wave rectifier circuit or a three-phase, half-wave (three-phase star) rectifier circuit, relatively little filtering is required to smooth out the ripple and produce a steady dc voltage.

The peak inverse voltage across a rectifier (multiple or stacked units) in a secondary leg of the three-phase, half-wave (double-wye secondary) rectifier circuit during the period of time the rectifier is non-conducting is approximately 2.45 times the rms voltage across the secondary winding of one phase.

The regulation of the circuit is considered to be very good, and is better than that of a single-phase rectifier or a three-phase, half-wave (single "Y" secondary) rectifier circuit having equivalent power-output rating. The output of the three-phase, half-wave (double-wye secondary) rectifier circuit is connected to a suitable filter circuit to smooth the pulsating direct current for use in the load circuit. (Filter circuits are discussed in the Filter Section of this handbook.)

Failure Analysis.

No Output. In the three-phase, half-wave (double-wye secondary) rectifier circuit, the no-output condition is likely to be limited to one of three possible causes: the lack of applied ac voltage, a shorted load circuit (including shorted filter capacitors), or an open input choke.

NOTE

Most filter circuits used in Navy equipment employ two-section choke-input filters; thus, an open choke in either section will cause no output.

With the primary voltage removed from the circuit, continuity measurements should be made of the secondary and primary windings, to determine whether one or more than one winding is open, and whether the common terminals of the wye-connected secondaries are connected to the load circuit through the interphase reactor or balance coil. If necessary, the ac secondary voltage may be measured at one (or more) of the high-voltage secondaries (between the common terminal of the wye-connected secondaries and one or more rectifiers), to determine whether voltage is present and of the correct value. Also, if necessary, measure the applied three-phase primary voltage to determine whether it is present and of the correct value.

With primary voltage removed from the rectifier circuit, resistance measurements can be made at the output terminals of the rectifier circuit (across load) to determine whether the load circuit, including the filter, is shorted. A short in the components of the load circuit (including filter circuit) will cause an excessive load current to flow, and considerable output voltage will be developed across each half of the interphase reactor, L1. If an open should develop in both halves or in the center-tap lead of the interphase reactor, no output will be developed. Likewise, an open choke in the filter circuit will cause no output. (See note above.) An excessive load current caused by shorted components in the circuit may result in permanent damage to the rectifiers. Therefore, once the difficulty in the load (including filter) circuit has been located and corrected, the rectifiers should be checked to determine whether they have been damaged as a result of the overload condition.

Low Output. An open circuit in one half of the interphase reactor will disconnect its associated three-phase, wye-connected secondary; the output voltage will decrease as a result, and the rectifier circuit will continue to operate as a three-phase, half-

wave rectifier with single-wye secondary. Therefore, the continuity of each half of the interphase reactor (L1) should be checked to determine whether one half of the winding is open.

With the three-phase primary voltage removed from the circuit, continuity measurements should be made of the primary and secondary windings, to determine whether one (or more) of the windings is open. If necessary, the ac voltage of each secondary winding in each set of secondaries may be measured between the common terminal of the wye connection and the individual secondary terminal of the corresponding rectifier, to determine whether voltage is present and of the correct value. Also, if necessary, measure the applied three-phase primary voltage at each phase, to determine whether voltage is present and of the correct value, since a low applied primary voltage can result in a low secondary voltage.

Shorted turns in either the primary or secondary windings will cause the secondary voltage to measure below normal. (A check for shorted turns is outlined in the failure analysis described for the electron-tube equivalent circuit given earlier in this section of the handbook.)

The load current should be checked to make sure that it is not excessive, because a decrease in output voltage can be caused by an increase in load current (decrease in load resistance); for example, excessive leakage in the capacitors of the filter circuit will result in increased load current.

Failure of a rectifier to conduct will cause a loss of current delivered to the load, and the output voltage will be reduced accordingly. Therefore, each rectifier should be checked to determine whether the low output is due to normal rectifier aging, or to one or more defective rectifiers. A relative check of rectifier condition can be made by using an ohmmeter, as outlined in a previous paragraph of this section. A comparison can be made by checking one rectifier against each of the others to determine whether the rectifiers have similar characteristics. If the forward resistance of the rectifier increases, the output voltage will decrease. Also, if the reverse resistance decreases, the output voltage will decrease and the amplitude of the ripple voltage will also increase.

PART 2-3. VOLTAGE MULTIPLIERS

HALF-WAVE VOLTAGE DOUBLER (ELECTRON TUBE)

Application.

The half-wave voltage-doubler circuit is used to produce a higher dc output voltage than can be obtained from a conventional half-wave rectifier circuit. This voltage doubler is normally used in "transformerless" circuits where the load current is small and voltage regulation is not critical. The circuit is frequently employed as the power supply in small portable receivers and audio amplifiers and, in some transmitter applications, as a bias supply.

Characteristics.

Input to circuit is ac; output is pulsating dc.

DC output voltage is approximately twice that obtained from equivalent half-wave rectifier circuit; output current is relatively small.

Output requires filtering; dc output ripple frequency is equal to ac source frequency.

Has poor regulation characteristics; output voltage available is a function of load current.

Depending upon circuit applications, may be used with or without a power isolation transformer.


Uses indirectly heated cathode-type rectifiers.

Circuit Analysis.

General. The half-wave voltage doubler circuit is used with or without a transformer to obtain a dc voltage from an ac source. As the term *voltage doubler* implies, the output voltage is approximately twice the input voltage. The half-wave voltage doubler derives its name from the fact that the output charging capacitor (C2) across the load receives a charge once for each complete cycle of the applied voltage. The half-wave voltage doubler is sometimes called a *cascade* voltage doubler. The voltage regulation of the circuit is poor and, therefore, its use is generally restricted to applications in which the load current is small and relatively constant.

Circuit Operation. In the accompanying circuit schematics, parts A, B, and C illustrate basic half-wave voltage-doubler circuits. The circuit shown in part A uses a transformer, T1, which can be either a step-up transformer to obtain a high value of voltage in the secondary circuit, or an isolation transformer to permit either dc output terminal to be placed at

ground (chassis) potential. The circuits shown in parts B and C do not use a transformer, and operate directly from the ac source. In the circuit illustrated in part A, either output terminal may be placed at ground (chassis) potential. The circuit illustrated in part B places one side of the ac source at a negative dc potential, and thus restricts the circuit to use as a positive dc supply. The negative dc supply variation of this circuit is illustrated in part C.

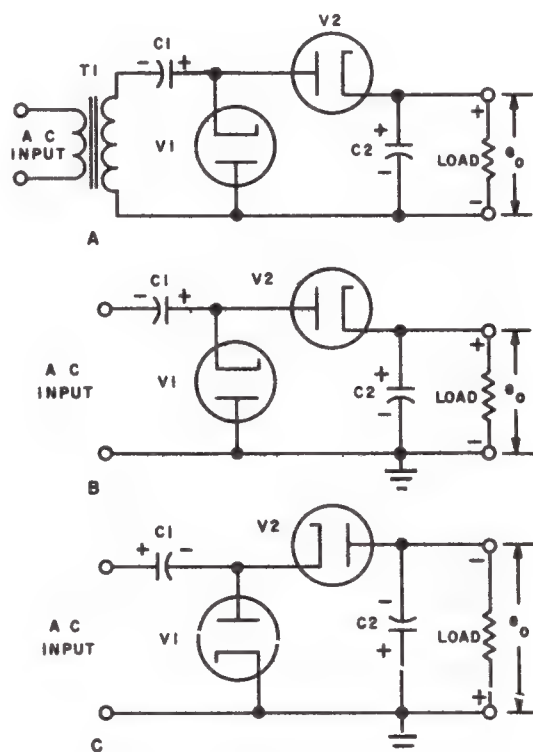


Basic Half-Wave Voltage-Doubler Circuits

The rectifiers, V1 and V2, are of the indirectly heated cathode type, and are identical-type diodes. Although the circuit schematic illustrates two separate rectifiers, a twin-diode is generally used in the circuit. Typical twin-diode electron tubes designed specifically for use in voltage-doubler circuits are: 25Z6, 50Y6, and 117Z6. As indicated by the tube-type numbers, these tubes require nominal filament-supply voltages of 25, 50, and 117 volts, respectively. Because there are several possible circuit combinations, the actual filament circuits for V1 and V2 are

not shown on the circuit schematics. The filament voltage for the rectifiers is usually obtained directly from the ac source if the filament is rated at the source voltage, by use of a voltage-dropping resistance in series with the rectifier filament (s) to reduce the ac source voltage to the correct value, or from a transformer secondary winding of the correct value. In some equipments, the filaments of other tubes within the equipment are connected in series (or series-parallel), and this combination is then placed in series with the rectifier filament (s) across the ac source; when this is done, a voltage-dropping resistor may be required.

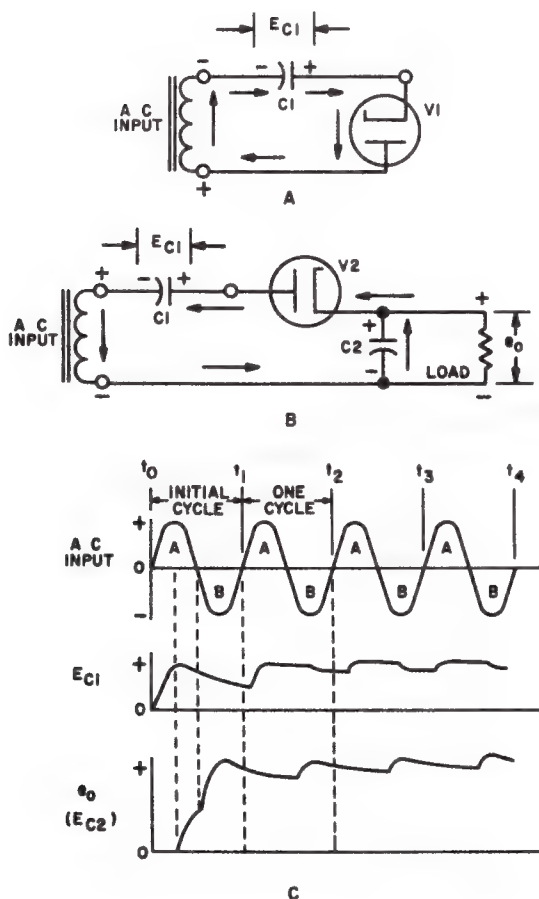In the three circuits illustrated, the functions of rectifiers V1 and V2, and of charging capacitors C1 and C2, are the same for each of the circuits.



Typical Half-Wave Voltage-Doubler Circuit
Operation and Waveforms

The operation of a half-wave voltage doubler circuit can be understood from the simplified circuits, parts A and B, and the waveforms, part C, shown in the following illustration.

Assume that the ac input to the voltage doubler during the initial half-cycle is of the polarity indicated in part A of the illustration. Electrons flow in the direction indicated by the small arrows from the positive plate of charging capacitor C1, through rectifier tube V1 (cathode to plate), and to the dc source. The left-hand (negative) plate of capacitor C1 now has a surplus of electrons, while the right-hand (positive) plate lacks electrons. Thus, during initial half-cycle, capacitor C1 assumes a charge (E_{C1}) of the polarity indicated, which is equal to approximately the peak value of the applied ac voltage.

During the next half-cycle the polarity of the applied ac input to the voltage doubler is as indicated in part B of the illustration. The charge (E_{C1}) existing across capacitor C1 is in series with the applied ac and will therefore add its potential to the peak value of the input voltage. Electrons flow in the direction indicated by the small arrows from the positive plate of capacitor C2, through rectifier tube V2 (cathode to plate), and to the positive plate of capacitor C1. Thus, during the second half-cycle capacitor C2 assumes a charge (E_{C2}) of the polarity indicated which is equal to the peak value of the applied ac voltage plus the value of the charge (E_{C1}) existing across charging capacitor C1. Thus the value of the voltage (E_{C2}) across capacitor C2 is equal to approximately twice the peak voltage of the applied ac, provided that charging capacitor C1 does not lose any initial charge.

In a practical circuit, the values of capacitors C1 and C2 are at least $16 \mu\text{f}$; therefore, with such a large value of capacitance in the circuit and because there is always some resistance (rectifier-tube plate resistance and ac source impedance) in the circuit, each capacitor may not immediately attain its maximum charge until several input cycles have occurred. Capacitor C2 is charged only on alternate half-cycles of the applied ac voltage, and is always attempting to discharge through the load resistance; therefore, the resulting waveform of the output voltage, e_o (or E_{C2}), varies as shown in part C of the illustration.

The output waveform contains some ripple voltage; therefore, additional filtering is required to obtain a steady dc voltage. The frequency of the main component of the ripple voltage is the same as the

frequency of the ac source, because capacitor C2 is charged only once for each complete input cycle. The regulation of the voltage-doubler circuit is relatively poor; the value of output voltage obtained is determined largely by the resistance of the load and the resulting load current, since the load (and the filter circuit, if used) is in parallel with capacitor C2.

Failure Analysis.

No Output. In the half-wave voltage-doubler circuit, the no-output condition is likely to be limited to one of several possible causes: the lack of filament voltage or an open filament in the rectifier (s), the lack of applied ac voltage, a shorted load circuit (including capacitor C2 and filter circuit components), or an open capacitor C1.

A visual check of a glass-envelope rectifier tube can be made to determine whether the filament (s) is lit; if the filament is not lit, it may be open or the filament voltage may not be applied. The tube filament should be checked for continuity; also, the presence of voltage at the tube socket should be determined by measurement.

The ac supply voltage should be measured at the input of the circuit to determine whether the voltage is present and is the correct value. If the circuit uses a step-up or isolation transformer (T1) measure the voltage at the secondary terminals to determine whether it is present and is the correct value. With the primary voltage removed from the transformer, continuity measurements of the primary and secondary windings should be made to determine whether one of the windings is open, since an open circuit in either winding will cause a lack of secondary voltage.

With the ac supply voltage removed from the input to the circuit and with the load disconnected from capacitor C2, resistance measurements can be made across the terminals of capacitor C2 and at the output terminals of the circuit (across load). These measurements will determine whether the capacitor (C2) or the load circuit (including filter components) is shorted. Because capacitor C2 and the filter-circuit capacitors are usually electrolytic capacitors, the resistance measurements may vary, depending upon the test-lead polarity of the ohmmeter. Therefore, two measurements must be made, with the test leads reversed at the circuit test points for one of the measurements, to determine the larger of the two resistance measurements. The larger resistance value is then

accepted as the measured value. Capacitor C1 may be checked in a similar manner.

Low Output. The rectifiers (V1 and V2) should be checked to determine whether the cause of low output is low cathode emission. The load current should be checked to make sure that it is not excessive, because the voltage-doubler circuit has poor regulation and an increase in load current (decrease in load resistance) can cause a decrease in output voltage.

One terminal of each capacitor, C1 and C2, should be disconnected from the circuit and each capacitor checked, using a capacitance analyzer, to determine the effective capacitance and leakage resistance of each capacitor. A decrease in effective capacitance or losses within either capacitor can cause the output of the voltage-doubler circuit to be below normal, since the defective capacitor will not charge to its normal operating value. If a suitable capacitance analyzer is not available, an indication of leakage resistance can be obtained by using an ohmmeter; the measurements are made with one terminal of the capacitor disconnected from the circuit and, using the ohmmeter procedure outlined in the previous paragraph, two measurements are made (with the test leads reversed at the capacitor terminals for one of the measurements). The larger of the two measurements should be greater than 1 megohm for a satisfactory capacitor.

HALF-WAVE VOLTAGE DOUBLER (SEMICONDUCTOR)

Application.

Same application as electron tube version.

Characteristics.


Same characteristics as electron tube version except that it uses two semiconductor rectifiers (single, multiple, or stacked units) instead of electron tubes.

Circuit Analysis.

General. The half-wave voltage-doubler circuit is used with or without a transformer to obtain a dc voltage from an ac source. As the term *voltage doubler* implies, the output voltage is approximately twice the input voltage. The half-wave voltage doubler derives its name from the fact that the output charging capacity (C2) across the load receives a

charge once for each complete cycle of the applied voltage. The half-wave voltage doubler is sometimes called a *cascade* voltage doubler. The voltage regulation of the circuit is poor, and, therefore, its use is generally restricted to applications in which the load current is small and relatively constant.

Circuit Operation. In the accompanying circuit schematics, parts A, B, and C illustrate basic half-wave voltage doubler circuits. The circuit shown in part A uses a transformer, T1, which can be either a step-up transformer to obtain a high value of voltage in the secondary circuit, or an isolation transformer. The circuits shown in parts B and C do not use a transformer, and operate directly from the ac source. In the circuit illustrated in part A, the use of transformer T1 permits either output terminal to be placed at ground (chassis) potential. The circuit illustrated in part B places one side of the ac source at a negative dc potential, and thus restricts the circuit to use as a positive dc supply. A variation of this circuit is illustrated in part C; this variation provides a negative output voltage.

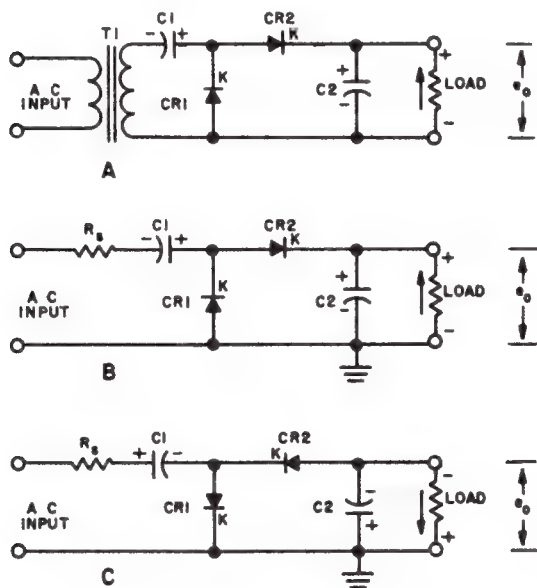

Basic Half-Wave Voltage-Doubler Circuits

The rectifiers, CR1 and CR2, are identical-type semiconductor diodes. In the three circuits illustrated, the functions of rectifiers CR1 and CR2, and of charging capacitors C1 and C2, are the same for

each of the circuits. Electrons flow through the load in the direction indicated by the arrow adjacent to the load resistance. The dc output polarity for each circuit is indicated by the signs associated with the load resistance.

The circuits shown in parts B and C have a resistor, R_s , in series with the ac source. The resistor, called the *surge resistor*, limits the peak current through each rectifier to a safe value. The value of resistor R_s is influenced by the circuit design; determination of its value includes the consideration of several other factors, such as the applied ac voltage, the resistance of the load circuit, the capacitance value of the charging capacitors, and the peak current rating of the semiconductor diodes. In the circuit shown in part A, the resistor has been omitted since there is normally sufficient resistance in the secondary winding of transformer T1 to limit the peak current through each rectifier; however, some circuits may include a resistor (R_s) between the charging capacitor (C1) and the transformer secondary winding.

The operation of the half-wave voltage-double circuit can be readily understood from a study of the equivalent electron-tube circuit description, simplified circuits, and associated waveforms given previously in this section of the handbook. The action of the semiconductor rectifiers in this voltage-doubler circuit is essentially the same as that described for the equivalent electron-tube circuit. Semiconductor rectifiers CR1 and CR2 correspond directly to rectifiers V1 and V2 in the electron-tube circuit description. For these reasons, an explanation of circuit operation is not given here.

Charging capacitor C2 is charged only on alternate half-cycles of the applied ac voltage, and is always attempting to discharge through the load resistance; therefore, the output voltage, e_o , contains some voltage variation, or ripple. The frequency of the ripple voltage is the same as the frequency of the ac source, because capacitor C2 is charged only once for each complete input cycle; thus, additional filtering is necessary to obtain a steady dc voltage. (Filter circuits are discussed in the Filter Section of this handbook.)

The regulation of the voltage-doubler circuit is relatively poor; the value of output voltage obtained is determined largely by the resistance of the load and the resulting load circuit, since the load (and the filter circuit, if used) is in parallel with capacitor C2.

Failure Analysis.

No Output. In the half-wave voltage-doubler circuit, the no-output condition is likely to be limited to one of several possible causes: the lack of applied ac voltage (including the possibility of a defective transformer or an open surge resistor R_s), an open capacitor C_1 , a shorted load circuit (including capacitor C_2 and filter circuit capacitor), an open filter choke, or defective rectifiers.

The ac supply voltage should be measured at the input of the circuit to determine whether the voltage is present and is the correct value. If the circuit uses a step-up or isolation transformer (T1), measure the voltage at the secondary terminals to determine whether it is present and is the correct value. With the primary voltage removed from the transformer, continuity measurements of the primary and secondary windings should be made to determine whether one of the windings is open, since an open circuit in either winding will cause a lack of secondary voltage.

If the circuit includes a surge resistor (R_s), a resistance measurement can be made to determine whether the resistor is open. If the resistor is found to be open, the voltage-doubler and load circuit should be checked further to determine whether excessive load current, a defective rectifier, or a shorted capacitor has caused the resistor to act as a fuse and to open.

With the ac supply voltage removed from the input to the circuit and with the load disconnected from capacitor C_2 , resistance measurements can be made across the terminals of capacitor C_2 and at the output terminals of the circuit (across the load). These measurements will determine whether capacitor C_2 or the load circuit (including filter components) is shorted. Because capacitor C_2 and the filter-circuit capacitors are electrolytic capacitors, the resistance measurements may vary, depending upon the test-lead polarity of the ohmmeter. Therefore, two measurements must be made, with the test leads reversed at the circuit test points for one of the measurements, to determine the larger of the two resistance measurements. The larger resistance value is then accepted as the measured value. Capacitor C_1 may be checked in a similar manner.

The rectifiers should be checked to determine whether they are open or otherwise defective. A relative check of the rectifier condition can be made by use of an ohmmeter, as outlined in a previous paragraph of this section. However, failure of one or both

rectifiers may be the result of other causes; therefore, tests of the filter and load circuit are necessary.

Low Output. The ac supply voltage should be measured at the input of the circuit to determine whether the voltage is the correct value, since a low applied voltage can result in a low output voltage.

Each rectifier should be checked to determine whether the low output is due to normal rectifier aging. A relative check of rectifier condition can be made by use of an ohmmeter, as outlined in a previous paragraph of this section. If the forward resistance of the rectifier increases, the output voltage will decrease. Also, if the reverse resistance decreases, the output voltage will decrease, and the amplitude of the ripple voltage will increase.

The load current should be checked to make sure that it is not excessive, because the voltage-doubler circuit has poor regulation and an increase in load current (decrease in load resistance) can cause a decrease in output voltage.

One terminal of each charging capacitor, C_1 and C_2 , should be disconnected from the circuit and each capacitor checked, using a capacitance analyzer, to determine the effective capacitance and leakage resistance of each capacitor. A decrease in effective capacitance or losses within either capacitor can cause the output of the voltage-doubler circuit to be below normal, since the defective capacitor will not charge to its normal operating value. If a suitable capacitance analyzer is not available, an indication of leakage resistance can be obtained by use of an ohmmeter; the measurements are made with one terminal of the capacitor disconnected from the circuit. Using the ohmmeter procedure outlined in a previous paragraph for the no-output condition, two measurements are made (with the test leads reversed at the capacitor terminals for one of the measurements). The larger of the two measurements should be greater than 1 megohm for a satisfactory capacitor.

**FULL-WAVE VOLTAGE DOUBLER.
(ELECTRON TUBE)****Application.**

The full-wave voltage-doubler circuit is used to produce a higher d-c output voltage than can be obtained from a conventional rectifier circuit utilizing the same input voltage. This voltage doubler is normally used where the load current is small and voltage

regulation is not too critical; however, the regulation of the full-wave voltage doubler is better than that of the half-wave voltage doubler. The circuit is frequently employed as the power supply in small portable receivers and audio amplifiers and, in some transmitter applications, as a bias supply.

Characteristics.

Input to circuit is ac; output is pulsating dc.

DC output voltage is approximately twice that obtained from half-wave rectifier circuit utilizing the same input voltage; output current is relatively small.

Output requires filtering; dc output ripple frequency is equal to twice the ac source frequency.

Has relatively poor regulation characteristics; output voltage available is a function of load current.

Depending upon circuit application, may be used with or without a power or isolation transformer.


Uses indirectly heated cathode-type rectifiers.

Circuit Analysis.

General. The full-wave voltage-doubler circuit is used either with or without a transformer to obtain a dc voltage from an ac source. As the term *voltage doubler* implies, the output voltage is approximately twice the input voltage. The full-wave voltage doubler derives its name from the fact that the charging capacitors (C1 and C2) are in series across the load, and each capacitor receives a charge on alternate half-cycles of the applied voltage; therefore, two pulses are present in the load circuit for each complete cycle of the applied voltage. Although the voltage regulation of the full-wave voltage doubler is better than that of the half-wave voltage doubler, it is nevertheless considered poor as compared with conventional rectifier circuits. Therefore, use of the circuit is generally restricted to applications in which the load current is small and relatively constant.

Circuit Operation. A basic full-wave voltage-doubler circuit is shown in the accompanying circuit schematic. Fundamentally, the circuit consists of two half-wave rectifiers, V1 and V2, and two charging capacitors, C1 and C2, arranged so that each capacitor receives a charge on alternate half-cycles of the applied voltage. The voltage developed across one capacitor is in series with the voltage developed across the other; thus, the output voltage developed across the load resistance is approximately twice the applied voltage.

The rectifiers, V1 and V2, are of the indirectly heated cathode type, and are identical-type diodes. Although the circuit schematic illustrates two separate rectifiers, a twin-diode is generally used in the circuit. Typical twin-diode electron tubes designed specifically for use in voltage-doubler circuits are: 25Z6, 50Y6, and 117Z6. As indicated by the tube-type numbers, these tubes require nominal filament-supply voltages of 25, 50, and 117 volts, respectively. Because there are several possible filament circuit combinations, the actual filament circuit for V1 and V2 is not shown on the circuit schematic. The filament voltage is usually obtained directly from the ac source if the filament is rated at the source voltage, by use of a voltage-dropping resistance in series with the rectifier filament (s) to reduce the ac source voltage to the correct value, or from a transformer secondary winding of the correct value. In some equipments, the filaments of other tubes within the equipment are connected in series (or series-parallel), and this combination is then placed in series with the rectifier filament (s) across the ac source; when this is done, a voltage-dropping resistor may be required.

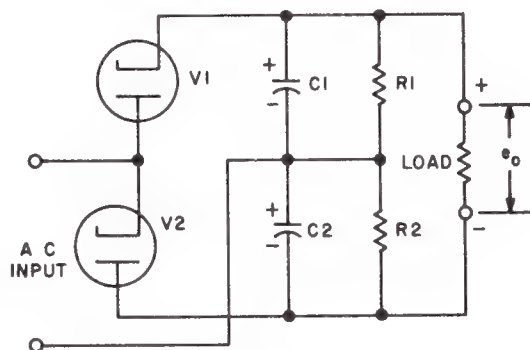

Basic Full-Wave Voltage-Doubler Circuit

The charging capacitors, C1 and C2, are of equal capacitance value and are usually relatively large (10 to 16 μf). Equalizing resistors R1 and R2, are connected across charging capacitors C1 and C2, respectively; they are of equal value and are generally greater than 2 megohms. Resistors R1 and R2 are not necessary for circuit operation; however, when included in the circuit, they have a dual purpose in that

they tend to equalize the voltages across the charging capacitors and also act as bleeder resistors to discharge the associated capacitors when the circuit is de-energized. When capacitors C1 and C2 are large, the peak charge current, during the period of time the rectifier conducts, may be excessive. To limit the charge current and offer protection to the rectifiers, a protective "surge" resistor is placed in series with the ac source. The value of the surge resistor is relatively small, generally 50 to 1000 ohms.

One disadvantage of the full-wave voltage-doubler circuit is that neither dc output terminal can be directly connected to ground or to one side of the ac


source; however, when a step-up or isolation transformer is used to supply the input to the voltage doubler, either output terminal may be connected to ground or to the chassis.

The operation of the full-wave voltage-doubler circuit can be understood from the simplified circuits, parts A and B, and the waveforms, part C, shown in the accompanying illustration.

Assume that the ac input to the voltage doubler during the initial half-cycle is of the polarity indicated in part A of the illustration. C2 does not enter into circuit operation here. Electrons flow in the direction indicated by the arrows from the positive plate of charging capacitor C1, through rectifier tube V1 (cathode to plate), through the ac source, and to the negative plate of charging capacitor C1. The upper (positive) plate of capacitor C1 lacks electrons, while the lower (negative) plate has a surplus of electrons. Thus, during the initial half cycle, capacitor C1 assumes a charge (E_{C1}) of the polarity indicated, which is equal to approximately the peak value of the applied ac voltage. The voltage (E_{C1}) developed across charging capacitor C1 does not remain constant, as shown by waveform E_{C1} , but tends to vary somewhat because of a small discharge current flowing through the parallel equalizing resistor ($R1$) and because there is a tendency to discharge through the series circuit consisting of the ac source, rectifier V2, and the load.

During the next half-cycle the polarity of the applied ac input to the voltage doubler is as indicated in part B of the illustration. C1 does not enter into circuit operation here. Electrons flow in the direction indicated by the arrows from the positive plate of charging capacitor C2, through the ac source, through rectifier V2, to the negative plate of charging capacitor C2. Thus, during the second half-cycle, capacitor C2 assumes a charge (E_{C2}) of the polarity indicated, which is equal to approximately the peak value of the applied ac voltage. The voltage (E_{C2}) developed across capacitor C2 does not remain constant, as shown by waveform E_{C2} , but tends to vary somewhat because of the small discharge current flowing through the parallel equalizing resistor ($R2$), and because there is a tendency to discharge through the series circuit consisting of the load, rectifier V1, and the ac source.

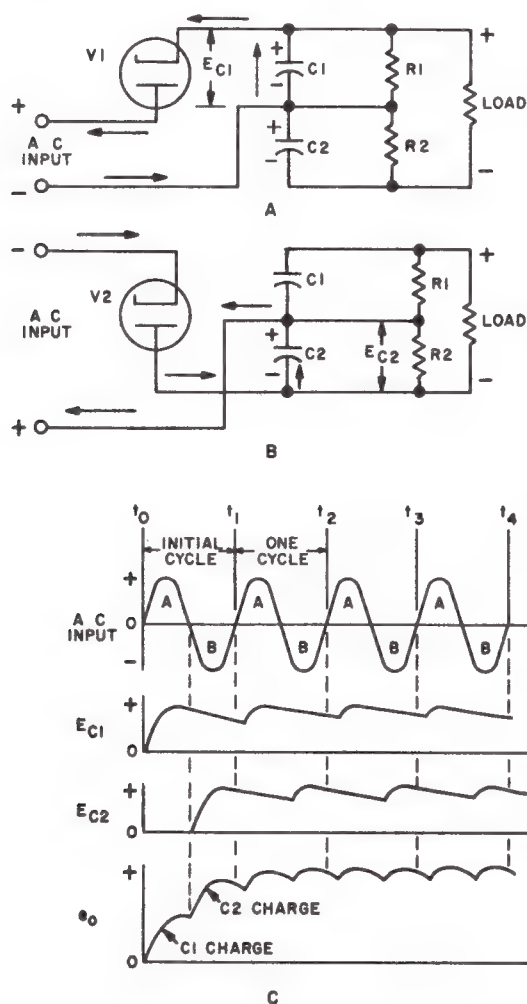Charging capacitors C1 and C2 are connected in series across the load resistance, and the current delivered to the load results from the discharge of these



Typical Full-Wave Voltage-Doubler Circuit Operation and Waveforms

capacitors. The instantaneous sum of the charging-capacitor voltages, E_{C1} and E_{C2} , is equal to approximately twice the peak voltage applied to the input of the voltage-doubler circuit, and is shown by the waveform of the output voltage, e_o .

The output waveform contains some ripple voltage; therefore, additional filtering is required to obtain a steady dc voltage. The frequency of the main component of the ripple voltage is equal to twice the frequency of the ac source, since each charging capacitor receives a charge on alternate half-cycles of the applied voltage. The regulation of the voltage-doubler circuit is relatively poor; the value of the output voltage obtained is determined largely by the resistance of the load and the resulting load current. If the load current is large, the voltage across capacitors C1 and C2 is reduced accordingly.

Failure Analysis.

No Output. In the full-wave voltage-double circuit, the no-output condition is likely to be limited to one of several possible causes: the lack of filament voltage or an open filament in the rectifier(s), the lack of applied ac voltage, or a shorted load circuit (including filter circuit components).

A visual check of a glass-envelope rectifier tube can be made to determine whether the filament(s) is lit; if the filament is not lit, it may be open or the filament voltage may not be applied. The tube filament should be checked for continuity; also, the presence of voltage at the tube socket should be determined by measurement.

The ac supply voltage should be measured at the input of the circuit to determine whether the voltage is present and is the correct value. If the circuit uses a step-up or isolation transformer, measure the voltage at the secondary terminals to determine whether it is present and is the correct value. If necessary, the primary voltage should be removed from the transformer and continuity measurements of the primary and secondary windings made to determine whether one of the windings is open, since an open circuit in either winding will cause a lack of secondary voltage.

With the ac supply voltage removed from the input to the circuit and with the load (including filter circuit) disconnected from capacitor C1, resistance measurements can be made across the load to determine whether the load circuit (including filter components) is shorted. Measurements should be made across the terminals of charging capacitors C1 and C2

to determine whether one or both capacitors are shorted. (If the circuit includes equalizing resistors R1 and R2, the resistance measured across a capacitor will normally measure something less the value of the equalizing resistor.) Because C1 and C2 are electrolytic capacitors, the resistance measurements may vary, depending upon the test-lead polarity of the ohmmeter. Therefore, two measurements must be made, with the test leads reversed at the capacitor terminals for one of the measurements, to determine the larger of the two resistance measurements. The larger resistance value is then accepted as the measured value.

Low Output. The rectifiers (V1 and V2) should be checked to determine whether the cause of low output is low cathode emission. The load current should be checked to make sure that it is not excessive, because the voltage-doubler circuit has poor regulation and an increase in load current (decrease in load resistance) can cause a decrease in output voltage.

One terminal of each capacitor, C1 and C2, should be disconnected from the circuit and each capacitor checked, using a capacitance analyzer, to determine the effective capacitance and leakage resistance of each capacitor. A decrease in effective capacitance or losses within either capacitor can cause the output of the voltage-doubler circuit to be below normal, since the defective capacitor will not charge to its normal operating value. If a suitable capacitance analyzer is not available, an indication of leakage resistance can be obtained by using an ohmmeter. The measurements are made with one terminal of the capacitor disconnected from the circuit; using the ohmmeter procedure outlined in a previous paragraph, two measurements are required (the test leads are reversed at the capacitor terminals for one of the measurements). The larger of the two measurements should be greater than 1 megohm for a satisfactory capacitor.

FULL-WAVE VOLTAGE DOUBLER (SEMICONDUCTOR)

Application.

Same application as electron tube version.

Characteristics.


Same characteristics as electron tube version except that it uses two semiconductor rectifiers

(single, multiple, or stacked units) instead of electron tubes.

Circuit Analysis.

General. The full-wave voltage-double circuit is used either with or without a transformer to obtain a dc voltage from ac source. As the term *voltage doubler* implies, the output voltage is approximately twice the input voltage. The full-wave voltage doubler derives its name from the fact that the charging capacitors (C1 and C2) are in series across the load, and each capacitor receives a charge on alternate half-cycles of the applied voltage; therefore, two pulses are present in the load circuit for each complete cycle of the applied voltage. Although the voltage regulation of the full-wave voltage doubler is better than that of the half-wave voltage doubler, it is nevertheless considered poor as compared with conventional rectifier circuits. Therefore, use of the circuit is generally restricted to applications in which the load current is small and relatively constant.

Circuit Operation. A basic full-wave voltage-doubler circuit is shown in the accompanying circuit schematic. Fundamentally, the circuit consists of two half-wave rectifiers, CR1 and CR2, and two charging capacitors, C1 and C2, arranged so that each capacitor receives a charge on alternate half-cycles of the applied voltage. The voltage developed across one capacitor is in series with the voltage developed across the other; thus, the output voltage developed across the load resistance is approximately twice the applied voltage.

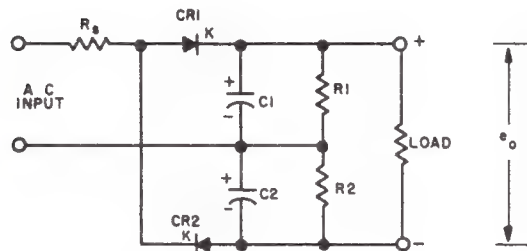

Basic Full-Wave Voltage-Doubler Circuit

The rectifiers, CR1 and CR2, are identical-type semiconductor diodes, and the charging capacitors, C1 and C2, are of equal value. Equalizing resistors R1 and R2 are connected across charging capacitors C1

and C2, respectively; they are of equal value and are generally greater than 2 megohms. Resistors R1 and R2 are not necessary for circuit operation; however, when included in the circuit, they have a dual purpose in that they tend to equalize the voltages across the charging capacitors and also act as bleeder resistors to discharge the associated capacitors when the circuit is de-energized. When capacitors C1 and C2 are large, the peak charge current, during the period of time the rectifier conducts, may be excessive. To limit the charge current and offer protection to the rectifiers, a protective "surge" resistor, R_s , is placed in series with the ac source; however, if a transformer is used and if there is sufficient resistance in the secondary winding, the series resistor is usually omitted.

One disadvantage of the full-wave voltage-doubler circuit is that neither dc output terminal can be directly connected to ground or to one side of the ac source; however, when a step-up or isolation transformer is used to supply the input to the voltage doubler, either output terminal may be connected to ground or to the chassis.

The operation of the full-wave voltage-doubler circuit can be readily understood from a study of the equivalent electron-tube circuit description, simplified circuits, and associated waveforms given previously in this section of the handbook. The action of the semiconductor rectifiers in this voltage-doubler circuit is essentially the same as that described for the equivalent electron-tube circuit. Semiconductor rectifiers CR1 and CR2 correspond directly to rectifiers V1 and V2 in the electron-tube circuit description. For these reasons, an explanation of circuit operation is not given here.

Charging capacitors C1 and C2 are connected in series across the load resistance, and each capacitor receives a charge on alternate half-cycle of the applied voltage; therefore, the output voltage, e_o , contains some voltage variations, or ripple. The frequency of the main component of the ripple voltage is equal to twice the frequency of the ac source and, therefore, additional filtering is required to obtain a steady dc voltage. (Filter circuits are discussed in the Filter Section of this handbook.)

The regulation of the voltage-doubler circuit is relatively poor; the value of the output voltage obtained is determined largely by the resistance of the load and the resulting load current. If the load current is large, the voltage across capacitors C1 and C2 is reduced accordingly.

Failure Analysis.

No Output. In the full-wave voltage-doubler circuit, the no-output condition is likely to be limited to one of several possible causes: the lack of applied ac voltage (including the possibility of a defective transformer or an open surge resistors R_s), a shorted load circuit (including filter circuit capacitor), an open filter choke, or defective rectifiers.

The ac supply voltage should be measured at the input of the circuit to determine whether the voltage is present and is the correct value. If the circuit uses a step-up of isolation transformer, measure the voltage at the secondary terminals to determine whether it is present and is the correct value. With the primary voltage removed from the transformer, continuity measurements of the primary and secondary windings should be made to determine whether one of the windings is open, since an open circuit in either winding will cause a lack of secondary voltage.

If the circuit includes a surge resistor (R_s), a resistance measurement can be made to determine whether the resistor is open. If the resistor is found to be open, the voltage-doubler and load circuit should be checked further to determine whether excessive load current, a defective rectifier, or a shorted capacitor has caused the resistor to act as a fuse and to open.

With the ac supply voltage removed from the input to the circuit and with the load (including filter circuit) disconnected from capacitor C1, resistance measurements can be made across the load to determine whether the load circuit (including filter components) is shorted. Measurements should be made across the terminals of charging capacitors C1 and C2 to determine whether one or both capacitors are shorted. (If the circuit includes equalizing resistors R1 and R2, the resistance measured across a capacitor will normally measure something less than the value of the equalizing resistor.) Because C1 and C2 are electrolytic capacitors, the resistance measurements may vary, depending upon the test-lead polarity of the ohmmeter. Therefore, two measurements must be made, with the test leads reversed at the capacitor terminals for one of the measurements, to determine the larger of the two resistance measurements. The

larger resistance value is then accepted as the measured value.

The rectifiers should be checked to determine whether they are open or otherwise defective. A relative check of the rectifier condition can be made by use of an ohmmeter, as outlined in a previous paragraph of this section. However, failure of the rectifiers may be the result of other causes; therefore, tests of the filter and load circuit are necessary.

Low Output. The ac supply voltage should be measured at the input of the circuit to determine whether the voltage is the correct value, since a low applied voltage can result in a low output voltage.

Each rectifier should be checked to determine whether the low output is due to normal rectifier aging. A relative check of rectifier condition can be made by use of an ohmmeter, as outlined in a previous paragraph of this section. If the forward resistance of the rectifier increases, the output voltage will decrease. Also, if the reverse resistance decreases, the output voltage will decrease, and the amplitude of the ripple voltage will increase.

The load current should be checked to make sure that it is not excessive, because the voltage-doubler circuit has poor regulation and an increase in load current (decrease in load resistance) can cause a decrease in output voltage.

One terminal of each charging capacitor, C1 and C2, should be disconnected from the circuit and each capacitor checked, using a capacitance analyzer, to determine the effective capacitance and leakage resistance of each capacitor. A decrease in effective capacitance or losses within either capacitor can cause the output of the voltage-doubler circuit to be below normal, since the defective capacitor will not charge to its normal operating value. If a suitable capacitance analyzer is not available, an indication of leakage resistance can be obtained by using an ohmmeter; the measurements are made with one terminal of the capacitor disconnected from the circuit and, using the ohmmeter procedure outlined in a previous paragraph for the no-output condition, two measurements are made (with the test leads reversed at the capacitor terminals for one of the measurements). The larger of the two measurements should be greater than 1 megohm for a satisfactory capacitor.

VOLTAGE TRIPLER. (ELECTRON TUBE)

Application.

The voltage-tripler circuit is used to produce a higher dc output voltage than can be obtained from a conventional rectifier circuit utilizing the same input voltage. It is normally used in "transformerless" circuits where the load current is small and voltage regulation is not critical.

Characteristics.

Input to circuit is ac; output is pulsating dc.

Dc output voltage is approximately three times the voltage obtained from a half-wave rectifier circuit utilizing the same input voltage; output current is relatively small.

Output requires filtering; dc output ripple frequency is either twice or equal to ac source frequency, depending upon triple circuit arrangement.

Has poor regulation characteristics; output voltage available is a function of load current.

Depending upon circuit application, may be used with or without a power or isolation transformer.


Uses indirectly heated cathode-type rectifiers.

Circuit Analysis.

General. The voltage-tripler circuit is used with or without a transformer to obtain a dc voltage from an ac source. As the term *voltage tripler* implies, the output voltage is approximately three times the input voltage. The voltage regulation of the voltage tripler is relatively poor as compared with the regulation of either the half-wave or the full-wave voltage doubler circuit. Assuming that a given voltage-multiplier (doubler, tripler, or quadrupler) circuit uses the same value of capacitors in each instance, the greater the voltage-multiplication factor of the circuit, the poorer is the regulation characteristics. However, the regulation characteristics can be improved somewhat by increasing the value of the individual capacitors used in the voltage-multiplier circuit. Because of the regulation characteristics of the voltage tripler, the use of the circuit is generally restricted to applications in which the load current is small and relatively constant.

Circuit Operation. A basic voltage-tripler circuit is shown in the accompanying circuit schematic. Fundamentally, this circuit consists of a half-wave voltage-doubler circuit and a half-wave rectifier circuit arranged so that the output voltage of one circuit is in series with the output voltage of the other; thus, the

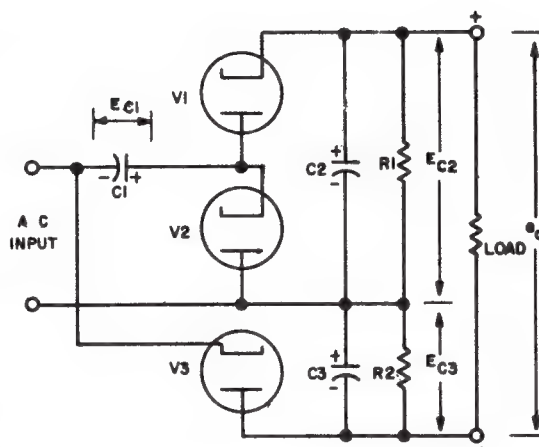total output voltage developed across the load resistance is approximately three times the applied voltages.



Basic Voltage-Triple Circuit

Rectifiers V1 and V2, charging capacitors C1 and C2, and resistor R1 form a half-wave voltage-doubler circuit (the operation of the voltage-doubler circuit was previously described in this section). Rectifier V3, charging capacitor C3, and resistor R2 form a simple half-wave rectifier circuit. Rectifiers V1, V2, and V3 are all identical-type diodes with indirectly heated cathodes. Because there are several possible filament circuit arrangements, the actual filament circuit for V1, V2, and V3 is not shown on the circuit schematic. It is usually necessary to isolate the filament circuits from each other and supply the filament (heater) voltages from independent sources because of heater-to-cathode breakdown voltage limitations imposed by the rectifier tubes themselves.

Charging capacitors C1, C2, and C3 are of equal capacitance value and are usually rather large (10 to 20 μf) for 50- to 60-hertz ac input. Resistors R1 and R2 are connected across charging capacitors C2 and C3, respectively; they are generally greater than 2 megohms. Resistors R1 and R2 are not necessary for circuit operation; however, when included in the circuit, they act as bleeder resistors to discharge the associated capacitors when the circuit is de-energized.

One disadvantage of the basic voltage-triple circuit illustrated is that neither dc output terminal can be directly connected to ground or to one side of the ac

source; however, when a step-up or isolation transformer is used to supply the input to the voltage


tripler, either output terminal may be connected to ground or to the chassis.

The operation of the basic voltage-tripler circuit can be understood from the simplified circuits, parts A, B, and C, and the waveforms, part D, shown in the accompanying illustration.

Assume that the ac input to the voltage-tripler circuit (during the initial half-cycle) has the polarity indicated by the signs adjacent to the input terminals in part A of the illustration. Electrons flow in the direction indicated by the arrows from the right-hand (positive) plate of charging capacitor C1, through rectifier tube V2 (cathode to plate), through the ac source, and to the left-hand (negative) plate of charging capacitor C1. (The positive plate of capacitor C1 lacks electrons, while the negative plate has a surplus of electrons.)

While the action described above for the simplified circuit of part A is taking place, a similar action occurs (during the initial half-cycle) for the simplified half-wave circuit given in part B. (Note that in part B, the ac input has the polarity indicated by the signs adjacent to the input terminals, and, since these two circuits operate simultaneously, the input polarity is the same as that shown in part A.) Electrons flow in the direction indicated by the arrows from the upper (positive) plate of charging capacitor C3, through the ac source, through rectifier tube V3 (cathode to plate), and to the lower (negative) plate of charging capacitor C3. Thus, during the initial half-cycle, charging capacitor C1 assumes a charge (E_{C1}) of the polarity indicated in part A, and this voltage is equal to approximately the peak value of the applied ac voltage; also, charging capacitor C3 assumes a charge (E_{C3}) of the polarity indicated in part B, and this voltage is equal to approximately the peak value of the applied ac voltage.

During the next half-cycle, the applied ac input to the voltage tripler has the polarity indicated by the signs adjacent to the input terminals in part C of the illustration. The charge (E_{C1}) existing across charging capacitor C1 is in series with the applied ac and will therefore add its potential to the peak value of the input voltage. Electrons flow in the direction indicated by the arrows from the upper (positive) plate of capacitor C2, through rectifier tube V1 (cathode to plate), through charging capacitor C1 and the ac source in series, and to the lower (negative) plate of charging capacitor C2. Thus, during the second half-cycle, charging capacitor C2 assumes a charge (E_{C2})

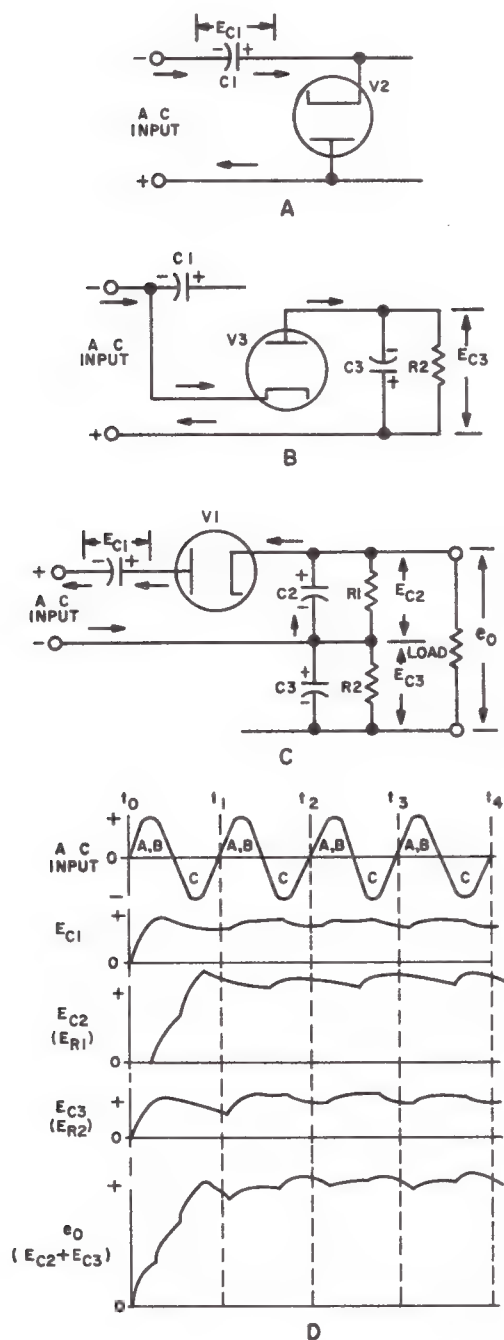

Typical Voltage-Tripler Circuit Operation and Waveforms

of the polarity indicated which is equal to the peak value of the applied ac voltage pulse the value of the charge (E_{C1}) existing across charging capacitor C1. As a result, the value of the voltage (E_{C2}) across capacitor C2 is equal to approximately twice the peak voltage of the applied ac, provided that charging capacitor C1 does not lose any of its initial charge.


Charging capacitors C2 and C3 are connected in series across the load resistance; therefore, the dc voltage delivered to the load is the sum of the voltages ($E_{C2} + E_{C3}$) developed across charging capacitors C2 and C3. The value of the dc output voltage, e_o , is approximately three times the peak voltage applied to the input of the voltage-tripler circuit.

The output waveform, e_o , contains a ripple component; therefore, filtering is required to obtain a steady dc voltage. The frequency of the main component of the ripple voltage is equal to twice the frequency of the ac source because charging capacitors C2 and C3 receive charges on alternate half-cycles of the applied voltage. The value of the output voltage obtained from the voltage tripler is determined largely by the resistance of the load and the resulting load current. Assuming the same value for each of the charging capacitors in either rectifier circuit, the regulation of the voltage-tripler circuit is poor as compared with that of a typical voltage-doubler circuit.

Two possible arrangements for a modified voltage-tripler circuit are given in the accompanying illustration; part A shows a modified tripler circuit arranged for positive output with the negative output terminal common to one side of the ac source, and part B shows the circuit arranged for negative output with the positive output terminal common to one side of the ac source.

In these two circuit variations, the basic half-wave rectifier circuit, represented by V3 and C3, has a voltage-doubler circuit connected to it in such a manner that the full output voltage is developed across charging capacitor C2. The operation of either tripler circuit (part A or part B) is briefly described in the following paragraph.

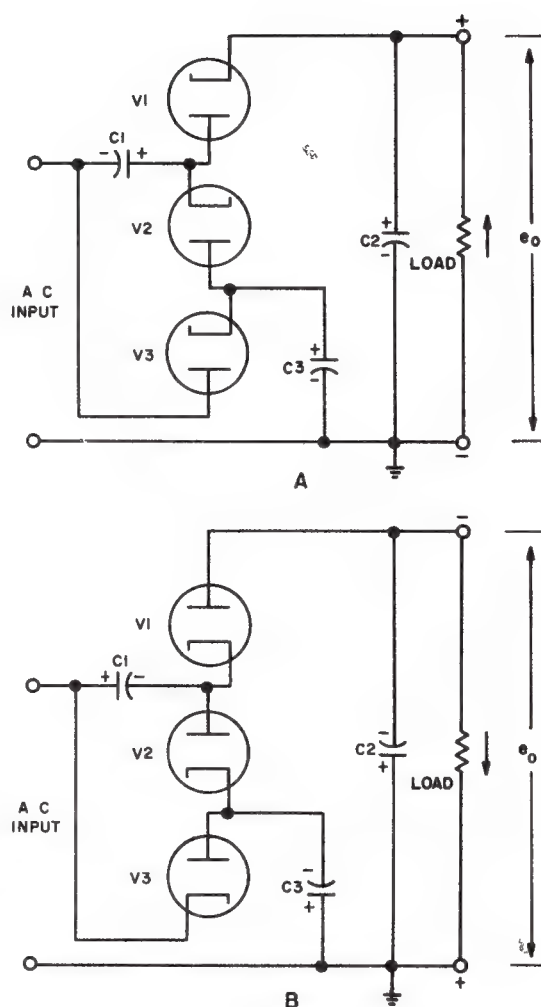During the initial half-cycle of the applied voltage, rectifier V3 conducts to charge capacitor C3. During the next half-cycle, the voltage across capacitor C3 is in a series with the applied voltage, and rectifier V2 conducts to charge capacitor C1 to approximately twice the value of the peak input voltage. On the next half-cycle, rectifier V3 again conducts to charge



Modified Voltage-Tripler Circuits

capacitor C3; at the same time, since the voltage across capacitor C1 is in series with the applied voltage, rectifier V1 also conducts to charge capacitor C2 to approximately three times the peak value of the input voltage. Thus, the voltage developed across capacitor C2 is the dc output delivered to the load.

The output of the tripler circuits illustrated in parts A and B requires filtering to obtain a steady dc voltage. The frequency of the ripple voltage for either circuit arrangement is equal to the frequency of the ac source because charging capacitor C2 receives a charge only once for each complete cycle of the applied voltage. For this reason, the regulation is not as

good as the regulation of the basic voltage-tripler circuit described earlier.

Failure Analysis.

No Output. In the basic voltage-tripler circuit, the no-output condition is likely to be limited to one of the following possible causes: the lack of filament voltage to all rectifiers, the lack of applied ac voltage, or a shorted load circuit (including filter circuit components).

A visual check of the glass-envelope rectifier tubes can be made to determine whether the filaments are lit; if the filaments are not lit, the presence of voltage should be determined by measurement.

The ac supply voltage should be measured at the input to the circuit to determine whether the voltage is present and is the correct value. If the circuit uses a step-up or isolation transformer, measure the voltage at the secondary terminals to determine whether it is present and is the correct value. If necessary, the primary voltage should be removed from the transformer and continuity measurements of the primary and secondary windings made to determine whether one of the windings is open, since an open circuit in either winding will cause a lack of secondary voltage.

With the ac supply voltage removed from the input to the circuit and with the load (including filter circuit) disconnected from the terminal of capacitor C2, resistance measurements can be made across the load to determine whether the load circuit (including filter components) is shorted. Measurements should be made across the terminals of charging capacitors C2 and C3 in the basic tripler circuit, or across charging capacitor C2 in the modified tripler circuit, to determine whether the no-output condition is caused by shorted capacitors. The basic tripler circuit includes resistors R1 and R2; therefore, the resistance measured across capacitors C2 and C3 will normally be something less than the value of the associated bleeder resistor. Since the charging capacitors are electrolytic capacitors, the resistance measurements may vary, depending upon the test-lead polarity of the ohmmeter. Therefore, two measurements must be made, with the test leads reversed at the capacitor terminals for one of the measurements, to determine the larger of the two resistance measurements. The larger resistance value is then accepted as the measured value.

Low Output. The rectifiers (V1, V2, and V3) should be checked to determine whether the cause of

low output is low cathode emission. The load current should be checked to make sure that it is not excessive, because the voltage-tripler circuit has poor regulation and an increase in load current (decrease in load resistance) can cause a decrease in output voltage.

One terminal of each charging capacitor (C1, C2, and C3) should be disconnected from the circuit and each capacitor checked, using a capacitance analyzer, to determine its effective capacitance and leakage resistance. A decrease in effective capacitance or losses within the capacitor can cause the output of the voltage-tripler circuit to be below normal, since the defective capacitor will not charge to its normal operating value. If a suitable capacitance analyzer is not available, an indication of leakage resistance can be obtained by using an ohmmeter. First, disconnect one terminal of the capacitor from the circuit; then, using the ohmmeter procedure outlined for the no-output condition, make two measurements (reverse the test leads at the capacitor terminals for one of the measurements). The larger of the two measurements should be greater than 1 megohm for a satisfactory capacitor.

VOLTAGE TRIPLER (SEMICONDUCTOR)

Application.

Same application as electron tube version.

Characteristics.

Same characteristics as electron tube version except that it uses three semiconductor rectifiers (single, multiplier, or stacked units) instead of electron tubes.

Circuit Analysis.

General. The voltage-tripler circuit is used with or without a transformer to obtain a dc voltage from an ac source. As the term *voltage tripler* implies, the output voltage is approximately three times the input voltage. The voltage regulation of the voltage tripler is relatively poor as compared with the regulation of either the half-wave or the full-wave voltage-doubler circuit. Assuming that a given voltage-multiplier (doubler, tripler, or quadrupler) circuit uses the same value of capacitors in each instance, the greater the voltage-multiplication factor of the circuit, the poorer the regulation characteristics. However, the regulation

characteristics can be improved somewhat by increasing the value of the individual capacitors used in the voltage-multiplier circuit. Because of the regulation characteristics of the voltage tripler, the use of the circuit is generally restricted to applications in which the load current is small and relatively constant.

Circuit Operation. Three voltage-tripler circuits are shown in the accompanying illustration. The schematic of part A shows a basic voltage-tripler circuit, which is fundamentally a half-wave voltage-doubler and a half-wave rectifier arranged so that the output voltage of one circuit is in series with the output voltage of the other. The schematic of part B shows a modified tripler circuit arranged for positive output, with the negative output terminal common to one side of the ac source; part C shows this same circuit

arranged for negative output, with the positive terminal common to one side of the ac source. In each of the voltage-tripler circuits shown in the accompanying illustration, the total output voltage developed across the load resistance is approximately three times the applied voltage.


The rectifiers, CR1, CR2, and CR3, are identical-type semiconductor diodes in each of the three circuits illustrated. Charging capacitors C1, C2, and C3 are of equal capacitance value in each of the three circuits; however, because of the higher voltage developed across capacitor C2, the voltage rating of C2 is always greater than the voltage rating of either C1 or C3. Resistors R1 and R2, shown in the circuit of part A, are not necessary for circuit operation; however, when they are included in the circuit, resistors R1 and R2 stabilize the voltage developed across the two series capacitors, C2 and C3, respectively, and also act as a bleeder to discharge the capacitors when the circuit is de-energized. The value of resistor R1 is generally twice the value of resistor R2.

A surge resistor, R_s , is placed in series with the ac source; however, if a transformer is used in the circuit, and if there is sufficient resistance in the secondary winding, the resistor may be omitted.

Each tripler circuit illustrated has one disadvantage in that neither dc output terminal can be directly connected to ground (chassis). (The circuits shown in parts B and C have one output terminal in common with the ac source.) If a step-up or isolation transformer is used to supply the input to a tripler circuit, either output terminal may be connected to ground or to the chassis.

The operation of the tripler circuits can be readily understood from a study of the equivalent electron-tube circuit descriptions given perviously in this section of the handbook. The action of the semiconductor rectifiers in a tripler circuit is essentially the same as that described for the equivalent electron-tube circuit. Semiconductor rectifiers CR1, CR2, and CR3 correspond directly to rectifiers V1, V2, and V3 in the electron-tube circuit description. For these reasons, an explanation of circuit operation is not given here.

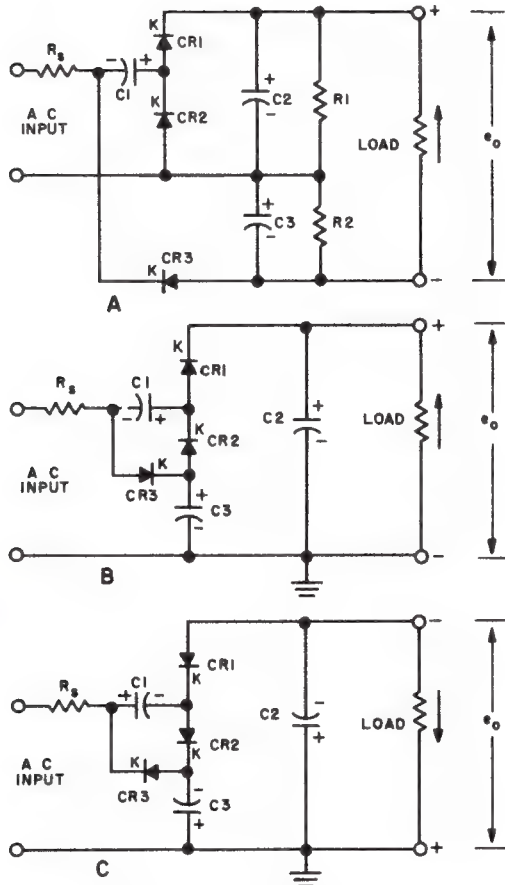In the circuit shown in part A, charging capacitors C2 and C3 are in series across the load resistance, and each capacitor receives a charge on alternate half-cycles of the applied voltage; as a result, the output voltage contains some ripple. In this tripler circuit, the frequency of the main component of the ripple



Voltage-Tripler Circuits

voltage is equal to twice the frequency of the ac source. In the circuits shown in parts B and C, charging capacitor C2 receives a charge on alternate half-cycles only; thus, the output voltage of these two circuits contains a ripple voltage which has a frequency equal to that of the ac source.

As stated previously, the regulation of a voltage-tripler circuit is relatively poor; therefore, the value of the output voltage obtained from the voltage tripler is determined largely by the resistance of the load and the resulting load current. The output of each of the circuits illustrated requires filtering to obtain a steady dc voltage. (Filter circuits are discussed in the Filter Section of this handbook.)

Failure Analysis.

No Output. In the voltage-tripler circuit, the no-output condition is likely to be limited to be limited to one of several possible causes: the lack of applied ac voltage (including the possibility of an open surge resistor, R_s , or a defective step-up or isolation transformer), a shorted load circuit (including filter circuit components), open charging capacitors (dependent upon circuit configuration), or defective rectifiers.

The ac supply voltage should be measured at the input to the circuit to determine whether the voltage is present and is the correct value. If the circuit uses a step-up or isolation transformer, measure the voltage at the secondary terminals to determine whether it is present and is the correct value. If necessary, the primary voltage should be removed from the transformer and continuity measurements of the primary and secondary windings made to determine whether one of the windings is open, since an open circuit in either winding will cause a lack of secondary voltage.

If the circuit includes a surge resistor, R_s , a resistance measurement can be made to determine whether the resistor is open. If the resistor is found to be open, the voltage tripler and the load (including filter) circuit should be checked further to determine whether excessive load current, a defective rectifier, or a shorted capacitor has caused the resistor to act as a fuse and to open.

With the ac supply voltage removed from the output to the circuit and with the load (including filter circuit) disconnected from the load terminal of capacitor C2, resistance measurements can be made across the load to determine whether the load circuit (including filter components) is shorted. Measurements should be made across the terminals of charging capacitors C2 and C3 in the tripler circuit shown in part

A, or across charging capacitor C2 in the tripler circuit of part B or part C, to determine whether the no-output condition is caused by shorted capacitors. The tripler circuit shown in part A includes resistors R1 and R2; therefore, the resistance value measured across capacitors C2 and C3 will normally be something less than the value of the associated bleeder resistor. Since the charging capacitors are electrolytic capacitors, the resistance measurements will vary, depending upon the test-lead polarity of the ohmmeter. Therefore, two measurements must be made, with the test leads reversed at the capacitor terminals for one of the measurements, to determine the larger of the two resistance measurements. The larger resistance value is then accepted as the measured value. Capacitor C1 may be checked in a similar manner.

The rectifiers should be checked to determine whether they are open or otherwise defective. A relative check of rectifier condition can be made by use of an ohmmeter, as outlined in a previous paragraph of this section. However, failure of one or more rectifiers may be the result of other causes; therefore, tests of the filter and load circuit are necessary.

Low Output. The ac supply voltage should be measured at the input of the circuit to determine whether the voltage is the correct value, since a low applied voltage can result in a low output voltage.

Each rectifier (CR1, CR2, and CR3) should be checked to determine whether the low output is due to normal rectifier aging. A relative check of rectifier condition can be made by use of an ohmmeter, as outlined in a previous paragraph of this section. If the forward resistance of the rectifier increases, the output voltage will decrease. Also, if the reverse resistance decreases, the output voltage will decrease.

The load current should be checked to make sure that it is not excessive, because the voltage-tripler circuit has poor regulation and an increase in load current (decrease in load resistance) can cause a decrease in output voltage.

One terminal of each charging capacitor (C1, C2, and C3) should be disconnected from the circuit and each capacitor checked, using a capacitance analyzer, to determine its effective capacitance and leakage resistance. A decrease in effective capacitance or losses within the capacitor can cause the output of the voltage-tripler circuit to be below normal, since the defective capacitor will not charge to its normal operating value. If a suitable capacitance analyzer is not available, an indication of leakage resistance can

be obtained by use of an ohmmeter. First, disconnect one terminal of the capacitor from the circuit; then, using the ohmmeter procedure outlined for the no-output condition, make two measurements (reverse the test leads at the capacitor terminals for one of the measurements). The larger of the two measurements should be greater than 1 megohm for a satisfactory capacitor.

VOLTAGE QUADRUPLER (ELECTRON TUBE)

Application.

The voltage-quadrupler circuit is used to produce a higher dc output voltage than can be obtained from a conventional rectifier circuit utilizing the same input voltage. It is normally used in "transformerless" circuits where the load current is small and voltage regulation is not critical.

Characteristics.

Input to circuit is ac; output is pulsating dc.

DC output voltage is approximately four times the voltage obtained from a half-wave rectifier circuit utilizing the same input voltage; output current is relatively small.

Output requires filtering; dc output ripple frequency is either equal to or twice the ac source frequency, depending upon quadrupler circuit arrangement.

Has poor regulation characteristics; output voltage available is a function of load current.


Depending upon circuit application, may be used with or without a power or isolation transformer.

Uses indirectly heated cathode-type rectifiers.

Circuit Analysis.

General. The voltage-quadrupler circuit is used with or without a transformer to obtain a dc voltage from an ac source. As the term *voltage quadrupler* implies, the output voltage is approximately four times the input voltage. The voltage regulation of the voltage quadrupler is very poor as compared with the regulation of either the half-wave or the full-wave voltage doubler circuit. Assuming that a given voltage-multiplier (doubler, tripler, or quadrupler) circuit uses the same value of capacitors in each instance, the greater the voltage-multiplication factor of the circuit, the poorer will be the regulation characteristics. Because of the poor regulation characteristics of the voltage quadrupler, the use of the circuit is generally restricted to applications in which the load current is small and relatively constant.

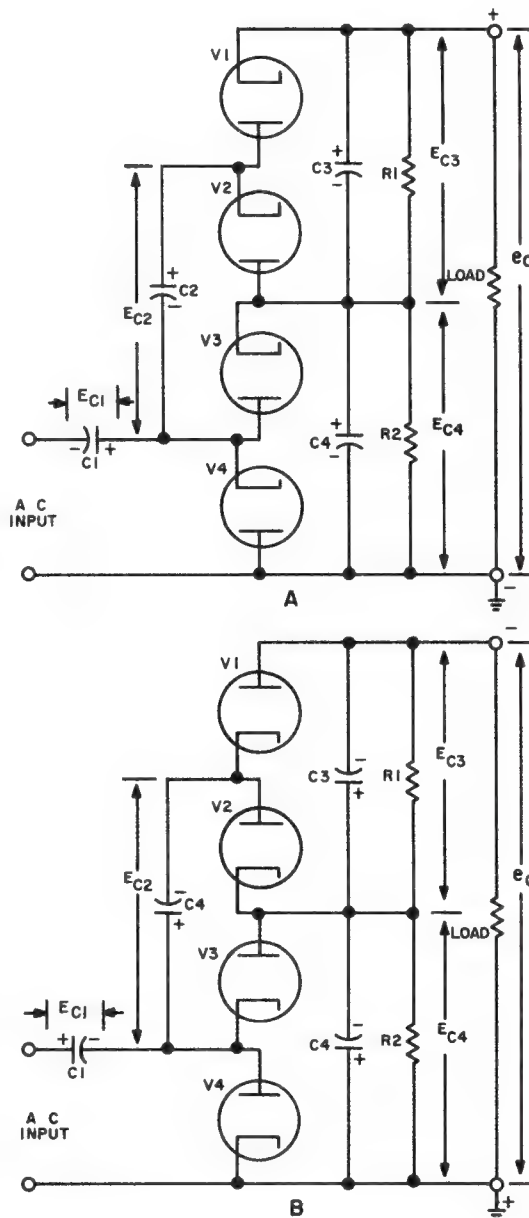Circuit Operation. Two basic voltage-quadrupler circuits are shown in the accompanying circuit schematic. Each circuit (part A or part B of the illustration) consists of two half-wave voltage doublers arranged so that the output of one doubler circuit is in series with the output of the other; thus, the total



Basic Cascade Voltage-Quadrupler Circuits

output voltage developed across the load resistance is approximately four times the applied voltage.

Rectifiers V3 and V4 and charging capacitors C1 and C4 form a conventional half-wave voltage-doubler circuit (the operation of the voltage-doubler circuit was previously described in this section). Rectifiers V1 and V2 and charging capacitors C2 and C3 form a second half-wave voltage-doubler circuit; however, this voltage-doubler circuit operates in cascade with the first voltage-doubler circuit and obtains its input from the voltage available across the series combination of charging capacitor C1, the applied ac input voltage, and charging capacitor C4.


Rectifiers V1, V2, V3, and V4 are identical-type diodes with indirectly heated cathodes. Because there are several possible filament circuit arrangements, the actual filament circuits are not shown on the schematic. It is necessary to isolate the rectifier filament circuits from each other because of the heater-to-cathode breakdown voltage limitation imposed by the rectifier tubes themselves; therefore, a filament transformer with separate well-insulated secondary windings, or a single transformer for each rectifier tube, is required. This requirement for an independent filament (heater) voltage source for each rectifier tube places a practical limitations on the use of electron tubes in voltage-multiplier circuits; for this reason, the voltage-quadrupler circuit and other voltage-multiplier circuits generally employ semiconductor diodes as rectifiers in lieu of electron-tube diodes.

Charging capacitors C1, C2, C3, and C4 are of equal capacitance and are usually relatively large (10 to 20 μf) for 50- to 60-hertz ac input; however, for some high-voltage, low-current applications, such as in the high-voltage supply for cathode-ray tube indicators, the charging capacitors may be relatively small (0.01 to 0.1 μf), especially if the ac input frequency is much higher than the normal 50- to 60-hertz input frequency.

Resistors R1 and R2 are equalizing resistors for charging capacitors C3 and C4, respectively; they are of equal value and are generally greater than 2 megohms. Resistors R1 and R2 are not necessary for circuit operation; however, when included in the circuit, they have a dual purpose—they tend to equalize the voltage across charging capacitors C3 and C4, and

they also act as bleeder resistors to discharge the capacitors when the circuit is de-energized.

The operation of the basic voltage-quadrupler circuit can be understood from the simplified circuits, part A, B, C, and D, given in the accompanying illustration. These simplified circuits are based upon the basic voltage-quadrupler circuit schematic (part A) given earlier in this discussion. The operation of a typical half-wave voltage-doubler circuit was described earlier in this section of the handbook; therefore, the discussion which follows will only briefly describe the circuit operation when two voltage-doubler circuits are arranged in cascade to obtain voltage-quadrupler action.

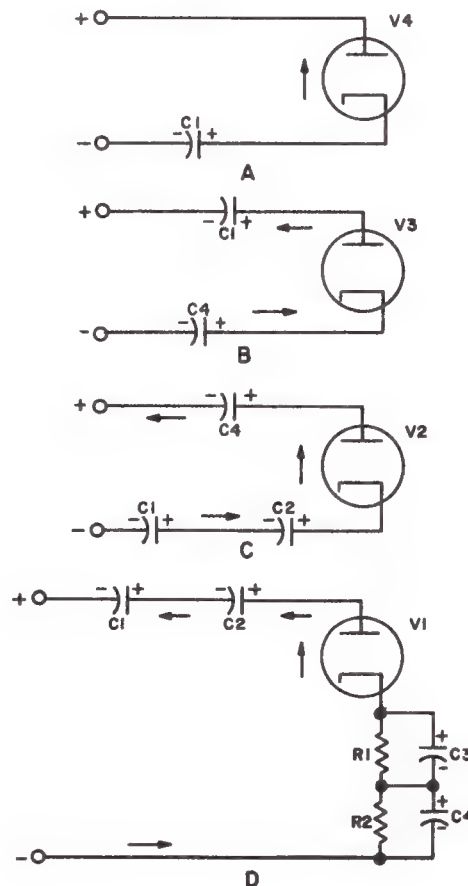


Voltage-Quadrupler Operation

Assume that the ac input to the voltage-quadrupler circuit (during the initial half-cycle) has the polarity indicated by the signs adjacent to the input terminals in part A of the accompanying illustration. Rectifier V4 conducts to charge capacitor C1 to the peak value of the applied ac input voltage. In part B of the illustration (during the next half-cycle) the applied voltage has the polarity indicated by the signs at the input terminals and is in series with the charge on capacitor C1 (E_{C1}); hence, rectifier V3 conducts to charge capacitor C4 to twice the peak value of the applied voltage and thereby discharge capacitor C1. In part C of the illustration, the applied voltage has the polarity indicated and is in series with the charge on capacitor C4 (E_{C4}) which causes rectifier V2 to conduct. This action charges capacitor C2 to twice the peak value of the input voltage, capacitor C1 to the peak value of the input voltage, and discharges capacitor C4 to zero. In part D of the illustration, the applied voltage has the polarity indicated and is in series with the charge on capacitor C1 (E_{C1}) and capacitor C2 (E_{C2}). At this time rectifier V1 conducts charging capacitors C3 and C4. Capacitors C3 and C4 are equal value capacitors and each will charge to twice the peak value of the applied voltage (ac input plus E_{C1} and E_{C2} .) Since C3 and C4 are in series, the dc voltage delivered to the load resistance is the sum of the voltage (E_{C3} plus E_{C4}) developed across capacitors C3 and C4. Because the voltage across each of these capacitors is equal to twice the applied voltage, the value of the dc output voltage is approximately four times the peak voltage of the ac input to the voltage-quadrupler circuit.

The dc output contains a rippler component; therefore, filtering is required to obtain a steady dc voltage. The frequency of the main component of the ripple voltage is equal to the frequency of the ac source because capacitors C3 and C4 simultaneously receive a charge, once for each complete cycle of the applied voltage. The value of the output voltage obtained from the voltage quadrupler is determined largely by the resistance of the load and the resulting load current. The regulation of the circuit is very poor; for this reason, if the output voltage is to be maintained at a high level, the load current must be kept small.

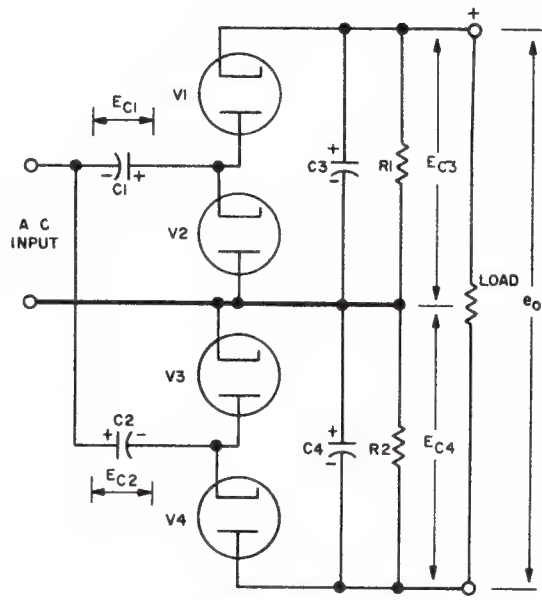The voltage-quadrupler circuit given in the accompanying circuit schematic is a variation of the basic cascade voltage-quadrupler circuits given earlier.



**Two Half-Wave Voltage-Doublers
Connected Back-to-Back To Form a
Voltage-Quadrupler Circuit**

In this circuit, two basic half-wave voltage-doubler circuits are arranged back-to-back; each doubler-circuit input is connected to the common ac source, and the two output voltages, E_{C3} and E_{C4} , are in series to produce the total output voltage, e_o . Rectifiers V1 and V2 and charging capacitors C1 and C3 form one doubler circuit; rectifiers V3 and V4 and charging capacitors C2 and C4 form the other doubler circuit. Each doubler circuit operates to charge its associated output capacitor (C3 or C4) to a value which is twice the peak value of the applied input voltage; as a result, the voltage produced across capacitors C3 and C4, in series, is four times the value of the applied input voltage. Because charging capacitors C3 and C4 receive a charge on alternate half-cycles of the applied input voltage, the ripple frequency for this quadrupler circuit is equal to twice the frequency of the ac source.

Once it is recognized that this quadrupler circuit consists of two complete half-wave voltage-doublers connected back-to-back sharing a common input input source and that measurements on each doubler

circuit may be made as though they were two independent circuits, then failure analysis becomes relatively simple. The circuit operation and failure analysis for each doubler circuit is identical to that given for the basic half-wave voltage-doubler circuit described earlier in this section of the handbook and, therefore, will not be discussed here.

The operation of these quadrupler circuits can be readily understood from a study of equivalent electron-tube circuit descriptions given previously in this section of the handbook. The action of the semiconductor rectifiers in the quadrupler circuit is essentially the same as that described for the equivalent electron-tube circuit. For these reasons, an explanation of circuit operation is not given here.

In the circuit shown in part A, charging capacitors C3 and C4 are in series across the load resistance, and each capacitor simultaneously receives a charge, once for each complete cycle of the applied voltage; as a result, the output ripple voltage has a frequency which is equal to the frequency of the ac source. In part B, charging capacitor C4 in parallel with the load resistance is charged only on alternate half-cycles of the applied ac voltage; therefore, the frequency of the ripple voltage is the same as the frequency of the ac source. In part C, charging capacitors C3 and C4 are in series across the load resistance, and the capacitors receive a charge on alternate half-cycles of the applied voltage; as a result, the output ripple voltage for this circuit has a frequency which is equal to twice the frequency of the ac source.

Since all three circuits described contain a ripple voltage, additional filtering is required to obtain a steady dc voltage. (Filter circuits are discussed in the Filter Section of this handbook.)

As stated previously, the regulation of the voltage quadrupler is relatively poor; the value of the output voltage obtained is determined largely by the resistance of the load and the resulting load current. If the load current is large, the output voltage is reduced accordingly.

Failure Analysis.

No Output. In the voltage-quadrupler circuit, the no-output condition is likely to be limited to one of several possible causes: the lack of applied ac voltage (including the possibility of an open surge resistor, R_s , or a defective step-up or isolation transformer), a shorted load circuit (including filter circuit com-

ponents), open charging capacitors (dependent upon circuit configuration) or defective rectifiers.

The failure analysis procedures for the no-output condition, such as voltage and resistance measurements, and capacitor and rectifier checks, etc, are essentially the same as those given for the voltage-tripler and voltage-doubler circuits described previously in this section of the handbook. Therefore, these procedures are not repeated here.

Low Output. The failure analysis procedures for the low-output condition consist of voltage, resistance, and load-current measurements, capacitor and rectifier checks, etc. These procedures are essentially the same as the procedures given for the voltage-tripler circuit described previously, and are somewhat similar to those given for the half-wave voltage-doubler circuit described earlier in this section of the handbook.

Failure Analysis.

No Output. In the voltage-quadrupler circuit, the no-output condition is likely to be limited to one of the following possible causes: the lack of filament voltage or an open filament in two or more rectifiers, the lack of applied ac voltage, a shorted load circuit (including filter circuit components), or an open in one or both of the charging capacitors, C1 and C2.

The failure analysis procedures for the no-output condition are essentially the same as those given for the voltage-tripler and half-wave voltage-doubler circuits described previously in this section of the handbook.

Low Output. The failure analysis for the low-output condition is essentially the same as that given for the voltage-tripler circuit described previously and is somewhat similar to that given for the half-wave voltage-doubler circuit described earlier in this section of the handbook.

VOLTAGE QUADRUPLER (SEMICONDUCTOR)

Application.

Same application as the electron tube version.

Characteristics.


Same characteristics as the electron tube version except that it uses four semiconductor rectifiers

(single, multiplier, or stacked units) instead of electron tubes.

Circuit Analysis.

General. The voltage-quadrupler circuit is used with or without a transformer to obtain a dc voltage from an ac source. As the term voltage *quadrupler* implies, the output voltage is approximately four times the input voltage. The voltage regulation of the voltage quadrupler is very poor as compared with the regulation of either the voltage-doubler or voltage-tripler circuit. Assuming that a given voltage-multiplier (doubler, tripler, or quadrupler) circuit uses the same value of capacitors in each instance, the greater the voltage-multiplication factor of the circuit, the poorer will be regulation characteristics. Because of the poor regulation characteristics of the voltage quadrupler, the use of the circuit is generally limited to applications in which the load current is small and relatively constant.

Circuit Operation. Three voltage-quadrupler circuits are shown in the accompanying illustration. The schematic of part A shows a basic cascade voltage-quadrupler circuit; fundamentally, this circuit consists of two voltage doublers whose outputs are in series. The schematic of part B shows a circuit arrangement which is a variation of that given in part A. The schematic of part C is a quadrupler circuit consisting of two complete half-wave voltage-doublers connected back-to-back and sharing a common ac input. The circuits shown in parts A and B have the negative output terminal common to one side of the ac source; both of these circuits can be arranged to have the positive output terminal common to one side of the ac source by simply reversing the connections to each rectifier (CR1 through CR4) and to each charging capacitor (C1 through C4).

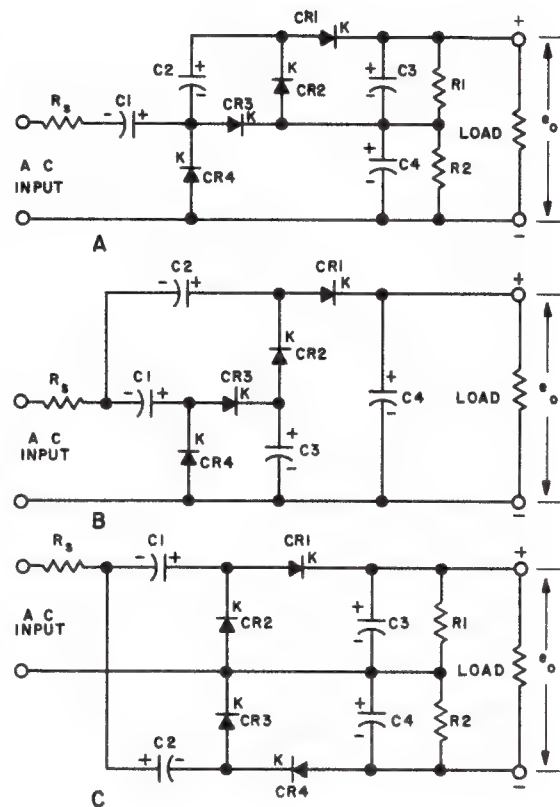

Voltage-Quadrupler Circuits

The rectifiers, CR1, CR2, CR3, and CR4, are identical-type semiconductor diodes in each of the three circuits illustrated. Charging capacitors C1, C2, C3, and C4 are of equal capacitance value in each of the three circuits; however, because of the differences

in the voltages developed across individual capacitors in a particular circuit, the voltage ratings of the capacitors will differ. In the circuit of part A, the voltage rating of capacitors C3 and C4 is the same for each capacitor; the voltage rating of capacitor C2 is less than that of C3 or C4, and the rating of capacitor C1 is less than that of C2. In part B, the voltage rating of capacitors C2 and C4 is the same for each capacitor; the rating of C3 is less than that of C2 or C4, and the rating of C1 is less than that of C3. In part C, the voltage rating of capacitors C3 and C4 is the same for each capacitor, and the rating of capacitors C1 and C2 is the same for each capacitor; however, the rating of capacitors C1 and C2 is less than that of C3 and C4.

Equalizing resistors R1 and R2, shown in the circuits of parts A and C, are not necessary for circuit

operation; however, when they are included in the circuit, resistors R1 and R2 equalize the voltages developed across capacitors C3 and C4, respectively, and also act as a bleeder to discharge the capacitors when the circuit is de-energized. A surge resistor, R_s , is placed in series with the ac source to limit the peak current in the rectifier circuit.

One disadvantage common to all three quadrupler circuits illustrated is that neither dc output terminal can be directly connected to ground or to the chassis; however, when a step-up or isolation transformer is used to supply the input to any one of these quadrupler circuits, either output terminal may be connected to ground or to the chassis. Furthermore, if a transformer is used and if there is sufficient resistance in the secondary winding, the surge resistor, R_s , may be omitted.

PART 2-4. DC-TO-DC CONVERTERS

DC-TO-DC CONVERTER, AUDIO OSCILLATOR TYPE (ELECTRON TUBE)

Application.

The audio-oscillator type dc-to-dc converter is used in electronic equipment for applications requiring extremely high-voltage dc at a small load current. The output circuit can be arranged to furnish negative or positive high voltage to the load. The supply is commonly used to provide the high voltage for accelerating and final anodes, ultor (element with highest voltage) and other similar electrodes of cathode-ray tubes used in indicators. It is sometimes used as a keep-alive voltage source in radar equipment.

Characteristics.

Uses a self-excited oscillator circuit combined with a full-wave voltage doubler circuit.

Typical operating frequency is between 400 to 3000 Hz.

Output is high-voltage dc at low current.

Regulation is fair; may be improved by regulating oscillator dc supply voltage.

The rectifier circuit can be arranged to provide either positive- or negative-polarity output voltage.


Circuit Analysis.

General. The audio-oscillator type dc-to-dc converter is a self-excited oscillator operation in the audio-frequency range. The oscillator generates a voltage which is either sinusoidal or square wave in form, depending upon the circuit design. The rectifier circuit used in conjunction with the oscillator circuit is commonly a half-wave rectifier or a full-wave voltage-doubler circuit and uses either electron tubes or semiconductor diodes as rectifiers. The dc output filter component values are determined by the desired output impedance of the high-voltage supply and by the frequency of the applied ac generated by the oscillator circuit. In most cases, the output impedance is given first consideration in the design of the filter circuit, rather than the reduction or elimination of the ripple-frequency component from the dc output.

The dc output of a self-excited oscillator supply under a given load, such as the load offered by a cathode-ray tube circuit, can be maintained nearly as constant as the dc source supplying the oscillator circuit. For this reason, it is desirable to provide the

oscillator circuit with a regulated supply voltage which approaches ± 1 percent so that the output voltage can be maintained reasonably constant for a given load current.

Circuit Operation. The accompanying circuit schematic illustrates a push-pull, self-excited oscillator circuit used in conjunction with a full-wave voltage-doubler circuit to obtain high-voltage output. The operation of the self-excited, push-pull oscillator is essentially the same as that described in the Oscillator Section of this handbook; the operation of a typical full-wave voltage-doubler circuit has already been described in this section of the handbook. For these reasons, the discussion which follows will be somewhat limited because the circuit is a combination of two basic circuits discussed elsewhere in this handbook.

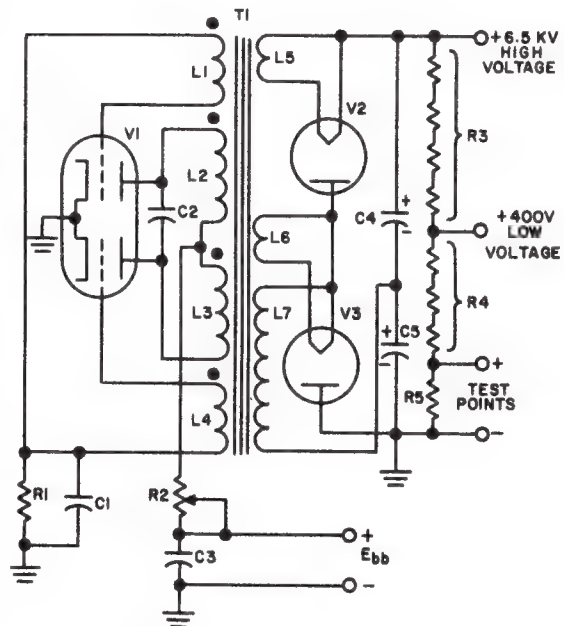

DC-TO-DC CONVERTER, Audio-Oscillator
Type Using Twin-Triode Tube

Electrode tube V1 is a twin-triode, such as the type 5670 or 6J6; if desired, two identical-type triode tubes may be used in this circuit in lieu of the single twin-triode. Electron tubes V2 and V3 are identical diodes using directly-heated cathodes, such as the type 1B3, 1V2, or 1X2, and are specifically

designed for high-voltage applications. The parallel combination of resistor R1 and capacitor C1 is used to obtain operating (grid-leak) bias for the self-excited oscillator circuit. Transformer T1 is the oscillator and high-voltage transformer; in the schematic the dots adjacent to windings L1, L2, L3, and L4 are used to indicate similar winding polarities. Windings L1 and L4 are the push-pull oscillator grid windings, and windings L2 and L3 are plate windings. Capacitor C2 forms a resonant circuit with the inductance of windings L2 and L3 to determine the frequency of oscillation. Transformer windings L5 and L6 supply the filament current to the diodes, V2 and V3, respectively. Although windings L5 and L6 are shown as part of transformer T1, a separate filament transformer with independent, well-insulated windings is sometimes used as the filament supply. (A filament supply is not necessary when semiconductor diodes are used in the rectifier circuit, and windings L5 and L6 may be omitted.) Transformer winding L7 is the high-voltage (step-up) winding and is the ac source for the rectifier circuit. Depending upon the design of the transformer and the circuit constants used, the oscillator circuit generates a sinusoidal waveform at the high-voltage winding, or, if the circuit operates in a switching mode, it generates a square wave.

Capacitor C3 and variable resistor R2 form a decoupling filter to prevent interaction between the oscillator circuit and the dc supply. Resistor R2 is also used to vary the dc potential applied to the oscillator circuit. A change in the applied voltage affects the amplitude of the voltage across winding L7 which is applied to the rectifier circuit; therefore, the setting of resistor R2 determines the high-voltage output within certain limits and may be adjusted to obtain a predetermined output voltage.

Capacitors C4 and C5 are the charging capacitors of the voltage-doubler circuit. Since the frequency of the applied voltage is in the audio range and the load current is small, the value of these capacitors is relatively small. Resistors R3, R4, and R5 in series form a bleeder and a voltage-divider resistance for the output of the doubler circuit. The tap at the junction of resistors R3 and R4 enables a lower voltage to be supplied to a low-current load, such as the lower-


voltage electrodes of a cathode-ray tube. In actual practice, resistors R3 and R4 are made up of a number of resistors in series to obtain the desired value of total resistance for each portion of the bleeder (R3 and R4). To prevent failure, the voltage drop across each resistor must be less than the maximum terminal-voltage rating of the resistor.

Resistor R5 is used for test metering purposes, to permit measurement of the high-voltage dc output without the requirement for a special voltmeter or high-voltage probe. A precalculated voltage drop across R5, when read with a high-resistance voltmeter, will indicate the presence of the correct value of high voltage.

In general, the output-voltage regulation of this supply is sufficient for most cathode-ray-tube circuit applications since the stability of the output voltage can be held to ± 1 percent by regulating the dc supply voltage applied to the oscillator circuit.

The oscillator circuit using a twin-triode tube offers several advantages; its efficiency is relatively high and it requires fewer parts than does a comparable circuit which uses a single pentode. Furthermore, the reliability of the twin-triode oscillator circuit is better than that of a comparable pentode circuit, because it has the ability to oscillate even after failure of one triode section of the tube. If a failure of this nature should occur at a time when continued operation is vital to the mission, sufficient voltage will normally be available to sustain emergency operation with reduced efficiency until corrective maintenance can be performed.

The accompanying circuit schematic illustrates a single pentode used in a self-excited oscillator circuit to produce a sinusoidal voltage. The oscillator is fundamentally a series-fed Hartley oscillator with grid stabilization; the operation of this circuit is similar to that of the conventional Hartley oscillator described elsewhere in this handbook. The rectifier circuit commonly used with the pentode oscillator is a full-wave voltage doubler and employs neither electron tubes or semiconductor diodes as rectifiers; however, the schematic does not show the associated rectifier circuit because it can be the same as that illustrated for the twin-triode oscillator given earlier in this discussion.

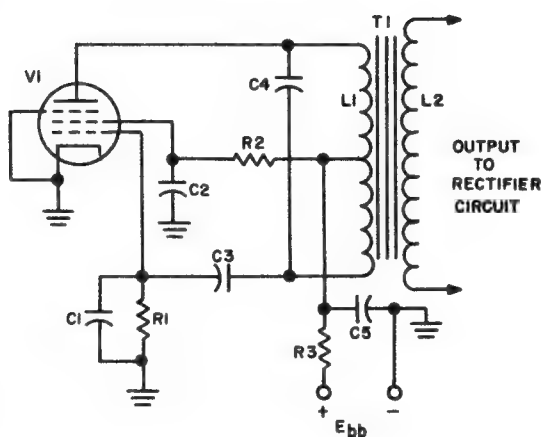

**DC-to-DC Converter, Audio-Oscillator
Type Using Pentode Tube**

Electron tube V1 is a pentode such as the type 5763. The parallel combination of resistor R1 and capacitor C1 is used to obtain operating bias for the self-excited oscillator circuit. Transformer T1 is the oscillator and high-voltage transformer. In this transformer, winding L1 is tapped for the series-fed oscillator circuit and is in parallel with capacitor C4 to determine the resonant frequency of the oscillator. Winding L2 is the high-voltage winding and is the ac source for the rectifier circuit. (The pentode oscillator circuit generates a sinusoidal waveform.) Although not shown, if electron-tube diodes are used in the rectifier circuit, additional windings may be required to supply the rectifier filament current. Capacitor C3 couples the grid of V1 to the grid-winding portion of L1 and also acts as a dc blocking capacitor. Capacitor C2 is the screen bypass, and resistor R2 is the screen-dropping resistor. Capacitor C5 and resistor R3 form a decoupling filter; capacitor C5 also returns the tap of winding L1 to signal ground (cathode) potential.

The pentode oscillator circuit found in various equipments may differ somewhat from the circuit given in the accompanying schematic. Several typical variations are as follows: A small capacitor may be connected between the control grid and the plate of V1 to increase the grid-to-plate capacitance and thus provide additional feedback to sustain oscillator; a resistance may be placed in series with capacitor C3

to help stabilize the circuit and limit the amplitude of oscillations; and a variable resistor may be placed in series with either screen-dropping resistor R2 or decoupling resistor R3 to permit adjustment of the screen voltage or both the plate and screen voltages. A change in the applied oscillator voltage(s) will affect the output amplitude of the oscillator and will therefore affect the high-voltage output of the supply.

Failure Analysis.

General. The audio-oscillator type dc-to-dc converter consists of two basic circuits—an oscillator and a rectifier. It must be determined initially whether the oscillator or the rectifier portion of the power-supply circuit is at fault. Tests must be made to determine whether the oscillator is performing satisfactorily; if it is, the trouble is then assumed to be located within the associated rectifier circuit. The failure analysis outlined in the following paragraphs is somewhat brief because the subject of electron-tube oscillators is discussed in another section of this handbook; furthermore, the particular high-voltage rectifier circuit may be the same as one of the rectifier circuits described earlier in this section. Since the audio-oscillator type dc-to-dc converter is a combination of two basic circuits, information concerning failure analysis for either portion of the high-voltage supply can be obtained by reference to the applicable basic circuit given elsewhere in this handbook.

No Output. When the oscillator is in a nonoscillating condition, negative grid voltage will not be developed across R1C1, and the measured plate (and screen) voltage of oscillator tube V1 will be below normal. The applied filament and plate (and screen) voltages should be measured to determine whether these voltages are present and of the correct value. The oscillator tube V1 should be checked to determine if it is defective. Excessive losses in the L-C resonant circuit formed by the transformer and its associated capacitor will prevent sustained oscillation; the transformer windings should be checked for continuity, and the associated capacitor should be checked to determine whether it is open or shorted. Shorted capacitor in the circuit will prevent oscillation; therefore, all capacitors should be checked with a suitable capacitance analyzer to determine whether they are satisfactory. An open transformer winding

would normally prevent sustained oscillations, however, in the twin triode oscillator circuit, there is a possibility that one coil could resonate with stray capacity and oscillate (at a higher frequency) and produce a low output.

If the oscillator circuit is found to be functioning normally, then it must be assumed that the trouble is associated with the rectifier circuit or its load, and a check of the rectifier circuit must be made in accordance with the procedures outlined earlier in this section for the applicable rectifier circuit.

Low Output. A relative indication of oscillator output can be obtained by measuring the amount of bias voltage developed across R1C1. A value of bias which is below normal is an indication of low oscillator output. Also, if the applied plate (and screen) voltage is below normal, a reduction in output will occur. The applied filament and plate (also screen) voltages should be measured to determine whether they are within tolerance; a 10-percent variation in applied filament voltage will not appreciably affect the output of the supply, but a small change in applied plate voltage will produce a noticeable change in output.

In the twin-triode oscillator circuit, trouble in one triode section (such as low cathode emission, low transconductance, or an open tube element) or an open winding in transformer T1 will cause a reduction in output. Continuity measurements of the windings of transformer T1 can be made to determine whether any of the windings are open. In the pentode oscillator circuit a leaky screen bypass (C2) will form a voltage divider with the screen-dropping resistor (R2) and a result in a decreased screen voltage; thus, the output of the supply will be low.

If the oscillator is found to be operating normally, a defect within the rectifier circuit or associated load must be suspected as the cause of low output. For example, because of the relatively high-impedance rectifier and filter circuits, an excessive load current can cause the output voltage to be low. Failure analysis procedures for typical rectifier circuits used in high-voltage supplies are outlined earlier in this section.

DC-TO-DC CONVERTER, SQUARE-WAVE (AUDIO) OSCILLATOR TYPE (SEMICONDUCTOR)

Application.

Same application as electron tube audio oscillator type.


Characteristics.

Same characteristics as electron tube audio oscillator type, except that typical operating frequency is between 400 and 2000 Hz.

Circuit Analysis.

General. The square-wave oscillator type dc-to-dc converter includes a self-excited oscillator which has an operating frequency in the range between 400 and 2000 Hertz. The oscillator circuit operates most efficiently as a square-wave generator with the transistors functioning as high-speed switching elements. The transistors provide a form of astable, or free-running, multivibrator circuit; the action can be compared to the switching action which occurs with a mechanical vibrator in a nonsynchronous vibrator supply. The oscillator circuit is frequently referred to as a saturable core square-wave oscillator. The square-wave output from the oscillator circuit may be stepped up or down and rectified to provide a dc voltage higher or lower than the input voltage. The circuit described here is used in conjunction with a full-wave voltage-doubler circuit to obtain high-voltage dc. Because of the square-wave output and the relatively high frequency of oscillation, very little filtering is required to eliminate the ripple voltage from the output; this is especially true when a full-wave rectifier circuit is used.

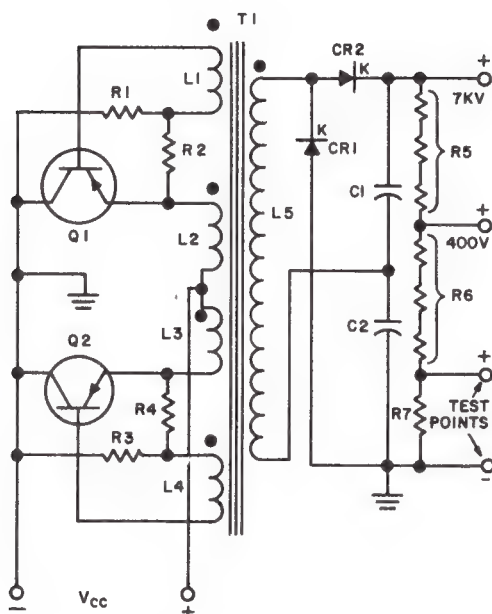Circuit Operation. The accompanying circuit schematic illustrates a push-pull, self excited oscillator circuit used in conjunction with a full-wave voltage-doubler circuit to obtain a high-voltage output. The discussion which follows is limited to the oscillator circuit, since the operation of a typical full-wave voltage-doubler circuit has been described earlier in this section of the handbook.



DC-to-DC Converter, Square-Wave Oscillator Type
Using PNP Power Transistors

Transistors Q1 and Q2 are identical PNP, alloy-junction type, power transistors. The power transistors used in this common-emitter circuit configuration normally have the collector connected to the case or shell of the transistor; thus, the circuit shown here permits the collectors to be in physical and electrical contact with a metal chassis or a grounded heat sink. Rectifiers CR1 and CR2 are identical semiconductor diodes; although the schematic shows only two rectifiers in the voltage-doubler circuit, each graphic diode symbol represents two or more diodes in series to obtain the necessary peak-inverse characteristics for high-voltage operation in the voltage-doubler circuit.

Transformer T1 provides the necessary regenerative feedback coupling from the emitter to the base of the power transistors, Q1 and Q2, and is also the source of high voltage for the rectifier circuit. Transformer windings L2 and L3 are emitter windings; L1 and L4 are the feedback, or base, windings. The load for the transistors is formed by windings L2 and L3 connected between the emitters and the

voltage source. Transformer winding L5 is the high-voltage (step-up) winding, and is the ac source for the voltage-doubler circuit. In the schematic, the dots adjacent to the transformer windings are used to indicate similar winding polarities.


Resistors R1 and R2 form a voltage divider to provide forward-bias voltage for the base of transistor Q1, in like manner, resistors R3 and R4 establish the bias for the base of transistor Q2. Separate voltage dividers are used in this push-pull circuit to provide an independent base-voltage source for each transistor and thereby increase the reliability of the circuit. In the event of failure of one transistor, such as an open circuit in one of the transistor junctions, the independent base-biasing arrangement enables the remaining transistor of the oscillator circuit to continue operation at reduced efficiency, and the dc output of the power supply is reduced accordingly.

Capacitors C1 and C2 are the charging capacitors of the voltage-doubler circuit. Since the frequency of the applied voltage is generally between 400 and 2000 Hz, the value of these capacitors is relatively small, usually between 5600 pf and 0.02 μ f. Resistors R5, R6, and R7 in series form a bleeder and voltage-divider resistance for the output of the doubler circuit. The tap at the junction of resistors R5 and R6 enables a low voltage to be supplied to a low-current load, such as the lower-voltage electrodes of a cathode-ray tube. In actual practice, resistors R5 and R6 are made up of a number of resistors in series to obtain the desired value of total resistance for each portion of the bleeder (R5 and R6). To prevent failure, the voltage drop across each resistor must be less than the maximum terminal-voltage rating of the resistor.

Resistor R7 is used as a shunt resistor for test metering purposes, to permit measurement of the high-voltage dc output without the requirement for a special voltmeter or high-voltage probe. The test points located at each end of R7 permit a low-resistance microammeter to be connected across the resistor; in this case the bleeder resistance (R5 and R6) is used as a series multiplier for the test microammeter. When this test circuit is employed, the high-voltage output can be calculated by using Ohm's law, once the bleeder current is determined by measurement and the total resistance of R5 and R6 is known. As an alternative, an electronic voltmeter can be connected to the test points, to measure the voltage drop

across R_7 ; the output voltage can then be calculated by taking into account the voltage division provided by the bleeder resistance. In other cases, a predetermined (calculated) voltage drop across R_7 , when measured by use of a high-resistance voltmeter, will indicate the presence of the correct value of high-voltage output.

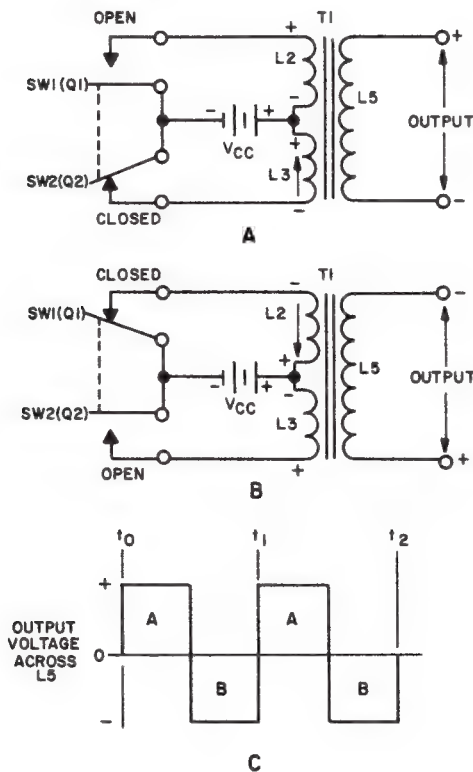The operation of transistors functioning as high-speed switching elements can be understood by reference to the accompanying illustration below for a fundamental switching circuit. The reference designations used for the windings of transformer T_1 in the illustration correspond to those used in the schematic given earlier in this discussion.



Fundamental Switching Circuit and Resulting Output Waveform

The switching action, such as occurs with a mechanical vibrator, is represented in the simplified schematic by ganged switches SW_1 and SW_2 , mechanically linked together so that when one switch is

closed, the other switch is opened. When switch SW_1 is open (transistor Q_1 cut off), switch SW_2 is closed (transistor Q_2 conducting heavily), as shown in part A of the illustration, and heavy current flows in transformer winding L_3 . When the switches are reversed, as shown in part B, switch SW_1 is closed (Q_1 conducting heavily) and switch SW_2 is open (Q_2 cut off); thus, heavy current flows in winding L_2 . The polarities of the voltages produced across the primary and secondary windings are as indicated in parts A and B of the illustration. Assuming a rapid rate of switching, the resulting output voltage developed across secondary winding L_5 is essentially a square waveform, as shown in part C.


Bias and stabilization techniques employed for a transistor oscillator are essentially the same as those employed for a transistor amplifier. The grounded-collector, common-emitter configuration illustrated earlier in the discussion utilizes a single-battery power source; as mentioned previously, this dc source produces the required bias voltages through the voltage-divider action of resistors R_1 and R_2 , and resistors R_3 and R_4 . Since the connector is at negative (ground) potential and the emitter is at a positive potential, each pair of resistors form a voltage divider to place the base of the associated transistor as a negative potential with respect to its emitter; the required forward bias for the PNP transistor is thereby established.

The square-wave oscillator can be compared to an amplifier with feedback of the proper phase and amplitude. In the PNP transistor schematic given earlier, feedback is obtained by transformer coupling from the emitter to the base in order to sustain oscillations; the feedback signal must be in phase with the emitter signal. If NPN transistors are used in the oscillator circuit, the polarity of the supply voltage must be opposite to that indicated in the schematic; however, for either type of transistor the feedback signal must be in phase with the emitter signal.

When dc power is first applied to the circuit, the current which flows through each primary winding, L_2 and L_3 , is initially determined by the effective resistance offered by transistors Q_1 and Q_2 , and their associated bias resistors R_1 and R_2 and resistors R_3 and R_4 . The push-pull circuit appears to be balanced, since each half of the circuit is identical to the other; however, there will always be minor differences in circuit resistance and within the transistors themselves. As a result of this inherent unbalance, the

initial current in one primary winding of transformer T1 does not exactly equal the initial current in the other. It is this unequal current flow in primary windings L2 and L3 which starts the oscillation in a manner which is typical of free-running multivibrators or relaxation oscillators.

In order to compare the action of the square-wave oscillator with the action of the fundamental switching circuit, assume that more current flows through primary winding L3 than flows through primary winding L2 because of the circuit unbalance mentioned previously. As emitter-current flow increases through winding L3, a voltage is induced in the feedback (or base) winding, L4. This voltage is in phase with the voltage produced across winding L3. The induced voltage across L4 effectively increases the forward bias, and transistor Q2 rapidly approaches saturation. As this regenerative process continues, core saturation is eventually reached; at this time no further increase in the emitter current through L3 can occur, and the effective inductance of the transformer windings decreases. The flux in the core of transformer T1 during this period has changed from point O to point A on the hysteresis curve, as shown in the accompanying illustration.

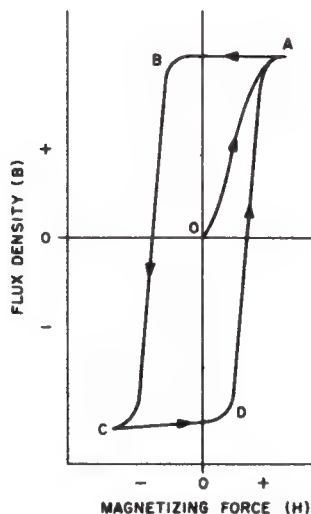

Core Hysteresis Curve

During the interval the transistor Q2 is approaching saturation, voltage is induced in winding L1 by the resultant field of L2 and L3. This induced voltage is in opposition to the initial voltage developed when the dc supply voltage was first applied to the circuit. As a result of the action occurring in the circuit associated with transistor Q2, the voltage across winding L1 causes the base of transistor Q1 to approach a condition of reverse bias. The emitter current of transistor Q1 decreases rapidly, and Q1 reaches cutoff because the feedback from winding L1 has driven the base of Q1 to a condition of reverse bias. Since no further increase or change in current through L3 occurs, the base of transistor Q2 is no longer driven by a voltage from L4, and it starts to return to the normal (forward) bias condition. Also, the magnetic flux developed in the core of T1 starts to decrease to point B on the hysteresis curve. Consequently, the voltage induced in L4 starts to drive the base of Q2 to a reverse bias condition. The emitter current of transistor Q2 decreases rapidly and Q2 finally reaches cutoff. As a result of this regenerative process, the magnetic flux developed in the core rapidly changes from point B on the hysteresis curve. At the same time, transistor Q1 receives a signal from L1 and its base is driven toward the forward bias condition. Q1 conducts heavily, causing the flux in the core to reach point C. During the interval when transistor Q1 is at saturation, no further change in the current through winding L2 occurs; thus, the base of transistor Q1 is no longer driven by a voltage from L1, and it starts to return to the normal (forward) bias condition. Also, the magnetic flux developed in the core of T1 starts to decrease to point D on the hysteresis curve. Consequently, the voltage induced in L1 starts to drive the base of Q1 to a reverse bias condition.

The emitter current of transistor Q1 decreases rapidly, and Q1 finally reaches cutoff. As a result of this regenerative process, the flux developed in the core rapidly changes from point D on the hysteresis curve. At the same time, transistor Q2 receives a signal from winding L4, and its base is driven into the forward bias condition. Q2 conducts heavily, causing the flux in the core to reach point A once again. At this time, transistor Q2 is at saturation (point A on the hysteresis curve) and transistor Q1 is cut off; the cycle is now complete and ready to be repeated.

The output frequency and secondary voltage are determined by the turns ratio of the transformer windings and by the saturation flux of the core. The core laminations of transformer T1 are usually made of nickel-iron or other material exhibiting similar magnetic characteristics. The nickel-iron material has a high permeability and a square-loop hysteresis curve, which is ideal for use with transistors operating in a switching mode. The transistors, functioning as high-speed switches, operate alternately from cutoff to saturation; when this action is combined with the flux characteristics of the transformer core, the output voltage produced is essentially a square wave. This is because the core flux changes rapidly at a relatively constant rate from point B to point C and from point D to point A on the hysteresis curve.

The output-voltage regulation of this high-voltage supply is sufficient for most cathode-ray-tube circuit applications without additional circuitry, especially if the dc input supply voltage is regulated. The output-voltage stability could be improved somewhat by the use of a regulator in the collector circuit of the transistors, but the added regulator circuit would become rather complex if stability better than that already provided by the circuit were to be obtained.

The transistorized push-pull oscillator circuit offers several advantages; its efficiency is relatively high, the physical size of the supply is small and much of the circuit can be encapsulated, and the grounded-collector configuration simplifies the method used to dissipate heat developed by the transistors. Furthermore, the circuit has the ability to continue to operate, but with reduced output, even though an open circuit develops in one of the transistors. If a failure of this nature occurs at a time when continued operation is vital to the mission, sufficient output voltage will normally be available to sustain emergency operation until corrective maintenance can be performed. With such a failure, the cathode-ray-tube indicator brilliance is likely to decrease somewhat, and an increase in deflection may be noticed.

Failure Analysis.

General. The square-wave oscillator type dc-to-dc converter consists of two basic circuits - a push-pull oscillator and a voltage doubler. It must be determined initially whether the oscillator or the voltage-doubler portion of the power-supply circuit is at fault. Tests must be made to determine whether the

oscillator is performing satisfactorily, if it is, the trouble is then assumed to be located within the associated voltage-doubler circuit. The failure analysis outlined in the following paragraphs is somewhat brief because the subject of oscillators is discussed in another section of this handbook; furthermore, the voltage-doubler circuit is described earlier in this section. Since the square-wave oscillator type high-voltage supply is a combination of two basic circuits, additional information concerning failure analysis for either portion of the high-voltage supply can be obtained by reference to the applicable basic circuit given elsewhere in this handbook.

No Output. The dc input voltage, V_{cc} , should be measured to determine whether it is present and of the correct value.

The push-pull oscillator can be quickly checked to determine whether it is oscillating by using an oscilloscope to observe the emitter-to-collector waveform at each transistor. When the push-pull oscillator is functioning normally, the emitter-to-collector waveform is essentially a square wave having a peak-to-peak amplitude which is approximately equal to twice the value of the dc input voltage, V_{cc} .

Each biasing resistor should be disconnected and, using an ohmmeter, the value of each resistor should be measured to determine whether the resistor is within tolerance. If the values of the biasing resistors (R1 through R4) change appreciably, it is likely that the forward bias will change for the associated transistor; if the forward bias increases, such a condition may cause thermal runaway, with eventual damage to the transistor(s) and failure of the circuit to oscillate. Thus, with one transistor conducting heavily or with a shorted junction within the transistor, the resulting current flow in the windings of transformer T1 will cause the effective inductance to be decreased; the core may reach saturation, in which case the circuit will not oscillate because of the loading on the circuit caused by the defective transistor.

Any defect in transformer T1, such as an open base or emitter winding, or shorted turns in any of the windings, will prevent the circuit from operating properly, since oscillations in each half of the circuit depend upon regenerative feedback from the transformer.

A shorted secondary circuit, reflected to the emitter and base windings, may cause excessive losses which will prevent sustained oscillations. Also, if the

high-voltage winding, L5, should open, the circuit will continue to oscillate; however, no output will be obtained from winding L5 for the input to the voltage-doubler circuit.

If the oscillator circuit is found to be functioning normally, then it must be assumed that the trouble is in the voltage-doubler circuit or its associated load, and a check of the rectifier circuit must be made in accordance with the procedures outlined earlier in this section for the applicable rectifier circuit.

Low Output. The dc input voltage, V_{cc} , should be measured to determine whether it is of the correct value.

If one transistor should develop an open circuit in one of its junctions, the high-voltage output will decrease (for a given load current), and the peak-to-peak amplitude of the ripple voltage will increase. Because of the independent base-biasing arrangement, the remaining good transistor will continue to oscillate. Under these conditions the transformer core may not reach saturation. In this case there will be a reduction in the efficiency of the circuit, together with an accompanying decrease in the output voltage; furthermore, the oscillator frequency will increase to two or three times the normal operating frequency when only one transistor is operating. A calibrated oscilloscope can be used to observe the emitter-to-collector waveform at each transistor. If the oscillator is functioning normally, the emitter-to-collector waveform is essentially a square wave having a peak-to-peak amplitude which is approximately equal to twice the value of the dc input voltage, V_{cc} . However, if only one transistor is functioning and the other transistor has an open circuit in one of its junctions, the emitter-to-collector waveform will not resemble a square wave on both halves of the cycle; instead it will resemble a square wave for one half-cycle and a trapezoid for the other half-cycle. As mentioned previously, the frequency of oscillation will be higher than normal under these conditions.

If the oscillator circuit is found to be operating normally, a defect within the voltage-doubler circuit or associated load must be suspected as the cause of low output. For example, because of the relatively high-impedance rectifier and filter circuits, an excessive load current can cause the output voltage to be low. Failure analysis procedures for typical rectifier circuits used in high-voltage supplies are outlined earlier in this section.

DC-TO-DC CONVERTER, R-F OSCILLATOR TYPE (ELECTRON TUBE)

Application.

The r-f oscillator type high-voltage supply is used in electronic equipment for applications requiring extremely high-voltage dc at a small load current. The output circuit can be arranged to furnish negative or positive high voltage to the load. The supply is commonly used to provide the high voltage for the accelerating and final anodes, the ultor (element with highest voltage), and other similar electrodes of cathode-ray tubes used in video indicators.

Characteristics.

Uses a self-excited r-f oscillator circuit combined with a voltage doubler circuit.

Typical operating frequency is between 40 and 600 kilohertz.

Output is high-voltage dc at low current.

Regulation is poor; may be improved considerably by additional circuitry to control the oscillator output.

The rectifier circuit can be arranged to provide either positive- or negative-polarity output voltage.

Circuit may require shielding to prevent undesirable radiation from interfering with other equipments.


Circuit Analysis.

General. The r-f oscillator type high-voltage supply is a self-excited oscillator operating in the low- and medium-frequency range. The oscillator generates a sinusoidal output which is coupled through the air-core step-up transformer to the high-voltage rectifier circuit. Sometimes two identical oscillator tubes are connected in parallel to increase the current output capability of the supply over that obtainable with single-tube operation. The rectifier circuit used in conjunction with the oscillator circuit is commonly a half-wave rectifier or a voltage-doubler circuit. The rectifier circuit may employ either electron-tubes or semiconductor diodes as rectifiers.

The dc output from the r-f oscillator high-voltage supply is subject to considerable variation with a change in load current, and, therefore, because of its poor regulation characteristics, the use of this circuit is usually limited to applications where the load is

constant. Although the regulation characteristics of the supply can be improved considerably by the addition of regulator circuits to control the oscillator output, the additional circuitry required in some cases makes it impracticable to do so because of the added space, weight, number of components, etc.

Circuit Operation. The accompanying circuit schematic illustrates a self-excited pentode power oscillator used in conjunction with a full-wave voltage-doubler circuit to obtain high-voltage dc output. The oscillator is fundamentally a series-fed tuned-plate, untuned-grid (tickler) oscillator circuit. The operation of the oscillator is essentially the same as the Tuned-Plate Armstrong Oscillator circuit described in the Oscillator Section of this handbook; the operation of a typical full-wave voltage-doubler circuit has already been described in this section of the handbook. For these reasons, the discussion which follows will be somewhat limited.

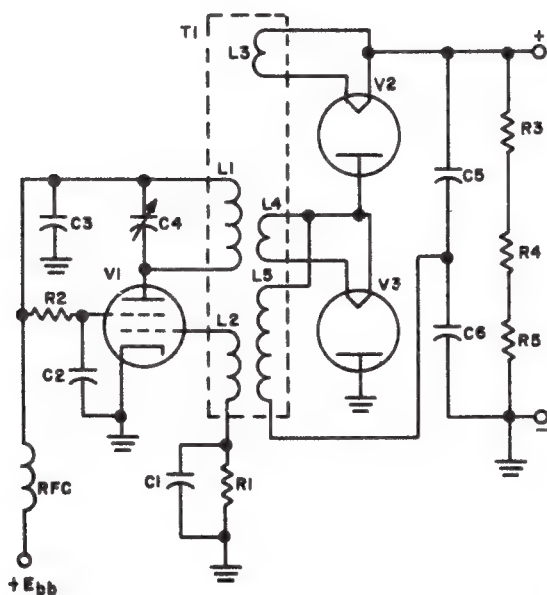

DC-to-DC Converter, R-F Oscillator Type

Electron tube V1 is a pentode tube, such as type 6V6 or 6Y6. Electron tubes V2 and V3 are identical directly-heated diodes, such as type 1B3, IV2, or

1X2. The parallel combination of resistor R1 and capacitor C1 is used to obtain operating (grid-leak) bias for the self-excited oscillator circuit. The air-core transformer, T1, is the oscillator tank circuit and high-voltage transformer. Winding L1 is the primary winding of the transformer, and is resonated by tuning capacitor C4 to determine the frequency of oscillation. Winding L2 is the untuned-grid (tickler) coil, which supplies the necessary feedback to the grid of V1 to sustain oscillations. (The ratio of the relative reactances of L1 and L2 determines the exciting voltage for the oscillator grid.) Windings L3 and L4 supply the filament current to the rectifier diodes, V2 and V3, respectively. Winding L5 is the high-voltage (step-up) winding, and is the ac source for the rectifier circuit.

Capacitor C2 is the screen bypass capacitor, and resistor R2 is the screen dropping resistor. Bypass capacitor C3 returns the series-fed primary winding, L1, to r-f ground potential, and the r-f choke (RFC) prevents any radio-frequency currents from entering the plate-voltage source, E_{bb} .

Capacitors C5 and C6 are the charging capacitors of the voltage-doubler circuit. Since the frequency of the applied voltage is between 40 and 600 kilohertz, and the load current is a low value, the value of these capacitors is relatively small, generally about 1000 μmf . Furthermore, because the ripple-frequency component is also in the radio-frequency range, there is little need for large-value filter components. Resistors R3, R4, and R5 in series form a bleeder and voltage-divider resistance for the output of the doubler circuit.

As previously mentioned, primary winding L1 is tuned to resonance by capacitor C4. The resonant frequency of the high-voltage winding, L5, is determined primarily by the shunting capacitances of rectifier V3 and capacitor C6 in series, as well as stray circuit capacitance resulting from wiring and the physical placement of other circuit components. The r-f oscillator power supply is normally designed so that the maximum output voltage obtainable is greater than the output voltage required to be delivered to the load. Maximum output voltage is developed when the oscillator frequency is equal to the natural resonant frequency of L5 is parallel with its shunting capacitance; therefore, the desired value of output voltage is obtained by adjusting tuning capacitor C4 to set the oscillator frequency near the natural

resonant frequency of L5 and its shunting capacitance. The voltage produced across winding L5 is applied to the voltage-doubler circuit, and since the dc output voltage contains a ripple-frequency component which is twice the frequency of the applied ac voltage, the output requires very little filtering.

The use of grid-leak bias (R1C1) tends to make the oscillator self-regulating with respect to its power output, because the oscillator operates as a Class C stage, the efficiency is fairly high. The regulation of the supply is considered adequate for most cathode-ray-tube circuit applications where the load current is always constant; however, any change in the voltages applied to the oscillator circuit, a change in the oscillator frequency, or a change in the load current will affect the output voltage and thus cause poor regulation. Therefore, if good regulation is required, a voltage regulator circuit must be added. Another disadvantage of the r-f oscillator power supply is that it must be well shielded to prevent the oscillator fundamental frequency or its harmonics from being radiated as an undesired signal, causing interference within the associated equipment or perhaps affecting nearby electronic equipments.

Failure Analysis

General. The r-f oscillator type high-voltage supply consists of two basic circuits—an oscillator and a rectifier. It must be determined initially whether the oscillator or the rectifier portion of the power-supply circuit is at fault. Tests must be made to determine whether the oscillator is performing satisfactorily; if it is, the trouble is then assumed to be located within the associated rectifier circuit or its load circuit. The failure analysis outlined in the following paragraphs is somewhat brief because the subject of electron-tube oscillators is discussed in another section of this handbook; furthermore, the particular high-voltage-rectifier circuit may be the same as one of the rectifier circuits described earlier in this section. Since the r-f oscillator high-voltage supply is a combination of two basic circuits, information concerning failure analysis for either portion of the high-voltage supply can be obtained by reference to the applicable basic circuit given elsewhere in this handbook.

No Output. When the oscillator is in a nonoscillating condition, negative grid voltage will not be developed across R1C1, and the measured plate and screen voltages of oscillator tube V1 will be below normal. The applied filament, plate, and screen volt-

ages should be measured to determine whether these voltages are present and are of the correct value. The oscillator tube V1 should be tested to determine if it is defective.

Excessive losses in the air-core transformer, T1, or shorted capacitor C1, C2, C3, or C4 will prevent the oscillator from operating. Also, defective components in the rectifier circuit associated with the high-voltage winding, L5; may introduce losses into the oscillator circuit which will prevent oscillator operation. With all voltages removed from the circuit, disconnect one lead from winding L5, or remove rectifiers V2 and V3 from their sockets; then reapply the voltages and again perform tests on the oscillator to determine whether the oscillator will operate under no-load conditions.

If the oscillator circuit is found to be functioning normally, it must be assumed that the trouble is associated with the rectifier circuit or its load, and a check of the rectifier circuit must be made in accordance with the procedures outlined in this section for the applicable rectifier circuit.

Low Output. A relative indication of oscillator output can be obtained by measuring the amount of bias voltage developed across R1C1. A value of bias which is below normal is an indication of low oscillator output. Also, if the applied plate and screen voltages are below normal, a reduction in output will occur. A leaky screen bypass capacitor, C2, will form a voltage divider with screen dropping resistor R2 and result in a decreased screen voltage; thus, the output of the supply will be low. Oscillator tube V1 should be checked to determine if it is the cause of the low output. Where the oscillator circuit employs two tubes in parallel, one or both tubes may be suspected as causing low output.

It is possible that the low output condition may be caused by a change in oscillator frequency away from the resonant frequency of the high-voltage winding L5. (A change in the oscillator frequency toward the resonant frequency of L5 will ordinarily cause a higher than normal output.) An adjustment of tuning capacitor C4 can be made in this case in an attempt to obtain the normal output voltage.

If the oscillator is found to be operating normally, a defect within the rectifier circuit or the associated load must be suspected as the cause of low output. For example, because of the relatively high-impedance rectifier and filter circuits and the generally poor regulation characteristics of this type of

supply, an excessive load current can cause the output voltage to be low. Failure analysis procedures for typical rectifier circuits used in high-voltage supplies are outlined earlier in this section.

DOSIMETER CHARGER (DC-TO-DC CONVERTER) (SEMICONDUCTOR)

Application.

The dosimeter charger is one typical application of the dc-to-dc converter circuit. The dosimeter charger is a self-contained, portable, battery-operated, transistorized power supply which is used to generate a dc output (charging) voltage at a small load current. The circuit can be arranged to furnish either a negative or a positive high-voltage output. The dosimeter charger is commonly used to provide a high-voltage charge for radiation detectors employed for personnel monitoring. The dc output voltage developed by the charger is transmitted, through an appropriate connection or receptacle, to the dosimeter being charged.

Characteristics.

Uses single transistor self-excited oscillator circuit combined with a half-wave rectifier circuit.

Typical operating frequency is between 400 and 2000 Hz.

Output is high-voltage dc at low current.

Regulation is poor; however, for the application the regulation is not important.

Rectifier circuit can be arranged to provide either positive- or negative-polarity output voltage; rectifier is semiconductor diode.

Circuit Analysis.

General. The dosimeter charger consists of a tickler-coil (Armstrong) audio-frequency oscillator operating in conjunction with a rectifier to convert a low dc voltage to a high dc voltage. The oscillator described here operates in the range between 400 and 2000 Hz as a sine-wave generator, although with slight modification the circuit can operate as a blocking oscillator to produce a square-wave. The high-voltage ac output from the oscillator is rectified to provide a dc output voltage which is then filtered to remove ripple, and applied to the electroscope assembly of the dosimeter (or radiacmeter).

A brief description of a small, direct-reading pocket dosimeter, used to measure X and gamma radiation, is in order at this time so that the application of the charger may be better understood.


The pocket dosimeter is one of several radiation monitoring instruments utilizing the ability to radiation to produce ionization in gases. The dosimeter is approximately the size of a fountain pen, and consists of a hermetically sealed metal tube, or barrel, with an inner ionization chamber electrically connected to the metal tube. An electroscope assembly, consisting of a stiff support wire mounted in a clear plastic insulator and a freely moving quartz fiber supported by the wire, is mounted within the ionization chamber. The support wire is connected to a charging contact which is insulated from, and mounted in, the sealed end of the metal tube. A sealed optical system, consisting of an eyepiece lens, a calibrated scale, and an objective lens, is mounted axially in the other end of the metal tube.

Before the dosimeter can be used to detect radiation, it must be charged. This is accomplished by applying a dc voltage between the metal tube and the charging contact located on the end of the tube. The charging voltage causes a mutual repulsion between the support wire and the quartz fiber, and a mutual attraction between the ionization chamber wall (tube) and the quartz fiber. As a result, the quartz fiber is deflected away from the support wire toward the chamber wall. The amount of deflection is a direct function of the charging voltage; the greater the voltage, the greater the deflection. The dosimeter is charged prior to use by looking into the eyepiece and adjusting the voltage output of the charger until the quartz fiber indicates "O" on the internal calibrated scale of the optical system.

As radiation passes through the dosimeter, the gas within the chamber ionizes. The ionized gas is capable of electrical conduction, and thus partially neutralizes the charge existing on the quartz fiber. As a result, the fiber moves toward the support wire a distance equivalent to the amount of radiation received. The amount of total radiation exposure can be read directly from the calibrated scale by viewing it through the eyepiece.

Circuit Operation. The accompanying circuit schematic illustrates a self-excited, tickler-coil (Armstrong) audio-frequency oscillator used in conjunction with a half-wave rectifier circuit. The discussion

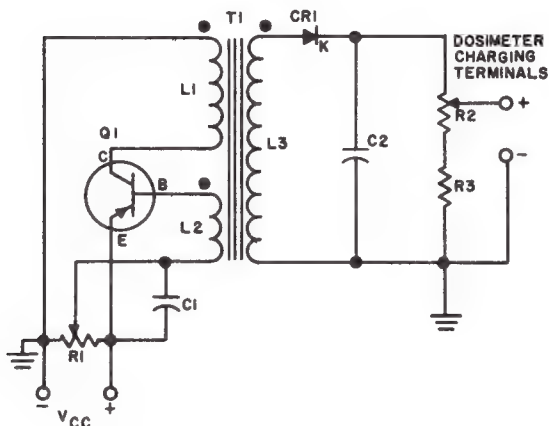which follows is limited to a brief discussion of the oscillator circuit, since the operation of the Single Phase Half-Wave Rectifier Circuit using a semiconductor diode has been described earlier in this section of the handbook.



Typical Dosimeter Charger Circuit

Transistor Q1 is a PNP transistor, either a point-contact or a diffused-junction type, used in a common-emitter circuit configuration. Since the power output required of the charger is extremely small, the transistor need not be a power transistor as was the case in other DC-to-DC Converter Circuits described previously in this section. Rectifier CR1 is a semiconductor diode used in a conventional half-wave rectifier circuit. Because the dc output voltage is usually limited to approximately 400 volts, dc, a single rectifier having the necessary peak-inverse voltage characteristics is normally employed.

Transformer T1 provides the necessary regenerative feedback coupling from the collector to the base of the transistor, and is also the source of high voltage for the half-wave rectifier circuit. Transformer winding L1 is the collector winding, winding L2 is the feedback (tickler coil), or base, winding, and winding L3 is the high-voltage secondary (step-up) winding. In the schematic, the dots adjacent to the transformer windings are used to indicate similar winding polarities.

Potentiometer R1 is used as a voltage divider to provide forward bias for the base of the transistor.

Once R1 has been set to establish forward bias for proper operation of the transistor, it normally does not require further readjustment unless the transistor is replaced or a change in transistor characteristics occurs.

Capacitor C1 is an audio bypass capacitor provided to return the end of feedback winding L2 to the emitter of transistor Q1. Capacitor C2 is the filter capacitor of the half-wave rectifier circuit. Since the frequency of the oscillator is relatively high (400 to 2000 Hz), the value of capacitor C2 need not be very large (usually 0.01 to 0.02 μf) in order to effectively remove any trace of ripple voltage; furthermore, since the load is an extremely high impedance and the load current is small, the capacitor charges to the peak value of the applied ac.

Potentiometer R2 and resistor R3 form a voltage divider across the output of the rectifier circuit. The value of R2 is usually several times greater than the value of R3, and the total series resistance is usually 15 to 20 megohms; thus, the voltage available at the output terminals of the supply can be varied between approximately 125 and 425 volts, dc. Potentiometer R2 is controlled by a front panel knob, and permits the dc output voltage of the charger, which is applied to the dosimeter electroscope assembly, to be adjusted and thus calibrate the instrument prior to use.

The common-emitter configuration illustrated earlier in this discussion utilizes a single-battery power source; as mentioned previously, this dc source produces the required base-bias voltage through the voltage-divider action of potentiometer R1. Since the collector of Q1 is at a negative potential and the emitter is at a positive potential, the base is effectively placed at a negative potential with respect to its emitter; thus, forward bias is established for the PNP transistor.

The oscillator circuit can be compared to an amplifier with feedback of the proper phase and amplitude. The oscillator may be operated Class A if a linear waveform is required, or Class C if the output waveform is not very important. In the PNP transistor schematic given earlier, feedback is obtained by transformer coupling from the collector to the base in order to sustain oscillations. If an NPN transistor is used in the circuit, the polarity of the supply voltage must be opposite to that shown on the schematic; however, for either type of transistor, the feedback signal must be 180 degrees out of phase with the collector signal. Although the transistor can also be

arranged in a common-base or a common-collector circuit, the common-emitter circuit is most commonly used because greatest gain is achieved with this configuration. The oscillator circuit shown in the schematic is essentially a transformer-coupled, feedback oscillator; its operation is similar to that of the common-emitter circuit described for the Tickler Coil (Armstrong) Oscillator Circuit in the Oscillator Section of this handbook. Although the circuits described are L-C oscillators, the operation of the audio-frequency oscillator discussed here is essentially the same; the frequency of oscillation is determined primarily by the inductance of collector winding L1, stray circuit capacitance, and the collector-to-emitter capacitance of the transistor itself. When voltage is first applied to the oscillator, the initial rush of current through L1 and L2 induces a feedback voltage in the windings. The feedback is regenerative and causes emitter and collector current to increase rapidly until the collector is saturated and no further change of current occurs. At this time the magnetic field around the windings of T1 collapses, and causes a reversed feedback voltage. This feedback is now in a direction which causes a reduction of collector and emitter current. Thus the collector is quickly driven to cutoff, and once again the collapsing magnetic field (at cutoff) causes a reversal of current flow through the induced feedback voltage. As the current through L1 alternately flows back and forth at the oscillation period, it induces a similar but higher alternating voltage in winding L3, the high-voltage winding.

The voltage produced across the high-voltage secondary winding, L3, may be either a sine wave or essentially a square wave, depending upon the class of transistor operation. This voltage is rectified by semiconductor diode CR1, is filtered by capacitor C2, and is applied across R2 and R3. A dc output voltage which is determined by the setting of potentiometer R2 is applied to the dosimeter charging contact for calibration of the radiation monitoring instrument.

Failure Analysis.

General. The dosimeter charger is self-contained, battery-operated power supply. The unit is usually very small and operates from a self-contained, 1.5 volt-battery power source. It must be determined initially whether the battery, the oscillator, or the rectifier portion of the power supply is at fault. Since the most common failure for a battery-powered

device is the battery itself, a quick check can be made by substituting a known good battery in the power supply and checking the operation once again to determine whether the battery is at fault. If the operation is not satisfactory after battery substitution, tests must then be made to determine whether the oscillator or the rectifier circuit is at fault.

As stated before, the dosimeter charger is a combination of two basic circuits, an oscillator and a half-wave rectifier using a semiconductor diode. Therefore, the failure analysis outlined in the following paragraphs is somewhat brief since oscillators are completely discussed in the Oscillator Section of this handbook, and the Half-Wave Semiconductor Diode Rectifier is discussed earlier in this section of the handbook.

No Output. The battery power source (V_{cc}) should be measured to determine whether it is present and of the correct value.

The oscillator can be quickly checked to determine whether or not it is oscillating by using an oscilloscope to observe the collector-to-emitter waveform.

If potentiometer R1 should change value (or is misadjusted), the forward bias will change accordingly. If the forward bias decreases the collector current also decreases, and, conversely, if the forward bias increases the collector current increases. At either extreme of these two conditions, oscillations will cease.

Any defect in transformer T1, such as an open feedback or collector winding, or shorted turns in any of the windings, will prevent the circuit from oscillating. A shorted secondary circuit, reflected to the collector and feedback windings, will cause excessive losses in the circuit and prevent sustained oscillations. If the high-voltage winding, L3, should open, the circuit will oscillate; however, no output will be obtained from winding L3 for the rectifier circuit.

A shorted junction or an open junction in the transistor, Q1, will cause the circuit to stop oscillating.

If the oscillator circuit is found to be functioning normally, then it must be assumed that the trouble is in the associated rectifier circuit.

Low Output. The battery power source (V_{cc}) should be measured to determine whether it is present and of the correct value.

In the common-emitter configuration, a relatively small change in base current produces a relatively large change in collector current. Therefore, the value of the forward-bias voltage applied to the base of the

transistor is rather critical, since the bias voltage has a direct effect upon collector current and thus upon the oscillator power output. While reduced output can result from a loss of gain in the transistor, this condition is not very common; therefore, it is more logical to measure the supply and bias voltages before deciding to replace the transistor.

A change in the resistance ratio of potentiometer R1, an open or short in a portion of potentiometer R1, or leakage in bypass capacitor C1 will affect the output, since any of these conditions will cause a change in bias; however, a change in bias is easily detected by measuring the operating bias with a high-resistance voltmeter, or preferably an electronic voltmeter. For example, if the positive end of R1 should open, the base of Q1 is returned to $-V_{cc}$ through the remaining portion of R1; in this case, since the base remains in a forward-bias condition, the circuit will continue to oscillate. However, the oscillator output will no longer remain a sine wave, and the oscillator may start to pulse in a manner similar to that of a blocking oscillator. On the other hand, if the negative

end of R1 should open, the base of Q1 is returned to $+V_{cc}$, and oscillations will cease. Either of these two conditions can be detected by a measurement of the bias voltage.

If resistance measurements are to be made on potentiometer R1, at least two of the terminals should be disconnected from the circuit, or the transistor removed from the circuit, in order to obtain valid resistance measurements (that is, measurements that are unaffected by the junctions of the transistor).

If the oscillator circuit is found to be operating normally, a defect within the rectifier circuit must be suspected as the cause of low output. Since the rectifier circuit is a high-impedance circuit, an excessive load current caused by a decrease in the value of R2 or R3, or by a leaky bypass capacitor (C2), can result in reduced output. Also, a defective semiconductor diode (CR1) can cause decreased output. Failure analysis procedures for the Half-Wave Semiconductor Diode Circuit are given earlier in this section of the handbook.

PART 2-5. SILICON-CONTROLLED RECTIFIERS

SINGLE-PHASE FULL-WAVE SCR

Application.

The single-phase full-wave silicon-controlled rectifier is usually used where a high dc current output is required from the power supply. It is used as a power supply in electronic equipments such as transmitters and computers, or industrially in battery charges, in welders, and as a control device.

Characteristics.

Input is alternating current and output is pulsating direct current.

Uses a center-tapped transformer.

DC output ripple frequency is twice the primary line voltage frequency.

Uses two silicon-controlled rectifiers.


May be connected to supply either positive or negative output voltage.

Circuit Analysis.

General. Except that it is controlled by a gate, the silicon-controlled rectifier operates in a manner similar to the conventional semiconductor diode rectifier. For full-wave operation two diodes are required; one for each half of the cycle.

In the ordinary diode, conduction occurs in a forward direction as soon as the anode becomes more positive than the cathode. In the silicon-controlled diode, conduction does not occur until the unit is turned on by a positive current gate (or until the forward breakdown voltage is exceeded). Once triggered, conduction continues for the remainder of the ac half-cycle until the reducing forward voltage causes the forward current to fall below the holding current value, whereupon conduction ceases. At the same time, the polarity of the ac input changes, and a reverse voltage is applied to the diode. During the second half-cycle, the other controlled rectifier diode is gated and conducts in a similar manner. By controlling the gate firing time, the output voltage and current may be controlled over any desired portion of the operating cycle.

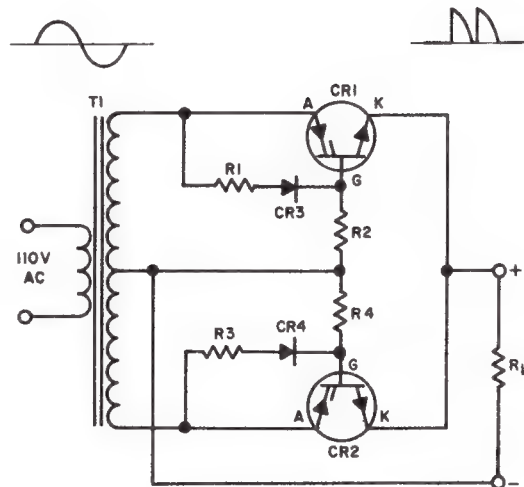Circuit Operation. The schematic of a typical full-wave controlled rectifier circuit is shown in the accompanying illustration.



Full-Wave Controlled Rectifier

Transformer T1 is the supply voltage transformer with a center-tapped secondary. The secondary voltage may be any value within the rating of the controlled rectifier diodes. Diodes CR1 and CR2 are similar types of silicon-controlled rectifiers. The gate firing network for CR1 consists of current-limiting resistors R1 and R2, with semiconductor diode CR3. The gating network for CR2 consists of current-limiting resistors R3 and R4 with semiconductor diode CR4.

When primary voltage is applied to T1, one end of the secondary becomes positive with respect to the center tap, while the other end is negative with respect to the center tap.

Assume that the anode of CR1 is driven positive while the anode of CR2 is driven negative. Since a negative voltage is applied to CR2, only reverse leakage current flows through the diode. Meanwhile, since CR1 is not triggered and the forward voltage is below the firing level, CR1 will not conduct. As the positive half-cycle increases from zero toward maximum, a positive voltage is also applied to gate-control diode CR3 which conducts and produces a positive voltage drop across R2. The positive voltage applied to the gate electrode of CR1 forward-biases CR1 and permits a flow of electron current from cathode to

anode of the silicon-controlled rectifier. The current flow path is from the center tap of T1 through load R_L , and through diode CR1 to the top of the secondary winding. Conduction through CR1 continues until the secondary voltage drops to zero, and reverses during the next half-cycle. At the same time, the anode of gate-control diode CR3 is also driven negative and does not conduct. Hence, with no gate voltage, and a negative anode voltage, CR1 ceases conduction for the negative half-cycle.

The anode of controlled rectifier CR2 is now driven positive, but CR2 remains blocked until gated. The positive half-cycle also drives the anode of gate-control diode CR4 positive, and current flow through resistor R4 eventually provides a positive gating voltage. When CR2 is gated, electrons flow from cathode to anode until the next half-cycle occurs, and the polarity is reversed. Current flow is from the center tap of T1 through load resistor R_L and controlled rectifier CR2 to the bottom of the secondary winding. Since current flows through the load in the same direction when either rectifier is conducting, a positive dc voltage is obtained at the output of the power supply. Thus, for each half cycle of ac, a positive output pulse is produced, creating a ripple frequency of twice the input frequency. This ripple component is eliminated by using a low-pass filter, as required.

The use of a simple resistor-diode type of gating is shown and described for simplicity and ease of discussion. Usually a more complicated firing circuit is used, and the output is controlled over the entire half-cycle of operation, as desired. With the resistor-diode control circuit, control is limited to a maximum of 90 electrical degrees of the half-cycle of operation, as determined by the values of resistors R1, R2, R3, and R4. Increasing the resistance value delays the firing time, while decreasing the resistance value lengthens the firing time. Delaying the firing time also changes the pulse shape from a sinusoidal waveform toward a square waveform, since the leading edge is straightened. Hence, in control circuits which fire only over a small portion of the ac half cycle, an almost pure square-wave output voltage is produced. Thus, the silicon-controlled rectifier tends to be more difficult to filter than the conventional semiconductor or electron tube power supply, since it contains more harmonic output.

For high currents at standard line voltages, the center-tapped transformer may be dispensed with, and the controlled rectifiers are connected across the

line in series with the load. In addition, surge voltage suppressors and transient elimination circuits are required to stabilize the line voltage. Since circuits of this type are usually used on industrial equipment such as spot welders, they are beyond the scope of this handbook; the interested reader is referred to standard commercial design data and manufacturers' handbooks.

Failure Analysis.

No Output. Lack of output may be caused by loss of line voltage, a defective supply transformer, a defective controlled rectifier, or a defective gate control circuit. Check the line voltage with a voltmeter to determine that primary voltage is available and that a defective supply or blown power fuse is not at fault.

With the proper primary voltage available, check the secondary voltage with an ac voltmeter to determine that T1 is not defective. If voltage exists across the primary of T1 but does not appear across the secondary, remove the power and check both primary and secondary windings with an ohmmeter for continuity. Lack of continuity indicates an open winding. A shorted winding will usually blow the primary fuse or open the circuit breaker. Use an oscilloscope to check the gating waveform and amplitude. Presence of the proper firing pulse and no output usually indicates that the controlled rectifier diode is defective.

If the gating waveform is incorrect, or does not appear, check the firing circuit (R1, R2, R3 and R4) with an ohmmeter. Check the forward and reverse resistance of CR3 and CR4. Normally, the reverse resistance should be high and the forward resistance low. If a low reading is obtained in both directions, the diode is shorted; if a high resistance is obtained in both directions, the diode is open. If the components are checked and found to be normal, but there is still no output, check the output resistance and load. Where a ripple filter is used, it is possible for the input capacitor to be shorted. Usually such a condition will create a load sufficient to blow the fuse or open the primary circuit breaker.

Low Output. Low line voltage, a defective controlled rectifier, or a defective firing circuit can cause a low output. Use an accurate ac voltmeter to measure the line voltage. To determine if the controlled rectifier is defective, use an SCR tester. It is also possible to have only one controlled rectifier operative, so that instead of functioning as a full-wave rectifier, it

operates only as a half-wave rectifier. Hence, it is necessary to make similar measurements on both sides of the circuit. Equal secondary voltages must exist between the center tap and each side of the secondary of T1 to ensure that equal outputs are obtained at the cathode. Likewise, both firing gates must be equal in waveshape and amplitude to fire over the same range. If one diode fires sooner or later than the other, so that conduction occurs for different periods of time, a lower than normal output can be obtained.

When checking the firing circuits, the values of R1 and R3 should preferably be the same; differences in the resistance values of these resistors have a greater effect on the firing time than do the differences between R2 and R4. For best results, gating diodes CR3 and CR4 should be matched also. Where a large value of input capacitance is used on the ripple filter following the rectifier, a greater mismatch between firing components can be allowed, since the long charge and discharge time constant of the filter averages out the changes between half-cycles of operation.

Erratic Firing. In the simple resistance-diode firing circuit described in this full-wave rectifier circuit, the trigger pulse is obtained from line voltage. Therefore, it is possible for line transients of sufficient amplitude to cause false triggering. These transients can be observed on an oscilloscope connected across the line. It may be necessary to employ surge suppressors or a line regulator to prevent such erratic operation. When encountering trouble of this sort, it is important not to neglect the location and dressing of input and output cabling, particularly where the transients are being induced by unnecessary inductive coupling between the rectifier and the line or device causing the trouble.

THREE-PHASE FULL-WAVE SCR

Application.

The three-phase full-wave silicon-controlled rectifier is generally used in high voltage and high current

three-phase power supplies for electronic and industrial equipments.

Characteristics.

Input to circuit is three-phase ac; output is dc with amplitude of ripple voltage less than that for a single-phase rectifier.

Uses six controlled rectifiers.

Output requires very little filtering; dc output ripple frequency is equal to six times the primary line-voltage frequency.

Circuit has good regulation characteristics.


Can be connected for either positive or negative output voltage.

Uses multi-phase transformer with wye-connected secondary. Primary may be connected either delta or wye.

Circuit Analysis.

General. The three-phase silicon-controlled full-wave rectifier is similar in operation to the conventional semiconductor rectifier, except for its gating circuitry. Usually the primary is connected in delta and the secondary in wye to obtain a step-up of voltage. A delta-to-delta connection will produce a lower output voltage in comparison with the delta-to-wye connection. Usually the gating circuit is of the variable-phase control type, allowing full control over each phase to provide a uniform balance, maximum voltage, and better efficiency.



Circuit Operation. A typical three-phase, full-wave silicon-controlled rectifier schematic is shown in the accompanying illustration. The gate firing control circuitry is not shown since there is no single basic firing circuit, but each manufacturer has his own proprietary claims for his own devices. In the discussion of circuit operation, an adequate firing pulse will be presumed to occur at the desired instant and of sufficient amplitude, duration, polarity, and value to produce forward conduction in the controlled rectifier.

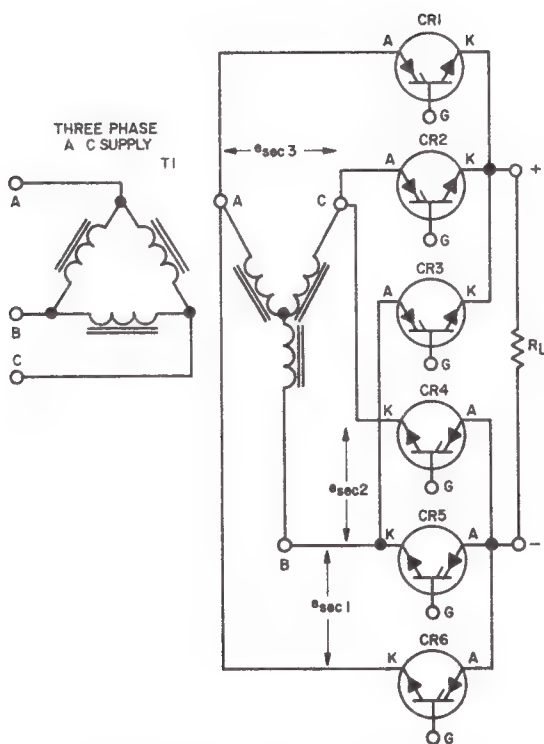

Three-Phase Full-Wave Controlled Rectifier

In the schematic, T1 is a three-phase transformer with the primary delta connected and the secondary wye connected. Silicon-controlled rectifiers CR1, CR2, and CR3 operate on one-half of the ac cycle, while CR4, CR5, and CR6 operate on the other half-cycle since they are connected in reverse (these connections are similar to those used for electron tube and conventional semiconductor diodes also).

The secondary voltages between terminals A, B, and C ($e_{\text{sec } 1}$, $e_{\text{sec } 2}$ and $e_{\text{sec } 3}$, respectively) are 120 electrical degrees out of phase, producing three separate single-phase ac voltages over a complete 360-degree cycle. Thus, a positive or a negative peak of voltage occurs every 60 electrical degrees. With three rectifiers connected to operate on each half-cycle, six conduction periods occur during one 360-degree period of operation. The individual circuits are shown for each conduction period in the accompanying illustration. The arrows show the direction of electron flow through the circuit. Since the path through the load is always in the same direction, a dc output voltage and current are produced. Since the output ripple frequency is six times that of the line frequency, the output is much easier to filter than the conventional single-phase supply.

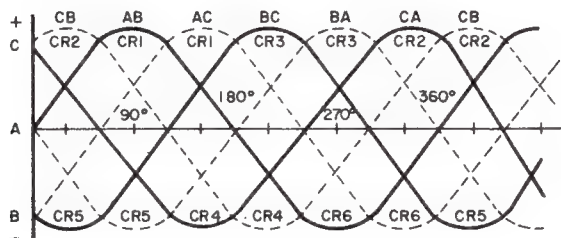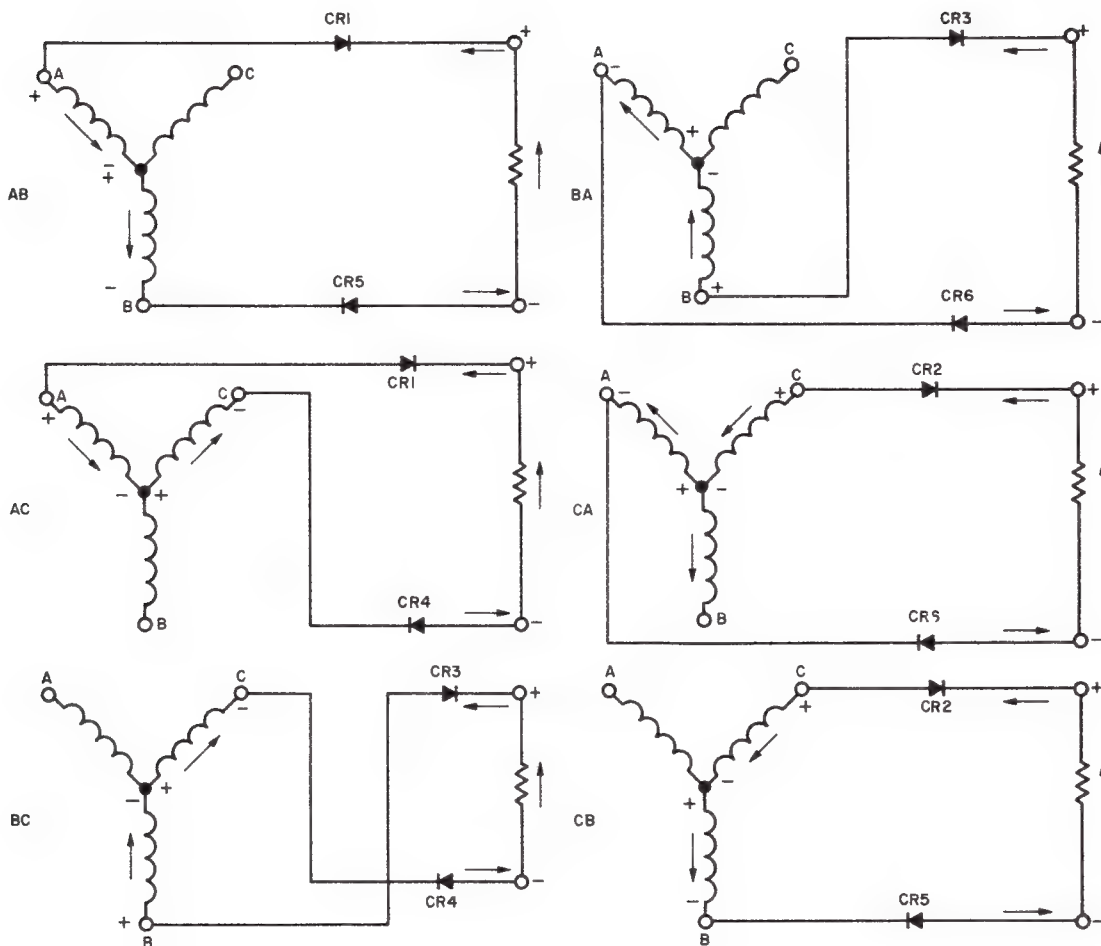

Rectifier Circuits and Waveforms

When voltage is applied, the diodes do not conduct since they are not gated and the normal forward voltage is insufficient to cause them to fire. At time t_0 , assume that phase A (terminal A on the secondary) is at zero and voltage $e_{\text{sec } 1}$ is increasing in a positive direction. At this time, phase B (terminal B) is negative 60 degrees and increasing toward its maximum negative potential at -90 degrees. Phase C has reached and passed its maximum positive peak and is becoming less positive (approaching zero) during its final 60 degrees of positive half-cycle. Since half of the rectifiers conduct during the positive half-cycle, and half during the negative half-cycle of operation, there are always two rectifiers conducting. Thus, over a 360-degree period of operation, each rectifier conducts for 120 degrees and is off for 60 degrees. If we assume that the controlled rectifier gate is arranged to trigger each rectifier when the voltage reaches 60 degrees amplitude (positive or negative), then the rectifier will continue to conduct for 120 degrees until the applied voltage reaches zero at the 180-degree point where the polarity reverses during the following half-cycle. The accompanying waveform illustration shows the ac secondary voltage relationships.

Starting at t_0 , voltage CB reaches its 60-degree positive position while voltage BC reaches its 60-degree negative position. Controlled rectifiers CR2 and CR5 are gated and forward conduction occurs in each. During period CB, electron flow is from terminal B through CR5, through the load, and CR2, back to terminal C. During the interval of voltage from C to B, terminal C voltage is falling toward zero while terminal B is increasing negatively. Meanwhile, the voltage at terminal A is increasing from zero in a positive direction. When voltage A reaches the 60-degree point, CR1 is gated by a positive firing pulse and CR1 conducts. Simultaneously, terminal C voltage reaches zero and CR2 ceases conduction. Since CR5 is still negatively biased and conducting, the current path for period AB is from terminal B through CR5, through the load, and CR1, to terminal A. Thus the same current direction is maintained and the output voltage remains positive. During the period AB, terminal B voltage declines from a maximum negative value to zero, turning off CR5 when terminal B becomes zero, and starts increasing in a positive direction. Simultaneously, the voltage at terminal C is increasing negatively from zero and reaches the 60-degree firing point as CR5 turns off, and transfers conduction to CR4. Thus, during the period AC, elec-

tron flow is from terminal C, through CR4, through the load and CR1, back to terminal A. At the end of period AC, the positive voltage on terminal A has reduced to zero, turning off CR1. Meanwhile, terminal B voltage is increasing in a positive direction, and reaches the firing point 60 degrees later when period AC ends and BC begins, and turns on CR3. Conduction now occurs from terminal C through CR4, the load and CR3 to terminal B. Since the current flow is still in the same direction through the load, the output voltage is still positive.

During the period BC, terminal A voltage increases from zero toward a maximum negative value, and at the end of period BC reaches the firing value for CR6. Meanwhile, voltage C has reached zero and turns off CR4 as CR6 is turned on. During period BC, voltage BA is increasing from zero toward a positive maximum, so that CR3 still conducts for the period BA. Meanwhile, the voltage at terminal C increases from zero in a positive direction, and at the end of period BA fires CR2. The conduction path for period CA is now from A, through CR6 and the load, and through CR2 back to C.

At the end of period CA, voltage A has declined from a maximum negative value to zero and turns off CR6. Meanwhile, voltage B has increased negatively to the firing point and turned on CR5. Thus, conduction continues for period CB from terminal B through CR5, the load and CR2 to terminal C. The sequence of on-and-off gating just described for the 360-degree period of operation now continues in the same manner, producing a continuous dc output voltage.

Although the firing time has arbitrarily been chosen at the 60-degree point for ease of discussion, it is usually possible to control operation over any desired portion of the cycle. In those cases where it is desired to turn off the rectifier before the end of the half cycle, it is necessary to include in the control circuit some form of turn-off voltage.

Failure Analysis.

No Output. A no-output condition can be caused by lack of supply voltage, or a blown line fuse, by a defective firing circuit, or by a defective controlled rectifier. Use a voltmeter to determine if line voltage is present. If line voltage is not present, check for a blown line fuse or a defective transformer. If line voltage is present in the primary but no secondary voltage exists, remove the power and check the secondary windings for continuity. Since there are three

separate windings involved in three-phase circuits, each must be checked individually. Usually only one phase opens at a time, so that no-output conditions are usually caused by short circuits across the output, which are usually indicated by continuous blowing of fuses. The more probable event is a defective firing circuit which prevents any of the rectifiers from operating. Use an oscilloscope to observe the firing waveform and amplitude. If firing waveforms are present and no output is obtained, the rectifier is defective.

Low Output. Low output voltage can be caused by low line voltage, improper transformer connections, or a defective transformer or controlled rectifier. Check the line voltage with a voltmeter, and in addition check for poor or loose primary connections. Check the transformer connections to make certain that the secondary is wye-connected, since a delta connection will automatically produce a lower output voltage. Check the transformer for equal voltages across each winding. If unequal voltages are measured, remove the power and check the resistance between each terminal and ground, since a partially shorted or grounded secondary can exist. If equal secondary resistances exist with equal primary and secondary voltages, but the output voltages are different, the low reading controlled rectifier is probably defective.

A firing circuit adjusted for short conduction periods, or with defective components which can cause a shorter than normal conduction period, will also provide a low output. If a slight readjustment of the firing circuit control will return the output voltage to normal, the trouble is probably a change in component values in the firing circuit. Voltage and resistance checks of the firing circuit will usually determine the part at fault. Increased resistance in the circuit usually causes delayed firing, while decreased resistance values lengthen the firing time. Where an output filter is used, it is possible for a faulty filter to produce a lower than normal voltage.

BRIDGE-CONNECTED SCR

Application.

The bridge-connected SCR is used to supply high voltage at relatively high current in electronic and industrial equipments. Low-voltage applications are also possible.

Characteristics.

Does not require a center-tapped transformer; full potential of winding is available.

Only requires two controlled rectifiers and two semiconductor diodes.

Input circuit is ac, output is pulsating dc.


Polarity of output may be either positive or negative, as desired.

Output frequency is twice the input frequency and requires ripple filtering.

Circuit Analysis.

General. The bridge rectifier uses a minimum of two controlled rectifiers firing on each half-cycle of input voltage, in conjunction with two semiconductor diodes, to provide a full-wave rectifier circuit. Since one diode and one controlled rectifier are always connected across the line in series with the load, gating the controlled rectifier also controls diode operation. Since the full secondary winding of the high voltage transformer is used, twice the voltage of a center-tapped secondary is available. For special applications, it is also possible to use four controlled rectifiers in the bridge by substituting controlled rectifiers for the two diodes. The increased complexity of the firing circuit, plus the cost of the extra controlled rectifiers, makes the two controlled rectifier bridges a more preferred circuit for general use.

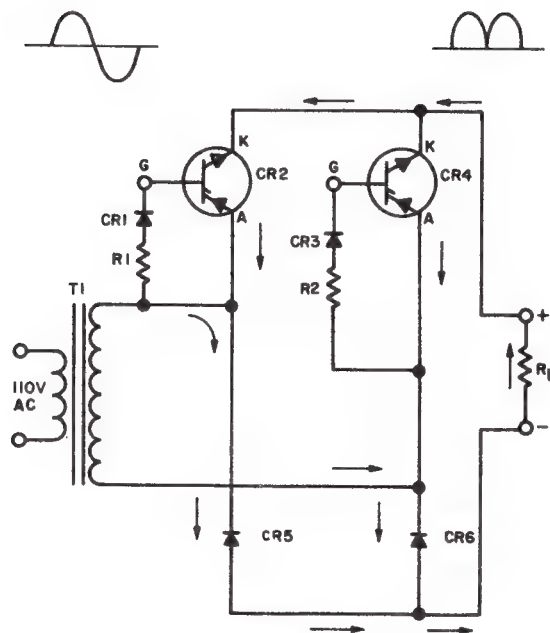Circuit Operation. The accompanying schematic illustrates a typical controlled rectifier bridge using two controlled rectifiers and two semiconductor diodes.



Controlled Bridge Rectifier

As shown in the schematic, firing of the controlled rectifiers is accomplished by a resistance-diode network. Transformer T1 supplies the secondary voltage across which the bridge, consisting of diode CR5 and controlled rectifier CR2 on one arm, and diode CR6 and controlled rectifier CR4 on the other arm, are connected. Resistors R1 and R2 are current-limiting firing resistors, and diodes CR1 and CR3 are gating diodes. Diode CR1 controls the firing of controlled rectifier CR2, while diode CR3 controls the firing of controlled rectifier CR4.

At the instant when power is first applied, both controlled rectifiers are in a nonconducting condition, since they are not gated and the forward voltage is not sufficient to cause self-firing. Assume for the moment that the top of the secondary winding of T1 is positive, while the bottom of the winding is negative. For this half-cycle the cathode of diode CR6 is biased negatively, permitting a forward flow of current. However, with controlled rectifier CR2 blocked open, the current path across the secondary is open, and current will not flow until CR2 is gated. Since the top of the secondary is positive, a positive poten-

tial is placed on the anode of control diode CR1, forward biasing the diode. Thus, as the secondary voltage of T1 increases, the positive gate voltage on CR2 also increases. When the gate voltage reaches an amplitude which causes sufficient gate current to flow, CR2 becomes forward-biased, closing the circuit path across the secondary. Current now flows from the bottom of the secondary through diode CR6, through load R_L and controlled rectifier CR2 to the top of the secondary, and a positive output voltage is produced. Conduction now occurs for the remainder of the positive half-cycle, and ceases as the anode voltage drops to zero and is unable to sustain sufficient holding current through CR2. At this time, the secondary voltage also reverses polarity, reverse-biasing control diode CR1 and controlled rectifier CR2, and forward-biasing diode CR5. When the top of the secondary of T1 is made negative, the bottom of the secondary becomes positive, and a positive gate voltage is applied to the anode of gating diode CR3 through R2. Although the anode of controlled rectifier CR4 is also made positive, the forward voltage is insufficient to cause firing. No current flows through the circuit until the positive gate voltage increases to the firing level and produces forward conduction in CR4. When CR4 conducts, current flows from the top of the secondary winding through diode CR5, the load, and controlled rectifier CR4, back to the bottom of the secondary, and a dc output voltage is produced across the load.

Since the current flows through the load in the same direction for both half-cycles of operation, the current flows continuously in one direction and the ac input is changed to a dc output. Controlled rectifier CR4 continues to conduct until the anode voltage drops to zero at the end of the half-cycle and reverses polarity. Once again, the top of the secondary winding becomes positive and eventually CR2 is gated, and the cycle repeats. Since conduction in the rectifiers does not occur until they are gated and varies with the applied voltage amplitude, the output voltage is pulsating direct current with a ripple frequency twice that of the input. Therefore, an output filter is required for those applications requiring pure direct current. Filter circuits are discussed in the Filter Section of this handbook.

When the two controlled rectifier bridge circuit is used, it is necessary that the associated diodes are capable of handling the same current and voltage as the controlled rectifiers. The gating diodes, however,

need only be rated sufficiently to carry the gating current and voltage. The time of firing is mainly controlled by the values of firing resistors R1 and R2.

Failure Analysis.

No Output. Loss of line voltage or a defective transformer are the most likely causes for a no-output condition. While it is also possible that a defective firing circuit or faulty rectifiers can also cause lack of output, it is necessary that both rectifiers, both diodes, or both firing circuits be simultaneously defective to cause a complete loss of output. Failure of one half of the circuit will cause a low output, rather than none at all. Check the primary line voltage with an ac voltmeter; if no voltage is present, a fuse or circuit breaker is most likely at fault. If primary voltage exists, check the secondary voltage. If no secondary voltage exists, check transformer T1 for continuity with an ohmmeter. Usually a short-circuited secondary will continue to blow the primary fuse. If secondary voltage is present but there is still no output voltage, check each firing circuit with an oscilloscope to see if a firing waveform exists. Check the value of R1 and R2 with an ohmmeter, and check the forward and reverse resistance of gating diodes CR1 and CR3. If the gating diodes are defective they will indicate the same resistance in both directions. Also check diodes CR5 and CR6. If a firing gate is present on CR2 and CR4, and diodes CR5 and CR6 are satisfactory, controlled rectifiers CR2 and CR4 are probably defective. Where a filter is used at the output, it is possible for the filter to be shorted, but usually such a condition results in continuous blowing of the primary or line fuse.

Low Output. Low output voltage can be caused by low line voltage, a defective transformer, a faulty circuit, or a faulty rectifier. Check the primary and secondary voltages with a voltmeter to make certain they are normal. Use an oscilloscope to check that both firing circuits operate. Check the value of both R1 and R2 with an ohmmeter. A reduced firing time, caused by either R1 or R2 increasing in value, can produce a lower output than normal. A similar condition could also be caused by either CR1 or CR3 being defective.

SCR INVERTER (DC to AC)

Application.

The SCR inverter is used to change a dc input voltage to an ac output voltage for power-supply use aboard ship, small craft, aircraft, and mobile equipment, which primarily have only a source of direct current available.

Characteristics.

Input to inverter is dc, output is ac.

Oscillator frequency determines output frequency.

Two SCR's are used (one for each half-cycle).


Conversion efficiency is high (85 to 90 per cent).

Output waveform may vary between that of a square wave and a sine wave (usually a filter is required to produce a sine wave).

Circuit Analysis.

General. The inverter changes a dc input to an ac output. The output of a square-wave multivibrator, pulse generator, or oscillator, is used to gate a silicon-controlled rectifier (SCR) and produce a flow of current in one direction through a transformer primary for one half-cycle of operation. A means of applying a reverse voltage is used to block and turn off the first controlled rectifier at the time that a second SCR is triggered during the next half-cycle, or the phase between the output current and voltage is controlled so that the current drops to zero or below the minimum holding value to stop the SCR from conducting at the end of the half-cycle. During the second half-cycle of operation, the other SCR is gated and causes current to flow in the opposite direction through the transformer primary. Thus, the output in the secondary of the transformer is an alternating current and the voltage is at a frequency which is half that of the primary oscillator. Normally, the output frequency is fairly stable, but does tend to vary somewhat with the load. Therefore, in the more expensive inverters, provisions are usually made to insert a synchronizing voltage to make the output frequency constant. In the basic inverter, the output voltage also varies somewhat with the load, so that for precise voltage applications voltage regulator circuits are also included.

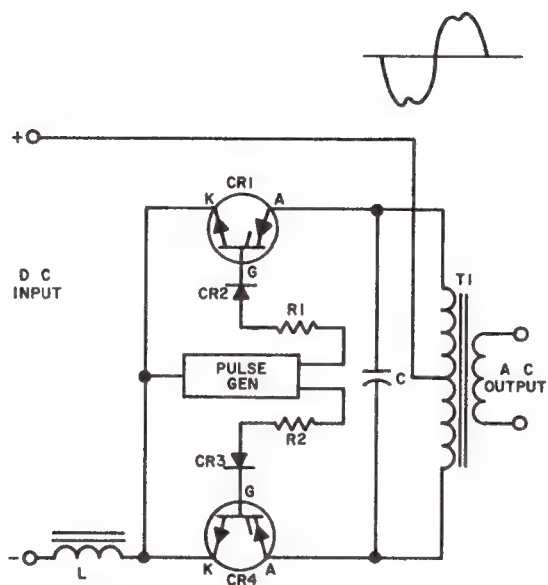Circuit Operation. The schematic of a simple basic single-phase inverter using silicon-controlled rectifiers is shown in the accompanying illustration.




Typical SCR Parallel Inverter

In the schematic, the pulse generator is shown in block diagram form, since it may be any one of a number of types of oscillators or multivibrators described in the Oscillators or Multivibrators Sections of this handbook. It is only necessary that it produce an output sufficient in amplitude and duration to gate the controlled rectifiers. Resistors R1 and R2 are current-limiting resistors used to hold the dc firing current, rectified by diodes CR2 and CR3, to a safe value. Capacitor C is used to provide a turn-off voltage for the controlled rectifiers. Transformer T1 is the output and ac supply transformer, and inductor L provides an increase in efficiency, permitting each SCR to fire for a complete half-cycle of operation. CR1 and CR4 are silicon-controlled rectifiers, employed as polarity reversing switches for the transformer primary.

Assume for the moment that controlled rectifier CR1 is conducting; hence, electron current flows from the negative dc supply lead through choke L, controlled rectifier CR1, and the top half of the primary of transformer T1, and returns to the positive

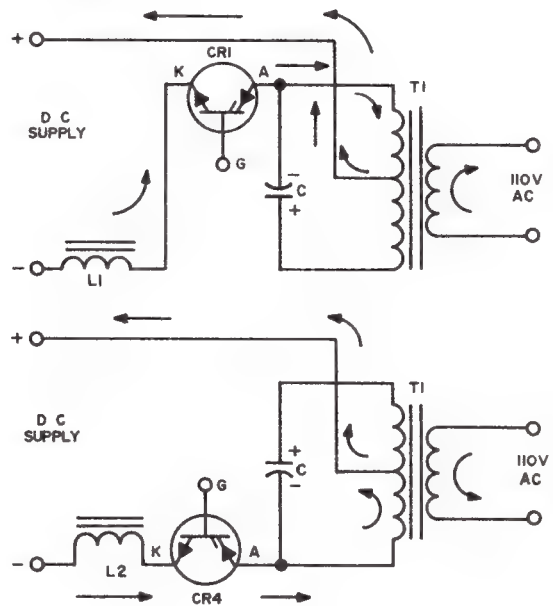supply lead through the center tap, as shown in the accompanying figure.



Primary Current Flow

As the dc current through the primary of T1 increases, it develops an output voltage in the transformer secondary. At the same time, capacitor C is negatively charged through controlled rectifier CR1, since the opposite plate is connected to the positive supply through T1. The inductance of choke L causes the leading edge of the output waveform to taper slightly, and as the current flow reaches its peak value, the resistance of the choke produces a small voltage drop for the duration of current flow through T1. This voltage drop causes the normally flat top of the output waveform to taper off slightly toward zero. By this time, the driving oscillator waveform reverses polarity, and applies a negative pulse to the anode of CR2 through R1, which stops the CR1 gate from conducting, but controlled rectifier CR1 remains forward-biased and continues to conduct. As the oscillator reverses polarity, a positive pulse is applied to gating diode CR3 through R2, and a positive gating voltage is produced as the diode rectifies the positive portion of the oscillator pulse. Thus, controlled rectifier CR4 is forward-biased and conducts. The instant CR4 conducts, capacitor C is connected

across both CR1 and CR4, and the full negative voltage of the capacitor is applied to the anode of CR1 and blocks forward current flow. Hence current flow through the top half of the primary of T1 drops to zero, developing the trailing edge of the ac output waveform in the secondary. Controlled rectifier CR1 now remains in the turned-off condition until the driving oscillator again changes polarity. Meanwhile, current flows through the primary of T1 in the opposite direction, as shown in the figure. Electron flow is now from the negative terminal of the dc input supply, through CR4 and the bottom half of the primary of T1, and out of the center tap to the positive lead. Since current flow in the primary is reversed, the voltage induced in the secondary is also reversed, and is polarized oppositely to the output produced by CR1 operation. Thus, dc current flow through the primary of T1 produces an ac output in the secondary.

When CR1 stops conducting and CR4 conducts, capacitor C is quickly discharged through CR4 (it is only required to hold its charge long enough to turn off CR1) and is recharged in the opposite direction, since the bottom plate is connected to the negative dc supply, while the top plate of the capacitor is connected to the positive lead through T1. As current flows through CR4 and the bottom half of the primary of T1, the leading edge of the output waveform is developed. The inductance of choke L causes the leading edge of the output waveform to taper off slightly, and as the current flow reaches its peak value, the resistance of the choke produces a small voltage drop for the duration of current flow through T1. This voltage drop causes the normally flat top of the output waveform to taper off slightly toward zero. When the oscillator again reverses polarity, a negative pulse is applied to gating diode CR3, stopping the gate, while a positive pulse is applied to gating diode CR2 through R1 and forward-biases controlled rectifier CR1, which again conducts. The instant CR1 conducts, capacitor C is again connected across both CR4 and CR1, and this time the full negative voltage of the capacitor is applied to the anode of CR4, blocking forward current flow. Current flow through the bottom half of the primary of T1 now drops to zero, and develops the trailing edge of the positive waveform in the secondary. Controlled rectifier CR4 now remains in the turned-off condition until the driving oscillator again changes polarity. Meanwhile, current flows through the top half of the

primary of T1 in the opposite direction as shown in the figure, and the initial condition of operation is resumed. As the oscillator changes polarity, the current through the primary of T1 is switched in synchronism, first in one direction and then in the other direction, producing an ac output in the secondary from a dc input in the primary of T1. The large inductance of L1 prevents any sudden current surges from interfering with the turning off of one SCR as the other is switched on, giving the blocking SCR sufficient time to recover its forward blocking characteristic.

Although the output of the inverter without a filter normally resembles a square wave, this is not necessarily a detriment, since it has been found that many ac devices such as motors and power supplies can be efficiently operated from these waveforms. It should be noted, however, that because of the change in waveform, the rms and average values do not have the same numerical relationships as for sine waves. Usually, a larger amplitude output is required when no filter is used. Although only single-phase inverters have been discussed herein, three-phase inverters may also be obtained. Operation is similar and can be considered as three single-phase inverters operating with a 120-degree phase separation.

Failure Analysis.

No Output. An open inductor, L, a shorted capacitor, C, or a defective transformer, T1, as well as a defective pulse generator, firing circuit, or controlled rectifier can cause a no-output condition. Check the input voltage with a dc voltmeter to make certain that the dc source is available, and check both L and the primary and secondary of T1 for continuity with an ohmmeter. Also check T1 and capacitor C for shorts. Check the outputs of the pulse generator with an oscilloscope to determine that both output pulses are present. If the firing output pulses are present, check the values of R1 and R2 with an ohmmeter, and the forward and reverse resistance of firing diodes CR2 and CR3. Normally, to cause a loss of output it is necessary for both firing circuits and both controlled rectifiers to be defective simultaneously. If only one rectifier and one firing circuit operate, there will be a partial output rather than none at all. If there is no output from the firing circuit, both controlled rectifiers will remain blocked, and no ac output will be obtained. If dc firing gates are present but

neither CR1 or CR4 fires, both controlled rectifiers are probably defective. Firing of the controlled rectifiers may be checked by measuring the potential between anode and cathode with a dc voltmeter. If full supply voltage indication is obtained, the rectifier is not firing. If no voltage or only a few volts indication is obtained, the rectifier is conducting, since the forward resistance of the SCR is only a few ohms at most.

Low Output. Low dc supply voltage, a high resistance in controlled rectifiers CR1, CR4, or both, a leaky capacitor, C, or a defective transformer, T1, as well as erratic firing can cause a low output voltage. Check the dc supply voltage with a dc voltmeter, and measure the dc resistance of inductor L with an ohmmeter. Check capacitor C for leakage with a capacitance checker. Check the primary and secondary of T1 with an ohmmeter for a higher or lower resistance than normal.

Erratic firing can be caused by a change in the constants of the firing circuit, or a change in the gating characteristics of the controlled rectifier. Observe the firing circuit and the output with an oscilloscope. If the firing pulses occur at the same instant from the start of operation, but the controlled rectifiers fire at different times, it is most probable that the SCR characteristic has changed and the value of the firing resistor for that rectifier is incorrect. If the firing pulse appears normal and the parts in the gating circuit check normal, the fault must be a defective controlled rectifier. When the firing pulses are erratic or occur at different times in each cycle, each part in the pulse generator must be checked to determine where the lack of symmetry occurs.

SCR REGULATOR

Application.

The silicon-controlled rectifier regulator is generally used as a combined rectifier and regulator for high-current, high-voltage power supplies, particularly for transistorized equipments.

Characteristics.

Operates both as a rectifier and a regulator.

Controls on and off time of rectifier to regulate voltage and power output.

Uses a unijunction transistor as a relaxation oscillator to develop the firing pulse.


Uses bridge rectification with a transformer.

Circuit Analysis.

General. The silicon-controlled rectifier regulator uses a phase-controlled or time-controlled arrangement of rectifiers. Under normal load, the output is maintained by conduction over a portion of the ac cycle. When a load change produces a tendency for the output voltage to rise, the conduction cycle is reduced, providing a reduction in output voltage. When the load increases and the output voltage tends to fall, the conduction cycle is increased, providing an increase in output voltage. Thus, by controlling the conduction time of the rectifiers, the output is automatically regulated. Since there is no series resistance used to produce a controlled voltage drop, as in other types of regulators, the controlled rectifier circuit is usually more efficient. Normally, the circuit operates directly from the line and does not require a voltage transformer. Where higher voltages than line voltages are required, a transformer may be used to supply the

desired high voltage, provided that the proper voltage ratings are observed when selecting the semiconductor rectifiers.

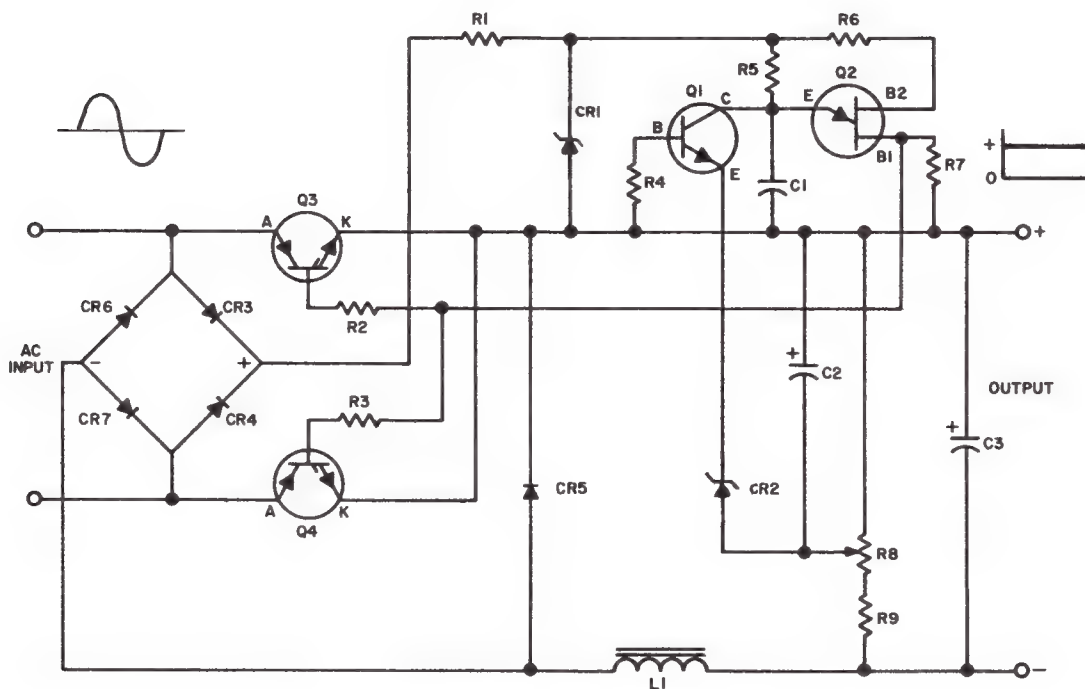Circuit Operation. The schematic of a typical silicon-controlled rectifier regulator is shown in the accompanying illustration.



Silicon-Controlled Rectifier Regulator

Transistor Q1 is the NPN control amplifier with base bias supplied by R4 and emitter voltage by breakdown diode CR2. Resistors R8 and R9 form a voltage divider across the output to provide a sensing voltage, with C2 used as a stabilizing capacitor. Resistor R1 and breakdown (Zener) diode CR1 provide a constant supply voltage to the control circuit from the secondary diode bridge rectifier consisting of CR3, CR4, CR6, and CR7. Silicon-controlled rectifiers Q3 and Q4 also form a primary bridge rectifier with diodes CR6 and CR7. Resistors R2 and R3 are current-limiting resistors for the firing circuit, which uses unijunction transistor Q2 to supply the firing pulse. The firing pulse is developed across the base B1 resistor R7, with R6 supplying the base voltage to B2; R5 is the emitter resistor of Q2 and also the collector resistor of Q1, while capacitor C1 is the charging capacitor. Inductor L1 and capacitor C3 are conventional power-supply filter elements for smoothing the dc output. Diode CR5 is a protective and stabilizing

element which discharges inductor L1 through the load when the controlled rectifiers are not conducting; it also eliminates any inductive transients generated by the rapid on-off switching of the rectifiers.



Normally, controlled rectifiers Q3 and Q4 are in a non-conducting condition until gated by a firing pulse. During this period, the secondary bridge circuit consisting of diodes CR3, CR7 and CR4, CR6 alternately conducts and produces a dc output for operation of the control circuit. This output is applied to current-limiting resistor R1 and breakdown diode CR1, which furnishes a relatively constant voltage to base-2 of unijunction transistor Q2 through R6, and charging current through R5 for capacitor C1. The secondary bridge circuit also supplies emitter voltage to Q2 and collector voltage to control transistor Q1. The circuit, consisting of R5, R6, R7, C1 and Q2, comprises a relaxation type oscillator. Normally, Q2 is biased practically to cutoff, and capacitor C1

charges at a rate determined by the RC value of R5 and C1. When C1 charges to a value sufficient to overcome the bias, heavy emitter current flows, and C1 is discharged through base-1 and R7. A positive pulse is developed across R7 by the heavy flow of current. When C1 is sufficiently discharged, the bias again cuts off current flow until C1 again reaches a peak firing charge. The pulse developed across R7 is used as a firing pulse for controlled rectifiers Q3 and Q4. Since Q3 and Q4 have their outputs connected in parallel, each rectifier will conduct when a positive anode voltage is applied coincident with a positive firing pulse, and since the anodes are connected across opposite sides of the line, one anode will be positive while the other is negative. Thus, a controlled rectifier fires for each half-cycle of applied ac. Current-limiting resistors R2 and R3 prevent excessive current flow in the trigger circuit. Once a rectifier fires, it continues to conduct until the ac polarity reverses, whereupon the reverse voltage applied to the cathode stops conduction; both rectifiers remain non-conducting until the next trigger pulse fires the other rectifier during the next half-cycle of operation. The length of the conduction period determines the output voltage and current delivered. Without filter L1 and C3, the dc output would be a series of pulses, but the filter, following conventional power supply filter action, smooths the output and provides a steady continuous voltage and current. To ensure this continuous current flow, CR5 conducts during the time that both Q3 and Q4 are inoperative because of the reverse voltage developed by the discharge of choke L1. Thus current continues to flow through the load as L1 discharges. The value of L1 (and C3) is very large to ensure a practically constant current supply.

Control amplifier Q1 uses a shunt form of control circuit operating on unijunction transistor Q2 to maintain a practically constant output voltage. Regulation is accomplished by using an NPN transistor and biasing the base in a forward direction. The base of Q1 is returned through R4 to the positive output voltage bus, and the emitter is biased with a fixed reference voltage through breakdown diode CR2, which is returned to voltage divider R8 and R9 connected across the power supply. Resistor R8 is adjustable, to permit setting the bias on Q1 for the desired operating voltage. Bypass capacitor C2 is a large value which helps stabilize the emitter voltage of Q1. Thus, with the emitter held at a fixed voltage by breakdown

diode CR2, any change of base voltage changes the conduction of Q1. When the base voltage of Q1 increases with an increase in output voltage, Q1 draws a larger emitter current and effectively shunts relaxation capacitor C1. Hence, C1 takes a longer time to charge and fire Q2, and controlled rectifiers Q3 and Q4 conduct for a smaller period of time, reducing the output voltage. When the output voltage tends to drop, the base bias on Q1 is reduced, and capacitor C1 charges more quickly as the shunting effect of Q1 emitter current is reduced. Hence Q3 and Q4 fire earlier in the cycle and produce a larger output voltage.

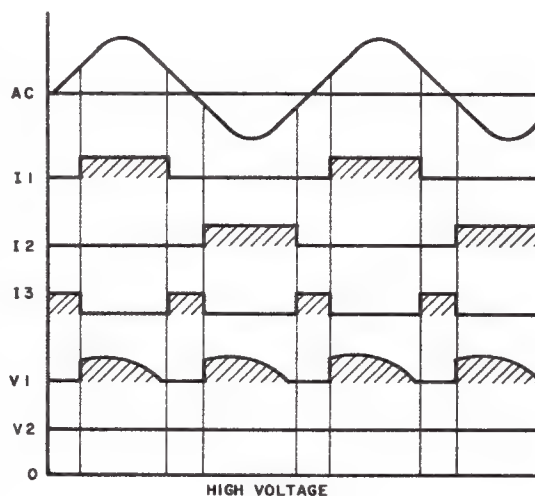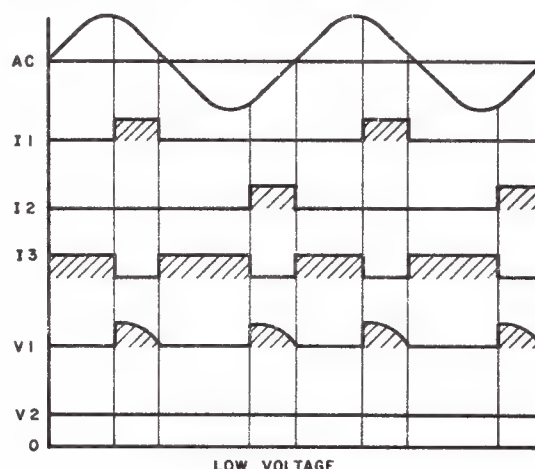The accompanying waveform charts show two typical forms of operation, one for a low voltage output and the other for a high voltage output.



Typical Waveforms

The ac input is a typical sine wave for both conditions. For the low-voltage output, I1, which is the current passed by Q3, occurs during the latter part of the positive half-cycle of input, while I2, the current passed by Q4, occurs for a corresponding period during the negative half-cycle. For each of these conduction periods, a dc output pulse is produced as shown by V1. During the non-conducting period, I3 flows through CR5, discharging inductance L1. The smoothing filter averages out the dc pulse to a constant value at the output, shown as V2. For the high voltage output, I1 and I2 occur earlier in the ac cycle and last for a longer period of time, producing a larger dc pulse output, as shown by V1. Because of the longer periods of controlled rectifier conduction, L1 discharges for a smaller period, shown by I3. With less discharge of L1 and a larger dc pulse output, the smoothing filter averages out a higher dc output voltage.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low-voltage ranges of conventional volt-ohmmeters. Be careful also to observe proper polarity when checking continuity, since a forward bias through any of the transistor or diode junctions will cause a false low-resistance reading.

No Output. Lack of line voltage, defective controlled rectifiers Q3 and Q4, lack of a firing pulse, a defective control circuit, or an open filter circuit can cause loss of output. Measure the line voltage to make certain that a blown primary fuse is not at fault. An oscilloscope will determine that there is a firing pulse at the gates of Q3 and Q4. If the firing pulse is present, both Q3 and Q4 are defective. If no firing pulse is present, the control circuit is at fault, or R2, R3 and R7 may be open; check them for proper value. If the resistors are satisfactory, measure the voltage across CR1. If no voltage is present, either CR3 or CR4 is defective, R1 is open, or CR1 may be shorted. Measure the value of R1 and check the diodes. Check that voltage is present at C1 and at

base-2 of Q2. If no voltage is present on base-2, check R6 for continuity and resistance. If no voltage is present at C1, check R5 for continuity and resistance, and check capacitor C1 for a short. If voltage is present at C1, there is still the possibility that either Q1 or Q2 is defective. The remaining circuit components, if defective, should not cause a no-output condition, but most probably a low output. If in doubt, check the value of R4, R8 and R9, and capacitor C2, and diode CR2. An open filter choke L1, or shorted output filter capacitor C3, may also be at fault; check L1 for resistance and continuity, and check C3 for a short with a capacitor checker.

Low Output. A low output can be caused by low line voltage; check the line voltage to make certain that the supply is not at fault. If the line voltage is normal but the output is constantly low, either the control circuit is defective, or controlled rectifiers Q3 and Q4, or diodes CR6 and CR7, may be defective. If low voltage persists, adjust R8 first in one direction, and then in the other direction and observe with a voltmeter whether the output can be returned to normal. If normal output can be obtained by readjustment of R8, the values of the parts in the control circuit may have changed; check the values of resistors R4, R5, R6, R7, R8, and R9. It is also possible for the value of C1 to change, or for it to be leaky, or for Q1, Q2, or CR2 to be defective. If the control circuit appears satisfactory, it is also possible for CR5 or filter capacitor C3 to be defective. Should the low voltage condition still persist, the possibility exists that choke L1 has developed a high resistance. Check the dc resistance.

High Output. A constant high output is most probably caused by too long a firing time resulting from a defective control circuit. First try readjusting R8 to determine if the voltage can be reduced to normal. If it cannot, transistor Q1 is probably being biased off, so that it has little shunting effect on the charging of C1. Measure the value of resistors R4, R5, R8, and R9, and check C2 for a short. If the high voltage still persists, measure the voltage across CR2 to be certain that it is operating. There also remains the possibility of C1 changing value and producing a smaller time constant and faster charge, or that Q1 is defective.

PART 2-6. ELECTROMECHANICAL POWER SUPPLIES

DYNAMOTOR

Application.

A dynamotor performs the dual functions of motor and generator to change the relatively low voltage of a dc power source into a much higher value for use in electronic equipments which employ electron tubes. The dynamotor may be contained within the electronic equipment, or it may be a separate unit external to the equipment. The dynamotor is frequently used in aircraft, small-craft, and portable-equipment applications where the primary source of power is dc.

Characteristics.

Input to dynamotor is dc; output is dc (or ac).

Dc output requires filtering to remove commutation ripple.

Requires filtering of input and output leads, and shielding of complete assembly to eliminate radiated interference.

A rotating machine; field poles are common to both motor and generator windings.

Has fair regulation characteristics.

Efficiency as high as 45 percent can be obtained.

Circuit Analysis.


General. The dynamotor is a rotating electro-mechanical device used to change one value of dc voltage to a different value of dc voltage. By definition, a dynamotor is a combination electric motor and a generator having two (or more) separate rotor windings and a common set of field poles; one winding receives direct current from a primary power source and operates as a motor to produce rotation of the armature assembly, while the remaining winding(s) operate(s) as a generator to produce a dc output voltage.

Circuit Operation. A simplified schematic for a typical dynamotor is shown in part A of the accompanying illustration, and a functional diagram is shown in part B of the illustration.

Capacitor C1 is an input filter capacitor provided to remove variations in the input dc voltage, caused by sparking of the brushes at the motor commutator; the capacitor also reduces interference which can be

radiated to other equipments connected to the same power source. Capacitor C2, r-f choke RFC, and capacitor C3 form a filter network at the output of the dynamotor to remove the effects of sparking at the generator commutator. Depending upon the design of the dynamotor, inductance-capacitance filters may be installed at both the input and the output to prevent undesirable voltage transients (hash), caused by commutation, from being radiated or coupled through the input and output leads to other electronic equipments. Also, in many dynamotor output circuits, because the generator commutation ripple frequency is relatively high, an iron-core choke and a capacitor (4 μ f or larger) are used to filter the dc output and remove the ripple-voltage component.

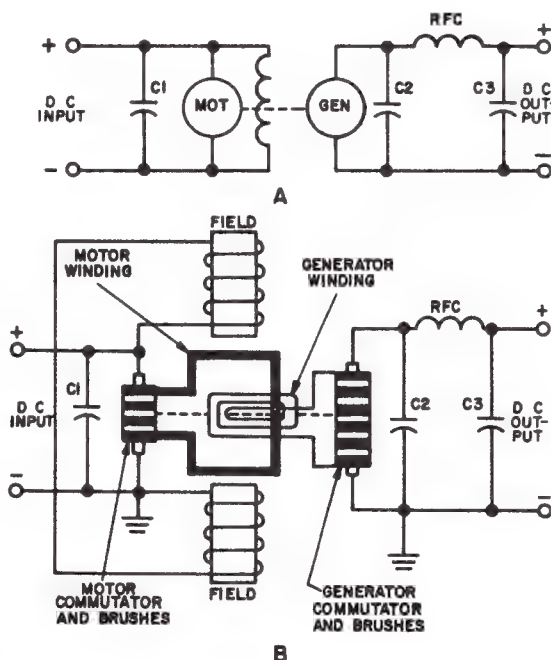The single, rotating armature assembly carries both the motor winding and the generator winding. Each winding terminates in a separate commutator; the commutators are usually located at opposite ends of the armature assembly. The two windings occupy the same set of slots in the armature, and terminate in their respective commutators. Since the motor and



Simplified Schematic and Functional Diagram of Typical Dynamotor

generator windings are both on the same rotor assembly, the field is common to both the motor and the generator. Because the field winding is connected in parallel with the motor winding, the motor is called a *shunt-connected*, or *shunt-wound*, motor. One of the desirable characteristics of this type of motor is that the speed of armature rotation remains relatively constant, regardless of the changes in load placed upon the motor; as a result, the output voltage is also held relatively constant.

When a dc voltage is applied to the low-voltage motor commutator (input terminals) of the dynamotor, current flows in the motor winding of the armature. At the same time, the applied voltage appears across the field coils and a current flows in them to produce a strong magnetic field. The flux produced by the field reacts with the flux produced by the motor winding; this results in torque, which causes the armature assembly to rotate. Because the generator winding is wound on the same assembly, it also rotates in the same magnetic field produced by the field coils. Therefore, since the generator winding cuts the magnetic field as it rotates, this action induces a voltage in the generator winding. The dc output voltage is taken from the generator commutator of the dynamotor, is filtered if necessary, and is applied to the load.

Since the motor and generator share a common magnetic field, the relationship of input voltage to output voltage depends on the ratio of the number of turns in the motor winding to the number of turns in the generator winding. For example, if the number of turns in the generator winding is increased (with respect to a given motor winding), the output voltage will increase accordingly; whereas, if the number of turns in the generator winding is decreased, the output voltage will decrease. In like manner, changing the number of turns in the motor winding (for a given generator winding) will affect the output voltage and also the speed of armature rotation. Changing the strength of the magnetic field will not appreciably affect the voltage ratio of the dynamotor. If the field strength is increased, the armature is slowed down, but the induced voltage in the generator winding remains unchanged; on the other hand, if the field strength is decreased, the armature speed increases, but the induced voltage remains the same. This is true because the field strength and the speed of rotation are inversely proportional to each other. For example, when the magnetic flux is increased in the

field, the armature speed decreases and the generator winding cuts more lines of flux at a lower speed; conversely, when the magnetic flux is decreased, the armature speed increases and the generator winding cuts fewer lines of flux at a higher speed. In either case, the induced voltage in the generator winding remains essentially the same.

The inverse relationship between armature speed and field strength is a basic principle of dc motors, and exists because of the counter emf which is generated by the armature cutting flux as it rotates through the magnetic field. The current induced by the counter emf flows in a direction opposite to that of the applied current. If the field strength of a motor is reduced, the value of the counter emf, which is dependent upon the strength of the field flux, is also reduced. A drop in counter emf allows a greater current to flow in the armature and this causes the motor speed to increase. The speed increases because the effect of the increase in armature current far exceeds that of the decrease in field flux. When the field strength is increased, the reverse action takes place. The increase in field current, and thus field strength, causes the counter emf to increase. This action decreases the applied current and thus reduces the motor speed.

One disadvantage of the dynamotor is that the output voltage cannot be adjusted to different values without changing the input to the motor and field windings. For this reason, the dynamotor must be designed for a given output voltage and load current.

Dynamotors operating from a dc source commonly have an input voltage rating of 6, 12, or 24 volts, and, depending upon the design and output requirements, can deliver 1200 volts or more to the load. A dynamotor is not necessarily restricted to only one generator winding—more than one winding is sometimes placed on the armature to provide for additional outputs, as required. For example, a low-voltage winding for the operation of electron-tube filaments may be incorporated in the armature assembly. In this case a separate commutator for dc output (or separate slip rings for ac output) and associated brushes are required for connection to the low-voltage winding.

One variation of this motor has, in addition to the shunt-connected field coils, another set of field coils connected in series with the motor winding. See the accompanying illustration. This type of motor is called a *compensated*, *compound*, or *stabilized shunt*

motor; the flux components developed in the shunt and series field coils are combined within the dynamotor to produce a strong magnetic field. Still another variation in design utilizes a permanent magnet to furnish the magnetic field; this variation is satisfactory for many applications, and is somewhat more efficient than an equivalent dynamotor with field coils, because less input current is required for operation.

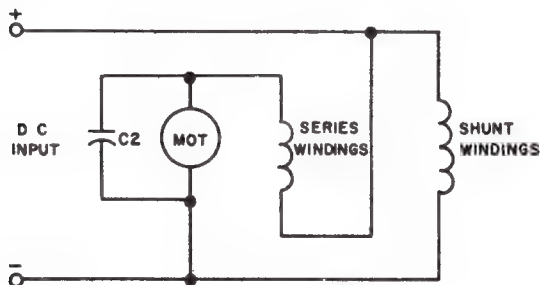


Diagram of Compound Motor

Failure Analysis.

General. Dynamotors are built to high standards and are characterized by long life and relatively trouble-free operation. If normal preventive maintenance is carried out at regular intervals as recommended by the equipment maintenance handbook, few failures will result. However, many dynamotors are subject to operation under conditions which are less than ideal, and, as a result, failures do occur.

The dynamotor can best be thought of as two separate machines combined in a single frame and sharing a common magnetic field. The relationship between motor and generator is purely mechanical. There is no electrical connection between the motor and generator windings. Since the currents in the two windings flow in opposite directions, their resultant magnetic effect is zero, which effectively isolates one winding from the other. In failure analysis procedures for the dynamotor, the two windings are treated separately; that is, the input circuit is treated as a conventional dc motor, and the output circuit is treated as a conventional dc generator.

In testing the dynamotor, the procedures are the same as those given in Navy publications for similar dc machinery (dc motors and generators). It must be

first established whether the trouble is of an electrical or a mechanical nature, or both; therefore, several of the more common dynamotor troubles are given in the paragraphs which follow, to help the technician recognize typical failures.

No Output. If the dynamotor fails to start, the input circuit and fuse should be checked to make certain that the applied input voltage is present and of the correct value. If necessary, the associated primary power source control or relay circuit should be checked to make certain that it is functioning normally. Also, a low applied input voltage or an open field circuit can prevent the motor from starting. If the dynamotor is operating but there is no output, the load should be disconnected and checks made to determine whether the load is shorted; after the load is disconnected, a voltage measurement can be made at the output terminals of the dynamotor to determine whether voltage is present. As a further check, a voltage measurement can be made at the high-voltage brush terminals to determine whether voltage is present at the output of the generator winding. If filter capacitor C2 or C3 should become shorted, there will be no output from the dynamotor; if capacitor C3 should become shorted, it is likely to result in the opening of the filter choke, RFC. If voltage is found to be present at the high-voltage brush terminals, the filter circuit used to remove the ripple voltage from the dc output should be checked for a shorted capacitor or an open filter choke in a manner similar to the procedures used for any other type of dc power supply.

Low Output. The primary power source is normally connected to the input of the dynamotor, using relatively short and heavy leads. Since a low applied voltage can cause a low output condition, the input to the dynamotor should be measured to determine whether the voltage is of the correct value.

A low-output condition can be the result of one or a combination of causes, and may be accompanied by a temperature rise or mechanical noise, or both. Opens or shorts in the armature windings, excessive sparking at either commutator, poor commutation because of the presence of dirt or oil, worn brushes, and brushes improperly seated are all typical troubles which contribute to a low-output condition.

If the load current is excessive, the output voltage may be below normal; therefore, the load current should be checked to determine whether it is within tolerance. As mentioned previously, this condition is

likely to be accompanied by a temperature rise in the machine and by sparking at the commutator. A leaky bypass capacitor (C2 or C3) or a leaky filter circuit capacitor, used to remove the ripple voltage from the dc output, may cause additional load and drop the output voltage accordingly.

Mechanical Noise. Excessive mechanical noise in a dynamotor is another indication of impending trouble. Although the dynamotor itself (or the unit in which the dynamotor is located) is usually mounted on some form of shock-mount support, to reduce mechanical vibration and noise resulting from armature rotation, various abnormal mechanical noises can still be heard, identified, and traced to the source. High mica, an out-of-round or eccentric commutator, high or low commutator segments, and worn bearings are all typical causes of abnormal operating noise.

Broken or chipped brushes, or brushes which are not seating properly, develop a characteristic high-frequency whine, while worn or dirty bearings generally cause a low-frequency (or grinding) sound. Bearing failure is frequently the result of wear caused by lack of proper lubrication; badly worn bearings may allow the rotating armature assembly to strike the field poles and create additional noise.

Commutator Sparking. Excessive sparking at the commutator is generally an indication of brush or commutator trouble. Sparking brushes may also be an indication of excessive load current; therefore, the load current should be measured to determine whether it is excessive. As mentioned previously, this condition will likely be accompanied by a rise in the temperature of the dynamotor.

Worn brushes, lack of brush pressure, and brushes not seating properly are common causes of brush sparking; open coils in the armature assembly will also cause brush sparking. Typical commutator troubles are high or low segments, an out-of-round or eccentric commutator surface, and a high mica condition. The high-mica condition occurs when the commutator segments have worn down below the insulating mica separator strips between the copper segments. If any one of the three commutator conditions mentioned is found to exist in the dynamotor, the machine will require disassembly and repair (by the electrical shop), since it will be necessary to turn down the commutator in a lathe and then undercut the mica to a level which is below the surface of the commutator segments.

Temperature Rise. An excessive temperature rise is one of the first indications of trouble. Dynamotors are designed for either continuous or intermittent duty, and are rated accordingly. Occasionally, a dynamotor which is rated for intermittent duty is run continuously; in this case the dynamotor is not being operated in accordance with its design rating, and a temperature rise may be expected.

An overload condition is a common cause for overheating; therefore, the load current should be checked to determine whether it is excessive. Poor ventilation resulting from restricted cooling vents or clogged internal air passages can cause a temperature rise because of the lack of adequate cooling-air circulation. Shorts in the commutator segments, shorted turns in the armature or field windings themselves, or winding shorts to metal parts of the armature or frame are all typical causes of dynamotor heating. Also, worn brushes or high mica on the commutator, or both, can contribute to an abnormal temperature rise. In any event, excessive heating of a dynamotor should always be considered an effect rather than a cause of trouble.

INVERTER

Application.

An inverter is one form of rotary converter, and is used to change the relatively low voltage of a dc power source to ac for use by the electrical load. Depending upon the design of the inverter, the output can be either single-phase or polyphase (multi-phase) ac; the frequency of the output voltage is generally 60, 400, or 800 Hz. The inverter is frequently used in aircraft, shipboard, and small-craft applications where the primary source of power is dc.

Characteristics.

Input to inverter is dc; output is ac.

Requires filtering of input leads to eliminate possible interference resulting from commutation.

A rotating machine; commonly uses two sets of rotors and stators, one set (rotor and stator) functioning as a motor and the other as a generator.

AC output commonly obtained by either of two methods: a stationary field with output taken from a rotating armature, using slip rings and brushes, or a rotating field (rotor) with output taken from one or more stationary armature (stator) windings.

Frequency of output controlled by speed of rotation.

Has fair regulation characteristics; output varies with dc input.

Maximum efficiency obtained when power factor of load is near unity.

Circuit Analysis.

General. The inverter is a rotating electro-mechanical device for converting direct current into alternating current. The inverter is a combination electric motor and alternator; the motor is the prime mover which produces the necessary rotation of an armature, field, or rotor assembly. By definition, the winding in which the output voltage is generated is called an *armature winding*, and the winding through which dc is passed to produce an electromagnetic field is called the *field winding*.

Inverters fall into three general classes, depending upon the ac generator design. These classes are called the *rotating- or revolving-armature*, the *rotating- or revolving-field*, and the *inductor-type alternator*.

In the rotating- or revolving-armature ac generator, the stator provides a stationary electromagnetic field. The rotor, acting as the armature, revolves in the magnetic field, cutting the lines of force, and produces the desired output voltage. The armature ac output is taken through slip rings and brushes. One limitation of this type of generator is that the output is taken through sliding contacts (slip rings and brushes); therefore, this type of machine is usually limited to low-power, low-voltage applications.

The rotating- or revolving-field ac generator is most widely used. In this type of machine, current from a dc source is passed through slip rings and brushes to field coils wound on a rotor. Thus, a magnetic field is produced in the rotor of fixed polarity, and, since the rotor is driven by the motor, a rotating magnetic field is created. The rotating magnetic field extends outward and cuts the stationary armature (stator) windings; as the rotor turns, ac is produced in the stationary windings. The output is taken from the stationary windings, either single-phase or polyphase, through the output terminals to the load without the need for slip rings and brushes.

In the inductor-type alternator, a field (exciter) winding and an armature winding are both contained within the same stator frame. The rotor, including its pole pieces, is made of soft-iron laminations. DC is supplied to the field (exciter) winding, thus estab-

lishing a magnetic field in the stator. As the rotor revolves, the poles of the rotor become aligned with the poles of the stator, and maximum flux density is produced. As the poles move out of alignment, the flux decreases. The sinusoidal increase and decrease in magnetic flux in the rotor and stator as the rotor rotates induces an alternating voltage in the stationary armature windings. The ac output is taken from the stationary armature windings without the need for slip rings and brushes. This type of machine is frequently used to generate single-phase, high-frequency ac.

The frequency of the ac generator voltage depends upon the speed of rotation of the rotor and the number of pairs of poles in the machine. That is:

$$F = \frac{P \times \text{rpm}}{60}$$

where P is the number of pairs of poles, and rpm is the revolutions of the rotor per minute. The following examples are provided to illustrate the use of the formula in solving for rpm, F, and P.

Alternators are generally designed with a multipole rotor and a multipole stator; however, for simplicity, the first example will consider a basic alternator having only a two-pole rotor and a two-pole stator. In this machine one complete cycle of ac voltage will be induced in the armature winding for each complete revolution of the rotor as it passes under the two (north and south) poles of the stator. When the rotor of this simple machine rotates at a rate of 3600 rpm, the frequency (in Hz) of the ac output voltage is easily found by using the basic formula. Thus:

$$\begin{aligned} F &= \frac{P \times \text{rpm}}{60} \\ &= \frac{1 \times 3600}{60} \\ &= 60 \text{ Hz} \end{aligned}$$

If six poles are provided on the rotor and on the stator of an ac generator, then during each revolution each pair of rotor poles passes under three pairs of stator poles, and thus generates three complete cycles of ac output. Since there are three pairs of poles provided on the rotor, it follows that three times as many cycles will be generated during one rotor revolution as will be for a single pair, or a total of nine

hertz. Assuming again that the output frequency is 60 Hz, the required rpm of the rotor may be found by transposing the basic formula to solve for rpm. Thus:

$$\begin{aligned} \text{rpm} &= \frac{60 F}{P} \\ &= \frac{60 \times 60}{3} \\ &= \frac{3600}{3} \\ &= 1200 \text{ rpm} \end{aligned}$$

This example clearly illustrates the inverse relationship existing between the speed of rotor rotation and the number of pairs of poles of the alternator. For the same output frequency as in the first example (60 Hz), when the number of pairs of poles was increased by a factor of three, the required rpm of the rotor was decreased by one third, that is, from 3600 to 1200 rpm.

When the speed of rotor rotation and the output frequency of the alternator are known, the number of pole pairs is easily found. For example, if $F = 400$ Hz and the rotor rotation is 3000 rpm, then the number of pairs of poles is found as follows:

$$\begin{aligned} P &= \frac{60 F}{\text{rpm}} \\ &= \frac{60 \times 400}{3000} \\ &= \frac{24000}{3000} \\ &= 8 \text{ pairs of poles} \end{aligned}$$

When the load on a generator is changed, the terminal voltage varies with load. The amount of variation depends on the design of the generator and the power factor of the load. Unless the load is fixed and constant, some form of voltage regulation is necessary to maintain the output voltage relatively constant under conditions of varying load. In practice, once a machine is designed and built, the output voltage is controlled by varying the dc excitation voltage applied to the field winding. When an ac generator is


equipped with a voltage regulator, the regulator uses the ac output voltage which is to be regulated as a sensing voltage to control the amount of current used to excite the field.

The operation of a typical regulation system can be briefly explained as follows: a drop in output voltage sensed by the regulator causes the regulator to increase the field current, and an increase in field current causes a corresponding increase in output voltage to compensate for the original drop in output voltage. Stated conversely, if the output voltage should rise, the regulator decreases the field current, causing a corresponding decrease in output voltage to compensate for the original rise in voltage. Thus, the regulator senses a change in output voltage and compensates for this change by altering the field (exciting) current accordingly. A detailed description of the construction and operation of various voltage regulators can be found in Navy publications covering basic electricity, or in course materials for EM and AE ratings.

Several typical inverters will be discussed briefly in the paragraphs that follow.

Inverter with Permanent-Magnet Rotor. One of the simplest inverters is the permanent-magnet-type inverter shown in the accompanying schematic. This rotating-field-type inverter is designed to supply single-phase ac at a frequency of either 400 or 800 Hz to a constant and relatively light load.

The inverter consists of a dc motor and a permanent-magnet-type ac generator assembly combined within a single housing. The dc motor is a shunt-connected, or shunt-wound, motor with armature and commutator mounted on a single shaft, and rotating within the stationary field (stator) windings. The motor armature rotates within the stationary field, and the commutator rotates between a pair of spring-loaded brushes. The motor brushes are

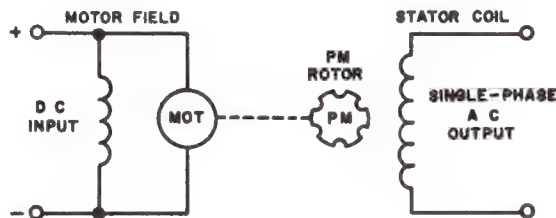

Simple Inverter with Permanent-Magnet Rotor;
Single-Phase Output


mounted in holders that are placed on opposite sides of the motor housing; the construction is such that the brushes may be easily removed for inspection and replacement.

The ac generator portion of the inverter consists of a stationary armature and a rotating permanent-magnet field. The permanent-magnet rotor is mounted on the same shaft as the motor armature and commutator. The rotating magnetic field is produced by a six-pole, permanent-magnet rotor, with alternate poles around the circumference magnetized alike. The stationary armature (stator) is a six-pole, six-slot, laminated stator with the single-phase output winding mounted in the slots of the stator. A magnetic field exists about the poles of the permanent-magnet rotor, and as the rotor revolves the poles of the rotor align with the poles of the stator to produce maximum flux density in the stator. As the poles move out of alignment, the flux decreases in the stator to a minimum, and the flux polarity reverses as the rotor poles move into alignment with the stator once again. The sinusoidal changing of flux polarity as the rotor poles move past the stator poles induces an alternating current in the armature windings located in the slots of the stator. The ac output is taken from the stationary armature windings, without the need for slip rings and brushes. Since this inverter is designed for use with a constant load, no provision is made for either voltage or speed regulation.

The permanent-magnet-type inverter can also be made to furnish three-phase output. The three-phase inverter, shown in the accompanying schematic, is essentially the same size and weight as the single-phase inverter described above.


The dc motor is essentially the same as that described for the single-phase machine. Also, the six-pole, permanent-magnet rotor of the generator is placed on the same shaft and rotates with the motor armature, as described for the single-phase machine. The three-phase stationary armature consists of a nine-pole laminated stator. In this generator nine separate coils are wound in the stator slots; each set of three coils, located 120 degrees apart on the stator, are connected in series to form an output winding for each phase. The three sets of series coils produce output voltages which differ in phase by 120 electrical degrees; the stator windings are shown on the schematic as a three-phase wye, or star, connection.

As in the single-phase machine, a magnetic field exists about the six poles of the permanent-magnet rotor. When three of the rotor poles spaced 120 degrees apart are in alignment with three of the stator poles of the same winding phase, the remaining three rotor poles are positioned between the remaining six stator poles. Thus, when maximum flux is produced in one set of stator poles, one of the remaining two sets of stator poles is increasing in flux density, while the other set is decreasing in flux density. The flux polarity in any stator pole reverses as alternate rotor poles have past the individual stator poles; as a result, the changing flux induces an alternating current in each of the three armature windings which is 120 degrees out-of-phase with the current produced in either of the other two armature windings. The three-phase ac output is taken from the three stationary armature windings without the need for slip rings and brushes. Since this inverter is designed for use with a constant load, no provision is made for either voltage or speed regulation.

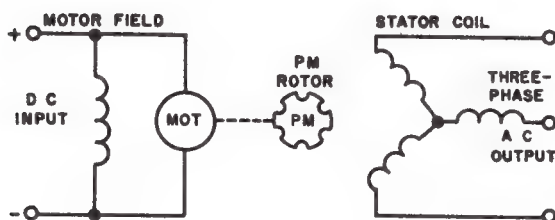

Simple Inverter with Permanent-Magnet Rotor;
Three-Phase Output

Inverter with Rotating Armature. The inverter shown in the accompanying schematic is typical of many inverters with separate dc fields for the motor and generator sections. This type of inverter has a stationary field, and the armature windings rotate within the magnetic field produced by the field. Although the schematic shows an inverter with three-phase output, the same principles discussed here apply to an inverter with single-phase output.

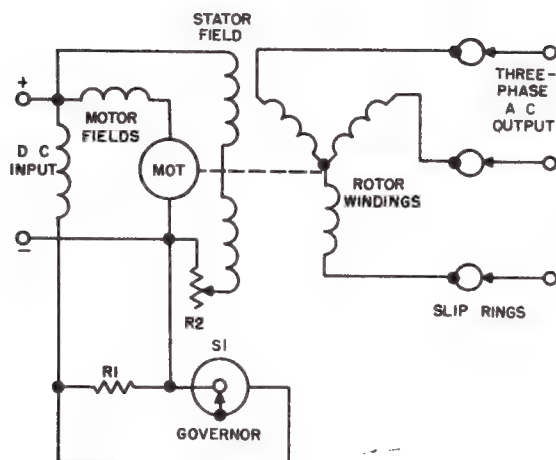

Inverter With Rotating Armature

The dc motor shown in the accompanying schematic has a compounded field consisting of both a series and a shunt winding. This type of motor provides better speed regulation under conditions of varying load; as a result, the output frequency can be held relatively constant. To further improve the frequency stability of the inverter, a speed governor is incorporated in series with the shunt winding to control the shunt-field current and, therefore, the magnetic flux developed by the shunt field. The governor is a centrifugal type, mounted on the armature shaft of the motor. Electrical connection to the governor contacts is accomplished by two slip rings, located at the commutator end of the armature; brushes are used to contact the slip rings and complete the circuit to the speed regulating resistor, R1. The governor controls the speed of the motor by placing resistor R1 into and out of the shunt-field circuit. For example, when the motor attempts to increase speed, the governor contacts close to shunt the resistor, R1. (The governor contacts open and close by centrifugal action.) As a result, the current through the shunt-field winding increases, the magnetic flux developed by the field increases, and the motor speed is reduced accordingly. Conversely, when the motor attempts to decrease speed, the governor contacts open and resistor R1 is placed in series with the shunt-field winding. In this case, the current through the shunt-field winding decreases the magnetic flux developed

also decreases, and the motor speed is increased accordingly. By controlling the motor speed, the centrifugal governor thus controls the resulting frequency of the ac output.

The generator portion of the inverter consists of a stationary four-pole field and a three-phase, wye- or star-connected rotating armature. The armature windings are distributed and mounted in the slots of the laminated rotor core, and are brought out to three slip rings which are mounted on the rotor shaft; brushes contact the slip rings to complete the circuit.

The stationary field, consisting of four series-connected coils (each placed on a pole piece), is supplied direct current from the dc input to the motor. The strength of the magnetic flux developed by the field is determined by the current which passes through the field windings; consequently, this current also determines the amplitude of the output voltage produced in the armature windings. Resistor R2 is placed in series with the field windings to adjust the value of current through the windings and thus control the amplitude of the ac output voltage in all three phases.


If the electrical load on the inverter is relatively constant, the output voltage is likely to remain relatively constant; thus, resistor R2 is usually adjusted under conditions of normal load to obtain the desired output voltage. However, when the electrical load is subject to considerable variation, a system of voltage regulation must be employed. As mentioned in a previous paragraph, voltage regulation can be achieved by sensing the ac output voltage and then controlling the magnetic field to compensate for the original output-voltage variation. A typical system for output-voltage regulation uses dc voltage rectifier from one of the phases to control a carbon-pile voltage regulator. The regulator, in turn, substitutes for resistor R2 in the field circuit and varies the current through the field windings; thus, the magnetic flux of the field is varied. As a result, the ac output voltage amplitude is controlled by action of the carbon-pile regulator to compensate for changes occurring in the output voltage. (A detailed description of generator and alternator voltage regulation is found in Navy publications covering basic electricity and, therefore, is not given in this handbook.)

In the inverter described here, the output can be set to a given value by adjustment of resistor R2, or the output can be automatically regulated by a regulating system which substitutes for resistor R2. The

governor assembly, together with resistor R1, on the dc motor controls the speed of rotation and thus the frequency of the ac output. One disadvantage of this inverter is that all current delivered to the load must pass through the slip rings and brushes of the armature assembly. Therefore, the use of this type of inverter is usually limited to low-power, constant-load applications, where the use of slip rings and brushes will not seriously affect operating efficiency.

Inverter with Rotating Field. The inverter shown in the accompanying schematic has a rotating field and stationary armature windings; the machine is similar to the inverter using a permanent-magnet rotor, described earlier, except in this instance a dc rotor field is used. Although the schematic shows an inverter with three-phase output, the same principles discussed here apply to an inverter with single-phase output.

The dc motor shown in the accompanying schematic has a compounded field consisting of both a series winding and a shunt winding. The motor is identical with the motor just described for the inverter with a rotating armature. The motor is equipped with a centrifugal governor, which controls the motor speed by shunting resistor R1 into and out of the shunt-field circuit. (The speed-regulating action of the governor assembly and its effect upon output frequency was described in a preceding paragraph.)

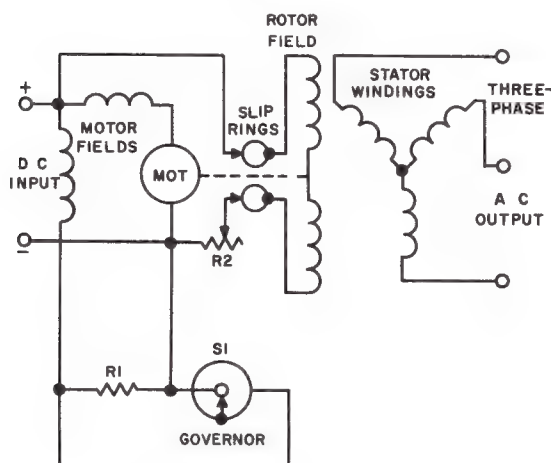

Inverter With Rotating Field

The generator portion of the inverter consists of a rotating field assembly and stationary armature

windings. DC exciting coils for the rotating field are wound on the six-pole rotor, and are brought out to two slip rings which are mounted on the rotor shaft; brushes contact the slip rings to complete the dc circuit to the rotating field. The direct current for the rotating field is obtained from the dc input to the motor. The strength of the magnetic flux developed by the rotating field is determined by the current which passes through the field windings; consequently, this current also determines the amplitude of the output voltage produced in the stationary armature windings. Resistor R2 is placed in series with the field windings to adjust the value of current through them, and thus controls the amplitude of the ac output voltage in all three phases.

The three-phase stationary armature consists of a nine-pole, laminated stator, similar to the armature described previously for the three-phase inverter using a permanent-magnet rotor. The nine separate coils of the stator are connected to form three sets of three series coils each; the three sets of series coils produce output voltages which differ in phase by 120 electrical degrees. The armature (stator) windings are shown on the schematic as a three-phase wye or star connection.


If the electrical load on the inverter is relatively constant, the output voltage is likely to remain relatively constant; thus, resistor R2 is usually adjusted under conditions of normal load to obtain the desired output voltage. However, when the electrical load is subject to considerable variation, a system of voltage regulation must be employed. The voltage and output-frequency regulation principles for this inverter are identical with those given in previous paragraphs for the inverter with rotating armature.

One advantage of this type of inverter is that the three-phase ac output is taken directly from the stationary armature windings without the need for slip rings and brushes; for this reason the inverter is commonly used for high-power applications, because the load current is not required to pass through the resistance offered by moving contacts (slip rings and brushes).

Inductor-Type Alternator. The inverter shown in the accompanying schematic is typical of inverters which operate on an induction principle and employ stationary field and armature windings located side-by-side in a common frame; the stator windings and their associated poles share a common rotor assembly.

The dc motor shown in the accompanying schematic has a compounded field consisting of both a series winding and a shunt winding. The motor is identical with the motor previously described for the inverter with a rotating armature. The motor is equipped with a centrifugal governor which controls the motor speed by shunting resistor R1 into and out of the shunt-field circuit. (The speed-regulating action of the governor assembly and its effect upon output frequency were described in the discussion on Inverter with Rotating Armature.)


The generator portion of the inverter consists of a six-pole, laminated rotor mounted on the end of the dc motor shaft, and a stator assembly with two dual-pole pieces on which the stator windings are mounted. The two dc field (exciting) coils, connected in series, are mounted around both dual-pole pieces, which are opposite each other in the stator assembly; the four ac armature coils, connected in series, are mounted around the individual poles of the two dual-pole pieces.

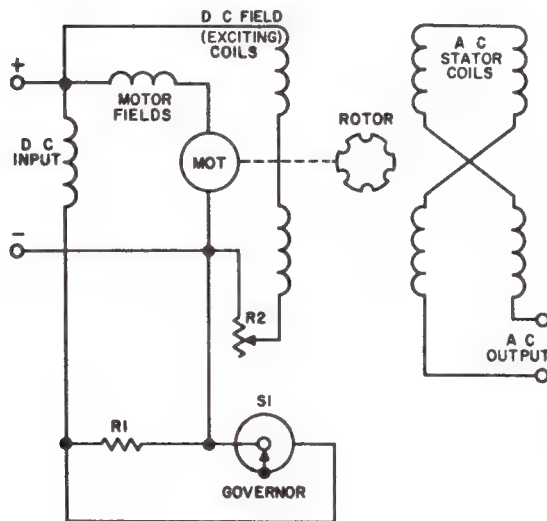

**Inverter With Inductor-Type Alternator;
Single-Phase Output**

Direct current is supplied to the dc field (exciting) coils of the stator from the dc input to the motor. The field coils establish a magnetic field in each of the two dual-pole pieces that make up the stator as-

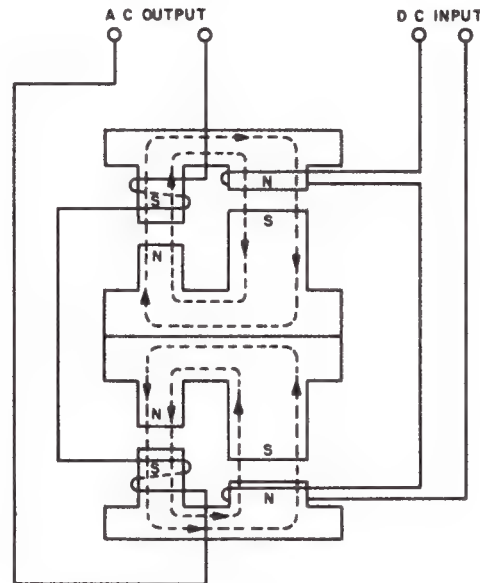sembly, as shown in the illustration below. The current passing through the field determines the strength of the magnetic flux developed by the dc field winding, and thus the amplitude of the output voltage. Resistor R2 is placed in series with the field winding to adjust the value of field current, in order to control the amplitude of the ac output voltage.



Basic Inductor-Type Alternator

For a given value of current in the dc field winding (as determined by the adjustment of resistor R2), the strength of the field flux linking the ac armature coils on the stator will vary as the reluctance of the magnetic circuit is varied. Because of the high permeability (as compared with air) of the soft iron laminations of the rotor, the reluctance is varied as the poles of the revolving rotor continuously move in and out of alignment with the poles of the stator. As the rotor revolves and varies the reluctance of the magnetic circuit, the strength of the magnetic field and, consequently, the amount of induction coupling to the ac coils will also vary. The periodic variation in induction coupling, which is sinusoidal in nature, induces an alternating current in the ac armature coils. This current achieves a maximum value at a time when the poles of the rotor and stator are in alignment, and reaches a minimum value when the

rotor and stator poles are farthest out of alignment. One cycle of generated voltage occurs in the armature winding as the rotor rotates through an angle equal to the angle of separation for adjacent rotor poles. Since it is relatively easy to build a machine with a large number of rotor poles, the inductor-type design is readily adaptable to the generation of high frequencies. For a given number of rotor and stator poles, the induced voltage in the armature windings alternates at a frequency determined by the speed of the rotor assembly.

If the electrical load on the inverter is relatively constant, the output voltage is likely to remain relatively constant, and, as for the other inverters previously described, resistor R2 is usually adjusted under conditions of normal load to obtain the desired output voltage. However, when the electrical load is subject to considerable variation, a system of voltage regulation must be employed. The voltage and output-frequency regulation principles for the inductor-type alternator are identical with those given in previous paragraphs for the inverter with rotating armature.

The inductor-type alternator is frequently used in applications where high-frequency output at a moderate power level is required. One advantage of this type of inverter is that no slip rings or brushes are used for the alternator portion of the inverter, the output being taken directly from the armature windings.

Failure Analysis.

General. Inverters generally provide trouble-free operation as long as normal preventive maintenance is performed in accordance with the procedures recommended by the equipment maintenance handbooks. However, the technician must be aware of possible failures and be able to recognize such failures when they occur.

The inverter can best be thought of as two separate machines combined in a single housing and sharing a common rotating shaft. The relationship between the dc motor and ac generator (or alternator) is essentially a mechanical one; therefore, in failure-analysis procedures for an inverter, the dc motor and ac generator are usually treated as separate machines mechanically coupled to each other. In testing inverters, the procedures are the same as those given in Navy publications for similar dc motors and ac generators. It must be first established whether the

trouble is of an electrical or a mechanical nature, or both; therefore, several of the more common dc motor and ac generator troubles are given in the paragraphs which follow to help the technician recognize typical failures.

Temperature Rise. As stated previously for the dynamotor, an excessive temperature rise in an inverter is one of the first indications of trouble. Excessive heating of an inverter should always be considered as an effect rather than a cause of trouble.

An overload condition is a common cause for overheating; therefore, the load current should be checked to determine whether it is excessive. The three-phase inverter offers a problem in distributing the electrical load equally between the three phases. For this reason, it is possible that one phase may become overloaded and cause overheating of the machine because of the load unbalance; therefore, the load current in each phase should be checked to determine whether it is excessive and whether the load is balanced for each phase.

Poor ventilation, resulting from restricted cooling vents or clogged internal air passages, can cause a temperature rise because of the lack of adequate cooling-air circulation. Shorts in the dc motor commutator segments or shorted turns in the motor armature windings, shorted turns in the motor field windings themselves, or windings shorted to metal parts of the armature or frame are all typical causes of motor heating. Worn brushes or high mica on the commutator, or both, can also contribute to an abnormal temperature rise in the motor. Shorted turns in the windings of the ac generator (alternator) rotor or stator can also contribute to a temperature rise in the machine.

Mechanical Noise. Excessive mechanical noise in an inverter is another indication of impending trouble. Although the inverter itself (or the unit in which the inverter is located) is usually mounted on some form of shock-mount support, to reduce mechanical vibration and noise resulting from the rotating parts of the machine, various abnormal mechanical noises can still be heard, identified, and traced to the source. High mica, an out-of-round or eccentric motor commutator, high or low motor commutator segments, and dry or worn bearings are all typical causes of abnormal operating noise.

Broken or chipped motor brushes, or brushes which are not seating on the commutator properly, develop a characteristic whine; however, this noise

may not be readily heard because loose rotor or stator laminations in the ac generator portion of the machine may develop a high-frequency sound which masks the commutation noise. Worn or dirty bearings generally cause a low-frequency (or grinding) sound, and may also result in the generation of additional heat. Bearing failure is frequently the result of wear caused by lack of proper lubrication; badly worn bearings may allow the rotor assembly to strike the stator and create additional noise. Furthermore, a rotor which is not centered in the stator because of worn bearings, although it may not strike the stator, is likely to cause some localized heating in the stator.

Motor Commutator Sparking. Excessive sparking at the motor commutator is generally an indication of brush or commutator troubles. Sparking brushes may also be an indication of open or shorted coils in the armature winding, or an indication of a grounded, open, or shorted field winding. As mentioned previously, this condition will likely be accompanied by a rise in temperature of the machine. Worn brushes, lack of brush pressure, brushes sticking in their holders, or brushes not seating properly are also causes for sparking.

Typical dc motor commutator troubles are high or low segments, an out-of-round or eccentric commutator surface, or a high mica condition. (The high mica condition occurs when the commutator segments have worn down below the insulating mica separator strips between the copper segments.) If any one of the three conditions mentioned is found to exist in the motor commutator, the machine will require disassembly and repair (by the electrical shop), since it will be necessary to turn down the commutator in a lathe and then undercut the mica to a level which is below the surface of the commutator segments.

No Output. If the inverter fails to start, the input circuit should be checked to make certain that the applied dc voltage is present and of the correct value. If necessary, the associated primary power source control or relay circuit should be checked to make certain that it is functioning normally. A low applied input voltage or an open field circuit can also prevent the motor from starting.

If the inverter is running but there is no output, the load should be disconnected and checks made to determine whether the load is shorted; a voltage measurement can be made at the output terminals of

the ac generator after the load is disconnected to determine whether voltage is present. In the case of the three-phase inverter, measurements should be made on each of the three phases. With the inverter disconnected from its input and output circuits, continuity measurements can be made in accordance with the equipment maintenance handbook instructions to determine whether any of the windings are open.

Low Output. A low-output condition can be the result of one or a combination of causes, and may be accompanied by a temperature rise or mechanical noise, or both. Low input dc to the exciter coils, poor slip ring contact because of the presence of dirt or oil, worn brushes, and improper brush tension are typical troubles which contribute to a low-output condition.

Shorted windings can cause low output, and this condition is nearly always accompanied by a temperature rise in the inverter. If the load current is excessive, the output voltage may be below normal; therefore, the load current should be checked to determine whether it is within tolerance. For the three-phase generator or alternator, the load current for each phase should be checked to determine whether it is within tolerance and whether the load is balanced for each phase. As mentioned previously, an unbalance in the load of the three-phase machine is likely to cause a temperature rise in the machine.

A low-output condition can also be caused by a decrease in the current through the exciting field; as a result, the magnetic flux in the field decreases and the output voltage decreases accordingly. If the dc (exciting) field current is controlled by a voltage regulating system, it is possible that the system is faulty. If the field current is established by means of an adjustable resistor (resistor R2), it is possible that the value of the resistor is too high. In the case of the inverter with rotating field, the slip rings and brushes may cause this condition because of excessive contact resistance.

High Output. A high-output condition is usually caused by an excessive current in the exciting field; as a result, the magnetic flux in the field increases and the output voltage increases accordingly. If the dc (exciting) field current is controlled by a voltage regulating system, it is possible that the system is faulty. If the field current is established by means of an adjustable resistor (resistor R2), it is possible that the value of the resistor is too low.

Unsteady Output Voltage. The cause of unsteady or fluctuating output voltage, sometimes called *voltage hunting*, varies, depending on the design of the inverter and the method incorporated in the machine to regulate the value of the output voltage. If the output voltage fluctuates (assuming the speed of rotation to be relatively constant), this condition may be caused by fluctuations of the current in the exciting field; as a result, the magnetic flux in the field will also fluctuate. This condition may also be caused by a defective voltage-regulating system (mentioned previously under the high-output and low-output conditions discussed above), or, if the inverter has a rotating field, the slip rings and brushes may not be in good contact with each other.

Unsteady or Incorrect Output Frequency. The cause of unsteady output frequency, sometimes called *frequency hunting*, or simply *hunting*, and the cause of incorrect output frequency varies, depending on the design of the inverter and the method incorporated in the machine to regulate the speed of rotation. If the speed of rotation fluctuates, the output frequency will also fluctuate, since the speed of the rotor determines the frequency of the alternations in the armature windings. Thus, if the rotor speed is below normal, the output frequency will also be below normal, and, conversely, if the rotor speed is above normal, the output frequency will also be above normal. If the dc motor has a centrifugal-governor assembly, the governor contacts, slip rings, and brushes should be inspected for possible defects. Instability in the motor speed may also be evidenced by mechanical noises, temperature rise, brush sparking, etc, mentioned earlier in this discussion.

NONSYNCHRONOUS VIBRATOR SUPPLY

Application.

The nonsynchronous vibrator supply is commonly employed in many portable and mobile equipments where the primary power source is a storage battery. This supply produces a relatively high value of dc voltage at a moderate load current from a low-voltage dc source. The supply is commonly used to provide high voltage for the operation of small receivers, transmitters, and public-address systems, although in many recent equipments the transistorized dc-to-dc converter, described earlier in this section of the handbook, is used in lieu of the vibrator supply.

Characteristics.

Input is low-voltage dc; output is high-voltage dc.

Input voltage is usually 6, 12, or 24 volts; special vibrators for other input voltages are available.

Typical vibrator operating frequency is between 60 and 250 Hz.

Output high-voltage dc is normally between 180 and 300 volts; load current is normally between 60 and 200 milliamperes.

Output circuit can be arranged to furnish negative or positive high voltage to the load.

Output dc requires filtering; ripple-voltage frequency is relatively high, and is determined by the vibrator frequency and the rectifier circuit used.

Electron-tube or semiconductor diodes are used in the rectifier circuit; rectifier circuit may be half-wave, full-wave, bridge, or voltage-doubler.


Regulation is fair; output voltage regulation may be employed.

Vibrator must be shielded and leads filtered to prevent r-f radiation and interference to other circuits.


Circuit Analysis.

General. A nonsynchronous vibrator supply converts direct current from a low-voltage power source into alternating current that can be rectified and used to obtain a higher dc output voltage for use as the plate and screen voltages in the operating equipment. The supply offers the advantages of light weight, small physical size, and good efficiency; its main disadvantages are the limitation in output current and the tendency to produce interference to other circuits. Therefore, the vibrator must be well-filtered and shielded. Another disadvantage is that, although the vibrator itself is relatively inexpensive, its useful life is shorter than that of a dynamotor or of the transistors in a dc-to-dc converter. However, when this type of power supply is used within its rating, it will furnish reliable power for low-power communications and public address equipment.

Nonsynchronous Vibrator Types. A vibrator is an electromechanical mechanism, sometimes called an *interrupter*, which acts as a high-speed reversing switch to control (or interrupt) the current in each half of a tapped primary winding in a special step-up power transformer. The operation of a simple vibrator as a high-speed switching device can be understood by reference to the accompanying illustration of a fundamental vibrator circuit.

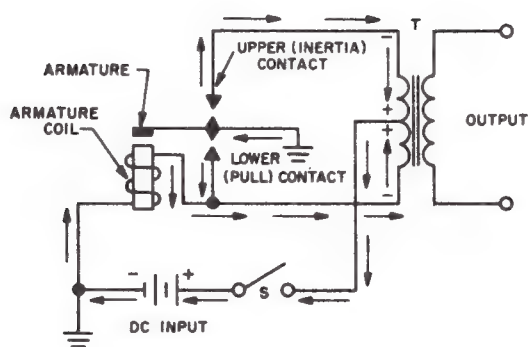

A

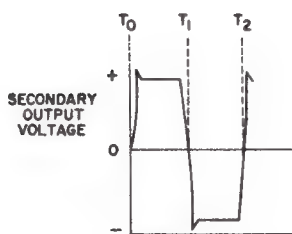

B

Fundamental Vibrator Circuit and Output Voltage Waveform

In part A of the illustration, when switch S is closed, current flows from the battery, through the vibrator coil, and the lower half of the transformer primary. The magnetic field created by current flow through the vibrator coil attracts the armature and pulls it down against the lower contact. This places a short circuit across the vibrator coil, which causes it to de-energize and release the armature. Spring action draws the armature away from the coil, carries it through the neutral position, and drives it against the upper contact. Since the short circuit is now removed from the vibrator coil, a magnetic field again exists, which draws the armature down until it again touches the lower contact. This action continues at a rate dependent on the natural frequency of the vibrator (typically about 100 Hz).


During the time when the armature is against the lower contact, the lower portion of the transformer

primary is in the circuit. The direction of current flow in this half of the primary is such that the bottom of the primary winding is negative with respect to the center tap. The voltage induced in the secondary, as a result of this current, will be of like polarity, that is, positive-going with respect to the bottom of the secondary winding. This condition is indicated at time t_0 in part B of the illustration. When the armature switches to the upper contact, the upper portion of the transformer primary is placed in the circuit. Since the current through this half of the primary winding flows in a direction opposite to that in the lower half of the winding, a voltage pulse of opposite polarity will be induced in the secondary. This is shown at time t_1 . The start of another complete cycle of operation, which is identical in every respect to the cycle just described, is shown at time t_2 .


The closing of the lower and upper contacts (in succession) corresponds to one complete cycle of the vibrator frequency, and two pulses of current in alternate directions through the two halves of the transformer primary. The magnetic field created by these current pulses induces a voltage in the transformer secondary which is essentially a square wave, as shown in part B of the illustration. The output voltage does not achieve the shape of an ideal square wave because of the inductance of the transformer. As the current is continuously interrupted in the primary circuit, the alternate build-up and decay of the magnetic field both require a certain finite time. This results from the inductive reactance of the windings, which opposes both the build-up and the decay of the field. Because of this action, and of the high-voltage inductive effect (overshoot), the shape of the output voltage waveform will be as shown in the illustration. Because the vibrator switching action produces a current flow in opposite directions in the two halves of the primary during one complete mechanical cycle of the vibrating reed, the vibrator is sometimes called a *full-wave nonsynchronous vibrator*.

As shown in the accompanying diagram, a nonsynchronous vibrator consists of five basic parts: a heavy frame, an electromagnetic driving coil and core or pole piece, a flexible reed and armature, one or more contacts attached to each side of the reed, and one or more stationary contacts mounted on each side of the reed and armature assembly. There are two basic electrical variations in full-wave nonsynchronous vibrators; the first type is called a *shunt-drive* vibrator and the second is called a *series-drive*, (or *separate-drive*)

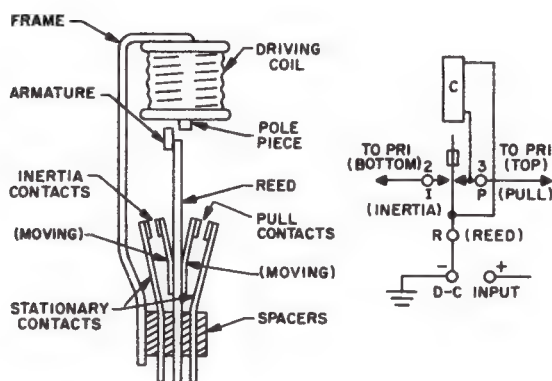vibrator. These names are derived from the manner in which the electromagnetic driving coil receives its excitation. Refer to the accompanying illustration of two typical nonsynchronous vibrators; part A shows the construction of a shunt-drive vibrator together with its graphic symbol, and part B shows the construction of series-drive vibrator and its graphic symbol.



A
SHUNT DRIVE VIBRATOR

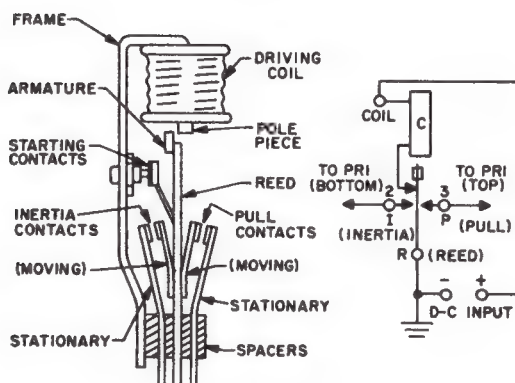

B
SERIES-DRIVE (OR SEPARATE-DRIVE) VIBRATOR



Nonsynchronous Vibrator Types

The electromagnetic driving coil is mounted on one end of the frame, as shown in the illustration, and the reed is rigidly clamped in insulating spacers and fixed to the opposite end of the frame. The sta-

tionary contacts are similarly clamped at the end of the frame, on each side of the reed. Electrical connections to the vibrator are also made at this point on the frame. The vibrator assembly is usually mounted in a sound-absorbing and cushioning material, such as foam or sponge rubber, which, in turn, is sealed within a metal can. The material placed around the vibrator reduces the amount of mechanical noise created by the vibrating reed, and the metal can acts as an r-f shield to reduce direct radiation of electrical noise. The connecting leads from the vibrator are brought out to metal prongs at the base of the can, and the complete unit is plugged into a special socket in the same manner that an electron tube is installed in a tube socket; the socket also grounds the can to the chassis to completely shield the vibrator. Since the vibrator may require replacement at intervals throughout the useful life of the power supply, the plug-in method of electrical connection insures convenient and easy replacement of a defective vibrator unit.

The shunt-drive vibrator, shown in part A of the illustration, has one end of the driving-coil winding connected to the vibrating reed, which is normally connected to ground. The other end of the winding is connected to an insulated stationary contact on the electromagnetic *pull* (or *power*) side of the reed; this contact is connected to the top of the primary winding. As shown by the graphic symbol in Part A of the illustration, both sets of contacts are open when the vibrator is at rest; however, when voltage is applied to the vibrator circuit, current flows through the driving coil, which magnetizes the core and causes the reed armature to be pulled toward the pole piece. As this occurs, the pull (or power) contacts close to shunt or short out the driving coil as well as to complete one half of the primary circuit. (Refer to the accompanying illustration below showing typical nonsynchronous vibrator supplies.) This shunting action of the pull contacts causes the driving coil to lose its magnetic attraction for the reed armature and, as a result of the spring action stored in the reed, causes the reed to swing back away from the pull contacts to interrupt the primary circuit. The inertia of the reed carries it back across the neutral (at rest) position to the other set of contacts, called the *inertia* contacts, closing these contacts to complete the other half of the primary circuit. While the inertia contacts are closed, current once again flows through the driving coil and causes a high magnetic attraction to be

imparted to the reed armature. As the reed moves away from the inertia contacts, these contacts open to interrupt the primary circuit. The cycle is then repeated as the reed is carried across the neutral (at rest) position to close the pull contacts and once again shunt the driving coil. It should be noted at this time that the peak voltage applied to the driving coil, during the time the inertia contacts are closed, is approximately twice the value of the normal dc input voltage to the supply; this is because the voltage induced by autotransformer action in the half of the primary winding which is connected to the stationary pull contact is in series with the dc input voltage.

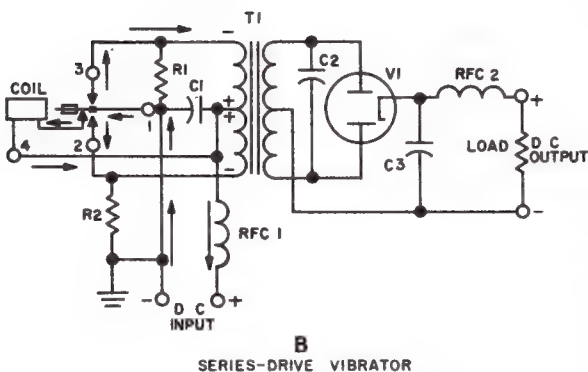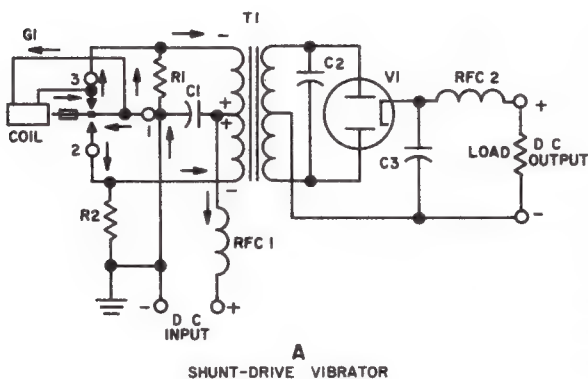

Typical Nonsynchronous Vibrator Supplies

By referring to the diagram of the shunt-drive vibrator, it will be seen that when the armature is in

the neutral position (all contacts open), a complete series circuit exists from the negative side of the input source, through the driving coil and pull winding, to the positive side of the dc source. For a given value of current, as determined by the total resistance in the circuit, the portion of the input voltage that will be dropped across each of the two circuit elements will be in direct proportion to the resistance present in each element. Since the transformer primary winding offers only negligible resistance to the comparatively small and steady dc current which flows under the conditions stated, no appreciable voltage will be developed across the pull winding.

When the inertia contacts are closed, the series circuit through the driving coil and pull winding remains completed. The voltage existing across the pull winding and the voltage developed in the inertia winding have opposite polarities. Through the autotransformer action which takes place across the tapped primary, the rapidly changing magnetic field around the inertia winding induces a voltage in the pull winding; this voltage has the same polarity as that of the inertia winding. As a result, the voltage now present across the pull winding will be the difference between the induced voltage and the existing voltage. Since the induced voltage has the greater value, the polarity of the difference voltage will be the same as that of the induced voltage. Thus, not only is the counteracting effect of an opposing voltage neutralized, the the voltage in the inertia winding is effectively aided.

The series-drive (or separate-drive) vibrator, shown in part B of both illustrations (the Nonsynchronous Vibrator Types and the Typical Nonsynchronous Vibrator Supplies), differs from the shunt-drive vibrator just described in that it has an extra pair of contacts. These contacts, called *starting* contacts, are normally closed when the vibrator is at rest. The moving contact of this pair is mounted on the armature reed, which is normally connected to ground. The stationary starting contact is wired to one end of the driving coil. The other end of the coil is connected to the high side of the dc input voltage source, through a terminal in the base of the vibrator provided for this purpose. As shown in part B of both illustrations, both the inertia contacts and pull contacts are open when the vibrator is at rest. However, when voltage is applied to the vibrator circuit, current flows through the driving coil and causes the reed

armature to be attracted to the pole piece (magnetized core); thus, the moving pull contact is drawn against the stationary pull contact. The closing of these contacts completes a circuit through one half of the transformer primary. The armature, in moving toward the pole piece, opens the starter contacts, which prevents any further current flow in the driving coil; this results in the collapse of the magnetic field. The reed, now no longer attracted by the pole piece, swings back from the driving coil; this opens the pull contacts and interrupts the primary circuit. The inertia of the reed carries it back across the neutral (at rest) position to the inertia contacts, closing these contacts to complete the other half of the primary circuit. At the same time, the starting contacts close and current once again flows through the driving coil to produce a magnetic attraction for the reed armature. As the reed moves away from the inertia contacts, these contacts open to interrupt the primary circuit; at the same time the starting contacts open to interrupt the circuit to the driving coil. The cycle is then repeated as the reed is carried across the neutral (at rest) position to close the pull contacts and once again complete the primary circuit. It should be noted at this time that if the series-drive vibrator is connected in the circuit so that the driving coil receives voltage directly from the input source (through a separate contact in the vibrator base), the vibrator will continue to vibrate mechanically, even though the transformer center tap and end leads are open. This will not occur with the shunt-drive vibrator since the current to energize the driving coil must pass through one half of the primary winding.

In both the shunt-drive vibrator and the series-drive vibrator the current is alternately switched through each half of the transformer primary, and, as a result of these alternate pulses and the magnetic field they produce in transformer T1, a stepped-up voltage is induced in the transformer secondary. The resulting secondary voltage is essentially square in waveform, and is applied to the full-wave rectifier circuit. In the circuits illustrated by the diagrams of typical nonsynchronous vibrator supplies, transformer T1 has a center-tapped secondary winding; each end terminal of the secondary is connected to a plate of the electron tube, V1. On alternate half-cycles of the secondary voltage, alternate diodes of the full-wave rectifier conduct and produce an output voltage across the load resistance. Since only one diode conducts at any instant of time, electrons flow

through the load resistance in pulses to produce a pulsating output voltage. The output of the rectifier circuit is connected to a suitable filter circuit to smooth out the dc for use in the load circuit; because a square-wave voltage is applied to the rectifier circuit, and because the frequency of vibrator switching is fairly high (usually 100 to 120 Hz), very little filtering is required to obtain a dc output voltage which is free from voltage transients and relatively free from ripple.

In practice, the nonsynchronous vibrator is normally constructed with a four-prong base, and the socket into which the vibrator is plugged is wired to accept either a shunt-drive or a series-drive vibrator; therefore, the two vibrator types may be used interchangeably in a large number of vibrator-type supplies.

Circuit Operation. Both supplies shown in the Nonsynchronous Vibrator Supplies illustration utilize a full-wave rectifier circuit to obtain high-voltage output. The discussion which follows is concerned primarily with the vibrator and its associated transformer, since the operation of a full-wave rectifier circuit has been described previously in this section of the handbook. Furthermore, the nonsynchronous vibrator-type power supply is not necessarily restricted to the use of a full-wave rectifier circuit and, in many instances, the rectifier circuit is likely to be a bridge or voltage-doubler circuit employing either electron-tube or semiconductor diodes as rectifiers.

Vibrator G1 in the circuit of part A is a shunt-drive vibrator; vibrator G1 in the circuit of part B is a series-drive vibrator. Transformer T1, in both circuits, is a special power transformer with a center-tapped primary and center-tapped secondary; however, if a bridge or voltage-doubler rectifier circuit is used instead of a full-wave rectifier shown, the transformer secondary need not be center-tapped. Electron tube V1 is a twin-diode rectifier, and may be either an indirectly heated cathode rectifier or a gas-filled, cold-cathode rectifier. Bypass capacitor C1 and r-f choke RFC1 serve as a filter to eliminate or reduce impulse electrical noise (or "hash"), originated by arcing vibrator contacts, from being radiated by the dc input leads and coupled into other circuits of the equipment. Resistors R1 and R2 are connected across the interrupter contacts of the vibrator to reduce interference and sparking and also to increase the life of the vibrator contacts; the value of R1 and R2 is usually between 47 and 220 ohms, depending upon

the dc input voltage and circuit design. Resistors R1 and R2 also help to reduce the peak amplitude of any transient voltages which might occur in the primary circuit because of vibrator switching action. Capacitor C2, commonly called the *buffer* capacitor, and occasionally referred to as the surge or timing capacitor, is connected across the transformer secondary to effectively absorb the high transient voltages produced by the inductive reactance when the primary current is interrupted by the opening of the vibrator contacts. Because of the magnitude of these voltages, it is necessary that the buffer capacitor have a rating in working volts of from 6 to 8 times the voltage delivered by the power supply. For example, for a supply which delivers 250 volts, the capacitor should be rated between 1500 and 2000 working volts. A resistor of approximately 5000 ohms is sometimes connected in series with the buffer capacitor to limit the secondary current in case the buffer capacitor becomes shorted. The value of a buffer capacitor depends upon the circuit design (transformer turns ratio and effective inductance, vibrator frequency, etc), but is usually between .001 and .047 μ f. Capacitors used in this application generally have a breakdown voltage of 1000 to 2000 volts. In some circuits a buffer capacitor is connected across the transformer primary. Another circuit variation uses two buffer capacitors of equal value; a capacitor is connected at each end of the secondary to ground or to the secondary center tap. Bypass capacitor C3 and r-f choke RFC2 form an additional filter to prevent noise (or "hash") from being coupled to other circuits through the high-voltage, dc output lead.

When dc input power is applied to the circuit, the driving coil of vibrator G1 is energized to start the reed vibrating at its own natural frequency. (The operation of shunt-drive and series-drive vibrators was described in considerable detail in previous paragraphs; therefore, a description of vibrator switching action will not be repeated here.)

Failure Analysis.

General. A quick check to determine whether the vibrator is operating is to listen for the characteristic mechanical buzzing noise which is made by the vibrating action of the reed assembly; although the reed assembly is enclosed in a sealed can and is cushioned to deaden the sound, an audible indication can usually be detected. However, this simple check is not a

positive indication of correct vibrator operation; for example, the series-drive vibrator will often continue to operate even when there are discontinuities in the transformer primary circuit.

The most frequent trouble which develops in a vibrator-type supply is caused by a defective vibrator or a defective buffer capacitor. The power transformer and the rectifier-circuit components generally have a useful life which is comparable to the life of the components in a conventional power supply designed for ac input.

Although certain waveform measurements can be made with an oscilloscope to check for correct operation of the vibrator supply, this technique will not always immediately reveal troubles within the supply, since mechanical defects which may be of short duration sometimes occur only after the vibrator reaches a certain operating temperature.

An indication of vibrator operation can be quickly obtained by using an oscilloscope to observe the voltage waveform at the primary of the power transformer. If measurements are made at each end of the primary to chassis (ground), the peak-to-peak amplitude of the square wave will be approximately equal to twice the value of the dc input voltage; however, if the oscilloscope vertical input is connected across the entire primary winding, the peak-to-peak amplitude of the square wave will be approximately equal to four times the value of the dc input voltage. When the vibrator circuit is operating normally, a square wave will be observed with relatively smooth transition occurring after the contacts break and during the voltage reversal when another set of contacts make to produce the next half-cycle of the waveform. The flat portion of the square wave should be relatively smooth; if radical transients appear on the flat portion of the square wave, this is an indication of poor electrical contact, caused by chattering or bouncing of the contacts, and is a good reason to suspect that the vibrator is defective. Minor roughness, or "ripple", on the flat portion of the square wave is not usually sufficient cause to reject the vibrator, since this indication merely represents some small variation in contact resistance during the time the vibrator contacts are closed. The smoothness of the transition from one flat-topped portion of the square wave is controlled by the value of the buffer (timing) capacitor, the inductive reactance of the transformer, the natural frequency of the vibrator reed assembly, and the elapsed time between contact closures.

When the symptoms and checks indicate that the vibrator is definitely at fault, it is important that the replacement vibrator be the same, or an equivalent, type. There are many variations in vibrator terminal connections and operating characteristics; therefore, the replacement vibrator should be the same type as the original, or at least a vibrator which is recommended by the manufacturer as the correct replacement for the original.

No Output. The nonsynchronous vibrator supply consists of a vibrator and associated transformer, and a rectifier and filter circuit. Therefore, when checking the vibrator supply for a possible defect, tests must be made to determine whether the trouble is due to a defective vibrator and associated transformer, or to a defect within the rectifier circuit.

The dc input voltage should be checked to determine whether it is present and of the correct value.

The operation of the vibrator can be checked by an ac voltage measurement made at the secondary terminals of the transformer, or by use of an oscilloscope connected to the primary circuit to observe the switching-action waveform. If the vibrator and associated transformer are found to be functioning normally, as indicated by a secondary-voltage measurement or an oscilloscope check, it must be assumed that the trouble is in the rectifier circuit or the associated load. A check of the rectifier circuit can be made in accordance with the procedures outlined previously in this section for the applicable rectifier circuit; in the case of this particular vibrator-supply circuit, reference should be made to the Single-Phase Full-Wave rectifier circuit. When burned or pitted vibrator contacts stick together, a heavy current flows in the associated primary winding, and this current should be made with an ammeter to determine whether this current is within tolerance, or whether it is excessive. With the vibrator removed from its socket, continuity measurements of the transformer primary circuit may be made to determine whether the primary winding is open, shorted, or grounded.

A shorted buffer capacitor C2 can be detected by a higher than normal input current to the supply and a very low ac voltage at the secondary terminals of the transformer. The replacement buffer capacitor should be the same value as the original capacitor and of equal or greater voltage rating. A leaky or shorted filter capacitor C1 will also cause the input current to the supply to be above normal. As a general rule, any

time the vibrator is replaced the buffer capacitor should also be replaced.

The indirectly heated cathode rectifier, V1, is frequently subject to heater-to-cathode leakage, and, since the heater is normally at ground potential, this leakage will cause an abnormal load on the rectifier output; a complete short will result in no dc output from the supply. Also, a short in filter capacitor C3 or an open r-f choke RFC2 will result in no output from the power supply.

Low Output. A low-output condition in a nonsynchronous vibrator-type power supply usually results from a defective vibrator, a leaky buffer capacitor, low input voltage, or a defective component in the rectifier or filter circuit.

A voltage drop in the primary leads to the supply can result in low output; therefore, the input voltage should be checked at the transformer or vibrator terminals to determine whether the input voltage is present and of the correct value.

The ac secondary voltage may be measured at the transformer to determine whether it is approximately the value specified for normal operation of the supply. The test procedures described for the no-output condition and in previous paragraphs can be used to determine whether the vibrator is at fault. A defective vibrator with only one set of properly making contacts results in reduced output from the supply. A vibrator in which "frequency hunting" occurs may be detected by an uneven or irregular buzzing noise, which indicates that the armature is vibrating erratically and at frequencies other than its normal frequency of vibration. This unstable condition of the vibrator causes the stepped-up voltage induced in the secondary of the transformer to also be erratic, and the output voltage to be below its normal value. This trouble is usually caused by excessive load current, and is an indication of impending vibrator failure. Frequency hunting can also be caused by burned or pitted vibrator contacts which are sticking; this usually results in a higher than normal input current and reduced output from the supply. A check of the input current should be made with an ammeter to determine whether the current is within tolerance; also, an oscilloscope check of the waveform at the primary of the transformer should be made to determine whether the vibrator is faulty. Shorts, leakage, or excessive current drain in the filter circuit or in the high-voltage load circuit external to the supply will cause a heavy load on the vibrator contacts, and may

cause early failure of the vibrator. The output load current should be measured after installation of a replacement vibrator to determine whether the load current is within tolerance; if the load current is excessive, the replacement vibrator may be damaged unless the cause for the excessive load current is found and corrected.

Continuity measurements of the primary and secondary windings of transformer T1 should be made, since an open circuit in either of the windings will cause a reduction in output.

The rectifier, V1, may be weak and cause low output. The tube is usually an indirectly heated cathode type, such as a type 6X5, 6X4, or 12X4, or a gaseous rectifier, such as a type 0Z4. In an emergency, when the vibrator is urgently needed and no replacement is available, the vibrator may be opened and the contacts burnished as an interim corrective measure. The indirectly heated cathode rectifier is frequently subject to heater-to-cathode leakage, and, since the heater is normally at ground potential, this leakage will cause a load on the rectifier output; a complete short will result in no dc output from the supply.

The power supply output current should be checked to make sure that it is within tolerance. A low-output condition due to a decrease in load resistance will cause an increase in load current; for example, excessive leakage in the capacitors of the output filter circuit will result in increased load current.

SYNCHRONOUS VIBRATOR SUPPLY

Application.

The synchronous vibrator supply is commonly employed in many portable and mobile equipments where the primary power source is a storage battery. This supply produces a relatively high value of dc voltage at a moderate load current from a low-voltage dc source. The supply is commonly used to provide high voltage for the operation of small receivers, transmitters, and public-address systems, although in many equipments the transistorized dc-to-dc converter described previously in this section is used in lieu of the vibrator supply.

Characteristics.

Input is low-voltage dc; output is high-voltage dc.

Input voltage is usually 6, 12, or 24 volts; special vibrators for other input voltages are available.

Typical vibrator operating frequency is between 60 and 250 Hz.

Output high-voltage dc is normally between 180 and 300 volts; load current is normally between 60 and 200 milliamperes.

Output circuit can be arranged to furnish negative or positive high voltage to the load.

Output dc requires filtering; ripple-voltage frequency is relatively high, and is determined by the vibrator frequency.

Synchronous vibrator is self-rectifying; electron-tube or semiconductor rectifier circuit is not required.


Regulation is fair; output voltage regulation may be employed.

Vibrator must be shielded and leads filtered to prevent r-f radiation and interference to other circuits.

Circuit Analysis.

General. A synchronous vibrator supply converts direct current from a low-voltage power source into high-voltage dc that can be filtered for use as the plate and screen voltages in the operating equipment. A separate rectifier is not required with this circuit because rectification is accomplished by means of an extra set of contacts on the vibrator. The supply offers the advantages of light weight, small physical size, and good efficiency; its main disadvantages are the limitation in output current and tendency to produce interference to other circuits. Therefore, the vibrator must be well-filtered and shielded. Another disadvantage is that, although the vibrator itself is relatively inexpensive, its useful life is shorter than that of a dynamotor or of the transistors in a dc-to-dc converter. However, when this type of power supply is used within its rating, it will furnish reliable power for low-power communications and public address equipment.

Synchronous Vibrator Types. A vibrator is an electromechanical mechanism, sometimes called an *interrupter*, which acts as a high-speed reversing switch to control (or interrupt) the current in each half of a tapped primary winding in a special step-up power transformer; in addition, the synchronous vibrator is equipped with two additional sets of contacts, operating in synchronism with the primary circuit interrupter contacts, to provide rectification of the transformer secondary voltage. The operation of a simple vibrator as a high-speed switching device and its rectifying action can be understood by reference to the accompanying illustration.

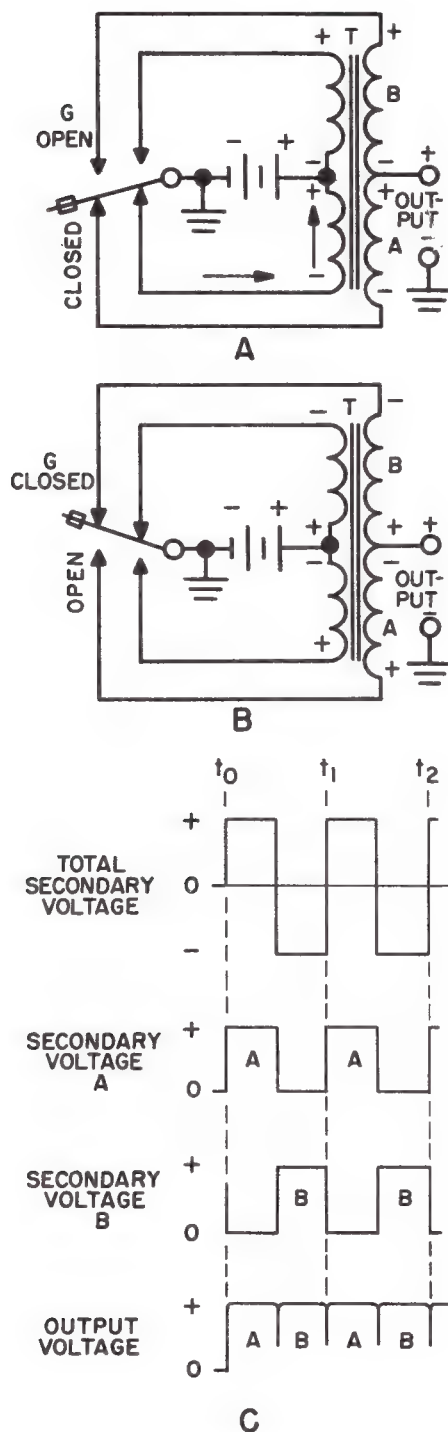

Fundamental Switching Circuit, Using Synchronous Vibrator, and Resulting Output Waveform

In this illustration, a vibrating reed is equipped with two sets of interrupter contacts arranged so that when one set of contacts is closed to complete one primary circuit, the other set of contacts is open to interrupt the other primary circuit. Two additional sets of contacts, called the *rectifier* contacts, operate in synchronism with the primary interrupter contacts. The action of the rectifier contacts is identical with the action of the primary contacts; that is, when one set of rectifier contacts is closed to complete one half of the secondary circuit, the other set of rectifier contacts is open to interrupt the other half of the secondary circuit. Thus, as shown in part A of the illustration, when the upper sets of contacts are open, the lower sets of contacts are closed, and heavy current flows in the lower primary winding of the transformer. Also at this time, the lower half of the secondary, marked "A", is grounded through the lower set of vibrator contacts to complete the secondary circuit and produce a voltage at the output terminals. The polarities of the voltages produced across the primary and secondary windings of the transformer, which are so wound that no phase reversal occurs, are as indicated in part A of the illustration.



When the vibrating reed reverses its position, as shown in part B, the upper sets of contacts are closed, and heavy current flows in the upper primary winding of the transformer. Also at this time, the upper half of the secondary, marked "B", is grounded through the upper set of rectifier contacts to complete the secondary circuit and produce a voltage at the output terminals. The polarities of the voltages produced across the primary and secondary windings of the transformer are as indicated in part B of the illustration.

Assuming a rapid rate of primary switching, the voltage developed across the entire secondary is essentially a square waveform, as shown in part C. The voltage produced in each half of the secondary on alternate half-cycles, when combined, results in an output voltage which is essentially pulsating dc voltage. Small transients occur in the output voltage during the time the vibrator reed is transferring from one set of contacts to the other; however, these transients are easily removed by a filter circuit connected to the output of the vibrator supply.

A synchronous vibrator consists of five basic parts: a heavy frame, an electromagnetic driving coil and core or pole piece, a flexible reed and armature, two contacts attached to each side of the reed, and two

(or more) stationary contacts mounted on each side of the reed and armature assembly. There are two basic electrical variations in synchronous vibrators; the first type is called a *shunt-drive* vibrator, and the second is called a *series-drive* (or *separate-drive*) vibrator. These names are derived from the manner in which the electromagnetic driving coil receives its excitation. The two types of synchronous vibrators are shown in the illustration below; part A shows the construction of a shunt-drive vibrator and its graphic symbol, and part B shows the construction of a series-drive vibrator and its graphic symbol.

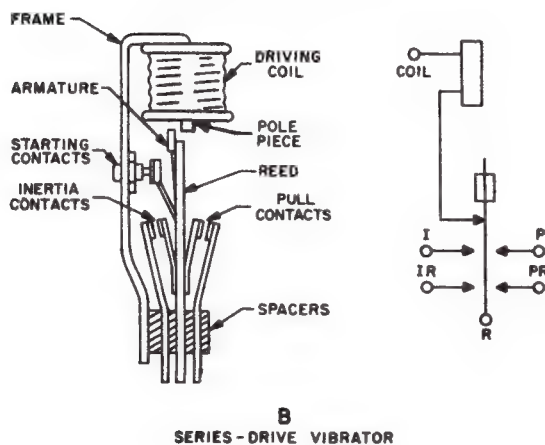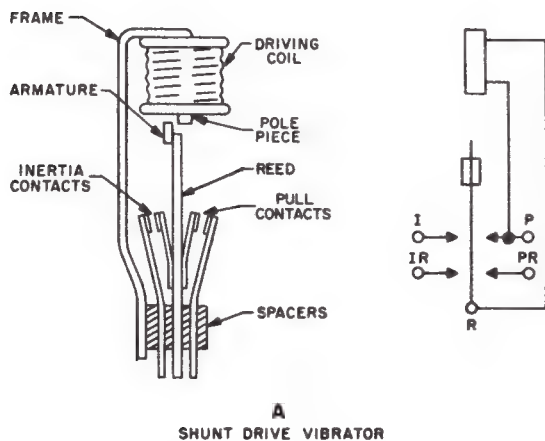The electromagnetic driving coil is mounted on one end of the frame, as shown in the illustration,



Synchronous Vibrator Types

and the reed is rigidly clamped in insulating spacers and fixed to the opposite end of the frame. The movable contacts are mounted on the sides of the reed. The stationary contacts are similarly clamped at the end of the frame, on each side of the reed. Electrical connections to the vibrator are also made at this point on the frame. The vibrator assembly is usually mounted within a sound-absorbing and cushioning material, such as foam or sponge rubber, which, in turn, is sealed within a metal can. The material placed around the vibrator reduces the amount of mechanical noise created by the vibrating reed, and the metal can acts as an r-f shield to reduce direct radiation of electrical noise. The connecting leads from the vibrator are brought out to metal prongs at the base of the can, and the complete unit is plugged into a special socket in the same manner that an electron tube is installed in a tube socket; the socket also grounds the can to the chassis to completely shield the vibrator. Since the vibrator may require replacement at intervals throughout the useful life of the power supply, the plug-in method of electrical connection insures convenient and easy replacement of a defective vibrator unit.

The shunt-drive vibrator, shown in part A, has one end of the driving-coil winding connected to the vibrating reed (normally connected to ground); the other end of the winding is connected to one of the insulated stationary primary contacts on the electromagnetic *pull* (or *power*) side of the reed. As shown in part A of the illustration, all contacts are open when the vibrator is at rest; however, when voltage is applied to the vibrator circuit through the power transformer primary, current flows through the driving coil and causes the reed armature to be pulled toward the pole piece. As this occurs, one set of primary contacts, called the *pull* or *power* contacts, close to shunt or short out the driving coil and also complete one half of the primary circuit. (An additional set of pull contacts, called the *rectifier* contacts, close to complete one half of the secondary circuit at this time.) The shunting action of the primary pull contacts causes the driving coil to lose its magnetic attraction for the reed armature and, as a result of the mechanical energy stored in the reed, causes the reed to swing back away from the pull contacts to interrupt the primary circuit and also break the secondary circuit. The inertia of the reed carries it back across the neutral (at rest) position to the other set of primary contacts, called the *inertia*

contacts, closing these contacts to complete the other half of the primary circuit. (An additional set of inertia contacts, called the *rectifier* contacts, close to complete the other half of the secondary circuit at this time.) While the inertia contacts are closed, current once again flows through the driving coil and causes a high magnetic attraction to be imparted to the reed armature. As the reed moves away from the inertia contacts, these contacts open to interrupt the primary circuit and also break the secondary circuit. The cycle is then repeated as the reed is carried across the neutral (at rest) position to close the primary pull contacts, thus shunting the driving coil, and also closing the rectifier pull contacts to complete the secondary circuit. It should be noted at this time that the peak voltage applied to the driving coil, during the time the inertia contacts are closed, is approximately twice the value of the normal dc input voltage to the supply; this is because the voltage induced by autotransformer action in the half of the primary winding which is connected to the stationary pull contact is in series with the dc input voltage.

By referring to the diagram of the shunt-drive vibrator, it will be seen that when the armature is in the neutral position (all contacts open), a complete series circuit exists from the negative side of the input source, through the driving coil and pull winding, to the positive side of the dc source. For a given value of current, as determined by the total resistance in the circuit, the portion of the input voltage that will be dropped across each of the two circuit elements will be in direct proportion to the resistance present in each element. Since the transformer primary winding offers only negligible resistance to the comparatively small and steady dc current which flows under the conditions stated, no appreciable voltage will be developed across the pull winding.

When the inertia contacts are closed, the series circuit through the driving coil and pull winding remains completed. The voltage existing across the pull winding and the voltage developed in the inertia winding have opposite polarities. Through the autotransformer action which takes place across the tapped primary, the rapidly changing magnetic field around the inertia winding induces a voltage in the pull winding; this voltage has the same polarity as that of the inertia winding. As a result, the voltage now present across the pull winding will be the difference between the induced voltage and the existing voltage. Since the induced voltage has the greater value, the


polarity of the difference voltage will be the same as that of the induced voltage. Thus, not only is the counteracting effect of an opposing voltage neutralized, but the voltage in the inertia winding is effectively aided.

The series-drive (or separate-drive), vibrator, shown in part B, differs from the shunt-drive vibrator just described in that it has an extra pair of contacts which are normally closed when the vibrator is at rest. These contacts, called *starting* contacts, are in series with the ground connection to one end of the driving coil, while the other end of the driving coil is connected to the dc input voltage, either through a separate terminal in the vibrator base or to one of the stationary primary contacts. As shown in the illustration (part B), all pull and inertia contacts are open when the vibrator is at rest; however, when voltage is applied to the vibrator coil circuit, either through a stationary primary-pull contact or through the driving coil and causes the reed armature to be pulled toward the pole piece. The reed continues to move toward the pull contacts and, as the pull contacts close to complete one half of the primary and secondary circuits, the starting contacts are opened, causing the driving coil to lose its magnetic attraction for the reed armature. The reed now swings back away from the pull contacts, because the driving coil has lost its magnetic attraction for the reed armature, and the pull contacts open to interrupt the primary and secondary circuits. The inertia of the reed carries it back across the neutral (at rest) position to the inertia contacts, closing both the primary and rectifier contacts to complete the other half of the primary and secondary circuits. At the same time, the starting contacts close and current once again flows through the driving coil to produce a magnetic attraction for the reed armature. As the reed moves away from the inertia contacts, the primary and rectifier inertia contacts open to interrupt both circuits; at the same time the starting contacts open to interrupt the circuit to the driving coil. The cycle is then repeated as the reed is carried across the neutral (at rest) position to close the pull contacts and once again complete the primary and secondary circuits. It should be noted at this time that if the series-drive vibrator is connected in the circuit so that the driving coil receives voltage directly from the input source (through a separate contact in the vibrator base), the vibrator will continue to vibrate mechanically, even though the transformer primary center-tap and end leads are open.

This will not occur with the shunt-drive vibrator, since the current to energize the driving coil must pass through one half of the primary winding.

The output polarity of a synchronous vibrator power supply depends upon the polarity of the dc input voltage. For this reason, means are often provided for reversing the dc output polarity. In practice, the synchronous vibrator is normally constructed with a special five-prong base, and the special seven-prong socket into which the vibrator is plugged accepts the vibrator in either of two positions. When installed in one position a positive output is obtained, and when installed in the other position a negative output is obtained. In other vibrator installations, a reversing switch (or flexible jumpers on a terminal board) is used to reverse the secondary-winding (or the primary-winding) connections to the power transformer.

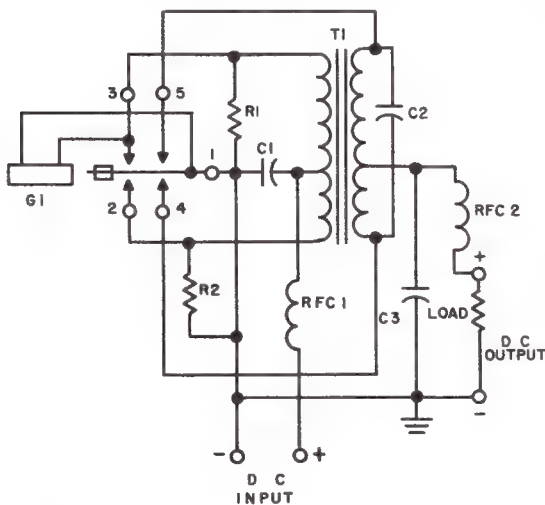Circuit Operation. The accompanying illustration shows a typical synchronous vibrator supply using a shunt-drive vibrator. (Except for the manner in which connections are made to the driving coil, the operation of a series-drive vibrator is essentially the same.)



Typical Synchronous Vibrator Supply Using a Shunt-Drive Vibrator

Vibrator G1 is a shunt-drive vibrator; transformer T1 is a special power transformer with a center-tapped primary and center-tapped secondary. Bypass capacitor C1 and r-f choke RFC1 serve as a filter to reduce or eliminate impulse electrical noise (or "hash"), originated by arcing vibrator contacts, from

being radiated by the dc input leads and coupled into other circuits of the equipment. Resistors R1 and R2 and connected across the primary interrupter contacts of the vibrator to reduce interference and sparking and also to increase the life of the vibrator contacts; the value of R1 and R2 is usually between 47 and 220 ohms, depending upon the dc input voltage and circuit design. Resistors R1 and R2 also help to reduce the peak amplitude of any transient voltages which might occur in the primary circuit because of vibrator switching action. Capacitor C2, commonly called the *buffer* capacitor, and occasionally referred to as the *surge* or *timing* capacitor, is connected across the transformer secondary to effectively absorb the high transient voltages produced by the inductive reactance when the primary current is interrupted by the opening of the vibrator contacts. A resistor of approximately 5000 ohms is sometimes connected in series with the buffer capacitor to limit the secondary current in case the buffer capacitor becomes shorted. The value of a buffer capacitor depends upon the circuit design (transformer turns ratio and effective inductance, vibrator frequency, etc), but is usually between .001 and .047 μf . Capacitors used in this application generally have a break-down voltage of from 1000 to 2000 volts. In some circuits a buffer capacitor is connected across the transformer primary. Another circuit variation, commonly used with the synchronous vibrator, uses two buffer capacitors of equal value; a capacitor is connected at each end of the secondary winding to ground (chassis). Bypass capacitor C3 and r-f choke RFC2 form an additional filter to prevent noise (or "hash") from being coupled to other circuits through the high-voltage, dc output lead.

When dc input power is applied to the circuit, the driving coil of vibrator G1 is energized to start the reed vibrating at its own natural frequency. (The operation of shunt-drive and series-drive vibrators was described in considerable detail in previous paragraphs; therefore, a description of vibrator switching action will not be repeated here.) The current is alternately switched through each half of the transformer primary, and, as a result of these alternate pulses and the magnetic field they produce in transformer T1, a stepped-up voltage is induced in the transformer secondary. The resulting voltage in each half of the secondary is essentially square in waveform. During the time that a square wave is being produced in the secondary winding, one set of rectifier contacts close in

the vibrator to connect the proper secondary winding to ground, and current flows through the load resistance. The rectifier contacts operate in synchronism with the primary interrupter contacts and alternately connect opposite ends of the secondary to ground; this action causes each half of the secondary to supply current to the load resistance on alternate half-cycles. Since only one half of the secondary is connected to the load circuit at any instant, electrons flow through the load resistance in pulses to produce a pulsating output voltage. (The action is similar to that of a full-wave rectifier circuit.) The output of the synchronous vibrator supply is connected to a suitable filter circuit to smooth out the dc for use in the load circuit. Because a square-wave voltage is switched in synchronism with the switching of the primary circuit, and because the frequency of the switching is fairly high (usually 100 to 120 Hz) very little filtering is required to obtain a dc output voltage which is free from voltage transients and relatively free from ripple.

Failure Analysis.

General. A quick check to determine whether the vibrator is operating is to listen for the characteristic mechanical buzzing noise which is made by the vibrating action of the reed assembly; although the reed assembly is enclosed in a sealed can and is cushioned to deaden the sound, an audible indication can usually be detected. However, this simple check is not a positive indication of correct vibrator action, but merely indicates that mechanical action is taking place.

The most frequent trouble which develops in a vibrator-type supply is caused by a defective vibrator or a defective buffer capacitor(s). The power transformer and the associated circuit components generally have a useful life which is comparable to the life of the components in a conventional power supply designed for ac input.

Although certain waveform measurements can be made with an oscilloscope to check for correct operation of the vibrator supply, this technique will not always immediately reveal troubles within the supply, since mechanical defects which may be of short duration sometimes occur only after the vibrator reaches a certain operating temperature.

An indication of vibrator operation can be quickly obtained by using an oscilloscope to observe the volt-

age waveform at the primary of the power transformer. If measurements are made at each end of the primary to chassis (ground), the peak-to-peak amplitude of the square wave will be approximately equal to twice the value of the dc input voltage; however, if the oscilloscope vertical input is connected across the entire primary winding, the peak-to-peak amplitude of the square wave will be approximately equal to four times the value of the dc input voltage. When the vibrator circuit is operating normally, a square wave will be observed with relatively smooth transition occurring after the contacts break and during the voltage reversal when another set of contacts make to produce the next half-cycle of the waveform. The flat portion of the square wave should be relatively smooth; if radical transients appear on the flat portion of the square wave, this is an indication of poor electrical contact caused by chattering or bouncing of the contacts, and is a good reason to suspect that the vibrator is defective. Minor roughness, or "ripple", on the flat portion of the square wave is not usually sufficient cause to reject the vibrator, since this indication merely represents some small variation in contact resistance during the time the vibrator contacts are closed. The smoothness of the transition from one flat-topped portion of the square wave, through the voltage reversal (contacts open), to the other voltage extreme of the square wave is controlled by the value of the buffer (timing) capacitor, the inductive reactance of the transformer, the natural frequency of the vibrator reed assembly, and the elapsed time between contact closures.

When the symptoms and checks indicate that the vibrator is definitely at fault, it is important that the replacement vibrator be the same, or an equivalent type. There are many variations in vibrator terminal connections and operating characteristics; therefore, the replacement vibrator should be the same type as the original, or at least a vibrator which is recommended by the manufacturer as the correct replacement for the original.

No Output. The synchronous vibrator supply consists of a vibrator, transformer, and associated filter circuit. It must be determined initially whether the vibrator is operating; if it is, tests must be made to determine whether the trouble is due to a defective vibrator or transformer, or to a defect located within the filter circuit.

The dc input voltage should be checked to determine whether it is present and of the correct value.

The operation of the vibrator can be checked by an ac voltage measurement made at the secondary terminals of the transformer, or by use of an oscilloscope connected to the primary circuit to observe the switching-action waveform. If the vibrator and associated transformer are found to be functioning normally, as indicated by a secondary-voltage measurement or an oscilloscope check, it must be assumed that the trouble is in the filter circuit or the associated load.

If the vibrator-type power supply blows its dc input fuse each time the supply is energized, the vibrator should be removed from its socket, and, with a new fuse installed, the input power applied once again to determine whether a defective vibrator is the cause of excessive input current. When burned or pitted vibrator contacts stick together, a heavy current flows in the associated primary winding; this current is likely to blow the fuse because of the low dc resistance of the winding. A check of the input current should be made with an ammeter to determine whether this current is within tolerance, or whether it is excessive. With the vibrator removed from its socket, continuity measurements of the transformer primary circuit may be made to determine whether the primary winding is open, shorted, or grounded.

A shorted buffer capacitor C2 can be detected by a higher than normal input current to the supply and a very low ac voltage at the secondary terminals of the transformer. The replacement buffer capacitor should be the same value as the original capacitor and of equal or greater voltage rating. A leaky or shorted filter capacitor C1 will also cause the input current to the supply to be above normal. Also, a short in filter capacitor C3 or an open r-f choke RFC2 will result in no output from the power supply.

Low Output. A low-output condition in a synchronous vibrator-type power supply usually results from a defective vibrator, a leaky buffer capacitor, low input voltage, or a defective component in the filter circuit.

A voltage drop in the primary leads to the supply, due to the high resistance of a defective terminal or connector, can result in low output; therefore, the input voltage should be checked at the transformer or vibrator terminals to determine whether the input voltage is present and of the correct value.

The ac voltage may be measured between the center tap and each end of the secondary to deter-

mine whether the two measurements are equal and approximately the values specified for normal operation of the supply. The test procedures described for the no-output condition and in previous paragraphs can be used to determine whether the vibrator is at fault. A defective vibrator with only one set of properly making contacts results in reduced output from the supply and poor filtering. A vibrator in which "frequency hunting" occurs may be detected by an uneven or irregular buzzing noise; this trouble is usually caused by an excessive load current, and is an indication of impending vibrator failure. Frequency hunting can also be caused by burned or pitted vibrator contacts which are sticking; this usually results in a higher than normal input current and reduced output from the supply. A check of the input current should be made with an ammeter to determine whether the current is within tolerance; also, an oscilloscope check of the waveform at the primary of the transformer should be made to determine whether the vibrator is faulty; an additional check should also be made at the secondary center tap to determine whether the rectifier contacts are operating correctly. Shorts, leakage, or excessive current drain in the filter circuit or in the high-voltage load circuit external to the supply will cause a heavy load on the vibrator contacts, and may cause early failure of the vibrator. The output load current should be measured after installation of a replacement vibrator to determine whether the load current is within tolerance; if the load current is excessive, the replacement vibrator may be damaged unless the cause for the excessive load current is found and corrected.

In one circuit variation of a synchronous vibrator supply, buffer capacitor C2 is actually two capacitors; one capacitor is connected at each end of the transformer secondary to ground (chassis). If one of these buffer capacitors becomes shorted, the output voltage will be reduced accordingly.

Continuity measurements of the primary and secondary windings of transformer T1 should be made, since an open circuit in either of the windings will cause a reduction in output.

The power supply output current should be checked to make sure that it is within tolerance. A low-output condition due to a decrease in load resistance will cause an increase in load current; for example, excessive leakage in the capacitors of the output filter circuit will result in increased load current.

SECTION 3 VOLTAGE REGULATORS

PART 3-0. INTRODUCTION

VOLTAGE REGULATION CIRCUITS

General.

Most electronic equipment can operate satisfactorily with a certain amount of variation in the supply voltage without affecting equipment performance. However, the operation of certain circuits is very sensitive to slight changes in supply voltage; thus, the use of a voltage regulator is required.

A voltage regulator is a device connected in the output of a supply to maintain the output voltage at a specified value. The regulator circuit reacts automatically within its design limits to compensate for any change in the output voltage, due either to a change in the supply voltage or to a change in the load current.

Voltage regulation can be provided by any of several means, depending upon the type of supply and the type of regulation required. The three basic classifications of voltage regulators discussed in this section are the electronic voltage regulators, electro-mechanical voltage regulators, and electromagnetic voltage regulators. General discussions of these three classifications are given below.


ELECTRONIC REGULATORS

General.

The electronic voltage regulator can be compared to a variable resistance, R_s , in series (series type) or in parallel (shunt type) with a load resistance, R_L , at the output of the power supply. The shunt type is commonly used where input voltage variations are small and the load remains relatively constant. The series is a more efficient regulator and is used in power supply applications where the load resistance and input voltage variations are large, or where a constant current rather than a constant voltage is the primary requirement.

Series Regulator.

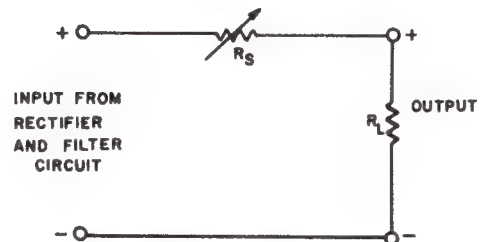A simple series type voltage regulator is shown in the illustration below.



Simple Series-Type Voltage-Regulator Circuit

Variable resistance R_s and load resistance R_L form a voltage divider. If the supply voltage increases, resistance R_s is increased, again maintaining a constant voltage across the load. Similar variations in R_s occur for any variations in the load. If the load resistance increases, with a decrease in load current, R_s is made smaller; thus the voltage dropped across it is less, and the voltage across the load is maintained constant. With a decrease in the load resistance and a corresponding increase in the load current, the resistance of R_s is made larger, causing a greater drop across it; again the constant voltage across the load is maintained.


Thus, it is seen that the voltage regulator is essentially a voltage-divider circuit, with the voltage drop across the series resistor absorbing any changes in the supply voltage or the load current, so that the voltage across the load is held constant.

Shunt-Type Regulator.

The shunt-type regulator, while one of the simplest regulators, is usually the least efficient. It may

be used to provide a regulated output where the load is relatively constant, the voltage low to medium, and the output current high. The shunt regulator utilizes the voltage-divider principle to obtain regulation of the output voltage.

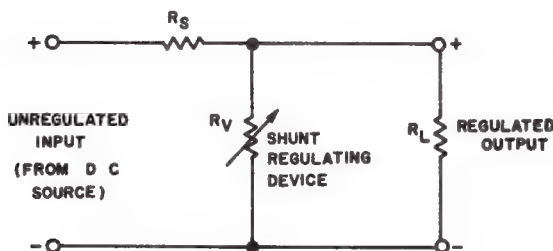The accompanying illustration shows the shunt-type regulator reduced to its fundamental form. The fixed resistor, R_S , is in series with the parallel combination of the load resistance, R_L , and the variable resistor, R_V , and forms a voltage divider across the input circuit.



Simple Shunt-Type Voltage-Regulator Circuit

All current that flows in the complete circuit passes through the series resistance, R_S . The magnitude of this current, and thus the value of the voltage drop across R_S , is controlled by variable resistance R_V . The voltage across R_S is equal to the difference between the larger voltage of the dc source and the output voltage across load resistance R_L . The difference voltage across R_S is varied by action of resistance R_V , as required, to compensate for circuit changes and maintain the output voltage to the load, constant, at the desired value.

If the input voltage to the regulator circuit decreases, the voltage across load resistance R_L and the variable resistance, R_V , tends to decrease. To counteract this decrease, the resistance of R_V is increased; this reduces the total current flow through R_S and thereby the voltage drop across it. Thus, by decreasing the difference voltage of R_S to compensate for the decrease in the input voltage, the output voltage remains constant at its nominal value. Conversely, if the input voltage increases, the voltage across R_L and R_V tends to increase. To counteract the increase, the resistance of R_V is decreased; this results in more current through R_S and thus an increase in the voltage


drop across it. The increase in the difference voltage compensates for the increase in the input voltage, and again, the output voltage remains constant at the regulated value.

The shunt regulator must be capable of withstanding the entire output voltage of the dc source; however, it does not have to carry the full load current unless it is required to regulate from the no-load to the full-load condition. Since series dropping resistor R_S , used with the shunt regulator, has relatively high power dissipation, the over-all efficiency of this type of regulator may be less than that of other types. One advantage of the shunt-type regulator is the inherent overload and short-circuit protection offered. This is because the series resistance, R_S , is between the dc source and the load; thus, a short circuit or overload merely decreases the output voltage from the regulator circuit. Note that under no-load conditions, however, the shunt regulating device must dissipate the full output; therefore, the shunt-type regulator is most often used in constant-load applications.

In the simple voltage-regulator circuit illustrated above, it is assumed that variable resistance R_V is varied manually to keep the voltage across the load constant. In an actual regulated power supply, the control action required to vary the series resistance, and, consequently, to produce a corresponding variable voltage drop, is completely automatic. This basic principle of voltage regulation can be accomplished by use of either a gas-tube regulator or by an electron tube regulator, both of which are described in this section of the handbook.

Gas-Tube Regulator.

The gas-tube regulator is the simplest type of automatic voltage regulator, as illustrated below. A characteristic of the gas-tube is that within the operating range of the tube, as the voltage across the tube increases, the resistance of the tube decreases and the current through the tube therefore increases. The tube thus acts as a variable resistance. This increase in current through the tube causes the current through R_S to increase and the voltage drop across it to increase. Thus the voltage increase is developed across R_S , and the voltage drop across V_1 (and across R_L which is in parallel with V_1) returns to normal. A decrease in the input voltage operates in the reverse manner. A more detailed discussion of the gas-tube regulator is given later in this section.

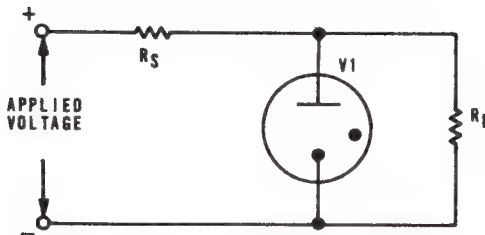


Simple Voltage Regulator Using Gas-Tube

Electron Tube Regulator.

An electron tube may also be considered as a variable resistance. Although the tube is conducting, its effective resistance is the plate-to-cathode voltage divided by the plate current. This calculated value of resistance is called the *dc plate resistance*, or R_p , of the tube. For a given applied plate voltage, the value of R_p depends on the current through the tube, which, in turn, depends on the grid bias of the tube. Therefore, varying the grid bias applied to the tube controls the amount of current through the tube and causes the dc plate resistance, R_p , to vary accordingly.

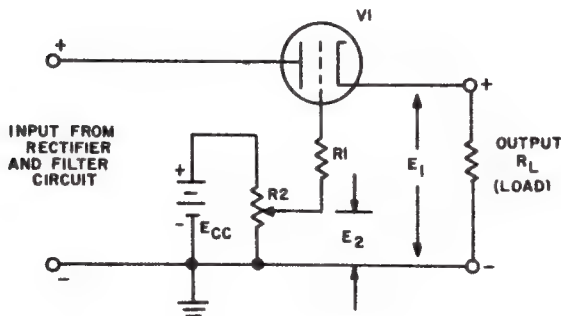The accompanying illustration shows a triode used as a variable resistance in a simple voltage-regulator circuit.



Simple Voltage-Regulator Circuit Using Triode Electron Tube

The dc plate resistance, R_p , of the series regulator tube, V_1 , is established by the grid bias of the tube. The actual grid bias, e_g , is the grid-to-cathode voltage; it equals $E_2 - E_1$. Potentiometer R_2 is placed across E_{CC} to provide a variable source of grid voltage. It is


adjusted until the grid bias is the value that will allow V_1 to conduct the exact value of load current required to produce the desired value of voltage E_1 across the load resistance R_L . Thus, adjustment of the bias alters the R_p of V_1 to control the current through the tube, the voltage drop across the tube, and, therefore, the voltage across the load. Consider the condition where voltage E_1 tries to increase, due either to an increase in the supply voltage, or to an increase in the load resistance. As E_1 goes more positive, e_g is made more negative ($e_g = E_2 - E_1$), the conduction of the tube is reduced, the voltage drop across the tube is increased, and the voltage across the load is kept constant. Conversely, if voltage E_1 tends to decrease, due either to a decrease in the supply voltage or to a decrease in the load resistance, e_g becomes less negative. This causes an increase in the conductivity of the tube, a decrease in its R_p , a corresponding decrease in the voltage drop across the tube; again the voltage across the load is maintained constant. In a properly designed regulator circuit, the voltage change which occurs across the series regulator tube is approximately equal to the voltage change which appears across the combined resistance of the regulator tube and the load; thus the voltage across the load remains constant.

Since the series regulator may not be sufficiently sensitive to small voltage changes, the output voltage of the simple voltage regulator may not be held absolutely constant. Therefore, where the regulation must be held to a small percentage, additional amplification must be used to increase the sensitivity of the regulator circuit.

Regulated Power Supplies.

A complete regulated power supply consists of a power source, a transformer, rectifier, and filter circuit, and a dc regulator circuit. The dc regulator circuit may, in turn, be subdivided into four parts: series regulator electron tube(s), dc amplifier, voltage-comparison circuit, and reference-voltage circuit. The dc amplifier, the voltage-comparison circuit, and the reference-voltage circuit are considered as one complete functional circuit, generally referred to as the *regulator-amplifier* circuit of the electronic voltage-regulated power supply. The design of the regulator-amplifier circuit depends primarily upon the degree of voltage regulation desired, and is relatively independent of the load current to be supplied. The majority of regulated power supplies which are used

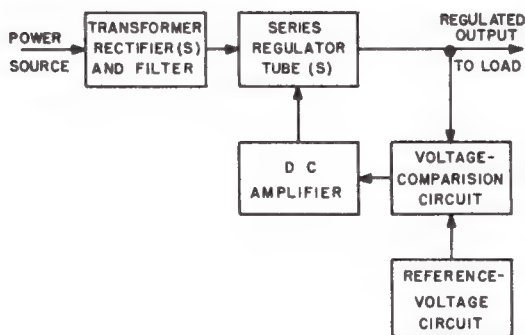to provide plate and screen potentials for electronic equipments provide an output voltage of 150, 250, or 300 volts, dc, with either a positive-output or a negative-output polarity. A typical electronic voltage-regulated power supply is shown in the accompanying block diagram.



Block Diagram of Electronic Voltage-Regulated Power Supply

The series regulator tube, sometimes called the series control tube, used in the electronic voltage regulator is generally one of three possible circuit configurations: a triode-connected beam power tube, such as the type 6L6 or 6Y6; a low- μ , high-conduction triode tube, such as the type 6AS7 or 6080; or a beam power tube, such as the type 6L6, operated with a separate screen supply. The first two configurations mentioned are in common use. The third configuration has the disadvantage of requiring a separate power supply for the screen potential; for this reason its use is somewhat limited.

The triode-connected beam power tube used as a series regulator tube has a higher gain characteristic and provides a greater useful percentage of rated capacity over the other circuit configurations. Additionally, the triode-connected beam power tube requires a lower plate-voltage swing of the associated dc amplifier. The low- μ , high-conduction triode offers the advantage of a low dc plate resistance, and is frequently used where minimum power loss in the regulator circuit is an important consideration. The beam power tube operated with a separate screen supply has the advantages of a high gain characteristic, a low plate resistance, and a generally higher plate dissipation than the first two configurations mentioned above, but it does have a disadvantage in that a separate screen-voltage supply is required.

Regulator-amplifier circuits generally fall into one of several circuit configurations: single pentode, twin-triode cascode, twin-triode cascade, twin-triode and pentode with balanced input, and pentode and twin-triode with balanced output. For each of these regulator-amplifier circuit configurations, there are basic circuit variations which result. There is different reference-voltage polarities, different connection points for the amplifier plate-load resistor(s), various methods used to obtain voltage comparison, and in the case of a pentode dc amplifier, various connection points for the screen-dropping resistor. These and other typical circuit variations will be discussed in connection with the various types of electronic voltage-regulator circuits described in this section of the handbook.

ELECTROMECHANICAL REGULATORS

General.


Electromechanical regulators are automatic devices which are mechanical rather than electronic in nature and affect the power source itself; these regulators hold the output of a dc generator, ac generator (alternator), or other source of primary power at a predetermined value, or vary the output according to a predetermined plan. Because the power source always has some internal resistance or reactance, the output voltage changes when the load is varied; the amount of output-voltage variation depends upon the design of the dc or ac generator. In the case of an ac generator (alternator), the power factor of the load also influences the amount of variation. Under conditions of varying load, some form of voltage regulation is necessary to maintain the output voltage relatively constant; thus, the primary purpose of the regulator is to automatically compensate for any changes in output voltage.

Electromechanical voltage regulators control the generator or alternator output by controlling the current flow through the field (or exciter) winding of the machine. In most cases, control is accomplished by changing the resistance of the field circuit, which controls the field current, thus controlling the output voltage.

The operation of a typical regulation system can be briefly explained as follows: a drop in output voltage sensed by the regulator causes the regulator to increase the field current, and an increase in field current causes a corresponding increase in output voltage to compensate for the original drop in output voltage.

If the output voltage should rise, the regulator decreases the field current, causing a corresponding decrease in output voltage to compensate for the original rise in voltage. Thus, the regulator senses a change in output voltage and compensates for this change by altering the field current accordingly. The major difference between voltage-regulator systems, concerns the method used to control the field current.

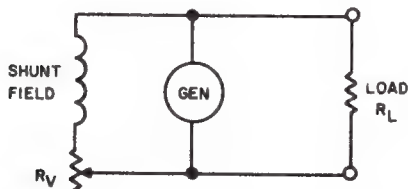The accompanying illustration shows a simplified circuit for controlling the output of a generator.




Simplified Circuit for Control of Generator Output

In this simplified circuit, variable resistor R_v is connected in series with the shunt field circuit of the generator. The purpose of this resistor is to control the current flow through the field winding and thus affect the strength of the magnetic flux developed by the field. (As the magnetic flux is either increased or decreased, the output voltage is either raised or lowered.) If the resistance of R_v is increased, less current flows through the shunt field, the magnetic flux developed by the field winding is decreased, and the voltage output developed across load resistance R_L is decreased. Conversely, if the resistance of R_v is decreased, more current flows through the shunt field, the magnetic flux developed by the field winding is increased, and the voltage output developed across load resistance R_L is increased. This principle of output-voltage control was briefly described in connection with rotating electromechanical power sources (generator and inverter), discussed in the Electromechanical Power Supplies.

There are three common types of electromechanical regulators in general use: the vibrating-contact regulator, the carbon-pile regulator, and the multitapped resistor regulator using a finger-type contactor or similar mechanical device. A brief description of the construction, operation, and application of the three types of voltage regulators is given in the following paragraphs.

Vibrating-Contact Regulator.

The vibrating-contact regulator is commonly used to control the output of battery-charging generators in automotive, small-boat, and some aircraft applications where the speed of generator rotation varies with engine speed. The vibrating-contact regulator operates on the principle that an intermittent short circuit applied across a resistor which is in series with the shunt field winding causes the output voltage of the generator to fluctuate within narrow voltage limits; such a regulator will maintain an average value of output voltage which is independent of load changes. The accompanying illustration shows a simplified circuit for a vibrating-contact regulator.

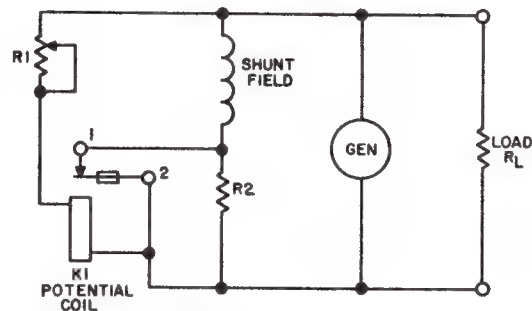

Simplified Circuit for Vibrating-Contact Regulator

In this simplified circuit, a vibrating-contact relay, K1, is used as a voltage regulator. Resistor R1 is a voltage-dropping resistor in series with a solenoid, called the *potential coil*, which is part of relay K1. Resistor R2 is in series with the shunt field winding of the generator. The value of resistor R2 is chosen so that if the vibrating contacts of the relay were not in the circuit (held open), the value of output voltage would be approximately 60 percent of the desired value of output voltage when the generator is running.

at normal speed. If the contacts of the relay are held closed, resistor R2 is shorted by the contacts and maximum current flows through the shunt field winding; thus, the output voltage of the generator is maximum. Thus, it can be seen that in actual practice when the contacts open and close rapidly to intermittently short out resistor R2, the output voltage will reach a value which is greater than 60 percent of the desired value and less than the maximum value. For example, when the output voltage of the generator rises above a critical value, the voltage developed across the potential coil of the relay develops sufficient magnetic flux to attract the armature (or reed), and contacts 1 and 2 of the relay momentarily open to place resistor R2 in series with the shunt field winding. Thus, the current through the field is momentarily reduced and the output voltage of the generator is also momentarily reduced. Then, when the output voltage of the generator drops below a critical value (after the opening of contacts 1 and 2), the voltage developed across the potential coil decreases so that there is no longer sufficient magnetic flux to attract the armature, and contacts 1 and 2 of the relay close to short out resistor R2. Thus, the current through the field winding is maximum and the output voltage of the generator is momentarily increased.

The cycle described above is repeated when the potential coil again develops sufficient magnetic flux to attract the armature and open the contacts of the relay; the action described is rapid, and continues at a rate of approximately 60 to 240 times a second, so that an average voltage is maintained regardless of changes in load. If the load is increased and the output voltage tends to fall, the momentary voltage decrease is reflected by a decrease in voltage applied to the potential coil; thus, the armature vibrates more slowly, permitting an increased average current flow in the field winding. As a result, the output voltage is returned to the normal value. On the other hand, if the load is decreased and the output voltage tends to rise, the momentary voltage increase, when reflected to the potential coil, causes the armature to vibrate more rapidly and thus decrease the average current flow in the field winding. As a result, the output voltage is returned to the normal value.

In a practical application of this type of regulation, means must be provided for adjusting the regulator to obtain the desired value of output voltage. This is accomplished by one or both of the following


methods: resistor R1 or resistor R2 is made adjustable to change the value of resistance in the circuit, or the armature (reed) tension is made adjustable to change the amount of magnetic flux required to attract the armature to the solenoid.

The vibrating-contact regulator is sometimes used to control the output of a multiphase ac generator (alternator). When this is the case, the potential coil receives its operating current from a rectifier connected to one phase of the ac output, and the regulation action is the same as that described for the dc generator.

From the brief discussion given here, it can be seen that the vibrating-contact regulator acts as an automatic variable resistance in the field circuit of the generator, to hold the output voltage at a steady value for any change in load which occurs within the no-load to full-load operating conditions of the generator.

Carbon-Pile Regulator.

The carbon-pile regulator is commonly used to control the output of generators, alternators, and inverters used in automotive, shipboard, and aircraft applications. The carbon-pile regulator operates on the principle of a variable resistance (in the form of a stack of carbon disks) in series with the shunt field winding, to control the current through the field and thus the output voltage of the generator. The accompanying illustration shows a simplified circuit for a carbon-pile regulator.

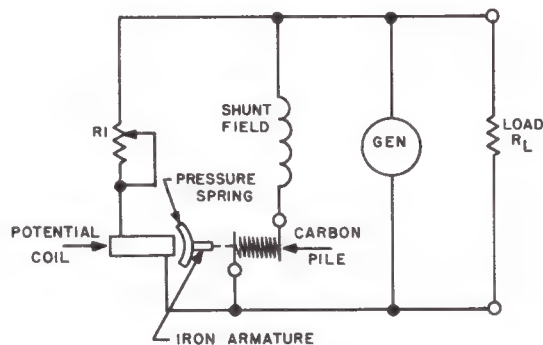

Simplified Circuit for Carbon-Pile Regulator

In this simplified circuit, resistor R1 is a voltage-dropping resistor in series with a solenoid (electromagnet), called the *potential coil*; the resistor determines the current flow through the solenoid, and thus affects the magnetic flux developed by the solenoid. A resistance in the form of a stack of carbon disks, called the *pile*, is placed in series with the shunt field winding, to act as a variable resistance which can be controlled automatically. The resistance of the carbon pile depends upon the mechanical pressure applied to the pile by a spring which presses a movable iron armature against the end of the pile. The greater the mechanical pressure applied to compress the carbon disks, the smaller will be the resistance of the pile; if the mechanical pressure is decreased, the resistance of the pile increases. A change in mechanical pressure is accomplished by placement of the solenoid in proximity to the iron armature so that the magnetic flux developed by the solenoid acts to pull (attract) the iron armature away from the carbon pile. In a steady-state condition, the magnetic force attracting the iron armature is opposed by the mechanical force of the spring against the iron armature.

For example, assume that the output voltage of the generator rises above a critical value. The voltage developed across the potential coil increases to develop a stronger magnetic field. Thus, the potential coil offers greater attraction to the iron armature and relieves the mechanical pressure exerted on the carbon disks; as a result, the resistance of the pile increases, the current through the shunt field winding decreases, and the output voltage returns to its former value. Conversely, when the output voltage falls below a critical value, the voltage developed across the potential coil decreases, and the strength of the magnetic field developed by the potential coil also decreases. Thus, the potential coil offers less attraction to the iron armature, and the spring places a greater mechanical pressure on the carbon disks; as a result, the resistance of the pile decreases, the current through the shunt field winding increases, and the output voltage returns to its former value.

The operation of the carbon-pile regulator may be briefly summarized as follows: when the output voltage rises, the spring pressure applied to the carbon pile decreases, causing an increase in pile resistance and a decrease in shunt field current; when the output voltage falls, the spring pressure applied to the carbon pile increases, causing decrease in pile resistance and an increase in shunt field current. The

resultant decrease or increase in shunt field current lowers or raises the generator output, accordingly.

In a practical application of this type of regulator, means must be provided to adjust the regulator in order to obtain the desired value of output voltage. This is normally accomplished by an initial adjustment of the mechanical spring pressure (with resistor R1 set at mid-range), to obtain a steady-state condition whereby the magnetic force and the mechanical force are in balance; minor variations in voltage characteristics during normal operation are compensated for by an adjustment of resistor R1, which controls the current through the potential coil, to set the generator output voltage to the desired value.


The discussion in the preceding paragraphs has been primarily concerned with the operation of the carbon-pile regulator in conjunction with a dc generator; however, this type of regulator can be used equally well in an ac generating system. In practice, the output voltage of a multiphase ac generator (alternator) is controlled by varying the dc excitation current applied to the field winding of the machine. In this case, the carbon-pile regulator obtains a dc voltage for operation of the potential coil from a rectifier which is connected to one phase of the ac output, and the regulation action is the same as that described for the dc generator.

From the brief discussion given here, it can be seen that the carbon-pile regulator acts as an automatic variable resistance in the field circuit of a dc generator or in the field (exciter) circuit of an ac generator (alternator), to hold the output voltage at a specified value of voltage regardless of changes in load.

Multitapped-Resistor Regulator.

The multitapped-resistor regulator is commonly used to control the output of generators, alternators, and inverters used in shipboard and shore-based applications. The multitapped-resistor regulator operates on the principle of a stepped, variable resistance connected in series with the generator field winding to control the current through the field, and thus the output of the generator. Basically, the multitapped-resistor regulator consists of a single multitapped resistor (or several resistors connected in series), the terminals of which are either selected or shorted out automatically to obtain the desired resistance value. The name given to a particular regulator configuration is derived from the manner in which the over-all series resistance is determined. For example, the

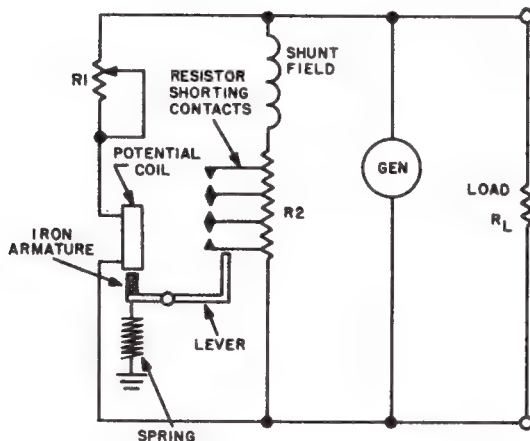name *finger-type* regulator, *tilted-plate* regulator, or *rocking-disk* regulator, merely signifies the electro-mechanical method used to achieve physical contact and thus obtain a variable-resistance action within the regulating device. The accompanying illustration shows a simplified circuit for a typical multitapped-resistor regulator.



Simplified Circuit for Multitapped-Resistor Regulator

In this simplified circuit, resistor R_1 is a voltage-dropping resistor in series with a solenoid, called the *potential coil*; the resistor determines the current flow through the solenoid, and thus affects the magnetic flux developed by the solenoid. Resistor R_2 is the series resistor in the shunt-field circuit; R_2 is a multitapped resistor, with the taps on the resistor connected to leaf springs (fingers) which are insulated from each other and are stacked one above the other. Electrical contacts are located at one end of each leaf spring. These contacts are arranged so that as mechanical pressure is increased at one end (lower end) of the stack, the number of electrical contacts that close is increased to short out sections of resistor R_2 . Thus, the greater the mechanical pressure applied to the stack of leaf springs, the smaller the effective series resistance of R_2 . If the mechanical pressure is decreased, the effective series resistance of R_2 will be increased. A change in mechanical pressure is accomplished by placement of the solenoid in proximity to the iron armature, which is spring-loaded and linked mechanically through a lever system to the stack of

leaf springs. In a steady-state condition, the magnetic force attracting the iron armature is opposed by the mechanical force of the armature spring pulling against the iron armature, and only a few contacts are closed on the stack of leaf springs to provide some intermediate value of resistance.

When a change in generator output voltage occurs, the voltage developed across the potential coil changes; thus, the magnetic flux developed by the potential coil also changes. As a result, the mechanical force exerted on the stack of leaf springs is altered to change the number of contacts which are closed. This, in turn, changes the value of resistance (R_2) in series with the shunt field winding and compensates for the change in output voltage. For example, assume that the output voltage of the generator rises above the critical value. The voltage developed across the potential coil increases to develop a stronger magnetic field. Thus, the potential coil offers greater attraction to the iron armature and decreases the mechanical pressure exerted on the stack of leaf springs (through the lever system); as a result, the value of resistance (R_2) in series with the shunt field winding increases, the current through the shunt field winding decreases, and the output voltage returns to its former value. Conversely, when the output voltage falls below a critical value, the voltage developed across the potential coil decreases, and the strength of the magnetic field developed by the potential coil also decreases. Thus, the potential coil offers less attraction to the iron armature, and the armature spring places a greater mechanical pressure on the stack of leaf springs; as a result, the value of resistance (R_2) decreases, the current through the shunt field winding increases, and the output voltage returns to its former value.

In a practical application of the multitapped-resistor regulator, regardless of the mechanical configuration employed to change the value of resistance, means must be provided for adjusting the regulator to the desired value of output voltage. This is normally accomplished by an initial adjustment of the mechanical spring tension which acts upon the armature and lever system (with resistor R_1 set at mid-range), to obtain a steady-state condition whereby the magnetic force and the mechanical force are in balance. Minor variations in voltage characteristics during normal operation are compensated for by an adjustment of resistor R_1 , which controls the current through the

potential coil, to set the generator output voltage to the desired value.

The discussion in the preceding paragraphs has been primarily concerned with the operation of the multitapped-resistor regulator in conjunction with a dc generator; however, this type of regulator is frequently used in an ac generating system. When the multitapped-resistor regulator is used to control the output of a multiphase ac generator (alternator), the regulator obtains a dc voltage for operation of the potential coil from a rectifier connected to one phase of the ac output voltage, and the regulation action is the same as that described for the dc generator.

In conclusion, it can be seen that the multitapped-resistor regulator acts as an automatic variable resistance in the field circuit of a dc generator or in the field (esciter) circuit of an ac generator (alternator), to hold the output voltage at a specified value of voltage regardless of changes in load.

From the brief descriptions of voltage regulators given in the preceding paragraphs, it can be seen that the vibrating-contact regulator, the carbon-pile regulator, and the multitapped-resistor regulator are merely controlled, automatic variable resistors. The detailed theory of operation and the construction of electro-mechanical regulators are covered in Navy publications on basic electricity (or in course materials for EM and AE ratings), and, therefore, will not be treated in this handbook. Only the basic principles will be discussed in this section of the handbook, as required, to provide a better understanding of the application and the failure analysis of the electro-mechanical regulators discussed.

ELECTROMAGNETIC REGULATORS


General.

Electromagnetic regulators are automatic devices which are magnetic rather than electronic or mechanical in nature. These regulators are of two basic types: the induction regulator, which employs a variable-inductor transformer, and the saturable-core-reactor regulator. An application of the induction regulator is its use in an ac power regulator and distribution system wherein the unregulated power from the generating source is converted into a form required by the electronic systems or equipment at a particular facility or installation. The saturable-core-reactor regulator is used in such applications as the regulation of

the ac voltage input to an electronic equipment or the equipment's power supply, or the regulation of the dc voltage output from the power supply in a given electronic equipment. Each of the two types of electromagnetic regulators will be discussed in the following paragraphs.

Induction Regulator.

An example of an induction regulator used in an ac regulation and distribution system is illustrated in the accompanying block diagram. The input power (in this case, three-phase, 60 Hz ac) is applied through a transfer switch that automatically connects to an emergency power source when the normal source voltage between any phase and the neutral line falls below a predetermined level. When the normal source voltage returns to the proper level, the transfer switch again connects to the normal source.

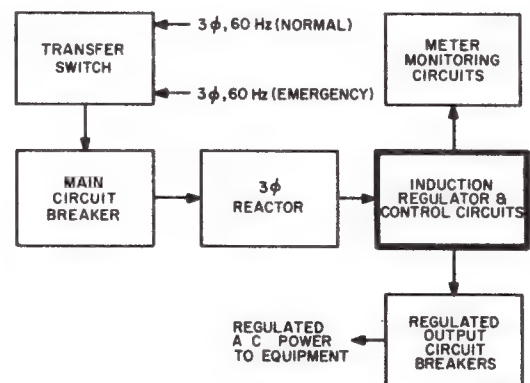


AC Regulation and Distribution System Using Induction Regulator

After passing through the transfer switch, the input power is applied through the system main circuit breaker to a three-phase reactor. The purpose of the three-phase reactor is to limit any short-circuit currents within the system to a preselected value of the regulator full-load current for any one phase. The reactor opposes large, rapid changes of current until a circuit breaker trips and opens the circuit; in this manner the system is protected and the effects of short circuits are localized. The output from the three-phase reactor is applied to the induction regulator and its associated control circuits. The regulated

ac output is then fed through a circuit-breaker panel to the applicable equipment. Voltage and current meters monitor the load voltages and currents at the output of the induction regulator.

A simplified diagram of a three-phase induction regulator and its control circuits is given in the accompanying figure. The voltage-regulating component of this regulator is a variable-inductor transformer which is split into a rotating section and a stationary section. The rotating section, or rotor, for each phase is connected across the input line; hence, it is in parallel with the load (R_L) for that phase. The stationary section, or stator, for each is connected in series with the input line; hence, it is in series with the load for that phase. A variation in the output (load) voltage is obtained by rotating the rotor inside the stator to change their flux linkage in both magnitude and direction. Thus, depending upon their relative angular positions, the rotor induces in the stator

a voltage that either aids or opposes the line voltage. When the stator voltage aids the rotor voltage, the load voltage is greater than the input voltage. That is, the load voltage will be maximum when both the flux linkage between rotor and stator and the voltage induced in the stator are maximum, and the stator voltage is in phase with the rotor voltage. When the rotor is turned 180 degrees, both the flux linkage between rotor and stator and the voltage induced in the stator will again be maximum, but the voltage induced in the stator will be out of phase with the rotor voltage. Hence, at this time the stator voltage opposes the rotor voltage and the load voltage is minimum. For relative angular positions of rotor and stator between the extremes noted, the load voltage likewise will be a value between the maximum and minimum extremes.

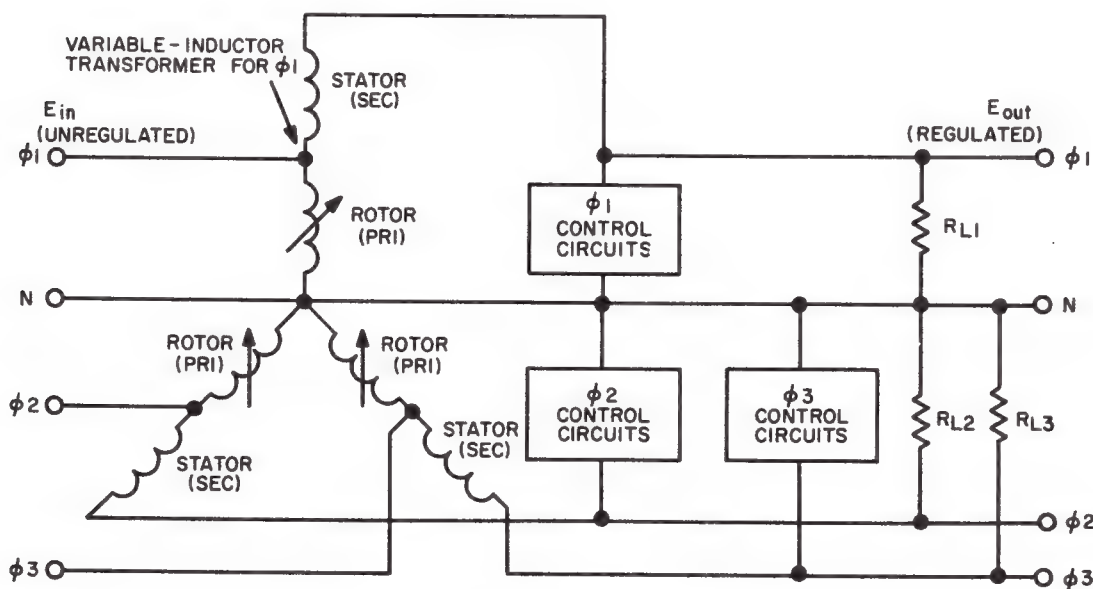


Three-Phase Induction Regulator,
Simplified Diagram

The rotation of the rotor is accomplished by a reversible motor, which, in turn, is controlled by the action of two relays; this arrangement is illustrated schematically in the accompanying diagram. In a typical application of an induction regulator, a variable-inductor transformer and its associated control cir-

cuits are placed in each phase line of the distribution system. In this case, however, only the control circuits for phase 1 will be analyzed; the phase 2 and phase 3 control circuits are identical to those of phase 1, and thus will not be considered in this discussion.

The output voltage of the selected-phase variable-inductor transformer is sensed by a voltage-regulating relay, K1, which causes a motor-control relay, K2, to operate a reversible motor. The motor, B1, drives the

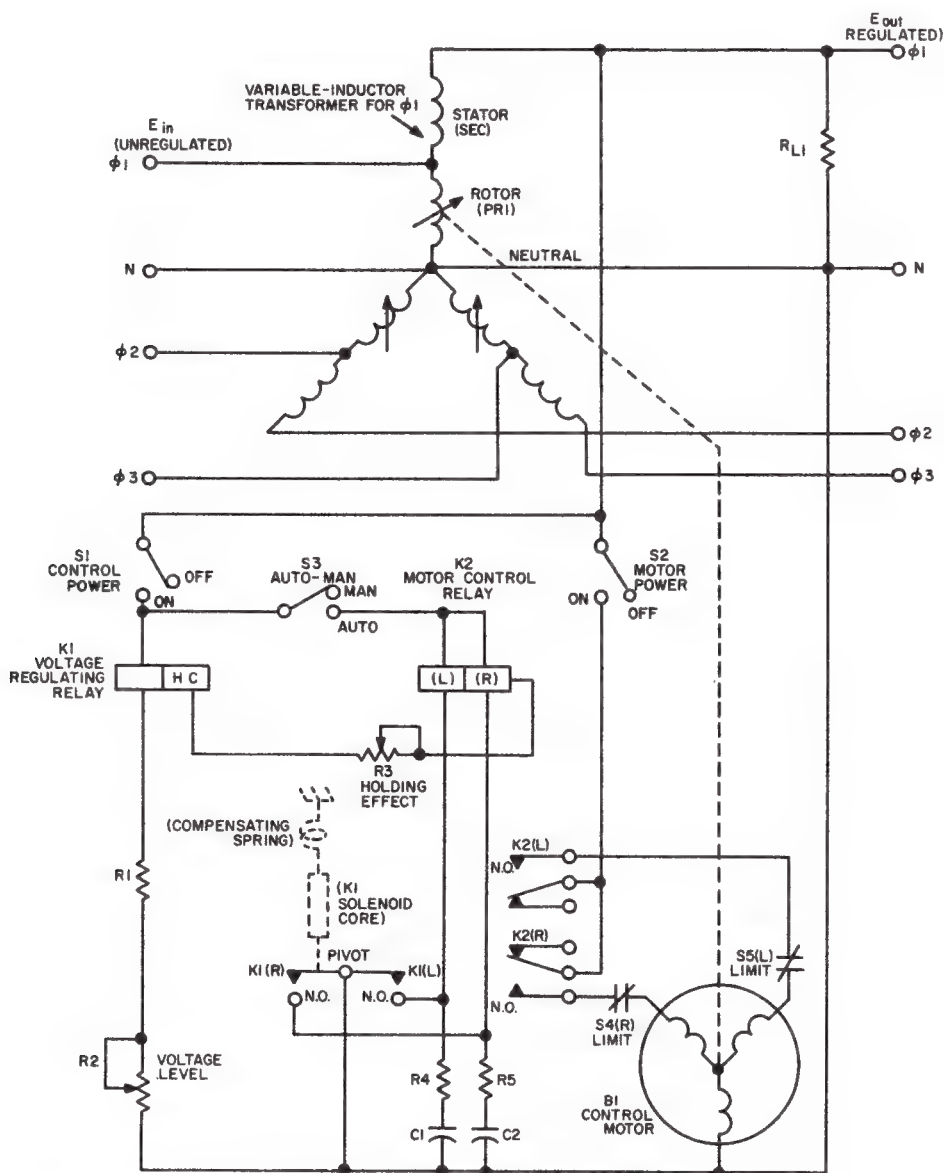rotor of the applicable variable-inductor transformer in the direction necessary to compensate for the output-voltage variation.



NOTES:

1. (R)-RAISE
2. (L)-LOWER
3. HC-HOLDING COIL FOR K1.
4. N.O.-NORMALLY OPEN CONTACT.

Induction Regulator and Control
Circuit for Phase 1

The sensing element of voltage-regulating relay K1 is an iron-core solenoid, which is suspended on a compensating spring. (The solenoid core and compensating spring are shown dotted in the illustration.) The solenoid current is made proportional to the output voltage by inserting limiting resistors R1 and R2 in series with the solenoid coil. In this manner, the solenoid current is maintained constant for a given voltage, and yet it can still change with the voltage to be regulated. A holding coil is wound in the opposite direction over the solenoid coil of K1; the holding coil, HC, is excited through the tapped sections of the K2 motor-control relay coils. The purpose of the holding coil is twofold: to modify the "pull" of the K1 solenoid, and to hold the contacts of K1 closed until the control motor has caused the variable-inductor transformer to correct the output voltage. When voltage-regulating relay K1 is in operation for a normal output voltage, the pull of its solenoid, which varies with the current through the coil, and the tension of the compensating spring are balanced against the weight of the solenoid core. The solenoid core operates a set of single-pole, double-throw contacts mounted on opposite ends of a pivoted beam and separated by equal distances from the stationary contacts; one normally open contact of the set closes when the output voltage increases, and the other normally open contact of the set closes when the output voltage decreases. This action causes voltage-regulating relay K1 to operate motor-control relay K2, which, in turn, causes control motor B1 to turn and thus rotate the rotor of the variable-inductor transformer to correct the output voltage when this voltage is higher or lower than normal. In the accompanying diagram, the symbols (L) and (R) denote the components that produce the action necessary to "lower" and "raise" the output voltage, respectively.

Consider, now, the operation of the induction regulator when the output voltage of phase 1 increases above the level determined by the setting of voltage-level potentiometer R2. To energize the control circuits, including the control motor, control-power switch S1 and motor-power switch S2 must be set to the "ON" position, and auto-manual switch S3 must be set to the "AUTO" position. Since the output voltage is higher than normal, the control motor must rotate the rotor of the variable-inductor transformer in the direction which will lower the voltage; this is accomplished in the manner described below. The

higher-than-normal output voltage of phase 1 causes an increase in the current through the solenoid coil of voltage-regulating relay K1. The stronger magnetic field resulting from the increased current exerts a greater pull and draws the solenoid core farther into the coil, thus relaxing the tension on the compensating spring. When the tension on this spring is relaxed sufficiently, the normally open contacts on the K1 (L) section of the voltage-regulating relay close. When this occurs, the "lower" (L) coil of motor-control relay K2 energizes and closes the normally open (N.O.) contacts on the K2 (L) section of this relay. Closing the K2 (L) contacts of the motor-control relay applies a voltage to the control motor, B1, thus energizing the motor and causing it to turn to the "lower" direction. The control motor is mechanically coupled to the rotor of the phase 1 variable-inductor transformer. Therefore, when the motor turns, it also turns the rotor of the variable-inductor transformer in the direction which will cause less flux linkage between the rotor (primary) and the stator (secondary). As a result, there will be less voltage induced in the stator; that is, since the stator, or output, voltage varies with the flux linkage between the rotor and the stator, reducing the flux linkage causes a reduction in the output voltage.

The control motor turns the rotor of the variable-inductor transformer until the output voltage again becomes normal. As this point is approached, the current through the solenoid coil of voltage-regulating relay K1 decreases, since this current is proportional to the output voltage. Thus, at the predetermined level of output voltage, sensed by the current through the coil of K1, the weaker magnetic field resulting from the decreased current exerts a lesser pull on the solenoid core of K1, so that the weight of the core and the tension of the compensating spring are again in balance. When this occurs, the (K1(L) contacts of the voltage-regulating relay open, thereby causing the "lower" (L) coil of K2 to de-energize and, in turn, to open the K2(L) contacts of the motor-control relay. Opening the K2(L) contacts of the motor control relay removes the energizing voltage from control motor B1, and the motor stops turning. When the motor stops turning, the rotor of the variable-inductor transformer also stops turning, and remains stationary at the normal output-voltage level until a further variation from normal occurs.

Assume that the output voltage of phase 1 now decreases below the predetermined level established by the setting of potentiometer R2. Since the output voltage is lower than normal, the control motor must turn the rotor of the variable-inductor transformer in the direction which will raise the voltage; this is accomplished in the manner described below. The lower-than-normal output voltage of phase 1 causes a decrease in the current through the solenoid coil of voltage-regulating relay K1. The weaker magnetic field resulting from the decreased current exerts a lesser pull on the solenoid core and thereby releases the core from the coil; the additional weight of the core now increases the tension on the compensating spring. When the solenoid core is released sufficiently, its weight causes the normally open contacts on the K1(R) section of the voltage-regulating relay to close. When this occurs, the "raise" (R) coil of motor-control relay K2 energizes and closes the normally open (N.O.) contacts on the K2(R) section of this relay. Closing the K2(R) contacts of the motor-control relay applies a voltage to the control motor, B1, thus energizing the motor and causing it to turn in the "raise" direction. The control motor is mechanically coupled to the rotor of the phase 1 variable-inductor transformer. Therefore, when the motor turns, it also turns the rotor of the variable-inductor transformer in the direction which will cause more flux linkage between the rotor (primary) and the stator (secondary). As a result, there will be more voltage induced in the stator; that is, since the stator, or output, voltage varies with the flux linkage between the rotor and the stator, increasing the flux linkage causes an increase in the output voltage.

The control motor turns the rotor of the variable-inductor transformer until the output voltage again becomes normal. As this point is approached, the current through the solenoid coil of voltage-regulating relay K1 increases, since this current is proportional to the output voltage. Thus, at the predetermined level of output voltage, as sensed by the current through the coil of K1, the stronger magnetic field resulting from the increased current exerts a greater pull on the solenoid core of K1, so that the weight of the core and the tension of the compensating spring are again in balance. When this occurs, the K1(R) contacts of the voltage-regulating relay open, thereby causing the "raise" (R) coil of K2 to de-energize and, in turn, to open the K2(R) contacts of the motor-control relay. Opening the K2(R) contacts of the


motor-control relay removes the energizing voltage from control motor B1, and the motor stops turning. When the motor stops turning, the rotor of the variable-inductor transformer also stops turning, and remains stationary at the normal output-voltage level until a further variation from normal occurs.

As previously explained, the voltage-regulating component of the induction regulator is the variable-inductor transformer, and the voltage-sensing element is the voltage-regulating relay, K1. The setting of voltage-level potentiometer R2, which is in series with the coil of relay K1, determines the desired normal-output-voltage level by establishing the initial magnitude of current to determine the amount of pull on the solenoid core of K1 required to just balance the tension of the compensating spring. Thus, the current through the coil of K1 will remain constant as long as the output voltage is normal; when the output voltage changes (increases or decreases), the magnitude of the current will change proportionally and cause the induction regulator to compensate for the change in voltage. By establishing the magnitude of current through the holding coil of relay K1, the setting of holding-effect potentiometer R3 determines the modified pull of the solenoid core and the length of time that the K1 contacts are held closed. In this manner, the holding coil helps the regulator control circuit to rapidly stop the rotor of the variable-inductor transformer when the output voltage reaches the predetermined normal level. The resistor-capacitor networks, R4-C1 and R5-C2, in the "lower" and "raise" sections, respectively, of motor-control relay K2 are used for arc suppression. Switches S4(L) and S5(R) are limiting switches in the "lower" and "raise" power-input lines to the control motor; these switches cut off power to the control motor and thereby prevent mechanical damage by preventing the motor from exceeding the desired maximum rotation in the respective directions.

Saturable-Core-Reactor Regulator.

An example of a saturable-core-reactor regulator used in the regulation of an ac voltage is illustrated in the accompanying simplified diagram. In this application, the saturable-core reactor is used to regulate the ac voltage applied to an electronic equipment or to the power supply within an equipment. The degree of saturation of the reactor core is controlled by a two-stage dc amplifier, the bias of which is provided by a full-wave rectifier that receives its input voltage

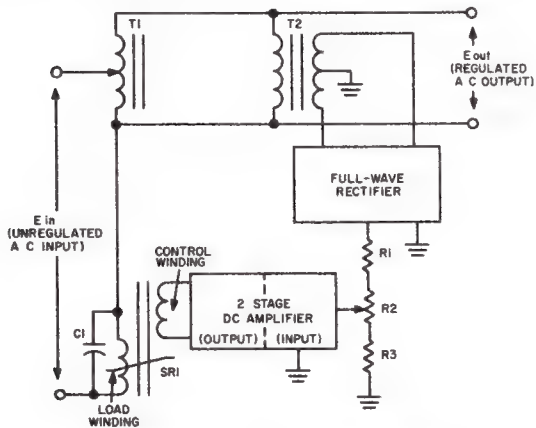from the regulated output. Before the discussion of the saturable-core-reactor regulator is continued, a brief review of the operation of a saturable-core reactor will be presented.



Regulation of AC Voltage with Saturable-Core Reactor

A saturable-core reactor (or simply "saturable reactor") is a device consisting of one or more coils of wire, or windings, placed on an iron core which has special magnetic properties. Thus, a saturable reactor resembles a transformer in that it has windings on an iron core. However, it differs from a transformer in that the reactor operates in the region of core saturation during part of each ac input cycle. The basic operating principle of a saturable reactor is self-induction, or that electromagnetic characteristic whereby a counter electromotive force is produced in a winding by a magnetic field which changes with the changes in current through the winding. The magnetic field concentrates in the iron core, and the flux density in the core varies directly with the current through the winding up to the point of core saturation. That is, when the current in a winding is increased from zero, the magnetic field surrounding each turn of the winding expands and cuts the other turns. As a result, a voltage is induced in the winding; this voltage opposes the applied voltage and tends to keep the current in the wire at a low value. While the current through the winding is less than the saturation current, the opposition (inductive reactance) of the winding is high and permits little current to flow. When the current is increased to the point where the core is saturated, the reactance becomes zero because the rate of change of flux density is zero. Thus, when the core becomes saturated, an increase in current in

the winding will no longer increase the flux density in the core; at this time, since the reactance is zero, only the dc resistance of the wire limits the current through the winding. When the current through the winding is decreased from a maximum value, the magnetic field begins to collapse and cut the turns of the winding. Again a voltage is induced in the coil. This voltage is opposite in direction to that which was induced by the rising current and the expanding magnetic field. Consequently, the voltage induced by the collapsing field tends to keep the current in the wire at a high value, even though it is decreasing toward zero.

A practical saturable reactor is different from an ordinary iron-core coil (just described) in that there are two windings associated with the core, as shown by the SR1 component in the accompanying figure. One of the windings is called the control winding, and the other is called the load winding. The control winding is in the plate circuit of the output stage of the two-stage dc amplifier, and the load winding is in the input circuit of the ac voltage applied from the source. Thus, the variation in impedance of the input circuit, of which the saturable reactor load winding is a part, can be used to regulate voltages in a manner similar to the use of the variable resistance characteristic of an electron tube.

The components in the circuit of the accompanying figure may be grouped into three sections: input, rectification, and sensing-control. The input ac is applied across autotransformer T1, which is in series with the load winding of saturable reactor SR1. Capacitor C1, which is across the load winding, forms a tuned circuit with the load winding. The resonant frequency to which the parallel circuit of capacitor C1 and the load winding is tuned is slightly lower than the input line frequency; that is, it is on the inductive slope of the line frequency impedance curve. This resonant frequency is selected so that the input circuit always appears inductive, even when the input-circuit impedance, which includes autotransformer T1, is shifted to increase or decrease the amount of apparent inductance in the circuit. Therefore, the input line voltage will be divided proportionally between autotransformer T1 and saturable reactor SR1, as determined by their impedance ratio.

The circuit operates in the manner described below. The unregulated ac input voltage, E_{in} , is applied across autotransformer T1 and the load winding of saturable reactor SR1 connected in series. The

autotransformer feeds power transformer T2, which is part of a conventional full-wave rectifier circuit. The dc output of the rectifier is developed across a voltage divider consisting of resistors R1, R2, and R3; the voltage divider provides the bias voltage for the input stage of the two-stage dc amplifier. The bias voltage, as selected by the setting of variable resistor R2, controls the conduction of the dc amplifiers, and thereby controls the resultant current through the control winding of saturable reactor SR1. Adjustment of autotransformer T1 and variable resistor R2, therefore, determines the value at which the ac output voltage, E_{out} , is regulated; any variations from the desired value of output voltage will be automatically compensated for by the action of the regulating circuit.


Assume, first, that there is an increase in the ac output voltage, E_{out} . The increased ac voltage coupled to the secondary of power transformer T2 results in a greater dc voltage across the voltage divider in the output of the rectifier. Thus, a higher positive voltage is sensed at the wiper arm of variable resistor R2, thereby causing a decrease in the bias of the input dc amplifier. This decrease in bias causes an increase in the conduction of the input dc amplifier which, in turn develops a bias on the output dc amplifier and decreases the conduction of the output stage. As a result, the current through the control winding of saturable reactor SR1 is reduced, thereby decreasing the degree of saturation of the reactor core. The saturable reactor now presents a greater impedance to the ac input voltage, thus permitting a greater voltage to be dropped across the reactor, and, consequently, lowering the voltage applied to autotransformer T1. With less voltage coupled from the autotransformer, the output voltage decreases; thus, the ac output voltage is returned to the initially desired value.

Consider, now, the analysis of the circuit operation for the condition of a decrease in the ac output voltage, E_{out} . The decreased ac voltage coupled to the secondary of power transformer T2 results in a lower dc voltage across the voltage divider in the output of the rectifier. Thus, a lower positive voltage is sensed at the wiper arm of variable resistor R2, thereby causing an increase in the bias of the input dc amplifier. This increase in bias causes a decrease in the conduction of the input dc amplifier, which, in turn, decreases the bias on the output dc amplifier and increases the conduction of the output stage. As

a result, the current through the control winding of saturable reactor SR1 is increased, thereby increasing the degree of saturation of the reactor core. The saturable reactor now presents a lower impedance to the ac input voltage, thus permitting less voltage to be dropped across the reactor, and, consequently, raising the voltage applied to autotransformer T1. With a greater voltage coupled from the autotransformer, the output voltage increases; thus, the ac output voltage is returned to the value desired initially.

The circuit will also compensate for variations in the unregulated ac input voltage, E_{in} . For an increase in the input voltage, the circuit operation is the same as previously described for an increase in the output voltage; also, for a decrease in the input voltage, the circuit operation is the same as previously described for a decrease in the output voltage. Although the configuration of the circuitry of the dc amplifiers may vary in the regulator circuit, the purpose of this section is always to sense the variation in the voltage coupled to the rectifier, and then to control the degree of core saturation of the saturable reactor to compensate for the variation in voltage.

With slight modifications the saturable-core reactor regulator circuit just described can be used for regulating the dc voltage output of an equipment's power supply; such a modified circuit is illustrated in the accompanying figure. Note that the full-wave rectifier of the previous circuit is omitted, and the output of the power supply is used in its place to furnish the bias voltage for the input stage dc amplifier. Thus, the dc output voltage of the power supply controls the ac input voltage to the power supply, to provide regulation. Otherwise, the circuit function and operation in all respects are the same as described previously under this heading.

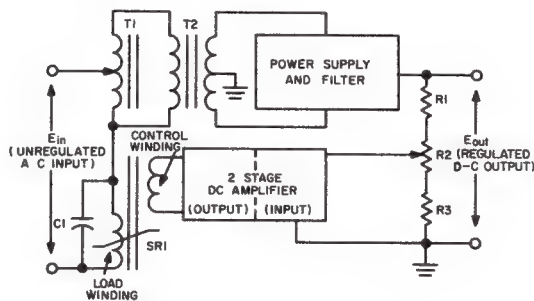

Regulation of DC Voltage with
Saturable-Core Reactor

PART 3-1. ELECTRONIC VOLTAGE REGULATORS

GAS-TUBE REGULATOR

Application.

The gas-tube regulator circuit is used in certain electronic equipment power supply circuits to obtain nearly constant output voltage(s).

Characteristics.

Regulated output voltage to load is nearly constant; voltage drop across regulator tube remains nearly constant for considerable range of tube currents.

Voltage-divider principle employed, using fixed resistance and variable resistance (gaseous regulator tube) in series; regulated load is taken from across regulator tube.


Variation in basic circuit permits positive (plate and screen) or negative (bias) supply voltages to be regulated.

Circuit Analysis.

General. The gas-tube regulator is one of the simplest types of voltage regulators. The regulator circuit consists of a fixed resistor in series with a cold-cathode, gas-filled regulator tube. The regulated output voltage is developed across the regulator tube; therefore, it is across this tube that the load is connected.

The regulator circuit develops a definite output voltage which is dependent upon the type of gas tube used in the circuit, provided that the variation in load current is within the operating range of the tube type employed. Gas tubes are rated according to the voltage appearing across the tube during normal operation and according to the maximum permissible current through the tube. Typical approximate operating voltage ratings for cold-cathode gas-filled tubes are 75, 90, 105, and 150 volts dc; typical maximum current ratings are 30, 40, and 50 milliamperes.

Circuit Operation. In the accompanying circuit schematic, parts A and B illustrate a gas tube used in a basic voltage regulator circuit. Resistor R_s is the series resistor; electron tube V1 is the gas-filled regulator tube. The circuit given in part A provides regulation of a positive input voltage, while the circuit given in part B provides regulation of a negative input voltage. Several regulator tubes may be connected in a series combination, if desired, to obtain a higher regulated output voltage. In the accompanying circuit schematic, parts C and D illustrate two regulator tubes in series. The circuit given in part C provides regulation of a positive input voltage, while the circuit given in part D provides regulation of a negative input voltage. Intermediate regulated voltages can be obtained from the junction of the regulator tubes in the latter two circuits (or from the junction of any series combination of regulator tubes), provided that the current drain of the associated load is kept low.

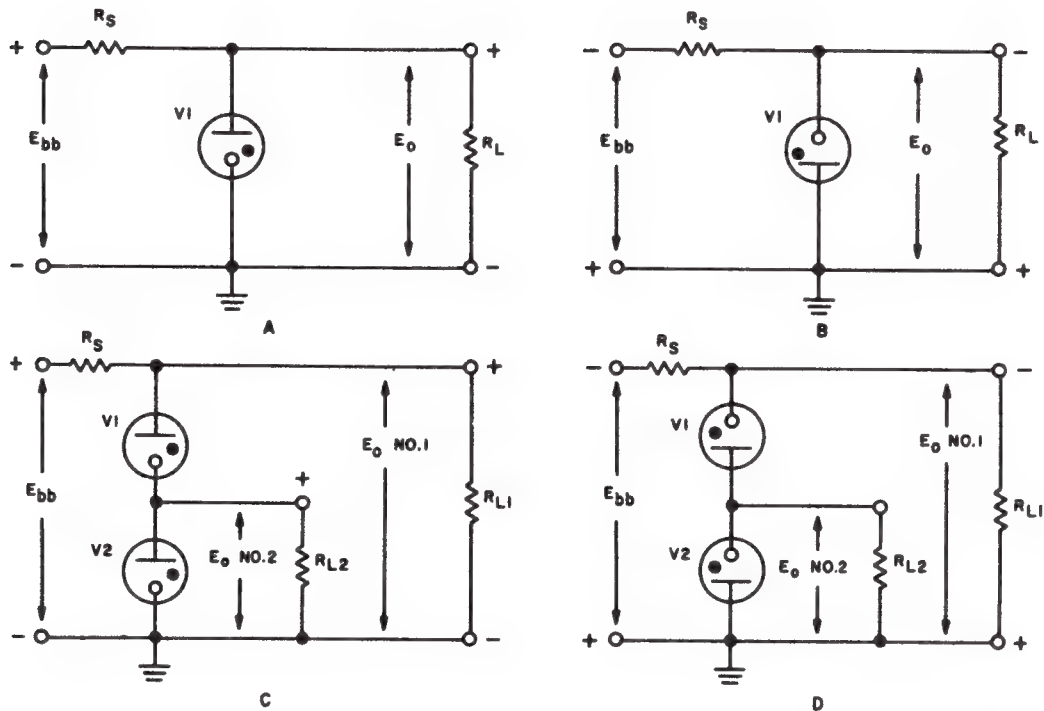

Gas-Tube Regulator Circuits

The cold-cathode gas-filled regulator tube is a two-electrode tube with a cathode and plate. The evacuated tube contains a small amount of gas, such as neon, which is sealed inside the tube. When sufficient voltage is applied to the tube, ionization of the gas molecules occurs and is responsible for the current passing through the tube during operation. If a gas tube is connected directly across a source of voltage which is high enough to ionize the gas, the current will immediately increase to such proportions that the tube may be damaged. The use of a series resistance is essential, therefore, to limit the current through the tube.

There are two separate voltages to be considered in discussing the conditions under which the regulator tube will ionize and operate; these voltages are the breakdown, or firing, voltage and the operating voltage. The breakdown (or firing) voltage is that voltage at which the gas becomes ionized and begins to pass

current. Below this starting voltage the gas will not ionize and current will not pass through the tube. The operating voltage is the voltage at which the tube will remain ionized after having started. There is a considerable difference between the supply voltage and the voltage at which the regulator operates. This difference is compensated for by the series resistor, R_s , which also serves to stabilize the load.

The value of the series resistor depends upon the maximum dc voltage input to the regulator circuit, the regulated dc output voltage, and the combined currents of the regulator tube and the load. The resistor is generally chosen to be of sufficient resistance to limit the current through the regulator tube to a value which is always less than the rated maximum operating current. The current through the regulator tube at the instant of ionization and before the load current has risen to its normal value may initially exceed the maximum value; however, as soon as the load

current rises to its normal value, the regulator tube current drops to a value which is within operating limits because of the series resistance in the circuit.

The ionization of the gas within the tube changes, depending upon the applied voltage; as a result, the internal resistance of the regulator tube changes. When the applied voltage increases, the ionization of the gas increases to lower the tube resistance, and a larger current is passed. Conversely, when the applied voltage decreases, the ionization of the gas decreases to increase the tube resistance, and a smaller current is passed.

From the accompanying circuit schematic, note that the load current and the regulator tube current both pass through the series resistor, R_s . If the dc input voltage to the regulator circuit drops, the voltage across the regulator tube also drops momentarily, at which time the gas within the tube deionizes slightly and less current passes through the regulator tube. Therefore, the current through the series resistor decreases by the amount of the decrease in the regulator tube. Since the current through the series resistor decreases, the voltage drop across this resistor also decreases, and the output voltage delivered to the load increases to return to its original value. In a similar manner, if the input voltage to the regulator circuit increases, the voltage across the regulator circuit increases, the voltage across the regulator also increases momentarily, at which time the gas within the tube is further ionized and more current passes through the regulator tube. Thus, the current through the series resistor is increased. Since the current through the series resistor increases, the voltage drop across the resistor also increases, and the output voltage delivered to the load decreases to return to its original value. When the value of the series resistance is the correct value for the load to be regulated, the output voltage is held nearly constant by the action of the regulator tube. As just described, this action depends upon the fact that changes in the ionization of the gas within the tube varies the amount of current that the tube conducts.

The discussion above assumed that a change occurred in the dc input voltage applied to the regulator circuit. However, the regulator circuit also compensates for changes occurring in the load current. If the load requirement causes the current to increase, the voltage drop across the series resistor, R_s , will

immediately increase. As a result, the voltage across the regulator tube decreases momentarily, at which time the gas within the tube deionizes slightly and less current passes through the regulator tube. Therefore, the current through the series resistor decreases by the amount of the decrease in the regulator tube. Since the current through the series resistor decreases, the voltage drop across the resistor also decreases, and the output voltage delivered to the load increases, returning to its original value. In a similar manner, if the load current should decrease, the voltage drop across the series resistor will immediately decrease. As a result, the voltage across the regulator tube increases momentarily, at which time the gas within the tube is further ionized and more current passes through the regulator tube. Thus, the current through the series resistor is increased. Since the current through the series resistor increases, the voltage drop across the resistor also increases, and the output voltage delivered to the load decreases, returning to its original value. From the discussion given here, it is seen that the output voltage is held nearly constant by action of the regulator tube when changes occur in the load current.

The dc input voltage required to cause ionization of the regulator tube when the circuit is first energized is approximately 30 percent greater than the operating voltage specified for the regulator tube. The output voltage of the regulator circuit quickly drops to the operating value of the regulator tube as soon as the tube ionizes and begins to conduct, causing a voltage drop to appear across the series resistance, R_s . In order to obtain stable operation, the regulator tube must be operated so that it is ionized at all times, and its operating current must fall within specified maximum and minimum current ratings. If, for some reason, the operating current exceeds the specified maximum current rating or if the voltage across the tube is excessive, the tube will become highly ionized, will lose its ability to regulate, and may be permanently damaged. Conversely, if the operating current drops below the specified minimum current rating (approximately 5 milliamperes), the tube will become deionized and will no longer regulate the output. Also, if the voltage across the regulator tube drops below the specified operating voltage to a value which is approximately 70 percent of the breakdown (or firing) voltage, the tube will become deionized.

The value of the series resistor, R_s , can be approximated using the following formula:

$$R_s = \frac{E_{bb} - E_o}{(I_p + I_{load})}$$

where:

E_{bb} = unregulated dc input (supply voltage)

E_o = regulated output voltage (to load)

I_p = regulator-tube current

I_{load} = load current

When operation of the regulator tube is desired at the midpoint of its rated current range, the value of tube current used in the above formula is given as:

$$I_p = \frac{I_{max} + I_{min}}{2}$$

where:

I_{max} = rated maximum tube current

I_{min} = rated minimum tube current

In applications where a regulated voltage greater than the voltage rating of a single regulator tube is required, several regulator tubes may be connected in series to obtain regulation of the desired voltage. Furthermore, if the current drain of the load is kept low, an intermediate regulated voltage can be obtained at the junction of any two regulator tubes of the series. Parts C and D of the accompanying circuit schematic illustrate two regulator tubes connected in series. This circuit configuration permits a lower regulated voltage (E_o No. 2) to be taken from the dc supply. Note that the current through regulator tube V2 and the load current of the lower regulated voltage (E_o No. 2) must pass through regulator tube V1; therefore, the load current of the lower voltage must be relatively small to prevent the combined currents from exceeding the maximum current rating of regulator tube V1.

Failure Analysis.

General. Initially, some indication of the trouble associated with a gas-tube regulator circuit can be obtained by visual inspection to determine the presence of the characteristic glow from the ionized gas within the tube. When current through the tube is near its maximum rating, the tube is highly ionized; when the current is near its minimum rating, the tube is lightly ionized; therefore, the intensity of the gaseous discharge within the tube is an indication of tube conduction. If the tube is not ionized, however, this does not necessarily mean that the tube is defective, since the same indication (lack of characteristic glow) may possibly occur if the series resistor (R_s) increases in

value, if the dc input voltage (E_{bb}) is below normal, or if the load current is excessive. It is therefore necessary to make dc voltage measurements at the input and output terminals of the voltage regulator circuit to determine whether the fault lies within the regulator circuit or whether it is external to the regulator circuit.

The value of the series resistor, R_s , can be checked by ohmmeter measurements to determine whether any change in resistance has occurred. If the maximum current rating of the regulator tube is exceeded for a considerable length of time, the tube may be damaged and lose its regulation characteristics; therefore, the regulator tube itself can be suspected as a possible source of trouble. Furthermore, a regulator tube which is subjected to a very strong r-f field may be unable to regulate while the field is present, because the r-f field may ionize the gas within the tube independent of the normal dc conduction current.

BREAKDOWN DIODE SHUNT-TYPE REGULATOR

Application.

The breakdown-diode shunt-type regulator is similar in operation to gas-tube regulators previously discussed in this section. It is used as a voltage regulator where the load is relatively constant. This circuit is frequently used in more complex regulator circuits as a reference-voltage source and as a preregulator in transistorized series-type regulators.

Characteristics.

Uses a breakdown, or Zener, diode as shunt regulating device.

Regulated output voltage to load is nearly constant, even though changes in input voltage or changes in load current occur.

Voltage-divider principle employed, using fixed resistance and breakdown diode in series; regulated load is taken from across diode.

Variation in basic circuit permits positive or negative voltages to be regulated.


Circuit Analysis.

General. The breakdown-diode regulator is the simplest form of shunt-type regulator. The regulator circuit consists of a fixed resistor in series with a breakdown, or Zener, diode. The regulated output voltage is developed across the diode; therefore, the

load is connected across the diode. The regulator circuit develops a definite output voltage which is dependent upon the characteristics of the particular breakdown diode; breakdown diodes are presently available with voltage ratings between 2 and 20 volts, in 5-, 10-, and 20-percent tolerances, and with power dissipation ratings as high as 50 watts.

The breakdown, or Zener, diode is a PN junction which has been modified during its manufacture to produce a specific breakdown voltage level; it operates with a relatively close voltage tolerance over a considerable range of reverse current. The breakdown diode is subject to a variation in resistance with a change in temperature of the diode; a circuit which compensates for this change in resistance is discussed later. The basic theory for the breakdown diode is discussed in the Introduction Section of Power Supplies in this handbook.

Circuit Operation. In the accompanying circuit schematics, parts A and B illustrate a breakdown diode used in a basic voltage-regulator circuit. The two parts are identical in configuration to the electron-tube, gaseous-type voltage regulators discussed earlier in this section of the handbook. Resistor R_1 is the series resistor; semiconductor CR1 is a breakdown, or Zener, diode. The circuit in part A provides regulation of a positive input voltage, while the circuit in part B provides regulation of a negative input voltage.

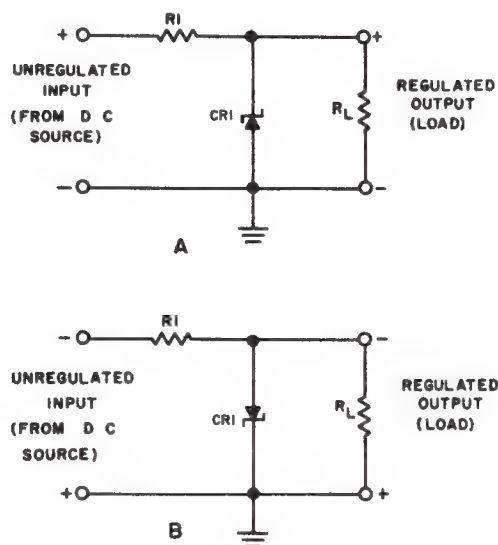

Simple Breakdown-Diode Regulator Circuit


The design of the breakdown-diode regulator differs from that of the gas-tube regulator circuit in that no "firing", or "ionizing", potential must be considered when the value of the series resistance is determined. It is likely that both the input voltage and the load current for the regulator will be subject to variation; therefore, the breakdown-diode regulator is designed to operate within the extremes to be encountered. The series resistor, R_1 , needs only to stabilize the load; it compensates for any difference between the diode operating voltage and the unregulated input voltage. The value of the series resistor depends upon the combined currents of the breakdown diode and the load. The series resistor is generally chosen with the following factors in mind: the minimum value of input voltage (unregulated), the maximum value of load current, the minimum value of breakdown-diode current, and, knowing the diode characteristics, the value of the highest voltage to be developed across the breakdown diode and its parallel load resistance. Once the value of series resistor R_1 is determined, the maximum power dissipation in the diode can be arrived at by considering the maximum value of input voltage (unregulated), the minimum value of load current, and the minimum value of voltage developed across the diode (using the value of series resistance established for R_1). In order to obtain stable operation, the breakdown diode must be operated so that its reverse current falls within its minimum and maximum ratings for the specified voltage. It is important to note that under no-load conditions, the breakdown diode must dissipate the full output power; therefore, this regulator circuit is never used in applications where a no-load condition is likely to exist. Instead, the breakdown-diode regulator is most often used in applications where the output voltage is fixed and the load current is relatively constant.

If the input voltage to the regulator circuit decreases, the voltage decrease appears across the breakdown diode, CR1, and immediately the current through the diode decreases; thus, the total current through series resistor R_1 decreases, and the voltage drop across R_1 decreases proportionately, so that for all practical purposes the output voltage across the load resistance (and breakdown diode) remains the same. Conversely, if the input voltage to the regulator circuit increases, the voltage increase appears across the breakdown diode, and immediately the current through the diode increases; thus, the total current

through series resistor R1 increases, and the voltage drop across R1 increases proportionately, so that for all practical purposes the output voltage across the load resistance (and diode) remains the same.

If the current drawn by the load resistance decreases, the total current drawn from the input source does not change; instead, a corresponding increase in current through the breakdown diode occurs and the current drawn from the source remains constant, so that the output voltage across the load resistance (and diode) remains constant. Conversely, if the current drawn by the load resistance increases, the total current drawn from the input source does not change; instead, a corresponding decrease in current through the breakdown diode occurs and the current drawn from the source remains constant, so that the voltage across the load resistance (and diode) remains constant.

Environmental temperature extremes, as well as junction temperature changes, may result in variations of the internal impedance of the breakdown diode, which, in turn, results in changes of the output voltage. Thus, in practical circuits, provisions must be made to compensate for any variation of the impedance of the breakdown diode. The temperature coefficient of resistance of the breakdown diode is normally several times larger than the negative temperature coefficient of resistance of either the forward-biased or reverse-biased junction diode. To obtain a zero coefficient of resistance over a wide range of temperatures, one commonly used method of temperature compensation uses negative-temperature devices, such as forward-biased diodes or thermistors, in series with the breakdown diode. This method is illustrated in the accompanying diagram.

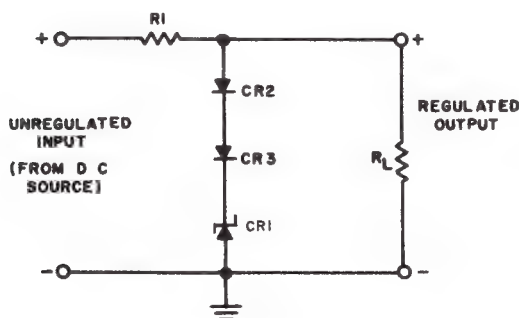

Temperature-Compensated Voltage-Regulator Circuits

The negative temperature coefficient of resistance of diodes CR2 and CR3 in series equals the positive temperature coefficient of resistance of the breakdown diode, CR1. By using forward biasing for diodes CR2 and CR3, the voltage drop across them will be kept to a minimum and, consequently, will have negligible effect on the value of the output voltage.

When the voltage-regulator circuit is temperature-compensated as described above, the total resistance of CR1, CR2, and CR3, in series, remains constant over a wide range of temperatures; the end result is a constant voltage output, even though temperature, applied input voltage, or load current may change during operation.

Silicon breakdown diodes are generally used as the reference-voltage source in the more complex transistorized regulators because the breakdown voltage of a silicon breakdown diode is relatively constant over a wide range of reverse current.

Failure Analysis.

General. The shunt-type voltage-regulator circuit should never be operated without a load, since the no-load condition causes the breakdown diode to conduct heavily and it must dissipate power which is normally dissipated by the load resistance. In this case, if the maximum power dissipation or maximum reverse current rating of the breakdown diode is exceeded for any length of time, the diode may be damaged; thus, breakdown diode CR1 may be suspected as a possible source of trouble. Therefore, the load circuit should be carefully checked to determine that a load is presented to the regulator circuit at all times. It is also necessary to make dc voltage measurements at the input terminals of the regulator circuit to determine whether voltage is applied and whether it is within tolerance.

The operation of the shunt-type regulator is based upon the voltage-divider principle; therefore, voltage measurements made across the output terminals of the regulator circuit and across series resistor R1 (observing correct voltmeter polarity) are necessary to determine whether the output voltage is within tolerance and whether the drop across series resistor R1 is excessive. If the load is shorted, there will be no output from the regulator circuit, and the full output voltage will be measured across series resistor R1. Also, if series resistor R1 should become open, there

will be no output from the circuit, and the full output voltage will be measured across the resistor. The value of series resistor R1 can be checked by ohmmeter measurement to determine whether any change in resistance has occurred; disconnect one terminal of R1 from the circuit when making the measurement.

If breakdown diode CR1, or diode CR2 or CR3, should become open, the output voltage will be higher than normal; if breakdown diode CR1 should fail and become shorted, the voltage will be lower than normal, and diodes CR2 and CR3 will become overloaded. If diodes CR2 and CR3 should fail and become shorted, the output voltage will be subject to changes with temperature variations, since the temperature coefficient of resistance for the series diode combination will be changed. In general, if the output voltage is above normal, this is an indication that either an open circuit or an increase in impedance has occurred in the shunt elements (CR1, CR2, and CR3) or in the load of the regulator circuit. If the output voltage is below normal, this indicates that either series resistor R1 has increased in value, the input voltage is below normal, or the load current is excessive because of a decrease in load resistance (excessive leakage or shorted components in the load circuit).

SHUNT TRANSISTOR REGULATOR

Application.

The shunt transistor regulator is used as a voltage regulator in electronic equipment where the load is fairly constant and relatively light, and where it cannot be adequately handled by a simple breakdown diode regulator.

Characteristics.

Capable of handling a larger load than the diode regulator.

Is smaller, weighs less, and provides better reliability and performance than the electron tube regulator.

Efficiency is relatively low, because it uses a series-dropping resistor which dissipates considerable power.


Requires a reference voltage source for control purposes.

Transistor cannot be damaged by an external overload or short circuit.

Circuit Analysis.

General. The shunt transistor regulator uses a series voltage-dropping resistor, whose voltage drop is controlled by the current drawn by a transistor connected across the output, to provide the desired change in output voltage. It is necessary that the series resistor be capable of carrying the load current and maximum transistor current; the transistor must be rated to handle the highest output voltage developed, since it is connected across the line. A source of reference voltage is required to bias the transistor. In addition, at no load, the transistor must be able to dissipate the full-load current. Under conditions of extreme load variation, the shunt regulator may be stabilized by adding a control amplifier stage. The shunt regulator is used to best advantage for fixed-load, fixed-voltage applications.

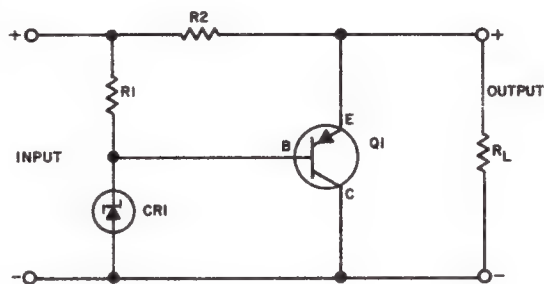Circuit Operation. The schematic diagram of a typical basic shunt transistor voltage regulator is shown in the accompanying illustration.



Shunt Transistor Regulator

Resistor R1 and Zener diode CR1 form a voltage divider across the supply which furnishes a fixed reference voltage across CR1. This is applied to the base of transistor Q1, biasing it at about midcurrent operating range. Meanwhile, the supply voltage is kept from dropping to the breakdown voltage of CR1 by resistor R1. Resistor R2 is the series voltage-dropping resistor through which the load voltage is regulated by the current drawn through shunt resistor Q1. The load resistance is represented by R_L .

With a fixed load and normal voltage applied, breakdown diode CR1 holds the base bias of Q1 at a fixed value. Hence, transistor Q1 draws a fixed value of current from the line. The sum of the transistor

current and the load current is such that the desired voltage drop is produced across R2. This voltage drop is the difference between the supply and the desired line voltage. With no change in load or transistor current drain, the difference voltage remains the same, and the line voltage remains constant. Assume for the instant that the load decreases slightly, reducing the difference voltage dropped across R2 and thereby increasing the line output voltage. This places a higher positive potential on the emitter of Q1, and, since the base is fixed by CR1, causes an increase of collector current through the transistor. The increase in collector current flowing through dropping resistor R2 produces a higher difference voltage and reduces the line output voltage back to normal.

When the load current increases again to the original value, a higher difference voltage is produced by the increased voltage drop across R2, and the line voltage is reduced below normal. The emitter-to-base voltage is now reduced below normal so that less forward bias is applied, and less collector current flows. The reduced voltage drop across R2, produced by the reduction of transistor current flow, reduces the difference voltage and the output line voltage increases back to normal value. To produce effective regulation, the change in transistor current must equal the change in load current. For large load changes power transistors are required.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low-voltage ranges of conventional voltohmmeters. Be careful also to observe the proper polarity when checking continuity, since a forward bias through any of the transistor junctions will cause a false low resistance reading.

No Output. If the load is short-circuited, Q1 is defective, or if R2 is open, no output voltage will be obtained. Check the input voltage. If the input voltage is normal, and there is no output voltage, measure the voltage drop across R2. If the output is shorted, full voltage will be indicated across R2 and the output will measure zero resistance with the power removed. Check the forward and reverse resistance of Q1. The reverse resistance should be high and the forward resistance low; if shorted, Q1 will indicate a low resistance in both directions.

High Output Voltage. If R1 is open or CR1 is defective, no reference voltage will be observed be-

tween base and collector, transistor Q1 will be inoperative, and a higher than normal voltage will be obtained (with normal load). Make certain also that the resistance of R2 is not lowered by checking for proper value with an ohmmeter with the power off. It is also possible that Q1 is inoperative.

Low Output Voltage. If the resistance of R2 increases, a lower than normal output will be obtained. Check R2 for proper value. If diode CR1 is defective or if R1 changes value, improper biasing of the Q1 base may cause higher than normal transistor current flow and create a continuous low output. Check R1 for proper value. There is also a possibility that transistor Q1 may be defective and drawing a heavier than normal current.

Erratic Operation. In the event that the output voltage appears occasionally to vary below normal and does not become higher than normal, check the voltage across R2, since the range of the regulator may be exceeded on heavy loads.

SERIES TRANSISTOR REGULATOR

Application.

The series transistor regulator is used as a voltage regulator in electronic equipment where small-load variations permit the increased efficiency of this circuit to be used advantageously.

Characteristics.

Is smaller, weighs less, and provides better reliability and performance than the electron tube regulator.

Efficiency is higher than the shunt-type regulator. Requires a reference voltage source for control purposes.

Transistor must be capable of carrying the full-load current.


Transistor is subject to damage from a heavy overload or short circuit, except where protective provisions are included in the circuit.

Circuit Analysis.

General. The series transistor voltage regulator uses a transistor connected in series with the load and voltage supply to act as a variable voltage-dropping resistor. The effective resistance of the transistor is controlled with respect to a reference voltage. When the regulated output voltage tends to change, a correction voltage biases the transistor in the opposite direction.

Thus, as the output voltage tends to rise, conduction through the transistor is reduced and the internal effective resistance tends to increase, automatically dropping the output voltage back to its original value. When the output voltage falls, conduction is increased, effectively reducing the transistor resistance and automatically increasing the output voltage back to normal. This action may be controlled by amplifiers to extend the range where large voltage swings are encountered, or to increase the sensitivity where only small ripple voltages are encountered, as desired.

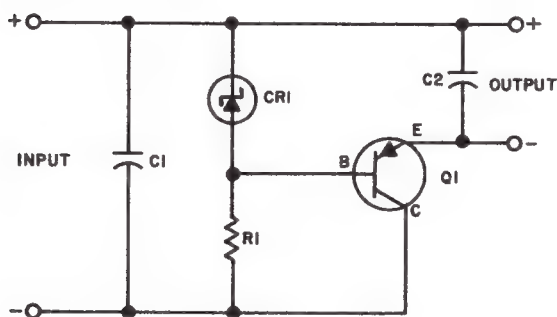Circuit Operation. The schematic diagram of a basic series voltage regulator is shown in the accompanying illustration.



Series Transistor Regulator

Capacitors C1 and C2 are conventional filter capacitors connected at the input and output, respectively. They tend to stabilize any small voltage variations and to eliminate any excess ripple present from the power supply. Breakdown diode CR1 and resistor R1 form a voltage divider across the supply, and are used to supply a constant base bias to regulator transistor Q1. Transistor Q1 is connected in series with the negative supply lead and operates as a voltage-dropping resistor.

Under normal operating conditions, the base-to-emitter bias is determined by breakdown diode CR1 and resistor R1 which form a voltage divider across the supply voltage. The base bias is fixed at a value which will produce the desired output voltage with a normal load. If the load is reduced, the output voltage will tend to rise. Since the base voltage is fixed by breakdown diode CR1, the emitter voltage will become more negative and reduce the effective base-emitter bias, causing the forward collector current to

decrease. A decrease in collector current will increase the effective internal resistance of the transistor. Since the entire load current flows through the transistor, the voltage drop across Q1 will increase and reduce the output voltage back toward its original value.

Conversely, when the external load increases, the voltage across the load tends to drop. Thus, the emitter of Q1 will become less negative and the base-emitter forward bias will be increased, causing a heavier flow of forward current through Q1. The increased current flow through transistor Q1 will effectively reduce the internal resistance of the transistor. Therefore, the load current flowing through the transistor will produce a smaller voltage drop across Q1, and the output voltage will increase toward the supply voltage, returning the output voltage back to normal.

When the load current is too large for a single transistor, it is possible to parallel similar transistors to obtain sufficient current-carrying capacity. In some instances, because of production differences causing different characteristics, it may be necessary to compensate for the difference between high and low tolerance units by inserting small emitter resistors in the off-tolerance units. The object is to divide the current equally, so that each transistor carries an equal portion of the load, or to use matched pairs of transistors. Operation basically remains the same, with the current varying equally between transistors.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low-voltage ranges of conventional ohmmeters. Be careful also to observe the proper polarity when checking continuity since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. If capacitors C1 or C2 are shorted, or if breakdown diode CR1 or transistor Q1 is open, there will be no output. Measure the input and output voltages. If there is no output voltage, check for a blown line fuse, and check capacitor C1 for a short. If input voltage exists but there is no output voltage, check capacitor C2 for a short. If C2 is satisfactory, measure the voltage across breakdown diode CR1. If the proper breakdown voltage is not obtained, check R1 for value and check breakdown diode CR1. If the

proper breakdown voltage exists, and still no output is obtained, transistor Q1 may be at fault.

Low Output Voltage. If the line voltage is low, capacitors C1 and C2 are leaky; if improper bias exists, or if Q1 is defective, a constant low output voltage can be obtained. Check the line voltage, and check C1 and C2 for leakage and value. Check the base bias, and if normal, but the output voltage still remains low, transistor Q1 is probably defective. If the base bias is lower than normal, R1 may have changed in value, or breakdown diode CR1 may have changed its characteristics.

High Output Voltage. If the output voltage is constantly higher than normal, transistor Q1 is probably conducting heavier than normal because of a short, or because of high forward bias. Check diode CR1 and check the value of R1. If both parts are satisfactory, Q1 may be defective.

DC REGULATOR USING PENTODE AMPLIFIER

Application.

The dc regulator with series tube, pentode amplifier, and gas tube voltage reference is used in certain electronic equipment power supply circuits to obtain nearly constant output voltage(s).

Characteristics.

Regulated output voltage to load is nearly constant, even though changes in input voltage or changes in load current occur.

Voltage-divider principle employed, using variable resistance (electron tube) in series with load resistance; series electron tube may be a triode, a triode-connected pentode or a pentode with separate screen-voltage supply.

Uses pentode amplifier circuit to control series electron tube.

Uses gas gas-tube regulator circuit as reference-voltage source.

Variation in basic circuit permits positive (plate and screen) or negative (bias) supply voltages to be regulated.


Circuit Analysis.

General. The dc regulator with triode series tube, single-pentode amplifier, and gas-tube voltage reference is capable of providing very stable output-voltage regulation. The high amplification obtained from the pentode amplifier stage enables the circuit to have good sensitivity to small output-voltage variations. In this type of voltage regulator, regulation

is accomplished by allowing the cathode-to-plate resistance of an electron tube, in series with the output of a power supply, to function as a variable resistance, and thus provide the voltage drop necessary to compensate for any change in output voltage. Voltage regulation which is better than 1 percent can be obtained with this type of regulator, depending upon circuit design.

Typical regulated output voltages obtained with this regulator circuit are 150, 250, and 300 volts, dc.

Circuit Operation. A typical voltage regulator circuit using a pentode amplifier and gas-tube voltage reference is illustrated in the accompanying circuit schematic. Electron tube V1 is a twin triode used as the series regulator tube; V2 is a pentode used as a dc amplifier; V3 is a cold-cathode, gas-filled regulator tube used to provide a reference voltage for operation of the regulator-amplifier circuit. Resistors R1 are voltage-dropping resistors connected in series with regulator tube V3 across the input circuit. In addition, they function as a voltage divider to provide dc potential for the screen grid of V2. C1, connected in parallel with regulator tube V3, is a bypass capacitor which provides a low-impedance path at the power supply ripple frequency (usually 120 Hz) to reduce the possibility of degeneration in the cathode circuit of V2.

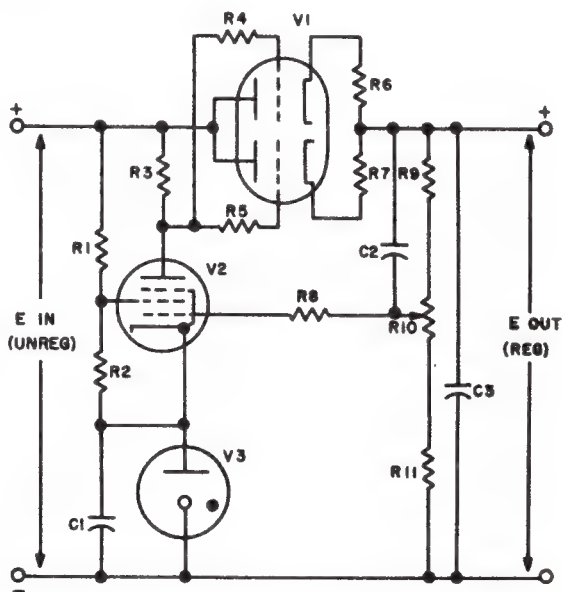

Typical Voltage Regulator Circuit Using Pentode Amplifier and Gas-Tube Voltage Reference

The value of capacitor C1 is usually a compromise between a value which offers low impedance to the power supply ripple frequency (usually 120 Hz) and a value which is not so large as to affect normal operation of the regulator tube, V3. Capacitor C2 couples the full value of ripple voltage from the output of the regulator circuit; if C2 were not used, only a portion of the ripple voltage would be applied to the grid of V2, as determined by the voltage-divider action of R9, R10, and R11. The value of this capacitor is chosen to be just large enough to provide satisfactory ripple suppression. If the value of C2 is made too large, the response time of the regulator circuit to normal dc output-voltage variations will be affected; a value of from 0.01 to 0.1 μf is typical in most regular-amplifier circuits. Capacitor C3 is connected across the output terminals to lower the output impedance of the regulator circuit; the value of this capacitor depends upon circuit design, but is usually 2 μf or larger. Resistor R3 is the plate-load resistor for the pentode amplifier, V2. Resistors R4 and R5, in the grid circuits of V1, are parasitic oscillation suppressors; they are of equal value, generally between 270 and 1000 ohms. Resistors R6 and R7, in the cathode circuits of V1, are included for the purpose of equalizing the current flow in the parallel triode sections; these equalizing resistors are of equal value, generally between 10 and 47 ohms, depending upon circuit design. Resistor R8, in the control-grid circuit of V2, is a parasitic oscillation suppressor. Resistors R9, R10, and R11 form a voltage divider across the output of the regulator circuit, and are in parallel with the resistance of the load; resistor R10 is adjustable, and is used to set the output voltage to the desired value the circuit is to maintain.

Electron tubes V1 and V2 are indirectly heated, cathode-type tubes; V1 normally has a high heater-to-cathode voltage rating, while V2 has a heater-to-cathode voltage rating which is typical for receiving-type tubes. Because of the heater-to-cathode breakdown voltage limitations imposed by the tubes themselves, it is usually necessary to isolate the filament circuits from each other and to supply the filament (heater) voltages from independent sources.

When the unregulated voltage, E_{in} is first applied to the input of the regulator circuit, voltage is applied to regulator tube V3 through resistors R1 and R2, in series; V3 ionizes and begins to conduct, thus establishing a reference voltage at the cathode of V2. The action which occurs is the same as that previously

described under *Gas-Tube Regulator Circuit*, in this section of the handbook. The voltage divider formed by resistors R1 and R2 establishes the voltage applied to the screen grid of V2. Regardless of the value of dc voltage applied to the input of the regulator circuit, the voltage at the cathode of V2 will be held constant by the action of V3 for use as a reference voltage; however, the voltage at the screen grid of V2 is subject to change if the input voltage changes. This screen-circuit configuration increases the gain of the amplifier stage and also the regulator-amplifier sensitivity to either input or output voltage changes.

As previously mentioned, this regulator circuit is based upon the voltage-driver principle of using a variable resistance in the form of electron tube V1 in series with the load resistance. The regulated output voltage, E_{out} , appears across the voltage divider formed by series resistors R9, R10, and R11, which are connected across the output of the regulator circuit and in parallel with the load. The total resistance of these series in parallel with the load resistance constitutes one part of the resistance in the series voltage-divider arrangement, the other part being the variable cathode-to-plate resistance of V1. When the cathode-to-plate resistance of V1 is controlled to vary the voltage drop across V1, the output voltage developed across the load can be regulated and maintained at a constant value.

The voltage appearing at the plate of V2 is dropped from the input to the regulator circuit through plate-load resistor R3 and is applied to the control grids of V1. The amount of current through R3 and the resulting value of voltage at the plate of V2 are control grid of V2. The voltage applied to the grid of V2 is obtained from the voltage divider circuit composed of R9, R10, and R11; the exact value of voltage applied to the grid of V2 is determined by the setting of R10. Since the potential at the cathode of V2 is maintained at a constant positive value by the action of regulator tube V3, adjustable resistor R10 is set to the point where the bias applied to the grid of V2 permits a predetermined value of current to be drawn by V2. When V2 is conducting, the voltage drop through plate-load resistor R3 develops a voltage at the grid of V1 which is less than either the plate or cathode voltage of V1; the difference in voltage between the cathode of V1 and the plate of V2 is the operating bias for V1. Thus, the setting of resistor R10 determines the current through V2, establishes the bias for V1, and initially determines the effective

internal resistance of V1 to obtain the desired output voltage from the regulator circuit.

Assume that the regulated output voltage, E_{out} , attempts to increase, either because of an increase in the input voltage to the regulator circuit or because of a decrease in the load requirement. Through the voltage-divider action of resistors R9, R10, and R11, a slightly higher positive voltage now appears across R10 and R11. This results in an increase in the positive voltage applied to the grid of V2 and a corresponding decrease in the bias voltage between the cathode and grid. (The cathode voltage of V2 remains constant because of the action of regulator tube V3.) As a result of the decreased bias, V2 now conducts more current, and this additional current flow through plate-load resistor R3 results in a greater voltage drop across R3; thus, the voltage at the plate of V2 decreases and causes the difference in voltage between the cathode of V1 and the plate of V2 to increase. This difference in voltage between the cathode of V1 and the plate of V2 is the operating bias for V1; thus, as a result of this voltage increase, the effective internal resistance of V1 increases. When the internal resistance of V1 increases, less load current flows through V1, the voltage drop across V1 increases, and the output voltage of the regulator circuit decreases to its original value.

An action similar to that just described occurs when the regulated output voltage, E_{out} , attempts to decrease. Through the voltage-divider action of resistors R9, R10, and R11, the bias voltage between the cathode and grid of V2 is increased, since a slightly low positive potential now exists across R10 and R11. As a result of the increased bias, V2 now conducts less current, and this decreased current flow through plate-load resistor R3 causes a smaller voltage drop to occur across R3; thus, the voltage at the plate of V2 increases and causes the difference in voltage between the cathode of V1 and the plate of V2 to decrease. The difference in voltage between the cathode of V1 and the plate of V2 is the operating bias for V1; thus, as a result of this voltage decrease, the effective internal resistance of V1 decreases. When the internal resistance of V1 decreases, more load current flows through V1, the voltage drop across V1 decreases, and the output voltage of the regulator circuit increases to its original value.

The actions described in the preceding paragraphs are practically instantaneous; consequently, the output voltage (E_{out}) remains practically constant.


Since all of the load current must pass through the series regulator tube, V1, the tube(s) must be capable of passing considerable current. In some circuit applications where the load current requirements exceed the capabilities of a single tube, two or more identical tubes are connected in parallel (as the sections of twin-triode V1 have been paralleled) in order to obtain suitable regulation characteristics and current-handling capability.

The output of the regulator circuit is coupled to the grid of the pentode amplifier tube, V2, through coupling capacitor C2. Any ripple component present in the output voltage is amplified by V2, and, since the circuit is basically a negative feedback circuit, the ripple component is suppressed. Also, since the screen-grid voltage for V2 is obtained from the unregulated input voltage to the regulator circuit, the sensitivity of the amplifier to voltage changes is increased. As a result, the regulator circuit is sensitive to any voltage changes and is very effective in removing any fundamental ripple-frequency component which is present in the unregulated voltage supplied to the input of the regulator circuit.

As previously mentioned in this section, there are several circuit variations possible for the series regulator tube, V1. These variations in the series regulator circuit include the use of a triode (a twin-triode is shown in the schematic), a triode-connected pentode, and a pentode with separate screen-voltage supply.

Also, there are several variations in the regulator-amplifier circuit which are commonly employed in electronic regulators (see illustrations below). For example, the screen-grid voltage for V2 may be obtained through a separate screen dropping resistor from the cathode circuit of V1, or from a tap placed on the bleeder resistance formed by resistors R9, R10, and R11; this is shown in part A of the accompanying illustration. In some cases the screen voltage is obtained from a separate regulated-voltage source. Another circuit variation, shown in part B of the illustration, is connection of the plate-load resistor, R3, to the cathode circuit of V1 instead of to the plate circuit as shown in part A; in this case, the voltage drop developed across plate-load resistor R3 is the bias voltage for V1. Still another circuit variation is obtaining the voltage for operation of regulator tube V3 through a separate series resistor connected to the cathode circuit of V1. An alternative method of obtaining the reference voltage (See part C) is to ground

the cathode of V2 and connect resistor R11 of the voltage divider (R9, R10, and R11) to a regulated negative-voltage source. Although there are many minor variations in the regulator-amplifier circuit configuration, the function of the regulator circuit remains the same, that is, to supply a regulated output voltage to the load which is independent of variations in input voltage or changes in load current.

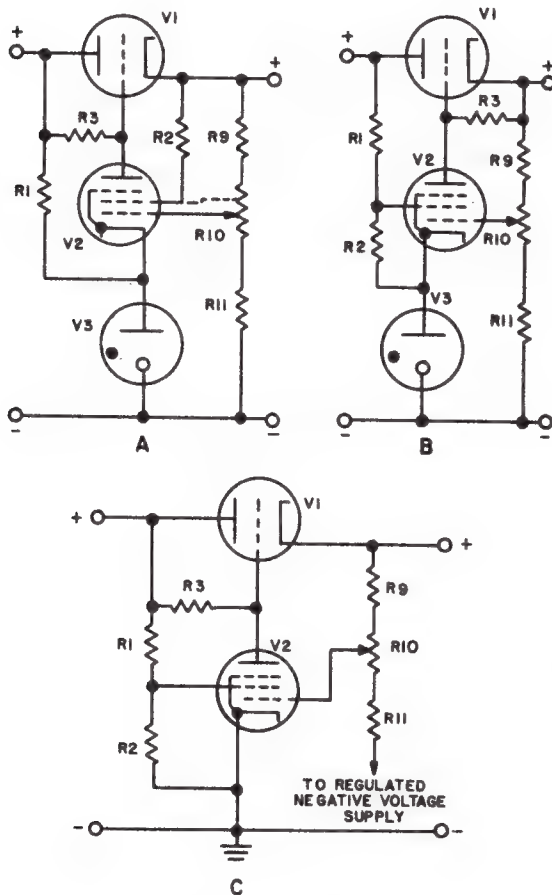

Typical Regulator-Amplifier Circuits
(Showing Variations)

Failure Analysis.

General. The voltage-regulator circuit includes several parts which are rather critical and directly affect operation of the regulator circuit. For this reason, resistors R9, R10, and R11, and perhaps resistors R1 and R2, are normally close-tolerance resistors

with good temperature stability characteristics. If for any reason these particular resistors should change in value, the operation of the circuit will be impaired.

Since the regulator circuit attempts to hold the output voltage constant, it is usually good practice to determine whether the load current is within tolerance between suspecting trouble within the regulator circuit. A load-current measurement may be made by inserting a milliammeter (having a suitable range) in series with the output of the regulator circuit. Also, a voltage measurement should be made at the input to the regulator circuit to determine whether the unregulated voltage output from the power supply (and filter circuit) is within tolerance.

No Output. In the voltage-regulator circuit using a pentode amplifier, the no-output condition is likely to be limited to one of the following possible causes: the lack of filament voltage applied to series regulator tube V1, the lack of applied dc voltage (from the associated power supply and filter circuit), or a shorted load circuit (including output capacitor C3).

A visual check of the glass-envelope series-regulator tube, V1, should be made to determine whether the filament(s) is lit; if the filament is not lit, it may be open or the filament voltage may not be applied. The tube filament should be checked for continuity; also, the presence of voltage at the tube socket should be determined by measurement.

The dc voltage applied to the regulator circuit should be measured at the input (plate of V1) to determine whether it is present and of the correct value, since the lack of input voltage from the associated power supply and filter circuit causes a lack of output voltage.

With the dc voltage removed from the input to the circuit, resistance measurements can be made across the load (resistors R9, R10, and R11) to determine whether the load circuit, including capacitor C3, is shorted. (The resistance measured across the load circuit will normally measure something less than the total value of series resistors R9, R10, and R11, depending upon the load circuit design.)

High Output. The high-output condition is usually caused by a decrease in operating bias for the series regulator tube, V1, which, in turn, causes the tube to decrease its internal resistance and permits the regulator output voltage to rise above normal; therefore, any defects in the regulator-amplifier circuit which can cause a decrease in the operating bias for V1 are to be suspected. Voltage measurements should be

made at the socket of V1 to determine whether bias (cathode-to-grid) is present.

A visual check of the gas-filled regulator tube, V3, which provides a reference voltage for operation of the regulator-amplifier circuit, should be made to determine whether the tube is conducting. A voltage measurement made between the plate and cathode of V3 will determine whether sufficient voltage is present at the tube to cause conduction. If the voltage is above normal, the tube may be defective. If the voltage measure across V3 is below normal, it is likely that resistor R1 or R2 is open or possibly the dc amplifier tube, V2, is not conducting.

A visual check of amplifier tube V2 should be made to determine whether the filament is lit; if the filament is not lit, it may be open or the filament voltage may not be applied. The tube filament should be checked for continuity; also, the presence of voltage at the tube socket should be determined by measurement. The grid voltage applied to V2 should be measured to determine whether the tube is improperly biased and causing the operating bias on V1 to decrease. Assuming that V3 is conducting normally to provide a reference voltage, if the voltage at the grid of V2 is below normal, it is possible that resistors R9 and R11 have changed in value or that resistor R10 is not set properly; however, if no voltage is present at the grid of V2, the tube will be biased to cutoff and V1 will conduct heavily as a result of decreased operating bias. In this case, it is likely that either resistor R9 or a portion of R10 (connected to R9) is open. If amplifier tube V2 has low emission, the voltage drop across plate-load resistor R3 will be below normal.

Low Output. The low-output condition is usually caused by an increase in operating bias for the series regulator tube, V1, which, in turn, causes the tube to increase its internal resistance and permits the regulator output voltage to fall below normal; therefore, any defects in the regulator-amplifier circuit which can cause an increase in the operating bias for V1 are to be suspected.

In the twin-triode series regulator tube, trouble in one section (such as low cathode emission or an open tube element) will cause a reduction in output. Voltage measurements should be made at the socket of V1 to determine whether the bias (cathode-to-grid) is excessive. The equalizing resistors, R6 and R7, in the cathode circuits of V1 should be measured to determine that neither one is open, that they have not

increased in value, and that they are of equal resistance.

A visual check of the gas-filled regulator tube, V3, which provide a reference voltage for operation of the regulator-amplifier circuit, should be made to determine that the tube is conducting. A voltage measurement made between the plate and cathode of V3 will determine whether sufficient voltage is present at the tube to cause conduction. If the voltage measured across V3 is below normal, or if no voltage is present, it is likely that capacitor C1 is either leaky or shorted.

The grid voltage applied to V2 should be measured to determine whether the tube is improperly biased, thus causing the operating bias on V1 to increase. Assuming that V3 is conducting normally to provide a reference voltage, if the voltage at the grid of V2 is above normal, it is possible that resistors R9 and R11 have changed in value or that resistor R10 is not set properly; however, if a high voltage is present at the grid of V2, the tube will conduct heavily and V1 will conduct less as a result of an increase in operating bias. In this case, it is likely that coupling capacitor C2 is either leaky or shorted, or that either resistor R11 or a portion of R10 (connected to R11) is open. Also, if amplifier tube V2 is shorted and conducting heavily, the voltage drop across plate-load resistor R3 will be excessive; therefore, a known good tube should be substituted and operation of the circuit observed to determine whether V2 is the cause of trouble.

As mentioned previously, excessive load current can cause the output voltage to be low, especially if the load current exceeds the maximum rating of series regulator tube V1 (resulting in excessive voltage drop across V1) or if the load current exceeds the rating of the power supply (resulting in a decrease in the applied voltage). For these reasons, output capacitor C3 should be checked to determine whether it is satisfactory; a leaky output capacitor could result in reduced output voltage, although the regulator-amplifier circuit may be functioning normally but is unable to compensate for the decrease in output.

Poor Regulation Characteristics. Voltage instability, slow response, etc, are frequently caused by weak or unbalanced triode sections in series regulator V1, unbalanced cathode resistors R6 and R7, or a defective dc amplifier, V2. The gain of the dc amplifier stage is determined primarily by amplifier tube V2 and its applied voltages; therefore, the condition of V2 and its applied voltages are important factors

governing satisfactory operation of the regulator circuit.

DC REGULATOR USING CASCODE TWIN-TRIODE AMPLIFIER

Application.

The dc regulator using a cascode twin-triode amplifier is employed in certain electronic equipment power supply circuits to obtain nearly constant output voltage (or voltages) despite variations of input voltage or output load current.

Characteristics.

Same characteristics as DC Regulator using Pentode Amplifier, except that it uses a cascode twin-triode dc amplifier circuit to control series electron tube.


Circuit Analysis.

General. The dc regulator with twin-triode series regulator tube, cascode twin-triode amplifier, and gas-filled voltage reference tube is capable of providing very stable output voltage regulation. The term "regulation" as used here means the maintenance of a nearly constant output voltage despite changes in the input voltage or the load current. The variation in output voltage that normally result from component aging, changes in operational environment, etc, are usually considered in the design of the circuit, and are compensated for by using close-tolerance (on the order of 1, 2, or 5 percent) components whose values do not deviate from the nominal by more than the strict limits specified.

In this type of voltage regulator, regulation is accomplished by allowing the cathode-to-plate conduction resistance of an electron tube, in series with the output of a power supply, to function as a variable

resistance, and thus provide the voltage drop necessary to compensate for any change in output voltage. That is, the change in output voltage is compared and amplified in the regulator-amplifier circuit, and applied as a bias voltage to the grid of the series regulator tube, thereby varying the conduction resistance of this tube. The varying conduction resistance of the regulator tube, in turn, varies and load current drawn by the series circuit and the voltage drop across the regulator tube; in so doing, the regulator tube absorbs the change in the output voltage. Voltage regulation of approximately 1 percent can be obtained with this type of electronic dc regulator, depending on the circuit design.

Circuit Operation. A typical dc regulator using a cascode twin-triode amplifier is illustrated in the accompanying circuit schematic. Electron tube V1 is a parallel-connected twin-triode used as the series regulator tube. (In applications where the current drain exceeds the current-handling capability of a single series regulator tube, two or more tubes of the same type may be connected in parallel.) Electron tube V2 is another twin-triode, in a cascode dc amplifier circuit configuration, used as the regulator amplifier. Tube V3 is a cold-cathode, gas filled tube used to provide a reference voltage for operation of the regulator-amplifier circuit. The use of the gas-filled regulator tube in this application is satisfactory as a reliable reference since there are no excessive currents in that branch of the circuit. Electron tubes V1 and V2 are indirectly heated, cathode-type tubes; V1 normally has a high heater-to-cathode voltage rating, while V2 has a heater-to-cathode voltage rating which is typical for receiving-type tubes. Because of the heater-to-cathode breakdown voltage limitations imposed by the tubes themselves, it is usually necessary to isolate the filament circuits from each other and to supply the filament (heater) voltages from independent sources.

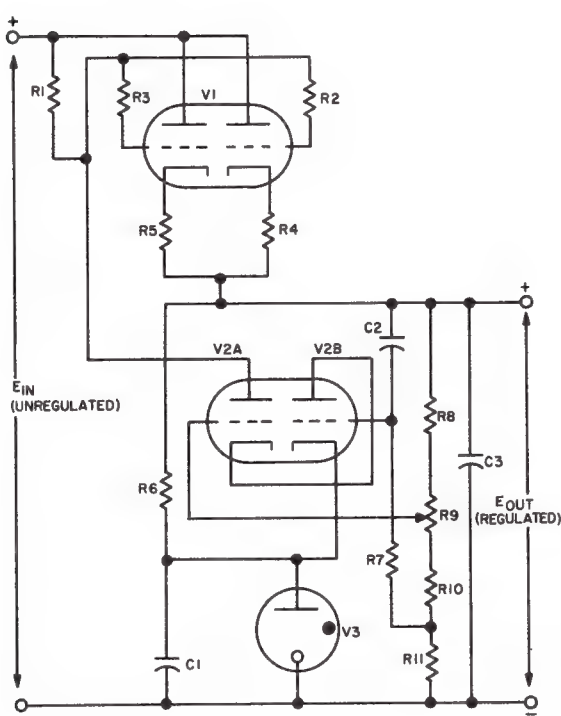

DC Regulator Using Cascode Twin-Triode Amplifier

Resistors R2 and R3, in the grid circuits of V1, are parasitic oscillation suppressors; they are of equal value general between 170 and 1000 ohms. Resistors R4 and R5, in the cathode circuits of V1, are included for the purpose of equalizing the current flow in the parallel-connected triode sections; these resistors are of equal value, generally between 10 and 47 ohms, depending upon the circuit design. Resistor R6, connected in series with reference tube V3 across the output circuit, serves to apply the full output voltage of the regulator to V3, to ensure a satisfactory striking potential and also to act as a current-limiting resistor once the tube is ionized. Capacitor C1, connected in parallel with reference tube V3, is a bypass capacitor which provides a low-impedance path at the power supply ripple frequency (usually 120 Hz), to reduce the possibility of degeneration in the cathode circuit of V2B. The value of capacitor C1 is usually a

compromise between a value which offers low impedance to the power supply ripple frequency and a value which is not so large as to affect the normal operation of the reference tube, V3.

Capacitor C2 couples the full value of ripple voltage from the output of the regulator circuit to the grid of V2B; if capacitor C2 were not used, only a portion of the ripple voltage would be applied to the grid of V2B, as determined by the voltage-divider action of R8, R9, R10, and R11. The value of capacitor C2 is chosen so that it is just large enough to provide satisfactory ripple suppression. If the value of capacitor C2 were made too large, the response time of the regulator circuit to normal dc output-voltage variations would be affected; a value of from 0.01 to 0.1 microfarad is typical in most regulator-amplifier circuits. Resistor R7 helps provide the bias for the grid of V2B. Capacitor C3 is connected across the output terminals to lower the output impedance of the regulator circuit; the value of this capacitor depends upon the circuit design, but is usually 2 microfarads or larger. Resistors R8, R9, R10, and R11 form a voltage divider across the output of the regulator circuit, and are in parallel with the resistance of the load. Resistor R9 is adjustable, and is used to set the output voltage to the desired value the circuit is to maintain.

The cascode configuration of the regulator-amplifier circuit, V2, can be considered as two triode amplifiers directly connected (direct-coupled) in series. The action of this circuit is similar to that of a pentode in that the isolating effect of the screen grid on the plate is achieved, with the advantage that no screen-voltage supply is required. The cascode circuit is used when the gain required of the regulator amplifier is too high for a single triode, yet it is desired to eliminate the pentode screen-voltage supply. However, in order to achieve adequate gain, the cascode circuit requires a large-value plate-load resistor (R1, on the order of 2.2 megohms); this requirement causes the frequency response to be reduced and thereby restricts the area of application of the circuit. The effects of poor frequency response can be reduced somewhat by using a relatively large-value capacitor (about 5 microfarads) for C3.

The two triodes of the cascode twin-triode regulator amplifier are the input section, which is the right-hand tube (V2B), and the output section, which is the left-hand tube (V2A). The cathode of the input section is at a positive potential determined by the

reference tube, V3. The control grid of the input section is returned through resistor R7 to the voltage divider at the junction of resistors R10 and R11. The voltage at the top of resistor R11 is slightly less positive than the operating potential of reference tube V3; hence, a bias voltage of only a few volts is established between the control grid and cathode of V2B. The plate of V2B is directly connected to the cathode of the output section, V2A. The control grid of V2A is returned to the wiper arm of voltage-divider variable resistor R9. The value of grid voltage of V2A, as determined by the setting of resistor R9, is of sufficient amplitude to keep the grid of V2A from drawing appreciable grid current. The operating range of V2A plate voltage, which is applied through plate-load resistor R1, is far enough above its grid voltage so that the current in the grid circuit of V2A does not approach or become comparable with the V2A plate current.

As previously mentioned, the operation of this regulator circuit is based upon the voltage-divider principle of using a variable resistance in the form of electron tube V1 in series with the load resistance. The regulated output voltage, E_{out} , appears across the voltage divider formed by resistors R8, R9, R10, and R11, which are connected across the output of the regulator circuit and in parallel with the load. The total resistance of these voltage-divider resistors in parallel with the load resistance constitutes one part of the resistance in the regulator series voltage-divider arrangement, which includes the variable cathode-to-plate resistance of series regulator tube V1. The currents which pass through the parallel branches (voltage-divider resistors and load resistance) combine, and this total current passes through series regulator tube V1. When the cathode-to-plate reference of V1 is controlled to vary the voltage drop across this tube, the output voltage developed across the load can be regulated and maintained at a constant value.

In order to understand how the dc regulator circuit operates under varying-load conditions, it is necessary to examine first the static voltage distribution under normal-load conditions. The cathode of series regulator tube V1 is held positive with respect to ground by the output voltage, E_{out} , while the grid is held somewhat less positive by the action of regulator amplifier V2. The difference between these two voltages is the bias voltage for V1, which now is at the proper value for series regulator tube V1 to have the

required amount of cathode-to-plate resistance to produce the correct output voltage. The output voltage is applied to reference tube V3 through resistor R6, causing V3 to ionize and conduct, thereby establishing a reference voltage at the cathode of the input section, V2B, of the cascode regulator amplifier. (The action of the gas-filled reference tube, V3, is the same as that previously described under Gas-Tube Regulator Circuit earlier in this section of the handbook.) Regardless of the value of dc voltage applied to the input, E_{in} of the regulator circuit, the voltage at the cathode of V2B will be held constant (by the action of V3) for use as reference voltage.

Cascode regulator-amplifier V2, in essence a two-stage series-connected triode amplifier, uses the plate load of the input section, V2B, as the cathode input impedance of the output section, V2A. Thus, the signal to the input stage is applied between the control grid and ground, while the output of this same stage is the input to the direct-coupled output stage, and is applied between the cathode and ground. The output section, V2A, has a fixed voltage on its grid, obtained from adjustable resistor R9 of the voltage-divider network. This bias voltage limits the excursions of the V2A cathode voltage, which is also the plate voltage of the input section, V2B. The grid voltage for V2B is obtained from voltage-divider resistors R11 and R7. Since the potential at the cathode of V2B is maintained at a constant positive value by the action of reference tube V3, the bias on V2B and V2A, as determined by voltage-divider resistors R11/R7 and R9, respectively, is such that it permits a pre-determined value of current to be drawn by V2. The plate voltage of V2A is obtained from the unregulated input, E_{in} , and applied to the regulator amplifier through plate-load resistor R1. When V2 is conducting, the voltage drop across plate-load resistor R1 develops a voltage at the plate of V2A; this voltage is coupled to the grids of V1. The voltage at the grids of V1 is less than the voltage at the cathodes of V1; hence, the operating bias for V1 is established. The setting of resistor R9, therefore, determines the current through V2A, establishes the bias for V1, and initially determines the effective internal resistance of V1 to obtain the desired output voltage, E_{out} , from the regulator circuit.

Assume, now, that the regulated output voltage, E_{out} , attempts to increase, either because of an increase in the input voltage, E_{in} , to the regulator circuit or because of a decrease in the load requirement.

Through the voltage-divider action of resistors R8, R9, R10, and R11, a slightly higher positive voltage now appears across resistors R9, R10, and R11. This results in an increase in the positive voltage applied to the grids of V2A and V2B, and a corresponding decrease in the bias voltage of this stage. (The cathode voltage of V2B remains constant because of the action of reference tube V3.) As a result of the decreased bias, V2 now conducts more current, and this additional current flow through plate-load resistor R1 results in a greater voltage drop across resistor R1. Thus the voltage at the plate of V2A, which is coupled to the grids of V1, decreases and causes the difference in voltage between the grids and cathodes of V1 to increase. This difference in voltage between the grids and cathodes of V1 is the operating bias for V1. As a result of the bias voltage increase, the effective internal resistance of V1 increases. When the internal resistance of V1 increases, less load current flows through V1, the voltage drop across V1 increases, and the output voltage, E_{out} , of the regulator circuit decreases to its original value.

An action similar to that just described occurs when the regulated output voltage, E_{out} , attempts to decrease. Through the voltage-divider action of resistors R8, R9, R10, and R11, the bias voltage on the grids of V2A and V2B is increased, since a slightly lower positive potential now exists across resistors R9, R10, and R11. As a result of the increased bias, V2 now conducts less current, and this decreased current flow through plate-load resistor R1 causes a smaller voltage drop to occur across resistor R1. Thus, the voltage at the plate of V2A (and the grids of V1) increases and causes the difference in voltage between the grids and cathodes of V1 to decrease. This difference in voltage between the grids and cathodes of V1 is the operating bias for V1. As a result of the bias voltage decrease, the effective internal resistance of V1 decreases. When the internal resistance of V1 decreases, more load current flows through V1, the voltage drop across V1 decreases, and the output voltage of the regulator circuit increases to its original value.

The actions described in the preceding paragraphs are practically instantaneous; consequently, the output voltage, E_{out} , remains practically constant. Since all of the load current must pass through the series control tube, V1, the tube must be capable of passing considerable current. In some circuit applications where the load current requirements exceed the

capabilities of a single tube, two or more identical tubes are connected in parallel (as the sections of twin-triode V1 have been paralleled) in order to obtain suitable regulation characteristics and current handling capability.

The output of the regulator circuit is coupled to the grid of the input section of the cascode twin-triode regulator-amplifier tube, V2B, through coupling capacitor C2. Any ripple component present in the output voltage is amplified in the regulator amplifier, and, since the circuit is basically a negative-feedback circuit, the ripple component is suppressed. As a result, the regulator circuit is sensitive to any voltage changes and is very effective in removing any fundamental ripple-frequency component which is present in the regulated voltage output. Although there are many minor variations in the regulator-amplifier circuit configuration, the function of the regulator circuit remains the same, that is, to supply a regulated output voltage to the load which is independent of variations in input voltage or changes in load current.

Failure Analysis.

Due to the similarity between the DC Regulator using Cascode Twin-Triode Amplifier and the DC Regulator using a Pentode Amplifier (discussed previously in this section), the discussion will not be repeated here. The only differences in Failure Analysis will be some component reference designations. For example: in the Pentode Amplifier, voltage divider resistors R9, R10, and R11 are close tolerance resistors; in this circuit, the close tolerance voltage divider resistors are R6, R8, R9, R10, and R11. The procedures are presented so that, with slight differences, they are applicable to both circuits.

DC REGULATOR USING CASCADE TWIN-TRIODE AMPLIFIER

Application.

Same application as DC Regulator Using Cascode Twin-Triode Amplifier.

Characteristics.

Same characteristics as DC Regulator Using Cascode Twin-Triode Amplifier


Circuit Analysis.

General. The dc regulator with twin-triode series regulator tube, cascade twin-triode amplifier, and gas-filled voltage reference tube is capable of providing very stable output voltage regulation. In this discussion the term "regulation" means the maintenance of a nearly constant output voltage, regardless of changes in the input voltage or the load current. The variations in output voltage that normally result from component aging, changes in operational environment, etc., are usually considered in the design of the circuit, and are compensated for by using close-tolerance (on the order of 1, 2, or 5 percent) components whose values do not deviate from the nominal by more than the strict limits specified.

In this type of voltage regulator, regulation is accomplished by allowing the cathode-to-plate conduction resistance of an electron tube, in series with the output of a power supply, to function as a variable resistance, and thus provide the voltage drop necessary to compensate for any change in output voltage. That is, the change in output voltage is compared and amplified in the cascade twin-triode amplifier circuit, and applied as a bias voltage to the grid of the series regulator tube, thereby varying the conduction resistance of this tube. The varying conduction resistance of the regulator tube, in turn, varies the load current drawn by the series circuit and the voltage drop across the series regulator tube; in so doing, the series regulator tube absorbs the change in the output voltage. Voltage regulation on the order of 1 percent can be obtained with this type of dc regulator, depending on the circuit design.

Circuit Operation. A typical dc regulator circuit using a cascade twin-triode amplifier is illustrated in the accompanying circuit schematic. Electron tube V1 is a parallel-connected twin triode used as the series regulator tube. (In applications where the current drain exceeds the current-handling capability of a single series regulator tube, two or more tubes of the same type may be connected in parallel.) Electron tube V2 is another twin triode, in a cascade dc amplifier circuit configuration, used as the regulator amplifier. Tube V3 is a cold-cathode, gas-filled regulator tube used to provide a reference voltage for operation of the regulator-amplifier circuit. The use of the gas-filled regulator tube in this application is satisfactory as a reliable reference since there are no excessive currents in that branch of the circuit. Electron tubes V1 and V2 are indirectly heated, cathode-

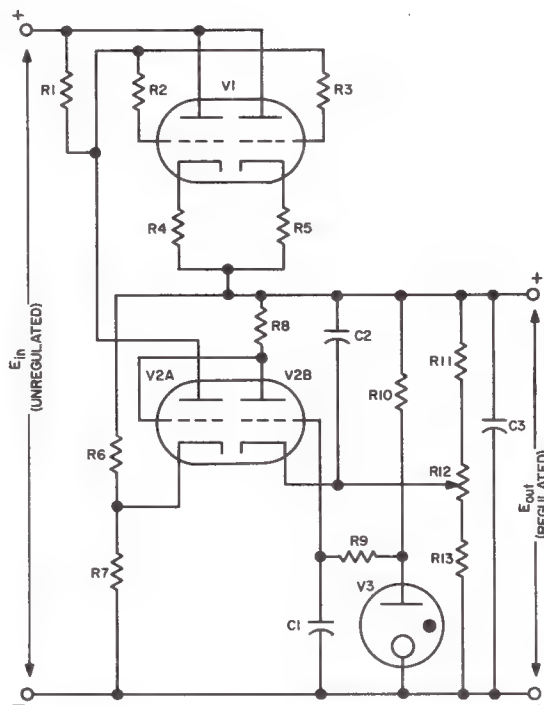type tubes; V1 normally has a high heater-to-cathode voltage rating, while V2 has a heater-to-cathode voltage rating which is typical for receiving-type tubes. Because of the heater-to-cathode breakdown voltage limitations imposed by the tubes themselves, it is usually necessary to isolate the filament circuits from each other and to supply the filament (heater) voltages from independent sources.



DC Regulator Using Cascade Twin-Triode Amplifier

Resistors R2 and R3, in the grid circuits of V1, are parasitic oscillation suppressors; they are of equal value, generally between 270 and 1000 ohms. Resistors R4 and R5, in the cathode circuits of V1, are included for the purpose of equalizing the current flow in the parallel-connected triode sections; these resistors are of equal value, generally between 10 and 47 ohms, depending upon the circuit design. Resistor R10, connected in series with reference tube V3 across the output circuit, serves to apply the full output voltage of the regulator to V3, to ensure a satisfactory striking potential and also to act as a current-limiting resistor once the tube is ionized. The choice

of current is a compromise between shortened tube life at high currents, and higher noise level at low currents. Resistor R9 returns grid of V2B to the positive reference voltage; also, resistor R9, in conjunction with capacitor C1, forms a series RC filter across V3 to suppress the transient noise generated by the gas tube and thereby prevent these undesirable signals from appearing on the grid of V2B. The value of capacitor C1 is usually a compromise between a value which offers low impedance to the transient noise and a value which is not so large as to affect the normal operation of reference tube V3.

Capacitor C2 couples the full value of the power supply ripple voltage (usually 120 Hz) appearing in the output of the regulator to the cathode of V2B. If capacitor C2 were not used, only a portion of the ripple voltage would be applied to the cathode of V2B, as determined by the voltage-divider action of resistors R11, R12, and R13. The value of capacitor C2 is chosen so that it is just large enough to provide satisfactory ripple suppression. If the value of capacitor C2 were made too large, the response time of the regulator circuit to normal dc output voltage variations would be affected; a value of from 0.01 to 0.1 microfarad is typical in most regulator-amplifier circuits, although values to 2 microfarads may occasionally be used. Capacitor C3 is connected across the output terminals to lower the output impedance of the regulator circuits; the value of this capacitor depends upon the circuit design, but is usually 2 microfarads or larger. Resistors R11, R12, and R13 form a voltage divider across the output of the regulator circuit, and are in parallel with the resistance of the load. Resistor R12 is adjustable, and is used to set the output voltage to the desired value that the circuit is to maintain.

The cascade configuration of the regulator-amplifier circuit, V2, can be considered as two triode amplifiers that use direct coupling. In a direct-coupled (dc) amplifier, operating plate voltage and current are usually established by the circuit design, and the grid bias is then adjusted to compensate for tube tolerance. Since, in order to function, the plate of a tube must have a positive voltage with respect to its cathode, and the grid of the next tube must have a negative voltage with respect to its cathode, the voltage-divider arrangements indicated in the diagram are required to obtain the necessary operating voltages for the cascade twin-triode direct-coupled amplifier, V2.

The two triodes of the cascade twin-triode amplifier are the input stage, which is the right-hand tube (V2B), and the output stage, which is the left-hand tube (V2A). The control grid of the input stage is at a positive potential determined by the reference tube, V3. The cathode of the input stage is returned to the wiper arm of voltage-divider variable resistor R12. The cathode voltage of V2B, as determined by the setting of resistor R12, is slightly more positive than the operating potential of reference tube V3; hence, a bias voltage of only a few volts is established between the control grid and cathode of V2B. Resistor R8 is the plate-load resistor for the input stage, V2B; since direct coupling is used from the plate of V2B to the grid of V2A, resistor R8 also serves as the grid-return resistor for the control grid circuit of the output stage, V2A. Thus, the plate voltage of V2B is also the grid voltage of V2A. The cathode of V2A is returned to the junction of resistors R6 and R7, which form a voltage divider across the regulator output, E_{out} . The V2A cathode voltage, which is the voltage developed across resistor R7, is slightly more positive than the voltage at the grid of V2A; hence, a bias voltage of only a few volts is established between the control grid and cathode of V2A. Plate voltage for V2A is obtained from the unregulated voltage input, E_{in} , through plate-load resistor R1.

As previously mentioned, the operation of this regulator circuit is based upon the voltage-divider principle of using a variable resistance in the form of electron tube V1 in series with the load resistance. The regulated output voltage, E_{out} , appears across the voltage dividers formed by resistors R11, R12, and R13, and resistors R6 and R7, which are connected across the output of the regulator circuit and in parallel with the load. The total resistance of these voltage-divider resistors in parallel with the load resistance constitutes one part of the resistance in the regulator series voltage-divider arrangement, which includes the variable cathode-to-plate resistance of series regulator tube V1. The currents which pass through the parallel branches (voltage-divider resistors and load resistance) combine, and this total current passes through series regulator tube V1. When the cathode-to-plate resistance of V1 is controlled to vary the voltage drop across this tube, the output voltage developed across the load can be regulated and maintained at a constant value.

In order to understand how the dc regulator circuit operates under varying-load conditions, it is

necessary to examine first the static voltage distribution under normal-load conditions. The cathode of series regulator tube V1 is held positive with respect to ground by the output voltage, E_{out} , while the grid is held somewhat less positive by the action of regulator amplifier V2. The difference between these two voltages is the bias voltage for V1, which is at the proper value for series regulator tube V1 to have the required amount of cathode-to-plate resistance to produce the correct output voltage. The output voltage is applied to reference tube V3 through resistor R10, causing V3 to ionize and conduct, thereby establishing a reference voltage at the grid of the input stage, V2B, of the cascade regulator amplifier. (The action of the gas-filled reference tube, V3, is the same as that previously described under Gas-Tube Regulator Circuit earlier in this section.) Regardless of the value of the dc voltage applied to the input, E_{in} , of the regulator circuit, the voltage at the grid of V2B will be held constant (by the action of V3) for use as a reference voltage.

Cascade regulator amplifier V2, in essence a two-stage series-connected triode amplifier, uses the plate load of the input stage, V2B, as the grid input impedance of the output stage, V2A. Thus, the signal to the input stage is applied between the cathode and ground; the output of this same stage, which is developed across resistor R8, is the input to the direct-coupled output stage, and is applied between the control grid and ground. The grid of V2B is connected through resistor R9 to the positive reference voltage established by V3, and the cathode of the same tube is at a potential slightly more positive than the reference voltage, since it is returned to the wiper arm of voltage-divider variable resistor R12; this arrangement establishes the operating bias for V2B. The plate of V2B is connected to the full voltage of the regulated output through resistor R8; because the plate of V2B is more positive than its cathode, and the proper bias is established, tube V2B conducts. When V2B plate current flows through resistor R8, a voltage is dropped across this resistor; this voltage is also the grid voltage of V2A, and is at a relatively high value.

A two-stage direct-coupled amplifier is usually designed so that approximately one-half of the available voltage of the regulated output, E_{out} , is used for the input stage. The plate of the output stage, V2A, of the two-stage configuration is connected through a suitable load resistor to the most positive point of the

available voltage, which, in this regulator circuit, is through resistor R1 to the unregulated input, E_{in} . The cathode of the output stage, V2A, must be connected to a positive voltage point suitable for providing the proper biasing voltage and the proper plate-operating voltage. This point is determined by the proper selection of voltage-divider resistors R6 and R7 so that the voltage developed across resistor R7, which is the cathode-bias voltage of V2A, is slightly more positive than the voltage at the grid (which is determined by the voltage drop across resistor R8).

Although the cascade twin-triode regulator-amplifier circuit is a rather complex resistance network which must be adjusted carefully to obtain the proper plate, grid, and cathode voltages for both stages, it provides a rather high gain and good frequency response; therefore, it serves very well as the dc amplifier in an electronic voltage regulator. That is, when regulator amplifier V2 is conducting, the voltage drop across V2A plate-load resistor R1 provides a voltage for the grids of series regulator tube V1; this voltage is less than either the plate or cathode voltage of V1. The difference in voltage between the cathodes and grids of V1 is the operating bias for V1. Thus, the setting of resistor R12 determines the current through V2B, which, in turn, determines the bias of V2A. This bias controls the conduction of V2A hence the voltage drop across resistor R1, which establishes the bias for V1. It is this bias level that initially determines the effective internal resistance of V1 to obtain the desired output voltage, E_{out} , from the regulator circuit.

Assume, now, that the regulated output voltage, E_{out} attempts to decrease, either because of a decrease in the input voltage to the regulator circuit or because of an increase in the load requirement. Through the voltage-divider action of resistors R11, R12, and R13, a slightly lower positive voltage now appears across R12, and R13. This results in a decrease in the positive voltage applied to the cathode of V2B and a corresponding decrease in the bias voltage between this cathode and the grid of V2B. (The grid voltage of V2B remains constant because of the action of reference tube V3.) As a result of the decreased bias, V2B now conducts more current, and this additional current flow through plate-load resistor R8 results in a greater voltage drop across R8; thus, the voltage at the plate of V2B decrease. Since the voltage at the plate of V2B is also the grid voltage of V2A, the bias on V2A now increases; this results

from the fact that a negative-going grid signal in conjunction with a fixed voltage on the cathode causes the difference in potential between these two electrodes to become greater. The increased bias of V2A reduces the conduction through this tube and causes a decrease of plate current through plate-load resistor R1, thereby producing a smaller voltage drop across this resistor to cause a rise in V2A plate voltage. This positive-going voltage at the plate of V2A is coupled to the grids of V1 and causes the difference in potential between the grids and cathodes of V1 to decrease. This difference in voltage between the grids and cathodes of V1 is the operating bias for V1. Thus, as a result of this bias voltage decrease, the effective internal resistance of V1 decreases. When the internal resistance of V1 decreases, more load current flows through V1, the voltage drop across V1 decreases, and the output voltage of the regulator circuit increases to its original value.

An action similar to that just described occurs when the regulated output voltage, E_{out} , attempts to increase. Through the voltage-divide action of resistors R11, R12, and R13, the bias voltage between the cathode and grid of V2B is increased, since a slightly higher positive potential now exists across R12 and R13. As a result of the increased bias, V2B now conducts less current, and this decreased current flow through plate-load resistor R8 causes a smaller voltage drop to occur across R8; thus, the voltage at the plate of V2B increases, and this positive-going voltage causes the bias of V2A to decrease. With a decreased bias, V2A conducts more heavily and the increased plate current through plate-load resistor R1 produces a negative-going voltage at the plate of V2A. This negative-going signal is coupled to the grids of V1, causing the difference in potential between the grids and cathodes of V1 to increase. This difference in voltage between the grids and cathodes of V1 is the operating bias for V1. Thus, as a result of this bias voltage increase, the effective internal resistance of V1 increases. When the internal resistance of V1 increases, less load current flows through V1, the voltage drop across V1 increases, and the output voltage of the regulator circuit decreases to its original value.

The actions described in the preceding paragraphs are practically instantaneous; consequently, the output voltage, E_{out} , remains practically constant. Since all the load current must pass through the series regulator tube, V1, the tube must be capable of passing considerable current. In some circuit applications

where the load current requirements exceed the capabilities of a single tube, two or more identical tubes are connected in parallel (as the sections of twin-triode V1 have been paralleled) in order to obtain suitable regulation characteristics and current-handling capability.

The output of the regulator circuit is coupled to the cathode of the input stage of the cascade twin-triode amplifier tube, V2, through coupling capacitor C2. Any ripple component present in the output voltage is amplified by V2, and, since the circuit is basically a negative feedback circuit, the ripple component is suppressed. As a result, the regulator circuit is sensitive to any voltage changes and it is very effective in removing any fundamental ripple-frequency component which is present in the regulated voltage output. Although there are many minor variations in the regulator-amplifier circuit configuration, the function of the regulator circuit remains the same, that is, to supply a regulated output voltage to the load which is independent of variations in input voltage or changes in load current.

Failure Analysis.

Due to the similarity between the DC Regulator using a Cascade Twin-Triode Amplifier to previous circuits discussed in this section (namely, the DC Regulator using a Pentode Amplifier and the DC Regulator using a Cascode Twin-Triode Amplifier), the discussion will not be repeated here. With minor changes in component designations, the same failure analysis is applicable.

DC REGULATOR USING TWIN-TRIODE AND PENTODE (BALANCED INPUT)

Application.

Same application as DC Regulator using a Pentode Amplifier.

Characteristics.

Same characteristics as DC Regulator using a Pentode Amplifier, with following exceptions:

Uses twin-triode differential amplifier and pentode amplifier circuit to control the series electron tube; the pentode amplifier uses a separate external screen-voltage supply.

The gas-tube regulators are fed from an external regulated negative-voltage supply.


Circuit Analysis.

General. The dc regulator using a twin-triode differential amplifier and pentode amplifier is capable of providing very stable output voltage regulation. In this discussion the term "regulation" means the maintenance of a nearly constant output voltage regardless of changes in the input voltage or the load current. The variations in output voltage that normally result from component aging, changes in operational environment, etc, are usually considered in the design of the circuit, and are compensated for by using close-tolerance (on the order of 1, 2, or 5 percent) components whose values do not deviate from the nominal by more than the strict limits specified.

In this type of voltage regulator, regulation is accomplished by allowing the cathode-to-plate conduction resistance of an electron tube, in series with the output of a power supply, to function as a variable resistance, and thus provide the voltage drop necessary to compensate for any change in output voltage. That is, the change in output voltage is compared and amplified in the twin-triode and pentode regulator-amplifier circuit, and applied as a bias voltage to the grid of the series regulator tube, thereby varying the

conduction resistance of this tube. The varying conduction resistance of the regulator tube, in turn, varies the load current drawn by the series circuit and the voltage drop across the series regulator tube; in so doing, the series regulator tube absorbs the change in the output voltage. Voltage regulation on the order of 1 percent can be obtained with this type of voltage regulator, depending on the circuit design.

Circuit Operation. A typical dc regulator circuit using a twin-triode differential amplifier and pentode amplifier is illustrated in the accompanying circuit schematic. Electron tube, V1 is a parallel-connected twin-triode used as the series regulator tube. (In applications where the current drain exceeds the current-handling capability of a single series regulator tube, two or more tubes of the same type may be connected in parallel.) Electron tube V2 is a high-gain pentode, and electron tube V3 is a high-gain twin-triode; V3 functions as a cathode-coupled differential amplifier and is the input stage of the regulator-amplifier circuit, whereas pentode amplifier V2 is the output stage of the same circuit. The high amplification obtain from differential amplifier V3 and pentode amplifier V2 enables the circuit to have good

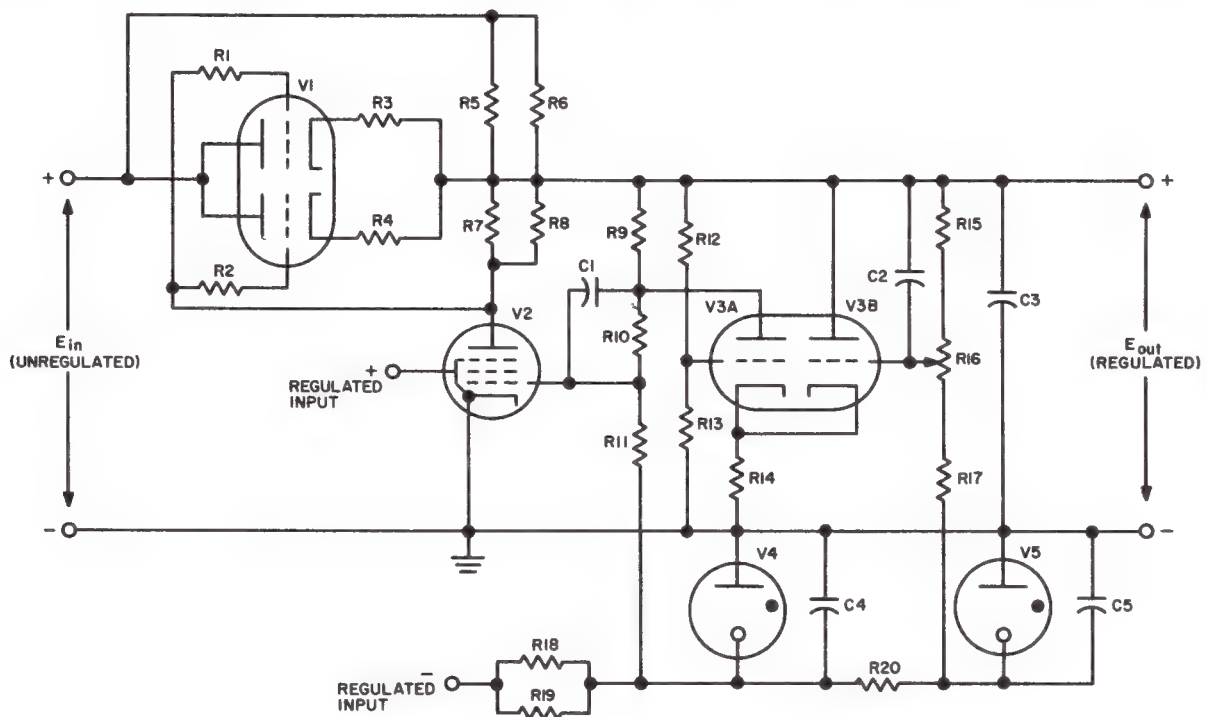

DC Regulator Using Twin-Triode and Pentode (Balanced Input)

sensitivity to small-voltage variations. Tubes V4 and V5 are cold-cathode, gas filled tubes used to provide reference voltages for operation of the regulator-amplifier circuit. The use of the gas-filled regulator tubes in this application is satisfactory as reliable references since there are no excessive currents in those branches of the circuit. Electron tubes V1, V2, and V3 are indirectly heated, cathode-type tubes; V1 normally has a high heater-to-cathode voltage rating, while V2 and V3 have a heater-to-cathode voltage rating which is typical for receiving-type tubes. Because of the heater-to-cathode breakdown voltage limitations imposed by the tubes themselves, it is usually necessary to isolate the filament circuits from each other and to supply the filament (heater) voltages from independent sources.

Resistors R1 and R2, in the grid circuits of V1, are parasitic oscillation suppressors; they are of equal value, generally between 270 and 1000 ohms. Resistors R3 and R4, in the cathode circuits V1, are included for the purpose of equalizing the current flow of the parallel-connected triode sections; these resistors are of equal value, generally between 10 and 47 ohms, depending upon circuit design. Resistors R5 and R6 are connected in parallel with series regulator tube V1 to reduce its plate dissipation. The value of these resistors is selected so that their current flow under all operating conditions is less than the minimum load current; this will ensure a current flow through series regulator tube V1 and thereby permit the regulator to function.

Gas-filled regulator tubes V4 and V5 provide reference voltage for the grid circuits of V2 and V3B, respectively. Parallel-connected resistors R18 and R19 apply to the cathode of V4 a negative potential which is sufficiently high to ensure satisfactory ionization; these resistors also limit the current through V4 once the gas in the tube is ionized. Because tube V5 provides a reference voltage less negative than of V4, its cathode potential is accordingly made less negative by the voltage drop across resistor R20, which also serves as a current-limiting resistor once tube V5 is ionized. In a typical dc regulator circuit, V4 may be a type OA2 gas tube to provide a reference voltage of -150 volts, and V5 may be a type 5651 gas tube to provide a reference voltage in the range of -82 to -92 volts. By supplying the reference tubes from an external regulator negative-voltage source rather than connecting the tubes in the cathode circuit of the regulator-amplifier stage (as is

done in some dc regulator circuits), several advantages are obtained. First, the cathodes of the regulator-amplifier stages are at ground rather than at a high positive potential, thereby allowing a larger plate swing of the stages; second, the reference tube is in a grid circuit rather than in a cathode circuit, and thus operates under constant-current conditions; and third, the regulator-amplifier stage gain is greater with this connection because cathode degeneration caused by gas-tube impedance is not present. The choice current for the respective gas-filled tubes, as determined by resistors R18, R19, and R20, is a compromise between shortened tube life a high currents and higher noise level at low currents. Capacitors C4 and C5, connected across V4 and V5, respectively, are bypass capacitors to suppress the transient noise generated by the gas tubes. The value of these capacitors is usually the largest value recommended by the tube manufacturer.

The regulator-amplifier circuit consists of cathode-coupled differential amplifier V3, used as a balanced input stage, cascaded with pentode amplifier V2, used as a single-ended output stage. The left-hand section of the differential amplifier, V3A, functions as a triode amplifier, and the right-hand section, V3B, functions as a cathode follower. The balanced-input configuration of twin-triode V3 reduces the effects of tube aging and heater voltage variations.

If an input signal is applied to the grid of the cathode follower (V3B) and the output signal is taken from the plate of the triode amplifier (V3A), the cathode-coupled differential amplifier will have a high input impedance and provide high amplification without signal inversion between the input and output. Resistors R15, R16, and R17 form a voltage divider across the regulator output and the regulated negative input to gas-filled reference tube V5. This voltage divider provides the operating bias for the grid of V3B; the value of bias voltage is selected by setting variable resistor R16. Resistor R14 is the common cathode resistor that provides the cathode coupling from cathode follower V3B to triode amplifier V3A. Resistors R12 and R13 also form a voltage divider, but this one is across the regulator output and ground. The voltage developed across resistor R13 provides the operating bias for the grid of triode amplifier V3A. Plate voltage for V3A is obtained from the regulator output through resistor R9; this resistor, along with resistors R10 and R11, is in a voltage divider across the regulator output and the

regulated negative input to gas-filled reference tube V4.

In addition to providing the plate voltage for V3A, voltage divider R9, R10, and R11 provides the operating bias for the grid of output pentode amplifier V2; this bias voltage is obtained from the junction of resistors R10 and R11. Resistor R10 provides direct coupling from the plate of V3A to the grid of V2. The RC combination of resistor R10 and capacitor C1 is a phase-lead network in the coupling circuit; the purpose of this network is to provide stabilization and thereby prevent oscillation within the regulator amplifier. The suppressor grid of pentode V2 is connected internally to the cathode, and the cathode is returned directly to ground. The pentode screen grid receives its operating voltage from an external regulated positive-voltage source. Plate voltage for output pentode amplifier V2 is obtained from the regulator output through parallel-connected, equal-value resistors R7 and R8; this arrangement lowers the effective plate-load resistance, but permits the pentode to handle higher plate currents. The decreased plate-load resistance improves the frequency response of the circuit.

Capacitor C2 couples the full value of the power supply ripple voltage (usually 120 Hz) appearing in the output of the regulator to the grid of V3B. If capacitor C2 were not used, a portion of the ripple voltage would be applied to the grid of V3B, as determined by the voltage-divider action of resistors R15, R16, and R17. The value of capacitor C2 is chosen so that it is just large enough to provide satisfactory ripple suppression. If the value of capacitor C2 were made too large, the response time of the regulator circuit to normal dc output-voltage variations would be affected; a value of from 0.01 to 0.1 microfarad is typical in most regulator-amplifier circuits, although values up to 2 microfarad may occasionally be used. Capacitor C3 is connected across the output terminals to lower the output impedance of the regulator circuit; the value of this capacitor depends upon the circuit design, ranging from 0.5 microfarad to 2 microfarads. The voltage dividers formed by the series-connected combinations of resistors R9, R10, and R11, resistors R12 and R13, and resistors R15, R16, and R17 are all across the output of the regulator circuit and are thereby in parallel with the load. Any resistance measurement across the output must take into consideration these parallel circuits. Voltage-divider resistor R16, in the grid circuit of

V3B, is adjustable and is used to set the output voltage to the desired value that the circuit is to maintain.

The cathode-coupled differential amplifier configuration of V3 provides a single-ended output signal having high amplification but no signal inversion from input to output. The single-ended output makes the circuit sensitive to power-supply voltage changes, and the common-cathode arrangement causes the cathodes to mutually offset the drift due to heater-voltage variations. The gain of the differential amplifier is a combination of the gains of the cathode-follower section, V3B, and the triode-amplifier section, V3A. The output impedance of the cathode follower acts as an impedance in series with the cathode input to the triode amplifier. To avoid an excessively large bias produced by a large-value cathode resistor (R14), the cathodes of the differential amplifier are returned to ground and the grids are returned to the regulator output. The sum of the plate currents of V3A and V3B is equal to the current through cathode resistor R14. This value of current is essentially constant; that is, an increase in cathode follower V3B plate current causes an almost equal decrease in triode amplifier V3A plate current. In this manner the current through resistor R14 is kept essentially constant.

As previously mentioned, the operation of this regulator circuit is based upon the voltage-divider principle of using a variable resistance in the form of electron tube V1 in series with the load resistance. The regulated output voltage, E_{out} , appears across the voltage dividers (previously pointed out) which are in parallel with the load. The total resistance of these voltage-divider resistors in parallel with the load resistance constitutes one part of the resistance in the regulator series voltage-divider arrangement, which includes the variable cathode-to-plate resistance of series regulator tube V1. The currents which pass through the parallel branches (voltage-divider resistors and load resistance) combine, and this total current passes through series regulator tube V1 (and parallel-connected resistors R5 and R6). When the cathode-to-plate resistance of V1 is controlled to vary the voltage drop across this tube, the output voltage developed across the load can be regulated and maintained at a constant value.

In order to understand how the dc regulator circuit operates under varying-load conditions, it is necessary to examine first the static voltage distribution under normal-load conditions. The cathode of

series regulator tube V1 is held positive with respect to ground by the output voltage, E_{out} , while the grid is held somewhat less positive by the action of the regulator amplifier (pentode amplifier V2 and differential amplifier V3). The difference between these two voltages is the bias voltage for V1, which is at the proper value for series regulator tube V1 to have the required cathode-to-plate resistance to produce the correct output voltage.

A negative voltage is fed from an external regulated source to the cathode of reference tube V4 through parallel-connected resistors R18 and R19, and to the cathode of reference tube V5 through resistor R20. Since the plate of each reference tube is at ground potential, the negative voltage at the cathode causes the gas to ionize and the tube to conduct. In this manner negative reference voltage are established for the voltage dividers feeding the grid of pentode amplifier V2 and the grid of the cathode-follower section, V3B, of the differential amplifier. (The action of the gas-filled reference tubes is the same as that previously described, under Gas-Tube Regulator Circuit, in this Section of the Handbook.) Regardless of the value of dc voltage applied to the input, E_{in} , of the regulator circuit, the negative-voltage references in the grid circuits of V2 and V3B will be held constant by the action of V4 and V5, respectively.

The regulator-amplifier circuit, which consists of pentode amplifier V2 and cathode-coupled differential amplifier V3, uses the cathode load impedance of cathode follower V3B as the cathode input impedance of triode amplifier V3A. Thus, the signal of the cathode follower is applied between the control grid and ground, while the output of this same stage is the input to the triode amplifier, and is applied between the cathode and ground. The grid voltage for the cathode follower is determined by the setting of voltage-divider resistor R16. The triode amplifier has a fixed voltage on its grid, obtained from the junction of voltage-divider resistors R12 and R13. The plate voltage of V3A and V3B is obtained from the regulated output, E_{out} ; the plate of V3B is returned directly to the regulator output, whereas the plate of V3A is returned to this potential through plate-load resistor R9, which is part of the voltage-divider network consisting of resistors R9, R10, and R11. Thus, the operating potentials at the electrodes of V3A and V3B are such that, under normal-load conditions, they permit a predetermined value of

current to be drawn by V3 and develop an output signal across plate-load resistor R9.

The output signal of V3A developed across resistor R9 is direct-coupled through resistor R10 to the grid of pentode amplifier V2. This signal, then, acts to control the conduction through V2. When V2 is conducting, the current through parallel-conducted plate-load resistors R7 and R8 develops a voltage at the plate of V2; this voltage is coupled to the grids of V1. The voltage at the grids of V1 is less than the voltage at the cathodes of this tube; hence, the normal-load operating bias for V1 is established. The setting of variable resistor R16, therefore, determines the current through V3, which, in turn, controls the current through V2 and thereby establishes the bias for V1. This bias voltage of V1 initially determines the effective normal-load internal resistance of V1 to obtain the desired output voltage, E_{out} , from the regulator circuit.

Assume, now, that the regulated output voltage, E_{out} , attempts to increase, either because of an increase in the input voltage, E_{in} , to the regulator circuit or because of a decrease in the load requirement. Through the voltage-divider action of resistors R15, R16, and R17, a slightly higher positive voltage now appears across resistors R16 and R17. This results in an increase in the voltage applied to the grid of V3B, and a corresponding decrease in the bias of this stage. As a result of the decreased bias, V3B now conducts more current, and this additional current flow through cathode-load resistor R14 results in a greater voltage drop across this resistor. The voltage at the cathode of V3, in going more positive, increases the bias on V3A and thereby reduces conduction through this stage. The reduced plate current of V3A causes a small voltage drop across a plate-load resistor R9, which, in effect, is a positive-going signal at the plate of V3A. The differential amplifier, therefore, amplifies but does not invert the positive going signal applied to the grid of V3B.

The positive-going signal at the plate of V3A is direct-coupled through resistor R10 to the grid of pentode amplifier V2, where it reduces the bias and causes an increase in the conduction of this stage. When the conduction of V2 is increased, the additional plate current through plate-load resistors R7 and R8 produces a greater voltage drop across these resistors, and thereby develops a negative-going signal at the plate of V2. This negative-going is coupled to the grids of V1, where it causes the difference in

voltage between the grids and cathodes of V1 to increase. The difference in voltage between the grids and cathodes of V1 is the operating bias for V1. As a result of the bias voltage increase, the effective internal resistance of V1 increases. When the internal resistance of V1 increases, less load current flows through V1, the voltage drop across V1 increases, and the output voltage E_{out} , of the regulator circuit decreases to its original value.

An action similar to that just described occurs when the regulated output voltage, E_{out} , attempts to decrease. Through the voltage-divider action of resistors R15, R16, and R17, the bias voltage on the grid of V3B is increased, since a slightly lower positive potential now exists across resistors R16 and R17. As a result of the increased bias, V3B now conducts less current, and the decreased current flow through cathode-load resistor R14 causes a smaller voltage drop to occur across this resistor. The voltage at the cathode of V3, in going negative, decreases the bias on V3A and thereby increases conduction through this stage. The increased plate current of V3A causes a greater voltage drop across plate-load resistor R9, which, in effect, is a negative-going signal at the plate of V3A. This negative-going signal is direct-coupled through resistor R10 to the grid of pentode amplifier V2, where it increases the bias and causes a decrease in the conduction of V2. When V2 conduction decreases, less plate current flows through plate-load resistors R7 and R8, thereby producing a smaller voltage drop across these resistors. Thus, the voltage at the plate of V2 (and the grids of V1) increases and causes the difference in voltage between the grids and cathodes of V1 to decrease. This difference in voltage between the grids and cathodes of V1 is the operating bias for V1. As a result of the bias voltage decrease, the effective internal resistance of V1 decreases. When the internal resistance of V1 decreases, more load current flows through V1, the voltage drop across V1 decreases, and the output voltage of the regulator circuit increases to its original value.

The actions described in the preceding paragraphs are practically instantaneous; consequently, the output voltage, E_{out} , remains practically constant. Since most of the load current must pass through series regulator tube V1, the tube must be capable of passing considerable current. In some circuit applications where the load current requirements exceed the capabilities of a single tube, two or more identical tubes are connected in parallel (as the sections of

twin-triode V1 have been paralleled) in order to obtain suitable regulation characteristics and current-handling capability. Also, in order to reduce the plate dissipation of series regulator tube V1, resistors can be connected in parallel with the tube (as resistors R5 and R6 have been connected in this regulator circuit).

The output of the regulator circuit is coupled to the grid of the cathode-follow section, V3B, of the differential amplifier through coupling capacitor C2. Any ripple component present in the output voltage is amplified in the regulator amplifier, and since the circuit is basically a negative-feedback circuit, the ripple component is suppressed. As a result, the regulator circuit is sensitive to any voltage changes and is very effective in removing any fundamental ripple-frequency component which is present in the regulated voltage output. Although there are many variations in the regulator-amplifier circuit configuration, the function of the regulator circuit remains the same, that is, to supply a regulated output voltage to the load which is independent of variations in input voltage or changes in load current.

Failure Analysis.

General. The dc regulator using a twin-triode and pentode regulator amplifier includes several components which are rather critical and thus directly affect the operation of the regulator circuit. For this reason, the resistors in the regulator-amplifier circuit are normally close-tolerance (on the order of 1, 2, or 5 percent) resistors with good temperature-stability characteristics. The operation of the circuit will be impaired if these resistors should change in value for any reason. Since the regulator circuit attempts to hold the output voltage constant, it is usually good practice to determine whether the load current is within tolerance before suspecting trouble within the regulator circuit proper. A load-current measurement may be made by inserting a milliammeter (having a suitable range) in series with the output of the regulator circuit. Also, a voltage measurement should be made at the input to the regulator circuit to determine whether the unregulated voltage output from the power supply (and filter circuit) is within tolerance.

No Output. In this dc regulator circuit, the no-output condition is likely to be limited to one of the following possible causes: the lack of filament voltage applied to series regulator tube V1, the lack of applied dc voltage (from the associated power supply

and filter circuit), or a short-circuited load (including output capacitor C3). A visual check of the glass-envelope series regulator tube, V1, should be made to determine whether the filament is lit; if the filament is not lit, it may be open or the filament voltage may not be applied. The tube filament should be checked for continuity; also, the presence of filament voltage at the tube socket should be determined by measurement. The dc voltage applied to the regulator circuit should be measured at the input (plate of V1) to determine whether it is present and of the correct value, since the lack of input voltage from the associated power supply and filter circuit will cause a lack of output voltage. With the dc voltage removed from the input to the circuit, resistance measurements can be made across the load to determine whether the load circuit, including capacitor C3, is shorted. (The resistance measured across the load circuit will normally be something less than the total value of the voltage-divider resistors, depending upon the load circuit design.)

If pentode amplifier V2 has low emission, the voltage drop across plate-load resistors R7 and R8 will be below normal; therefore, the bias of V1 will be decreased and a high output from the regulator will result. Under this circumstance, a tube known to be good should be substituted at V2 and operation of the circuit observed to determine whether tube V2 is the cause of the trouble.

High Output. The high-output condition is usually caused by a decrease in operating bias for the series regulator tube, V1, which, in turn, causes the tube to decrease its internal resistance and permit the regulator output voltage to rise above normal. Therefore, any defects in the electronic regulator circuit which can cause a decrease in the operating bias for V1 should be suspected. Voltage measurements should be made at the socket of V1 to determine whether bias (cathode-to-grid) voltage is present.

A visual check of gas-filled regulator tube V5, which provides a reference voltage for the operation of the cathode-follower section (V3B) of the differential amplifier circuit, should be made to determine whether the tube is conducting. A voltage measurement made between the cathode and plate of V5 will determine whether sufficient negative voltage is present at the tube to cause conduction. If the voltage is more negative than normal, the tube may be defective. If the voltage measured across V5 is less

negative than normal, it is likely that resistor R20 has changed in value.

A visual check of regulator-amplifier tubes V2 and V3 should be made to determine whether their filaments are lit; if the filaments are not lit, they may be open or the filament voltage may not be applied. The tube filaments should be checked for continuity; also, the presence of filament voltage at the tube sockets should be determined by measurement.

The bias voltages applied to V2 and V3 should be measured to determine whether these tubes are improperly biased, causing the operating bias on V1 to decrease. Assuming that V4 and V5 are conducting normally to provide the proper reference voltages, if the voltage at the grid of V2 or V2B is below normal, there will be an increase in the bias on the respective tube. In this case it is possible that the resistor R9, R10, or R11 has changed in value to increase the bias of V2, or that resistor R15 or R16 has changed in value to increase the bias of V3B; in addition, an improper setting of variable resistor R16 will affect the bias voltage at the grid of V3B. A high output from the regulator also will result when the voltage at the grid of V3A is above normal, and thereby causes a bias decrease on this stage; a change in the value of resistor R12 or R13 will produce this effect. If V2 or V3B is biased to cutoff, or if V3A is conducting heavily as a result of a high positive voltage at its grid, V1 will be made to conduct heavily as a result of a decreased operating bias. In this case, it is likely that resistor R9 or R10 is open to cut off V2, that resistor R15 or the top portion of resistor R16 is open to cut off V3B, or that resistor R13 is open to cause the heavy conduction of V3A.

Low Output. The low-output condition of the regulator is usually caused by an increase in operating bias for the series regulator tube, V1, which, in turn, causes the tube to increase its internal resistance and permit the regulator output voltage to fall below normal. Therefore, any defects in the electronic regulator circuit which can cause an increase in the operating bias for V1 should be suspected. Trouble in one section of V1 (such as low cathode emission or an open tube element) will cause a reduction in the output. Voltage measurements should be made at the socket of V1 to determine whether the bias (cathode-to-grid) voltage is excessive. The equalizing resistors, R3 and R4, in the cathode circuits of V1 should be measured to determine that neither one is open, that they have

not increased in value, and that they are of equal resistance.

A visual check of gas-filled regulator tube V4, which provides a reference voltage for the operation of pentode amplifier V2, should be made to determine that the tube is conducting. A voltage measurement made between the cathode and plate of V4 will determine whether sufficient voltage is present at the tube to cause conduction. If the voltage is more negative than normal, the tube may be defective. If the voltage measured across V4 is less negative than normal, it is likely that resistor R18 or R19 is open, thereby providing a voltage which is not sufficiently negative to cause gas tube V4 to ionize.

The bias voltages applied to V2 and V3 should be measured to determine whether these tubes are improperly biased, causing the operating bias on V1 to increase. Assuming that V4 and V5 are conducting normally to provide the reference voltages, if the voltage at the grid of V2 or V3B is above normal, there will be a decrease in the bias on the respective tube. In this case, it is possible that resistor R9, R10, or R11 has changed in value to decrease the bias of V2, or that resistor R15 or R16 has changed in value to decrease the bias of V3B; in addition, an improper setting of variable resistor R16 will affect the bias voltage at the grid of V3B. A low output from the regulator also will result when the voltage at the grid of V3A is below normal, and thereby cause a bias increase on this stage; a change in the value of resistor R12 or R13 will produce this effect. If V2 or V3B is biased by a high positive voltage on its grid so that either tube conducts heavily, or if V3A is biased to cutoff, V1 will be made to conduct less as a result of an increased operating bias. In this case, it is likely that resistor R11 is open or capacitor C1 is leaky or shorted, thus placing a high positive voltage on the grid of V2. A high positive voltage will be placed on the grid of V3B if the bottom portion of resistor R16 or resistor R17 is open, or if capacitor C2 is leaky or shorted. A bias sufficient to cut off V3A will result if resistor R12 is open; also, an open cathode resistor, R14, in the differential amplifier will cut off V3A.

It is possible for the symptom of a high positive voltage at the grid of V2 or V3B to be caused by a defect in the voltage reference circuits. For example, if capacitor C4 or C5 (paralleling reference tubes V4

and V5, respectively) is leaky or shorted, the grids of pentode amplifier V2 and cathode follower V3B will be returned to ground instead of to their respective negative voltage reference. As a result, the voltage distribution across the respective voltage dividers will be such that the voltage at the grid of V2 or V3B is made more positive. Separately, the voltage at the grid of V2 will be more positive if reference tube V4 is defective, and a similar condition will be noted for the grid of V3B if resistor R20 is open. The result of each of the foregoing defects will be an increase in the bias on series regulator tube V1, and a decrease in the regulator output voltage.

If plate-load resistor R7 or R8 (for pentode amplifier V2) is open, the bias voltage applied to the grids of V1 will be made larger, causing a decrease in the regulator output. Also, if tube V2 is shorted and conducting heavily, the voltage drop across plate-load resistors R7 and R8 will be excessive. If differential amplifier tube V3 has low emission, the voltage drop across its plate-load resistor (R9) will be below normal; therefore, the bias of V2 will be decreased, and in turn, cause an increase in the bias of V1 and a decrease in the output of the regulator.

As mentioned previously, excessive load current can cause the output voltage to be low, especially if the load current exceeds the maximum rating of series regulator tube V1 (resulting in excessive voltage drop across V1) or if the load current exceeds the rating of the power supply (resulting in a decrease in the applied voltage). For these reasons, output capacitor C3 should be checked to determine whether it is satisfactory. A leaky output capacitor could result in reduced output voltage, although the regulator-amplifier circuit (V2 and V3) may be functioning normally but still be unable to compensate for the decrease in output.

Poor Regulation Characteristics. Voltage instability, slow response, etc, are frequently caused by weak or unbalanced triode sections in series regulator tube V1, unbalanced cathode resistors R3 and R4, or defective regulator amplifier tubes V2 and V3. The gain of the regulator-amplifier stage is determined primarily by tubes V2 and V3 and their applied voltages; therefore, the condition of V2 and V3 and the applied voltages are important factors governing satisfactory operation of the regulator circuit.

DC REGULATOR USING PENTODE AND TWIN-TRIODE (BALANCED OUTPUT)

Application.

Same application as DC regulator using Pentode and Twin-Triode (Balanced Input).

Characteristics.

Same characteristics as DC Regulator using Pentode and Twin-Triode (Balanced Input).


Circuit Analysis.

General. The dc regulator using a pentode amplifier and a twin-triode differential amplifier is capable of providing very stable output voltage regulation. In this discussion the term "regulation" means the maintenance of a nearly constant output voltage, regardless of changes in the input voltage or the load current. The variations in output voltage that normally result from component aging, changes in operational environment, etc, are usually considered in the design of the circuit, and are compensated for by using close-tolerance (on the order of 1, 2, or 5 percent) components whose values do not deviate from the nominal by more than the strict limits specified.

In this type of voltage regulator, regulation is accomplished by allowing the cathode-to-plate conduction resistance of an electron tube, in series with the output of a power supply, to function as a variable resistance, and thus provide the voltage drop necessary to compensate for any change in output voltage. That is, the change in output voltage is compared and amplified in the pentode and twin-triode regulator-amplifier circuit, and applied as a bias voltage to the grid of the series regulator tube, thereby varying the conduction resistance of this tube. The varying con-

duction resistance of the regulator tube, in turn, varies the load current drawn by the series circuit and the voltage drop across the series regulator tube; in so doing, the series regulator tube absorbs the change in the output voltage. Voltage regulation of approximately 1 percent can be obtained with this type of electronic dc regulator, depending on the circuit design.

Circuit Operation. A typical dc regulator circuit using a pentode amplifier and twin-triode differential amplifier is illustrated in the accompanying circuit schematic. Electron tube V1 is a parallel-connected twin-triode used as the series regulator tube. (In applications where the current drain exceeds the current-handling capability of a single series regulator tube, two or more tubes of the same type may be connected in parallel). Electron tube V2 is another twin-triode, and is used as a cathode-coupled differential amplifier stage. Electron tube V3 is a high-gain pentode amplifier. Together, tubes V2 and V3 function as the regulator-amplifier circuit; pentode V3 is the input stage, and twin-triode V2 is the output stage. Tubes V4 and V5 are cold-cathode, gas-filled tubes used to provide reference voltages for operation of the regulator-amplifier circuit. The gas-filled regulator tubes in this application are satisfactory as reliable references since there are no excessive currents in those branches of the circuit. Electron tubes V1, V2, and V3 are indirectly heated, cathode-type tubes; V1 normally has a high heater-to-cathode voltage rating, while V2 and V3 have a heater-to-cathode voltage rating which is typical for receiving-type tubes. Because of the heater-to-cathode breakdown voltage limitations imposed by the tubes themselves, it is usually necessary to isolate the filament circuits from each other and to supply the filament (heater) voltages from independent sources.

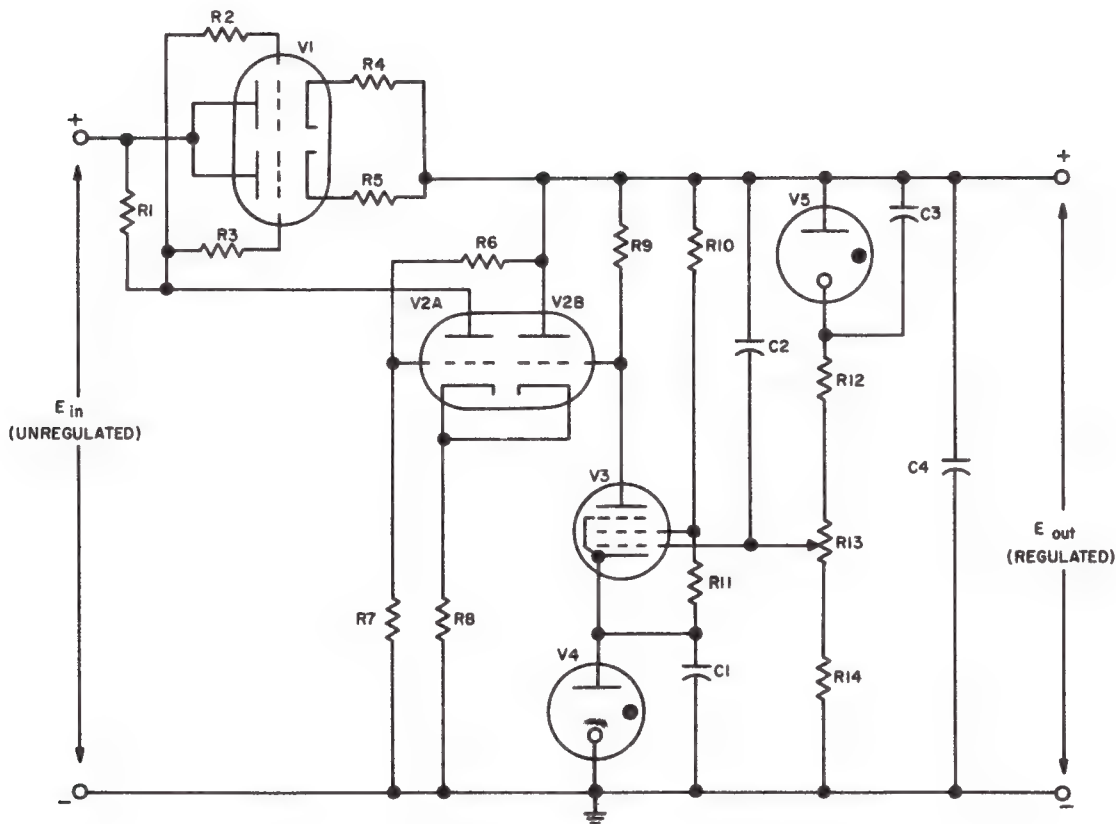

DC Regulator Using Pentode and Twin-Triode (Balanced Output)

Resistors R2 and R3, in the grid circuits of series regulator tube V1, are parasitic oscillation suppressors; they are of equal value, generally between 270 and 1000 ohms. Resistors R4 and R5, in the cathode circuits of V1, are included for the purpose of equalizing the current flow in the parallel-connected triode sections; these resistors are of equal value, generally between 10 and 47 ohms, depending upon the circuit design.

The regulator-amplifier circuit consists of pentode amplifier V3, used as a single-ended input stage, cascaded with cathode-coupled differential amplifier V2, used as a balanced output stage. The left-hand section of the differential amplifier, V2A, functions as a triode amplifier, and the right-hand section, V2B, functions as a cathode follower. The balanced configuration of twin-triode V2 reduces the effects of tube aging and heater voltage variations. If an input signal

is applied to the grid of the cathode follower and the output signal is taken from the plate of the triode amplifier, the cathode-coupled differential amplifier will have a high input impedance and provide high amplification without signal inversion between the input and the output. Resistor R1, connected to the source of unregulated input voltage, E_{in} , provides plate voltage for triode amplifier V2A. Control grid voltage for this same stage is obtained from voltage divider resistors R6 and R7, connected across the regulated output voltage, E_{out} . Resistor R8 is a common resistor for triode amplifier V2A and cathode follower V2B.

Gas-filled regulator tubes V4 and V5 furnish reference voltages for pentode amplifier V3; V4 is in the cathode circuit, and V5 is in the control grid circuit. Resistors R10 and R11, connected in series with reference tube V4 across the output circuit, serve to

apply the full output voltage of the regulator to V4, to ensure a satisfactory striking potential and also to act as current-limiting resistors once the tube is ionized. In addition, resistors R10 and R11 function as a voltage divider to provide the dc operating potential for the screen grid of pentode amplifier V3. Plate voltage for the pentode amplifier is furnished by the regulated output through plate-load resistor R9. Capacitor C1, connected in parallel with reference tube V4, is a bypass capacitor which provides a low-impedance path at the power supply ripple frequency (usually 120 Hz), to reduce the possibility of degeneration in the cathode circuit of V3. The value of capacitor C1 is usually a compromise between a value which offers low impedance to the power supply ripple frequency and a value which is not so large as to affect the normal operation of the reference tube, V4.

Gas tube V5 is in series with voltage-divider resistors R12, R13, and R14 across the regulated output, E_{out} . Because this arrangement permits a larger percentage of the output-voltage variations to be coupled to the control grid of the pentode amplifier, the over-all gain of the regulator amplifier is made greater. In some dc regulators, two or more gas tubes may be used in series with the voltage-divider resistors. The number and type of gas tubes used in this manner depends upon the voltage drop required between the output and the grid of pentode amplifier V3; it is usually desirable that the largest portion of the required voltage drop be obtained across the gas tube(s). With a gas tube placed in a grid circuit, such as V5 is in this dc regulator, an additional advantage is realized in that there is a constant current through the gas tube, and its dynamic resistance is of little consequence. Therefore, the gas tube is selected solely on the merits of its ability to regulate at the same voltage each time the power supply (equipment) is turned on and the degree to which the voltage is regulated at a constant value so long as the equipment is in operation. Capacitor C3, connected in parallel with V5, is used to suppress the transient noise generated by the gas tube, and thereby prevent these undesirable signals from appearing on the grid of pentode amplifier V3. The value of capacitor C3, which is usually the largest value recommended by the tube manufacturer, is a compromise between a value which eliminates the transient noise and a value which is not so large as to affect the normal operation of reference tube V5.

Capacitor C2 couples the full value of ripple voltage from the output of the regulator circuit to the grid of V3; if capacitor C2 were not used, only a portion of the ripple voltage would be applied to the grid of V3, as determined by the action of V5 and voltage-divider resistors R12, R13, and R14. The value of capacitor C2 is chosen so that it is just large enough to provide satisfactory ripple suppression. If the value of capacitor C2 were made too large, the response time of the regulator circuit to normal dc output-voltage variations would be affected. A value of from 0.01 to 0.1 microfarad is typical in most regulator-amplifier circuits. Capacitor C4 is connected across the output terminals to lower the output impedance of the regulator circuit; the value of this capacitor depends upon the circuit design, but is usually 2 microfarads or larger. Resistors R12, R13, and R14, which form a voltage divider in series with reference tube V5 across the output of the regulator circuit, are in parallel with the resistance of the load. Resistor R13 is adjustable, and is used to set the output voltage to the desired value the circuit is to maintain.

The cathode-coupled differential amplifier configuration of V2 provides a single-ended output signal having high amplification but no signal inversion from input to output. The single-ended output makes the circuit sensitive to power-supply voltage changes, and the common cathode arrangement causes the cathodes to mutually offset the drift due to heater-voltage variations. The gain of the differential amplifier is a combination of the gains of the cathode-follower section, V2B, and the triode-amplifier section, V2A. The output impedance of the cathode follower acts as an impedance in series with the cathode input to the triode amplifier. The sum of the plate currents of V2A and V2B is equal to the current through cathode resistor R8. This value of current is essentially constant; that is, an increase in the plate current of cathode follower V2B causes an almost equal decrease in the plate current of triode amplifier V2A. In this manner, the current through resistor R8 is kept essentially constant.

As previously mentioned, the operation of this regulator circuit is based upon the voltage-divider principle of using a variable resistance in the form of electron tube V1 in series with the load resistance. The regulated output voltage, E_{out} , appears across the voltage dividers formed by gas tube V5 and resistors R12, R13, and R14, and resistors R6 and R7, which

are connected across the output of the regulator circuit and in parallel with the load. The total resistance of these voltage-divider resistors in parallel with the load resistance constitutes one part of the resistance in the regulator series voltage-divider arrangement, which includes the variable cathode-to-plate resistance of series regulator tube V1. The currents which pass through the parallel branches (voltage-divider resistors and load resistance) combine, and this total current passes through series regulator tube V1. When the cathode-to-plate resistance of V1 is controlled to vary the voltage drop across this tube, the output voltage developed across the load can be regulated and maintained at a constant value.

In order to understand how the dc regulator circuit operates under varying-load conditions, it is necessary to examine first the static voltage distribution under normal-load conditions. The cathode of series regulator tube V1 is held positive with respect to ground by the output voltage, E_{out} , while the grid is held somewhat less positive by the action of the regulator-amplifier circuit. The difference between these two voltages is the bias voltage for V1, which is at the proper value for series regulator tube V1 to have the required amount of cathode-to-plate resistance to produce the correct output voltage. The output voltage is applied to reference tube V4 through resistors R10 and R11, causing V4 to ionize and conduct, thereby establishing a reference voltage at the cathode of pentode amplifier V3. In a like manner, gas tube V5 also ionizes and conducts to produce a constant voltage drop in the voltage-divider circuit consisting of that tube as well as resistors R12, R13, and R14. (The action of the gas-filled reference tubes, V4 and V5, is the same as that previously described under Gas-Tube Regulator Circuit earlier in this Section of the handbook.) Regardless of the value of the dc voltage applied to the input, E_{in} , of the regulator circuit, the voltage at the cathode of V3 will be held constant (by the action of V4) for use as a reference voltage. Likewise, the voltage at the top of resistor R12 will be held constant by the action of gas tube V5.

The input to the regulator-amplifier circuit, as determined by the setting of resistor R13, is applied to the grid of pentode amplifier V3. The output signal of this stage, developed across plate-load resistor R9, is direct-coupled to the grid of V2B—the cathode follower input section of cathode-coupled differential amplifier V2. The cathode load impedance of cathode

follower V2B is used as the cathode input impedance of triode amplifier V2A. Thus, the signal to the cathode follower is applied between the control grid and ground, while the output of this same stage is the input to the triode amplifier, and is applied between the cathode and ground. The grid voltage for the cathode follower is determined by the voltage drop across the pentode plate-load resistor, R9. The triode amplifier, V2A, has a fixed voltage on its grid, obtained from the junction of voltage-divider resistors R6 and R7. The plate voltage of V2A is obtained from the unregulated input, E_{in} , through plate-load resistor R1; the plate of V2B is returned directly to the regulator output. Thus, the operating potentials at the electrodes of V2A and V2B are such that, under normal-load conditions, they permit a predetermined value of current to be drawn by V2 and develop as output signal across plate-load resistor R1.

The output signal of V2A developed across resistor R1 is direct-coupled through resistors R2 and R3 to the grids of series regulator tube V1. This signal, then, acts to control the conduction through V1. That is, when differential amplifier V2 is conducting, the voltage drop across V2A plate-load resistor R1 provides a voltage for the grids of series regulator tube V1; this voltage is less than either the plate or cathode voltage of V1. The difference in voltage between the cathodes and grids of V1 is the operating bias for V1. Thus, the setting of resistor R13 determines the current through V3, which, in turn, determines the conduction of V2, and thus the voltage drop across resistor R1, which establishes the bias for V1. It is this bias level that initially determines the effective internal resistance of V1 to obtain the desired output voltage, E_{out} , from the regulator circuit.

Assume, now, that the regulated output voltage, E_{out} , attempts to decrease, either because of a decrease in the input voltage to the regulator circuit or because of an increase in the load requirement. Through the voltage-divider action of resistors R12, R13, and R14, a slightly lower positive voltage now appears across R13 and R14. This results in a decrease in the positive voltage applied to the grid of pentode amplifier V3 and a corresponding increase in the bias voltage between the cathode and the grid of V3. (The cathode voltage of V3 remains constant because of the action of reference tube V4.) As a result of the increased bias, V3 now conducts less current, and this reduced current flow through plate-load resistor R9 results in a smaller voltage drop

across R9; thus, the voltage at the plate of V3 increases. Since the voltage at the plate of V3 is also the grid voltage of cathode follower V2B, the bias on V2B now decreases. As a result of the decreased bias, V2B conducts more current, and this additional current flow through cathode-load resistor R8 results in a greater voltage drop across this resistor. The voltage at the cathode of V2, in going more positive, increases the bias on triode amplifier V2A, and thereby reduced conduction through this stage. The reduced plate current of V2A causes a smaller voltage drop across plate-load resistor R1, which, in effect, is a positive-going signal at the plate of V2A. The differential amplifier, therefore, amplifies but does not invert the positive-going signal applied to the grid of V2B. The positive-going voltage at the plate of V2A is coupled to the grids of V1 and causes the difference in potential between the grids and cathodes of V1 to decrease. This difference in voltage between the grids and cathodes of V1 is the operating bias for V1. Thus, as a result of this bias voltage decrease, the effective internal resistance of V1 decreases. When the internal resistance of V1 decreases, more load current flows through V1, the voltage drop across V1 decreases, and the output voltage of the regulator circuit increases to its original value.

An action similar to that just described occurs when the regulated output voltage, E_{out} , attempts to increase. Through the voltage-divider action of resistors R12, R13, and R14, the bias voltage between the cathode and grid of V3 is decreased, since a slightly higher positive potential now exists across R13 and R14. As a result of the decreased bias, V3 now conducts more current, and this increased current flow through plate-load resistor R9 causes a larger voltage drop to occur across R9; thus, the voltage at the plate of V3 decreases, and this negative-going voltage causes the bias of V2B to increase. As a result of the increased bias, V2B now conducts less current, and the decreased current flow through cathode-load resistor R8 causes a smaller voltage drop to occur across this resistor. The voltage at the cathode of V2, in going negative, decreases the bias on triode amplifier V2A, and thereby increases the conduction through this stage. The increased plate current of V2A causes a greater voltage drop across plate-load resistor R1, which, in effect, is a negative going voltage at the plate of V2A. This negative-going signal is coupled to the grids of V1, causing the difference in potential between the grids and cathodes of V1 to

increase. This difference in voltage between the grids and cathodes of V1 is the operating bias for V1. Thus, as a result of this bias voltage increase, the effective internal resistance of V1 increases. When the internal resistance of V1 increases less load current flows through V1, the voltage drop across V1 increases, and the output voltage of the regulator circuit decreases to its original value.

The actions described in the preceding paragraphs are practically instantaneous; consequently, the output voltage, E_{out} , remains practically constant. Since all the load current must pass through the series regulator tube, V1, the tube must be capable of passing considerable current. In some circuit applications where the load current requirements exceed the capabilities of a single tube, two or more identical tubes are connected in parallel (as the sections of twin-triode V1 have been paralleled) in order to obtain suitable regulation characteristics and current-handling capability.

The output of the regulator circuit is coupled to the grid of pentode amplifier V3 through coupling capacitor C2. Any ripple component present in the output voltage is amplified in the regulator amplifier, and, since the circuit is basically a negative-feedback circuit, the ripple component is suppressed. As a result, the dc regulator circuit is sensitive to any voltage changes and is very effective in removing any fundamental ripple-frequency component which is present in the regulated voltage output. Although there are many variations in the regulator-amplifier circuit configuration, the function of the dc regulator circuit remains the same, that is, to supply a regulated output voltage to the load which is independent of variations in the input voltage or changes in the load current.

Failure Analysis.

General. The dc regulator using a pentode and a twin-triode regulator amplifier includes several components which are rather critical and directly affect the operation of the regulator circuit. For this reason, the resistors in the regulator-amplifier circuit are normally close-tolerance (on the order of 1, 2, or 5 percent) resistors with good temperature stability characteristics. The operation of the circuit will be impaired if these resistors should change in value for any reason. Since the regulator circuit attempts to hold the output voltage constant, it is usually good practice to determine whether the load current is within

tolerance before suspecting trouble within the regulator circuit proper. A load-current measurement may be made by inserting a milliammeter (having a suitable range) in series with the output of the regulator circuit. Also, a voltage measurement should be made at the input to the regulator circuit to determine whether the unregulated voltage output from the power supply (and filter circuit) is within tolerance.

No Output. In this dc regulator circuit, the no-output condition is likely to be limited to one of the following possible causes: the lack of filament voltage applied to series regulator tube V1, the lack of applied dc voltage (from the associated power supply and filter circuit), or a short-circuited load (including output capacitor C4). A visual check of the glass-envelope series regulator tube, V1, should be made to determine whether the filament is lit; if the filament is not lit, it may be open or filament voltage may not be applied. The tube filament should be checked for continuity; also, the presence of filament voltage at the tube socket should be determined by measurement. The dc voltage applied to the regulator circuit should be measured at the input (plate of V1) to determine whether it is present and of the correct value, since the lack of input voltage from the associated power supply and filter circuit will cause a lack of output voltage. With the dc voltage removed from the input to the circuit, resistance measurements can be made across the load to determine whether the load circuit, including capacitor C3, is shorted. (The resistance measured across the load circuit will normally measure something less than the total value of the voltage-divider resistors, depending upon the load circuit design.)

High Output. The high-output condition is usually caused by a decrease in operating bias for the series regulator tube, V1, which, in turn, causes the tube to decrease its internal resistance and permits the regulator output voltage to rise above normal. Therefore, any defects in the electronic regulator circuit which can cause a decrease in the operating bias for V1 should be suspected. Voltage measurements should be made at the socket of V1 to determine whether bias (cathode-to-grid) voltage is present.

A visual check of the gas-filled regulator tubes, V4 and V5, which provide the reference voltages for the operation of pentode amplifier V3, should be made to determine whether the tubes are conducting. A voltage measurement made between the plate and cathode of V4 or V5 will determine whether suffi-

cient voltage is present at the tube to cause conduction. If the voltage is above normal, the tube may be defective. If the voltage measured across V4 is below normal, it is likely that resistor R10 or R11 is open. A below-normal voltage measurement across V5 will indicate that resistor R12, R13, or R14 is probably open.

A visual check of regulator-amplifier tubes V2 and V3 should be made to determine whether their filaments are lit; if the filaments are not lit, they may be open or the filament voltage may not be applied. The tube filaments should be checked for continuity; also, the presence of filament voltage at the tube sockets should be determined by measurement.

The bias voltages applied to V2 and V3 should be measured to determine whether these tubes are improperly biased, causing the operating bias on V1 to decrease. Assuming that V4 and V5 are conducting normally to provide the proper reference voltages, if the voltage at the grid of V2A or V3 is below normal, there will be an increase in the bias on the respective tube. In this case it is possible that resistor R6 or R7 has changed in value to increase the bias of V2A, or that resistor R12, R13, or R14 has changed in value to increase the bias of V3; in addition, an improper setting of variable resistor R13 will affect the bias voltage at the grid of V3. If V2A or V3 is biased to cutoff, V1 will be made to conduct heavily as a result of the decreased operating bias. In this case, it is likely that resistor R6 is open to cut off V2A, or that resistor R12 or the top portion of resistor R13 is open to cut off V3.

A high output from the regulator will also result when the voltage at the grid of V2B is above normal, thereby causing a bias decrease on this stage. This condition will result when pentode amplifier V3 is in cutoff because of a floating control grid or open cathode circuit. In the case of a floating control grid, it is likely that the bottom portion of resistor R13 or resistor R14 is open; and open cathode circuit of tube V3 will result if resistor R10 or R11 is open.

If the differential amplifier tube, V2, has low emission, the voltage drop across V2A plate-load resistor R1 will be below normal; therefore, the bias of V1 will be decreased and a high output from the regulator will result. An open cathode resistor, R8, will produce the same effects as a defective differential amplifier tube.

Low Output. The low-output condition of the regulator is usually caused by an increase in operating

bias for the series regulator tube, V1, which, in turn, causes the tube to increase its internal resistance and permits the regulator output voltage to fall below normal. Therefore, any defects in the electronic regulator circuit which can cause an increase in the operating bias for V1 should be suspected. Trouble in one section of V1 (such as low cathode emission or an open tube element) will cause a reduction in the output. Voltage measurements should be made at the socket of V1 to determine whether the bias (cathode-to-grid) voltage is excessive. The equalizing resistors, R4 and R5, in the cathode circuits of V1 should be measured to determine that neither one is open, that they have not increased in value, and that they are of equal resistance.

A visual check of the gas-filled regulator tubes, V4 and V5, which provide the reference voltages for the operation of the pentode amplifier circuit, should be made to determine that the tube is conducting. A voltage measurement made between the plate and cathode of V4, and also between the plate and cathode of V5, will determine whether sufficient voltage is present at the tube to cause conduction. If the voltage measured across V4 is below normal, or if no voltage is present, it is likely that capacitor C1 is either leaky or shorted. A below-normal voltage measurement across V5 will indicate that capacitor C2 or C3 is probably either leaky or shorted.

The bias voltages applied to V2 and V3 should be measured to determine whether these tubes are improperly biased, causing the operating bias on V1 to increase. Assuming that V4 and V5 are conducting normally to provide the reference voltages, if the voltage at the grid of V2A or V3 is above normal, there will be a decrease in the bias on the respective tube. In this case, it is possible that resistor R6 or R7 has changed in value to decrease the bias of V2A, or that resistor R12, R13, or R14 has changed in value to decrease the bias of V3; in addition, an improper setting of variable resistor R13 will affect the bias voltage at the grid of V3. If V2A or V3 is biased by a high positive voltage on its grid so that either tube conducts heavily, V1 will be made to conduct less as a result of an increased operating bias. In this case, it is likely that capacitor C2 is leaky or shorted, thus placing a high positive voltage on the grid of V3. A high positive voltage will be placed on the grid of V2A if resistor R7 is open.

If plate-load resistor R1 (for differential amplifier V2) is open, the bias voltage applied to the grids of

V1 will be made larger, causing a decrease in the regulator output. Also, if tube V2 is shorted and conducting heavily, the voltage drop across plate-load resistor R1 will be excessive. If pentode amplifier tube V3 has high emission, the voltage drop across its plate-load resistor, R9, will be above normal; therefore, the bias of V2B will be increased, thus causing an increase in the bias of V1 and a decrease in the output of the regulator. If resistor R9 is open, the cathode follower (V2B) control grid will be floating; this will cause the cathode follower to cut off. As a result, the regulator output will decrease.

As mentioned previously, excessive load current can cause the output voltage to be low, especially if the load current exceeds the maximum rating of series regulator tube V1 (resulting in excessive voltage drop across V1) or if the load current exceeds the rating of the power supply (resulting in a decrease in the applied voltage). For these reasons, output capacitor C4 should be checked to determine whether it is satisfactory. A leaky output capacitor could result in reduced output voltage, although the regulator-amplifier circuit (V2 and V3) may be functioning normally but still be unable to compensate for the decrease in output.

Poor Regulation Characteristics. Voltage instability, slow response, etc, are frequently caused by weak or unbalanced triode sections in series regulator tube V1, unbalanced cathode resistors R4 and R5, or defective regulator amplifier tubes V2 and V3. The gain of the regulator-amplifier stage is determined primarily by tubes V2 and V3 and their applied voltages; therefore, the condition of V2 and V3 and the applied voltages are important factors governing satisfactory operation of the regulator circuit.

BASE-CONTROLLED REGULATOR (SEMICONDUCTOR)

Application.

The base-controlled transistor regulator is used as a voltage regulator in electronic equipment where more precise voltage control is required.

Characteristics.

Is smaller, weighs less, and provides better reliability and performance than the electron tube regulator.

Efficiency is higher than the shunt-type regulator.

Requires a reference voltage source for control purposes.


Control amplifier provides more precise regulation.

Series transistor is subject to damage by heavy overload or short circuit, except where protective provisions are included with the circuit.

Circuit Analysis.

General. The base-controlled regulator uses a dc amplifier to control the conductivity of a series-connected transistor regulator. The dc control amplifier is controlled by base bias variations which, in turn, vary the base bias of the series regulator accordingly. Use of the control amplifier improves the sensitivity of the regulator and helps to stabilize output voltage variations. The control transistor must be large enough to carry only the base current, but the series transistor must be rated for full-load capability.

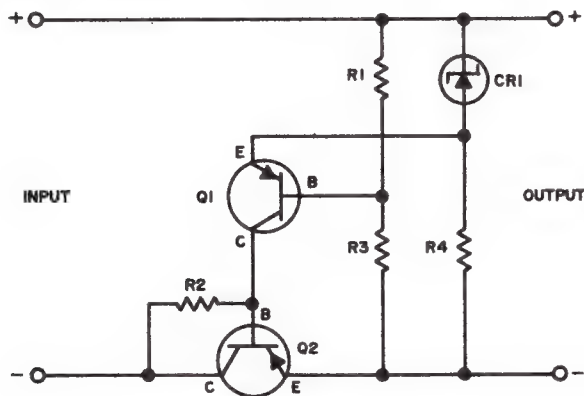Circuit Operation. The schematic of a typical base-controlled regulator is shown in the accompanying illustration.



Base-Controlled Regulator

Breakdown diode CR1, together with current-limiting resistor R4, supplies a constant voltage reference source to the emitter of Q1. Transistor Q1 is the regulator control amplifier whose base is biased by a fixed voltage divider, consisting of R1 and R3, connected across the output. Resistor R2 functions as the collector resistor for control transistor Q1, across which the bias for the base of series regulator transistor Q2 is developed.

During normal operation, resistor R4 provides a resistance low enough to keep breakdown diode CR1 conducting sufficiently to develop its rated breakdown voltage. Thus, the emitter of transistor Q1 is held at a fixed positive bias voltage. The resistive voltage divider, composed of R1 and R3, provides a nega-

tive (forward) base bias to control transistor Q1, which causes sufficient conduction to keep the current flow through Q2 at a value which produces the desired nominal regulated output voltage.

Assume for the moment that the output voltage tends to rise; an increasing negative voltage will appear across R1 and bias Q1 further in a forward direction to cause the collector current of Q1 to increase. Electron flow will develop a positive voltage across collector resistor R2 and reduce the base bias of Q2. When the base bias of series regulator transistor Q2 is reduced, less emitter current flows and the effective internal resistance of Q2 is increased. Thus, the load current flowing through Q2 produces a larger voltage drop between the emitter and collector, and causes the output voltage to decrease and return to its original value. Conversely, when the output voltage tends to drop, the base bias on Q1 is reduced, and causes the collector current of Q1 to decrease. A decreased flow of current through collector resistor R2 allows the collector voltage of Q1 to increase in a negative direction toward the supply value. Hence, the base of series regulator transistor Q2 is biased more negative and causes the emitter current of Q2 to increase. The increased current flow from collector to emitter of Q2 effectively reduces the internal resistance offered between collector and emitter and reduces the voltage drop across the transistor caused by load current. Thus, the output voltage rises back toward its normal value.

By connecting breakdown diode CR1 and resistor R4 across the regulated output voltage, instead of the supply voltage, a more stable reference voltage is obtained, and more precise control is achieved. If the amplification of control transistor Q1 is sufficient, ripple voltage variations, as well as ordinary load variations, will be compensated for, providing more precise regulation. If necessary more than one control amplifier may be used by connecting them in tandem.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low-voltage ranges of conventional volt-ohmmeters. Be careful also to observe the proper polarity when checking continuity, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. Lack of line voltage, an open transistor Q2, or a defective control amplifier circuit can cause loss of output. Check the line voltage to make certain that a blown primary fuse is not at fault. Measure the voltage across CR1 to determine whether the breakdown diode is operational, and measure the resistance of R1, R2, R3, and R4. If control amplifier Q1 is shorted, the base bias on Q2 will probably be sufficient to bias off Q2 and prevent an output voltage. If Q1 is satisfactory, and no output appears, Q2 is probably defective.

Low Output. A constant low output voltage can result from low line voltage, a defective series transistor Q2, or a defective control circuit. Check the line voltage. If the output voltage is still low, check the breakdown voltage across CR1 and the base bias of Q1 and Q2. If the breakdown voltage of CR1 is normal, but the base bias of Q1 is higher than normal, measure the values of R1 and R3. If CR1 voltage is other than normal, measure the value of R4 and check CR1. If the base bias on Q1 is normal, measure the base bias of Q2. If this bias is lower than normal, measure the value of R2. If resistor R2 is satisfactory, then Q1 is drawing less than normal current, and with fixed emitter bias and normal base bias, indicates a change of characteristics in Q1. If all parts check satisfactory but a low output still exists, the regulator is probably overloaded. Series transistor Q2 will become overheated and eventually fail.

High Output. If the output voltage is continuously higher than normal, it indicates that series transistor Q2 is conducting heavily and offering little resistance. Such a condition can be caused by a high forward base bias or a shorted transistor. If the base bias of Q2 is higher than normal, the trouble is in the control circuit. If the base bias of Q2 is normal or lower than normal, the transistor may be defective. With a higher than normal base bias on Q2 check the value of R2 to make certain it has not decreased. If R2 is satisfactory, low collector current in Q1 is indicated. Either R1 or R3 has increased in value or Q1 is defective. Measure the values of R1 and R3. If the resistors check normal, Q1 is probably defective.

EMITTER-FOLLOWER REGULATOR (SEMICONDUCTOR)

Application.

The emitter-follower regulator is commonly used as a voltage regulator in electronic equipments.

Characteristics.

Is smaller, weighs less, and provides better reliability and performance than the electron tube regulator. Efficiency is high.

Requires a reference voltage source.

Transistor must be capable of carrying full-load current.


Transistor may be easily damaged by an overload or short circuit.

May be used with a control amplifier for more precise regulation.

Circuit Analysis.

General. The emitter-follower regulator may be controlled by a Zener or breakdown diode, or by a dc control amplifier. The control amplifier may be base-controlled, or emitter-controlled. It is always connected as a series regulator; units may be paralleled for high current-carrying capacity. The base voltage or current is used to drive the unit into heavy conduction when a low series resistance and higher output voltage is desired, or to reduce conduction to produce a high series resistance and lower the output voltage. Normally, it operates at the middle of its range to produce the nominal output voltage.

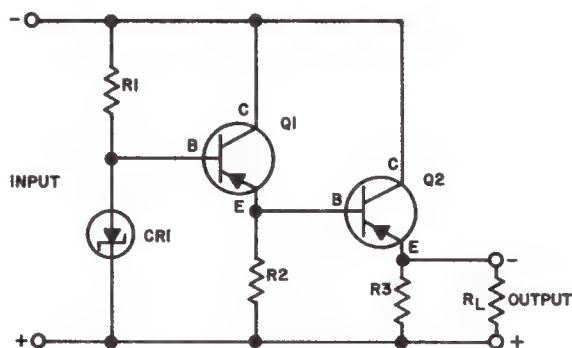Circuit Operation. The schematic of a typical emitter-follower regulator is shown in the accompanying illustration.



Emitter-Follower Regulator

As shown in the schematic, resistor R1 and breakdown diode CR1 form a voltage divider across the input which determines the base-emitter bias of transistor Q1. Transistor Q1 is connected as an emitter-

follower to drive the base of series regulator transistor Q2, which is also connected as an emitter-follower. Resistor R2 stabilizes the emitter bias of transistor Q1, while R3 ensures that a minimum emitter current in Q2 will always flow, even though the load current may drop to zero.

In normal operation, breakdown diode CR1 is isolated from regulator transistor Q2 by emitter-follower control stage Q1. Resistor R1 is chosen to have a value which permits breakdown diode CR1 to operate constantly, and maintains the base of Q1 at a fixed reference voltage. Emitter resistor R2 maintains an essentially constant minimum current through Q1 and stabilizes the base bias for regulator transistor Q2. When the emitter output voltage of Q1 increases, the bias voltage between base and emitter is reduced, less current flows through Q1, and the voltage drop across Q1 is increased, lowering the emitter output voltage. Similarly, when the emitter voltage of Q1 becomes lower than normal, the base-emitter bias increases and produces a greater flow of emitter current. Hence, the internal effective resistance between collector and emitter is decreased, the voltage drop across the transistor is less, and the emitter output voltage increases. Thus, the base bias voltage to transistor Q2 is stabilized with respect to the reference voltage produced by breakdown diode CR1, and transistor Q1 need only supply the base current for regulator transistor Q2.

Normally, the base bias on Q2 produces sufficient emitter current flow to produce an effective internal collector-emitter resistance sufficient to drop the source voltage at the collector to the nominal output voltage value. When the output voltage tends to increase because of a reduction in load, the emitter voltage of Q2 increases; the value of the base-emitter bias is lowered (since the base voltage is fixed), producing a reduced flow of emitter current through Q2. In this manner, the internal collector-to-emitter effective resistance is increased, producing a greater voltage drop across the transistor. The output voltage is reduced accordingly. Conversely, when the output voltage decreases, the forward base-to-emitter bias is increased and causes a greater forward flow of current. Hence, the effective collector-to-emitter internal resistance is decreased, the voltage drop across the transistor is reduced, and the output voltage is increased accordingly. Emitter resistor R3 is in parallel with the load and determines minimum emitter current flow at no-load. The major function of resistors

R2 and R3 are to determine minimum emitter current flow, and hence limit the minimum output voltage to the desired value.

Actually, these resistors are not absolutely required for operation of the regulator, since the two transistors will operate in tandem in a super-alpha connection without them. When these resistors are used, slightly better regulation is obtained.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low-voltage ranges of conventional volt-ohmmeters. Be careful also to observe the proper polarity when checking continuity, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. If R1 opens, breakdown diode CR1 is shorted and transistor Q1 or Q2 is defective; or if R2 or R3 is shorted, no output will occur. Measure the input voltage to determine that a blown line fuse is not at fault. In addition, measure the voltage across R1 and CR1. If no voltage is measured across R_L, either CR1 or R1 is open. Check the resistance of R1, and check CR1. With normal base voltage applied to Q1, check the voltage across R2. If no voltage exists, either Q1 is defective, or R2 is shorted, and no output will be obtained from Q2. Measure the value of R2, and check the forward and reverse resistance of Q1. If the forward and reverse resistance both are high, Q1 is probably defective. With normal base voltage on Q2 and no output, either Q2 is defective or R3 is shorted. Measure the value of R3, and check the forward and reverse resistance of Q2. If both the forward and reverse resistance of Q2 is high, Q2 is probably defective. Where a regulator is connected to a power supply filter, do not neglect the fact that the input capacitor of the filter can be shorted, and make R3 appear to be shorted.

Low Output Voltage. If the input voltage is low, or the base-emitter bias of Q1 or Q2 is reduced, a low output voltage can exist. Check diode CR1 and measure the value of R1. Measure the value of R2 and R3 and check transistors Q1 and Q2 for a higher than normal forward resistance. Do not neglect to check the load current, since it is possible that the range of the regulator is being exceeded. This will usually be indicated by the operation of Q2 at a higher than

normal temperature. If prolonged, this will lead to damage or burnout of the transistor.

High Output Voltage. If the output voltage is continuously higher than normal, it indicates that the voltage drop across Q2 is lower than normal because of excessive current flow, producing a lower effective internal resistance. If Q1 is defective, a larger than normal forward bias may be applied to Q2. Likewise, if Q2 is defective, a greater than normal emitter current can flow. If resistor R3 increases in value or opens, the minimum voltage may change, but the output voltage will not increase to a higher value. On the other hand, if R3 decreases in value, it will tend to increase the output voltage.

CONSTANT-CURRENT REGULATOR (SEMICONDUCTOR)

Application.

The constant-current regulator is used in electronic equipment to supply a constant current from a voltage source, regardless of load or voltage changes.

Characteristics.

Utilizes the constant-current characteristics of a triode transistor biased by a fixed base current.

Current regulator is connected in series with the load.

Voltage changes across a resistor are used to sense the proper control action against a reference voltage source.


Circuit is designed to produce a relatively constant high-output impedance.

Circuit Analysis.

General. In a voltage regulator, the attempt is made to reduce the output impedance to produce the smallest possible voltage variation, while the current regulator uses exactly the opposite approach. It is constructed to produce the highest possible output impedance, so that only fractional current changes are produced by large voltage variations. Instead of sensing the output voltage changes, the regulated current is passed through a series resistor and the voltage developed across the resistor is compared with a reference voltage source. Any voltage difference is amplified and applied to a series-regulating transistor which completes the regulated feedback connection by controlling the regulated current flow. The simpler types

of current regulator use the series transistor itself to supply the amplified error voltage, while the more complicated types use a separate control amplifier to control more precisely the output of the regulating transistor.

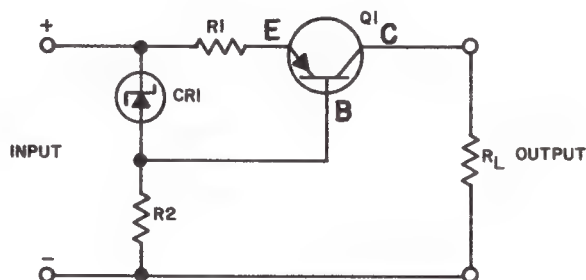Circuit Operation. The schematic of a typical series current regulator is shown in the accompanying illustration.



Series Current Regulator

Breakdown diode CR1 provides a source of reference voltage against which any current changes are compared. Resistor R2 limits the current through CR1 to a reasonable value which produces a constant voltage across the diode. Resistor R1 acts as the current-sensing resistor which develops the comparison voltage.

Since resistor R1 is connected in series with the emitter of Q1, current flow produces a voltage drop across R1 which varies directly with the amount of current drawn by the load. Normally, breakdown diode CR1 provides a constant voltage which holds the base of Q1 at a fixed bias value. The absolute value of bias is determined by the difference between the fixed base bias and the voltage developed across emitter resistor R1 by current flow. With a constant current flow, a constant bias is developed. Should the emitter current tend to increase, a larger voltage drop occurs across R1 and reduces the forward bias. Consequently, less current flows and the output current is returned to its normal value. Should the current tend to decrease, the voltage drop across R1 is decreased and the forward bias is increased, causing a greater flow of current and returning it back to normal. Although the current is held to a relatively constant value, the voltage may vary widely. Where better performance is required, or where only very small current changes occur, a dc control amplifier may be

added. In this type of regulator, the error voltage produced by the difference between the voltage drop across the sensing resistor and the reference source is amplified and applied to control the base of the regulator.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low-voltage ranges of conventional volt-ohmmeters. Be careful also to observe the proper polarity when checking continuity, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. If R1, or R2, or Q1 are open, no current can flow. First measure the line voltage to make certain that a blown fuse is not at fault. Then measure the resistance of R1 and R2. If both resistors are satisfactory, check for normal voltage across CR1. If no voltage appears across CR1 and R2 is of the proper value, CR1 is probably defective. If R1 is of the proper resistance and the voltage across CR1 is normal, but there is still no output, transistor Q1 is probably defective.

Improper Output. If the value of R1 changes, or if diode CR1 or transistor Q1 changes characteristics, an improper output will result. If the change produces a lower than normal bias, the output will be reduced. If a higher than normal bias is produced, the output will be increased.

CURRENT-LIMITED SERIES VOLTAGE REGULATOR (SEMICONDUCTOR)

Application.

The current-limited series voltage regulator is used as a regulated voltage supply for electronic equipments; it has a maximum current output limitation. This circuit is used to provide overload protection.

Characteristics.

Circuit output drops when a maximum output level is reached.

Voltage is constant up to the current limit.


Provides protection from current overload.

Base bias of regulator transistor is used to control output.

Circuit Analysis.

General. The current-limited series regulator operates as a conventional series constant-voltage regulator up to a specific current level, after which it operates effectively as a constant-current generator. Since the series voltage regulator is subject to instant damage in case of a short circuit or severe overload, the current-limiting feature automatically provides overload protection. Because circuit opening overload devices can cause voltage spikes or transients which can easily damage transistors, the current-limiting regulator circuit offers a more suitable arrangement for transistorized power supplies and regulators. Current limiting is usually accomplished by developing a control voltage which operates a diode and control transistor that reduce base current to the regulator diode and thus reduce the output.

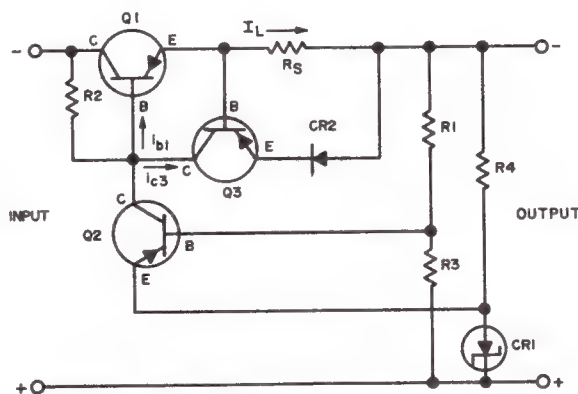Circuit Operation. The schematic of a simple current-limited voltage regulator is shown in the accompanying illustration.



Current-Limited Series Voltage Regulator

Examination of the schematic shows that the series regulator circuit is identical with the circuit described as the Base-Controlled Regulator, discussed earlier in this section of the handbook, except that a protective circuit involving transistor Q3, sensing resistor R_s , and switching diode CR2 has been added. Transistor Q1 is the series-regulating transistor, and Q2 is the control amplifier, with R2 as its collector resistor. Resistors R1 and R3 form the base bias voltage divider for control amplifier Q2, while breakdown diode CR1, together with current-limiting resistor R4, hold the emitter of Q1 at a fixed reference potential.

In normal operation, the base bias of control amplifier Q2 is varied above or below its normal value when the output voltage across R1 and R3 varies correspondingly. When the base bias of Q2 is increased, a larger collector current flows and develops a positive base bias across R2, which is applied to regulate Q1. A positive base bias on Q1 reduces current flow and increases the internal resistance between the emitter and collector of Q1, and the output voltage is reduced accordingly. Conversely, when the base bias increases, Q1 conducts heavier and a lower resistance between emitter and collector occurs, permitting the output voltage to increase. This is the normal operation of the voltage regulator, discussed in more detail in the Base-Controlled Voltage Regulator circuit description which appears earlier in this section of the Handbook. In this regulator circuit there is no protective arrangement, so that an overload or short circuit on the output will cause low output voltage, cause the base bias of Q1 to be increased to provide heavier current, and reduce the effective series resistance of the regulator. Hence, Q1 may be easily overloaded and burnt out.

It is at this point that the protective circuit consisting of Q3, CR2, and sensing resistor R_s begins to operate. Normally, switching diode CR2 is back-biased by leakage current through transistor Q3, and as the current through sensing resistor R_s increases, a positive voltage drop is produced across the resistor. At a definite current value, the voltage on the anode of CR2 becomes greater than the voltage applied to the cathode and forward-biases the diode into conduction. The emitter of Q3 is thus switched to a positive potential with respect to its base, produced by the voltage developed across R_s . The greater the emitter bias, the larger is the flow of collector current in Q3. Since the collector voltage of Q3 is supplied through R2, a positive base bias is developed on Q1 and automatically reduces current flow through Q1. Reducing the base bias of Q1 produces a higher effective collector-to-emitter resistance in Q1, and thus effectively places more resistance in series with the output. Hence, current flow through Q1 and R_s is restricted to a definite maximum value.

Actually, R2 is not essential to the operation of this circuit, since a flow of collector current through Q3 can also be obtained by reducing the collector current of Q2 and the base current of Q1 (if R2 is not used). A reduction of base current in Q1 means a reduction of drive, with a consequent reduction of

emitter current. When the overload is removed from Q1, the voltage on the anode of diode CR2 drops as the voltage across R_s decreases, until CR2 is again back-biased and effectively switched off. As a result, Q3 ceases conducting and returns the base bias of Q1 back to normal. Once again, Q2 resumes control of Q1 and regulates the output voltage. The current-limiting circuit operates only in one direction because of the switching action of diode CR2; Q3 remains inoperative until CR2 is forward-biased by excess current flow through R_s . Although the voltage drop across the series resistor will reduce the output voltage, it is usually on the order of a volt or two at maximum value, so that it has little effect on the total amount of output voltage.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low-voltage ranges of conventional voltmeters. Be careful also to observe the proper polarity when checking continuity, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. Lack of line voltage, an open transistor Q2 or series resistor R_s , a defective transistor Q3, or a defective control amplifier can cause loss of output. Check the line voltage to make certain that a blown primary fuse is not at fault. Measure the voltage across CR1 to determine whether the breakdown diode is operative; measure the resistance of R1, R2, R3, R4, and R_s . If control amplifier Q2 is shorted, the base bias on Q1 will probably be sufficient to bias off Q1 and prevent an output voltage. Transistor Q3 may also be defective and biasing off Q1.

Low Output. A constant low output can result from low line voltage, a defective series transistor Q1, a defective control circuit, or a defective protective circuit. Check the line voltage. If the output voltage remains low, check the breakdown voltage across diode CR1 and check the base bias of Q1 and Q2. If the breakdown voltage of CR1 is normal but the bias of Q2 is higher than normal, measure the value of R1 and R3. If the voltage of CR1 is other than normal, measure the value of R4 and check CR1. If the base bias is normal on Q2, measure the base bias on Q1. If this bias is lower than normal, measure the value of R2. If resistor R2 is satisfactory, the protective circuit may be faulty. If CR2 is excessively leaky or shorted, it will cause Q3 to operate and automatically

reduce the output. If the output still remains low, there is the possibility that control amplifier Q2 is defective.

High Output. Ordinarily, a defective control circuit or a defective series transistor Q1 can cause a high output. Such action is dependent upon heavier than normal conduction of Q1 to create a lower effective internal resistance from the emitter to the collector. With a current-limiting protective circuit, however, such a condition cannot happen except for currents which are lower than the limiting value, or unless the current-limiting circuit is inoperative. Q1 may be defective, or resistors R1, R2, R3 and R4, and diode CR1, or transistor Q2, may also be faulty.

HIGH-VOLTAGE SERIES STACK REGULATOR (SEMICONDUCTOR)

Application.

The high-voltage series stack type voltage regulator is used to regulate high voltage which exceeds the rated value for a single transistor. It is utilized in all types of semiconductor equipment using high-voltage power supplies.

Characteristics.

Each series stack transistor is of the same type, with equal voltage breakdown and current ratings.

A voltage divider is used to distribute the voltage equally across each transistor.

Only one stack transistor is directly controlled by the regulator circuit.

Uses a breakdown diode to ensure equal voltage distribution across each stack transistor.


Series regulator may use any type of control circuit.

Circuit Analysis.

General. When a high voltage which exceeds the transistor voltage rating is to be regulated, voltage breakdown may be prevented by using a number of series-connected transistors, in a stack arrangement, to reduce the voltage across each transistor to a value within the rating. A conventional base-controlled (or other type) series regulator is used to provide the voltage regulation, while the series stack of transistors is used to divide the high voltage equally across them. The simpler types use a resistive voltage divider to help equalize the voltage across each transistor of the

series stack. The more complicated circuits may use additional transistors to produce equal voltage distribution, and in addition, to provide temperature-compensating circuits.

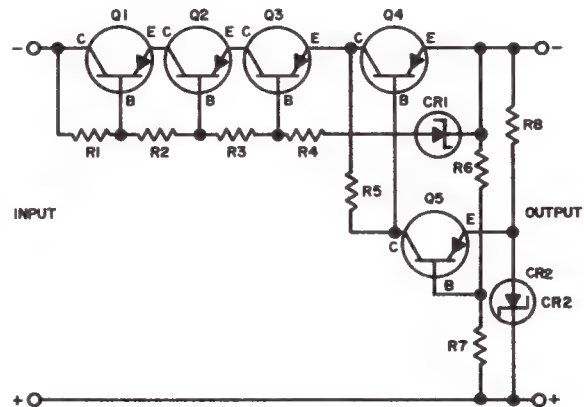Circuit Operation. A schematic of a typical high-voltage series stack regulator is shown in the accompanying illustration.



High-Voltage Series Stack Voltage Regulator

The high voltage transistor stack consists of transistors Q1, Q2, Q3, and Q4. Resistors R1, R2, R3, and R4, together with breakdown diode CR1, form a group of equalizing resistors connected as a series voltage divider. Resistor R5 is the collector resistor for control transistor Q5. Resistors R6 and R7 form a base bias voltage divider across the regulated output for control amplifier Q5. Resistor R8 is a current-limiting resistor for breakdown diode CR2, which holds the emitter bias of Q5 at a fixed value.

In normal operation, the base bias on transistor Q5 varies in accordance with the output voltage; when the output voltage increases the forward base bias also increases, and when the output voltage drops the forward bias decreases. As the forward bias increases, the collector current of Q5 also increases, and produces a positive voltage drop across R5. Thus a reverse bias is placed on the base of Q4. Since the base of Q4 is directly connected to the collector of Q5, an increase in collector current is obtained both through R5 and by reducing the base current of Q4. Reducing the base current of Q4 reduces the drive and has the same effect as reducing the base bias. Therefore, increasing the collector current of the Q5

control transistor reduces the base voltage and drive current of the Q4 regulator and reduces conduction. The reduced flow of emitter and collector current through Q4 effectively increases the internal emitter-to-collector resistance and produces a greater voltage drop across the transistor, reducing the output voltage.

When the output voltage drops, the forward bias applied to the base of Q5 from voltage divider R6 and R7 also reduces, and causes a reduction in collector current. The collector voltage of Q5 increases negatively, rising toward the supply voltage as the current flow through R5 decreases. Consequently, an increasing negative bias is applied to the base of regulator transistor Q4. The increased forward bias on Q4 causes an increased emitter current flow which reduces the effective internal resistance between the emitter and collector of Q4. Hence, less voltage drop occurs across the transistor, and the output voltage increases back to normal. Since all transistors in the stack are connected in series, the same current flows through each transistor. Therefore, it is only necessary to control directly one transistor (Q4) to control current flow through the stack.

Resistors R1, R2, and R3 are of equal value and are series-connected with R4 and breakdown diode CR1; therefore, a current determined by the total voltage drop across the stack (difference between input and output voltages) will flow through each resistor. With equal resistances and the same series current flow, equal voltage drops appear across each resistor. Thus, the bases of Q1, Q2, and Q3 have equal voltages applied, and R4 is chosen in conjunction with CR1 also to have an equal drop. Breakdown diode CR1 keeps the emitter of Q4 at a fixed voltage with respect to the base of Q3. Thus, when the output voltage increases, the voltage across the stack increases, and the collector-to-base voltage across each of the stack transistors increases. Since equal voltages appear across resistors R1, R2, and R3, equal voltages appear across transistors Q1, Q2, and Q3. Likewise, since R4 and CR1 are chosen to produce an equal voltage drop, the same drop appears across Q4, less the amount of breakdown voltage of CR1. Thus, the collector of Q4 and the emitter of Q3 are held at a small voltage difference from the emitter of Q4; it is this difference which provides the collector voltage for the regulator action of Q4. Consequently, the voltage drops across the four transistors are practically identical. When the control amplifier operates to

lower the base bias of Q4 and reduce the output voltage, the voltage across the stack is automatically reduced. With a lower collector-to-base voltage applied to Q1, Q2, and Q3, the base bias on these transistors is also reduced, and equal reduced current flow through each stack transistor produces approximately equal voltage distribution across each of the transistors.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low-voltage ranges of conventional volt-ohmmeters. Be careful also to observe proper polarity when checking continuity since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. An open-circuited series stack, defective transistors, breakdown diodes, or regulator control circuit can cause loss of output. If any of the series stack transistors is defective, the series circuit will be open and the only output will be the small output across breakdown diode CR1. Measure the line voltage first to be certain that a blown supply fuse is not at fault. Measure resistors R1, R2, R3, and R4 to determine if they are within tolerance. If there is input voltage present at the emitters of Q1, Q2, and Q3, but not at Q4, the control circuit is probably at fault, causing Q4 to be cut off. Transistor Q5 is most probably shorted.

Low Output. If transistors Q1, Q2, Q3, or Q4 are open, only the small breakdown voltage across CR1 will be obtained at the output. Check the line voltage to make certain the input is normal and that the power supply is not at fault. If either R1, R2, R3, or R4 is open the voltage will be below normal; check the resistance of each resistor for proper value. If diode CR2 is open, the bias on Q5 may be sufficient to reduce the output of Q4. Check diode CR2 and check the value of resistor R8. If R6 or R7 changes in value, the base bias of Q5 may be changed and cause a low output. Measure the values of R6 and R7; if they are satisfactory, regulator control transistor Q5 may be defective. Also check the value of collector resistor R5, as it may be open; in which case, Q5 can operate only by reducing the drive on the base of Q4.

High Output. A high output can be caused by one of the stack transistors shorting and producing less than the normal voltage drop. Measure the voltage from the emitter of each stack transistor to the posi-

tive terminal to determine where the high voltage exists. Check the base bias of Q5 to make certain that it has not decreased because of a change in resistors

R6 and R7. If the base bias is low, resistors R6 and R7, or transistor Q5, may be at fault. Also, check the value of R8 and the operation of diode CR2.

SECTION 4 FILTERS

PART 4-1. POWER SUPPLY

POWER-SUPPLY FILTERS


General.

While the output of most types of rectifiers is a pulsating direct current, most electronic circuits require a substantially pure direct current for operation. To provide this type of output, single- or multiple-section filter circuits (which effectively eliminate any alternating or ripple-voltage components by smoothing out the dc pulsations) are placed between the output of the rectifier and the load.

Filtering is accomplished with various combinations of resistors, inductors, and/or capacitors, usually arranged as a low pass filter. Inductor, as series impedances, oppose the flow of alternating (pulsating dc) current, while capacitors, as shunt elements, by-pass the alternating components that succeed in passing through the series impedances. (Resistors are used in the place of inductors for very low-current outputs.) The four basic types of filter circuits are the shunt-capacitor filter, the R-C capacitor-input filter, the L-C capacitor-input filter, and the L-C choke-input filter. A fifth type of filter, the resonant filter, employs one of the basic filter configurations in conjunction with a series-resonant, or parallel-resonant circuit.

Shunt-Capacitor Filters.

The shunt-capacitor filter (which is discussed more thoroughly later in this section) is the simplest type of filter. As shown in part A of the accompanying illustration, it consists of only a single filter element, capacitor C, connected across the rectifier in parallel with the load. In order to obtain good smoothing action when using this filter, the R-C time constant of the circuit should be large. Hence, both the capacitance and the load resistance should be large. Better filtering also results when the ripple frequency is high.

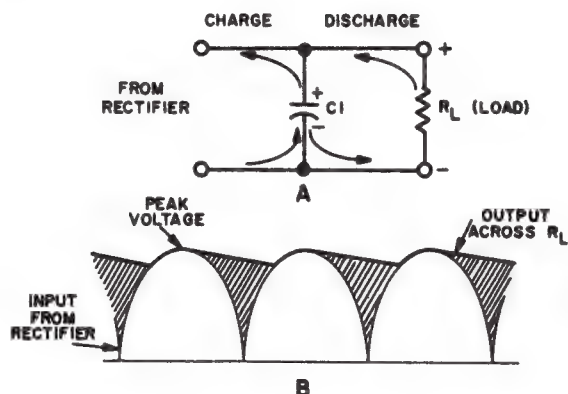

Shunt-Capacitor Filter and Associated Waveforms


Part B of the illustration shows the input and output waveforms of the shunt-capacitor filter, using a medium to large value of capacitance in a full-wave rectifier circuit. Capacitor C initially charges up to the peak value of the applied voltage and discharges through the load (R_L) between the rectified pulses. The charge and discharge of C is indicated in part A of the illustration as is the polarity of the voltage developed across the capacitor and the load.

The chief disadvantage of the shunt-capacitor filter is poor regulation, which precludes its use in most power supply applications. However, the advantages of simplicity and effectiveness recommend its use in some high-voltage applications in preference to more elaborate filters. It finds wide use in power supplies that furnish high-voltage anode potentials to cathode-ray and similar tubes where the current drain is insignificant.

R-C Capacitor-Input Filters.

The addition of a series resistor and a second shunt capacitor to the shunt-capacitor filter results in the basic R-C capacitor-input filter, as shown in the accompanying illustration. Because of its resemblance

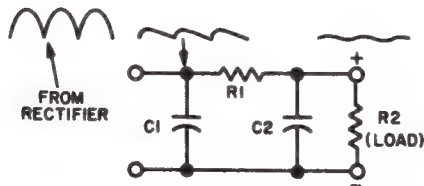to the Greek letter Pi (π), it is known as a *Pi-section* filter. The input to the filter is the output voltage from the rectifier developed across input capacitor C1. Typical waveforms of these voltages are included in the illustration.



R-C Capacitor-Input Filter and Associated Waveforms


Both the ac and dc components of the rectified current flow through series resistor R1. Because the reactance of C2 is small at the frequency of pulsation, most of the ac component flows through this capacitor and is bypassed to ground around the load resistor. The dc component flows through load resistor R2. The charging and discharging of C2, due to the passage of the pulsating component, results in a smoothing out of the ripple fluctuations, and a relatively pure direct current is delivered to the load, as is indicated by the output waveform.

The reduction in output voltage due to the excessive voltage drop across the series filter resistor when load current is high makes the R-C filter impracticable for most applications requiring even a moderate amount of current. This type of filter is used effectively in high-voltage, low-current applications. It is also commonly used as a decoupling network in multistage amplifier circuits.

L-C Capacitor-Input Filters.

The basic L-C capacitor-input filter has an identical configuration, and is similar in every respect to the R-C capacitor-input filter with one exception—a choke coil (iron-core inductor) replaces the series resistor in the Pi-section network, as shown in the accompanying illustration. The L-C capacitor-input filter is probably used to a greater extent than any other type of filter in power supply applications. The input to the filter section comprising L and C2 is the output voltage of the rectifier, developed across capacitor C1. Typical rectifier output and capacitor

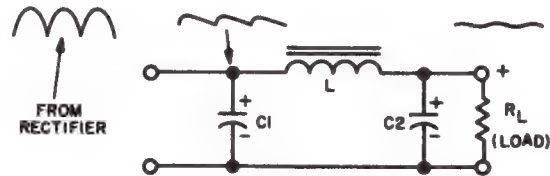C1 input voltage waveforms are included in the illustration. Inductor L and capacitor C2, working together, materially reduce the ac component remaining in the voltage across C1, and thus supply a substantially pure dc output voltage to the load.




L-C Capacitor-Input Filter and Associated Waveforms

As in the case of the shunt-capacitor filter, and also the R-C capacitor-input filter, the poor regulation of the L-C capacitor-input filter is a major disadvantage. In fact, assuming equal values of C, the regulation of a power supply using an L-C capacitor-input filter is actually worse than that of a power supply using a shunt-capacitor filter. An advantage of the capacitor-input filter is the provision of a much higher output voltage than can be obtained from a comparable filter of the choke-input type.

L-C Choke-Input Filters.

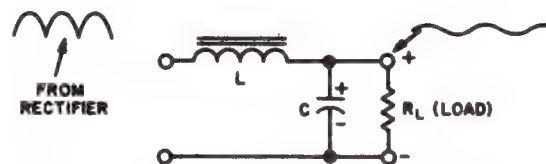With the elimination of capacitor C1, the L-C capacitor-input filter becomes an L-C choke-input filter. This type of filter, together with the associated waveforms, is illustrated below.



L-C Choke-Input Filter and Associated Waveforms

When rectified pulses are applied to the choke coil (series inductor L), the inductance opposes any change in current through the coil. Thus, the inductance of the coil acts to oppose any increase in current during the rapid positive excursion of the pulses, as well as any decrease in current during the

equally rapid negative excursion of the pulses. This action tends to keep a constant current flowing to the load throughout the cycle. Because of this, the pulsating voltage (resulting from the inductance effect) which is developed across capacitor C is maintained relatively constant at a value which approaches the average value of the input voltage. The low reactance presented by capacitor C to the pulsating component functions to decrease the ripple amplitude in the output and thereby to increase the average dc output voltage.


One disadvantage of the choke-input filter is the significantly lower output voltage of this type of filter as compared with the higher voltage provided by a comparable filter of the capacitor-input type. Another disadvantage, concerned with economics, is that for equivalent filtering, the choke-input filter must employ higher-value components than are required in the capacitor-input filter.

However, the advantage of lower peak currents in the choke-input system, which effects important savings in tube and transformer costs, somewhat offsets the second disadvantage mentioned in the preceding paragraph. Two additional advantages of the choke-input arrangement, in comparison with the capacitor input arrangement, are a greater power capability and much better dc voltage regulation.

Multiple-Section Filters.

To further enhance the filtering action and provide a smoother rectified output voltage (beyond that possible with the simple filter circuits discussed in the preceding paragraphs), one or more additional sections may be added to the basic filter circuit. The accompanying circuits illustrate two multiple-section filters. The capacitor-input type is shown in part A, and the choke-input type is shown in part B. Representative waveforms indicating the approximate shape of the voltage at several different points in each

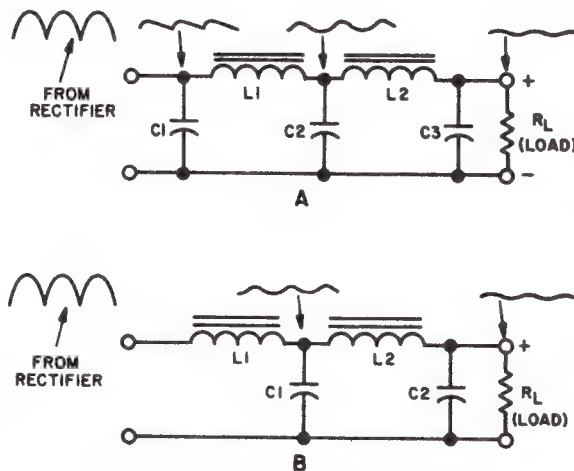type of multi-section filter are included in the illustration.




Multiple-Section Capacitor-Input and Choke-Input Filters

Multiple-section filters are effective in those applications where only a minimum ripple content can be tolerated in the rectified output voltage to the load. If the ripple attenuation ratio of one L-C section is 100 to 1, then an over-all 10,000-to-1 attenuation ratio will be obtained with two such sections, and a 1,000,000-to-1 attenuation ratio with three L-C sections. While additional filter sections do reduce the ripple component in the output to a minimum, they also result unfortunately, in reduced regulation. With additional sections, more resistance is placed in series with the power supply, which causes greater variations in the output voltage with variations in the load current. Most multiple-section filters consist of a combination of identical L-C sections. However,

multiple-section filters are not restricted to this type of design; combinations of L-C and R-C sections may be used effectively to satisfy specific filtering requirements in certain applications.

Resonant Filters.

Resonant filters are incorporated in the design of some power supply circuits. This type of filter is usually made up of two basic types of circuits. One common type of resonant filter uses a series-resonant (or a parallel-resonant) circuit in conjunction with one of more L-C filter sections. Another type employs a parallel-resonant circuit with shunt capacitors in a Pi-section filter arrangement. This type of resonant filter is shown in the accompanying illustration.

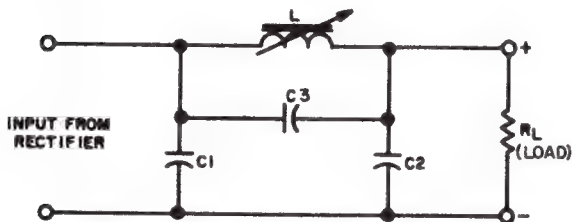

Resonant Filter

The parallel-resonant circuit, consisting of L and C, is tuned to the fundamental ripple frequency, and is connected in series with the output of the rectifier. Since this type of circuit presents an extremely high impedance at resonance, the fundamental-ripple-frequency component will therefore be greatly attenuated in the output voltage to the load.






Two serious disadvantages which limit the use of the resonant filter are as follows: (1) A change in the inductance of L with a change in load current results in detuning of the circuit, and thus a loss in its effectiveness. (2) Harmonics see a much lower impedance than the fundamental ripple frequency (since the circuit is tuned to the fundamental), and are therefore

less effectively attenuated. A conventional L-C filter section is sometimes added to the resonant filter shown in the illustration to offset the latter disadvantage.

Filter Output-Voltage Considerations.

The unfiltered output from a rectifier can be considered as a pulsating (ac) voltage superimposed on a dc voltage. The pulsating component of the rectified voltage is commonly referred to as *ripple*. The frequency components of the ripple and their amplitudes are the major factors which determine the amount of filtering required.



The accompanying illustration shows four typical rectifier output waveforms (part B, C, D, and E). For contrast, part A shows the smooth dc output of a battery. The frequency of voltage pulsation, or ripple frequency, is different for each of the rectifier output waveforms. The output of a single-phase, half-wave rectifier, shown in part B, produces pulsations at the frequency of the applied ac voltage. If the applied ac voltage has a frequency of 60 Hz, the frequency of the ripple component will also be 60 Hz. The output of a single-phase, full-wave rectifier, shown in part C, produces pulsations at twice the frequency of the applied ac voltage because both alternations of the input voltage are rectified. The output of a three-phase, half-wave rectifier, shown in part D, produces pulsations at three times the frequency of the applied voltage; the output of a three-phase, full-wave rectifier, shown in part E, produces pulsations at six times the frequency of the applied voltage. From a comparison of the four typical output waveforms, it can be seen that for an applied ac voltage of a given frequency, each of the rectifier circuits produces a different ripple frequency. Also, it will be noted that when the output pulses overlap (as shown in parts D and E), an increase in ripple frequency results in a decrease in ripple amplitude. As the ripple frequency is increased and the ripple amplitude is decreased, the rectifier output becomes easier to filter.

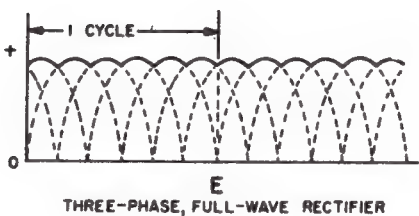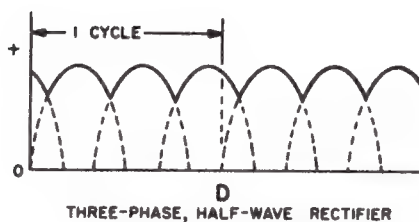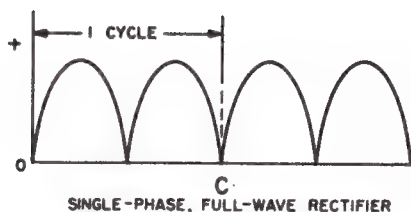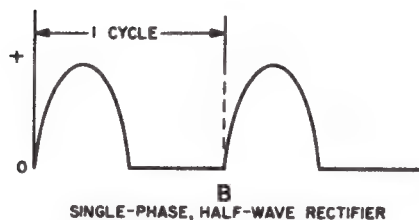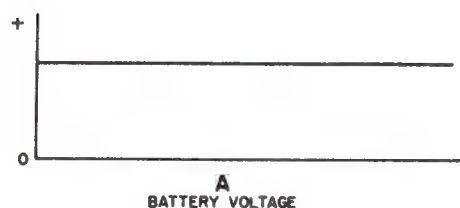

Typical Rectifier Output Waveforms Compared with Voltage Output of a Battery

It is desirable to furnish a voltage to the load which is free from any ripple component; however, there are several practical limitations (over-all regulation characteristics of the power supply; size, weight, and design of filter components; cost of components; etc) which influence the extent of filtering which is possible. Furthermore, the equipment design may tolerate a small percentage of ripple without any adverse effects upon equipment performance. As a result, the filtered output from the rectifier circuit may contain a small amount of residual ripple voltage which is applied to the load circuit.

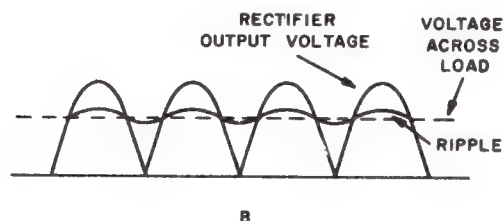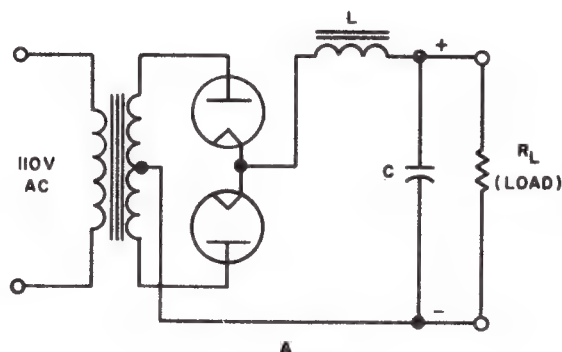Part A of the accompanying illustration shows a typical single-phase, full-wave rectifier system using a choke-input filter to provide dc voltage to a resistance load. The idealized curves of part B of the illustration show the shape of the output voltage from the rectifier, together with that of the voltage across the load. Since the output voltage of the rectifier can be considered as consisting of a dc component upon which is superimposed an ac ripple voltage, it can be shown that (by means of a Fourier analysis) the dc component of the output wave is $2/\pi$ times the peak value



Single-phase Full-wave Rectifier System and Associated Output Voltage Waveform

of the ac input wave. The lowest frequency component of ripple in the output is twice the input frequency and two-thirds the magnitude of the dc component of the output voltage. The remaining ripple components are harmonics of this lowest-frequency component, and rapidly diminish in amplitude as the order of harmonics is increased. This is graphically illustrated in the accompanying tabulation, which provides pertinent characteristics of three of the four rectifiers considered in this discussion.

Characteristics of Three Typical Rectifier Circuits Having Choke-Input Filter Systems

Note: Relative voltage amplitudes are with reference to the dc component of output voltage, taken as 1.0.	Rectifier Circuit		
	Single-Phase, Full-Wave (Center-tapped)	Three-Phase, Half-Wave	Three-Phase, Full-Wave
a. RMS value of transformer secondary voltage (one-half)	1.11	0.855	0.428
b. Maximum inverse voltage	3.14	2.09	1.05
c. Lowest frequency in rectifier output (F = frequency of applied ac voltage)	2F	3F	6F
d. Peak value of first three ac components of rectifier output (ripple frequency):			
Fundamental	0.667	0.250	0.057
Second harmonic	0.133	0.057	0.014
Third harmonic	0.057	0.025	0.006
e. Ripple peaks with reference to dc axis:			
Positive peak	0.363	0.209	0.0472
Negative peak	0.637	0.395	0.0930

In addition to the ripple frequencies present and their respective magnitude, another very important factor which must also be considered is the amount factor which must also be considered is the amount (percentage) of residual ripple that can be tolerated by the equipment which uses the filtered voltage from the rectifier system. The effectiveness of the filter circuit in this respect is determined from the ratio of the rms value of the ripple voltage to the

average value of the output voltage. This ratio is expressed as percentage of ripple, as follows:

$$\text{Percentage of ripple} = \frac{E_r}{E_{av}} \times 100$$

Where: E_r = effective (rms) value of ripple voltage

E_{av} = average value of output voltage

As a sine wave, the effective (rms) value of ripple voltage can be expressed by the following equation:

$$E_r = 0.354 (e_{\max} - e_{\min})$$

(Refer to preceding tabulation of rectifier voltage relations for percentage values of $e_{\max}$ and $e_{\min}$.) An alternate way of stating the percentage of ripple, which may be found preferable in some instances, is (for a single-section filter) as follows:

$$\text{Percentage of ripple} = \frac{mX_C}{(X_L - X_C)}$$

where: X_C = filter capacitance reactance
 X_L = filter inductive reactance
 C = filter capacitance in microfarads
 L = filter inductance in henries

The factor m equals 70 for a single-phase, full-wave rectifier, 24 for a three-phase, half-wave rectifier, and 5 for a three-phase, full-wave rectifier.

For a double-section filter, the expression becomes:

$$\text{Percentage of ripple} = \frac{mX_C^2}{(X_L - X_C)^2}$$


In a filter system, as the frequency of the applied voltage is increased (in this case a ripple voltage), the reactance of a shunt capacitor decreases and the reactance of a series inductance increases. The means that the filtering effectiveness of any filter made up of shunt capacitance and series inductance is increased as the frequency of the applied voltage is increased; thus, at the higher ripple frequencies, filter components of smaller size and lighter weight can be

used to provide the same degree of filtering as can be obtained at lower ripple frequencies with filter components of larger size and heavier weights.

Voltage Regulation.

The output voltage of a power supply decreases as the load current increases because of losses occurring in the various resistances in the rectifier and filter circuit. The accompanying illustration compares the voltage output for varying load currents from a rectifier for a simple capacitor-input filter and for a choke-input filter. In each case, the same type of tube and transformer are used in a center-tapped full-wave circuit to supply power to an identical resistance load. It is immediately apparent, when comparing the two curves on the graph, that while the output voltage for each value of load current is higher for the capacitor-input arrangement, the regulation of the power supply is far greater for the choke-input filter.

Further study of the curves reveals that in the case of the capacitor input, a change in load current from around 25 milliamperes to 250 milliamperes results in a drop in output voltage from 600 to 425 volts, or a total drop of 175 volts. For the same change in load current in the case of the choke input, the dc output voltage drops from 400 volts to 350 volts, or a total of only 50 volts (as compared with the 175 volts for the capacitor input).

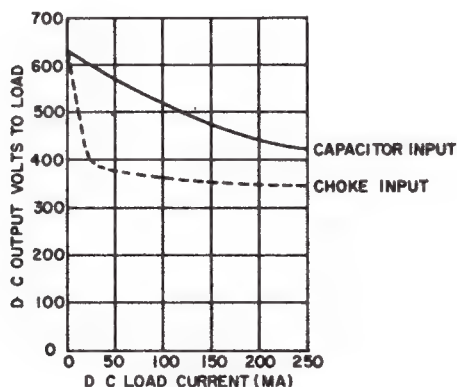

Comparison of Voltage-Regulation Characteristics for Capacitor-Input and Choke-Input Filters

Voltage regulation is a measure of the degree to which a power supply maintains its output-voltage stability under varying load conditions. The amount of change in the output voltage between the no-load and full-load conditions is usually expressed in terms of the percentage of voltage regulation. The percentage of voltage regulation is defined as the ratio of the difference between the no-load and full-load output voltages to the full-load output voltage, times 100. This can be expressed as follows:

$$\text{Percentage of voltage regulation} = \frac{(E_1 - E_2)}{E_2} \times 100$$

where: E_1 = no-load output voltage
 E_2 = full-load output voltage

An ideal power supply would have zero internal resistance (impedance), and the percentage of regulation would be zero because there would be no difference between the output voltage for the no-load and full-load conditions. However, since this is not practicable, then the lower the percentage of regulation the better the power supply and the nearer the supply approaches an ideal supply. Well-designed power supplies generally have a regulation of 10 percent or less.

The regulation of the choke-input filter is always better than that of the capacitor-input filter, provided that some minimum value of load current flows through the choke at all times. Under this condition, the output voltage changes only slightly with small changes in load current. However, if the load current is reduced to approach a no-load condition, the choke cannot prevent the associated filter capacitor from charging to the peak value of the applied voltage; thus, the output voltage rises to its maximum value. If the load current is normally a low value, or if the load current varies between zero and a low value, the regulation will be poor as compared with the same circuit operating with a slightly greater load current. When this is the case, an additional load in the form of a resistor, called a *bleeder resistor*, is placed across the output of the filter to improve the regulation and establish a minimum value of load current for the supply. This minimum value of current, which flows

through the filter choke, improves the regulation of the power supply. The value of the current drawn by the bleeder resistor is usually 10 to 15 percent of the total current available from the supply.

The bleeder resistor across the output terminals of the power supply not only assists in maintaining good voltage regulation, but also prevents the capacitors in the filter system from charging up to the peak value of the applied voltage. In addition, the bleeder reduces the possibility of electrical shock to personnel, because the capacitors will discharge through the bleeder resistor after the power supply has been turned off. In many power supplies the bleeder resistor takes the form of a voltage divider, either a tapped resistor or a number of series resistors selected so that several values of output voltage can be supplied to various loads having different voltage and current requirements.

Filter Capacitors.

A common type of capacitor used as a filter element in many receiver-type power-supply circuits is the dc electrolytic capacitor. Within the container of the electrolytic capacitor, rolled aluminum-foil plates are immersed in an electrolyte which is commonly an aqueous solution of boric acid and sodium borate. The actual dielectric in this type of capacitor is the thin oxide film which forms on one set of plates in the presence of a dc polarizing voltage. The aluminum foil acts as the anode (positive terminal), and the electrolyte acts as the cathode (negative terminal) of the electrolytic capacitor.

There are two general types of electrolytic capacitors—the wet type and the dry type. The physical characteristics of the electrolyte used determines the particular type of capacitor. The wet type uses an aqueous electrolyte in a metal container; the dry type uses a viscous or paste electrolyte, and is available in either a paper (cardboard) or metal container.

The most common working voltages for electrolytic capacitors (both types) run between 6 and 600 volts. Practical values of capacitance run anywhere from 1 or 2 microfarads to as high as 2000 microfarads, the particular value depending on the requirements of a given application.

In keeping with the necessity for a wide range of working voltage and capacitance values, electrolytic capacitors are available in a variety of physical sizes.

Generally speaking, the higher the voltage and the greater the capacitance, the larger the physical size. For low-voltage applications, much greater capacitance is provided in units of smaller size than paper-type capacitors (which provide only about one ten-thousandth as much capacitance).

Multiple-section electrolytic capacitors, which have two or more capacitor units housed in a single container, are extensively used in receiver power-supply circuits. For example, a Pi-section filter circuit may use a dual-section electrolytic capacitor having two 8-microfarad sections, one connected on each side of the series filter element. However, the capacitance of the different sections need not be the same. In a typical three-section capacitor, for instance, each section may have a different capacitance, or two sections may have the same value and the third section of different value. Any number of combinations are possible, and standardization is the exception rather than the rule.

In addition to the electrolytic capacitor many other nonpolarized types of capacitors are in use; for example: paper-foil, wax-impregnated or oil-impregnated, oxide film, mica, and ceramic. For high-voltage applications such as transmitter power supplies, the individual units are larger and have insulated bushing-type terminals. The higher the voltage, the larger the unit for a given capacitance. Paper-foil types are generally used at voltages from 750 to 2500 volts. Oil-impregnated types are used for voltages of 1500 to 3500 volts (up to 30 kv for large commercial installations). Mica and ceramic capacitors are generally used as blocking capacitors or in tuned filters, since their size is usually limited to values less than 0.25 microfarad. Small, hand-portable equipments sometimes use series-connected receiving or low-voltage-type electrolytic capacitors for economy (the price of two low-voltage units is considerably lower than on high-voltage unit). Since the introduction of transistors, extremely low-voltage (2, 4, 6, and 12-volt) capacitors of very small physical size, with capacitance values on the order of 50, 100, and 150 microfarads or more, are in common use to supply high currents at the low voltages employed. These capacitors are used in power supplies which eliminate the necessity for, and expense of, battery replacement.

SHUNT-CAPACITOR FILTER

Application.

The shunt-capacitor filter, as previously stated, is the simplest type of filter. The application of this filter is very limited; it is sometimes used in extremely high-voltage, low-current power supplies for cathode-ray and similar electron tubes which require very little load current from the supply. This filter is also used in applications where the power-supply ripple frequency is relatively high, e.g., to filter the output of a dynamotor.

Characteristics.

Capacitance and load-resistance values must be high (large R-C time constant required).

Load current must be relatively small if filter is to have good regulation.


Filtering efficiency increases as ripple frequency is increased.

Regulation of rectifier-type power supply is poor with this type of filter; voltage regulation depends mainly on value of capacitor.

Circuit Analysis.

General. The rectifier circuits previously described in this section of the handbook provide a rectified output voltage, across the load resistance, which has a pulsating waveform. The accompanying illustration shows a simple shunt-capacitor filter and the waveforms obtained when the input to the filter is ob-

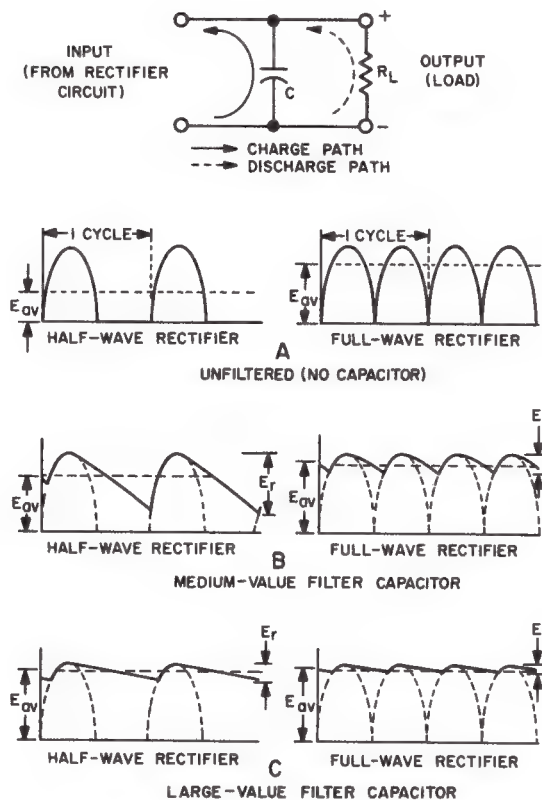tained from either a half-wave or a full-wave (single-phase) rectifier circuit.



Shunt-Capacitor Filter and Waveforms

The waveforms given in part A of the illustration represent the unfiltered output (without capacitor C) from the rectifier circuit when current pulses flow through the load resistance, R_L each time the rectifier conducts. Note that the dashed line indicating the average value of output voltage, E_{av} for the half-wave rectifier is less than half (approx 0.318) the amplitude of the voltage peaks; the average value of output voltage, E_{av} , for the full-wave rectifier is greater than half (approx 0.637), but is still much less than the maximum peak amplitude of the applied waveform. With no capacitor connected across the output of the rectifier circuit, the waveform has a large value of pulsating component as compared with the average (or dc) component.

When a capacitor is connected across the output of the rectifier (across load resistor R_L), the average value of output voltage, E_{av} , will be increased because of the filtering action of the capacitor. In part B of the illustration a capacitor of medium value is placed in shunt (parallel) with the load resistance, R_L . The value of the capacitor is fairly large; it thus presents a relatively low reactance to the pulsating current and stores a substantial charge. The rate of charge for the capacitor is limited only by the impedance of the ac source (transformer) and the internal resistance of the rectifier, both of which are relatively low; therefore, the R-C charge time for the circuit is relatively short. As a result, when the pulsating voltage is first applied to the shunt-capacitor filter, the capacitor charges rapidly and almost reaches the peak voltage within the first few cycles. The charge on the capacitor approximates the peak value of the rectified voltage when the rectifier is conducting, and tends to retain its charge when the rectifier output falls to zero (since the capacitor cannot discharge immediately). The capacitor slowly discharges through the load resistance, R_L , during the time the rectifier is nonconducting.

The rate of discharge for the capacitor is determined by the load resistance; if the capacitor and load-resistance values are large, the R-C discharge time for the circuit is relatively long. From the waveforms shown in part B of the illustration, it can be seen that the addition of capacitor C to the circuit results in an increase in the average value of output voltage, E_{av} , and a reduction in the ripple component, E_r , present across the load resistance.

As previously stated, the capacitor partially discharges through the load, dropping the output voltage

until the next positive pulse occurs; when the amplitude of this pulse exceeds the value of voltage of the capacitor, the capacitor once again starts charging to the peak value.

If the value of the capacitor used in the filter circuit is increased, the average value of the output voltage, E_{av} , is also increased. In part C of the illustration, the effect of increasing the value of capacitor C (over that used in part B) is shown. The time constant of the charging circuit is still relatively short, but the time constant of the discharging circuit is considerably greater. Because of the increased discharge time constant, the large value capacitor does not discharge as rapidly as the medium-value capacitor; therefore, the average voltage is higher and the amplitude of the ripple component, E_r , is decreased.

Compare the increased filtering action shown in the waveform of part C with that of part B. Theoretically, the shunt-capacitor filter can provide any desired degree of filtering; the larger the value of capacitor C, the better the filtering action, because of the lowered impedance (X_C) offered to the pulsating component and the ability of the capacitor to retain a charge longer because of the increased R-C discharge time constant. However, there is a practical limitation to the maximum value of the capacitor used in the filter. If the peak-current rating of the rectifier is exceeded during the charging time for the capacitor, the rectifier will be damaged; thus, a compromise in the value of the capacitor is necessary in order to keep the maximum charging current within the peak-current rating of the rectifier.

The load resistance is also an important consideration. If the load resistance is made small, the load current increases and the average value of output voltage (E_{av}) decreases. The R-C discharge time constant is a direct function of the value of the load resistance; therefore, the rate of capacitor voltage discharge is a direct function of the current through the load. The greater the load current, the more rapid the discharge of the capacitor, and the lower the average value of output voltage. For this reason, the shunt-capacitor filter is seldom used with rectifier circuits that must supply a relatively large load current.

The pulsations across capacitor C and load resistance R_L , no matter how small in amplitude, are in effect a form of distortion. Although these pulsations represent a fundamental frequency, many other frequency components are also present in the output. In the majority of equipment applications, the presence

of a ripple-voltage component is not desirable; therefore, for most equipment application it is impracticable to use a simple shunt-capacitor filter; additional filtering (or another type of filter) is necessary to reduce the ripple amplitude to an acceptable minimum.

Circuit Operation. Consider now a complete cycle of operation, using a single-phase, half-wave rectifier operating with shunt capacitor C and load resistance R_L , shown in the preceding illustration. Capacitor C is assumed to be large enough to insure small reactance to the pulsating rectified current. The resistance of R_L is assumed to be much greater than the reactance of C at the input frequency.

When the circuit is energized, the rectifier conducts on the positive half of the cycle, and current flows into and charges capacitor C to approximately the peak value of the input voltage. The charge is less than the peak value of voltage by the amount of the voltage drop across the rectifier tube. The charge on C is indicated by the heavy lines on the waveforms in parts B and C of the illustration.

On the negative half-cycle the rectifier cannot conduct, since the plate is negative with respect to the cathode. During this interval, capacitor C discharges through load resistance R_L . The discharge of C produces the downward slope of the heavy lines in parts B and C of the illustration. In contrast to the abrupt fall of the applied ac voltage from peak value to zero (shown in dotted lines), the voltage across C (and thus across R_L) during the discharge period decreases at a gradual rate until the time of the next half-cycle of rectifier operation. For a given value of load current, the value of C determines the rate at which the discharge voltage decreases. This rate of voltage decline and the value of C are inversely related. Thus the rate is greater for smaller values of C and less for greater values of C . This indicates that for the same load current, if C (or R_L) is increased, the ripple component in the output to the load is decreased. (A longer time constant requires a longer time to charge and discharge.)

Since practical values of C and R_L insure a more or less gradual decrease of the discharge voltage, a substantial charge remains on the capacitor at the time of the next half-cycle of operation. As a result, no current can flow the rectifier until the rising ac input voltage on the rectifier plate exceeds the voltage of the

charge remaining on C , because this charge voltage is the cathode-to-ground potential of the rectifier tube. When the plate voltage exceeds the charge voltage across C , the rectifier again conducts, and again charges C to approximately the peak value of the applied voltage. Shortly after the charge on the capacitor reaches its peak value, the tube stops conducting. Because the fall of the ac input voltage on the plate is considerably more rapid than the decrease in the capacitor voltage, the cathode quickly becomes more positive than the plate, and the rectifier ceases to conduct. During the charging period, capacitor C is connected across the output of the rectifier, and the charge time is determined by the effective series resistance, which is only that of the tube plate-to-cathode (forward) resistance and the transformer impedance, plus that of the leads to the tube and capacitor. Hence, the resistance is low and C charges very quickly. During the nonconducting period, the discharge path is through R_L , which is relatively large, so that the time constant is long. Thus capacitor C does not discharge appreciably before the conduction cycle again begins.

The repeated charge and discharge of capacitor C (as described above) with the respective rise and fall of the input voltage constitutes the basic filtering action of this circuit. To reduce the ripple amplitude and increase the dc component in the output voltage, capacitor C charges up and stores energy when the tube is conducting and discharges to furnish current to the load when the tube is nonconducting.

Using Ohms law, $R = \frac{E}{I}$, it is evident that a heavy

current drain, for the same output voltage, represents a lower load resistance. Therefore, with a heavy load and lower R_L , capacitor C discharges more quickly. Since the output voltage represents the average charge retained in the capacitor, it can be seen that with heavy loads the capacitor will discharge further between the periods of tube conduction. Hence, the output voltage will also be lower. This is why the single-capacitor filter is used only for very light current drains. Since the output voltage for heavy loads is lower and the output ripple voltage component is also higher, the effective filtering is good only for light loads.

Failure Analysis.

General. With the supply voltage removed from the input to the filter circuit, one terminal of the filter capacitor can be disconnected from the circuit. The capacitor should be checked, using a capacitance analyzer, to determine its effective capacitance and leakage resistance. During these checks it is very important, when the capacitor is electrolytic, that correct polarity be observed. A decrease in effective capacitance or losses within the capacitor can cause the output to be below normal and also cause excessive ripple amplitude.

If a suitable capacitance analyzer is not available, an indication of leakage resistance can be obtained by using an ohmmeter. Resistance measurements can be made across the terminals of the capacitor to determine whether it is shorted, leaky, or open. When testing electrolytic capacitors, set the ohmmeter to the high range and connect the test prods across the capacitor, being careful to observe polarity. This is important because current flows with less opposition through an electrolytic capacitor in one direction than in the other. If the current polarity is not observed, an incorrect reading will result. When the test prods are first connected, a large deflection of the meter takes place, and then the pointer returns slowly toward the infinite-ohms position as the capacitor charges. For a good capacitor with a rated working voltage of 450 volts, dc, the final reading on the ohmmeter should be over 500,000 ohms. (A rough rule of thumb for high-voltage capacitors is at least 1000 ohms per volt.) Low-voltage electrolytic capacitors (below 100 volts rating) should indicate on the order of 100,000 ohms.

If no deflection is obtained in the ohmmeter when making the resistance check explained above, an open-circuited capacitor is indicated.

A steady full-scale deflection of the pointer at zero ohms indicates that the capacitor being tested is short-circuited.

An indication of a leaky capacitor is a steady reading on the scale somewhat between zero and the minimum acceptable value. (Be certain this reading is not caused by an in-circuit shunting part.) To be valid, these capacitor checks should be made with the capacitor completely disconnected from the circuit in which it operates.

In high-voltage filter capacitor applications, paper and oil-filled capacitors are used, as also are mica and

ceramic capacitors (for low-capacitance values). In this case, polarity is of no importance unless the capacitor terminals are marked + or -. It is, however, good maintenance practice to use the output polarity of the circuit as a guide, connecting positive to positive and negative to negative. Thus any effects of polarity on circuit tests are minimized and the possibility of damage to components or test equipment is avoided. *Remember-* an undischarged capacitor retains its polarity and holds its charge for long periods of time. To be safe, discharge the capacitor to be tested with the *power OFF* before connecting test equipment or disconnecting the capacitor.

R-C CAPACITOR-INPUT FILTER**Application.**

The R-C capacitor-input filter is limited to applications in which the load current is small. This type of filter is used in power supplies where the load current is constant and voltage regulation is not necessary, such as in the high-voltage power supply for a cathode-ray tube or as part of a de-coupling network for multistage amplifiers.

Characteristics.

Filter is composed of shunt input capacitor, series resistor, and shunt output capacitor.

Filtering efficiency increases as ripple frequency is increased.


Output current is much less than that obtained corresponding filter which uses a choke instead of a resistor.

Regulation of rectifier-type power supply is poor with this type of filter; requires relatively constant load current.

Rectifier peak current is high with this circuit because of input capacitance.

Circuit Analysis.

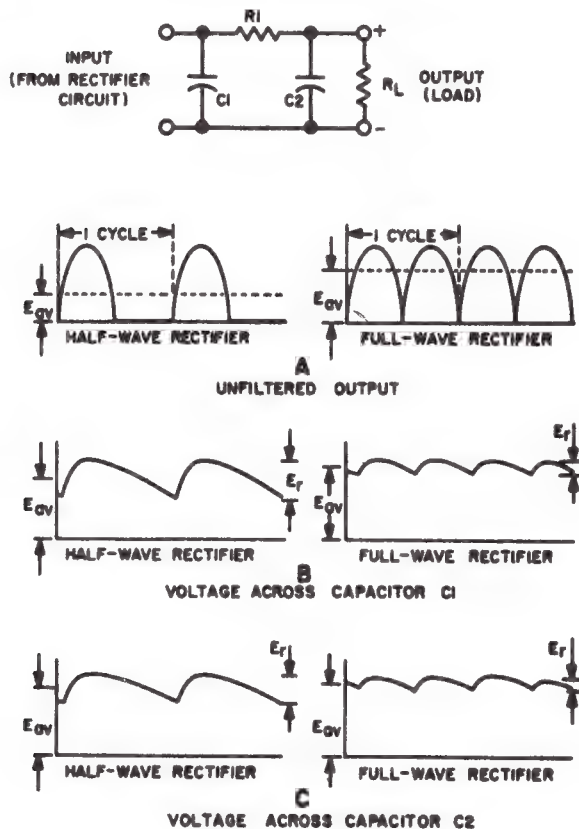General. The rectifier circuits previously described in this section of the handbook provide a rectified output voltage (across the load resistance) which has a pulsating waveform. The accompanying illustration shows an R-C capacitor-input filter and the waveforms obtain from either a half-wave or a full-wave (single-phase) rectifier circuit.



R-C Capacitor-Input Filter and Waveforms

The waveforms shown in part A represent the unfiltered output from a typical rectifier circuit when current pulses flow through the load resistance each time the rectifier conducts. Note that the dashed line indicating the average value of output voltage, E_{av} , for the half-wave rectifier is less than half the amplitude of the voltage peaks (approx 0.318). The average value of output voltage, E_{av} , for the full-wave rectifier is greater than half (approx 0.637), but is still much less than the peak amplitude of the rectifier-output waveform. With no filter circuit connected across the output of the rectifier circuit (unfiltered), the waveform has a large value of pulsating component as compared with the average (or dc) component.

The RC filter shown in the schematic of the illustration consists of an input filter capacitor, $C1$, a series resistor, $R1$, and an output filter capacitor, $C2$.

This filter is called an *R-C capacitor-input filter*, and is sometimes referred to as an *R-C Pi-section filter* because the configuration of the schematic resembles the Greek letter π .

Capacitor $C1$ is placed at the input to the filter, and is in shunt with the output of the rectifier circuit; capacitor $C1$ has the same filtering action in this circuit that the capacitor does in the Shunt-Capacitor Filter, described earlier in this section of the handbook. In the capacitor-input filter, the major portion of the filtering action is accomplished by the input capacitor, $C1$. The average value of voltage across capacitor $C1$ is shown in part B of the illustration for half-wave and full-wave rectifier circuits. Note that the average value of voltage across capacitor $C1$ is greater than the average value of voltage for the unfiltered output of the rectifier, shown in part A. The value of the input capacitor is relatively large in order to present a low reactance (X_C) to the pulsating current, and to store a substantial charge. The rate of charge for the input capacitor is limited only by the impedance of the ac source (transformer) and the internal (or forward) resistance of the rectifier, both of which are relatively low; therefore, the R-C charge time constant for the input circuit is relatively short. As a result, when the pulsating voltage is first applied to the capacitor-input filter, capacitor $C1$ charges rapidly and reaches the peak voltage within the first few cycles. The charge on capacitor $C1$ approximates the peak value of the pulsating voltage when the rectifier is conducting, but when the rectifier output falls to zero, the capacitor partially discharges through the series resistor, $R1$, and the load resistor, R_L during the time the rectifier is nonconducting. The larger the value of the input capacitor, $C1$, the better the filtering action; however, there is a practical limitation to maximum value of the capacitor. If the peak-current rating of the rectifier is exceeded during the charging time for the capacitor, the rectifier will be damaged; for this reason, a compromise in the value of the input capacitor is necessary in order to keep the maximum charging current within the peak-current rating of the rectifier.


The R-C capacitor-input filter is similar to the L-C Chunt-Capacitor Filter, described later in this section, except that a resistor is used in place of the series inductor. Although the series resistor affords filtering action, a resistor can never be as effective as an inductor unless a considerable dc voltage drop can be

tolerated. However, the RC capacitor-input filter circuit is an improvement over the shunt-capacitor filter, described earlier in this section, because additional filtering results from the added reactances of resistor R1 and capacitor C2.

The pulsating output from the rectifier circuit, which is applied to the input of the filter, can be considered as being composed of two components: an ac component, represented by pulsations, and a dc component, represented by the average value of voltage (E_{av}). Because these pulsations occur at a relatively low frequency (which is the input frequency for a half-wave rectifier, or a multiple of the input frequency for full-wave and other types of rectifiers), the value of the shunt capacitors, C1 and C2, is purposely made large so that their reactances are very low at the pulsating (ripple) frequency. Both the ac and dc components of the rectifier output (present at the input to the filter) flow through the filter resistor, R1; therefore, a voltage drop occurs across R1, which results from the voltage-divider action of resistor R1 in series with the parallel combination of capacitor C2 and load resistance R_L . Since the reactance of C2 is very low at the ripple frequency, most of the ac component bypasses the load resistance, R_L , and the dc component flows through the load resistance. The efficiency of the filter depends, to a great extent, upon keeping the reactance of capacitor C2 very small as compared with the load resistance, R_L . The charging and discharging of capacitor C2 tends to smooth out the voltage fluctuations and reduce the ripple amplitude (E_r) applied to the load. The final result is the waveform shown in part C of the illustration. The average value of voltage developed across capacitor C2 and load resistance R_L is always less than the average value of voltage across capacitor C1, because of the voltage drop occurring across the filter resistor, R1. When the load current is even moderate, an R-C filter is not normally used, because the voltage drop across the series resistor, R1, becomes excessive for most applications.

The output from a Pi-section R-C filter may contain an amount of ripple which is considered excessive for the equipment application. By adding another series filter resistor, R2, and a shunt capacitor, C3, to the basic capacitor-input filter, the ripple component across the load resistance can be further attenuated. However, the addition of series resistors increases the voltage drop within the filter, resulting in poorer regulation and a decrease in output voltage.

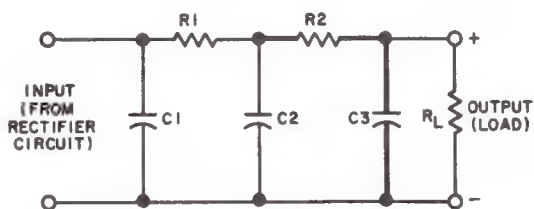For these reasons, the number of sections that may be added, as well as the size of the resistors, is limited. As shown in the accompanying illustrations, the added R-C filter components, R2 and C3, resemble an inverted letter L. For this reason it is referred to as an L-Section filter.



Capacitor-Input Filter with L-Section Added

Failure Analysis.

General. The shunt capacitors are subject to open circuits, short circuits, and excessive leakage; the series filter resistors are subject to changes in value and, occasionally, to open circuits. Any of these troubles can be easily detected.

The input capacitor has the greatest pulsating voltage applied to it, is the most susceptible to voltage surges, and has a higher average voltage applied; as a result, the input capacitor is frequently subject to voltage breakdown and shorting. The remaining shunt capacitor(s) in the filter circuit is not subject to voltage surges because of the protection offered by the series filter resistor(s); however, a shunt capacitor can become open, leaky, or shorted.

Shorted capacitors or an open filter resistor will result in a no-output indication. An open filter resistor will result in an abnormally high dc voltage at the input to the filter and no voltage at the output of the filter. Leaky capacitors or filter resistors that have increased in value will result in a low dc output voltage. Open capacitors, capacitors which have lost their effectiveness, or filter resistors that have decreased in value will result in an excessive ripple amplitude in the output of the supply.

With the supply voltage removed from the input to the filter circuit, one terminal of each capacitor can be disconnected from the circuit. Each capacitor should be checked, using a capacitance analyzer, to determine its effective capacitance and leakage resistance. It is important, when the capacitor is electrolytic, that correct polarity be observed at all times.

A decrease in effective capacitance or losses within the capacitor can cause the output to be below normal and also cause excessive ripple amplitude. The value of resistors can be checked by using an ohmmeter.

If a suitable capacitance analyzer is not available, an indication of leakage resistance can be obtained by using an ohmmeter. Resistance measurements can be made across the terminals of the capacitor to determine whether it is shorted, open, or leaky. When testing electrolytic capacitors, set the ohmmeter to the high range and connect the test prods across the capacitor, being careful to observe polarity. This is important because current flows with less opposition through an electrolytic capacitor in one direction than in the other. If the correct polarity is not observed, an incorrect reading will result. When the test prods are first connected, a large deflection of the meter takes place, and then the pointer returns slowly toward the infinite-ohms position as the capacitor charges. For a good capacitor with a rated working voltage of 450 volts, dc, the final reading on the ohmmeter should be over 500,000 ohms. (A rough rule of thumb for high-voltage capacitors is at least 1000 ohms per volt.) Low-voltage electrolytic capacitors (below 100 volts rating) should indicate on the order of 100,000 ohms.

If no deflection is obtained on the ohmmeter when making the resistance check explained above, an open-circuited capacitor is indicated.

A steady full-scale deflection of the pointer at zero ohms indicates that the capacitor being tested is short-circuited.

An indication of a leaky capacitor is a steady reading on the scale somewhere between zero and the minimum acceptable value. (Be certain this reading is not caused by an in-circuit shunting part.) To be valid, these capacitor checks should be made with the capacitor completely disconnected from the circuit in which it operates.

In high-voltage filter capacitor applications, paper and oil-filled capacitors are used, as also are mica and ceramic capacitors (for low-capacitance values), in this case, polarity is of no importance unless the capacitor terminals are marked + or -. It is, however, good maintenance practice to use the output polarity of the circuit as a guide, connecting positive to positive and negative to negative. Thus any effects of polarity on circuit tests are minimized and the possibility of damage to components or test equipment is

avoided. *Remember*—an undischarged capacitor retains its polarity and holds its charge for long periods of time. To be safe, discharge the capacitor to be tested with the *power OFF* before connecting test equipment or disconnecting the capacitor.

L-C CAPACITOR-INPUT FILTER

Application.

The L-C capacitor-input filter is one of the most commonly used filters. This type of filter is used primarily in radio receiver and small audio amplifier power supplies, and in any type of power supply where the output current is low and the load current is relatively constant.

Characteristics.

Filter is composed of shunt input capacitor, series inductor, and shunt output capacitor.

Filtering efficiency increases as ripple frequency is increased.

Output voltage is greater than that of choke-input filter; output current is less than that of choke-input filter.


Regulation of rectifier-type power supply is only fair with this type of filter; requires relatively constant load current.

Rectifier peak current is high with this circuit because of input capacitance.

Circuit Analysis.

General. The accompanying illustration shows an L-C capacitor-input filter and the waveforms obtained from either a half-wave or a full-wave (single-phase) rectifier circuit.

The waveforms shown in part A represent the unfiltered output from a typical rectifier circuit when current pulses flow through the load resistance each time the rectifier conducts. Note that the average value of output voltage, E_{av} (indicated by the dashed line), for the half-wave rectifier is less than half the amplitude of the voltage peaks; the average value of output voltage, E_{av} , for the full-wave rectifier is greater than half, but is still much less than the peak amplitude of the rectifier-output waveform. With no filter circuit connected across the output of the rectifier circuit (unfiltered), the waveform has a large value of pulsating component as compared with the average (or dc) component.

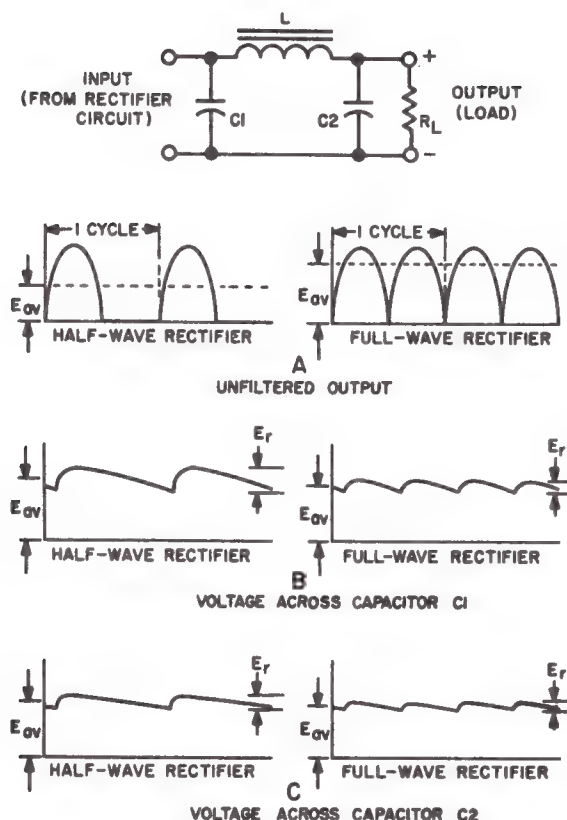

L-C Capacitor-Input Filter and Waveforms

The filter shown in the schematic of the illustration consists of an input filter capacitor, C_1 , a series inductor, L , and an output filter capacitor, C_2 . It is called a *capacitor-input filter*, and is often referred to as a *Pi-section filter* because the configuration of the schematic resembles the Greek letter π .

Capacitor C_1 is placed at the input to the filter, and is in shunt with the output of the rectifier circuit; capacitor C_1 exhibits the same filtering action in this circuit that C_1 does in the R-C Capacitor-Input Filter, described earlier in this section of the handbook. In the capacitor-input filter, the major portion of the filtering action is accomplished by the input capacitor, C_1 . The average value of voltage across the input capacitor, C_1 , is shown in part B of the illustration for the half-wave and full-wave rectifier circuits. Note that the average value of voltage across capacitor C_1 is greater than the average value of voltage for the


unfiltered output of the rectifier, shown in part A. The value of the input capacitor is relatively large in order to present a low reactance (X_C) to the pulsating current and to store a substantial charge. The rate of charge for the capacitor is limited only by the impedance of the ac source (transformer) and the internal resistance of the rectifier, both of which are relatively low; therefore, the R-C charge time constant for the input circuit is relatively short. As a result, when the pulsating voltage is first applied to the capacitor-input filter, capacitor C_1 charges rapidly and reaches the peak voltage within the first few cycles. The charge on capacitor C_1 approximates the peak value of the pulsating voltage when the rectifier is conducting, but when the rectifier output falls to zero, the capacitor partially discharges through the series inductor, L , and the load resistance, R_L , during the time the rectifier is nonconducting. The larger the value of the input capacitor, C_1 , the better the filtering action; however, there is a practical limitation to the maximum value of the capacitor. If the peak-current rating of the rectifier is exceeded during the charging time for the capacitor, the rectifier will be damaged; for this reason, a compromise in the value of the capacitor is necessary in order to keep the maximum charging current within the peak-current rating of the rectifier.

The inductor (or filter choke), L , serves to maintain the current flow to the filter output (capacitor C_2 and load resistance R_L) at a nearly constant level during the charge and discharge periods of input capacitor C_1 . The rate of discharge for capacitor C_1 is determined by the dc resistance of the filter choke, L , and the load resistance, R_L , in series. The average value of voltage developed across capacitor C_2 and load resistance R_L is somewhat less than the average voltage developed across capacitor C_1 . As the load current is increased, the voltage drop across inductor L increases because of the internal dc resistance of the inductor. Also, there is a decrease in the discharge time constant for capacitor C_1 which, in turn, results in a decrease in the average value of voltage across C_1 because of the greater discharge between rectifier pulses; thus, the average voltage across output capacitor C_2 is also reduced.

Series inductor L and capacitor C_2 form a voltage divider across capacitor C_1 . As far as the ripple component is concerned, the inductor offers a high impedance and capacitor C_2 offers a low impedance

to the ripple component; as a result, the ripple component, E_r , appearing across the load resistance is greatly attenuated. Since the inductance of the filter choke opposes changes in the value of the current flowing through it, the average value of the voltage produced across the output capacitor, C_2 , contains a much smaller value of ripple component, E_r , as compared with the value of ripple produced across the input capacitor, C_1 . Since inductor L operates in conjunction with capacitor C_2 , if either filter element is decreased in value, the other must be increased accordingly to maintain the same degree of filtering. The pulsations across capacitor C_2 , which are present in spite of the action of capacitor C_1 and inductor L , cause C_2 to charge and discharge in the same manner as C_1 . The final result is the waveform shown in part C of the illustration.

Some electronic equipments require a high degree of filtering, while other equipments are not critical in this respect. The output from a single shunt-capacitor filter, or from an R-C or L-C capacitor-input (single Pi-section) filter, may contain an amount of ripple which is considered excessive for the equipment application. When this is the case, it is necessary to use additional filtering to further attenuate the ripple component and reduce the ripple content to a minimum. By adding another series inductor (L_2) and shunt capacitor (C_3) to the basic capacitor-input filter, the ripple component across the load resistance can be further attenuated. As shown in the accompanying illustration, the added filter components, L_2 and C_3 , are called an *L-section filter* because the schematic configuration resembles an inverted letter L.

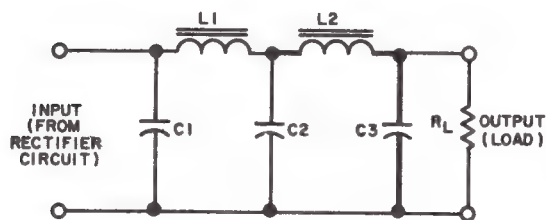

Capacitor-Input Filter with L-Section Added

In a partial filter circuit, the reactance of the additional shunt capacitor (C_3) is much less than the reactance of the additional series inductor, L_2 , and of the load resistance, R_L . Therefore, each L-section filter which is added to the basic filter further reduces the output ripple amplitude. When using a multiple-section filter, the operating voltage may be taken from each separate filter section. However, when the L-section (L_2 and C_3) is added to the basic filter circuit, the regulation of the supply suffers, because adding resistance in series with the load causes greater variation of the output voltage when changes in load current occur. The voltage regulation of a power supply using a capacitor-input filter circuit is relatively poor (as compared with a choke-input filter); for this reason, the use of a capacitor-input filter is usually restricted to low-current applications such as receivers, amplifiers, and the like, where the load current is relatively constant.

Circuit Operation. Consider now a complete cycle of operations, using a single-phase, full-wave rectifier circuit to supply the input voltage to the filter. The rectifier voltage is developed across capacitor C_1 . The ripple voltage in the output of the filter is the alternating component of the input voltage reduced in amplitude by filter action, as shown in the preceding illustration.

Each time the plate of the rectifier goes positive with respect to the cathode, the tube conducts and C_1 charges to the peak value of the voltage less the internal voltage drop in the tube. Conduction occurs twice during each cycle for a full-wave rectifier; for a 60-Hz supply this produces a 120-Hz ripple voltage. Although each tube alternates (first one conducts while the other is nonconducting, and then the other conducts while the first one is nonconducting), the filter input voltage is not steady. As the positive conducting plate voltage increases (on the positive half of the cycle), capacitor C_1 charges rapidly, the charge being limited only by the transformer secondary impedance and the tube forward (cathode-to-plate) resistance. During the nonconducting interval (when the plate voltage drops below the capacitor charge voltage), C_1 discharges through choke L and load resistance R_L . The discharge path is an R-L long-time constant path; thus C_1 discharges much more

slowly than it charges, as indicated by the waveforms in the illustration above. In this respect, the action of C1 is similar to that of the shunt-capacitor filter described previously in this section, with one exception. This exception is the effect of choke L.

Choke L is usually chosen to be a large value, on the order of 10 to 20 henries, and offers a large inductive reactance to the 120-Hz ripple component produced by the rectifier. Thus each time C1 starts to discharge, the inertia of the choke inductance effectively opposes a change in the ripple current through L. As far as the d-c component of this voltage is concerned, it is affected only by the time constant consisting of the dc resistance of L and R1 in series with C1.

The effect of L on the charging of capacitor C2 must not be considered. Since C2 is connected in parallel with C1 through choke L, any charge on C1 will also tend to change C2. However, both the impedance and resistance of L are in series with C2, and a voltage division of both the ripple (ac) voltage and dc output voltage occurs. The greater the impedance of the choke to the ripple frequency, the less the ripple voltage appearing across C2 and the output. The dc output voltage is fixed mainly by the dc resistance of the choke. For each specific value of current there is a voltage drop across the choke. Thus the dc voltage across C2 is always less than that across C1 (the higher the output current, the lower the voltage across C2). Since C2 is simplified from C1, which has maximum and minimum voltages produced by the charge and discharge action (the ripple voltage), C2 also follows this charge and discharge pattern. The difference is that the C2 action is smoothed out by the longer time constant. While the peaks and valleys exist, the values are lower. As can be seen from the waveform in part C of the illustration above, the over-all effect is to provide a purer direction current (less ripple).

Failure Analysis.

General. Shunt capacitors are subject to open circuits, short circuits, and excessive leakage; series inductors are subject to open windings and occasionally shorted turns or a short circuit to the core.

The input capacitor has the greatest pulsating voltage applied to it, is the most susceptible to voltage surges, and has a generally higher average voltage applied; as a result, the input capacitor is frequently

subject to voltage breakdown and shorting. The output capacitor is not as susceptible to voltage surges because of the protection offered by the series inductor, but the capacitor can become open, leaky, or shorted.

A shorted capacitor, an open filter choke, or a choke winding which is shorted to the core results in a no-output indication. A shorted capacitor, depending on the magnitude of the short, may cause a shorted rectifier, transformer, or filter choke. When proper precautions are taken, it may only blow a protective fuse. An open filter choke results in an abnormally high dc voltage at the input to the filter and no voltage at the output of the filter. A leaky or open capacitor in the filter circuit results in a low dc output voltage; this condition is generally accompanied by an excessive ripple amplitude. Shorted turns in the winding of a filter choke reduce the effective inductance of the choke and decrease its filtering efficiency; as a result, the ripple amplitude increases.

When the supply voltage removed from the input to the filter circuit, one terminal of each capacitor can be disconnected from the circuit. Each capacitor should be checked, using a capacitance analyzer, to determine its effective capacitance and leakage resistance, being careful always to observe correct polarity. A decrease in effective capacitance or losses within the capacitor can cause the output to be below normal and also cause excessive ripple amplitude.

If a suitable capacitance analyzer is not available, an indication of leakage resistance can be obtained by using an ohmmeter. Resistance measurements can be made across the terminals of the capacitor to determine whether it is shorted or leaky. If the capacitor is of the electrolytic type, the resistance measurement may vary, depending on the test-lead polarity of the ohmmeter. Therefore, two measurements must be made, with the test leads reversed at the capacitor terminals for one of the measurements, to determine the larger of the two resistance measurements. The larger resistance value is then accepted as the measured value.

L-C CHOKE-INPUT FILTER

Application.

The L-C choke-input filter is used primarily in power supplies where voltage regulation is important

and where the output current is relatively high and subject to varying load conditions. The filter is used in high-power applications such as those found in the power supply circuits of radar and communication transmitters.

Characteristics.

Filter is composed of series input inductor and shunt output capacitor.

Filtering efficiency increases as ripple frequency is increased.


Output voltage is less than that of capacitor-input filter; output voltage from filter approaches average value of voltage from rectifier at filter input.

Regulation of rectifier-type power supply is good with this type of filter; further improvement in regulation characteristics can be realized with swinging-choke input inductor.

Rectifier output current approaches maximum rated current; output current is generally greater than that of capacitor-input filter.

Circuit Analysis.

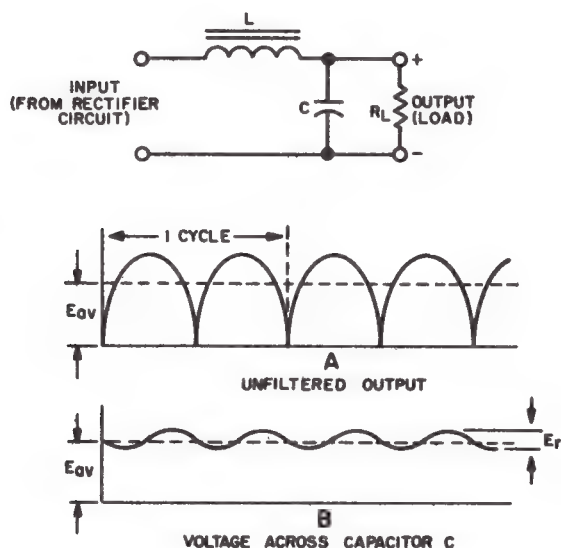General. The accompanying illustration shows an L-C choke-input filter and the waveforms obtained from a single-phase, full-wave rectifier circuit.



L-C Choke-Input Filter and Waveforms

The output from a single-phase, half-wave rectifier circuit is not illustrated because the choke-input filter is seldom used with this circuit. The unfiltered output obtained from three-phase, half-wave and full-wave rectifier circuits produces a higher average voltage and ripple frequency; however, the principle of filter action is essentially the same as that illustrated for the single-phase, full-wave rectifier; therefore, these waveforms are not illustrated.

The waveform given in part A represents the unfiltered output from a typical single-phase, full-wave rectifier circuit when current pulses flow through the load resistance each time the rectifier conducts. Note that the dashed line indicating the average value of output voltage, E_{av} , is slightly greater (0.637) than half the amplitude of the voltage peaks. With no filter circuit connected across the output of the rectifier circuit (unfiltered), the waveform has a large value of pulsating component as compared with the average (dc) component.

The filter shown in the schematic of the illustration consists of an input inductor or filter choke, L , and an output filter capacitor, C . The filter illustrated is called a *choke-input filter*, and is often referred to as an *L-section filter* because the schematic configuration resembles an inverted letter L.

Inductor L is placed at the input to the filter and is in series with the output of the rectifier circuit. Since the action of an inductor is to oppose any change in current flow, the inductor tends to keep a constant current flowing to the load throughout the complete cycle of the applied voltage. As a result, the output voltage never reaches the peak value of the applied voltage; instead, the output voltage approximates the average value of the input to the filter. Also, the reactance of the inductor (X_L) reduces the amplitude of ripple voltage without reducing the dc output voltage an appreciable amount.

The shunt capacitor, C , charges and discharges at the ripple frequency, but the amplitude of the ripple voltage, E_r , is relatively small because the inductor, L , tends to keep a constant current flowing from the rectifier circuit to the load. The reactance of the shunt capacitor (X_C) presents a low impedance to the ripple component existing at the output of the filter, and the capacitor attempts to hold the output voltage relatively constant at the average value of the voltage. Since the reactance of the series inductor (S_L) is

greater than the reactance of the shunt capacitor (X_C), and the reactance of the shunt capacitor (X_C) is less than the load resistance, R_L , the amplitude of the ripple frequency at the output of the filter is considerably reduced from that present at the input to the filter circuit. The output waveform is shown in part B of the accompanying illustration; assuming a single-phase, full-wave rectifier circuit, note that the frequency of the ripple voltage, E_r , is twice the frequency of the applied voltage.

Both the output voltage from the filter and the peak current of the rectifier depend upon the inductance of the choke and the resistance of the load. The minimum value of inductance necessary to keep the output voltage from increasing above the average value of rectified ac is called the *critical value* of inductance. If the inductance of the input filter choke is less than the critical value for the circuit, the filter acts more like a capacitor-input filter and the output voltage will rise above the average value.

The critical value of inductance is given by the expression:

$$L_h = \frac{E_{out}}{I_{out}}$$


where: L_h = critical inductance in henries
 E_{out} = output of power supply in volts
 I_{out} = current drawn from power supply milliamperes

An increase in the value of choke inductance above the critical value will decrease the ratio of peak-to-average rectifier current and maintain a more uniform current flow through the inductor. Increasing the value of inductance above a certain value, called the *optimum value* of inductance, does not provide any appreciable improvement in performance or filtering efficiency. In practice, the optimum value of inductance for a given set of conditions is considered to be twice the critical value of inductance.

The value of inductance required for the filter varies directly with the effective load resistance, R_L . Since the inductance of a filter choke varies inversely with the current flowing through it, an increase in the load resistance causes the ratio of peak-to-average current to decrease; conversely, a decrease in the load resistance causes the ratio of peak-to-average current to increase.

The regulation characteristics of a power supply using a choke-input filter can be improved by the use of a swinging choke as the input inductor. A swinging choke is a choke whose inductance varies inversely with respect to the current flowing through it over the specified operating range. It is designed to have slightly more than the critical value of inductance at full load and an optimum value of inductance at no load. This characteristic maintains the peak-to-average current ratio within certain limits over a considerable range of changing load currents, and results in improved regulation for the supply.

The choke-input filter is widely used in electronic equipments where the power supply is required to deliver relatively high values of current to the load with good regulation characteristics. In some cases the equipment requires a high degree of filtering, while in other cases the equipment is not critical in this respect. The output from a single choke-input filter (single L-section) may contain an amount of ripple which is considered excessive for the equipment application. When this is the case, it is necessary to use additional filtering to further attenuate the ripple component. By adding another series inductor, L_2 , and a shunt capacitor, C_2 , to the basic choke-input filter, the ripple component across the load resistance can be further attenuated. As shown in the accompanying illustration, the added filter components, L_2 and C_2 , are called an *L-section filter* because the schematic configuration resembles an inverted letter L.

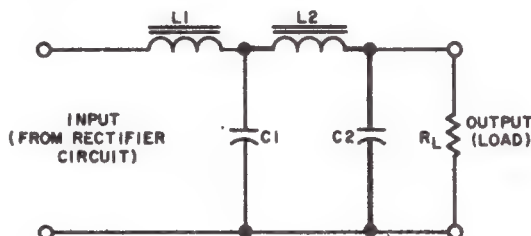


Choke-Input Filter with L-Section Added

In a practical filter circuit, the reactance of the shunt capacitor (C_2) is much less than the reactance of the series inductor (L_2) and of the load resistance, R_L . Therefore, each L-section filter which is added to the basic filter further reduces the output ripple

amplitude. However, when the L-section, L2 and C2, is added to the basic filter circuit, the regulation of the supply suffers somewhat because the added resistance of inductor L2 is in series with the load and thus causes a variation of the output voltage when changes in load current occur. Although the voltage regulation of a power supply using a choke-input filter circuit is good (as compared with the capacitor-input filter), the regulation can be further improved if inductor L1 is a swinging choke. In fact, the circuit may be designed to over-regulate, in which case the rise in average voltage across capacitor C1 compensates for the additional voltage drop occurring across inductor L2; as a result, the output voltage tends to remain constant.

The inductance of any iron core inductor shows a marked decrease as magnetic saturation is reached. The core of ordinary inductors is designed so that saturation occurs at a value just above the maximum current rating. Swinging chokes are generally designed to have one or more air gaps in the laminated core. The accompanying diagram illustrates a swinging choke which has two air gaps—one large and one small. (The sizes of the gaps are exaggerated in the illustration.)

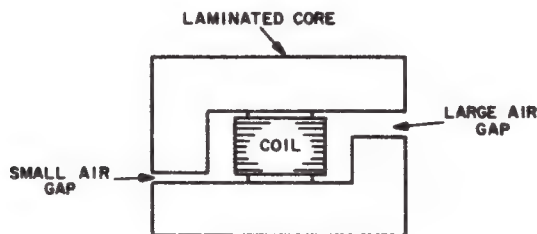

Swinging Choke with Two Air Gaps

The purpose of the large gap is to provide effective inductance at the largest currents, while that of the small gap is to assure high inductance at the smallest currents. Saturation of the core starts at some specified current; at full rated current, saturation is almost complete. Swinging chokes are rated to indicate the variations of inductance with variations of current through the coil. A rating of 15 to 3 henries at 25 to 250 ma, for example, means that the value of inductance is 15 henries at 25 ma, and reduces to only 3 henries at 250 ma. When handling small currents, the swinging choke functions as a

conventional choke-input filter. For larger currents, where the output voltage tends to drop, the inductance decreases and the filter starts to approach the characteristics of a capacitor-input filter. Because the decrease in inductance permits the capacitor to charge more nearly to the peak value instead of the average value, the loss of voltage in the dc resistance of choke L2 is thereby compensated for, and the output voltage tends to remain constant. As a result, regulation is greatly improved.

The output voltage available from a power supply using a choke-input filter circuit is much less than that obtained with a capacitor-input filter. However, since the input choke opposes a rapid build-up of current, there are no abrupt peak-rectifier currents with the choke-input filter, as there are with capacitor-input filter. Therefore, the rectifier can deliver a higher continuous current to the load without exceeding its maximum safe ratings.

Detailed Circuit Operation. Consider now one cycle of operation of the basic choke-input filter, as illustrated previously with waveforms.

The input to the filter circuit is the output of the single-phase, full-wave rectifier. The rectified pulses applied to the filter are as shown in part A of the illustration. During the rising portion of the input voltage, choke L produces a back emf which opposes the constantly increasing input voltage. The net result is to effectively present the rapid charging of filter capacitor C. Thus, instead of reaching the peak value of the input voltage, capacitor C is charged only to the average value of input voltage. After the input voltage reaches its peak and decreases, the back emf tends to keep the current flowing in the same direction, in effect broadening the peak.

During the rising portion of the pulse, the current flow through L is reduced, and during the falling portion of the pulse, the current continues to rise. The pulse, as it approaches zero, becomes insufficient to maintain the current, which then commences to decrease.

When the next pulse starts, the back emf is still opposing an increase in current, and the current continues to decrease. (The choke, in effect, shifts the ripple peaks almost 90 degrees with respect to the rectifier output.) When the rectified pulse nears the peak value, the rate of change and the inductive effect decrease, and once again the current through L starts to rise. This cycle of operation is continuously repeated during the time the circuit is energized and

rectified pulses are applied to choke L. The fluctuating voltage which results from the action of choke L appears across capacitor C and load resistor R_L in parallel. The low reactance of the capacitor to this ripple voltage effectively bypasses the ripple voltage to ground, so that the amplitude of the ripple voltage in the filter output is significantly reduced.

The voltage across C is the dc component or output voltage, and is produced by the charging of C through L. Essentially, the charging of C is controlled by the value of the time constant, consisting of the dc choke resistance in series with C. Such a typical time constant is on the order of tenths of a second or seconds rather than micro-seconds or milliseconds. Thus it takes many cycles of operation to charge C. The discharging of C through the load is usually slower than the charge time, since the load resistance is normally greater than that of the choke. Therefore, the output voltage tends to remain fairly constant. The choke-input filter is effective in reducing the ripple voltage because choke L and capacitor C act as an ac voltage divider for ripple voltage. With the impedance of L high and the impedance of C low, any ripple voltage appearing across C is small, because of the large voltage drop across L, and is effectively bypassed around the load by the low value of X_C .

Failure Analysis.

General. The shunt capacitors are subject to open circuits, short circuits, and excessive leakage; the series inductors are subject to open windings and, occasionally, shorted turns or a short circuit to the core.

Shorted turns in the input choke may reduce the value of inductance below the critical value of inductance; this will result in excessive peak-rectifier current, accompanied by an abnormally high output voltage, excessive ripple amplitude, and poor voltage regulation. Shorted turns in the smoothing choke (in the case of a multisection filter) will reduce the effective value of inductance; this will result in less filtering efficiency, with an attendant increase in the output ripple amplitude. An open filter choke, or a choke winding which is shorted to the core, will result in a no-output condition. A choke winding which is shorted to the core may cause overheating of the tubes, blown fuses, etc.

The shunt capacitor(s) in the choke-input filter is not subjected to extreme voltage surges because of the protection offered by the input inductor; how-

ever, the capacitor can become open, leaky, or shorted. An open capacitor results in excessive ripple amplitude in the output voltage; a leaky capacitor results in a lower-than-normal output voltage, and a shorted capacitor results in a no-output condition.

With the supply voltage removed from the input to the filter circuit, one terminal of the capacitor can be disconnected from the circuit. The capacitor should be checked, using a capacitance analyzer, to determine its effective capacitance and leakage resistance. It is important when the capacitor is electrolytic, that correct polarity be observed at all times. A decrease in effective capacitance or losses within the capacitor can cause the filtering efficiency to decrease and produce excessive ripple amplitude.

If a suitable capacitance analyzer is not available, an indication of leakage resistance can be obtained by using an ohmmeter. Resistance measurements can be made across the terminals of the capacitor to determine whether it is shorted, open, or leaky. When testing electrolytic capacitors, set the ohmmeter to the high range and connect the test prods across the capacitor, being careful to observe polarity. This is important because current flows with less opposition through an electrolytic capacitor in one direction than in the other. If the correct polarity is not observed, an incorrect reading will result. When the test prods are first connected, a large deflection of the meter takes place, and then the pointer returns slowly toward the infinite-ohms position as the capacitor charges. For a good capacitor with a rated working voltage of 450 volts, dc, the final reading on the ohmmeter should be over 500,000 ohms. (A rough rule of thumb for high-voltage capacitors is at least 1000 ohms per volt.) Low-voltage electrolytic capacitors (below 100 volts rating) should indicate on the order of 100,000 ohms.

If no deflection is obtained on the ohmmeter when making the resistance check explained above, an open-circuited capacitor is indicated.

A steady full-scale deflection of the pointer at zero ohms indicates that the capacitor being tested is short-circuited.

An indication of a leaky capacitor is a steady reading on the scale somewhere between zero and the minimum acceptable value. (Be certain this reading is not caused by an in-circuit shunting part.) To be valid, these capacitor checks should be made with the capacitor completely disconnected from the circuit in which it operates.

In high-voltage filter capacitor applications, paper and oil-filled capacitors are used, as are also mica and ceramic capacitors (for low-capacitance values). In this case, polarity is of no importance unless the capacitor terminals are marked + or -. It is, however, good maintenance practice to use the output polarity of the circuit as a guide, connecting positive to positive and negative to negative. Thus any effects of polarity on circuit tests are minimized and the possibility of damage to components or test equipment is avoided. *Remember*—an undischarged capacitor retains its polarity and holds its charge for long periods of time. To be safe, discharge the capacitor to be tested with the *power OFF* before connecting test equipment or disconnecting the capacitor.

RESONANT FILTER

Application.

The resonant filter is quite limited in its application to power-supply filter systems. It is normally used in conjunction with L-type or Pi-type filter sections, rather than by itself, since it is designed to offer maximum attenuation only to the fundamental ripple frequency.

Characteristics.

Parallel-resonant filter is composed of an inductor and a capacitor in parallel; series-resonant filter is composed of an inductor and a capacitor in series.

Filter is resonant at fundamental frequency of ripple voltage.

Parallel-resonant filter offers maximum impedance at resonance; series-resonant filter offers minimum impedance at resonance.


Parallel-resonant filter requires constant load current.

Circuit Analysis.

General. For special applications where maximum attenuation of the ripple frequency is desired, a resonant filter is sometimes used in power-supply circuits. This filter may be either the parallel-resonant or the series-resonant type, and is always tuned to the fundamental ripple frequency. Since the filter is tuned only to the fundamental ripple frequency, harmonics of the fundamental frequency are attenuated very little, if at all. For this reason, the resonant filter is seldom used by itself; it is normally used in conjunc-

tion with other filtering sections. A disadvantage of the parallel-resonant filter is that the inductance is subject to change when the load current is changed. Since the load current must flow through the inductor of the parallel-resonant filter, this current determines the value of inductance and, consequently, affects the resonant frequency of the tuned circuit.

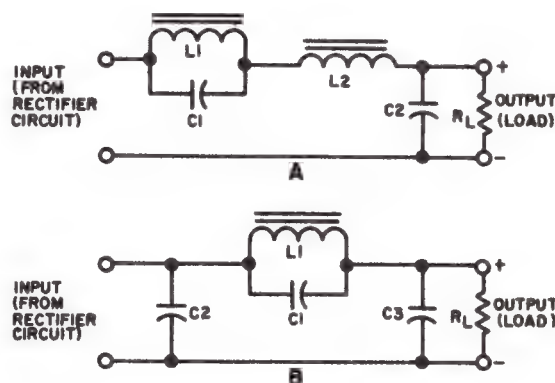Parallel-Resonant Filter. The accompanying illustration shows a parallel-resonant filter, sometimes called a *parallel-resonant trap*, used in two typical power-supply filter circuits.



Typical Power-Supply-Filter Circuits Using a Parallel-Resonant Filter

The circuit in part A shows a parallel-resonant filter, L_1 and C_1 , used with an L-section filter, L_2 and C_2 ; the circuit in part B shows a parallel-resonant filter, L_1 and C_1 , used in conjunction with a shunt input capacitor, C_2 , and a shunt output capacitor, C_3 . Note that in both filter circuits the load current must flow through inductor L_1 of the parallel-resonant filter.


The parallel-tuned circuit, L_1 and C_1 , is made resonant at the fundamental ripple frequency. When this is done, the fundamental ripple-frequency component is greatly attenuated because of the extremely high impedance offered by the parallel-resonant circuit. In a practical filter circuit, the inductor is fixed in value and one or more specific-value capacitors are selected and placed in parallel with the inductor to obtain exact resonance at the ripple frequency. In a few special cases, and also when the ripple frequency is relatively high, the capacitor is fixed in value and the inductor is made variable. In either case, however,

if the load current through the inductor should change from the design value of current, the inductance of L_1 will change and the circuit will no longer be resonant at the ripple frequency. The circuit loses its effectiveness rapidly as the load current is changed from the design value and the circuit is detuned from resonance. At resonance, the filter offers maximum impedance to the ripple-frequency component. The filter provides less attenuation at other frequencies; it has a progressively lower impedance, both above and below the resonant frequency, the farther the frequency is from resonance. Therefore, the parallel-resonant filter is nearly always used with additional filters to overcome this disadvantage and effectively attenuate harmonic frequencies.

In the circuit shown in part A, the parallel-resonant filter, L_1 and C_1 , is connected in series with the output of the rectifier circuit and ahead of an L-section filter, L_2 and C_2 . The L-section filter circuit has the general characteristics previously described for the L-C Choke Input Filter, in this section of the handbook. The ripple-frequency component from the rectifier output is attenuated by the high impedance offered to the ripple frequency by L_1 and C_1 , and the remaining fluctuations in the form of harmonic frequencies of the fundamental ripple frequency are attenuated by the L-section filter, L_2 and C_2 . The upper waveform in part A of the accompanying illustration shows the shape of the output voltage obtained from a single-phase, half-wave rectifier. The frequency of the ac input voltage is assumed to be 60 Hz. When the rectifier output is applied directly to the input of the parallel-resonant filter, the fundamental ripple component is highly attenuated in the output of the filter. This is shown by the lower waveform in part A.

In the circuit shown in part B, the parallel-resonant filter, L_1 and C_1 , is located between two shunt capacitors, C_2 and C_3 . This filter circuit has the general characteristics previously described for the L-C Capacitor-Input Filter, in this section of the handbook. The ripple-frequency component which remains after being reduced in amplitude by the action of shunt capacitor C_2 is further attenuated by the impedance offered by the parallel-resonant filter and any remaining fluctuations are smoothed by shunt capacitor C_3 . The upper waveform in part B of


the illustration shows the shape of the output voltage of a single-phase, half-wave rectifier, developed across C_2 . The frequency of the ac input voltage is assumed to be 60 Hz. When the voltage developed across C_2 is applied to the input of the parallel-resonant filter, the fundamental ripple component is greatly attenuated and appears in the filter output as shown by the lower waveform in part B.

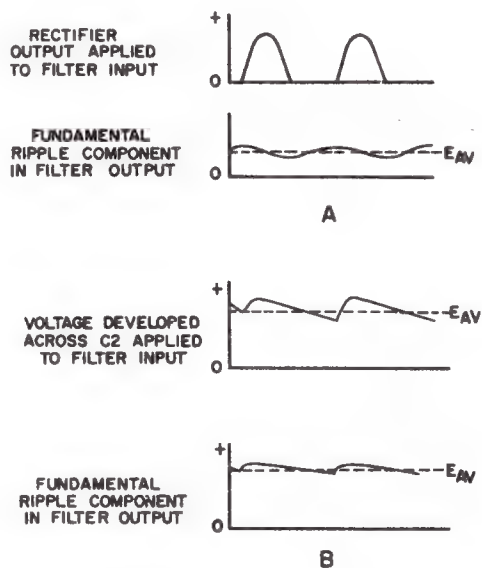

Typical Output Waveforms for Two Different Types of Input to the Parallel-Resonant Filter

The circuits shown in parts A and B of the illustration above have one important disadvantage, mentioned previously; that is, changes in load current affect the filtering efficiency of the parallel-resonant filter by changing the inductance and thus detuning the circuit from resonance. In a practical filter circuit, this effect can be tolerated for small changes in load current by making inductor L_1 small as compared with capacitor C_1 , so that the detuning will be minimized.

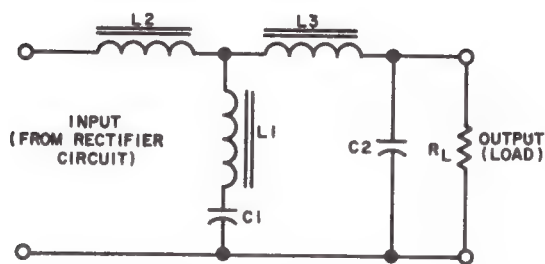Series-Resonant Filter. The accompanying illustration shows a series-resonant filter, sometimes called a *series-resonant shunt filter*, used in a typical power supply filter circuit.



Typical Power-Supply-Filter Circuit Using a Series-Resonant Filter

The series-resonant filter is composed of $L1$ and $C1$ in series. The filter is used in conjunction with an input inductor, $L2$, and an L-section filter, $L3$ and $C2$. Note that the circuit is essentially a choke-input filter with two L-sections; the first L-section includes the series-resonant filter used as a shunt element instead of a shunt capacitor. The series-tuned circuit, $L1$ and $C1$, which is made resonant at the fundamental ripple frequency, offers extremely low impedance to the ripple frequency at resonance. The bypassing action of the resonant filter to the fundamental ripple-frequency component is, therefore, much better than that obtained with a shunt capacitor alone, since the capacitive reactance (X_C) of a shunt capacitor alone will normally be greater than the impedance of the series-resonant filter. The filter circuit illustrated has the same general characteristics previously described for the L-C Choke-Input Filter, in this section of the handbook. The ripple-frequency component which remains after passing through inductor $L2$ is bypassed by the resonant filter, $L1$ and $C1$; the remaining fluctuations are further smoothed by the L-section filter, $L3$ and $C2$.

The series-resonant filter must always be used with an input inductor ($L2$) in series with the rectifier output. If the series-resonant filter were shunted directly across the rectifier output, the filter would act as a short circuit (low impedance to the fundamental ripple frequency) and cause extremely high rectifier peak currents to flow; these currents, in turn, would

damage the rectifier. In a practical filter circuit, the inductor ($L1$) is fixed in value, and one or more specific-value capacitors ($C1$) are paralleled and placed in series with the inductor to obtain exact resonance at the ripple frequency. At resonance, the filter offers extremely low impedance to the ripple-frequency component, but the filter provides very little bypassing action at other frequencies; it has a progressively higher impedance, both above and below the resonant frequency, the farther the frequency is from resonance. Therefore, the series-resonant filter is always used with additional filter sections to overcome this disadvantage and effectively attenuate harmonic frequencies.

Failure Analysis.

General. When analyzing the failure of a resonant filter to perform satisfactorily, it should be remembered that resonance of the filter is most important, and that any change in the inductance, capacitance, load current, or applied ripple frequency will directly affect the filtering efficiency. The inductors used in a resonant filter can be checked for the proper value of inductance (no dc) by using an impedance bridge; the capacitors can be checked by using a capacitance analyzer.

As previously mentioned, the inductance of the inductor ($L1$) employed in a parallel-resonant filter depends on the load current which flows through it; therefore, the load current must be measured to determine that the current is within tolerance in order that the parallel-resonant filter operate effectively and remain tuned to the fundamental ripple frequency.

Because a resonant filter offers little attenuation to higher-order ripple frequencies (harmonics), it is normally employed in conjunction with other filter sections, such as choke-input or capacitor-input filter sections. Therefore, the failure analysis procedures for a power supply filter system which contains a resonant filter are essentially the same as those given earlier in this section of the handbook for the applicable choke-input or capacitor-input filter circuit.

PART 4-2. SIGNAL

HIGH-PASS FILTERS

Application.

High-pass filters are universally used in circuits where it is desired to pass the higher frequencies and to attenuate the lower frequencies below a selected cutoff frequency (F_0).

Characteristics.

Resistance-capacitance-type filters are used only for audio frequencies, whereas inductance-capacitance-type filters are used for both audio and radio frequencies, and wherever sharp cutoff is required.

The higher the frequency above cutoff, the lower the attenuation; below the cutoff frequency the attenuation increases as the frequency decreases.

May be half-section, single-section, or multiple-section, with the multiple-section (ladder) type providing the greatest attenuation and sharpest cutoff.


May be of either the "constant K" or "m-derived" form, or combinations thereof.

Circuit Analysis.

General. A filter consists of a circuit containing a number of impedances grouped together in such a manner that it has a definite frequency response characteristic. It is designed to permit the passage (transmit) signals freely over a certain desired range of frequencies, and to attenuate (transmit poorly) over another range of frequencies. The frequency range over which the passage occurs freely is called the *pass band*, (or transmission band) and the range over which attenuation (poor transmission) occurs is called the *attenuation band*. The frequency at which the attenuation of the signal starts to increase rapidly is known as the *cutoff* frequency. The basic configurations into which the high-pass filter elements can be assembled or arranged are the *L* or *half-section*, the *T-section*, and the *Pi-section*. The L-section consists of one series capacitive element and one parallel (shunt) element of either resistance or inductance, forming an inverted L (since two L-sections may be connected together to form a symmetrical T or Pi-network it is referred to as a half-section). The T-

section consists of two series capacitive arms and one shunt arm, resembling the letter T. The Pi-section consists of one series capacitive arm with two shunt arms, resembling the Greek letter π . Several sections (or half-sections) of the same circuit configuration can be joined to improve the filter attenuation or transmission characteristic. When several sections are cascaded together, they form a *ladder* type of filter. When a filter is inserted into a circuit, it is usually terminated (matched) by a resistance of the same value at the input ends. The value of the terminating resistance is usually determined by the circuit with which the filter is used and the type of filter circuit employed. In some instances, circuit parts may be arranged basically in the form of a simple filter, even though it is not desired to provide such filter action initially. For example, the simple R-C coupling network in an audio amplifier grid circuit provides a high-pass filter effect with low-frequency cutoff, and creates a design problem because equal amplification of both the low and high frequencies is usually desired. The cutoff frequency of a filter is determined by the circuit configuration, type of filter (constant k or m -derived), and the values of the capacitors and resistors (or inductors) in the filter circuit. When the cutoff frequency is known, the values of the parts required to produce this response and the desired attenuation may be calculated mathematically by use of the proper formulas. This handbook will not be concerned with design data, but will show the circuit configurations, explain the circuit action, and provide information with which the technician can determine or recognize the type of filter and determine the cutoff frequency, if needed.

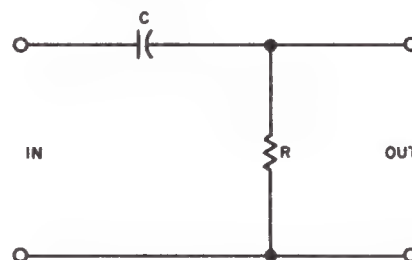
Circuit Operation. A typical half-section R-C high-pass filter is shown in the accompanying illustration.



Half-Section R-C High-Pass Filter

The simple high-pass filter shown in the figure is equivalent to an R-C coupling network placed in the grid of an amplifier stage. Note that the output voltage is taken across the resistor, and the capacitor is series-connected. The circuit is basically that of a voltage divider in which C forms the reactive arm and R the resistive arm. If the value is selected so that the capacitive reactance is equal to the resistance of resistor R at frequency f_1 , then the output voltage of the network will be attenuated approximately 3 dB with respect to the input voltage. This frequency is called the *theoretical cutoff frequency*, and its value is given by: $f_1 = 1/(2\pi R C)$ in Hz. The values of R and C are in ohms and farads (or in megohms and microfarads), and RC is the *time constant* in seconds. Thus, if the low-frequency response of an R-C-coupled amplifier is specified as having a time constant of, for example, 2000 microseconds (which is sometimes done), f_1 equals 80 Hz (apply the values in the formula above and calculate). In the example, the theoretical cutoff frequency is approximately 80 Hz, and since only a simple half-section filter is used the cutoff is not sharp, but varies directly with the capacitive reactance of C. However, with a sufficient number of cascaded filters of the proper value, it could be made reasonably sharp.

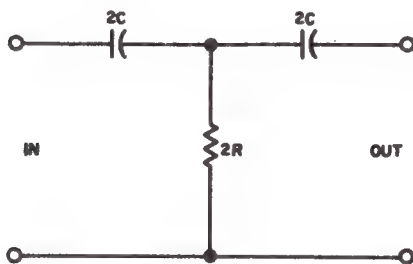
Consider now a T-section filter as illustrated in the accompanying figure.



T-Section R-C High-Pass Filter


This circuit arrangement forms a full-section which can be considered as two half-sections (L-sections) placed back to back with resistor R common to both. Note that in this circuit arrangement the two capacitors are connected in series; consequently, the design value of C is doubled. Likewise, the design value of R is also doubled since the two resistors are paralleled, thereby making the effective value of R that of the single L-section. The T arrangement provides a

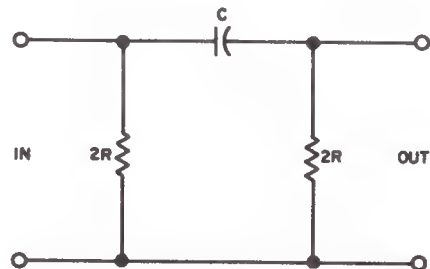symmetrical input and output with the same time constant as the single section L-type filter. A typical Pi-section filter network is shown in the accompanying figure.



Pi-Section R-C High-Pass Filter

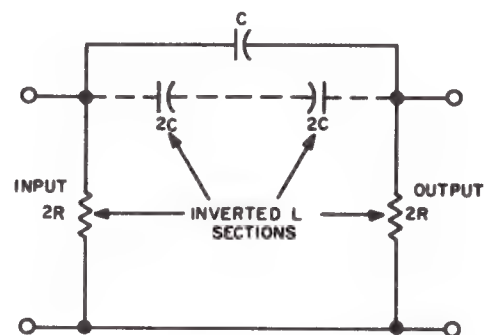In this full-section arrangement the value of the resistive arms is, likewise, chosen to be double that of the half-section arrangement, and C is equal to the total value of the two series capacitors of the T-section arrangement. Development of the Pi-section from two inverted L-section filters is illustrated in the following diagram.




Development of Pi-Section Filter

The values used are those of the basic half-section L-filter. Note that in any of the three previously shown filter arrangements the actual time constant values are identical. Therefore, the response and attenuation of each are also identical. L-sections are used where only a simple unbalanced input and output is needed. The T- and Pi-sections are used where balanced arrangements are required. Multiple-section filters are used to obtain greater phase shift and more attenuation. Thus, a two-section filter using identical

values of parts will multiply the phase shift and attenuation by a factor of two. For complete design data refer to a standard text.

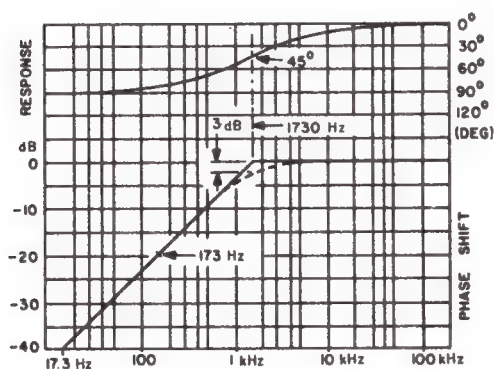In any of the filter arrangements previously discussed, the attenuation is assumed to be zero immediately above the cutoff frequency, f_0 , and very large for frequencies below f_0 , as shown in the following response graph.




Phase and Amplitude Response Characteristics for High-Pass R-C Filter ($f_0 = 1730$ Hz)

However, as can be seen from the chart, the attenuation (for a single-section filter) becomes relatively constant at about 12 dB/octave (20 dB per decade) at frequencies considerably below the cutoff frequency. The phase shift range from zero at the higher frequencies above f_0 to 45 degrees at f_0 . Below the cutoff frequency the phase shift soon becomes constant at 90 degrees. The dotted line indicates how this typical Bode plot is rounded off to simulate practical conditions. As a result, a 3-dB difference exists between the actual and theoretical response at the cutoff frequency.

The effect of a high-pass filter on the response of a rectangular pulse is indicative of the action produced by this type of filter. Since the output voltage of the high-pass filter is taken from across the resistor which is in series with the capacitor and the input circuit, it is evident that before the pulse is applied, there is no charge in the capacitor and no current in the circuit. Therefore, no voltage output is obtained. Upon application of the rectangular pulse, the initial current is equal to E/R . Since the output voltage is equal to the current times the resistance, the output voltage also

rises instantaneously to E . Thus the rise time in this circuit is maintained without any change. However, as the capacitor charges, the current through the resistance decreases; hence, the output voltage decreases. Eventually, the capacitor charges to the input voltage and the output voltage drops to zero.

The following figure shows the over-all response of a high-pass filter to a rectangular pulse of 15 microseconds duration with different time constant values (R times C). From the previous paragraph it is clear that the rise time is unaffected, as shown in the figure. When the time constant is long with respect to the pulse duration, little effect on the pulse shape is obtained. For example, with a time constant of 150 microseconds in the filter, and a pulse of 15 microseconds time duration applied to the filter input, the output voltage will drop to only 0.9 of the input voltage, as shown by the dotted line in the figure (for an RC/t ratio of 10). On the other hand, when the pulse duration is equal to the time constant, the capacitor charges to approximately 63% of its full value and the current flow through the resistor is such as to produce an output voltage of only 0.37 that of the input ($RC/t = 1$ in the figure).

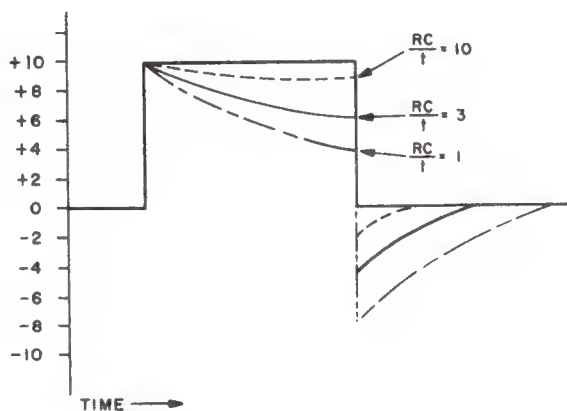


Typical Pulse Response Variation with Time Constant or Pulse Width Changes

When the input voltage drops to zero at the end of the pulse duration period, the output voltage of the filter is equal to the voltage across the capacitor. For instance, in the previous example of the large time constant ratio of 10, the output voltage dropped to only 0.9 of the input. Therefore, a charge of 0.1E must exist on the capacitor at the end of the pulse.

The capacitor voltage is negative with respect to the input voltage since it opposes the input voltage. Therefore, when the input voltage drops to zero, the output voltage drops to $-0.1E$, and the capacitor then discharges to zero volts. It is evident, then, that the greater the voltage drop across the capacitor at the end of the duration period of the pulse, the greater will be the negative voltage at the output of the circuit when the input pulse falls to zero.

Since R-C filters respond to the time constant of the circuit, it is evident that while filters of many sections can be used, the simple equivalent time constant of the entire network will basically determine the filter characteristics, and that really sharp cutoff cannot be obtained. With the use of L-C filter circuits, however, it is possible to produce the desired pass band with a much sharper cutoff and attenuation characteristics. Since both inductance and capacitance are used, a single-section L-C filter is capable of a 180-degree phase shift.

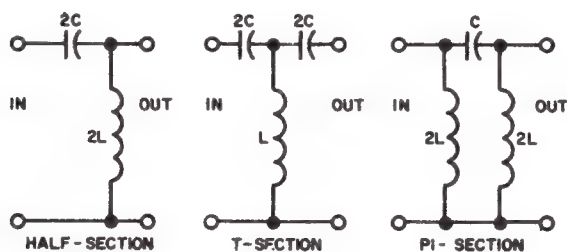High-pass filter circuits using inductance and capacitance follow the same type of circuit configuration as do R-C filters, as shown in the following figure.




High-Pass L-C Filter Circuits

Basic filter theory stipulates that where reactances of the same sign (either all capacitance or all inductance) are used, the characteristic impedance presented by the filter to the input or output circuit is a reactance. On the other hand, where reactances of opposite sign are used (such as capacitance and inductance), the characteristic impedance becomes resistive over one range and reactive over another range. Thus the design and matching of filters becomes an engineering problem, and is treated on an ideal theoretical basis. This means that while a filter may be considered to have infinite rejection beyond a

particular cutoff frequency, in practice the result may not be as great as predicted. Likewise, the cut-off frequency may not be as critical or as sharp as the design figures indicate.

All the previously discussed filter arrangements are of the *constant k* type, which has gradual rather than a sharp cutoff frequency. In this simple type of filter the series filter arm impedance, Z_1 , and the shunt filter arm impedance, Z_2 , are so related that their product is a constant at all frequencies ($Z_1 \times Z_2 = k^2$). Therefore, it derives its name from this relationship. This constant, in turn, is also equal to R^2 , since Z_1 and Z_2 are reciprocal reactances (X_C and X_L , respectively), and $R^2 = L/C$. Thus, the formula for determining the cutoff frequency becomes; $f_0 = 1/4\pi\sqrt{LC}$, where L and C are in henrys and farads, respectively.

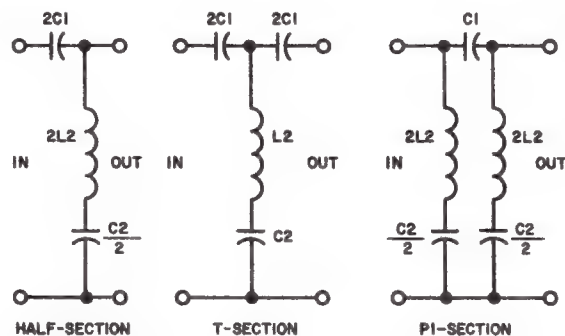
A more complex form of high-pass filter circuit is the *m-derived* type. In this type the cutoff frequency is sharper and the total attenuation of the unwanted frequencies is greater. Typical circuits of the series-connected, *m-derived* type are shown in the following illustration.



Series m-Derived High-Pass Filters


As can be seen from the illustration, a series-connected L-C network ($L2C2$) is placed across the output or across the mid-termination of the filter circuit. As designed, this network is made series-resonant at a frequency below the usual cutoff frequency. For the high-pass filter this resonant frequency, called the *frequency of infinite attenuation* (f_∞), is selected at a value of about $0.8 f_0$. Since f_∞ is resonant and is series-connected across the input or output, it represents a short circuit across the filter

for the resonant frequency (with a pass band determined by the Q and resistance of the circuits). Therefore, the normally sloping attenuation characteristic which approximates 12 dB/octave for the constant k filter is "notched" off. In effect, the m -derived filter is sharply separated from the frequencies below f_∞ , and thereby provides sharper and better cutoff of the lower frequencies. The action described can be visualized clearly when the attenuation (response) characteristics for the two types of filters are compared, as shown in the following figure.

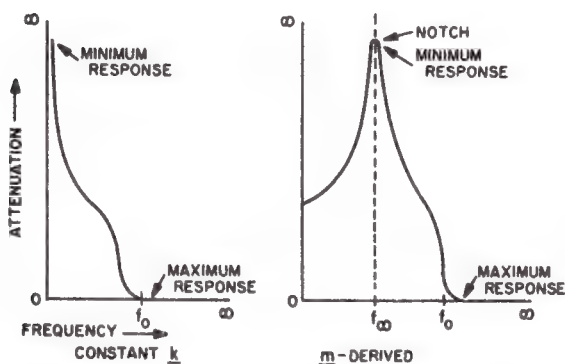


Comparison of Filter Attenuation Characteristics

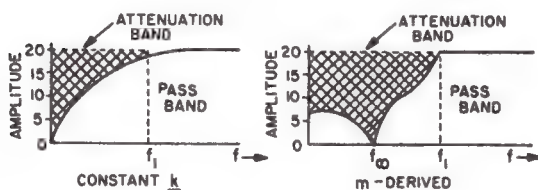While a constant attenuation is shown for the constant k type, with a reduced value of attenuation below f_∞ for the m -derived type, the sharpness of the m -derived cutoff at f_∞ (assuming zero circuit resistance at resonance) provides better high-pass performance, as illustrated below.



Comparison of Transmission Characteristics

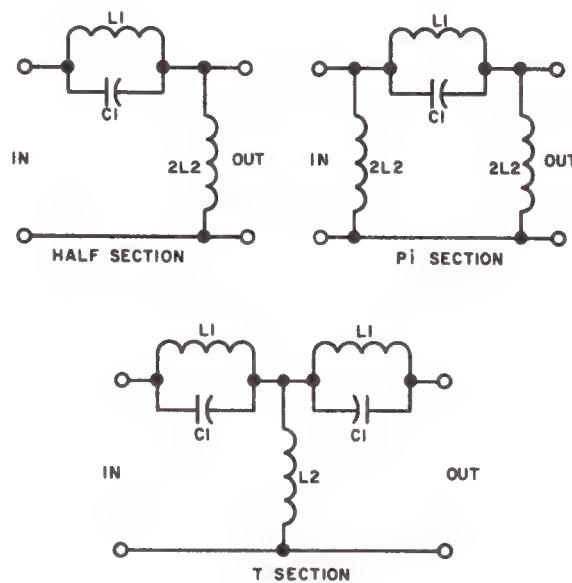The shunt-connected type of m -derived filter is shown in the following figure.



Shunt m -Derived High-Pass Filters

In the shunt-type filter, the high-pass action occurs by passage of the signal through the filter via capacitor $C1$ for those frequencies above f_∞ , and by attenuation of the signal due to the action of the parallel resonant circuit of $L1C1$ at the infinite attenuation frequency, f_∞ . In addition, since the inductive reactance of $L2$ increases with frequency, the lower frequencies below f_0 are shunted across the output and lost. Since the parallel-resonant circuit of $L1C1$ represents a high impedance at resonance, frequencies around f_∞ (depending upon the circuit Q) are greatly attenuated and are prevented from passing through the filter. This type of operation is mostly used for the band-rejection type of filter, to be discussed later in this section.

In the m -derived filter, m is a design constant from which the filter gets its name. This constant basically represents a coupling factor, and appears in all the design formulas. It is some value less than 1, usually 0.6. Thus, the frequency of infinite attenuation is:

$f_{\infty} = f_0 \sqrt{1-m^2}$, which for a cutoff frequency of 7000 kHz and an m of 0.6 is, by substituting values, $7000 \times \sqrt{1-0.36} = 7000 \times 0.8$, or 5600 kHz. The cutoff frequency for the m -derived high-pass filter is: $f_0 = 1/(\pi\sqrt{LC})$.

In this case the value of m determines the final values of L and C . When the cutoff frequency and the frequency of infinite attenuation are known, m can be determined from the formula:

$$m = \sqrt{1 - \frac{f_{\infty}^2}{f_0^2}}$$

If the frequency values in the example above are substituted in this formula, it will be seen that m is 0.6, as selected above. When m is equal to 1, the m -derived filter and the constant k filter are identical. Values of m smaller than 0.6 move f_{∞} closer to f_0 (sharpen the cutoff), and values greater than 0.6 move f_{∞} farther from f_0 (broaden the cutoff).

In the schematic illustrations of the filter sections shown previously, various values of L and C are indicated. These indicators merely show that the design values of L and C as chosen are either that of the original value, or are multiplied by (or divided by) 2 to produce the proper total value for use in the configuration illustrated. This change of value is necessitated by the requirements for proper matching, and for the connection of cascaded filter sections to produce the desired performance. For example, when connecting two Pi-sections together, the input and output inductors parallel the output and input inductors, respectively, of the next or preceding section. Since inductors in parallel have half the value of the original inductance, these networks normally use a value of $2L$ where more than a single section is to be connected in a ladder-type network. For further information, the interested reader is referred to standard textbooks on filter design.

Failure Analysis.

Generally speaking, either the filter performs as designed or it does not. Any open or short-circuited condition of the individual parts can lead to one of three possibilities: the open part may cause a no-output condition; the short-circuited part may cause a no-output or a reduced-output condition; or the defective part may be located in a position in the circuit that markedly affects the filter cutoff fre-

quency, pass band, or attenuation characteristics. Usually, all three of these last mentioned conditions are affected to some extent. Therefore, it becomes rather difficult to determine whether the filter is faulty and to spot the defective part with simple servicing techniques. In most instances, a check for continuity with an ohmmeter will indicate any open-circuited parts. In the case of the capacitors in the network, they can be checked with an in-circuit type of capacitance tester for the proper capacitance. Any short-circuited capacitor should be found during the resistance and continuity check. Where a low-frequency inductor is under suspicion, the resistance may be used as a guide; but when the resistance is so low that it is less than an ohm (as in high-frequency coils), the suspected coil must be disconnected and checked in an inductance bridge.

If a filter is suspected of operating improperly and the cutoff frequency is known (if not, it can be calculated approximately by using the formulas referenced in the preceding discussion of circuit operation), a pass band check can be made with an oscilloscope (and an r-f probe) and a signal generator. With the signal generator modulated and simulating the input signal, the output of the filter is observed on the oscilloscope (use the vertical height of the modulation supplied by the r-f probe as an indication of relative amplitude). For a high-pass filter, the height of the pattern should decrease rapidly as the cutoff frequency is passed (while reducing frequency), and the pattern should stay at approximately the same height for frequencies above cutoff. If such indications are obtained, the filter is probably operative, and some other portion of the associated circuit is at fault. If these indications are not obtained, the filter is definitely at fault, and each part must be individually checked for the proper value.

LOW-PASS FILTERS

Application.

Low-pass filters are used in circuits where it is desired to pass only the lower frequencies and to attenuate any frequencies above a selected cut-off frequency.

Characteristics.

Resistance-capacitance (RC) type filters are generally used for audio frequency applications, whereas

inductance-capacitance (LC) types of filters are used for both audio and radio frequencies, particularly for wherever sharp cutoff is required.

The lower the frequency below cut off, the lower is the attenuation; above the cut-off frequency the attenuation increases as the frequency increases.

May consist of half-sections, single sections, or multiple sections, with the multiple-section type providing the greatest attenuation and the sharpest cutoff.

May be of either the constant k or m -derived form, or any combination thereof.

Circuit Analysis.


General. The low-pass filter circuit consists of resistance or inductance together with capacitance combined and connected in such a manner that they have a definite frequency response characteristic. The low-pass filter is designed to permit the passage of low frequency signals over a desired range of frequencies, and to attenuate the higher frequencies above this range. The frequency range over which the passage occurs is called the *pass band*, the range over which attenuation or poor transmission occurs is called the *attenuation band*. The frequency at which the attenuation of a signal starts to increase rapidly is known as the *cutoff frequency*. The basic configurations into which the low-pass filter elements can be assembled or arranged are the "L" or half-section, the "T" or full section, and the Pi type.

The L-section filter consists of one series resistor or inductor, and one parallel component of either resistance or capacitance. The T-type filter consists of two series inductors and one shunt resistance or capacitance. The Pi-type consists of one series inductor and two resistive or capacitive shunts, resembling the Greek letter π (Pi) from whence it takes its name. Several sections (or half sections) of the same circuit configuration can be joined to improve the attenuation or transmission characteristics of the filter. When several sections are cascaded together, they form a *ladder* type of filter. When a filter is inserted into a circuit it is usually terminated (matched) by a resistance or impedance of the same value at the input end. The value of the terminating resistance or impedance is usually determined by the circuit with which the

filter is used and the type of filter circuit employed.


The cutoff frequency of a filter is determined by the circuit configuration, type of filter (constant k or m -derived), and the values of the inductors and resistors (or capacitors) in the filter circuit. When the cut-off frequency is known, the value of the parts necessary to produce this response and the desired attenuation may be calculated mathematically by the use of the proper formulas. This handbook will not be concerned with design data, but will show the circuit configuration, explain circuit action, and provide information with which the technician can determine or recognize the type of filter and determine the cut-off frequency, if needed.

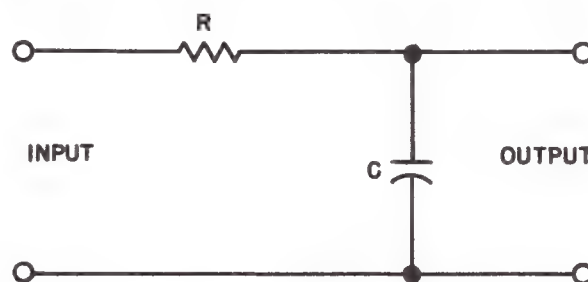Circuit Operation. A typical half-section R-C low-pass filter is shown in the accompanying illustration.



Half-Section R-C Low Pass Filter


Note that the output is taken across the capacitor and the resistor is connected in series. The circuit is basically that of a voltage divider in which C forms the reactive part, and R the resistive arm. If the values are selected so that the capacitive reactance of C is equal to the resistance of R at frequency f_0 , then the output voltage of the voltage divider network will be attenuated approximately 3 dB with respect to that of the input voltage. This frequency is called the theoretical *cutoff frequency*, and its value is given by: $f_0 = 1/2\pi RC$ in Hertz. The values of R and C are in ohms and farads (or in megohms and microfarads), and RC is the time constant in seconds. A similar half-section low-pass filter arrangement using inductance and resistance (R-L) is shown in the accompanying illustration.

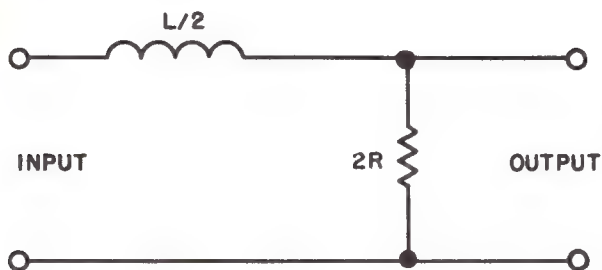

Half-Section R-L Low Pass Filter

Note that in this instance the output is taken across the resistor and that the reactance is connected in series. The circuit also is a voltage divider in which L forms the reactive arm, and R the resistive arm. If the values are selected so that the inductive reactance of L is equal to the resistance of R at f_0 , then the output voltage of the voltage divider will be attenuated approximately 3 dB with respect to the input voltage. The theoretical frequency in this instance is found by the formula: $f_0 = 2 \pi RL$, in Hertz, with R and L in ohms and farads, and RL is the time constant in seconds.

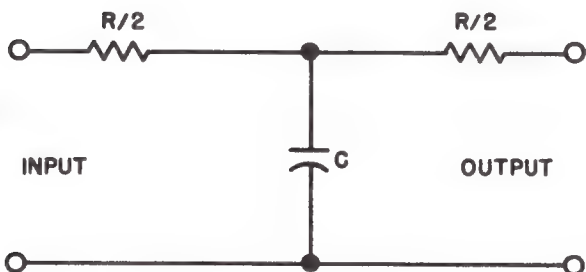
Consider now a T-section filter as illustrated in the accompanying figure. This circuit arrangement forms a full section which can be considered as two half-sections (L sections) placed back to back.



T-Section R-C Low-Pass Filter

Note that in this circuit arrangement the two resistors are connected in series; consequently the design value of R is halved. Likewise, the design value of C is halved, since the two capacitors are paralleled thereby

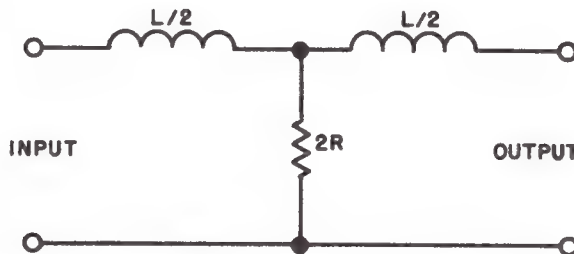
making the effective capacitance equal to the value of a single half section. The T-arrangement provides a symmetrical input and output with the same time constant as the single-section L-type figure. A typical T network using RL components is shown in the accompanying illustration.



T-Section R-L Low-Pass Filter

In this instance, since the inductors are in series, only half the inductance is used in each and, since the resistors are effectively in parallel, the half-section resistance value is multiplied by 2. The T-section supplies a symmetrical input and output with a time constant equal to that of the single half-section.

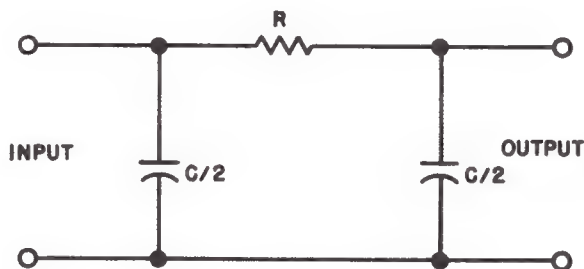A typical Pi-section filter network is shown in the accompanying diagram.




Pi-Section R-C Low Pass Filter

In this full section arrangement the value of the resistive arm is equal to the value of two half sections, while the value of the capacitor is half the total value. Note that in any of the previously discussed filter arrangements the actual time constant values are identical. Therefore, the response and attenuation of each

are also identical. L-sections are used where only a simple unbalanced input and output is needed. The T- and Pi-sections are used where balanced arrangements are required. Multiple section filters are used to obtain greater phase shift and more attenuation. Thus, a two-section filter using identical values of parts will multiply the phase shift and attenuation by a factor of two. For complete design data refer to a standard text.

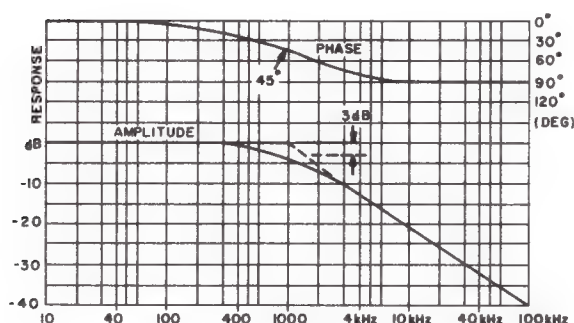In any of the filter arrangements previously discussed the attenuation is assumed to be zero immediately below the cutoff frequency, f_0 , and very large for frequencies above f_0 , as shown in the following response graph.




Phase and Amplitude Response Characteristics
for Low Pass Filter ($f_0 = 1,000 \text{ Hz}$)

However, as can be seen from the chart, the attenuation (for a single-section filter) becomes relatively constant at 12 dB/octave (20 dB per decade) at frequencies considerably above cutoff. The phase shift ranges from zero at the lower frequencies below cutoff to 45 degrees at f_0 . Above the cutoff frequency the phase shift soon becomes constant at 90 degrees. The dotted line indicates how this typical Bode plot is rounded off to simulate practical conditions. As a result, a 3 dB difference exists between the actual and theoretical response at the cutoff frequency.

The effect of a low-pass filter on the response of a rectangular pulse is indicative of the action produced by this type of filter. Since the output voltage is taken from across the capacitor, which is in series with the resistor and the input circuit, it is evident before the pulse is applied, there is no charge in the capacitor and no current in the circuit. Therefore, no voltage output is obtained. Upon application of the rectangular pulse the initial current is equal to E/R .

Since the capacitor cannot change its charge instantly, the high charging current drops the voltage across the resistance and the output voltage rises exponentially as the capacitor charges. Thus, as the capacitor charges the current through the resistor decreases, while the voltage across the capacitor increases correspondingly. Eventually the capacitor charges to the full input voltage and the output voltage is at a maximum. The output voltage stays at this value for the remainder of the pulse. At the end of the pulse the capacitor discharges, also exponentially, and the output voltage eventually decreases to zero.

The following figure shows the overall response of a low-pass filter to a rectangular pulse of 15 microseconds duration with different time constant values (R times C). From the previous explanation, it is clear that both the rise and fall times of the pulse are greatly affected. The effect is least for a small time constant. For example, consider the response of an RC circuit with a time constant of 1 microsecond to a rectangular pulse of 15 microseconds duration.

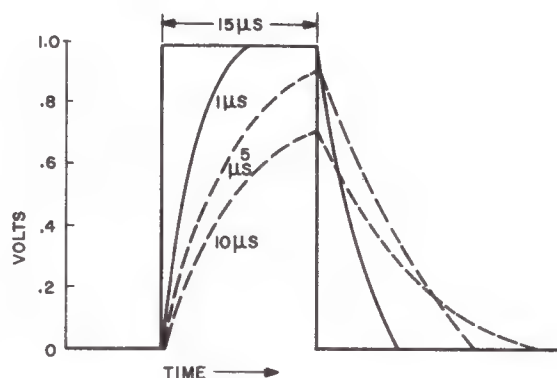


Typical Pulse Response Variation with Time
Constant or Pulse Width Changes

Since the rise time is taken between the 10% and 90% amplitude limits of the pulse, we see from a universal time constant table that the leading edge reaches its maximum of 90% amplitude in 2.2 microseconds and remains approximately at this value for the remaining 12.7 microseconds (7 time constants are required to reach full amplitude). When the pulse ends, the decay time follows the same curve and the

capacitor is 90% discharged in 2.2 microseconds, and completely discharged before the beginning of the next pulse. Consider now the response curve for a 5 microsecond time constant. In this case the leading edge of the pulse rises to 90% of maximum in two time constants, the pulse is terminated and decays to zero in the next two time constants. Because of the increase of time constant the capacitor charges to only 90% of the maximum and the output voltage is 10% less than for the 1 microsecond condition. For the extremely long time constant of 10 microseconds it takes the entire pulse duration of 15 microseconds for the pulse to reach approximately 78% amplitude. Thus the longer the time constant the lower is the output amplitude and the more distorted is the pulse.

Since RC filters respond to the time constant of the circuit, it is evident that while filters of many sections can be used, the simple equivalent time constant of the circuit basically determines the filter characteristics, and that really sharp cutoff cannot be obtained. With the use of L-C filter circuits however, it is possible to produce the desired pass band with much sharper cutoff and attenuation characteristics. Since both inductance and capacitance are used, a single-section L-C filter is capable of a 180 degree phase shift.

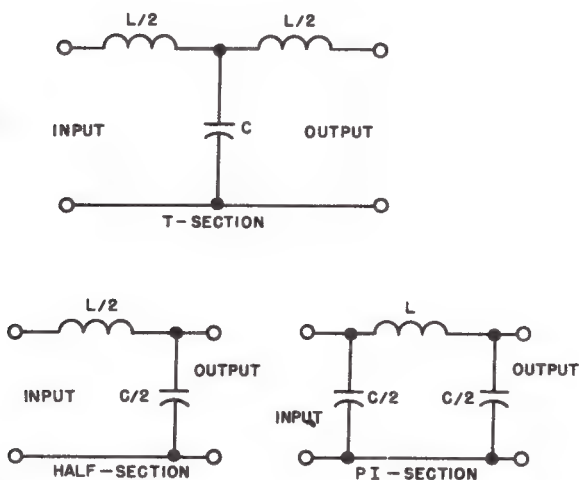Low pass filter circuits using inductance and capacitance follow the same type of circuit configuration as do R-C filters as shown in the accompanying figure.



Low-Pass L-C Filter Circuits


In the L-type low-pass filter using L-C components the high frequencies applied to the input are offered a relatively high inductive reactance by series inductor L , and a low capacitive reactance through the shunt path to ground provided by capacitor C . Therefore, the high frequency signals are attenuated by L and effectively shunted to ground by C if they pass the inductor. On the other hand, the low frequencies are offered little opposition by L and high opposition by C . Therefore, the lower frequencies pass from input to output with little attenuation. The T-type filter operates identically with the half section filter, but provides a symmetrical input and output configuration with the same time constant as a single section L-type filter. The Pi-type filter is actually formed from two inverted L-type filters and provides slightly better cutoff and attenuation. In this case the high frequencies are first offered a low impedance path to ground by the first filter capacitor with high attenuation offered by the series inductor. Any remaining high frequency signals are then effectively shunted to ground by the low impedance of the second (output) capacitor. The basic L-type filter is used where only a simple unbalanced input and output are required. The T- and Pi-types of filter are used where balanced arrangements are necessary.

Basic filter theory stipulates that where reactances of the same sign (either all capacitance or all inductance) are used, the characteristic filter impedance presented by the filter to the input or the output circuit is a reactance. On the other hand, where reactances of opposite sign are used (such as capacitance and inductance), the characteristic impedance becomes resistive over one range and reactive over another range. Thus the design and matching of filters becomes an engineering problem, and is treated on an ideal theoretical basis. This means that while a filter may be considered to have infinite rejection beyond a particular cutoff frequency, in practice the result may not be great as predicted. Likewise, the critical cutoff frequency may not be as sharp or as critical as the design figures indicate.

All the previously discussed filter arrangements are of the *constant k* type, which has a gradual rather than a sharp cutoff frequency. In this simple type of filter the series filter arm impedance, Z_1 and the shunt filter arm impedance, Z_2 , are so related that their product is a constant at all frequencies ($Z_1 \times Z_2 = k^2$). Therefore, it derives its name from this relationship. This constant, in turn, is also equal to R^2 ,

since Z_1 and Z_2 are reciprocal reactances (X_L and X_C , respectively), and $R^2 = L/C$. Thus the formula for determining the cutoff frequency becomes: $f_0 = 1/4\pi\sqrt{LC}$, where L and C are in henrys and farads, respectively.

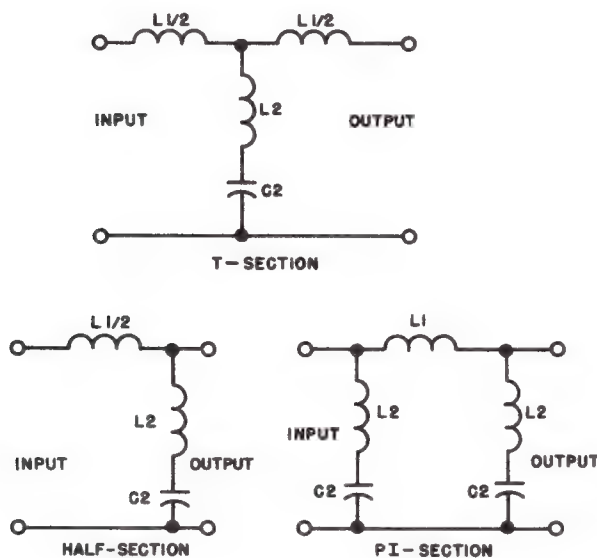
A more complex form of low-pass filter circuit is the *m-derived* type. In this type of filter the cutoff frequency is sharper, and the total attenuation of the unwanted frequencies is greater. Typical circuits of the series-connected *m-derived* type are shown in the accompanying illustration.



Series *m*-Derived Low-Pass Filters


As can be seen from the illustration, a series-connected L-C network (L_2C_2) is placed across the input/output or across the mid-termination of the filter network. As designed, this network is made series-resonant at a frequency above the usual cutoff frequency. For the low-pass filter this resonant frequency, called the *frequency of infinite attenuation* (f_∞) is selected at a value of about $1.25 f_0$. Since f_∞ is resonant and is series connected across the input or the output it represents a short circuit across the filter for the resonant frequency (with a pass band de-

termined by the Q and resistance of the circuits). Therefore, the normally sloping attenuation characteristic which approximates 12 dB/octave for the constant k filter is "notched" off. In effect, the *m*-derived filter is sharply separated from the frequencies above f_∞ and therefore, provides sharper and better cut-off of the higher frequencies. The action described can be visualized more clearly when the attenuation (response) characteristics for the two types of filters are compared as shown in the following figure.

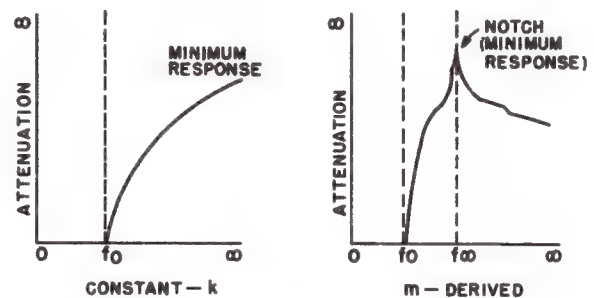


Comparison of Filter Attenuation Characteristics

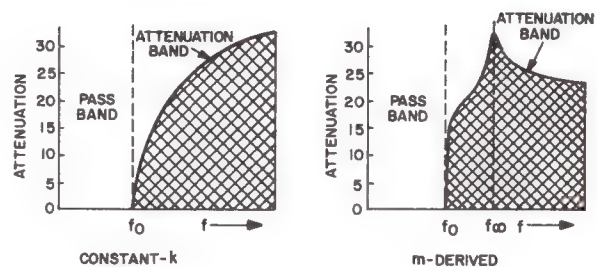While a constant attenuation is shown for the constant k type, with a reduced value of attenuation below f_∞ for the *m*-derived type, the sharpness of *m*-derived cutoff at f_∞ (assuming zero circuit resistance at resonance) provides better low-pass performance, as illustrated below.



Comparison of Transmission Characteristics

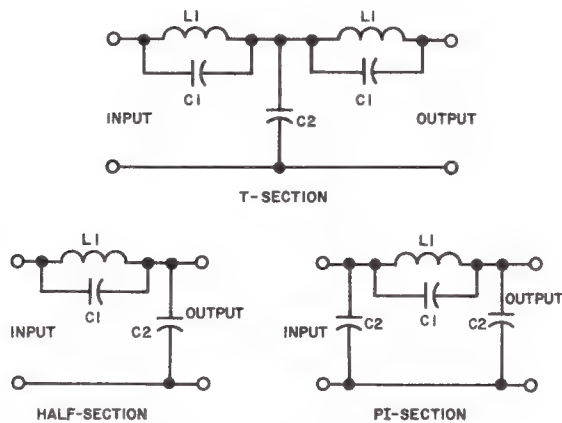The shunt-connected type of m -derived filter is shown in the following figure.



Shunt m -Derived High Pass Filters

In the shunt-type filter the low-pass action occurs by the shunting of the high frequencies to ground via capacitor $C2$ for those frequencies above f_∞ , and by attenuation of the signal due to the action of the parallel resonant circuit of $L1-C1$ at the infinite attenuation frequency f_0 . Since the capacitive reactance of $C2$ decreases with frequency the higher frequencies above f_0 are shunted to ground and lost. Since the parallel-resonant circuit of $L1C1$ represents a high impedance at resonance, frequencies around f_∞ (depending upon the circuit Q) are greatly attenuated and are prevented from passing through the filter. This type of action is mostly used for the band rejection type of filter to be discussed later in this section.

In the m -derived filter, m is a design constant from which the filter gets its name. This constant basically represents a coupling factor, and appears in all the design formulas. It is some value less than 1, usually 0.6. Thus the frequency of attenuation if $f_\infty = f_0/\sqrt{1-m^2}$, which for a cutoff frequency of 1000 Hz and an m of 0.6, is by substituting values, $1000/\sqrt{1-0.36} = 1000/.8$, or 1250 Hz. The cutoff frequency for the m -derived filter is $f_0 = 1/(\pi\sqrt{LC})$.

If the frequency values in the example above are substituted in this formula, it will be seen that m is equal to 0.6 as selected above. When m is equal to 1, both the constant k and the m -derived filters are identical.

Values of m smaller than 0.6 move f_∞ closer to f_0 (sharpen the cutoff), while values greater than 0.6 move f_∞ farther from f_0 (broaden the cutoff).

In the schematic illustrations of the filters shown previously, various values of L and C are indicated. These indicators merely show that the design values of L and C are shown to be multiplied or divided by 2 to produce the proper value for the configuration illustrated. This change of value is necessitated by the requirements for proper matching, and for the connection of cascaded filter sections to produce the desired performance. For example, when connected two Pi-sections together the input and output capacitors parallel the input and output capacitors, respectively of the next or preceding section. Since capacitors in parallel have twice the value of the original capacitance, these networks normally use a value of $C/2$ where more than a single section is to be connected in a ladder type network. For further information, the interested reader is referred to standard textbooks on filter design.

Failure Analysis.

Generally speaking, either the filter performs as designed or it does not. Any open or short circuited condition of the individual parts can lead to one of three possibilities: the open part may cause a no-output condition; the short-circuited part may cause either a no-output or a reduced-output condition; or the part may be located in a portion of the circuit that markedly affects the filter cutoff frequency, pass band, or attenuation characteristics. Usually all three of these last mentioned conditions are affected to some extent. Therefore, it becomes rather difficult to determine whether the filter is faulty and to spot the defective part with simple servicing techniques. In most instances, a check for continuity with an ohmmeter will indicate any open-circuited parts. In the case of the capacitors in the network, they can be checked with an in-circuit type of capacitance tester for the proper capacitance. Any short-circuited capacitor should be found during the resistance and continuity check. Where a low frequency inductor is under suspicion, the dc resistance may be used as a guide; but where the resistance is so low that it is less than one ohm (as in high frequency coils) the suspected coil must be disconnected and checked with an inductance bridge.

If a filter is suspected of operating improperly and the cutoff frequency is known (if not, it can be calculated approximately by using the formulas referenced in the preceding discussion of circuit operation), and a band-pass check can be made with an oscilloscope and a signal generator. With the signal generator modulated and simulating the input signal, the output of the filter is observed on the oscilloscope. For a low pass filter the height of the pattern should decrease rapidly as the cutoff frequency is passed (while increasing the frequency), and the pattern should stay at approximately the same height for frequencies below cutoff. If such indications are obtained the filter is most probably operative, and some other portion of the associated circuit is at fault. If these indications are not obtained, the filter is definitely at fault, and each part must be checked individually for proper value.

BAND-PASS FILTERS

Application.

Band-pass filter circuits are used to allow frequencies within a certain frequency band to be passed or transmitted with minimum attenuation and to block all frequencies above and below this frequency band.

Characteristics.

Uses L-C type filters.

Frequencies between lower and upper cutoff frequencies are passed with little attenuation; frequencies above and below these values are attenuated.

Series and parallel resonant circuits combined with a series or shunting inductance or capacitor are used to develop each configuration.

Attenuation and cutoff varies with the number of elements used (the greater the number of elements, the greater is the attenuation and the sharper the cutoff).

Circuit Analysis.

General. The band-pass filter circuit consists of inductive and capacitive components combined and connected in such a manner that they have definite frequency response characteristics. The band-pass filter is designed to permit the passage of frequencies within a desired range or band width, and to attenuate any frequencies not in this range. The range of frequencies which is capable of being passed is re-


ferred to as *pass-band*, the range of frequencies above and below the pass band, where attenuation or poor transmission occurs is called the *attenuation band*. The frequency at which the attenuation of a signal starts to increase rapidly is known as the *cutoff frequency*. The basic configurations into which the band-pass filter elements can be assembled or arranged are the "L" or *half-section*, the "T" or *full-section*, and the *Pi* section.

The L-section filter consists of one inductive component, capacitive component, or one combination of inductive and capacitive components in series with the input and output, together with one inductive component, capacitive components, or combination of inductive and capacitive components shunting the input and output. The T-type filter consists of two series (inductive and/or capacitive) component groups separated by one component group shunting the input and output. The Pi-type consists of one series component group between two component groups shunting the input and output. Several sections or half-sections can be joined to improve the attenuation or transmission characteristics of the filter. When several sections are cascaded together, they form a *ladder* type of filter. When a filter is inserted into a circuit it is usually terminated (matched) by a resistance or impedance of the same value at the input end. The value of the terminating resistance or impedance is usually determined by the circuit with which the filter is used and the type of filter circuit employed.

The cutoff frequency of a filter is determined by the circuit configuration, type of filter (*constant k* or *m derived*), and the values of the inductors and capacitors in the filter circuit. When the cutoff frequency is known, the value of the parts necessary to produce this response and the desired attenuation may be calculated mathematically by the use of the proper formulas. This handbook will not be concerned with design data, but will show the circuit configuration, explain circuit action, and provide information with which the technician can determine or recognize the type of filter and in most cases, determine the cutoff frequencies if needed.

Circuit Operation. A typical half-section band-pass filter is shown in the accompanying illustration. This is a *constant k* type band-pass filter. The band-pass of frequencies is offered a low impedance by the series resonant circuit, and a high impedance by the parallel resonant circuit which shunts the input and output. The resonant circuits are tuned to frequencies within

the band-pass. All frequencies on either side of the band-pass are offered a high impedance by the series resonant circuit and a decreased impedance by the shunting resonant circuit; therefore, the frequencies outside of the band-pass are transferred with little or no attenuation. The T-type filter operates identically to the half-section or L-section filter, but provides a symmetrical input and output configuration. The Pi-type filter is actually formed from two series connected inverted L-type half-section filters and provides slightly better cutoff and attenuation than the single half-section. In this case, the attenuation-band of frequencies is offered a low impedance path to ground by the first shunting parallel resonant circuit and a high impedance by the series resonant circuit. Any remaining attenuation-band frequency signals are shunted to ground by the low impedance of the second parallel resonant circuit. The basic L half-section filter is used where only a simple unbalanced input and output are required. The T- and Pi-section filters are used where balanced arrangements are necessary.

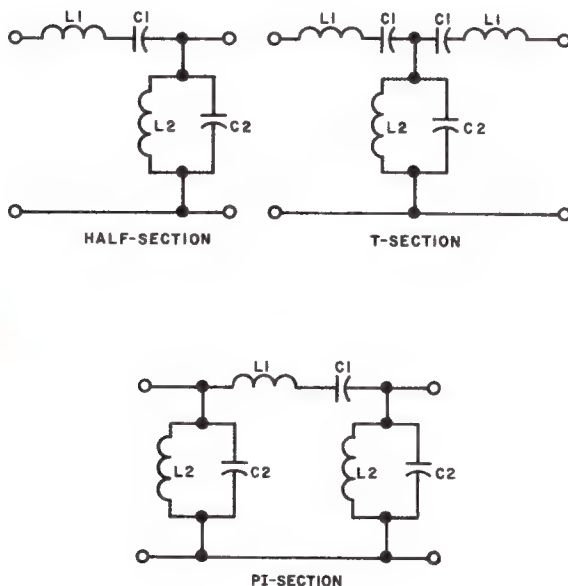


Constant k Band-Pass Filters

The design and matching of filters becomes an engineering problem, and is treated on an ideal theoretical basis. This means that while a filter may be considered to have infinite rejection beyond a particular cutoff frequency, in practice the result may not be as great as predicted. Likewise, the critical cutoff frequency may not be as sharp or as critical as the design figures indicate.

All of the previously discussed filter arrangements are of the *constant k* type, which has fairly sharp cutoff frequencies, even in its simplest form. In *constant k* type filters the product of the impedance in series with the input and output, and the impedance shunting the input and output is constant regardless of the frequency ($Z_{\text{series}} \cdot Z_{\text{shunt}} = k^2$). Therefore, it derives its name from this relationship. This constant, in turn, is also equal to R^2 (R is the value of the terminating resistance). To determine the bandwidth of the pass-band of an L-section k type filter, the formula $f_2 - f_1 = R/L_1$ may be used. To determine the value of the center frequency of the band-pass (f_c), the formula $f_c = C_1 R^2 / L_2$ may be used.

A more complex form of band-pass filter circuit is the *m-derived* type. An *m-derived* type of filter may be composed of various numbers of inductive and capacitive components in series or parallel connection within a section of the filter. An L-section *m-derived* filter for example, may contain three, four, five, or six elements within two possible series configurations and two possible shunt configurations. In order to obtain the same degree of sharpness in attenuation at both upper and lower cutoff frequencies as is obtained in a *constant k* type filter an *m-derived* filter of at least 5 elements would be required. Typical circuits of one series connected *m-derived* type 5-element, band-pass filter are shown in the accompanying illustration.

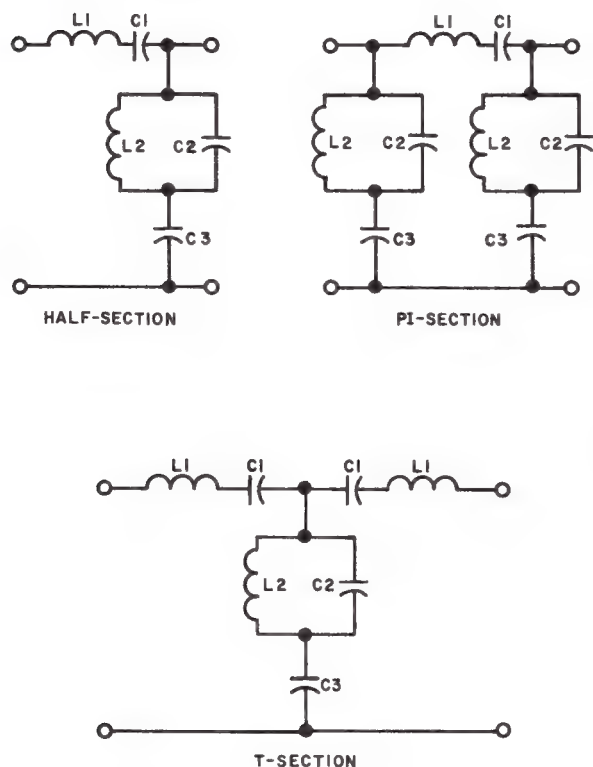


Series m -Derived, 5-Element Band-Pass Filter

These m -derived type of filters offer low series impedance, and high shunt impedance to the band-pass frequencies, since the series and shunt resonant circuits are tuned to the frequencies within the band-pass. All frequencies on either side of the band-pass are offered a greater impedance by the series resonant circuit and a decreased impedance by the shunting resonant circuit. Capacitor $C3$ is of such a value that frequencies below the band-pass are attenuated to a greater degree. Thus frequencies outside the band-pass are attenuated and the frequencies within the band-pass are not attenuated.

In the band-pass filter $f_{1\infty}$ represents the *lower frequency of infinite attenuation* and $f_{2\infty}$ represents the *higher frequency of infinite attenuation*. At f_1 and f_2 the filter effectively appears as a short circuit across the output. The 5 element series arrangement of m -derived filter (the 5th element is a capacitor) has a low frequency minimum response notch at $f_{1\infty}$, and therefore, provides sharper and better cutoff of the

lower frequencies. The action described can be visualized more clearly when attenuation (response) curves for the *constant k* and the m -derived filters are compared as shown in the accompanying diagrams. The response of the 5 element shunt arrangement m -derived filter is the same as the 5 element series arrangement m -derived filter if the fifth element of the shunt arrangement is an inductance and the fifth element of the series arrangement is a capacitor.

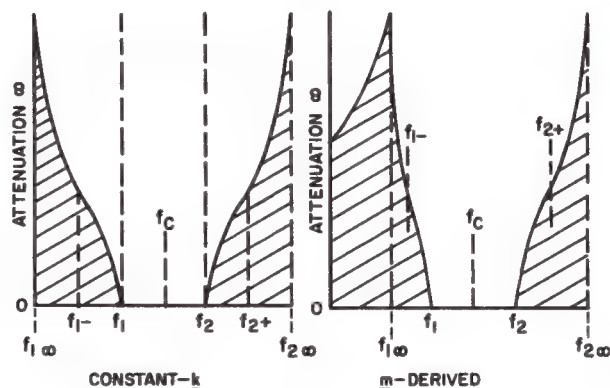


Comparison of Filter Attenuation Characteristics

The *constant k* type filter shows equal attenuation above f_2 and below f_1 (the cutoff frequencies). A steep increase in attenuation is apparent between frequencies f_2 to f_{2+} and to f_{1-} , however, once frequencies f_{2+} and f_{1-} are reached, the attenuation curve becomes more gradual until $f_{1\infty}$ and $f_{2\infty}$ are reached. In this case frequencies $f_{1\infty}$ and $f_{2\infty}$ exist at the lowest possible and highest possible frequencies. A similar attenuation slope occurs between f_2 and higher frequencies of the five element, m -derived, band-pass filter. A different slope, with a sharp minimum notch however, exists between frequency f_1 and the lower frequencies in the m -derived filter. Frequency $f_{1\infty}$ does not occur at the lowest possible frequency, but at some intermediate frequency above zero. Thus, the slope between f_1 and $f_{1\infty}$ produces a much steeper attenuation curve than the *constant k* filter for the lower frequencies, even though there is still a gradual widening of the slope between f_{1-} and $f_{1\infty}$. Between $f_{1\infty}$ and the lowest possible frequency the attenuation decreases slightly.

The shunt-connected type of five element m -derived band-pass filter is shown in the accompanying

illustration. This shunt connected filter uses three capacitors and two inductors to comprise the five necessary components as does the series-connected *m*-derived filter just described.

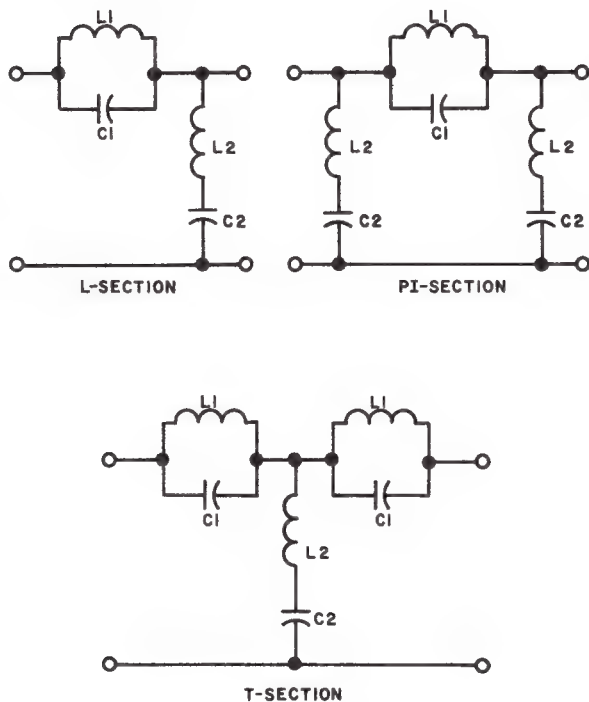

Shunt *m*-Derived Band-Pass Filter

In this 5 element shunt *m*-derived band-pass filter L_1 and C_1 form a series resonant circuit at the band-pass frequencies and L_2 - C_2 form a parallel resonant circuit. The series resonant circuit is aided by capacitor C_3 in offering a low series impedance to the band-pass, and the parallel resonant circuit offers a high impedance to the band-pass. This shunt arrangement has an attenuation curve just opposite to that of the series arrangement previously discussed, where $f_{2\infty}$ is a frequency less than a maximum frequency and $f_{1\infty}$ is at the lowest possible frequency. By using a series arrangement with three inductive components and two capacitive components the same attenuation curve is obtained.

In the *m*-derived filter, *m* is a design constant from which the filter gets its name. This constant basically represents a coupling factor, and appears in all of the design formulas. In the case of the band-pass filter

there are two *m* factors. These *m* factors have a value of 1, or less and are assigned designations m_1 and m_2 . The values of m_1 and m_2 can be computed by complex formulas based on the quantities of the lower cutoff angular frequency (f_1), the upper cutoff angular frequency (f_2), and the upper and lower frequencies of peak attenuation ($f_{2\infty}$ and $f_{1\infty}$). These design formulas are beyond the scope of this book.

Failure Analysis.

The failure analysis of the band-pass filters is essentially the same as that of the previously described low-pass filters. For this reason a failure analysis will not be repeated here. The reader is instructed to refer to the low-pass filter circuits discussion in this section of the handbook for detailed failure analysis.

BAND-REJECTION FILTERS

Application.

Band-rejection, or band-stop, filters are used in circuits where it is desired to reject or block a band of frequencies from being passed, and to allow all frequencies above and below this band to be passed with little or no attenuation.

Characteristics.

Uses L-C type filters for sharp cutoff.

Frequencies between lower and upper cutoff frequencies are attenuated; frequencies lower and greater than these values are passed with little attenuation.

May be either *constant k* or *m*-derived types.

Attenuation and cutoff varies with the number of elements used (the greater the number of elements, the greater is the attenuation and the sharper the cutoff).

Circuit Analysis.



General. The band-stop filter circuit consists of inductive and capacitive networks combined and connected in such a manner that they have a definite frequency response characteristic. The band-stop filter is designed to attenuate a specific frequency band and permit the passage of all frequencies not within this specific band. The frequency range over which attenuation or poor transmission occurs is called the *attenuation band*; the frequency range over which the

passage of signal readily occurs is called the *band-pass*. The lowest frequency at which the attenuation of a signal starts to increase rapidly is known as the *lower cutoff frequency* (f_1); and the highest frequency at which the attenuation of a signal starts to increase rapidly is known as the *upper cutoff frequency* (f_2). The basic configurations into which the band-elimination filter elements can be arranged or assembled are the L or half-section, the T-section, and the Pi-section.

The L-section filter consists of one parallel combination of inductance and capacitance in series with the input and one series combination of inductance and capacitance shunting the input. The T-type filter consists of two parallel combinations of inductance and capacitance in series with the input separated by one shunting combination of inductance and capacitance. The Pi-type filter consists of two series combinations of inductance and capacitance shunting the input and output separated by one parallel combination of inductance and capacitance connected in series with the input. Several sections (or half sections) of the same circuit configuration can be joined to improve the attenuation or transmission characteristics of the filter. When several sections are cascaded together, they form a *ladder* type of filter. When a filter is inserted into a circuit it is usually terminated (matched) by a resistance or impedance of the same value at the input end. The value of the terminating resistance or impedance is usually determined by the circuit with which the filter is used and the type of filter circuit employed.

The cutoff frequencies of a filter are determined by the circuit configuration, type of filter (*constant k* or *m-derived*), and the values of the inductors and capacitors in the filter circuit. When the cutoff frequencies are known, the value of the parts necessary to produce this response and desired attenuation may be calculated mathematically by the use of the proper formulas. This handbook will not be concerned with design data, but will show the circuit configuration, explain circuit action, and provide information with which the technician can determine or recognize the type of filter and determine the cutoff frequencies, if needed.

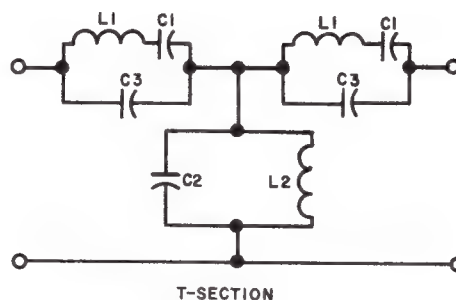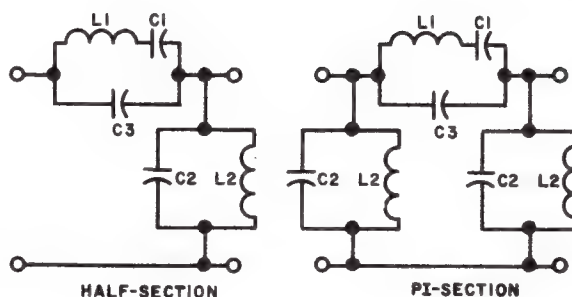Circuit Operation. Band-elimination filter circuits are shown in the accompanying illustration in L-section, T-section, and Pi-section arrangements.



Band-Rejection k-Type Filter


In the L-section band-rejection filter any frequencies not within a selected band are offered low series impedance by L_1 and C_1 and offered a high shunting impedance by L_2 and C_2 . For this reason those frequencies not within the band are easily passed from input to output with little or no attenuation. Those frequencies within the selected band are those frequencies to which L_1 and C_1 are resonant and L_2 and C_2 are resonant. The parallel resonant circuit of L_1 and C_1 offers a large series impedance to the frequencies within the rejection band and thus tends to block passage of these frequencies through the filter. The series resonant circuit of L_2 and C_2 offers almost no impedance to the frequencies within the rejection band, thus any signals in the rejection-band which may have passed through L_1 and C_1 are shunted across the output. Therefore, those frequencies within this band are greatly attenuated. The T-section series resonant circuits offer minimum impedance because at resonance the inductive reactance (X_L)

equals the capacitive reactance (X_C); and in a series circuit the impedance (Z) is equal to $\sqrt{R^2 + (X_L - X_C)}$. The impedance then, is simply equal to $\sqrt{R^2}$ or R , the dc resistance of the coil. A parallel circuit offers maximum impedance at resonance. The impedance in a parallel resonant circuit can be expressed as $Z = X_C^2/R = X_L^2/R$, (X_C being equal to X_L at resonance). By using $Z = X_L^2/R$ the formula $Z = X_L Q$ can be derived, since $Q = X_L/R$. The Q of any circuit is maximum at resonance; therefore, the impedance of a parallel resonant circuit is maximum at resonance. The T-section filter operates identically to the L-section filter, but provides a symmetrical input and output configuration with approximately the same cut off and attenuation as a single L-section filter. The Pi-section filter is actually formed from two inverted L-section filters and provides slightly better cutoff and attenuation. In this case, frequencies within the rejection-band are first offered a low impedance by the first series resonant circuit shunting the input. Any remaining signal within the rejection-band that is not shunted across the input is then attenuated by the remainder of the filter in the same manner that an L-section filter attenuates the undesired frequency band. The basic L-section filter is used where only a simple unbalanced input and output are required. The T- and Pi-sections are used where balanced arrangements are necessary.

All the previously discussed filter arrangements are of the *constant k* type. In this simple type of filter the series impedance arm, Z_1 , and the shunt filter arm impedance, Z_2 , are so related that their product is a constant at all frequencies ($Z_1 \times Z_2 = k^2$). Therefore, it derives its name from this relationship. This constant, in turn, is also equal to R^2 the squared value of the terminating resistance. In these series *constant k* type band-rejection filters the center frequency, f_c , is equal to $1/\sqrt{LC}$. Once the center frequency is obtained the bandwidth can be computed by the formula $f_2 - f_1 = f_c/Q$, where Q represents the amount of selectivity of a circuit. This value of Q equals the inductive reactance of L_1 divided by the value of the dc resistance of the inductor ($Q = X_{L1}/R$).

A more complex form of band-rejection filter circuit is the *m-derived* type. In this type of filter the cutoff frequencies (f_1 and f_2) are much sharper, and the total attenuation of the unwanted frequencies is greater. Typical circuits of the series-connected *m*-

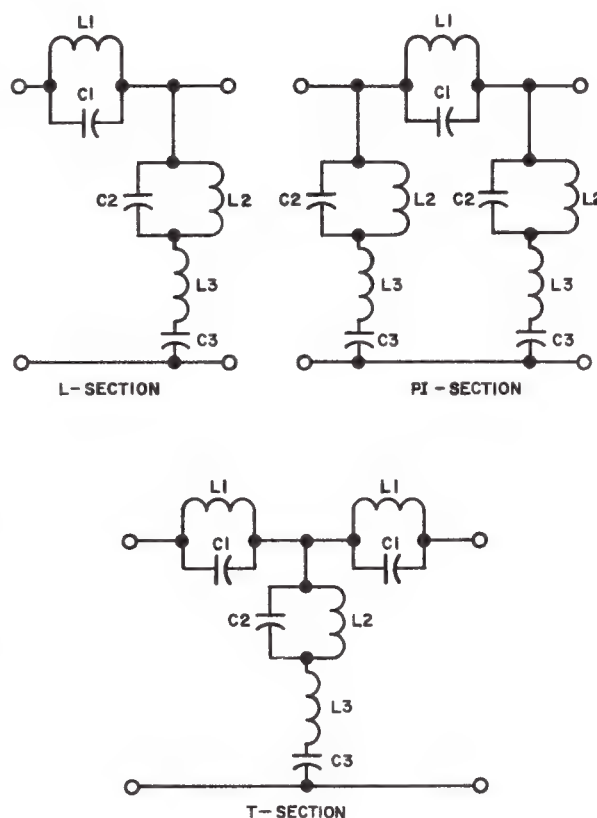
derived filters are shown in the accompanying illustration.



Series *m*-Derived Band-Stop Filters

These *m-derived* type of filters offer high series impedance, and low shunt impedance to the rejection-band frequencies, since the series and shunt resonant circuits are tuned to the frequencies within this band. All frequencies on either side of the rejection band are offered less impedance by the parallel circuit (L_1 and C_1) in series with the input and output and greater impedance by the series circuit shunting the input and output. Inductance L_2 and capacitance C_2 form a parallel circuit, which is in series with L_3 and C_3 . The values of L_2 and C_2 are chosen such that at some frequency, which corresponds to the *lower frequency of infinite attenuation* ($f_{1\infty}$), their combined reactance will form a series resonant circuit with the reactances of L_3 and C_3 . Another series resonant circuit will be formed from

these same components at the *higher frequency of infinite attenuation* ($f_{2\infty}$). At the frequencies where these resonant points occur the attenuation curve indicates sharp peaks or notches. These resonant points are not as broad as the band-width to which $L1$ and $C1$ are tuned to resonance. Therefore, the frequencies between $f_{1\infty}$ and $f_{2\infty}$, although being attenuated, are attenuated less than $f_{1\infty}$ and $f_{2\infty}$. The action described can be visualized more clearly when attenuation (response) curves for the *constant k* and *m-derived* filters are compared as shown in the accompanying illustration.

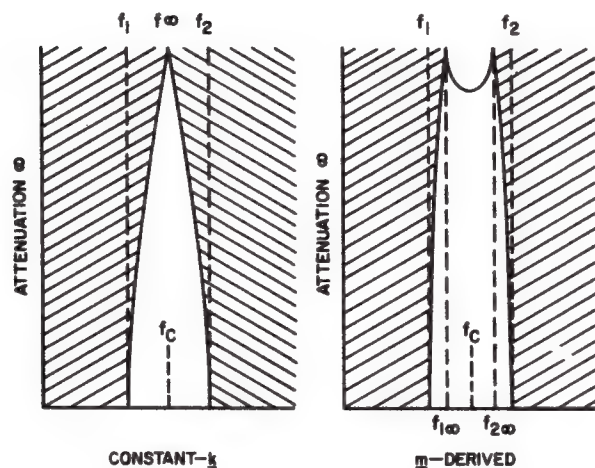


Comparison of Filter Attenuation Characteristics

The *constant k* attenuation curve shows gradual attenuation of signal from frequencies f_1 and f_2 to the center frequency f_c . The attenuation on both sides is equal, causing the resulting attenuation curve to look like an inverted cone. The frequencies of infinite attenuation intersect at f_c , and thus occur at a single frequency.

The *m-derived* attenuation curve shows a much steeper and sharper attenuation at frequencies f_1 and f_2 . Furthermore, the attenuation slopes from f_1 and f_2 do not intersect at the center frequency, but reach frequencies of infinite attenuation on both sides of the center frequency represented by $f_{1\infty}$ and $f_{2\infty}$. From these frequencies of infinite attenuation the

attenuation decreases nonlinearly toward the center frequency. This *m-derived* attenuation curve is representative of both series *m-derived* and shunt *m-derived* band-rejection filters.

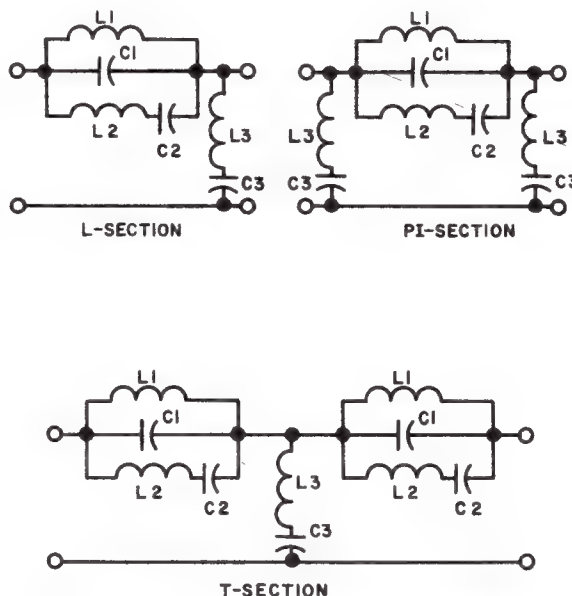The shunt *m-derived* band-rejection filter is shown in the accompanying illustration. It is composed of a parallel series network in series with the input and output, and a series network shunting the input and output.



Shunt *m*-Derived Band-Elimination Filter

In the shunt *m-derived* band-stop filter inductor $L2$ and capacitor $C2$ are added to a *constant k* configuration band-stop filter. $L2$ and $C2$ are of such a value that they in conjunction with $L1$ and $C1$ form a parallel resonant circuit at frequencies $f_{1\infty}$ and $f_{2\infty}$. This causes the attenuation to increase above the normal attenuation between the cutoff frequencies f_1 and f_2 caused by the parallel resonant circuit of $L1$ and $C1$ and the series resonant circuit $C3$ and $L3$. After $f_{1\infty}$ and $f_{2\infty}$ the attenuation decreases toward the center frequency, since $L2$ and $C2$ in conjunction with $L1$ and $C1$ are tuned very sharply to and the two frequencies $f_{1\infty}$ and $f_{2\infty}$.

In the *m-derived* filter, *m* is a design constant from which the filter gets its name. This constant basically represents a coupling factor, and appears in all design formulas. The *m* factor has a value of 1 or less. The value of *m* can be found by the following formula: $m = \sqrt{1 - (f_{2\infty} - f_{1\infty})^2 / (f_2 - f_1)^2}$.

Failure Analysis.

The failure analysis of the band-rejection filters is essentially the same as that of the previously described low-pass filters and band-pass filters. For this reason, a failure analysis will not be repeated here. The reader is instructed to refer to the low-pass filter circuits discussion in this section of the handbook for detailed failure analysis.



SECTION 5
AMPLIFIERS

PART 5-0. INTRODUCTION

BIASING METHODS (ELECTRON TUBE)

General.


An electron tube is normally biased through the application of a negative dc potential (grid bias) between the grid and cathode elements. Grid bias is either obtained from a separate voltage supply source set for a specific fixed voltage, or developed by the flow of cathode or control grid current in the tube; bias developed by tube current is referred to as "self-bias". The grid bias determines the static (quiescent) operating current for the applied plate voltage and thus sets the operating point. When an input signal is applied to the grid, it adds to or subtracts from the initial bias in accordance with instantaneous signal variations and correspondingly varies the plate current and voltage to produce the desired output signal.

Usually bias may be obtained by any of a number of methods; the basic circuits are discussed in the following paragraphs. For ease of explanation, triode type electron tubes are used, but biasing methods are applicable to other types of electron tubes if the currents and voltages taken by the additional electrodes are properly considered.


Cathode Bias.

When the cathode of an electron tube is biased positively with respect to the grid, the electron tube operates exactly as though an equivalent negative bias is applied to the grid. A tube using cathode bias is shown in the accompanying illustration. Since current flow within an electron tube is from cathode to plate, cathode resistor R_k can be inserted between cathode and B- to produce a voltage drop (cathode bias) as long as the plate current flows continuously. Since cathode current always flows in the same direction, the voltage drop remains more positive at the

cathode. Thus plate current flow within the electron tube itself produces a positive cathode bias. The amount of bias obtained depends upon the total tube current and the size of the cathode resistor ($I_{T_k} \cdot R_k$).

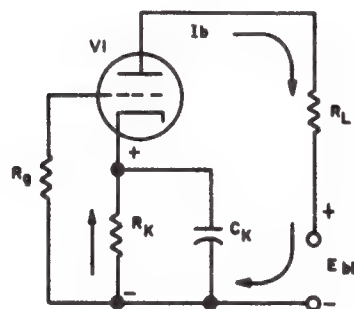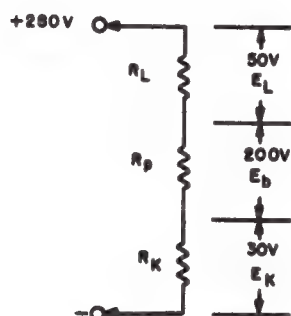**Cathode Bias**

This type of bias is restricted in use to amplifiers in which plate current flows for more than half of each cycle of operation, because plate current flow cannot be cut off, or the developed bias will be lost. But it can be used in combination with a fixed minimum bias to limit maximum plate excursions or as a protective bias which limits plate current to a safe value when grid drive is removed. An inherent disadvantage of this circuit is that the developed bias voltage is subtracted from the plate voltage applied to the electron tube. This if 30 volts cathode bias is needed with a 250-volt plate supply, the power supply must be able to furnish 280 volts, as shown in the accompanying illustration.




Bias Voltage Divider Network


Its greatest advantage is that it is simple to use and economical of parts. When used in audio, video, or radio-frequency circuits, the cathode resistor must always be adequately bypassed to prevent a constant change of bias with signal. If the cathode is not bypassed, any change in plate current will produce a corresponding change in cathode bias voltage. The change in cathode voltage will be in such a direction as to oppose the effects of the input signal, and therefore will have the same effect as degenerative feedback. While a controlled amount of degenerative feedback can be beneficial in extending the over-all frequency response and in reducing distortion, a large amount of degenerative feedback will result in a serious loss of amplification. When the cathode bias resistor is adequately bypassed, the fluctuating ac plate current caused by the input signal is effectively shunted around the cathode bias resistor, through a much lower reactance path offered by the bypass capacitor. Thus only the dc component of plate current flows through the bias resistor, and the total cathode current remains constant at the initial static (dc) value of no-signal current, and is unchanged by the varying input signal. For satisfactory bypassing, the bypass reactance should be about 10% of the dc bias resistance at the lowest frequencies used. Cathode bias is usually used in audio-frequency or video-frequency amplifiers and in low power r-f amplifiers and test equipment. In some applications, such as high fidelity audio amplifiers or video i-f amplifiers, a relatively small value of unbypassed cathode resistance may be used. The degenerative action of this resistance increases the fidelity (frequency response) of the stage and reduces the possibility of overloading from strong signals.

Grid-Leak Bias.

Grid-leak bias, sometimes called *signal bias*, is obtained by allowing grid current flow, produced by the ac input signal, to charge an R-C network in the grid-cathode circuit. Two basic circuits are used to develop this form of bias—the shunt type and the series type. These two types are shown in the accompanying illustration. The methods of developing grid voltage in these circuits are similar, but the physical connections of the network components are different.

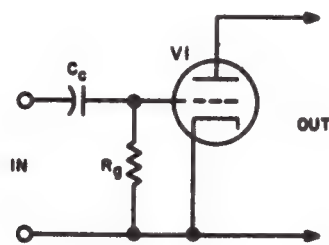

Shunt Grid-leak Bias

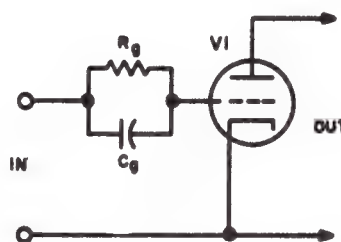



Series Grid-leak Bias

The grid-cathode circuit is used as a diode rectifier to develop a dc voltage that is proportional to the positive peak input (driving) signal amplitude. Grid-leak capacitor C_g operates as a coupling capacitor to apply the input (driving) signal to the grid. On the positive input signal excursions the grid is driven positive causing grid current to flow between grid and cathode and through grid-leak resistor R_g . The result is to produce a dc voltage across R_g which is polarized negatively at the grid. The grid-leak capacitor, C_g , is effectively connected in series with the applied input signal, as shown by the equivalent charging circuit shown in part A of the accompanying illustration.

As long as the input signal remains positive, the coupling capacitor charges. When the input signal

becomes negative (part B of the illustration), grid capacitor C_c begins discharging through the grid leak; during the discharge period the grid is held negative by the charge remaining in the capacitor plus the negative input signal, and no grid current flows. The grid-leak time constant is made long with respect to the signal frequency (usually seven times the period for one input cycle) so that the discharge is relatively slow. The charge time is much faster than the discharge time because the grid leak is effectively shunted by the flow of grid current and offers a low resistance of about 500 ohms (r_{gk} , part A) in comparison with the large resistance of R_g . When the signal begins its next positive excursion, C_c again starts to charge while still retaining a certain amount of residual charge. The cycle resumes and the action is repeated. After only a few more cycles, the grid bias stabilizes, since only a small portion of each charge leaks off before the application of the next positive half of the input signal. The residual charge on the coupling capacitor will not permit the next positive portion of the input signal to drive the grid as far positive as the positive portion did in the first half cycle. Thus the additional charge placed on C_c is not as great as it was for the first half cycle, but when added to the residual charge that remained, it causes the total bias to increase. This process of rapid charging and slow discharging of C_c leads to the steady state condition of operation, in which the

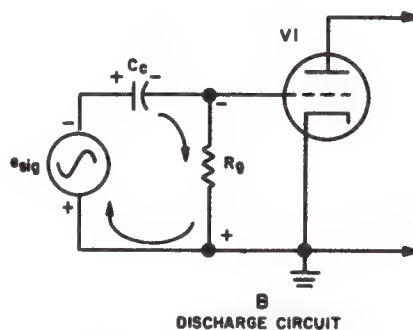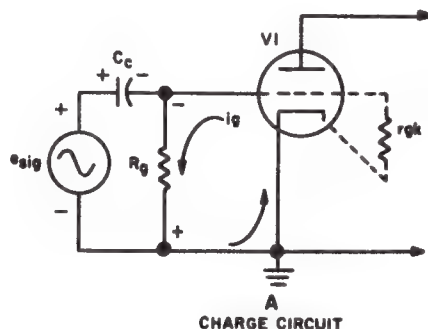amount of charge deposited on each positive half cycle exactly equals the amount of charge lost through discharge on each negative half cycle.



Simplified Charge and Discharge Circuits

The amount of bias developed in this manner depends upon the amplitude and frequency of the applied input signal and the time constant of the grid network. The greater the amplitude of the input (grid-driving) signal, the greater the amount of bias that will be developed. Also, the longer the time constant of the grid circuit with respect to the input frequency, the greater the amount of bias that will be developed. However, there are practical limitations to the length of time constant which may be employed. Too long a time constant will prevent the bias voltage from changing enough during a cycle, or group of cycles, to bring the stage out of cutoff. Therefore, the stage must wait until the bias has been reduced enough to allow it to come out of cutoff; as a result, the stage will operate intermittently (motorboat). When functioning properly, a grid-leak bias network should produce a dc voltage that is approximately 90% of the applied positive peak voltage. Under these conditions grid current will flow for only a small portion of the positive peak of the input cycle. Plate current, however, may flow for the entire cycle or for only part of the cycle, depending upon the amplitude of the input signal and the cutoff voltage of the electron tube.

Since the amplitude of the developed grid-leak bias is determined by the driving-signal amplitude, it is evident that Class A, B or C operation may be achieved with grid-leak bias merely by increasing the amount of drive (and by selecting the proper RC value). The limiting factor in this application is the amount of distortion that may be tolerated, because the plate current will be distorted for the portion of the cycle during which grid current flows. It is important to remember that grid-leak bias is developed by the rectification of the input (driving) signal and that loss of the input signal will result in a complete loss of this form of bias. In power amplifier circuits where loss of bias means excessive tube currents and

possible damage, a second method of biasing (either fixed or cathode bias) is usually employed as a protective feature.


The shunt type of grid-leak circuit is also used to develop contact bias, which also derives its bias from the flow of grid current, but does not require an input or driving signal to produce it. Since the heated cathode is placed very close to the metal structure of the control grid, a small potential difference called *contact potential* is generated between the cathode and the control grid. Random electron collisions with the grid structure, aided initially by the electrically neutral character of the grid, are the major contributors to contact potential. In diodes a contact potential exists between plate and cathode. The contact potential may be on the order of 0.5 to 1 volt depending upon the structure of the tube, emission characteristics, etc. The 6AT6 and the 6SQ7 are typical examples of the tube types frequently operated with contact bias. The distinguishing feature of contact bias is the extremely high value of grid resistance used. This high value is required because of the minute currents and small potentials involved (with 10 megohms of grid resistance only one micro-ampere of current will produce 1 volt of grid bias). Capacitor C_c (see preceding illustration of shunt grid-leak bias) isolates the grid from the preceding circuit as far as the dc bias is connected, but permits the application of an ac signal to the grid. Contact bias is usually limited to circuits which operate over very small grid swings, say one volt peak to peak, such as an audio preamplifier, or a driven oscillator in which it is desired not to have dc flow through the tuned circuits. Circuits employing contact bias are sensitive to overloading, because any grid current flow due to excessive signal swing will block the tube with a "signal bias" which requires considerable time to leak off through the very long time constant grid network, $R_g C_c$.

The series grid-leak circuit employs a parallel $R_g C_g$ combination in series between grid and cathode (see preceding illustration of series grid-leak bias). Usually grid resistor R_g is in the range of thousands of ohms (rather than megohms). This type of circuit is almost universally employed in the self-excited type of oscillator because of its self-regulating and self-starting action. Once the operating point is fixed by the value of R_g and C_g employed, the tube continues to oscillate about the grid operating point whether it be Class A, B, or C. If the amplitude of oscillations in the grid tank tends to increase, an increase in positive grid drive will occur causing the grid to draw more current. The increase in grid current will develop an increased bias and a consequent decrease of plate current which tends to reduce the plate current pulses back to their original amplitude. A similar sequence of events occurs if the grid drive tends to decrease, but in this event less bias is developed, so that the plate current pulses are increased, returning them toward their original amplitude. Bias is initially developed by the contact potential method during the first few oscillations, allowing the circuit to be self-starting. Then as the grid swings become greater, the capacitor is charged and discharged at the repetition rate of the tuned circuit, and the grid bias is determined by the time constant of the grid circuit and the value of the grid-voltage swing at that instant, averaged over a number of cycles of oscillation. Thus, if the grid capacitor is increased in value, the grid-leak resistance must be reduced to retain the desired charge and discharge rates. When the grid capacitor is sufficiently large and the grid leak resistance is adequate, quite a large voltage can be produced, and if the discharge rate is slow enough, plate current cutoff can be obtained to produce Class B or C operation. Thus this bias method is ideal for oscillators which are self-excited (produce their own feedback). In separately driven oscillators (buffer amplifiers), the shunt (signal) bias methods is used, and the bias voltage required is obtained by supplying sufficient grid current drive from the preceding stage.

Fixed Bias.

There are a number of methods of obtaining fixed bias. The most obvious of these methods is the use of a separate C-battery or a separate negative power (C-) supply. Two other widely used, but not so obvious, methods are shown in the following illustrations. The advantage of these methods is that they both use the

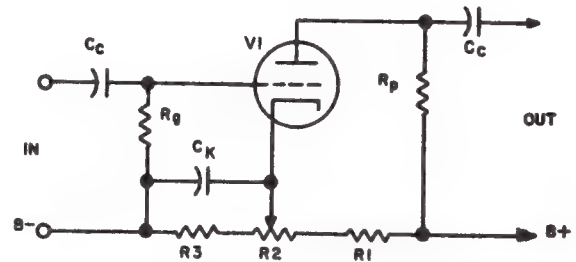equipment power supply to produce the fixed bias, so that no separate supply is necessary.




Fixed (Voltage-Divider) Bias


The fixed-bias circuit utilizes potentiometer R2 connected in series with resistors R1 and R3 to form a voltage divider between B+ and B-. The cathode of the tube (s) being biased is connected to the moving contact of R2, and the grid is returned through R_g to B-. Resistors R1 and R3 determine the voltage range over which potentiometer R2 operates. Thus for cutoff bias a positive cathode bias is produced by the voltage divider. For a bias less than cutoff the cathode current passing through R3 and the active portion of R2 determine the operating bias. Bypass capacitor C_k shunts the portion of the resistance affected by cathode current to present bias changes with signal current variations, as explained in the previous discussion of cathode bias.

The back-bias circuit uses the entire current flow of the power supply to develop a fixed "back-bias". The term *back-bias* refers to a combination of self (cathode) bias and fixed bias from another source. In this instance the self-bias is obtained from the cathode current of the tube being biased. The fixed bias is obtained from the total power supply current and the fixed bias resistor connected in series with the negative supply lead and chassis. There are two variations to this circuit, one using resistor R1 alone and the other using the dc resistance of the loudspeaker field coil L (or a separate choke coil) to act as R1. Use of the latter variation results in an economy of parts since the field coil also provides the bias. The back-bias circuit produces its result by virtue of the connection of the negative B supply lead to the chassis through field or choke coil L and resistor R1, when used. Since all of the tubes on the chassis have their cathodes grounded, the entire chassis current passes through the choke (and resistor) to B-. The voltage

drop across the choke coil (and R1) is the bias. If more bias is required, more current is returned through the chassis, or resistor R1 is added to produce the required voltage drop. It is usually necessary to use a decoupling filter (R2, C4 part B to prevent power supply ripple voltage from appearing on the grid. When more than one stage uses back bias (E_{cc}) a decoupling filter at the grid of each stage is necessary to prevent signal voltage fluctuations on the grid of one stage from affecting operation of the other stages through common impedance coupling. Where more than one value of fixed bias is necessary to suit the requirements of the individual stages a voltage divider arrangement may be used. In the case of equipments requiring large negative bias voltages a separate negative power supply is usually used to obtain the bias.

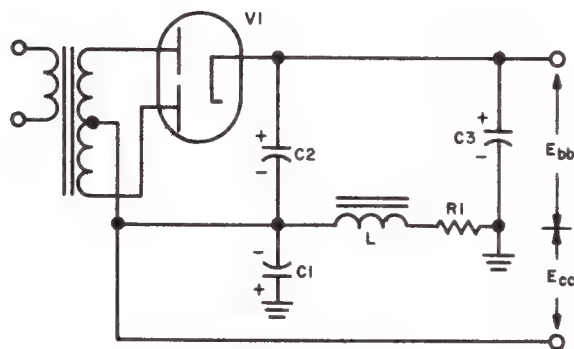

A
BACK BIAS CIRCUIT

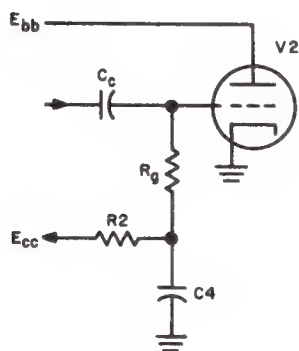


B
DECOUPLING CIRCUIT

Back-Bias Circuit


BIASING METHODS (SEMICONDUCTOR)

General.

Basically, a transistor consists of two junction diodes placed back-to-back with the center element being common to both junctions. Connecting the common elements of two junctions together externally will not produce proper results, but when manufactured as one piece, the PNP junction transistor can be considered as such for ease of understanding. The diode junctions of the transistor are biased with dc potentials, emitter to base in a forward direction, and collector to base in a reverse direction.

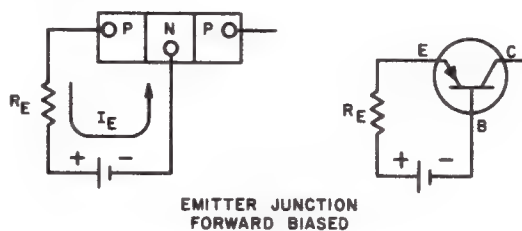

EMITTER JUNCTION
FORWARD BIASED

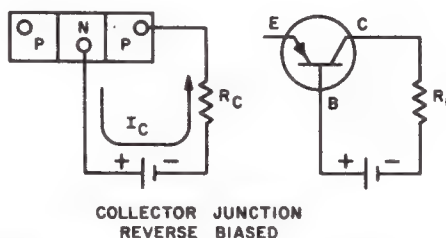

COLLECTOR JUNCTION
REVERSE BIASED

Forward- and Reverse-Biased Junctions

Transistors are made of NPN materials, as well as PNP materials. Current flow in one type is in exactly the opposite direction to that in the other type, and biasing polarities are reversed. Otherwise, they operate identically except that the internal current flow in the transistor is considered to be the result of hole conduction for the PNP type and electron conduction for the NPN type. All external flow in a transistor circuit is electron flow as in the electron tube. A more detailed discussion of transistor action follows below.


TRIODE COMMON-BASE CIRCUITS

In the common-base circuit, the input signal is injected into the emitter-base circuit, and the output signal is taken from the collector-base circuit, with


the base element being common to both. The common-base circuit is equivalent to the electron tube grounded grid circuit. It has a low input resistance (30 to 160 ohms) and a high output resistance (250K to 550K), and is mostly used to match a low-impedance circuit to a high-impedance circuit. It has a maximum voltage gain of about 1500 and a current gain of less than 1, with a power gain of 20 to 30 dB. There is no phase reversal between input and output signals; both signals are in-phase and of the same polarity. (That is both the input and output voltages move in the same direction, starting from zero at approximately the same time, throughout the complete positive and negative alternations. When the input signal is positive, so is the output signal, and vice versa.)

It is common practice to speak of a change of phase between an input and an output signal in both electron tube and semiconductor discussions when what actually occurs is only a change of polarity. Actually, in the semi-conductor, when a long transit time occurs (with respect to the frequencies being amplified), the output signal is delayed in starting because of the finite time taken for the input signal to reach the output terminal. This delay (transit time) produces an actual phase (time) difference between the input and output signals even through the polarities may be identical, or even opposite.

The common-base connections for PNP and NPN transistors are shown in the accompanying figures, together with polarities and external current paths. Emitter-base bias and collector-base bias are obtained from separate sources so that two voltage sources are required. With this type of connection, it is possible to ground the base directly for both ac and dc, if desired. The circuit for a single voltage source will be discussed later.

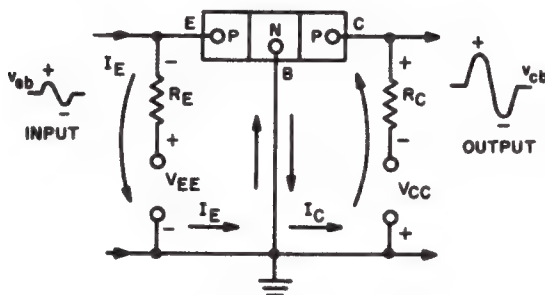

PNP Common Base Circuit

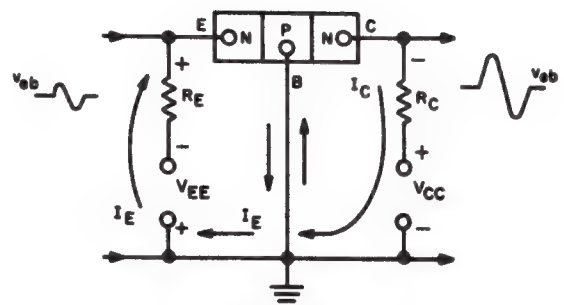


NPN Common Base Circuit

The semiconductor device symbol is used in the figures rather than the graphical transistor symbol for ease of presentation and understanding, since it better indicates the functioning and construction of the device. Both the PNP and NPN circuits are shown together so their operation can be more easily compared. Both circuits are forward-biased from emitter to base, and reverse-biased from collector to base. The polarities of the two circuits are opposite because the transistors are of opposite composition, and the currents in the external circuit flow in opposite directions. Note that in the PNP circuit the external current (electron) flows from emitter to collector, while in the NPN circuit it flows from collector to emitter. Internally, however, the flow is always from emitter to collector through the base region. (Current theory explains the internal flow through the medium of "holes" for PNP transistor and "electrons" for the NPN transistor.) There is one current from emitter to base and another from collector to base; in some instances these currents combine and in other instances they oppose each other, depending upon circuit configuration, biasing, and applied signal voltages. The emitter current is always greater than the collector current, and the algebraic difference between the two is the base current. The base current will be discussed when it is relevant to circuit action; otherwise, it will be ignored since it is a very small portion of the total current involved. In the junction type transistor, about 95 percent of the emitter current always reaches the collector. Transistor action is dependent entirely upon the fact that the signal applied to the low-impedance input (emitter) circuit causes a current flow change which, when transferred to the high-impedance output (collector) circuit, produces a voltage gain. The current gain (α) of the common-base circuit is defined as

$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$

or the ratio of a small change in emitter current to a small change in collector current produced by the emitter current change. It is always less than one.

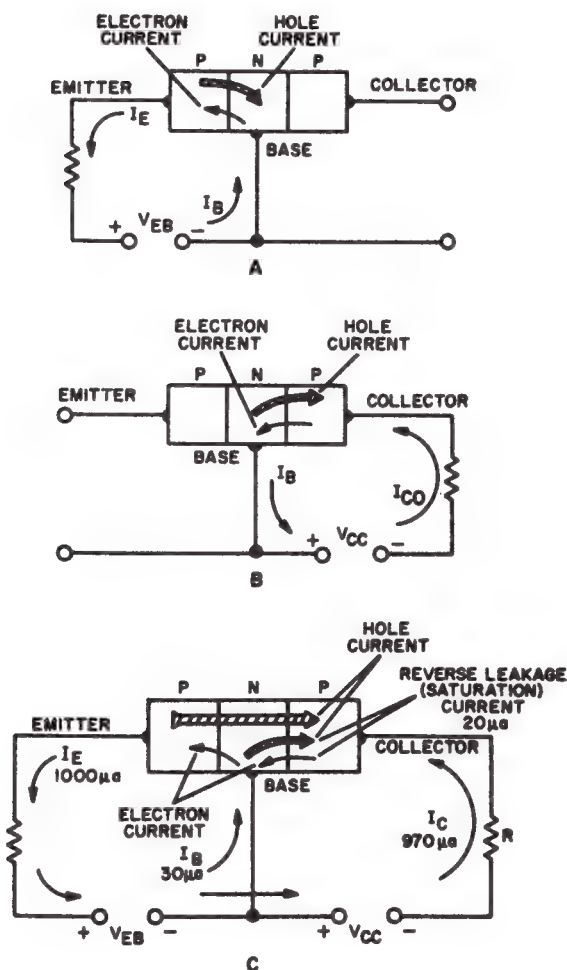A brief discussion of the basic current flow in a transistor is included at this point because the flow of current, both internally and externally, are important to a complete understanding of circuit action. The following figure illustrates the current flow in each junction separately and in the complete transistor.



Transistor Current Flow

In part A, current flow is shown for the emitter-base junction with forward bias applied and the col-

lector open-circuited. The flow externally is by electrons from the emitter to the base. Internally the flow is from emitter to base through the majority hole carriers and from base to emitter through the minority carriers. Assuming a value of 1 milliampere for the emitter current, I_E , the base current, I_B , is approximately the same because the collector is open (neglecting any external or internal leakage currents). The hole current predominates, there being on the order of 200 hole carriers to 1 electron carrier because of the P-doping effect. Since one milliampere of current amounts to 6.28×10^{15} carriers per second, it can be said that the internal emitter current flow consists of 6.24×10^{13} holes per second plus 3.14×10^{13} electrons per second, and the external flow is 6.28×10^{15} electrons per second.

In part B, the emitter is open-circuited and the collector-base junction is reverse-biased. Since reverse bias reduces current flow to a minimum, the collector current, I_C , is actually I_{CO} , the reverse leakage current from collector to base, plus any surface leakage effects, which are neglected in this discussion. Internally, there is a hole current from base to collector (minority carrier) plus an electron flow from collector to base (also a minority carrier). The minority carriers are the cause of current flow because of the reverse bias; the actual current flow is very small, being on the order of 20 microamperes (or less) for a typical transistor. Since the emitter is open, there is no flow from emitter to collector, and the base current, I_B , is approximately the same as I_{CO} .

In part C, both the emitter and collector circuits are completed, forward bias is applied to the emitter, calling for strong current flow, and reverse bias is applied to the collector, calling for minimum current flow (considering junction biasing only). However, because of the reverse bias on the collector, the collector is connected to the negative supply source. Therefore, the potential hill across the collector junctions is reduced, providing an attraction for the hole current diffusing through the base from the emitter. Thus, an easy flow of hole current is permitted and it accounts for most of the emitter current transfer from emitter to collector. As a result of base injection, however, there is an electron current flow from the base to emitter which cannot be collected through the collector because the collector junction barrier polarity opposes conduction of negative charges. There is also a recombination current which consists of holes that flow into the base; these holes

combine with electrons before reaching the collector and thereby cause an electron flow in the base lead and into the base. This current represents a loss, and reduces the amount of emitter current that can reach the collector. The current through the collector junction consists of the emitter current which is permitted to reach the collector, plus the reverse leakage current, I_{CO} . Assuming that 95 percent of the emitter current reaches the collector, the total current can be represented mathematically by a coefficient α (alpha) times I_E plus the saturation current I_{CO} ; that is,

$$I_C = \alpha I_E + I_{CO} \quad (1)$$

The base current is the difference between the portion of the emitter hole current that does not reach the collector (the group of holes which recombine with electrons in the base) and the saturation current. Therefore the expression for base current is:

$$I_B = (I_E - \alpha I_E) - I_{CO} \text{ or } I_B = I_E (1 - \alpha) - I_{CO}. \quad (2)$$

Using the values of base current ($20 \mu\alpha$), emitter current ($1000 \mu\alpha$), and alpha (.95) assumed previously, and substituting them into formula (1) gives the following result:

$$I_C = .95 (1000) + 20 = 950 + 20 = 970 \mu\alpha$$

Using formula (2) for base current and substituting:

$$I_B = 1000 (1 - .95) - 20 = 50 - 20 = 30 \mu\alpha$$

It can be seen from the numerical example that the value of the recombination current is $50 \mu\alpha$, that the base current is the difference between the recombination current and I_{CO} , that the collector current is the sum of I_{CO} and αI_E and that the various internal currents can be made equal to the external currents. In the example above, the external current is that indicated in the figure, and is an electron flow from emitter to collector with a small amount also flowing into the base. The discussion has assumed small-signal conditions and the use of a PNP transistor in the common-base connection. When other configurations such as common-emitter and common-collector circuits are used, the values of current change somewhat because of the differences in input and output connections and the current paths between them. When

the NPN transistor is employed, operation is the inverse of that for the PNP transistor, with electrons acting as majority carriers and holes as minority carriers. For large-signal conditions, operation is slightly different and will be discussed at the appropriate point in the circuit discussions in other sections of this handbook.

The PNP Common-Base Circuit (shown previously) shows a small input signal (V_{eb}) applied to the emitter-base junction of the PNP transistor. The circuit is considered to be biased so that it operates over the linear portion of its dynamic transfer characteristic, and is resting in a quiescent state in accordance with the dc potentials applied (similar to electron tube class A operation). Assuming a sine-wave input, it is apparent that as v_{eb} increases to its maximum positive value the forward-bias between emitter and base is increased, causing the emitter-base junction to produce an increased current flow, which passes through the external circuit and eventually through collector load resistor R_C . The increase of current through R_C causes an increased voltage drop in the positive direction, so that as the input signal reaches its positive maximum so does the output signal. Therefore, both signals are always in phase and of the same polarity.

On the negative swing of the input signal, as the negative signal voltage is added to the positive forward bias, the result is a reduction of the bias and less emitter current flows. In turn, a reduced collector current flow through R_C results in a decreased voltage drop across R_C and produces a reduced output voltage; the negative going output signal remains effectively in phase with the same polarity as the input signal.


The NPN circuit (shown previously) functions similarly but inversely to the PNP circuit; that is, on the positive swing of the input voltage, the collector current is reduced, and the drop across R_C is less negative (or more positive). On the negative input cycle forward bias is increased, and the collector current produces a greater negative drop across R_C ; thus the output voltage also follows the input voltage in phase and polarity.

Bias (Common Base).

Transistors are normally biased by placing a forward voltage on the emitter-base junction (increasing the bias voltage causes increased emitter and collector current flow), and a reverse polarity voltage on the

collector junction. The operating (or bias) point is determined by specifying the dc, no-signal (quiescent) values of collector voltage and emitter current. Biasing circuits and arrangements are varied; separate supplies such as batteries are commonly used, as well as so called self-bias arrangements, voltage dividers across the collector supply, and other transistors or diodes.

The common-base circuit is usually restricted to the use of separate bias for the emitter-base junction or to a voltage-divider arrangement using a single voltage supply which serves as the collector-base supply also. The following illustration is a typical single-supply type of arrangement. Resistors R_1 and R_2 form a voltage divider across the collector supply, with the base connected at their junction and the emitter connected to the high side of the supply. Thus the emitter is always at the highest potential, the base is at a lower potential because of the voltage drop across R_1 due to the current from the supply source flowing through the voltage divider, and the collector is at the lowest potential. The difference in potential between the emitter and base represents the forward bias applied to the emitter-base junction. For a PNP transistor, as shown, forward bias is achieved by making the emitter positive with respect to the base; for an NPN transistor, the polarity of the source is reversed, and the emitter is negative with respect to the base. Although the value of R_1 is normally low, it may be necessary in some cases for R_1 to be bypassed with a very-low reactance capacitor, to assure that the base is well grounded for ac.

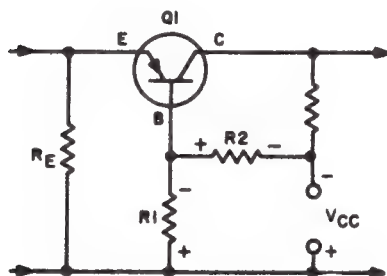

Single-Source, CB Fixed-Bias Circuit


The common-base configuration offers almost ideal thermal compensation, since the input resistance (R_E) in the emitter circuit acts as a swamping

resistor, and changes in collector current with temperature are minimized by low base-to-emitter resistance. See the paragraph on Diode Circuits later in this section for a discussion of diode circuits used for stabilization of bias; refer to the discussion below on Triode Common-Emitter Circuits for a discussion of emitter swamping resistors.


TRIODE COMMON-EMITTER CIRCUITS

In the common-emitter circuit, the input signal is injected into the base-emitter circuit and the output signal is taken from the collector-emitter circuit, with the emitter element being common to both. The common emitter is equivalent to the electron tube grounded-cathode (conventional) amplifier circuit. It has a somewhat low input resistance (500 to 1500 ohms) and a moderately high output resistance (30 K to 50 K or more), and is the most commonly used transistor circuit configuration. It is widely used for a number of reasons. Because the input signal is applied to the base rather than the emitter, a considerably higher input impedance is obtained than in the common-base circuit. High power gains are obtainable (25 or 40 dB), and an actual current gain is possible (from 25 to 60 or better). The actual voltage gain is slightly less than that of the common-base circuit because of the higher input impedance, but this is partially off-set by the current gain; in practice, voltage gain values of 300 to 1000 (or better) are obtained. Because the signal is applied to the base, a polarity reversal takes place, making the output signal of opposite polarity to the input signal, as in the conventional electron tube amplifier.

The common-emitter connection for PNP and NPN transistors is shown respectively in the following figures, together with polarities and external current paths. Base emitter bias is obtained from a separate supply than that of the collector-base junction so that two voltage sources are required. With this type of supply connection it is possible to directly ground the emitter both for ac and dc, if desired. Single voltage supply circuits will be discussed later. The PNP and NPN circuits are shown together for ease of comparison of operation. Both circuits are forward-biased from emitter to base and reverse-biased from collector to emitter. Current flow and polarities in both circuits are opposite because of the difference in material from which the transistors are manufactured.

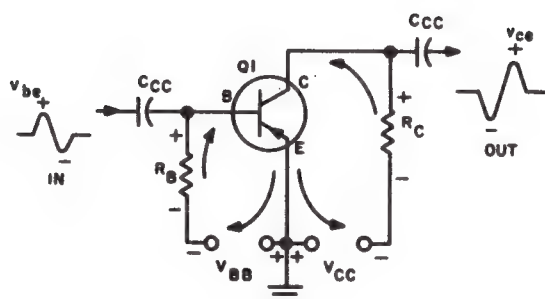

PNP Common-Emitter Circuit

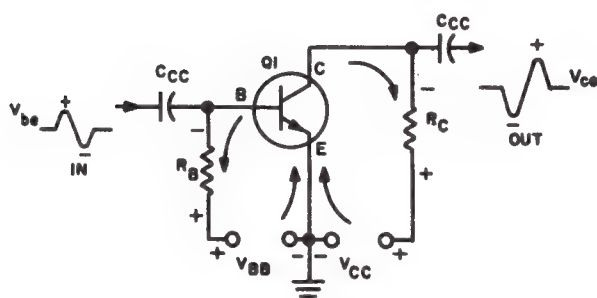

NPN Common-Emitter Circuit

Current flow is from the emitter to the collector through the base region as in the common-base connection, and, likewise, only a small amount of current is diverted in the base-to-emitter circuit. Transistor action also depends on the fact that a small change of current in the low-resistance input circuit produces a voltage gain when applied to the high-impedance output circuit. But unlike the common-base circuit, the current gain is not based on the emitter-to-collector current ratio alpha (α); instead it is based on the base-to-collector current ratio beta (β) because the signal is injected into the base, not the emitter. Therefore, since a small change of base current controls a large change in collector current, it is possible to obtain considerable current gain (a value of 60 is not unusual). Since the collector load resistance, R_C is less than the load resistance of the BC circuit, less voltage gain might be expected. However, the increased current in the collector produced by current gain off-sets the loss of output resistance, so that the voltage gain is nearly comparable to that of the CB circuit. By manipulation of circuit constants and selection of transistors, the voltage gain can be made to exceed that of the CB circuit.

Beta is defined as

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

with V_C constant, and is related to alpha of the CB circuit by

$$\beta = \frac{\alpha}{1 - \alpha}$$

thus the closer α is to 1, the larger is β ; as α approaches 1, β approaches infinity.


A small input signal is applied to the base of the PNP transistor. The circuit is biased to operate over the linear portion of its dynamic transfer characteristic, and rests in a quiescent state determined by the static dc potentials applied (similar to electron tube class A operation). Assuming a sine-wave input, it is apparent that, as v_{be} increases to its maximum positive value, the forward bias is reduced, less current flows in the emitter and collector circuits, and the drop across the collector output resistor (R_C) becomes less, producing a negative-going voltage. Conversely, as the input signal swings negative, the forward bias is increased and more emitter and collector current flows. The increased voltage drop across R_C is in a positive-going direction, and the output signal reaches a positive maximum. It is evident that, since the output signal is at a positive maximum when the input signal is at a negative maximum and vice versa, the input and output polarities are exactly opposite. Therefore, the common emitter circuit is similar to the vacuum-tube common-cathode circuit, producing a polarity reversal of the input signal (although not strictly accurate, this polarity reversal is commonly spoken of as a phase difference).

The NPN circuit shown functions similarly but inversely to the PNP circuit. That is, when the input signal is positive, the forward bias is increased, and the collector current increases and produces a negative-going output across R_C . On the negative input cycle, the collector output is positive; therefore, this circuit also produces an out-of-phase signal of opposite polarity. It is evident, then, that *the common-emitter circuit always produces a polarity reversal of the input signal.*



Bias Circuits (Common-Emitter).

Because the common-emitter circuit is more frequently used, it has a greater variety of biasing schemes than the other configurations. The basic principles though remain the same; that is, the emitter-base junction must be forward-biased while the collector-base junction is reverse-biased, and the dc no-signal values of base current and collector voltage specify the operating point.

The following illustration is a method of using two supply sources to produce a PNP emitter-base bias arrangement which series-aids the collector supply. It is evident that the emitter-base bias voltage is the voltage of the emitter-connected source, while the collector-emitter voltage is the total voltage between emitter and collector, or both sources in series. For an NPN transistor the polarities are reversed.

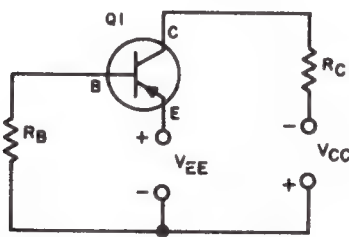**Series-Aiding Bias Circuit, PNP**

The connections for a single voltage supply source biasing arrangement are shown in the accompanying illustrations.

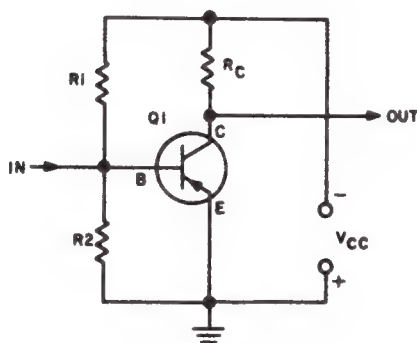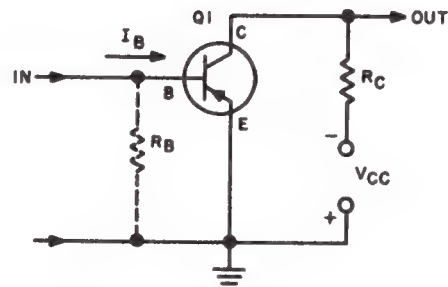**Voltage-Divider (Fixed) Bias, CE Circuit****PNP Internal Self-Bias CE Circuit**

The first figure is a voltage divider fixed-bias arrangement, with R_1 and R_2 connected across the collector supply, and the base connected at their common connection. Thus the base is kept at a lower positive potential than the emitter and is therefore negative with respect to the emitter.


The second figure is a self-biasing arrangement which involves the internal resistance inherent in the transistor junctions; it is similar to the contact bias of the electron tube. The emitter is at the higher positive potential, and the collector is at the lowest negative potential, so the emitter-collector relationships are correct. Since the base is sandwiched between these elements and floating, it is at some intermediate value, determined by the internal resistance parameters and the internal current flow. The potential between the emitter and base must be kept to a small value compared to that between the collector and base. This is achieved internally by the high-resistance action of collector-base junction and the low-resistance action of the emitter-base junction, which provide the desired voltage relationship. The supply voltage polarity is reversed for NPN transistors. By placing resistor R_B (shown dotted) from base to emitter, the base is effectively biased off and less base current (I_B) flows. The collector current is reduced by

$$\frac{1}{1 - \alpha}$$

for each I_B microampere, and more economical operation is achieved by reducing the battery drain.

A variation of the self-bias arrangement using external resistors is shown in the following illustration. Here the bias supply is connected in series with

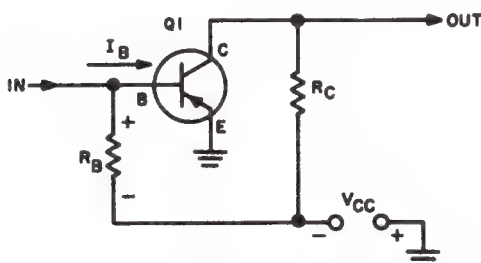the emitter, and the voltage divider made up of R_B in series with the internal emitter-base resistance, determines the proper bias potentials. The voltage across R_B is subtracted from that of the bias supply to determine the actual input bias. Collector resistor R_C is chosen to produce the desired operating collector voltage. The polarity of the supply voltage is reversed for NPN transistors.



PNP External Self-Bias CE Circuit


Bias Stabilization.

The discussion of the diode stabilization circuits paragraph, together with the discussion in this paragraph, covers basic thermal stabilization circuits. Since a number of variations of the circuits discussed below are possible, any other special circuits will be discussed in the sections of this manual as they appear. Stabilization as discussed here will be confined to thermal considerations; voltage stabilization is discussed later in this section in the paragraph titled *Diode Voltage Stabilization*.

The no-signal, dc values of collector voltage and emitter current are determined by the applied bias, which sets the operating point of the transistor. Under ideal conditions temperature would not affect the bias and the circuit would be thermally stable. Actually, however, a temperature increase causes an increase in the flow of reverse-bias collector (saturation) current (I_{CBO}), and the increase in I_{CBO} causes the temperature of the collector-base junction to increase with a consequent increase in saturation current. As this action continues, distortion occurs, and the transistor is rendered inoperative or it destroys itself. To reduce thermal instability (runaway), low values of resistance, rather than high values, must be employed in the base circuit. For a discussion of a reverse-biased diode which decreases its resistance with an increase in temperature, refer to the para-

graph titled *Reverse-Biased Diode Stabilization*, later in this section.

Another consideration is that the emitter-base junction of a transistor (or a diode) has a negative temperature coefficient. That is, as the temperature increases the emitter-base resistance decreases, causing a larger flow of collector current in addition to the flow of saturation current discussed above. To correct this condition R_E , a large-value resistor (swamping resistor), is placed in the emitter circuit, where it produces a resistance stabilizing effect (see accompanying figure). Actually, in this case, the variation of emitter-base resistance with temperature is such a small portion of the over-all emitter series resistance that it exerts little effect on the over-all operation of the circuit.

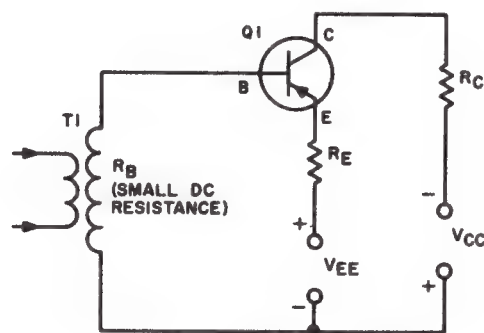


Emitter Swamping Circuit

In the following figure, resistors R_1 and R_B operate as a voltage divider across the collector voltage supply source to supply negative (forward) bias to the base-emitter circuit. This arrangement allows a single voltage supply to be used for both and collector voltages. When the value of R_1 together with R_B in parallel is less than R_E , the effects of voltage-divider voltage stabilization and the thermal compensation provided by the swamping effect of R_E combine to offer a more stable bias circuit. Unless the proper ratio is maintained, no compensation is achieved. The stabilization is improved as the following quantity approaches zero:


$$\frac{R_B \cdot R_1}{R_B + R_1} / R_E \cdot$$

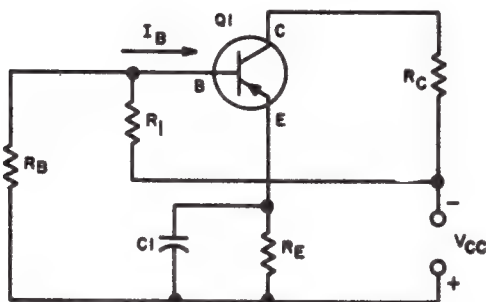Capacitor C_1 bypasses R_E for signal variations; otherwise, degeneration would be produced by the swamping resistor. The capacitor is chosen to have a reactance about one-tenth that of the swamping resistor at the lowest frequency to be passed.



Voltage-Divider Bias and Emitter Swamping Stabilization

The following illustration is a variation of the previous circuit; it uses only voltage-divider stabilization, the emitter swamping resistor being omitted. In this circuit, R_1 and R_2 from a voltage divider across the collector supply, and the effective bias is essentially the voltage existing at the junction of R_1 and R_2 . A large resistor, R_B , is connected from the divider junction point to the base to provide a higher input resistance and avoid the shunting effect of R_2 (R_2 is small in value because the base-to-emitter bias is only a fraction of a volt). The stabilizing action in this circuit is provided by the voltage divider alone, since the divider is less affected by variations in element currents or voltages than are self-bias arrangements. The disad-

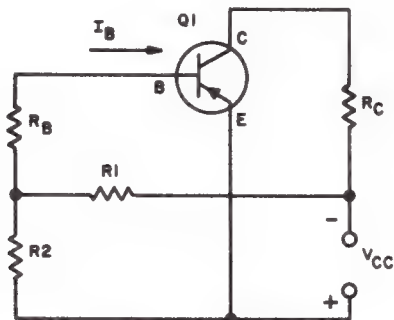


Voltage-Divider Bias

vantage of this circuit is that it consumes more dc power because of the voltage divider; the previously discussed circuit with both voltage divider bias and emitter swamping stabilization is preferable because of its increased stability.

Another method of compensating for emitter-base resistance change with temperature is to feed back an opposing voltage which is proportional to the temperature change per degree. An equivalent method is to correspondingly reduced the forward bias applied the circuit.

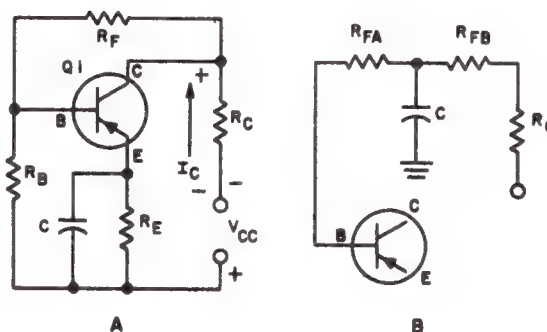In the following figure, the circuit of part A represents both ac and dc feedback. When resistor R_F is divided into two parts and bypassed by capacitor C as shown in part B, the feedback loop is shunted, and only dc bias variations affect operation.




Negative Feedback Bias Circuit

Compensation is achieved as follows: When the collector current (I_C) increases because of a temperature increase, the collector becomes less negative because of the larger positive voltage drop in resistor R_C . Since the drop across R_C opposes the initial bias, less forward bias is applied to the base through feedback resistor R_F , and the collector current automatically decreases to the original value (provided that the proper feedback ratio is maintained). There are two other types of compensation for the circuit in part A of the figure; voltage-divider stabilization through R_B and emitter current feedback through R_E .

Three variations of the voltage feedback circuit are shown in the accompanying illustrations. The circuit of part A represents voltage feedback alone. Actually for dc biasing conditions, R_F and R_C can be considered as one resistor having a value equal to that of

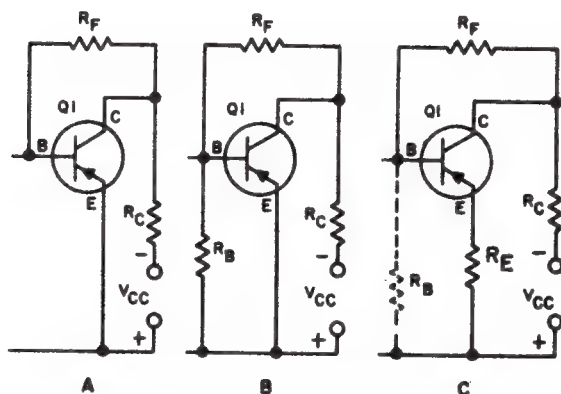the external self-bias resistor, R_B (see previously discussed figures showing PNP External Self-Bias CE Circuit). It is seen that any change of current through R_C , therefore, will either increase or decrease the bias applied through R_F .




Voltage Feedback Circuits

In part B of the figure, the addition of resistor R_E produces a voltage divider across the bias supply so that in addition to voltage feedback, the effect of voltage-divider stability is offered. In part C, current feedback through emitter resistor R_E is added, and when the resistor R_B shown in dotted is also added, a combination of voltage and current feedback together with voltage-divider stabilization is obtained, and the circuit is identical to the previously discussed *Negative Feedback Bias Circuit*.

In the above discussion of stabilization, it has been assumed that only the dc, no-signal operation is of interest, as all circuits are considered to be properly bypassed so that signal operation does not materially affect the bias.


A voltage-divider base-bias arrangement using a thermistor to compensate for emitter current changes with temperature, is shown in the following illustration. When the emitter current tends to rise with temperature, the thermistor, having a negative temperature coefficient of resistance, reduces in value as the temperature increases. This reduction in resistance increases the current flow from the V_{CC} supply and causes an increased voltage drop across R_1 . The base bias is reduced correspondingly, lowering the emitter current and compensating for the temperature change. Since the thermistor is constructed of a material different from that of the transistor, it does not

change resistance in exact proportion to the emitter current change; therefore, "tracking" is not very good and true compensating occurs at only a few points over the operable range. In this respect, semiconductor diodes provide much more ideal compensation. This method of stabilization is identical in concept to that described in the paragraph covering Forward-Biased Diode Stabilization, later in this section of the handbook.

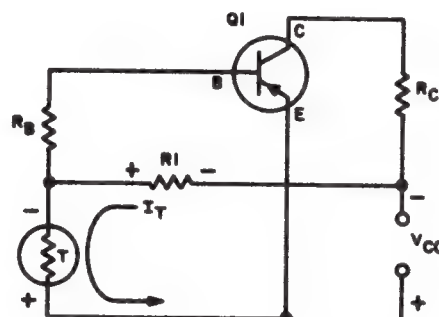

Thermistor Base-Bias Compensating Circuit

A number of thermistor compensation circuits have been developed, but they all use the same principle of changing bias inversely with temperature to compensate for the change. The accompanying illustration is an emitter bias compensator, in which the base bias is provided by a voltage divider consisting of R_1 and R_2 , and compensating emitter bias is provided by R_3 and the thermistor. The drop across R_3 applies a reverse bias to the emitter as the temperature increases, reducing the emitter current correspondingly.

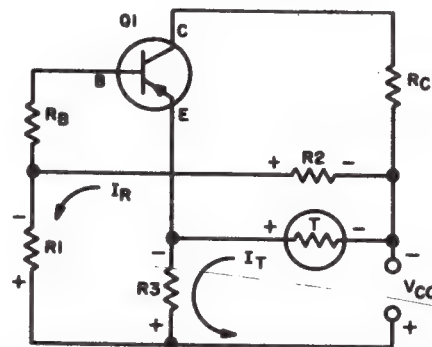


Thermistor Emitter-Bias Compensating Circuit

Normally ideal thermal compensation, as well as a reduction of the number of parts required, can be achieved by the use of crossconnected transistors arranged so that the element voltages or currents of one transistor compensate for thermal variations by producing correction voltage or currents in the other, while both transistors operate as amplifiers. For example, it is possible to use the variations of the emitter-base junction resistance with temperature of one transistor to control the emitter-base bias of a second transistor, or to stabilize the emitter-collector current of one transistor with the stabilized emitter-collector current of another transistor. Since these circuit arrangements become rather involved, they will be discussed as special circuits at appropriate points in other sections of this handbook. However, since thermal compensation is an important part of the dc amplifier, its use in a two-stage stabilized unit is discussed below.

In the following circuit, an increase in collector current produced by a temperature rise in transistor Q1 reduces the forward bias of transistor Q2. Transistor Q1 is connected as a CB amplifier, which basically has an ideal stability factor. Nevertheless, a very slight variation of collector current will occur with temperature variation. This slight temperature variation is the result of reverse leakage current (I_{CBO}) caused by the internal flow of minority carriers (electrons from collector to base). The reverse leakage current is substantially independent of collector voltage and mainly dependent upon temperature, being constant for a specific temperature, and increasing with temperature. The effects of temperature-caused variations of the base-emitter resistance of Q1 are minimized by the relatively large swamping resistance offered by R_E , and will not have any appreciable effect on the collector current, I_C . Thus, while the emitter junction is essentially stabilized, the collector junction is not. Although the collector junction is reverse-biased for normal forward current, this bias is actually a forward bias for reverse current. Therefore, the reverse current flow can reach values as high as 5 milliamperes. Although this high reverse current does not lead to thermal runaway, it does change the parameters, causing a change in the operating point and resulting in improper circuit operation. In addition, since the two transistors are direct-coupled, current changes in Q1 will be amplified by Q2, causing a much greater shift. While the total base current, I_B , is the net result of I_{CBO} plus the base-emitter current,

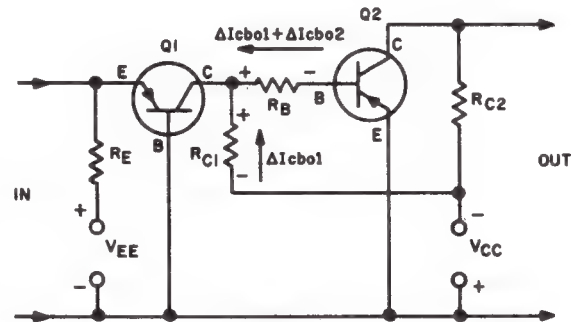the current of interest is the very small (incremental) changes of reverse leakage current, ΔI_{CBO} , with temperature; for this explanation then, the absolute values of base current may be disregarded.



Temperature-Stabilized D-C Amplifier

Referring again to the previous figure, the main current path for I_{CBO1} is through R_{C1} , the collector-base junction of Q1, and V_{CC} . An additional current path which is also the path of I_{CBO2} , is provided through R_{C2} , the collector-base junction of Q2, R_B , the collector base junction of Q1, and V_{CC} . Any Incremental change of I_{CBO1} and of $I_{CBO2} + I_{CBO1}$ will produce an incremental change in the voltage drops across R_{C1} and R_B , respectively. The change in voltage across R_{C1} will be in a direction to decrease the forward bias of Q2 (see polarity indicated in figure), while the change in voltage across R_B will be in a direction which increases the forward bias of Q2. If the values of R_{C1} and R_B are chosen so that the incremental change of voltage across R_{C1} is slightly greater than the incremental change across R_B , then a thermally caused increase of collector current will be compensated for by a reduction of the forward bias of transistor Q2.


The previous discussion considers only the very small changes in current produced by temperature variation in the collector junction of Q1; it does not consider the static operating conditions nor signal variations. Normally, Q1 operates as a conventional CB amplifier thermally stabilized by series emitter swamping resistor R_E , and biased by supply V_{EE} . The input signal is applied across R_E and amplified by Q1, appearing across R_{C1} as a direct-coupled input to the base of Q2, a conventional CE amplifier.

The output of the two stages is developed across collector load resistor R_{C2} . The collector supply for both stages is taken from the single V_{CC} source. For a complete discussion of dc amplifiers, see DC Amplifier Circuits, in another part of this section of the handbook.


TRIODE COMMON-COLLECTOR CIRCUITS

In the common-collector circuit, the input signal is injected into the base, and the output signal is taken from the emitter, with the collector being common to both circuits. The common-collector circuit is equivalent to the electron tube cathode-follower circuit. It has a high input resistance (2K to 500K) and a low output resistance (50 to 1500 ohms). It has a current gain similar to that of the common-emitter circuit, but a lower power gain than either the CB or CE circuits (10 to 20dB). The output signal is in phase and of the same polarity as the input signal, and the voltage gain is always less than unity. This circuit is used mostly for impedance-matching and isolation of output stages; thus its function is similar to that of the electron tube cathode follower. It has the ability to pass signals in either direction (bilateral operation), a feature which is particularly useful in switching circuitry.

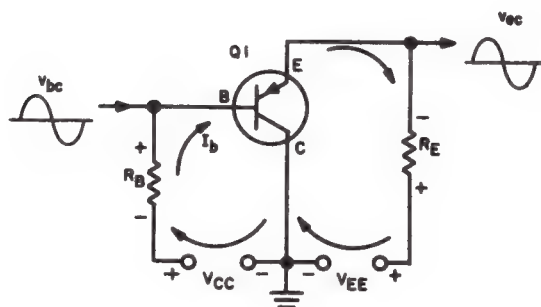The PNP and NPN common-collector connections are shown in the following figures, together with polarities and external current paths. Base-emitter bias and collector-base junction voltages are obtained from separate supplies and thus two voltage sources are required. Single voltage supply circuits are discussed later, under the paragraph titled *Bias (Common-Collector)*.



PNP Common-Collector Circuit

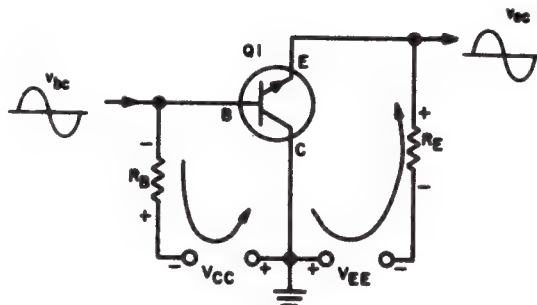

NPN Common-Collector Circuit

As in the CE and CB discussions, the PNP and NPN circuits are shown together for ease of comparison of operation. Both circuits are forward-biased from emitter to base and reverse-biased from collector to emitter. The currents and polarities in both circuits are opposite because of the different types of germanium used.

The current flow and transistor action of the CC circuit are as explained for the common-base connection, but the current gain is not based on the emitter-to-collector current ratio, alpha (α). Instead, it is based on the emitter-to-base current ratio, gamma (γ), because the output is taken from the emitter circuit. Since a small change in base current controls a large change in emitter (and collector) current, it is still possible to obtain considerable current gain. However, since the emitter current gain is offset by the low output resistance, the voltage gain is always less than unity, exactly as in the electron tube cathode-follower circuit.

Common-collector current gain, gamma (γ), is defined as

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$

with collector voltage constant, and is related to collector-to-emitter current gain, alpha (α), of the CB circuit by the formula:

$$\gamma = \frac{1}{1 - \alpha}$$

In the PNP circuit, a small input signal (v_{bc}) is shown applied between base and collector of the transistor. The circuit is biased to operate over the linear


portion of its dynamic transfer characteristic, and rests in a quiescent state determined by the static dc potentials applied (similar to electron tube class A operation). Assuming a sine-wave input, it is apparent that as v_{bc} increases to its maximum positive value the forward bias is reduced. Thus, the emitter and collector currents are reduced, producing a decreased voltage drop across the emitter output resistor, R_E , and producing a positive-going output voltage. Conversely, as the input signal swings negative the forward bias is increased and more emitter-collector current flows. The increased voltage drop across R_E is in the negative-going direction, and the output signal reaches a negative maximum. Since the output signal varies in the same direction as the input voltage, both reaching their positive and negative maximums simultaneously, it is evident that these signals are in phase. Therefore, the output of the common-collector circuit is of the same phase and polarity as the input signal and no phase reversal is produced, just as in common-base operation.

The functioning of the NPN circuit previously shown is similar to, but the inverse of, the functioning of the PNP circuit. When the input signal is positive, the forward bias is increased (its polarity is opposite to that of the PNP circuit bias), and the emitter current increases and produces a positive-going output across R_E . On the negative input cycle, the emitter output is negative; therefore, the output of this circuit is also of the same phase and polarity as the input signal. *Thus, the common-collector circuit always produces an in-phase output signal, regardless of the type of transistor used.*

Bias (Common-Collector).


Common-collector biasing schemes are similar to those of the CB and CE configurations, and the basic principles are the same. That is, the base-emitter junction is forward-biased, the base-collector junction is reverse-biased, and the dc, no signal values of base current and collector voltage specify the operating point.

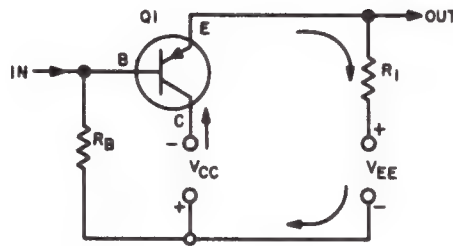The accompanying figure shows a series-siding bias arrangement in which two voltage supplies are used. This arrangement is similar to that for the Series-Aiding Bias Circuit, PNP, previously discussed under the heading *Bias Circuits (Common-Emitter)*, and the operation is also similar.



Series-Aiding Bias Circuit

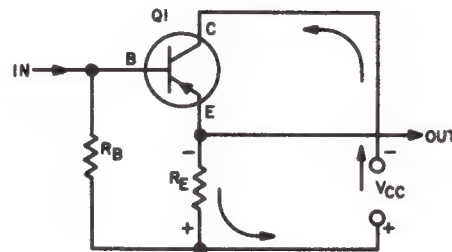In the following figure, a single voltage source bias arrangement is shown. Note that the flow of current through R_E is in a direction which produces a voltage drop that opposes the applied bias and collector voltage. The actual bias is the algebraic sum of the two voltages. Polarities and current flow are opposite for PNP circuits.



Self-Bias Circuit

Hybrid Parameters.

The hybrid parameters, or h-parameters, of the transistor are mostly of use to the circuit designer. However, manufacturers have found them convenient for use in defining the performance of their products. Therefore, a working knowledge of the use and meaning of h-parameters is essential to the technician.


The h-parameters appear in two forms which are interchangeable; one form employs letter subscripts, and the other numerical subscripts. At present, the numerical subscripts are commonly used for general circuit analysis, and the letter subscripts are used for specifying characteristics of transistors. Industry standardization accepts both forms, but the present

trend in usage indicates that the numerical subscripts may be preferred. In addition, there are other systems of parameters, such as "a", "b", "y", "g", "r", and "z" parameters, which have somewhat more specialized uses. All of these systems, which may seem confusing to anyone other than a trained engineer, represent different methods of mathematically defining transistor action, as well as the parameters limiting that action, for design purposes. Although the triode transistor is a 3-terminal device, it may be treated as a "black box" with two input and two output connections (a basic 4-terminal network). By utilizing the electrical characteristics (h-parameters) of this black box, it is possible to calculate performance of various circuits when various input signals are applied and various loads are connected. Basically, these h-parameters are limited to frequencies sufficiently low (270-100 Hz) that the capacitive and inductive effects of the transistor can be neglected. The h-parameters for common-base connection are usually shown in specification sheets because the emitter current and collector voltage can be maintained more precisely than for other configurations. Because of the trend toward the use of common-emitter circuits and the relative ease of measurement, some CE h-parameters will also be observed. In any event, formulas are available for conversion from one configuration to the other in most text books (and transistor manuals), so only the common-base connection will be discussed in here.

The simple common-base configuration shown in part A of the accompanying figure can be represented by the four-terminal h-parameter equivalent circuit shown in part B. In using the h-parameters, it is customary to ignore the bias and consider only the instantaneous ac values involved. Thus, the h-parameters represent operating conditions for a small signal close to the operating point. Therefore, the equivalent circuits do not show bias supplies and polarities. Conventional currents (not electron flow) and voltage polarities are assumed, and if erroneously assigned, will result in a negative answer when the problem is solved. Since the circuit is essentially a four-terminal network (two input and two output terminals), it can be described by two simultaneous equations in which the h-parameters are the coefficients, namely:

$$\begin{aligned} E_1 &= h_{11} i_1 + h_{12} E_2 \\ I_2 &= h_{21} i_1 + h_{22} E_2 \end{aligned}$$

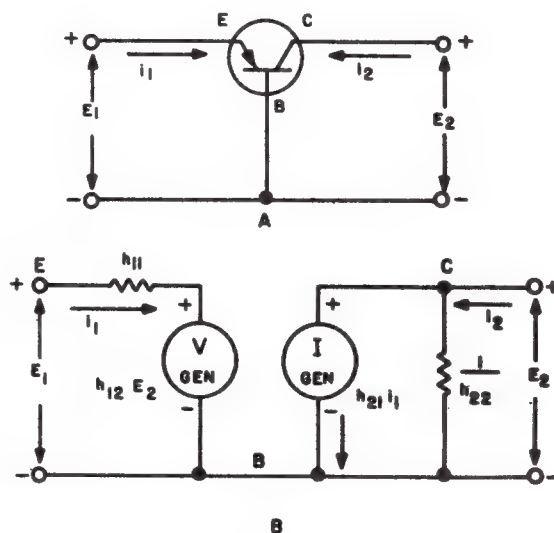To conform with Kirchhoff's law, h_{11} in part B of the figure must be an impedance and h_{22} an admittance, while h_{12} and h_{21} are essentially dimensionless ratios. For low frequencies h_{11} and h_{22} are resistive. Since these parameters involve two opposites—impedance and admittance—the term *hybrid* is used to describe them.



Transistor and Four-Terminal Network Equivalent Circuits

If the output terminals are short-circuited for ac (by a large capacitor), the output voltage (E_2) is zero, and the following simple formulas (like Ohm's law) show the relationships between input voltage and current and between input current and output current.

$$\begin{aligned} h_{11} &= \frac{E_1}{i_1} \\ h_{21} &= \frac{i_2}{i_1} \end{aligned}$$


If the ac input circuit is opened by the insertion of a large inductance in series with the bias, thereby reducing i_1 to zero, the following additional formulas will be obtained:

$$h_{12} = \frac{E_1}{E_2} \text{ and } h_{22} = \frac{i_2}{E_2}$$

Thus, h_{11} is effectively the transistor input impedance (with the output short-circuited), and h_{22} is the output admittance (with the input open-circuited). Similarly, h_{12} is the voltage feedback ratio with the input open-circuited (this represents the internal feedback due to reverse-current effects and common impedance coupling within the transistor). Parameter h_{21} is the forward current amplification ratio with the output short-circuited.

The functioning of the equivalent circuit and the meaning of the h-parameters can perhaps be more clearly understood by considering the following intuitive reasoning. Consider part B of the figure, and for the moment neglect the voltage produced by the voltage generator (V_{GEN}) in the input circuit. When the input signal voltage (E_1) is applied to the input terminals, current i_1 flows through resistor h_{11} and causes current $h_{21} i_1$ to flow in the output current source (current generator I_{GEN} in the figure). Thus, h_{21} is the current gain of the equivalent circuit. Current $h_{21} i_1$ divides between the output resistor, which is equal to $1/h_{22}$ (h_{22} is an admittance), and the external circuitry connected across the transistor output terminals. The voltage developed across the output as a result of this current is the output voltage (E_2). When voltage E_2 appears across the output it causes an internal feedback voltage to be fed back to the input; this voltage is $h_{12} E_2$, represented by voltage generator V_{GEN} at the source. This feedback voltage opposes the initial signal input (E_1) and effectively subtracts from it.

The following figure shows the hybrid equivalent circuits for the three basic transistor configurations. Note that the circuits are all the same because the defining equations must be satisfied. The parameter notation, however, is different for each configuration; it consists of the general parameter designations h_1 , h_r , h_f , and h_o with the additional subscript b, e, or c added to represent the common base, emitter, or collector configuration, respectively. The letter and numerical forms of the parameters are related as follows: h_1 is h_{11} , h_r is h_{12} , h_f is h_{21} , and h_o is h_{22} .

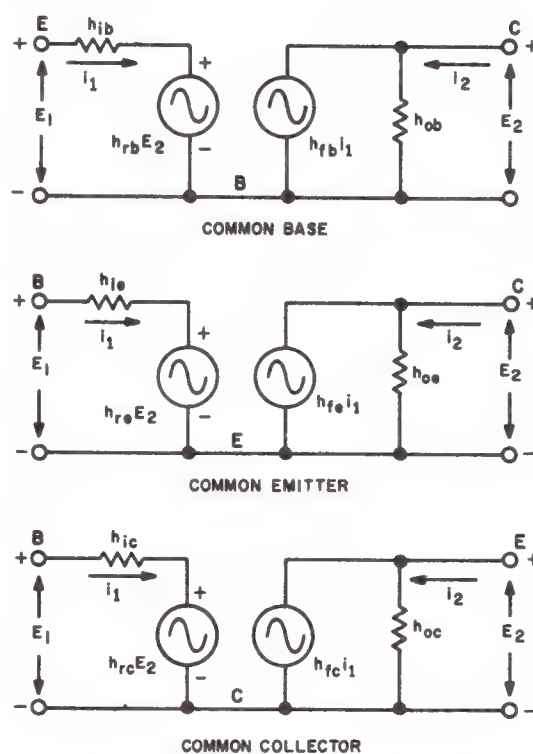

Basic-Hybrid Parameter Equivalent Circuits


From the preceding discussion, it is obvious that with a few external measurements the h-parameters of the typical "black box" can be determined, and that substitution of these values in the proper formulas will allow circuit performance to be approximated so that the proper matching values of external circuitry can be chosen by the designer.

DIODE STABILIZATION CIRCUITS

Forward-Biased Diode Stabilization.

The accompanying circuit employs junction diode CR1 as a forward-biased diode to compensate for

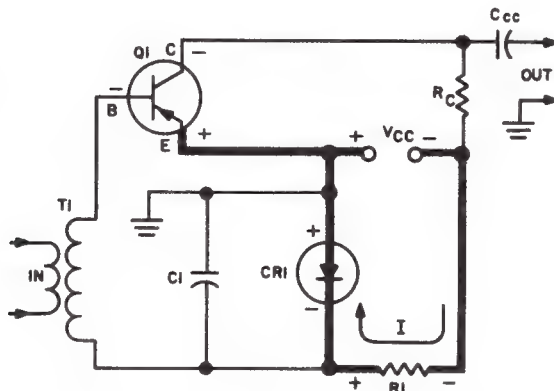transistor emitter-base resistance variations with temperature. This type of circuit compensation is effective over a range of from 10 to 50 degrees Centigrade (usually no compensation is needed below 10 degrees). Higher temperature ranges require additional compensation (see discussions on Reverse-Biased Stabilization and Double-Diode Stabilization, later in this section).




Forward-Biased Diode Stabilization, CE Circuit

Under static conditions, the emitter of transistor Q1 is biased positive with respect to the base (forward biased), and current flows through R1 and external diode CR1 connected across the source voltage, V_{CC} . In this condition, CR1 is forward-biased also, and the polarities around the circuit are as shown in the figure. Current flow is light (on the order of $100\mu\text{A}$ or less), and junction diode CR1 can be considered as a resistor (r_e about 25000 ohms). Thus the transistor emitter-base junction bias consists of the voltage drop across diode CR1. Since every junction diode has a negative temperature coefficient of resistance, an increase in temperature causes the transistor emitter-base junction resistance to decrease, and would normally produce an increased collector current in the transistor. However, the resistivity of junction diode CR1 also decreases with an increase of temperature, the diode voltage drop is lower, and increased diode current flow causes a larger voltage drop across R1 (which opposes the diode-developed bias); therefore, less actual bias is developed. The net effect is to reduce the total forward bias on the transistor and thus lower the collector current sufficiently

to compensate for the increase of collector current with temperature.

The dc secondary resistance of T1 does not offset the operation since the transistor base current flow is negligible. However, considering the collector-to-base reverse-bias (saturation) current, I_{CBO} , which flows from the base through T1, CR1, V_{CC} , and R_C to the collector, we find no compensation is provided by this circuit. The normal current through forward-biased diode CR1 is so heavy that it effectively swamps the small I_{CBO} current (on the order of 2 or $3\mu\text{A}$ as compared to 75–200 μA for the normal current). As far as signal variations are concerned, capacitor C1 effectively bypasses diode CR1 and the output voltage developed across R_C is applied to the next stage, through coupling capacitor C_{CC} , in the conven-

Reverse-Biased Diode Stabilization. The circuit shown in the following figure employs external junction diode CR1 as a reverse-biased diode to compensate for transistor collector-base saturation current variations with temperature. This type of circuit is effective over a wide range of temperatures when the diode is selected to have the same reverse-bias (saturation) current as the transistor. The reverse-bias diode provides a high input resistance, which is particularly advantageous when the preceding stage is resistance-capacitance coupled.

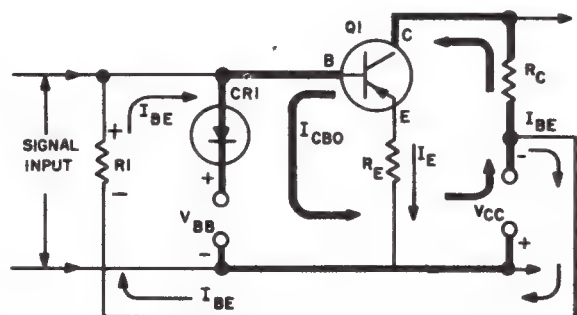


Reverse-Biased Diode Stabilization, CE Circuit

Two current paths are provided in the circuit shown. The base-emitter current (I_{BE}) flows internally from the base to the emitter, then externally through R_E and V_{CC} , and through resistor R1 back to the base, and is not materially affected by diode

CR1 because of its large resistance in the reverse direction. The other path provides for the saturation current from collector to base, through CR1, V_{BB} , and V_{CC} , and through collector load resistor R_C to the collector. Temperature variations in the emitter-base junction resistance are compensated for in the first path by swamping resistor R_E . Refer to the previous discussions in this section of Transistor Common-Base and Common-Emitter circuits. Variations of saturation current with temperature are compensated for by the second path, using diode CR1. When a temperature increase causes the transistor junction saturation current to rise, the diode saturation current also increases, so that there is no chance for the I_{CBO} current carriers in the junction to pile up, increase the transistor forward bias, and cause a consequent rise in emitter current. As a result, although the saturation current may increase, the emitter current does not, and there is only a negligible change in the total collector current. In effect, diode CR1 operates similarly to a variable grid-leak in an electron tube circuit. The reverse bias permits only a few microamperes of current to flow in the base-to-emitter circuit, and maintains a high input resistance, while simultaneously compensating for changes in I_{CBO} with temperature.

Double-Diode Stabilization.

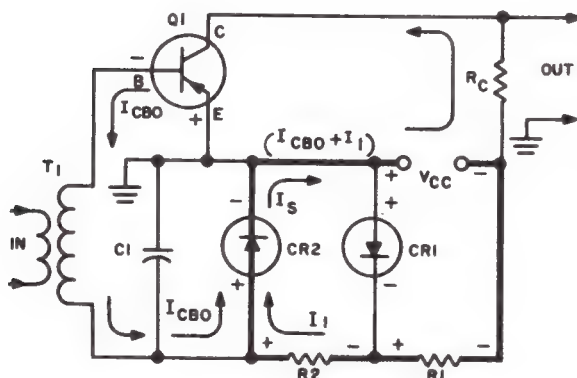The following circuit utilizes two junction diodes in a back-to-back arrangement. Junction diode CR1 is forward-biased and compensates for emitter-base junction resistance changes with temperature below



Double-Diode Stabilization, CE Circuit

50 degrees Centigrade, as described in the previous paragraph. Diode CR2 is reverse-biased and compensated for higher temperatures as discussed below.

Forward-biased diode CR1 operates in the same manner as in the previous discussion on Forward-Biased Diode Stabilization, and all comparable parts are labelled exactly as in the previous discussion.

Reversed-biased diode CR2 can be considered inoperative at room temperatures and below. When the junction temperature reaches the point where saturation current flows, CR2 conducts and current (I_1) flows through R2, producing a voltage drop with the polarity as shown. This voltage drop is in the proper direction to reduce the forward bias set up by diode CR1 and R1; its net effect is to reduce the total collector current, to compensate for the increase in transistor I_{CBO} due to temperature increase.

The reverse-biased diode is selected to have a larger saturation current (I_s) than the transistor it stabilizes, since I_s consists of the transistor Saturation current plus the current through R2 ($I_s = I_{CBO} + I_1$). Thus the diode saturation current controls the transistor at all times, effectively reducing the forward bias as the temperature increases and stabilizing the collector current. Capacitor C1 bypasses both diodes for ac so the bias circuit is not affected by signal variations.

Diode Voltage Stabilization.


If a junction diode is reverse-biased, current flow does not entirely cease, but continues at a low rate (a few microamperes), until the bias is increased to the point where it reaches the breakdown voltage. If the reverse-bias is increased beyond the breakdown point, the diode reverse-saturation current suddenly increases, because of the avalanche effect, and the applied voltage remains practically constant. In most cases this will destroy the diode because of overheating (except in the special case of the Zener diode). Reduction of the bias below the breakdown voltage level returns the junction to its normal operation again (provided that no damage has occurred). Application of the avalanche phenomenon has resulted in the development of a voltage-stabilizing diode known as the breakdown diode, often called a Zener diode.

The breakdown, or Zener, diode is a PN junction modified in the manufacturing process to produce a breakdown voltage level which is closely controlled over a range of from 2.5 to 200 volts or more. Each Zener diode has a specific breakdown voltage (and operates over a small voltage range), depending upon

its design characteristics, and must be selected for the desired operating voltage.

Because of its unique properties, this diode has many uses other than the basic voltage-regulating application. For example, it may be used for surge protection, as an arc reducer (across contact points), as a dc coupler in an amplifier, as a reverse polarity gate, or as a biasing element. Its basic properties will be discussed in the following paragraphs for proper understanding, and special applications will be treated as the need arises in other part of this handbook.

A typical dc voltage-regulating circuit of the most elementary type is shown in the accompanying illustration. Resistor R1 is selected to produce the proper breakdown voltage to maintain diode CR1 at the correct operating point. When the input voltage rises, current through the diode increases, and the drop across R1 becomes greater so that the output voltage remains the same. Conversely, when the input voltage decreases, current through the diode decreases, and the drop across R1 becomes less so that the output voltage again remains the same. Should the load resistance decrease, and more current be required, the current is divided between the load and the diode to ground path, so that no more current is drawn through R1 and the voltage across CR1 remains the same. When the load resistance increases so that less current is required, the additional current is absorbed in the diode current flow to ground, again dividing so that no additional or reduced current passes through R1, and the voltage across the diode remains the same. Thus through the avalanche effect, the breakdown diode operates similarly to the electron tube type of glow discharge voltage regulator.

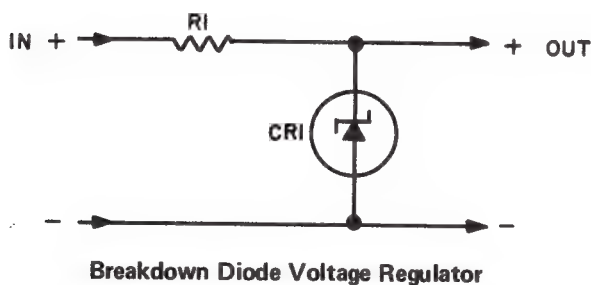


Temperature Compensation.

Forward-biased junction diodes have a negative temperature coefficient of resistance, and so do

reverse-biased junctions until the breakdown voltage is reached. Once the diode is operating in the avalanche-effect region, the temperature coefficient becomes positive and of a larger value. An uncompensated diode can vary as much as 5 percent (of the maximum rated voltage); with temperature compensation, however, it is possible to reduce this figure to .0005 percent (a few millivolts) or better.

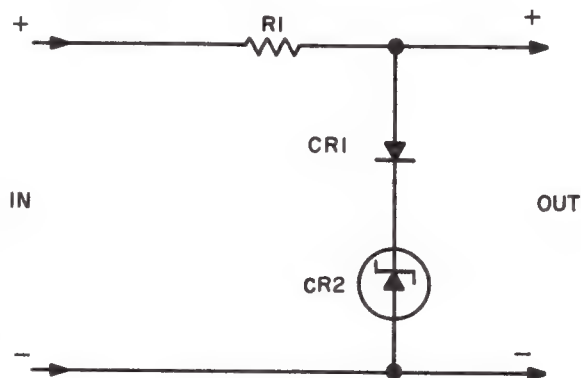Because a forward-biased junction diode changes resistance with temperature in exactly the opposite direction from the breakdown diode, it is possible to use one or more forward-biased diodes for temperature compensation. Following is a basic compensation circuit, in which CR1 is a forward-biased diode and CR2 is the breakdown diode.




Breakdown Diode Temperature Compensation

The CR1 diode is selected to have a temperature characteristic which is the exact inverse of the breakdown diode's temperature characteristic (if necessary more than one diode is used in series, but usually not more than three). Thus the combined resistance of both diodes (CR1 and CR2) in series remains constant over a wide range of temperatures and voltages to produce the desired compensation. The compensating diode must be able to pass the current taken by the breakdown diode, and should not introduce any appreciable voltage drop in circuit (across the diode itself). Fortunately, the use of forward bias produces only a very small voltage drop, depending on the material forming the junction (about 0.6 to 1.5 volts for silicon, and units with adequate current ratings are available

to produce the desired regulation. A particular advantage of the breakdown diode over the electron tube type of voltage regulator is that breakdown voltages are easily manufacturable over a wide range of approximately 2.5 to 200 volts, whereas the lowest tube voltage available is about 70 volts. Adequate voltage stabilization for quite a wide range of circuit operations and temperatures is therefore available. Unique applications of the preceding principles will be discussed in connection with applicable circuits in other sections of this handbook.

Shunt-Limiting Diode.

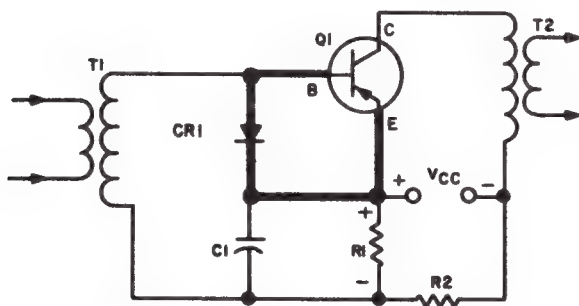The following circuit utilizes a junction diode connected in shunt between the base and emitter of the transistor as a protective peak limiter for transient voltages.



Basic Shunt-Limiting Diode Circuit

Under normal circuit conditions diode CR1 is inoperative, being reverse-biased by the potential across resistors R1 and R2, and the transistor is forward-biased by the drop across R1. When an oppositely polarized input signal (or noise transient) exceeds the bias voltage across R1, diode CR1 becomes forward-biased and conducts, effectively shunting the transistor base and emitter terminals. Thus the base-emitter junction of the transistor is prevented from becoming reverse-biased by excessive signal swing.

This peak limiting action is particularly applicable to transformer-coupled transistor stages because they develop transient voltages when the collector current is suddenly cut off by bias reversal. The resulting high collector-emitter voltage with base-emitter circuit reversed-biased can then produce strong internal oscillations and cause excessive power dissipation, which

could destroy the transistor. In this circuit C1 is a low-resistance bypass capacitor to shunt R1; it is not used to resonate with the secondary of T1.

CLASSES OF AMPLIFIER OPERATION (ELECTRON TUBE)

Amplifier operation is divided into three general classes: Class A, Class B, and Class C. The classes are determined by the operating bias applied, the amplitude of the input signal, and the amount of time during the operating cycle that plate current is allowed to flow.

These general classes of operation cover a large range of operation; since it is possible to operate an amplifier partially within one class and partially within another, additional designations are added to indicate whether or not grid current flows. *When grid current does not flow at all during the entire cycle of operation, the suffix (or subscript) 1 is added to the class letter; when grid current flows, for even a portion of the cycle, the number 2 is added.* Thus Class AB1 operation indicates that the circuit is biased to operate somewhere between the limits of Class A and Class B operation and that no grid current flows during the operating cycle. Similarly, Class AB2 operation indicates that the circuit is biased to operate somewhere between the limits of Class A and Class B operation, and that the input signal exceeds the bias sufficiently to produce grid current flow over a portion of the cycle.


Class A operation produces the lowest power conversion efficiency and the least amount of distortion, while Class C produces the greatest possible power efficiency with the most distortion, with Class B being intermediate between the two values. When no grid current is drawn during the operating cycle, there is no power loss in the grid circuit, and a minimum of driving power is required. When grid current is drawn, a power loss occurs in the grid circuit, and the driver stage must be able to supply power at the required maximum drive voltage.

Class A Operation.

In normal Class A operation, the electron tube is operated on the linear portion of the grid-plate transfer characteristic curve, and plate current flows continuously over the entire input cycle. Because operation is on the linear portion of the curve, distortion is

low (on the order of 2 to 3 percent maximum) and voltage gain is high. Because of plate current flow over the entire cycle, plate efficiency is extremely low (on the order of 20 to 30 percent) and power output is low.


Class A operation is usually employed where voltage amplification rather than power output is desired, or where low power output is desired with a minimum of distortion. Thus it is used in the r-f and i-f stages of receivers, in low-power test equipment, in the oscillator and driver stages of low-power transmitters, in video amplifiers, and in audio-amplifier applications where voltage gain with good fidelity is desired.

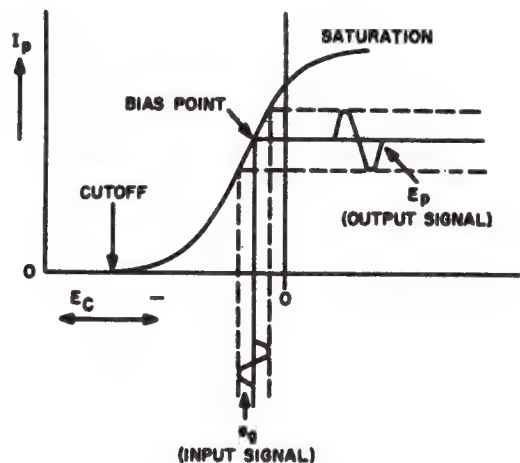

Class A Operation

Normally, no grid current flows during any part of the cycle and pure Class A operation is defined as A_1 . However, in common usage the subscript is dropped, and it is understood that unless otherwise indicated no grid current flows. When the input signal amplitude exceeds the bias voltage and grid current does flow over a portion of the cycle, the subscript 2 is used, e.g., A_2 . When grid current flows, a larger input signal is required to drive

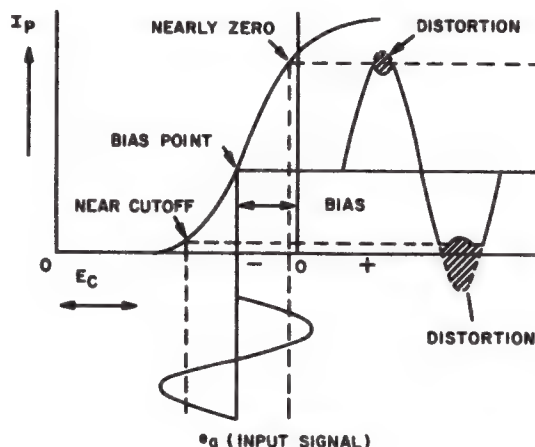the tube to the same output, and distortion increases; but at the same time, plate current flow reduces during the grid-current portion of the cycle and the overall plate efficiency is increased.




Class A_2 Operation

Class B Operation.

Biasing of Class B amplifiers is such that, with no grid input signal, the plate current is biased to cutoff; consequently, no plate current flows for approximately half the operating cycle (180°), and grid drive is sufficient to cause grid current flow. Since plate current flows for only half the cycle, it is necessary to use two tubes in a push-pull arrangement to reproduce the full positive and negative input swings, and to minimize distortion. An exception to this rule is in an r-f amplifier where the missing half of the signal is supplied by the tank circuit, and the distortion can be tolerated.

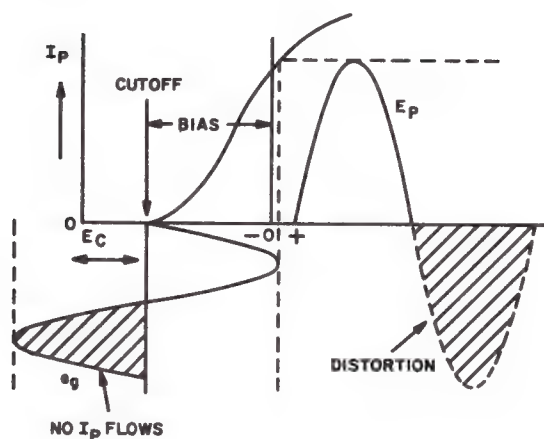Class B operation is normally characterized by moderate efficiency (40 to 60%) in the plate region, with low driving power, and somewhat greater output distortion (4 to 6%). Typical Class B operation for a single tube is illustrated in the following figure.



Class B Operation

Class B amplifiers are used extensively for audio output stages where high-power outputs are required; they are also used as the driver and power amplifier stages of transmitters and as audio modulators.

Special tubes have been developed, particularly for Class B operation, which normally rest at plate current cutoff without bias applied. These tubes, together with improved transformer design, make it possible at the present state of the art to design Class B stages which compare favorably in performance with Class A stages, and yet provide the increased power output and efficiency of Class B operation.


Class AB Operation.

In this type of operation, the bias is set between Class A and Class B so that the amplifier operates Class A for small input signals and Class B (really Class AB₁) for large input signals. Plate current flows for more than half the operating cycle, but not for the entire cycle. In addition, the input signal, although just about equal to the bias, is not great enough to produce grid current flow.

This type of operation is used where good fidelity and increased efficiency are desired but without sufficient drive to produce full Class B operation or excessive distortion.

As can be seen from the following illustration, the bias for Class AB operation is about halfway between the values for Class A and cutoff. The power output and efficiency are higher than with Class A operation, but at the expense of more distortion. To reduce the

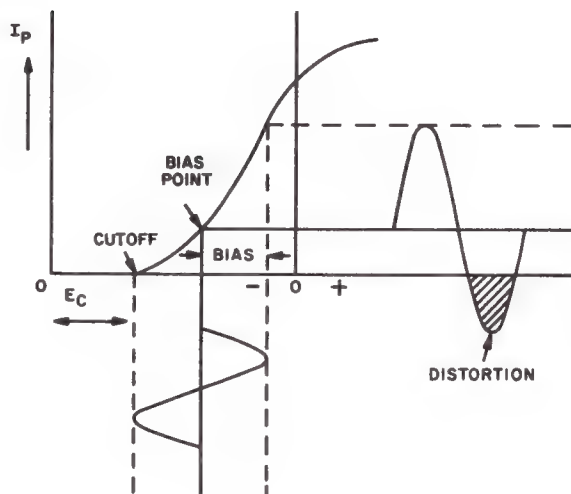effective distortion, Class AB audio amplifiers are operated push-pull, in which case the efficiency is much greater than that of Class A operation with about equal distortion.




Class AB Operation

Class AB₂ amplifiers require low-impedance grid drive sources because of grid-current flow and, therefore, are often transformer-coupled to power drivers. This class of operation provides power output and efficiency ratings more nearly equal to those of Class B operation.

Class C Operation.

In Class C operation, the bias is adjusted to twice the cutoff value or more (usually does not exceed four times cutoff value). Plate current flows only on the peaks of the driving signal, the grid is always driven positive, and extremely high efficiency is produced, (70 to 85%). Because of the high distortion produced, Class C has not been found useful for audio-frequency amplifier operation. But it has proven excellent for use in r-f amplifiers, where tank circuits provide the missing portion of the signal, and extremely high powers can be conveniently and efficiently handled. The fly-wheel effect of the tuned tank circuit serves to smooth the intermittent pulses of plate current into sine-wave oscillations in the tank circuit.

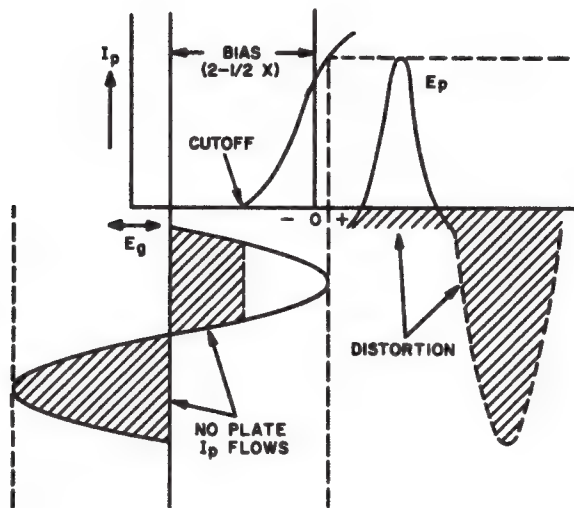Since grid current always flows, this type of operation should be designated as Class C₂ but, being generally understood, this notation is usually never used. The following figure illustrates Class C operation.



Class C Operation

CLASSES OF AMPLIFIER OPERATION (SEMICONDUCTOR)

Since transistors are analogous to vacuum tubes, the same general classes of amplification, input and output parameters, distortion, and efficiency are applicable. Thus the transistor can be operated as a Class A, Class B, Class AB, or Class C amplifier. Operating conditions and results for the ideal case are used in the following discussion to define the differences and relationships between the classes of operation.

Class A.

The Class A amplifier is biased so that it operates on the linear portion of the collector characteristic, providing for equal swings above and below the bias point. Collector current flows continuously (with or without signal) for 360 degrees of the operating cycle, and the transistor is operated so that the maximum collector dissipation is never exceeded (other classes momentarily exceed this rating).


The Class A amplifier is basically a small-signal amplifier, although it can be used as a large-signal amplifier provided that the quiescent current does

not exceed the maximum transistor ratings. Usually, large-signal amplifiers of the power type are operated as Class B amplifiers. Class A amplifiers may be operated in push-pull or as single-ended stages.


While the efficiency of a vacuum-tube amplifier operated Class A averages around 30 percent, the efficiency of a transistor operated Class A varies considerably, depending upon the circuit configuration and the parameters used. Considering the ideal case, it can be demonstrated mathematically that the direct-coupled Class A amplifier produces a theoretical maximum of 25 percent in either the CB or CE circuits. On the other hand, a resistance-coupled circuit will produce a maximum collector efficiency of 17 percent. The highest possible efficiency, 50 percent, is obtained with transformer-coupled configuration (assuming a perfect transformer, with no losses), or by use of a shunt collector feed.

For Class A operation, the transistor must be capable of dissipating more than the desired power output.

Typical Class A operation for CB and CE configurations are shown in the following illustrations. Note that operation does not extend into the saturation region since the knee of the curve makes operation here very nonlinear. Likewise, operation in the cutoff region is not permitted, because current would flow for less than the entire cycle. Comparing the graphs of these two figures it is seen that the CB circuit is inherently more linear since the constant-current curves are more equally spaced than those of the CE circuit. Therefore, the distortion is lower in the CB circuit than in the CE circuit. Other parameters which affect the distortion produced are: the amplitude of the input signal (if too large, it will be clipped), the value and linearity of the input resistance, and appreciable variation of the bias with temperature. To minimize distortion and produce maximum gain, the CB circuit uses an input resistance of about two times the source impedance, while the CE circuit uses an input resistance one to three times the source impedance, to minimize the over-all input resistance variations. Although the CB circuit produces less distortion and more power output for the same percentage distortion as the CE circuit, the CE circuit is usually preferred for all around use because it is easily cascaded and has a high power gain.

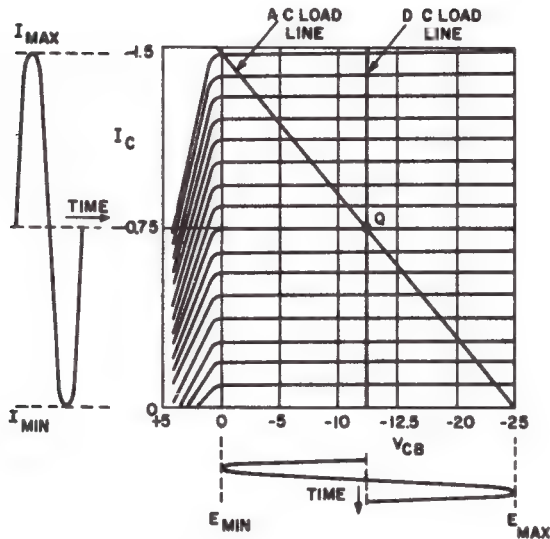

CB Class A Graphical Operation

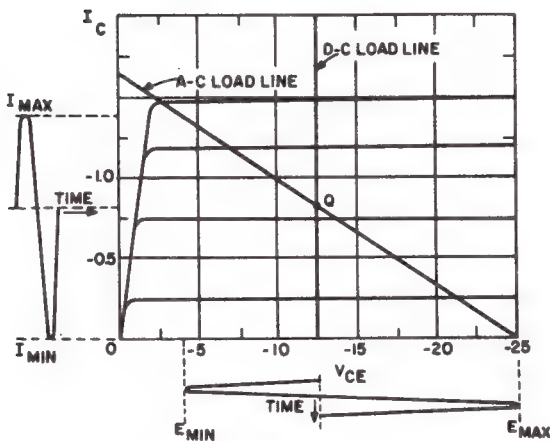

CE Class A Graphical Operation


Class B.

Class B amplifier operation is obtained when the collector current flows for one half of the operating cycle, and is entirely cutoff during the other half. The bias is set at the cutoff point (zero bias), and during the positive input signal swing on NPN transistor will amplify in a normal fashion; on the negative swing the transistor is cut off and does not operate. A PNP transistor will conduct during the negative half cycle of the input signal and remain cut off during the positive swing. To produce the full input signal, two

transistors must be employed, operating back-to-back in a push-pull arrangement. On one half of the cycle one unit operates, on the other half cycle the other unit operates, and the halves are combined and added in the load. Thus each transistor operates for only half the operating period.

A graph of Class B operation is shown in the accompanying illustration with the input and output signals projected from the transfer characteristic. Note that while collector cutoff is assumed there is a small flow of reverse leakage current, I_{CEO} , which reduces the total efficiency of the circuit. Ideal efficiency is 78 percent, which is quite an improvement over Class A operation. Distortion components are the same as for Class A plus an additional type, known as *crossover distortion*. Since two transistors are employed, even though operating only half the time, the distortion is greater than for Class A depending on the circuit design. At the present state of the art, no general figures to indicate the possible range of values of distortion are available, since to obtain the necessary gain or output it may be necessary to accept more distortion with one transistor and design than with another.

Figure A-209

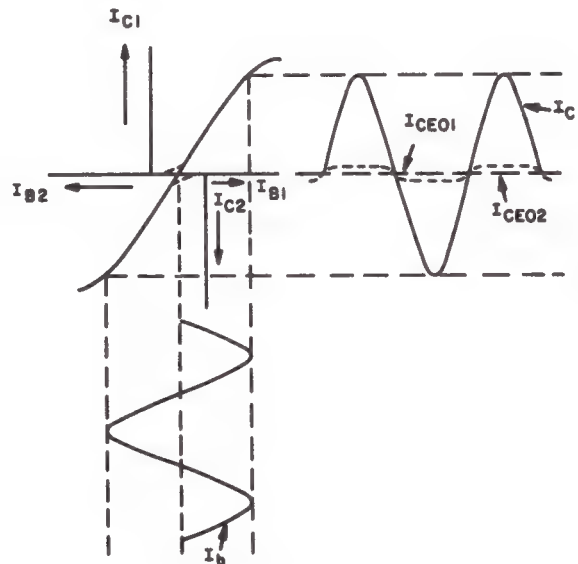


Typical Class B Operation

Because each transistor operates for only half the time and the power conversion efficiency is high, the

Class B operated transistor is required to dissipate only about 35 percent of the total output power desired. Hence, much greater power output is possible with lower rated transistors for the Class B amplifier. Since the ideal case is usually not obtained, the percentage to be dissipated should be calculated in each instance, but the value given above is a rough approximation for comparison purposes.

Class B operation is usually used for audio power amplifier stages, but is seldom employed single-ended. However, single-ended operation is applicable to transmitters using tank circuits to fill in the missing half of the output signal, as in vacuum-tube operation.

Crossover distortion is caused basically by the non-linearity of the transistor characteristics. At small input voltages the current change is small and varies exponentially, but at higher input voltages the transistor conduction is heavier and heavier. This action produces an inward belly, as shown in the following figure, and increased distortion. Compensation for crossover distortion is usually achieved by placing a slight forward bias on the base of the transistor, to move the bias point to a more linear portion of the transfer characteristic. While feedback can be used or the source resistance can be increased to minimize crossover effects, circuit design complications, together with the loss in the increased source resistance, make these types of compensation generally unsatisfactory for general use. Actually, the biasing-off type of compensation places the amplifier in the Class AB range of operation.

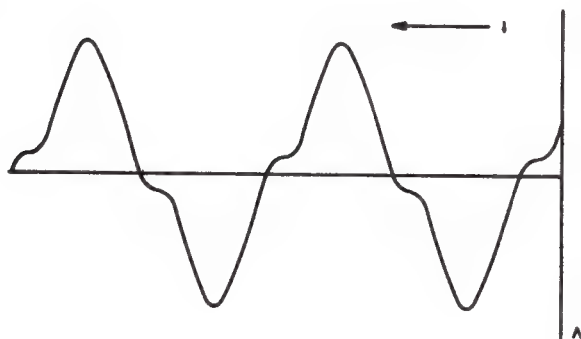


Crossover Distortion

Class AB.

Operation in the Class AB region is obtained by biasing to the point where collector current flows for more than a half cycle, but not for the entire cycle as in Class A operation. By arranging the bias properly, efficiencies between 50 and 78 percent are obtainable, with an average of 65 percent representing typical Class AB operation.

A graph of typical Class AB operation is shown in the accompanying illustration. Distortion is less than that of Class B and more than that of Class A. The circuit arrangement is usually pushpull. However, for those applications which can tolerate the increased distortion, it is possible to use single-ended operation with an increase of output over Class A operation. For push-pull operation, Class AB represents greater power output and slightly more distortion than Class A, but less power output and slightly less distortion than Class B.

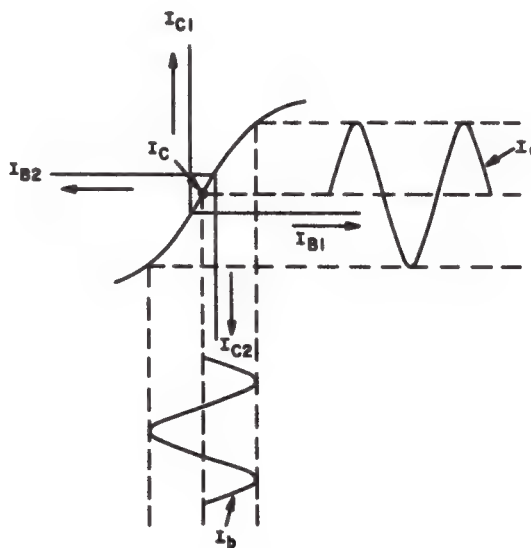

Typical Class AB Push-Pull Operation


Class C.

Class C operation is obtained by biasing to the point where collector current flows for less than a half cycle, with the transistor remaining in the cutoff condition and with a slight cutoff (reverse) current flowing during the inoperative portion of the cycle. Class C operation is not used for audio amplification

because of the severe distortion it produces. It is used for tank circuit applications where the distortion is smoothed out and minimized by the flywheel effect, as in vacuum-tube operation; also, it is used in single-ended or push-pull configurations. Switching circuits are usually operated as Class C amplifiers.

To achieve Class C operation with a bias point considerably below cutoff, it is necessary to reverse-bias the emitter (assuming a common-emitter circuit), as opposed to forward-bias for normal operation in the other classes.

The Class C amplifier can be considered to operate as a pulsed oscillator for r-f energy, where the input pulses cause conduction for a small portion of the operating cycle, and the transistor rests with a small steady current during the remainder of the cycle, in a cutoff condition, with the r-f oscillations being sustained by the parallel resonant tank circuit. Assuming an input sine wave, it is only necessary to supply the losses in the tuned inductor by transistor conduction, and obtain an amplified sine wave output produced by the voltage gain factor. Naturally this type of operation is restricted to essentially sine-wave oscillations produced at the frequency to which the tuned load circuit is resonant. A typical Class C amplifier circuit with input and output waveforms is shown in the following illustration.

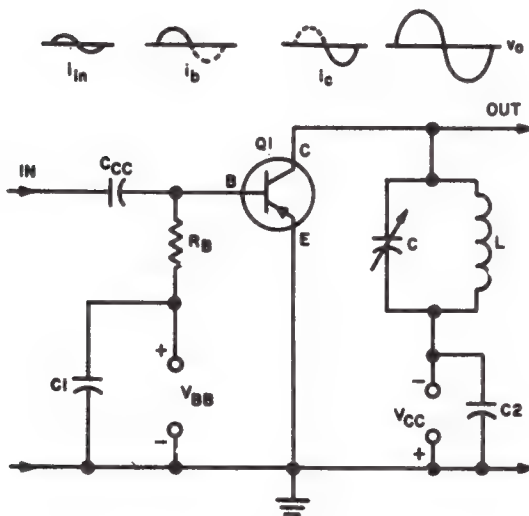


Class C Amplifier, CE Circuit

COUPLING METHODS (ELECTRON TUBE)

Usually more than one amplifier, operated in cascade, is needed to increase the amplitude of the feeble input signal to the required output value. Cascaded amplifier stages are connected (coupled) together by resistance-capacitance networks, impedance-capacitance networks, transformers, or direct coupling as described in the following paragraphs. While all coupling networks are frequency-responsive, some coupling methods provide better response than others, and their basic principles of operation remain the same, regardless of whether or not they are employed singly as input or output coupling devices, or in cascade. Discussion in this section will be limited to the actual types of coupling and important considerations involved in the various functional classes on a relative or comparative basis. Circuit discussions in other sections will fully cover the limiting parameters for the specific circuit arrangement.

R-C Coupling.

Although R-C coupling involves the use of two resistors and a capacitor, as shown in the following figure, it is usually referred to as resistance coupling. Because of the rather wide frequency response offered by this form of coupling, plus small size and economy, the resistance coupler finds almost universal use where voltage amplification is required with little or no power output. Basically the resistance coupler is a Pi-type, hi-pass network, with plate resistor R_L and grid resistor R_g forming the legs of the Pi and capacitor C_c the body. Since the plate and grid resistors are not frequency-responsive, it can be seen that basically over-all frequency response is limited by the capacitive reactance of C_c between the plate and grid circuits, plus the effect of shunt wiring and electrode-to-ground capacitances across the network. At dc or zero frequency the coupling capacitor separates, or blocks the plate voltage of the driving stage from the grid bias of the driven stage, so that bias and plate or element voltages are not affected between stages.

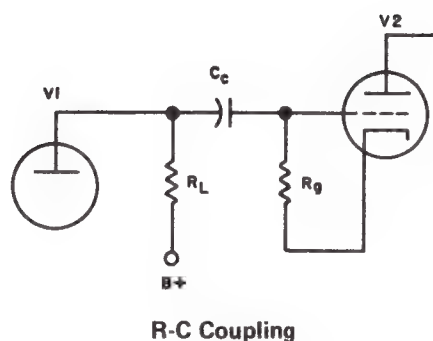


In the conventional R-C amplifier signal voltage variations on the grid produce plate current variations through plate load resistor R_L , and the resulting voltage developed across R_L represents an amplified replica of the input signal but 180 degrees out of phase. The amplified signal is coupled through capacitor C_c , and applied to the grid of the next stage across grid load resistor R_g . The same cycle of operation is repeated for each stage of the cascaded amplifier.

Since load resistor R_L is in parallel with the internal tube plate resistance, r_p , the load resistor of a triode is never made less than twice r_p . Usually the maximum undistorted output for a triode is obtained with a value of R_L that is 5 to 10 times the plate resistance of the tube. With pentodes the extremely high r_p makes this impractical; best results are usually obtained with a load resistor of 1/4 to 1/10 the value of r_p , or with a value that is as high as is practical for the plate voltage and current needed without requiring excessive supply voltage.

At low frequencies (below 100 Hz), the reactance of C_c , plus R_g in series, parallels the load resistor. But the reactance of C_c is in series between the plate and grid, and produces a large voltage drop (or loss of gain), while R_g shunts the grid and has the least voltage developed across it. Therefore, the interstage grid resistance has less over-all effect on the gain than the reactance of C_c , and the distributed circuit and electrode capacitance to ground is not effective and may be neglected. Low-frequency response, therefore, is controlled by the size of the coupling capacitor. Simplified equivalent circuits of R-C coupling (constant current generator form) are shown in the following illustration. Part A is a simplified equivalent low-frequency circuit. Only those circuit elements which are of significance at low frequencies are shown. When the coupling capacitor is excessively large,

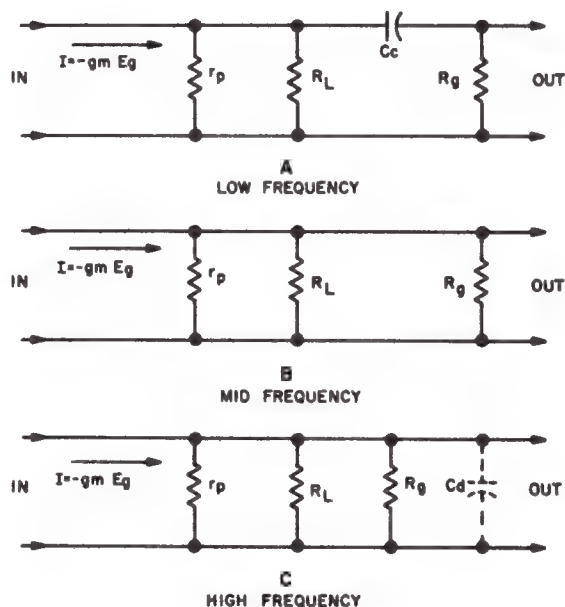distortion is caused by excessive phase shift, and motorboating may occur. Motorboating is caused by regenerative feedback at low frequencies through impedance coupling in multiple cascaded R-C stages with a common power supply.



**Simplified Equivalent Circuits
(Constant Current Generator Form)**

Over the mid-frequency range (100 to 20,000 Hz), amplification is relatively constant, and the coupling capacitor reactance is much lower than the resistance of grid resistor R_g . Therefore, the reactance of coupling capacitor C_c may be neglected as in the simplified equivalent mid-frequency circuit of part B. To insure that the plate resistor is not shunted excessively by the grid resistance of the following stage and to maintain a high input resistance, R_g is made two to four times R_L and never less than R_L . Usually in low-level stages the grid resistor is in the megohm range (from 1 to 5 megohms), with its value for grid leak bias ranging from 5 to 10 megohms; whereas in power amplifier stages the grid resistor is on the order of 0.5 megohm and usually never more than 1 megohm. High values of grid resistance tend to cause adverse effects due to the possibility of grid current flow caused by imperfect evacuation, grid emission, and leakage effects in the electron tube.

In the high-frequency range (over 20,000 Hz), the coupling capacitor reactance is neglected entirely and shunt capacitive effects become the limiting parameters. The shunt capacitance consists of the plate-to-ground (tube output) capacitance, the grid-to-ground (input) capacitance, plus the distributed wiring and network capacitance to ground. The effects of these individual capacitances are cumulative and may be lumped together, as shown by C_d in part C. The overall effect of this capacitance is to shunt the signal to ground and reduce the response.


In high-fidelity amplifier circuits, increased low-frequency response is usually desired and is achieved by bass compensating networks. Likewise, in video amplifiers both low- and high-frequency response must be increased, and is achieved through the use of shunt and series peaking circuits. For a discussion of R-C and R-L compensation considerations, refer to the discussion of time constants later in this section of the handbook.

Because of the low amount of gain available with R-C coupling at radio frequencies, it is seldom used in r-f amplifiers, but it may be encountered in special cases, particularly in test equipment.

Impedance Coupling.

When an impedance is substituted for the plate load resistor in a resistance-coupled circuit, the impedance coupling circuit results. Actually, an original circuit derivation also involved a substitution of an impedance for the grid resistor. By making the grid inductor series resonant with the coupling capacitor, bass response was improved. However, the grid impedance offered more of a disadvantage because of high-frequency shunt losses, so the L-C-R circuit as shown in the following figure became the standard impedance coupler. The impedance coupler operates in the same manner as the resistance coupler as far as C_c and R_g are concerned; the basic difference is in effect of the plate impedance. By using an impedance in the plate circuit, less voltage drop occurs for a given voltage supply. Therefore, a lower supply source will provide the same effective plate voltage, there is less I^2R (power) loss, and a better over-all efficiency results. Low-frequency response is dependent upon obtaining a high inductive reactance in

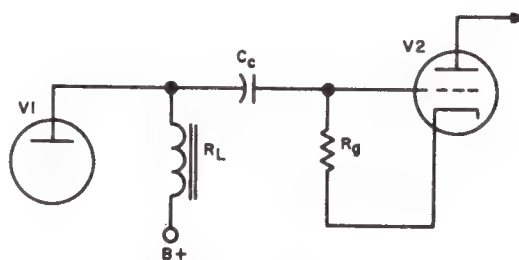the plate circuit, and requires a large number of turns for good low-frequency response. The distributed capacitance associated with a winding of many turns produces a large shunting capacitive reactance with a consequent drop in high-frequency response. Since the impedance of plate reactor varies with frequency, the response is not as uniform as that of the resistance coupler.




Impedance Coupling

The impedance coupling circuit is used where a limited response over a relatively narrow band of frequencies is required. As a result, impedance coupling is mostly employed in tuned or untuned amplifier applications such as i-f or r-f stages, and its use in audio applications has generally been discontinued in favor of the R-C or transformer-coupled circuit, except for special designs.

As in the resistance-coupled amplifier, series and shunt peaking compensating networks may also be employed to extend frequency response. Bass boost circuits in particular can be advantageously used. However, as frequency compensation is increased, the circuitry becomes complex and its use is restricted to a particular application, so that the basic type of coupling circuit is no longer of much significance.

Transformer Coupling.

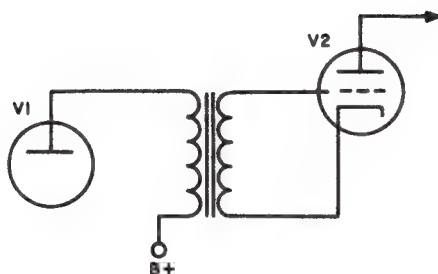When the primary of a transformer is connected as the plate load, and the secondary provides the output signal, either to the next stage or an output device, we have what is known as transformer coupling; see accompanying figure.



Transformer Coupling

With transformer coupling, response gain, and output considerations become more difficult to predict, because they depend primarily on the transformer design. Basically, the use of transformer coupling provides additional gain, achieved through the use of a step-up turns ratio of primary to secondary, but this gain usually does not exceed 2 or 3 to 1. Since there is no physical dc connection between stages, plate and bias voltages are kept separate, and the ac signal is coupled from the plate of one stage to the grid of the following stage by the mutual inductive coupling between primary and secondary windings.

Low-frequency response is primarily dependent on the inductive reactance of the primary, dropping off approximately 3 dB at the frequency where the inductive reactance is equal to the plate resistance plus the primary resistance ($2\pi fL = R_p + R_{pri}$).

Gain at the mid frequency is the highest and is essentially equal to the amplification factor of the electron tube multiplied by the transformer turns ratio. Response is considered to be relatively flat over a range of frequencies above and below the mid frequency, but such results are usually achieved only in the ideal case. In practice, the response curve is a continually changing curve, dropping off on either side of the mid frequency, with possible humps produced by circuit and transformer resonances.

Since the secondary contains more turns than the primary, a larger shunt capacitance to ground is produced and, together with the primary and secondary leakage reactances, limits the high-frequency response.

Transformer coupling is generally used for interstage applications with electron tubes having plate resistances of 5 to 10 thousand ohms maximum, since higher plate resistances require excessively large trans-


former primary inductances. For output stages, lower plate resistances are used, and the transformer is carefully designed to handle larger plate currents. Generally speaking, a lower plate resistance improves bass response, while a higher amplification factor provides greater gain, and lower plate current produces less dc core saturation effects.

Since the impedance transformation in a transformer varies as the square of the turns ratio between primary and secondary, output and input matching is possible and is extensively employed. For interstage applications, matching is not always used, because power output is not required; in this case, more attention is given to the step-up ratio to provide a higher voltage gain.

The limitations of frequency response generally restrict the use of transformer coupling to audio circuits which do not require an exceptionally wide bandpass or frequency response, but do require voltage or power outputs. Wide use is found for transformer coupling in the radio and intermediate frequency ranges where selective, high-Q bandpass filters and tuned transformers are universally used. See Tuned Interstage IF Amplifiers Circuit in another part of this section of the handbook for a discussion of tuned transformer coupling.

Direct Coupling.

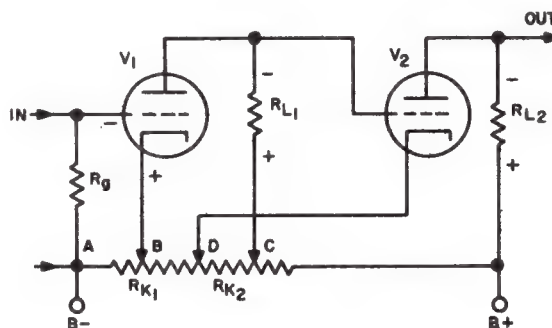Direct coupling is characterized by the direct connection of tube elements; that is, the plate of the driver stage is physically connected to the grid of the driven stage, and the coupling network is eliminated. A basic two-stage dc amplifier is shown in the following figure.



Direct-Coupled Amplifier Circuit

Since the plate and bias circuits are not isolated by a transformer or coupling capacitor the direct-coupling circuitry is slightly complicated by the arrangement necessary to produce an effective negative bias. Usually a voltage-divider bias arrangement similar to that shown is used.

The cathode of V1 is biased by R_{K1} between points A and B on the divider, while the plate is connected through R_{L1} to point C, which is at a potential equal to approximately half the supply voltage. Plate current through load resistor R_{L1} (which is also the grid resistor for V2) provides a negative voltage drop and bias on V2. The cathode of V2 is tapped back at point D on the divider, and produces a voltage in opposition to the drop across R_{L1} . When R_{K2} is correctly adjusted, the voltage on the cathode of V2 is always more positive than the plate of V1 (and the grid of V2), producing an effective negative bias on V2 of the desired value. Voltages must be chosen so that the grid of V2 is not driven positive by the input signal. Since the plate of V2 is at the highest positive point, it is more positive than the cathode and conduction occurs. Thus the plates are maintained positive and the grids negative, to provide the conditions required for operation.

Because there is no coupling network inserted between the output of one tube and the input of the following tube, there is no phase distortion, time delay, or loss of frequency response. Since the plate and grid of the tubes are directly connected, the low-frequency response is extended down to dc (zero frequency). The high-frequency response is limited only by the tube interelectrode-to-ground capacitance, plus the circuit distributed wiring capacitance. By appropriate matching (or mismatching) of tubes, high values of amplification and power output may be obtained.

Since the use of more than two stages requires plate voltages two or more times the normal value for one tube, plate supply considerations limit dc coupling to a few stages. Any change in the supply voltage affects the bias of all the tubes and is cumulative; therefore, special voltage supply regulation circuits are necessary. Noise and thermal effects in tubes produce circuit instability and drift that limit the use of this type of coupling in audio or r-f amplifiers.

Because of its ability to amplify direct current or zero frequency, dc coupled circuitry is often used in computer circuits, and in the output circuits of video amplifiers. Because response is practically instantane-

ous and no time delay occurs, it is especially valuable for pulse circuits. See Direct Coupled (DC) Amplifier circuit in another part of this section of the handbook for a more detailed discussion.


COUPLING METHODS (SEMICONDUCTOR)

The transistor, like the vacuum tube, is usually connected in cascaded stages to amplify the low input signal to the large output value needed. Coupling is accomplished by using resistance-capacitance networks, impedance networks, or transformers, or directly, by connecting the output element to the input element of the succeeding stage, as described in the following paragraphs. The discussion in this section will be limited to the basic circuit and important considerations involved for audio or relatively low-frequency circuits. When special combinations or design considerations are required to achieve a particular result (for example, r-f or i-f coupling), they will be discussed in the proper section with the special circuit with which they are used. Since all coupling networks are frequency responsive to a certain extent, some coupling methods afford better results than others for a particular circuit configuration. Generally speaking, resistance coupling affords a wide frequency response with economy of parts and full transistor gain capabilities, impedance and transformer coupling provide a more efficient power matching capability with moderate frequency response, while direct coupling provides the maximum economy of parts with excellent low-frequency response and dc amplification.

R-C Coupling.

The R-C coupler utilizes two resistors and a capacitor to form an interstage coupling device which provides a broad frequency response, with high gain, an economy of parts, and small physical size. It is used extensively in audio amplifiers, particularly in the low-level stages. Because of its poor input-output power conversion efficiency (17 percent for the ideal case), it is seldom used in power output stages.

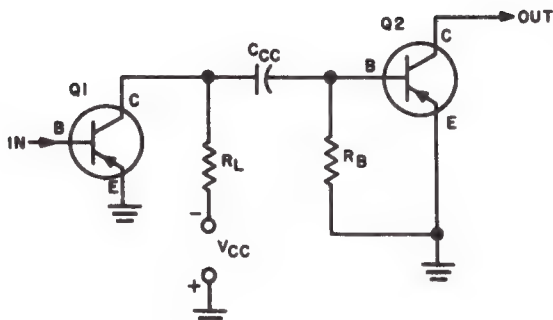A typical resistance coupler is shown in the accompanying illustration. Resistor R_L is the collector load resistor for the first stage, capacitor C_{cc} is the dc voltage-blocking and ac signal-coupling capacitor, and R_B is the input-load and dc-return resistor for the base-emitter junction of the second stage.



Resistance Coupling


Since the input resistance of the second stage is low (on the order of 1000 ohms for a CE circuit) and the reactance of the coupling capacitor is in series with the base-emitter internal input resistance, C_{CC} must have a low reactance to minimize low-frequency attenuation due to a large signal drop across the coupling capacitor. This is achieved by using a high value of capacitance; thus, for low audio frequencies, values of 10 to 100 microfarads or more are employed (compare this with the vacuum-tube coupling capacitance of less than 1 microfarad).

To prevent shunting the input signal around the low base-emitter input resistance, the base dc return resistor, R_B , is made as large as practical with respect to the transistor input resistance. Since increasing the base series resistance deteriorates the temperature stability of the base junction (see discussion of bias stabilization); the value selected for the input resistor is a compromise between reducing the effective shunting of the input resistance and maintaining sufficient thermal stability over the desired temperature range of operation.

The high-frequency response is normally limited by the stray circuit capacitance plus the input and output capacitance; hence, the transistor itself is usually the limiting factor. The low-frequency response is normally limited by the time constant of the coupling capacitor, C_{CC} , and the base return (input) resistance, R_B . For good low-frequency


response, the time constant must be long in comparison to the lowest frequency to be amplified.

Like the vacuum-tube coupling networks, transistor coupling networks may also be compensated to increase frequency response. Shown below are the basic equivalent circuits for three types of compensation: (A) shunt peaking; (B) series peaking, and (C) combined shunt-series peaking. Insertion of series inductor $L1$ (A) produces a parallel resonant effect with output capacitance C_{oe} and input capacitance C_{ie} and improves the high-frequency response about 50 percent. Insertion of inductor $L2$ (B) in series with C_{CC} produces a series resonant circuit with input capacitance C_{ie} and further increases the high-frequency response about 50 percent over that of shunt peaking. Using both series- and shunt-peaking effects (C) provides a gain about 80 percent greater than that of the series-peaking circuit alone.

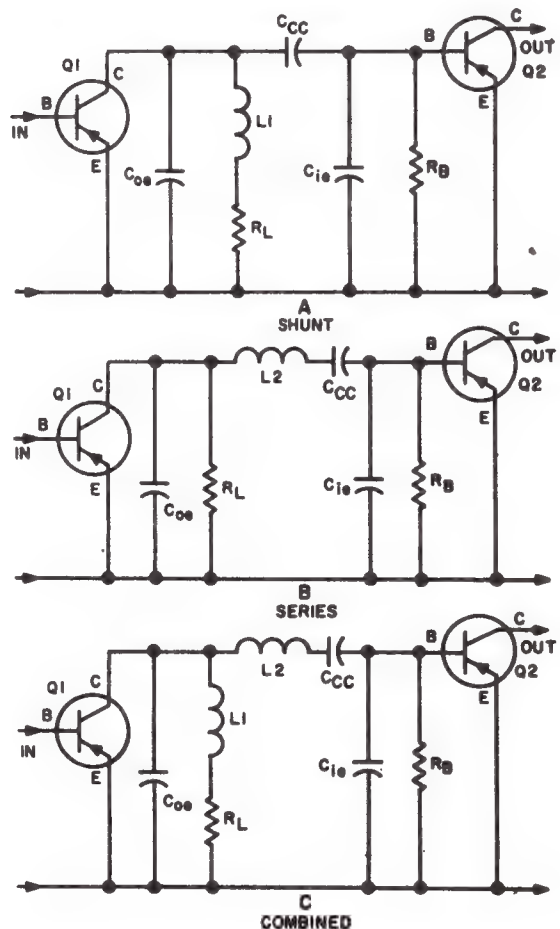

Shunt, Series, and Combined Peaking Circuits

Since the response to low frequencies is limited only by the coupling network, low-frequency compensation can be provided as in vacuum-tube circuits. The following figure shows a typical low-frequency compensation circuit. With resistor R_1 inserted in series with R_L , the collector load is increased at those frequencies for which the resistance of R_1 is effective. Since capacitor C_1 parallels or shunts R_1 , it is evident that the higher frequencies are bypassed around it, but, since the capacitive reactance of C_1 increases with a decrease of frequency, the low frequencies pass through R_1 . Thus, the load resistance for low frequencies is increased and so is the output at these frequencies. The combination of C_1 and R_1 is chosen to provide the desired frequency compensation. This type of compensation also corrects for phase distortion, which is usually more prevalent at the lower frequencies.

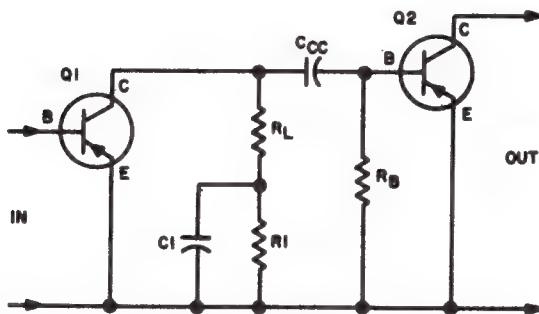


Low-Frequency Compensation Circuit

Impedance Coupling.


The impedance coupler is used extensively in the transistor field. Here the increased power-handling (and matching) capabilities of the inductor provides more output than the load resistor. While the overall frequency response of impedance coupling is not as good as that of resistance coupling, it is much better than that of transformer coupling, because there are no leakage reactance effects to deteriorate the high-frequency response.

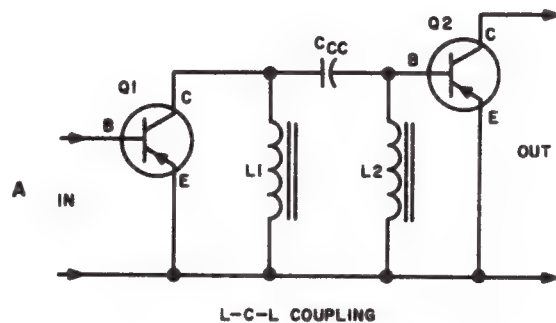Part A of the following figure shows the basic impedance-coupling circuit, and Part B shows a typical variation. The high-frequency response of the impedance coupler is limited mainly by the collector output capacitance, and the low-frequency response is limited by the shunt reactance of the inductor, L_1 .

The efficiency of the impedance coupler is approximately the same as that of the transformer-coupled circuit (50 percent for the ideal case).



L-C-L COUPLING

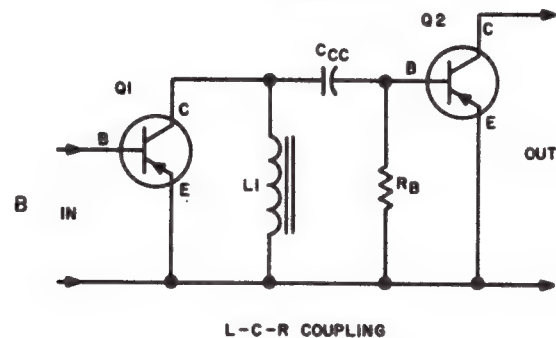

L-C-R COUPLING


Impedance-Coupling Circuits

Transformer Coupling.

Transformer coupling is used extensively in cascaded transistor stages and power output stages. It provides good frequency response and proper matching of input and output resistances with good power conversion efficiency. It is relatively much more costly and occupies more space than the simple R-C circuit components, but it compares favorably in these respects with the impedance coupler. Its frequency response is less than that of the resistance- or impedance-coupled circuit.

A typical transformer coupler is shown in the following illustration. Coupling between stages is achieved through the mutual inductive coupling of primary and secondary windings. Since these windings are separated physically, the input and output circuits are isolated for dc biasing, yet coupled for ac signal transfer. The primary winding presents a low dc resistance, minimizing collector current losses and allowing a lower applied collector voltage for the

same gain as other coupling methods, and it presents an ac load impedance which includes the reflected input (base-emitter) impedance of the following stage. The secondary winding also completes the base dc return path and provides better thermal stability because of the low dc (winding) resistance. Since the transistor input and output impedance can be matched by using the proper turns ratio, maximum available gain can be obtained from the transistor.

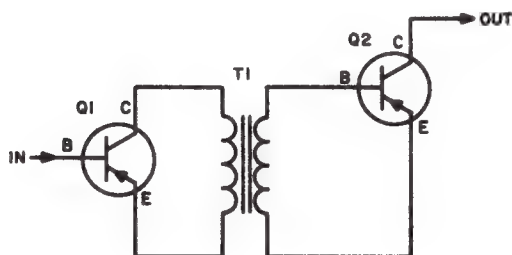

Transformer Coupling


As in the impedance coupler, the shunt reactance of the transformer windings causes the low-frequency response to drop off, while high-frequency response is limited by the leakage reactance between the primary and secondary windings, in addition to the effect of collector capacitance. Because of the low dc resistance in the primary winding, no excess power is dissipated, and the power efficiency approaches the maximum theoretical value of 50 percent.

Direct Coupling.

Direct coupling is used for amplification of dc and very low frequencies. As in vacuum-tube circuits, this method of coupling is limited to a few stages since all signals are amplified, including noise, and it is extremely susceptible to instability because of shift of operating point, cumulative dc drift, and thermal changes. Its use in power output stages is limited because of the low conversion efficiency (about 25 percent). It does offer an economy of parts, and it lends itself to the use of complementary-symmetry circuitry.


The following figure shows a base dc amplifier utilizing two PNP transistors and two power sources. When a signal is applied to the base of Q1, the amplified output is directly applied to the base of Q2 from the collector of Q1. The output is taken from load re-

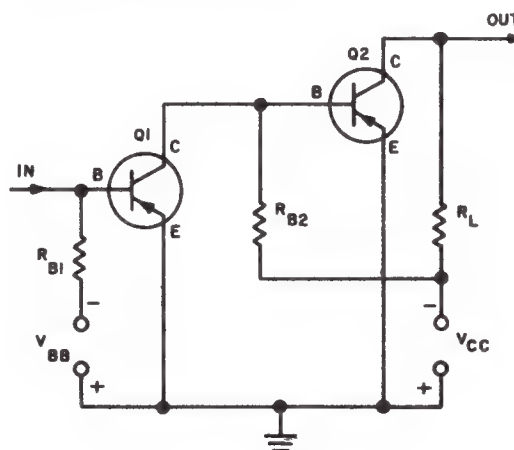sistor R_L of Q2. Since the base bias of Q2 is applied through R_{B2} , the amplified signal on the collector of Q1 must not drive the base of Q2 positive; that is, it must not exceed the negative bias.



DC Amplifier

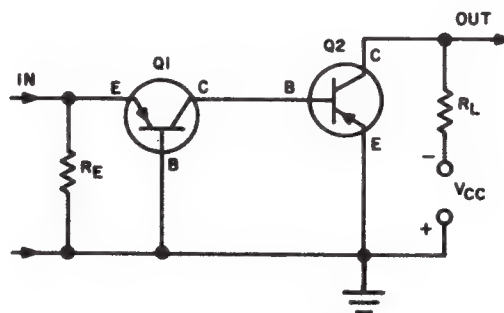
The following figure shows a basic connection not possible with electron-tube amplifiers. The grounded-base circuit of Q1 is direct-connected to the grounded-emitter circuit of Q2. Thus the input circuit of Q2 is the load for Q1, and collector bias for Q1 is obtained through the collector-to-base junction of Q2. Since Q2 biases Q1, only one power source is needed.



CB to CE DC Amplifier

A typical complementary-symmetry circuit using an NPN and a PNP transistor is shown in the following figure. Since the currents flow in opposite directions, thermal effects oppose and stabilize each other. As in

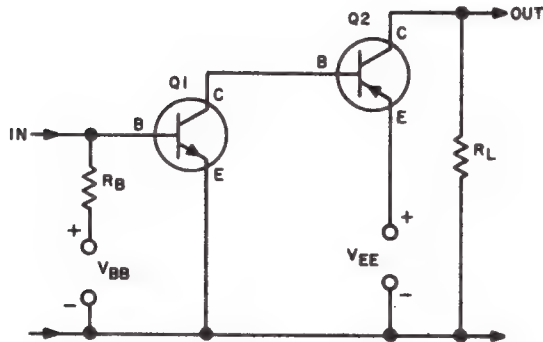the DC Amplifier circuit, the collector bias for Q1 is obtained from the base-collector junction of Q2.



Complementary-Symmetry DC Amplifier

If another stage were added an additional and larger collector bias supply would be required to maintain the collector-to-base potential negative for each stage. This limitation is analogous to that of the dc supply for the vacuum-tube amplifier. It is also evident that a shift of dc bias potential would be amplified and passed along to the second amplifier, whereas in the ac coupled (resistance-capacitance) amplifier such a dc shift would be blocked by the coupling capacitor.

Note the use of complementary symmetry or the use of one transistor to bias another with dc coupling affords the minimum of component parts possible, and represents an economic advantage that is possible only with transistors.

Special bias circuits are used with dc amplifiers to reduce thermal effects; see bias stabilization previously discussed for the basic circuitry.

TIME CONSTANTS


In the previous paragraphs on coupling circuits, it has been shown that lumped inductance, capacitance, and resistance are used to couple together various electronic circuits. It has also been shown that these basic components are affected in various ways when responding to signals of different frequencies. Properly connected they can be used to shape, control, or distort signal waveforms. Since R-C and L-R combinations contain lumped capacitance or inductance,

they always require a finite time to charge or discharge, and thus provide a simple arithmetical figure (time constant) which is useful in the discussion of the operation and performance of these circuits.

R-C Circuits.


The time constant (TC) of an R-C circuit is defined as the time in seconds that is required to charge (or discharge) the R-C network to an arithmetical value of 63.2 percent. As normally used, it is defined as the time it takes the charge to reach 63.2 percent of the maximum charge, or to discharge 63.2 percent and to reach 36.8 percent of the initial (maximum) value. To obtain the time constant, the value of the resistance in ohms is multiplied by the value of the capacitor in farads (or megohms and microfarads); that is, $TC = R \times C$.

Consider now the action of a series R-C circuit when a voltage is applied. The capacitor charges heavily in an exponential manner, following the charging curve shown in the following illustration. At the end of a period of time equal to one time constant the voltage across the capacitor reaches 63.2% of the maximum value of voltage applied. If the charge is continued, at the end of the second time constant interval it rises 63.2% of the value remaining at the end of the first time constant (36.8%), to reach a new value of 86.4% maximum voltage (23.2% remaining). Thus at the end of five time constants the voltage has reached a value of 99.3% of maximum or almost full charge. Theoretically, the condition of complete charge (or discharge) will not be obtained but the difference is so infinitesimally small after five time constants that the remaining value can be neglected.

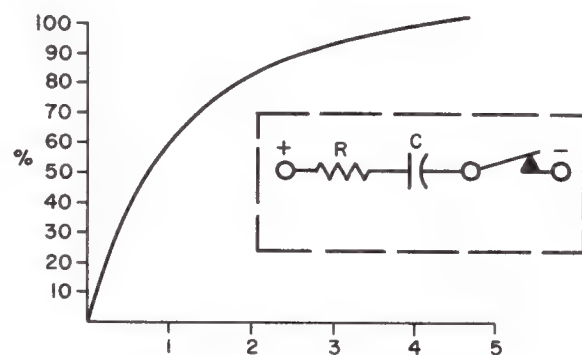

Capacitor Charging Curve

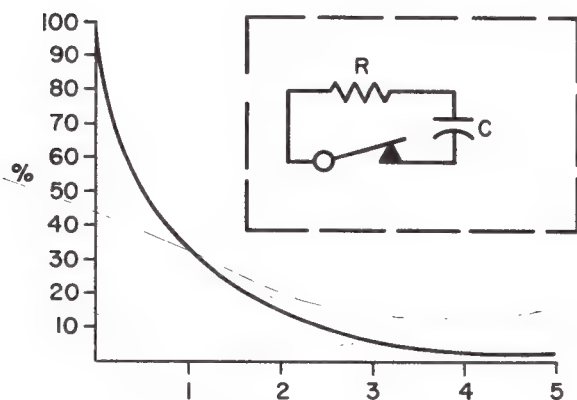When the capacitor is fully charged, if the applied voltage is removed and the capacitor is connected across the resistor, it begins to discharge through the resistor at an exponential rate. Discharge occurs as shown by the following curve. At the end of five time constant intervals of discharge the voltage across the capacitor is approximately zero.




Capacitor Discharge Curve

Comparing the illustrations showing the charge and discharge, it is evident that the curves are identical in shape, but that one is the reverse of the other. That is, while it takes one time constant interval to reach 63.2% of the applied voltage (or charge) with 36.8% to go, conversely, it also takes one time constant interval to reach 36.8% of the initial capacitor voltage (63.2% discharge). The vertical portion of each illustration represents the amount of voltage, current, or capacitor charge in percent.

A time constant interval may be considered short when the RC product is equal to, or less than, 1/10 of the period of the applied voltage. Likewise a time constant may be considered long when the RC product is equal to, or greater than, ten times the period of the applied (pulse) voltage.

Short time constant circuits are employed in differentiating circuits which change a square wave into positive and negative pips. Conversely, long time constant circuits are used to reproduce a square wave with fidelity, or to integrate (sum up) a series of pulses and change them into a single sawtooth, rectangular, or square wave. The following figure briefly illustrates

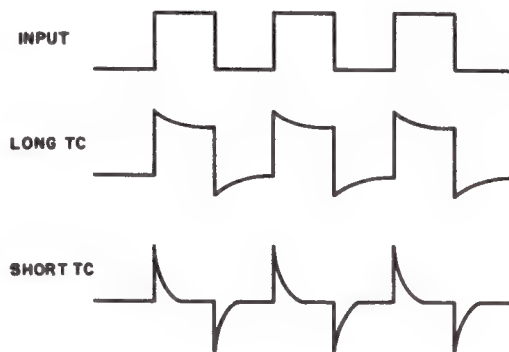the signal-shaping effects of long and short time constant circuits. For a complete discussion of the wave-shaping effect of the R-C circuit, refer to the Special Circuits section of this handbook.



Waveshaping Effects of RC Circuits

Time constants are sometimes used in audio coupling networks to define the low-frequency response. For example, the frequency at which the response of a single resistance-coupled stage falls 3 dB (theoretical cutoff frequency) is:

$$f_o = \frac{1}{2\pi RC}$$

Therefore, if the time constant of a network is 3000 microseconds, the low-frequency response limit of the network is found as follows:

$$f_o = \frac{1}{2\pi 3000 \times 10^{-6}}$$


Time constant is also related to frequency by the formula

$$F = \frac{1}{TC}$$

where F is in Hertz, and TC is in seconds. Thus a time constant of .01 second corresponds to a frequency of 100 Hertz. Since TC equals R times C, this time constant could be produced by a 0.01- μ f capacitor and a 1-megohm resistor (or 0.1 μ f and 100K).

R-C circuits are also used as decoupling networks, feedback networks, and high- and low-pass filters. The

figure following shows a few basic R-C circuit arrangements which illustrate possible combinations.

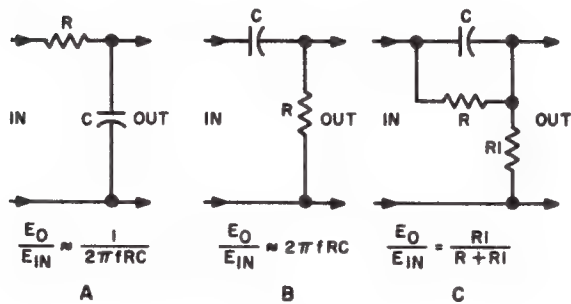

R-C Circuits

Part A of the figure illustrates a typical low-pass filter arrangement, where the low frequencies are passed without attenuation, but the higher frequencies are attenuated. Input and output relationships are shown by the formula, and for a specific time constant vary directly as the capacitive reactance. Part B shows a typical high-pass circuit which passes the higher frequencies and attenuates the low frequencies. Here the attenuation increases with a decrease of frequency, with greater output for the higher frequencies. Part C shows a parallel R-C network which is inserted in series with the coupled stages; it functions to bypass the higher frequencies across the resistor, with R and RI acting as a voltage divider at the lower frequencies.

Since most electron tube elements are biased through a series resistor bypass by a capacitor, it is evident that quite a number of time constant circuits exist in any circuit configuration. The effect that the time constant has with regard to frequency response and time delay becomes an important factor in the design of pulse circuits. See the Filter Circuits Section and the Special Circuits Section of this handbook for a complete discussion of these factors.


R-L Circuits.

The time constant (in seconds) of a circuit containing an inductor and a resistor connected in series can be found by dividing L (henrys) by R (ohms),

$$TC = \frac{L}{R}$$


If a dc voltage is applied to a series L-R circuit, the output current does not rise instantaneously to a maximum value at the instant the voltage is applied.

The rise of current is slowed down because the inductance produces a self-induced counter voltage which opposes the applied voltage, causing the inductance to oppose any change in current flow. Thus, current flow begins at a zero rate and increases exponentially as the self-induced counter emf decreases. When a voltage is applied to an R-L circuit, the voltage across the inductor declines as shown in the following illustration.

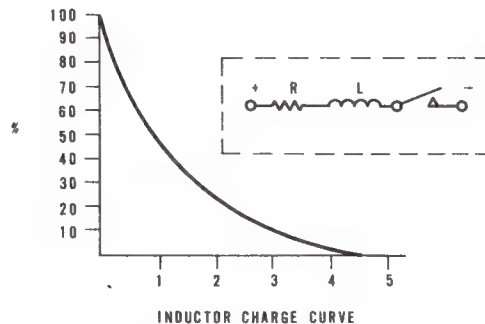

Inductor Charge Curve

At the end of five L/R time intervals, the counter voltage across L drops to approximately zero volts. During the same time interval the voltage drop across R, which results from the current flow in the circuit, begins at zero volts and increases at an exponential rate until, at the end of five time constant intervals, the voltage across R nearly equals the applied voltage (similar to inductor discharge curve illustrated.)

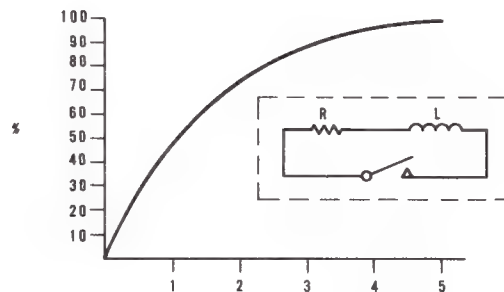


Inductor Discharge Curve

When the applied voltage is removed, the inductor again opposes the change in current flow by attempting to keep the current flowing. The counter

emf now produced causes the current to decrease at an exponential rate. The voltage across R (and across the inductance) during the decay period, shown in the inductor change curve, drops to approximately zero volts at the end of five time constant intervals.

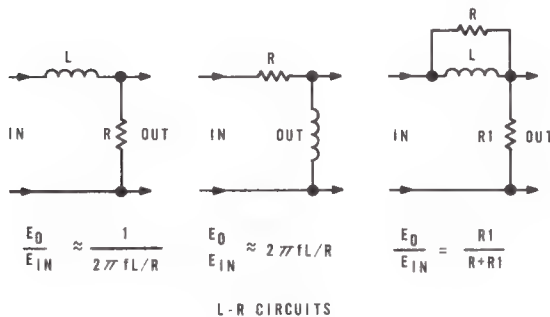
The following figure shows the circuit for basic L-R networks. Operation is identical for the comparable types of R-C networks, previously described.



L-R Circuits

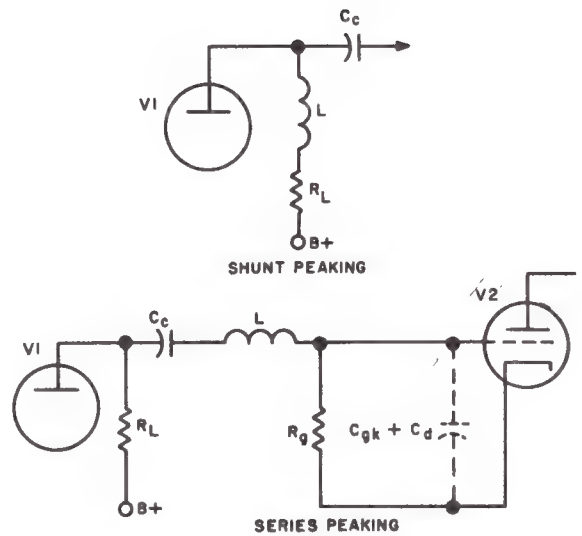Part A of the figure illustrates a typical low-pass filter arrangement. Since the reactance of L increases directly with frequency, the higher frequencies are attenuated and the lower frequencies are passed. Part B shows a typical high-pass circuit, which develops a larger voltage across the inductive reactance at the higher frequencies than at the lower frequencies. In part C the inductor acts as a variable shunt for R at the lower frequencies and as a voltage divider with R1 at the higher frequencies.

Since the inductor has distributed (turns) capacitance across it, undesired resonant responses may occur in L-R circuits containing large values of inductance; therefore, the use of these networks is usually limited to high-frequency applications. A practical application in resistance-coupled circuits is the insertion of a small inductance in series with the plate resistor or in series with the grid coupling capacitor to improve video response. These circuits are called shunt and series peaking circuits, respectively, and are illustrated in the following figure.



Shunt and Series Peaking Circuits

In the shunt peaking circuit, the increased inductive reactance at the higher video frequencies produces an effectively higher load impedance and larger output signal for coupling to the next stage. When the peaking inductance value is selected to resonate with the shunt capacitance to ground of the electron tube, a parallel resonant circuit is obtained which also boosts amplification at and around the resonant frequency. The series peaking inductance is usually selected to produce a series resonant circuit with the grid-to-ground tube and circuit capacitance. By combining both shunt and series peaking in a stage, greater high-frequency response is obtained. Excessive compensation, however, may cause unwanted transient responses. See discussion of Video Amplifiers in another part of this section of the handbook for a more complete discussion of peaking circuits.

SPECIAL CONSIDERATIONS FOR TRANSISTOR CIRCUITS.

The time constant as defined for electron tubes is the same for transistors. It is important to realize that transistors differ primarily from electron tubes in their input and output resistances and their capacitances. Where time constants are used in the grid

circuit of an electron tube with essentially infinite input impedance, it is not necessary to be concerned with the input-impedance effect on the time constant. Since the transistor has a finite and relatively low input impedance, however, it may affect a time-constant circuit. Also, the capacitance to base of the transistor is usually larger than the electron tube plate-to-ground or grid capacitance; hence, when it shunts the time-constant circuit, it must be considered.

Thus it can be seen that R-C and L-R circuits used for time-delay, coupling, and frequency-response effects and for the shaping of pulses and the controlling of switching circuits are practically interchangeable (except for shunting effects) between electron-tube circuits and transistor circuits.

Transient conditions which produce large overshoots must be avoided in transistor circuits because the transistor is more easily damaged than the electron tube by potentials which exceed the maximum rated voltages. Generally speaking, therefore, the R-L circuit is used less than the R-C circuit.

On the other hand, because of the shunting effects of the internal transistor parameters, the high-frequency response is degraded, even in the audio range. Consequently, when high frequency response is desired, more high-frequency compensating circuits are used with the transistor than with the electron tube. Therefore, the use of time-constant circuitry will be completely discussed in the applicable circuit analysis in other sections of this handbook, since it depends primarily on the type of transistor selected.

PART 5-1. DC AMPLIFIERS

DIRECT-COUPLED (DC) AMPLIFIER (ELECTRON TUBE)

Application

The direct-coupled amplifier, commonly known as the *dc amplifier*, is used where it is necessary to amplify extremely low-frequency signals extending down to, and including zero frequency (direct current). The most common application of the dc amplifier is in the dc vacuum-tube voltmeter. This amplifier also finds use in a balanced bridge circuit, where two dc voltages are to be compared, and the difference between them is to be indicated on a meter. Another important application is in the signal input amplifier of an oscilloscope which is designed to accept low-frequency or direct-current inputs for waveform display. Other uses of a direct-coupled amplifier are: to isolate two dc circuits while allowing a transfer of signal from the first circuit to the second but not in the reverse direction; to add two or more dc voltages to produce a dc output proportional to their sum multiplied by a constant factor; and to reverse the polarity of a dc voltage while either keeping its numerical value unchanged or increasing its numerical value by a constant factor.

Characteristics.

The connection between the output (plate) of one stage and the input (grid) of the dc amplifier is a direct metallic connection, without the use of any intervening coupling device such as a capacitor, impedance, or transformer.

Amplification of very low frequencies, or very slow variations of voltage, is accomplished without distortion and with uniform response.

Speed of response is practically instantaneous; pulse signals may be amplified without any distortion due to differentiation.

Input impedance is high; no grid current flows.

Output impedance is very low; can be made as low as one or two ohms.

Polarity (phase) of output signal is reversed by a single stage, or odd number of stages, of amplification. An inphase output signal may be obtained by use of an even number of stages.


Circuit Analysis.

General. In most vacuum-tube amplifier circuits, the coupling device used between the output (plate) circuit of the preceding stage and the input (grid) circuit of the amplifier stage allows only the alternating components of the output signal to pass through. At the same time, the coupling device serves to isolate the highly positive voltage, which often has a value of several hundred volts, at the plate of the preceding stage, from the low signal bias voltage at the grid of the amplifier stage. In resistance-capacitance-coupled and impedance-coupled amplifier circuits, the coupling capacitor prevents the plate supply voltage from being applied to the grid of the succeeding stage. In transformer-coupled amplifier circuits, the electrical isolation between the primary and secondary windings prevents the plate supply voltage, which is present in the primary winding, from being applied to the grid circuit, which includes the secondary winding.

In the direct-coupled (or dc) amplifier, the output (plate) of the preceding stage is connected *directly* to the input grid of the amplifier, without the use of any intervening means of coupling such as a transformer or capacitor. This requires a more complex method of supplying the required voltages to the amplifier tubes, since the plate of each tube must be supplied a positive voltage with respect to its cathode, and the grid of the following tube must be supplied a negative bias voltage with respect to its cathode; this grid, of course, is already supplied with the positive plate potential of the preceding plate through a direct connection. A special voltage-divider network is therefore required to supply the various values of bias and plate voltage for each amplifier stage.

Circuit Operation. A typical dc amplifier circuit is shown in the following illustration. In this circuit, the input signal is applied, across grid resistor R1, directly to the grid of the first section of twin-triode tube V1, which is used as a two-stage triode amplifier. The grid resistor is returned to the most negative point on voltage divider R4, designated as point a. The cathode is connected to point b on R4, which establishes the proper grid bias for operation of V1A, since point a is more negative than point b. The exact location of point b on voltage divider R4 is somewhat critical, since the terminal voltage at point b depends upon

the values of current flowing at each of the voltage divider taps b, c, and d, as well as upon the applied voltage, E_{bb} . Plate voltage is taken from tap d on R4, and applied through plate load resistor R2 to the plate of V1A. Plate load resistor R2 also serves as the grid resistor for the second amplifier stage, V1B, and the plate current flowing through the resistor establishes the grid voltage of V1B at the value existing at point d less the voltage drop across resistor R2. The location of point d on the voltage divider is such that approximately one half of the total power supply voltage, E_{bb} , is applied to the first amplifier stage, V1A.

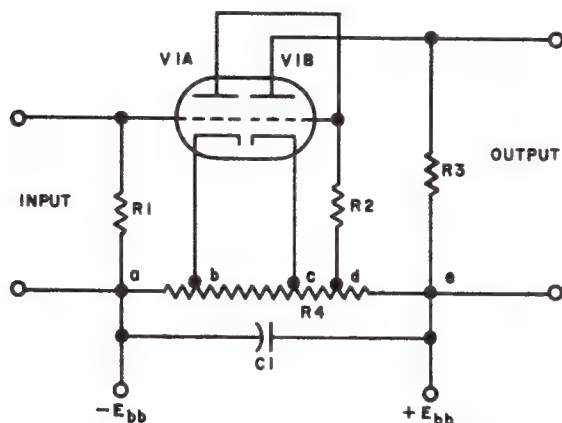


Two-Stage Direct-Coupled Amplifier Circuit

The cathode of the second amplifier stage, V1B, is connected to the voltage divider at point c, where the voltage is more positive than the voltage at the grid of V1B by the amount of the desired grid bias. (The voltage at point c is more positive than that at the grid of V1B because of the voltage drop through resistor R2.) The plate of the second stage furnishes the output of the amplifier, which is taken across plate resistor R3 by direct connection, without the use of any intermediate means of coupling. Resistor R3 is connected to the high side of voltage divider R4 at point e, and capacitor C1 acts to smooth out any ripple from the power supply. The entire circuit comprises a resistance network which, because of its complexity, requires careful adjustment at the voltage-divider taps, in order to obtain the proper grid and

plate voltages for both tubes. When these voltages are properly adjusted to obtain Class A operation, the circuit acts as a distortionless amplifier, having a uniform frequency response over a wide range, and a response time which is practically instantaneous.

Assuming that the voltages have been adjusted for Class A operation, the normal voltage conditions of the circuit with no signal applied to the input are shown in part a of the following illustration. The fixed value of grid bias, from the power supply, is indicated as a negative voltage, and the no-signal output voltage is indicated as a positive voltage. This is the value of voltage drop across plate resistor R2, resulting from the plate current-flowing under no-input-signal conditions. At time b of the illustration, a negative input signal voltage of fixed value has been applied to the grid. The negative input voltage adds to the fixed value of grid bias voltage, which is also negative, to make a new value of grid bias, shown by the lower solid line at time b. This more negative grid voltage causes less current to flow in the plate circuit through plate resistor R2, producing a higher voltage at the plate, as indicated by the upper (output voltage) solid line at time b of the illustration.

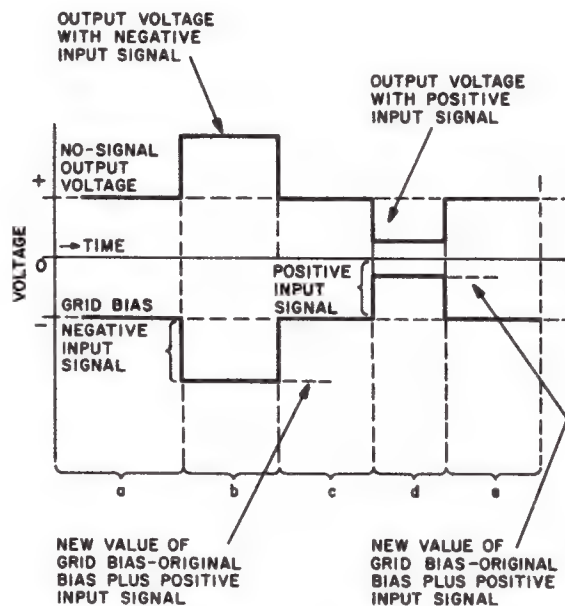


DC Amplifier Input-Output Voltage Characteristics
(For a Single Stage)

At time c the input signal has been removed, and the grid bias and output voltage values have returned to the levels shown at time a. At time d a positive input signal voltage has been applied to the grid of V1. The positive input voltage subtracts from the (negative) fixed value of grid bias voltage, to produce a new value of grid bias which is less negative, as shown by the lower solid line at time d of the illustration, close to the zero voltage bias level (if the positive input voltage is too high the grid will be drawn into the positive region, grid current will flow, and the output signal will be distorted. Under such conditions, the amplifier will not operate within Class A limits.) As a result of this less negative bias voltage, a greater current is caused to flow in the plate circuit, through plate resistor R2, and a lower voltage is produced at the plate, as indicated by the upper (output voltage) solid line at time d of the illustration. At time e the voltages have returned to their original values, following the removal of the input signal.

For purposes of explanation, the discussion of the effects of the input signal and the output voltage has referred to only one stage (V1A) of the two-stage direct-coupled amplifier circuit illustrated. The operation of the second stage (V1B) is identical. It should be noted that the signal at the output of the first stage is reversed in phase by 180 degrees. This is evident from the illustration of the input-output characteristics, where the negative input signal produced a positive output signal. An additional 180-degree phase reversal is produced by the second stage, giving an output signal from the two-stage amplifier circuit which is in phase with the input signal.

A very practical application of the dc amplifier circuit is found in its use as a dc vacuum-tube voltmeter. This circuit, utilizing a single triode, is shown in the following illustration. The voltage to be measured is applied, through a range switch, SW1, to a tapped voltage divider which allows several ranges of voltage to be measured. The voltage divider is composed of several resistors, R1 through R4, with R4 also serving as the grid resistor for the triode dc amplifier, V1. Plate load resistor R5, having a value of 22K or higher, acts as a current-limiting resistor to protect the meter in the event of excessive input voltages. Variable resistor R6 functions as a balance control to allow the voltmeter to indicate zero volts with no applied input voltage. Voltage divider R8, connected across the input voltage from the power sup-

ply, is tapped to provide the proper grid bias and voltmeter balance voltages. When variable resistor R6 is adjusted for a zero voltmeter indication with no input signal, the voltage at point c on voltage divider R8 is exactly equal to the voltage at the junction of R5 and R6. Now when an input signal is applied, additional plate current flows through R5, R6, and R7, causing the voltage at the junction of R5 and R6 to drop to a lower value, while the voltage at point c on voltage divider R8 remains relatively constant. When properly calibrated, the meter indicates this voltage drop as the applied input voltage.

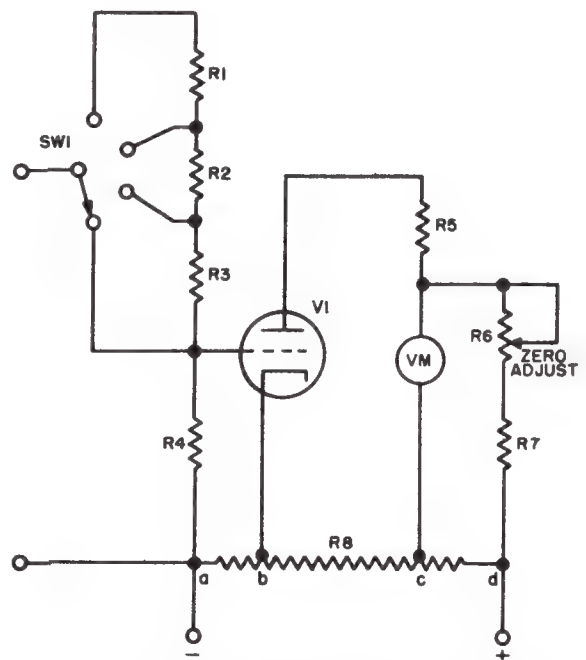

Vacuum-Tube Voltmeter Utilizing Direct-Coupled Amplifier Circuit

A disadvantage of this direct-coupled vacuum-tube voltmeter circuit lies in its poor stability of calibration. The plate current of the tube varies in a somewhat unpredictable manner with variations in filament temperature, age of the tube, and variations in resistance of the coupling element with temperature variations. These variations are especially evident when an attempt is made to read small voltages accurately.

Failure Analysis.

No Output. Assuming that a signal whose amplitude (either positive, negative, or a combination thereof) is within the design limits of the dc amplifier, is applied to the input terminals, the primary cause of no output is a defective tube. If the tube is capable of satisfactory operation, the cause of a no output condition is obviously an incorrect voltage, or lack of voltage, at some point in the circuit. Referring to the first illustration (two-stage direct-coupled amplifier circuit), an open voltage divider R4 would cause one or more of the voltage taps to fail to supply the required voltage to either the cathodes of V1A or V1B or the plate of V1A. As a result, either V1A or V1B would fail to operate. An open resistor R2 would remove plate voltage from V1A, resulting in no output; a similar condition would occur if plate load resistor R3 opened, removing plate voltage from V1B.

Reduced or Unstable Output. Assuming that a satisfactory signal is present at the input to the direct-coupled amplifier, an open grid resistor R1 would cause unstable output, along with intermittent grid blocking, or "motor-boating." A change in the supply potentials for any tube in a multi-stage dc amplifier would cause the currents and potentials of all succeeding stages to vary. If, for example, the grid potential of the first tube varies slightly, the gain of the amplifier will cause the current in the last tube to vary by a large amount, even to the point of decreasing to zero, or of increasing to an excessively high value. In either case, distortion will be introduced. A changed value of R4 (or portions of R4), or of plate resistors R2 and R3 would all have the effect of changing the supply potentials of the tubes. The amount of unbalance created, and, consequently, the amount of output distortion, will depend on whether the gain of one or both stages is involved in amplifying the unbalance. An open or partially shorted filter capacitor C1, if used, may cause hum or reduced output because of inadequate filtering of the input power, $+E_{bb}$. A decreased value of input power, $+E_{bb}$, due to a defective power supply, would also be a cause of reduced output.

**DIRECT COUPLED (DC) AMPLIFIER
(SEMICONDUCTOR)****Application.**

The direct-coupled amplifier is used where high gain at low frequencies, or amplification of direct current (zero frequency) is desired. The direct-coupled amplifier is also used where it is desired to eliminate loss of frequencies through a coupling network. This circuit has numerous applications, particularly in computers, measuring or test instruments, and industrial control equipment.

Characteristics.

Uses common-emitter circuit for high gain.

Usually requires thermal stabilization to prevent runaway.

Frequency response extends to zero frequency (direct current).

Responds equally well to pulses or sine waveforms.

Circuit Analysis.

General. The transistor is a device which uses the change of current flow through a resistor to produce amplifying action. DC bias potentials are applied to the transistor elements to fix the point of operation. In ac-coupled amplifiers, the dc biasing potentials are effectively isolated and remain unaffected by the operating signal. In dc coupled amplifiers, however, a change in voltage on one element (either ac or dc) appears also as a similar or amplified change on another element, so that the biasing point changes with the signal. In cascaded stages these changes are cumulative and thus present a problem in stability. Since transistors are also subject to thermal changes, it is evident that a thermal change appearing at one element is also applied to another element. No problem results if the circuit can be arranged so that the temperature increase or decrease is self-correcting in the following transistor. In most instances, however, thermal instability becomes a major problem if more than two stages of dc amplification are cascaded.

Germanium transistors are more subject to thermal instability than are silicon transistors, but in either case it is usually necessary to provide some form of temperature compensation if the temperature exceeds 55 degrees centigrade. The complexity of the compensation circuitry is dependent upon the amount of correction needed. Because of the rapid changes which are occurring in the semiconductor field, it is likely that temperature compensation will be eliminated or minimized to a great degree in the future. Even so, however, the primary limitation of direct coupling still remains, namely, the necessity for cumulatively increasing the bias and operating values as each stage is cascaded. While the use of low bias and collector voltage permits somewhat more range than can be obtained with the electron tube, the transistor, like the electron tube, is subject to maximum breakdown or reverse potential limitations.


In addition, noise is a problem since the dc amplifier amplifies any internal noise as well as the signal, and transistors are prone to produce greater noise at the lower frequencies. Thus, the ability of the dc amplifier to extend its response to low frequencies not normally available through other coupling methods is somewhat nullified by the amplification of the inherent noise in the transistor. Generally speaking, we can say the low-frequency response of the dc amplifier is limited only by the signal-to-noise ratio, while the high-frequency response is limited by the frequency-response characteristics of the transistor.

In the direct-coupled amplifier, the collector of the input stage is directly connected to the base of the second amplifier stage; therefore, any collector supply variation also appears at the base of the second stage, just as if it were a change in the input signal. Since the transistor in the second stage has no way of discriminating between actual input signal variation and first stage collector supply variation, it is evident that either type of variation will be amplified in the second stage.

By the same type of reasoning it can also be seen that, even in the absence of an input signal, a change in the gain of one stage (or the over-all gain of cascaded stages) as a result of collector supply variations, will produce an output signal. Similarly, a change in bias level in any stage or on any element will be amplified proportionally, and a change of output will occur. Such changes in bias levels normally occur as a result of temperature variations, aging, difference in

transistor characteristic due to manufacturing processes, or changes in transistor leakage current, and are referred to as *drift*. (This has no connection with the process which occurs in drift transistors.)

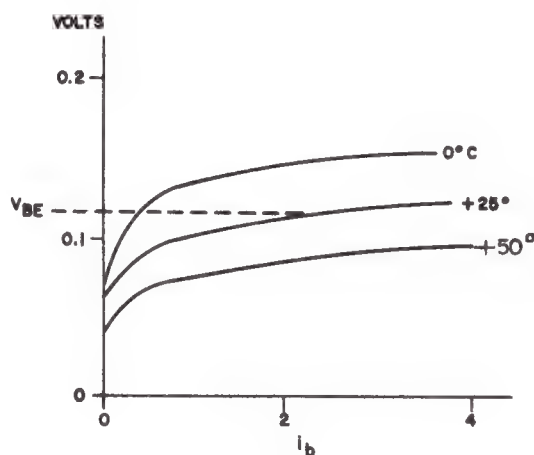The variation of the forward bias characteristics of a typical germanium diode with temperature is shown in the accompanying graph. The forward bias variation is usually expressed as a change in bias voltage with temperature at a constant forward bias current. It is usually small, but becomes significant because of the large amplification it receives because of the direct coupling arrangement.




Emitter-Base Diode Characteristic

The manner in which the collector-base diode varies its reverse saturation current with temperature is also shown in the following graph (for a typical germanium transistor). In this instance, the figure shows that the reverse-current characteristic is highly temperature-dependent, and relatively large current variations are produced as the temperature is increased.

In a similar manner, it can be shown that the forward-current transfer characteristic of a germanium transistor also varies with temperature. However, in this case the gain can either increase or decrease with temperature (silicon types generally increase with temperature). The percentage variation in gain with temperature varies greatly with the operating point, and many units show a change in sign as

well as magnitude. The gain variation of a silicon type may be from two to ten times that of a germanium type. Thus, we can see that the major sources of drift in transistors are changes in the dc properties of the collector-base and emitter-base diodes, and changes in the dc forward transfer ratio. Generally speaking, in comparing the operation and performance of germanium and silicon transistors, it can be said that at temperatures below that of the reference temperature, T_0 , the two types are comparable. At and above the reference temperature, the silicon type tends to have lower drift. The reference temperature for silicon is 100 degrees centigrade, and that for germanium is 60 degrees centigrade. With low source resistance low values of drift are obtained above T_0 , while with high source resistance the best performance occurs at temperatures where the reverse saturation collector current may be neglected.

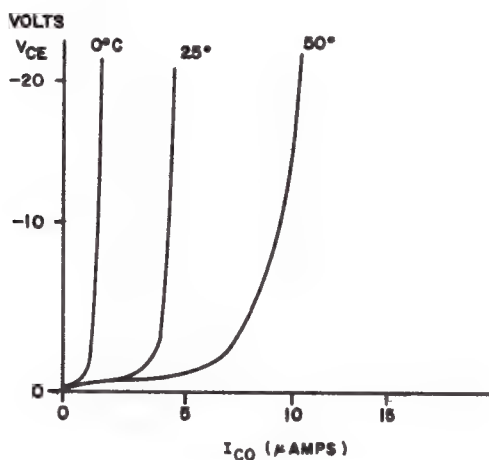

Variation of Collector-Base Diode
Reverse Current

In dc amplifiers, low drift is obtained by operating with low values of collector current; this reduces the reverse-leakage current by keeping the voltage between the collector and the base at a low value. This voltage is a forward bias for reverse current. Generally, any design precautions which reduce drift also reduce noise; conversely, with low noise less drift is obtained. When the collector current is reduced, the gain decreases and the internal emitter resistance increases. Because of the reduction of gain, the amount to which the collector current of the first stage can be


reduced is somewhat limited. In single-ended amplifier stages, both the current drift and the voltage drift in the second stage tend to help cancel the input stage drift; in a differential dc amplifier, however, the drift in the second stage may either aid or oppose that of stage 1, depending upon the design.

Despite the apparent disadvantages of the dc amplifier, it does produce (for a two- or three-stage unit) high gain the good fidelity, particularly in the low-frequency portion of the spectrum. It also provides amplification with as few parts as possible; thus, it is economical to build. In actual practice the dc amplifier is usually limited to one or two stages of amplification because of drift, especially where dc must be amplified or where frequencies of 0 to 12 Hertz are of importance. To overcome the effects of drift in dc amplifiers a special "chopper amplifier" has been developed; this amplifier converts the dc into ac so that the stages can be isolated and thus prevent the cumulative drift which normally occurs. This is a special type of amplifier, which will be discussed later in this section of the Handbook.

Circuit Operation — Basic Circuit. The schematic of a basic common-emitter dc amplifier is shown in the accompanying illustration. The input signal is represented by the a-f generator with an internal resistance equal to R_G . The input signal is applied between base and emitter. Transistor Q1 is biased by R_B , using the form of external PNP self-bias explained in the introduction to this section of the handbook. (R_B and the internal resistance of the base-emitter junction form a voltage divider across the collector supply, and a forward bias is developed across R_B .) The input signal opposes the bias between base and emitter, which is normally chosen for class A operation. The direction of electron current flow through the collector output load resistor, R_L , is indicated by the arrows. The polarity of the resulting dc voltage across the load resistor is as shown. When the positive alternation of the input signal is applied to the base, the base-to-emitter bias is reduced (since the signal and bias voltages are of opposite polarity). Because the base-to-emitter potential is now less than the normal value, the hole current from the emitter to the collector is lowered and electron flow through the output load resistor is reduced. The decrease in voltage drop across R_L produces a negative swing and, consequently, produces a negative output signal across R_L . As the sine-wave input signal goes negative, the bias potential is


aided by the input signal; and as the base-to-emitter bias is increased, more hole current flows to the collector. This produces more electron flow through the collector circuit, increasing the voltage drop across R_L , and produces a positive output signal swing during the time that the input signal is negative. This effectively produces an opposite-polarity output signal (sometimes referred to as a 180-degree phase reversal). Since R_L is the load for both dc and ac, there is only one load line, and any internal noise voltages flowing through the load resistor add to the developed output voltage. Since the output across R_L is applied directly to the base of the next stage, it can be seen that these noise components appear across the following input circuit. In an ac-coupled circuit these noise components, consisting of dc or very low frequencies, are usually eliminated (blocked by the coupling capacitor). These noise components are produced by thermal effects, and also result from electron flow through the load resistor. They include the so-called *white noise* generated by diffusion-recombination effects within the transistor (similar to shot noise in the electron tube), and surface and leakage noise from the transistor, which is sometimes referred to as *semiconductor* or *1/f noise* to distinguish it from white noise. Such noise is mostly confined to the region of from 1-to-10 kHz for white noise (in the audio range), with the semiconductor noise predominating and increasing for frequencies lower than 1 kHz. The dc noise results from supply voltage variations. Thus the noise components usually eliminated by the ac coupling capacitor in other types of amplifiers, creates a design problem in the small-signal type of dc amplifier. In large-signal amplifiers these noises are usually masked by the large input signal. Note also that any dc bias changes caused by thermal instability of the stage also appear across the load, and are applied to the input of the next stage. This is an inherent disadvantage of the dc amplifier. On the other hand, with proper input and output matching, maximum gain is obtained in the stage; moreover, with no coupling network to create a loss between stages, maximum output and efficiency are produced. Since all frequencies are present, including dc (zero

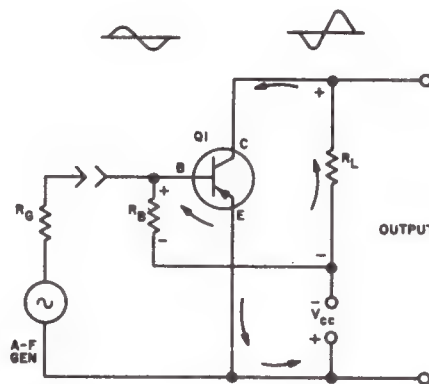frequency), and are applied equally to the next stage, it can be understood why the dc amplifier presents maximum gain with excellent frequency response, particularly at the lower frequencies.



Basic D-C Amplifier (CE)


Cascaded Stages. Because of the high gain possible per stage, many applications require only a single stage of dc-coupled amplification. Where more than one stage is required, transistors offer circuit arrangements that are not possible with electron tubes. For example, through the use of *complementary symmetry* it is possible to connect the collector of the input stage directly to the input of the second stage without disturbing bias arrangements, and to use the same supply. By using alternate arrangements of NPN and PNP transistors only one supply is needed. Recall that in the vacuum-tube dc amplifier, as each stage progresses the plate voltage is increased, with the grid being tapped back onto the preceding stage plate voltage to obtain the bias. Only tandem arrangements of similar type transistors can follow this principle. The term *complementary symmetry* is derived from the fact that the NPN transistor is the complement of the PNP transistor, with both circuits operating identically, but with opposite polarities. The accompanying figure shows a simple direct-coupling circuit using complementary symmetry.

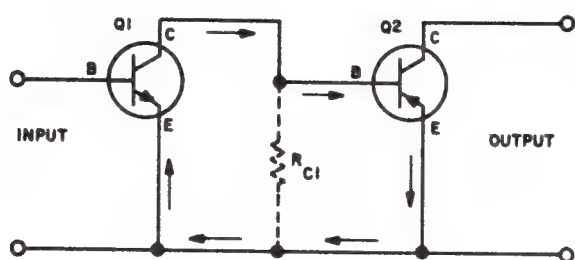

Tandem Coupling Arrangement

In this figure, the direction of electron flow is shown by the arrows. It is evident that the base-emitter junction of the second stage carries the collector current of the first stage. If the collector current of the first stage exceeds the maximum base-emitter current rating of the second stage, the collector resistor shown in dotted lines must be used. Otherwise, this resistor is not needed and proper design produces a saving in components. To do this, of course, the transistors must be of opposite types, (NPN to PNP, or PNP to NPN).

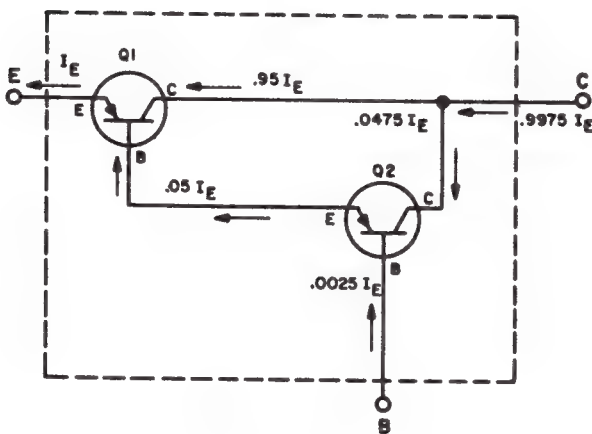
By the use of a special compounding connection, two transistors may be employed as a special type of dc amplifier to obtain linearity and almost unity gain (alpha). The accompanying figure shows the compound transistor connection using the common-base configuration.



Compound Connection

Note that the input to the second stage is the base current of the first stage. Effectively, the input impedance is the series combination of the two transistors, while the outputs are in parallel. Such a circuit is roughly analogous to the push-push electron-tube circuit. Actually, this circuit is employed as a single-transistor compounded-type circuit, with emitter, base, and collector resistors used externally. The direction and relative values of current flow are shown in the figure, assuming the use of two transistors with an equal a_{fb} of .95. When these values are converted to a_{fe} , the total combination value (.9975) is equal to a gain of 399 as compared with an a_{fe} of 19 for a single transistor, or more than the normal gain of two stages in cascade ($19 \times 19 = 381$). Compounded transistors may be employed single-ended, or in complementary symmetry as push-pull stages, exactly as for single transistors. They represent a special and unique circuit alone; however, they are shown here to illustrate how they are derived from the basic dc amplifier. In most applications the compounded circuits form the output stages of an amplifier, or are used as the dc amplifier in a voltage-regulator circuit. A typical high-gain preamplifier using an NPN and a PNP transistor in a direct-coupled, cascaded, complementary-symmetry amplifier is shown in the following schematic. For simplicity and convenience, separate bias and collector supplies are shown. The output of the microphone is transformer-coupled (for proper matching) to the base of transistor Q1. Fixed class A bias is supplied to the emitter from a separate supply, and emitter swamping is provided by R1 shunted by C1. Use of emitter swamping provides temperature stabilization for germanium transistors up to normal room temperatures, and for silicon transistors up to 100 degrees centigrade. The output of the first stage appears across collector resistor R2, and is direct-coupled to the base of PNP transistor Q2. Capacitor C2 and resistor R3 form a low-frequency compensating circuit (or filter) across the load, shunting the higher frequencies to ground and effectively boosting the lower frequencies. This helps to compensate for loss of low frequencies in the microphone and transformer circuits. Transistor Q2 is emitter-stabilized by swamping resistor R5, bypassed by C3. Resistor R4, which is unbypassed, is placed in series with the emitter to provide degenerative feedback for improvement of the linearity and response. Resistor R6 is the

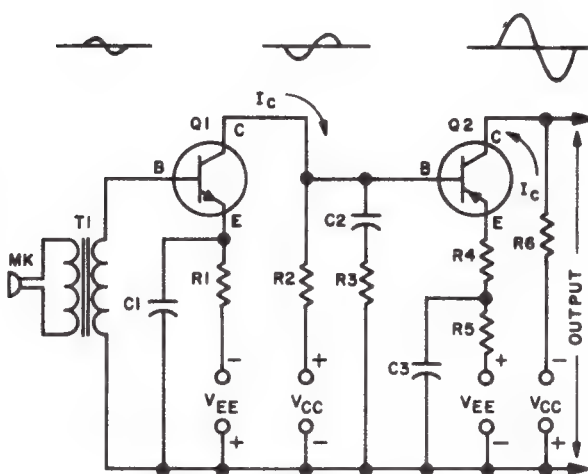collector load across which the output is developed. Fixed emitter bias is used with a separate collector supply for simplicity and convenience.



Two Stage DC Amplifier (CE)

Assume that a sine-wave signal is applied to the input of T1; as the signal increases in a positive direction it adds to the forward bias of NPN transistor Q1. The increased flow of electrons through Q1 increases the emitter, base, and collector currents, and the external electron flow out of the collector produces a negatively polarized voltage drop across collector load resistor R2. Thus, for the entire half-cycle that the input signal goes positive and aids the forward bias, the output signal (at the collector of Q1) goes negative.

As the input signal changes polarity and becomes negative, it opposes the forward bias, causing a decreased electron flow through the transistor, and a proportional reduction in the emitter, base, and collector currents. The voltage drop across R2 is reduced and the collector voltage approaches that of the source, so that a positively polarized output is produced. Thus, for the entire half-cycle that the input signal goes negative and opposes the forward bias, the output signal (at the collector of Q1) goes positive.

Since emitter resistor R1 is bypassed by C1, changes occurring during the audio cycle will have no effect. However, any slight changes in emitter current (produced by temperature variations in the transistor)

which occur at a very slow rate develop a voltage across R1; this voltage increases or decreases the bias in a direction which opposes the change; see the introduction to this section of the handbook for an explanation of bias stabilization. Any noise voltage, thermal bias changes not compensated for by R1, and the amplified signal appear across collector resistor R2, and are applied directly to the base of Q2. Note that the signal at this point is opposite in polarity to that of the input stage. Capacitor C2 and resistor R3 form a high pass filter between the base and emitter of Q2, which shunts the high frequencies to ground; this effectively boosts the base response of the amplifier and compensates for any loss of low frequencies in the input transformer.

Transistor Q2 is a PNP type; the function of Q2 is just the opposite of the function of Q1. When the input to Q2 is positive, it opposes the fixed emitter bias and effectively reduces the forward bias. With reduced forward bias, the flow of hole current through the transistor is decreased, and the emitter, base, and collector currents are reduced proportionally. Therefore, the external flow of electron current through collector resistor R6 is reduced, and the collector voltage approaches that of the source, producing a negatively polarized output signal. The output is now of the same polarity as the input signal to transistor Q1, so that during the entire half-cycle that the input signal to Q1 is negative, the output of Q2 is negative.


When the input to Q2 is negative, the polarity is such as to aid the base-emitter bias and increase the effective forward bias. As the forward bias is increased, hole current flow through the transistor increases, and the emitter, base, and collector currents increase proportionally. Thus, the external flow of electron current through R6 into the collector of Q2 is increased, and is in such a direction as to produce a positive output voltage. In a similar manner, this output voltage (of Q2) is of the same polarity as that at the input of Q1; thus, the effect of the two stages is to produce an output signal of the same polarity as the input signal (a similar effect is obtained when two electron tubes are used). To provide an oppositely polarized output signal, the stages must be an odd number.

Swamping resistor R5 is bypassed by C3, so that the audio-frequency changes will have no effect; however, slow thermal variations will produce a voltage

across R5 in the proper direction to compensate for the thermal change, thus helping to stabilize the circuit.

Resistor R4, which is unbypassed, has a voltage developed across it for dc changes, noise changes, and audio frequency changes; since this voltage is in opposition to the bias produced by R5, it is degenerative, thus providing a form of negative feedback. The negative feedback improves the low-frequency response and stabilizes the stage so that input voltage variations are minimized. The amplified output of Q2 is either applied directly to a speaker or other output device, or transformer-coupled to other stages as desired.

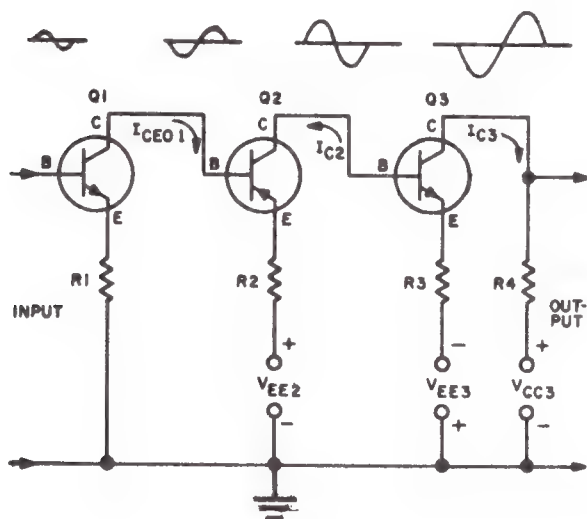A typical three-stage, single-ended dc amplifier is shown in the accompanying schematic. It represents the minimum of parts and dc supplies needed for a high-gain, three stage complementary symmetry type of dc amplifier for small signal applications.



Typical Three-Stage Amplifier

As shown, the base of the input stage is completed through the input device, it is effectively open, it has no driving voltage, and zero base current exists. The collector current, I_{CEO1} , flows through the base of stage 2, which is biased by supply V_{EE2} in series with the emitter of stage 2. Since stage 1 uses an NPN transistor, the positive emitter bias of stage 2 is of the proper polarity to act as collector voltage for Q1.

Any change in the collector current of stage 1 appears at the collector of stage 2 in amplified form; that is, $I_{C2} = B_2 I_{CEO1}$, where B_2 is the current gain of stage 2. Stage 2 uses a PNP transistor; therefore, by complementary symmetry, stage 3 must also be an NPN stage similar to stage 1. The emitter bias for stage 3 is supplied through V_{EE3} , which is connected positive to ground. Thus, the collector supply of stage 3 (V_{CC3}) is of series-aiding polarity, and the total collector voltage is that of both the collector and emitter supplies of stage 3. In a similar manner, the collector voltage of stage 2 is supplied by V_{EE2} and V_{EE3} . The collector current of stage 2 is the base current of stage 3. The output of the amplifier appears across collector resistor R4, and the collector current is that of stage 2 multiplied by the amplification factor, or $I_{C3} = B_2 B_3 I_{CEO1}$. Emitter resistor R1, R2, and R3, which are of a low value, provide degenerative feedback; they also act as emitter swamping resistors to help stabilize the amplifier with respect to temperature variations.

Assuming that the input stage has a collector current of 5 microamperes and assuming a gain of 38, the second stage will have a collector current of 190 microamperes. With a gain of 40, the third stage collector current will be 7.6 milliamperes. It is clear that any slight change in the current of stage 1 caused by temperature or noise will be greatly amplified and appear at the output of stage 3. With such sensitivity and amplification, therefore, it is almost mandatory that such an amplifier be temperature-compensated, even if room temperatures do not vary excessively. Naturally, the amplitude of the input signal must be limited if true fidelity is to be obtained. Driving the transistor into cutoff and saturation would clip the peaks of the signal, just as in electron tube operation. It is also evident that low-noise transistors must be used; otherwise, the noise might mask the signal. Note that in this amplifier the small emitter bias of stage 2 operates as the collector voltage of stage 1. Low collector voltage is used to minimize noise generated in the input stage; this is similar to the techniques used for high-gain vacuum-tube amplifiers, where the plate voltage of the input stage is usually about 1/3 that of the other stages.

Failure Analysis

No Output. A no-output condition is generally indicative of either an open or shorted circuit, or a defective transistor. Usually, improper bias will cause

distortion or low output rather than no output at all. A resistance analysis should quickly reveal any open-circuited components, since only a few parts are involved. A forward and reverse resistance check of the transistor can be made to determine whether the transistor needs replacement. For a good transistor the forward resistance is low (less than a few ohms), and the reverse resistance is high (50K and higher.) With continuity throughout and components of the proper resistance, a simple voltage check should indicate the cause of improper performance. Use a high-impedance vacuum-tube voltmeter; at the normally low voltages involved, the shunting effect of the usual 20,000 ohms-per-volt meter might be too great.

Low Output. Generally, low output results from improper biasing, causing either too great a flow of current or too small a flow of current (but not cutoff). Defective bypass capacitors provide a leakage path for current which, in flowing through an associated series resistor, produces a voltage drop greater than normal. Usually such a condition can be easily checked by means of a voltage analysis. Where high-resistance paths have been introduced, either because of poorly soldered joints or aging components, a loss of output will usually occur. Ordinarily, these paths can be located by means of a resistance analysis. With the small number of components involved, either a voltage check or a resistance check should quickly isolate the trouble to a particular portion of the circuit. When making ohmmeter tests, be sure to observe the correct polarity and not to apply a forward bias to a circuit requiring a reverse bias or vice versa; exceeding the permissible bias can ruin the transistor. The use of a shorting bar (screwdriver) to ground should be avoided to prevent overload or accidental short-circuiting of the supply through components not designed to withstand the extra current. If the trouble cannot be located quickly by means of the simple voltage and resistance checks described above, the most effective trouble-shooting method is to apply an input signal and use an oscilloscope to check the signal path through the circuit. The high-impedance oscilloscope input will have little effect on circuit operation, and the disappearance of the signal or a change in amplitude will be immediately apparent as the signal is followed from point to point.

Distorted Output. Distortion is usually caused by operating the circuit with improper bias or supply voltage or by overdriving. The bias voltage should be checked with a VTVM to determine that they are

approximately normal. Then a test signal should be applied to the input and followed from point to point with an oscilloscope. A change in waveshape caused by distortion will then be immediately apparent. Where the circuit appears normal but a high ambient temperature exists, it is possible that thermal effects are changing the circuit parameters. The use of a fan to temporarily cool the unit should quickly indicate whether a thermal problem exists. A condition often occurs whereby a thermal problem exists while the chassis is installed in the equipment cabinet, but disappears when the chassis is removed to the bench for checking. When this situation is indicated, it is sometimes possible to make sufficient checks with the chassis in the cabinet to isolate the trouble. Overdriving is apparent if a reduction of the input signal amplitude eliminates the distortion. Overdriving will appear on the oscilloscope as a squaring off of the input waveform, since the tops and bottoms of the modulation peaks will be clipped. Since nonlinearity in either the input or output circuits of the transistors will cause distortion, it should be clear that a small amount of distortion will always be present. Where the distortion is excessive and other tests indicate normal values of voltage and bias, it may be necessary to select a more linear transistor. (This condition should not occur if the components meet Military Standards except where an overload has caused damage to the transistor.)

PUSH-PULL DIRECT-COUPLED (DC) AMPLIFIER (ELECTRON TUBE)

Application.

The push-pull direct-coupled amplifier (as well as the single-ended direct-coupled amplifier) can be used where it is necessary to amplify signals having a wide band of frequencies, especially in the lower-frequency range, which may extend down to and include zero frequency (direct-current). When, in addition, the requirements demand the amplification of a signal which has a larger voltage swing above and below a zero voltage level than can be handled by the single-ended type, the use of the push-pull direct-coupled amplifier is mandatory. One application is in certain types of dc vacuum-type voltmeters, while another is in the signal amplifiers of an oscilloscope that is capable of displaying waveforms of various values of direct current. The push-pull dc amplifier is often utilized in the video circuitry of radar display systems.

In communications, it may be used as the amplifier for those teletype mark and space signals that consist of two voltage levels of direct current.

Characteristics.

The connections between the plates (outputs) of one stage and the grids (inputs) of the push-pull dc amplifier are direct, metallic connections; no intervening coupling devices such as capacitors, impedances, or transformers are used.

Amplification of direct-current signals of varying voltage levels, as well as signals of very low frequency, is realized without distortion and with uniform response.

Distortion due to differentiation is eliminated; pulse signals of large amplitude may be amplified without change in waveform.

Speed of response is practically instantaneous.

Input impedance is high; Class A operation allows no grid current to flow.

Relative phase (with respect to ground) of the output signal is reversed over that of the input signal when a single stage, or odd number of stages, is used.


Circuit Analysis.

General. The gain of an ordinary R-C coupled amplifier falls off rapidly as the frequency of the input signal is decreased below 40 Hz, because of the rapid increase in reactance of the coupling capacitor with a decrease in frequency. Therefore, the R-C amplifier is unsuitable for use in applications which require the amplification of very low frequencies, including zero frequency or direct current, without substantial loss of gain.

The push-pull direct-coupled amplifier is well suited for such applications, since the input signal is applied directly to the grids of two tubes, without the use of coupling capacitors. Frequency response is flat down to and including zero frequency, allowing the use of this circuit for amplification of steady-state dc voltages. The response at very high frequencies is limited by the stray capacitances in the circuit, which have a shunting effect, similar to that of the ordinary R-C coupled amplifier.

Circuit Operation. The accompanying schematic illustrates a typical two-stage push-pull direct-coupled (dc) amplifier. This type of circuit may be found in applications such as the deflection amplifiers of radar scopes designed for electrostatic deflection, and the

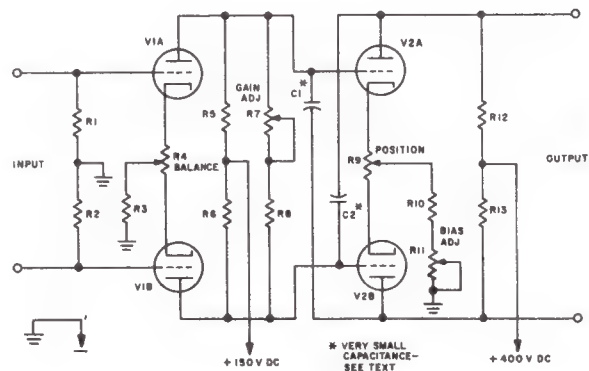signal amplifiers (vertical-deflection amplifiers) of high-quality test oscilloscopes designed for direct-current waveform analysis.



Typical Two-Stage Push-Pull Direct-Coupled (DC) Amplifier

The input signal, which may consist of positive or negative pulses, or both, or simply of a positive or negative dc level, is applied across the grids of **V1A** and **V1B**. These two triodes may be enclosed in the single envelope of a twin-triode such as type 12AU7A. Self-bias is provided both triodes by means of the common cathode resistor, **R3**, in combination with potentiometer **R4**, which provides a balance control for use in equalizing the gain of **V1A** and **V1B**. Plate voltage of a medium value (+150 volts) is applied through plate load resistors **R5** and **R6**. Variable resistor **R7** functions as a gain adjust control, and fixed resistor **R8** connected in series with it sets the low limit for the variable value of the total resistance between the two triode plates. This combination, **R7** and **R8**, affords a relatively simple means, from the standpoint of circuit components, of adjusting the over-all gain of the amplifier, and thereby the amount of vertical deflection in oscilloscope applications. Resistor **R8** should have a minimum resistance value on the order of 1.5K, in order to maintain this

minimum value of resistance as a plate-to-plate load when R7 is adjusted to its zero-resistance position. As R7 is adjusted from its maximum value, toward zero resistance, loading of the signal output from V1A and V1B is increased, reaching a minimum value when R7 is adjusted to remove its resistance from the circuit. The maximum positive and maximum negative excursions of the signal to be amplified may thereby be adjusted, while maintaining the over-all frequency response of the amplifier.


The amplified output signal from the plates of both triodes, V1A and V1B, is applied directly to the grids of the second stage triodes, V2A and V2B. Since the grids of the second stages are at the same positive potential as the plates of the first stage (some value less than +150 volts due to the voltage drop through R5 and R6), the cathodes of V2A and V2B must be placed at a somewhat greater potential than +150 volts (above ground), in order that the grids may be properly biased, i.e., negative with respect to cathodes. In this circuit, which utilizes self-bias, this is accomplished by the use of a large value of cathode resistance, composed of potentiometer R9 and resistors R10 and R11. Potentiometer R9 serves as a balance adjustment to equalize the gain in both halves of the second stage; in this application, it serves to "position" the waveform under observation on the oscilloscope screen. The bias on the cathodes is adjusted by means of variable resistor R11, while the total resistance of the combination R9, R10, and R11 establishes the total bias voltage at the cathodes of V2A and V2B. This relatively large value of cathode resistance, which amounts to approximately 12K, would introduce degeneration into the circuit, resulting in a decrease in gain, if this were an unbalanced (single-ended) stage. In this (push-pull) circuit, however, the degenerative effect of one half of the circuit at any instant immediately cancels an opposite effect of the other half of the circuit, and no loss of gain occurs. Conversely, any tendency toward an unbalance in one half of the circuit introduces degeneration which acts in opposition to the initial tendency, thereby keeping both halves of the circuit balanced. Such a tendency toward an unbalanced condition might be caused by circuit drift, due to unequal cathode emission in the two triodes.

Plate voltage for the second stage triodes is applied, from a considerably higher voltage source than that of the first stage, through plate load resistors R12 and R13. Although an applied voltage of +400

volts, dc may appear to be excessive, it should be noted that the actual voltage at the plates of V1A and V1B cannot exceed 250 volts positive with respect to the voltage at the grids, under any conditions (within Class A operating limits). Under normal operating conditions, with plate current flowing, the voltage on the plates will be considerably less than 250 volts positive with respect to the grids, due to the voltage drop in the plate load resistors, assuming that similar tubes are used in both stages (V1 and V2) with similar plate load resistors, and that no input signal is applied.

In the circuit illustrate, capacitors C1 and C2 are used in a compensation circuit; C1 connected between the output plate of one half of the circuit and the input grid of the opposite half, and C2 connected between the output plate of the second half of the circuit and the input grid of the first half. These capacitors are of very low value of capacitance, such as 0.5 pf, and function to allow positive (in-phase) feedback of the high frequencies only, leaving the mid-frequency and low-frequency response unaffected. When the proper values of capacitance are used (these values vary with the values of plate resistance, operating voltages, and tube types), the response of the over-all circuit, which normally drops off with increasing frequency, may be maintained flat to a considerably higher frequency than would be possible without this compensation. The value of capacitance used is somewhat critical, in that if the capacitance is too high the amount of positive feedback will be excessive, resulting in oscillation and severe frequency distortion. In addition to maintaining the high-frequency response over an extended range, the use of high-frequency feedback offers an additional advantage. When direct current input waveforms are being amplified, in the case of the circuit illustrated, the extended high-frequency response acts to decrease the rise time of the leading edge of the input waveform. If, for instance, the input waveform is a direct current whose voltage increases instantaneously (the leading edge of a square wave) from one value of voltage to a more positive value, this perpendicular wavefront will be found, upon analysis, to be composed of an infinite number of frequencies. If all of these test frequencies could be passed by the amplifier circuitry, the output would be a perfectly perpendicular wavefront, as shown by 1 in the following illustration. Since no amplifier can pass frequencies which approach infinite values, without attenuation,


the output of the amplifier will not be a waveform whose wavefront is perfectly perpendicular. Instead, the wavefront will begin to slope away from the perpendicular, causing an increased rise time, as shown by 2 in the illustration. As more and more of the high frequencies are attenuated by the amplifier circuitry (stated in another way, as the amplifier becomes more inferior in its high-frequency response), the sloping of the wavefront away from the perpendicular increases. Thus the originally perpendicular wavefront now becomes markedly sloped, with rounded corners as illustrated by waveform 3 below, whereas the original wavefront had sharp, 90-degree angles.

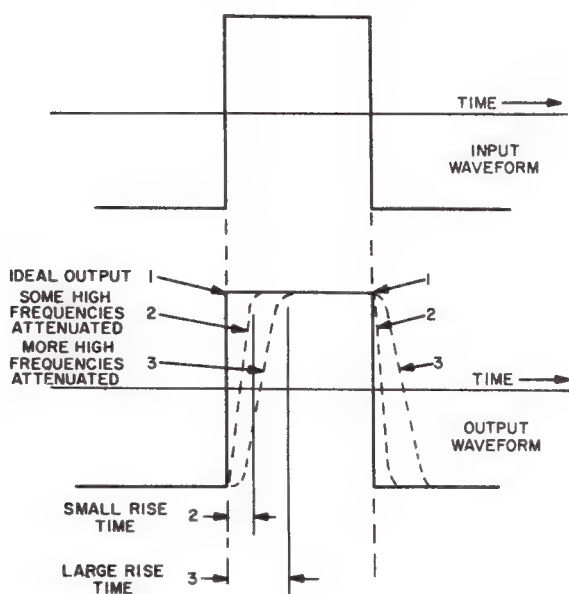

Waveform Distortion Due to High-Frequency Attenuation

Another typical circuit illustrating the use of a push-pull direct-coupled amplifier is given in the following illustration. Here, a voltmeter M having a zero-center scale is used in a vacuum-tube voltmeter circuit designed to indicate any unbalance between

the inputs to two halves of the push-pull circuit, and the direction and extent of such unbalance. The input circuit is center-tapped, to enable a comparison to be made between input A and B. The two direct-coupled triode amplifiers, V1 and V2, are connected in two legs of a bridge circuit, with the two input voltages to be compared applied to the grids of V1 and V2, respectively. The grids are returned through grid resistors R1 and R2 to a negative fixed bias voltage. Plate voltage is applied through plate load resistors R3 and R4, with a voltmeter M shunted across both plates. With tubes V1 and V2 and resistors R1 and R2 properly matched, and no input signal applied to input A or input B, the circuit is perfectly balanced and no difference of potential across the plates of V1 and V2 will be indicated by voltmeter M. This results from the fact that equal currents flowing through resistors R3 and R4 will give equal voltage drops across R3 and R4, and identical voltages will be present at the plates of both tubes. When a signal is applied across input A, the grid of V1 becomes more (or less) positive than the grid of V2, depending upon the polarity of the applied signal. If the input signal is positive, the more positive grid of V1 causes an increase in plate current through R3, creating an unbalance in the output circuit. As a result, the increased voltage drop across R3 causes the plate of V1 to become less positive than the plate of V2, and the difference between the two plate voltages will be indicated by voltmeter M. Voltmeter M is a center-scale-zero meter, and if the polarities of its connections in the circuit are correct, it will indicate a negative voltage. If a more highly positive signal is applied across input B, with the first signal remaining across input A, the grid of V2 will become more positive than the grid of V1. This will cause a higher value of current to flow through R4 than is already flowing through R3 due to the signal at input A, and the voltage at the plate of V2 will become less positive than the voltage at the plate of V1. As a result, the pointer of meter M will swing through zero to indicate a positive value of voltage difference between the two input signals.

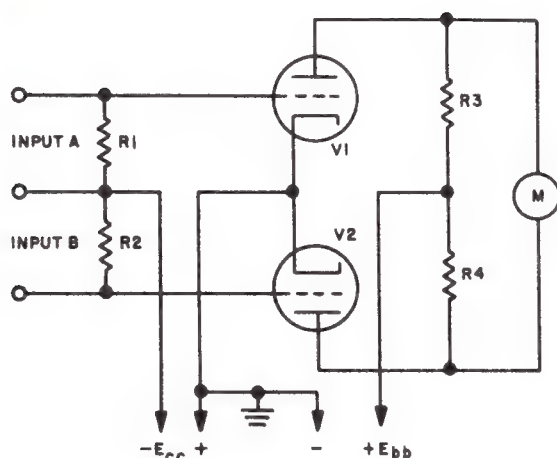

Push-Pull Direct-Coupled Amplifier Used in Vacuum-Tube Voltmeter Circuit for Two-Input Comparison

Failure Analysis.

No Output. If a signal having an amplitude within the design limits of the push-pull dc amplifier is furnished at the input terminals, a defective tube should be first suspected as the cause of no output. Note that one defective tube will cause a no-output condition in a push-pull circuit *only* if this tube is a twin-type, and then only if both halves become defective at the same time. Referring to the first illustration (typical two-stage push-pull direct-coupled (dc) amplifier), if V1A and V1B are the two halves of a twin-triode such as a type 12AU 7A, and if the V1A section of the tube should become defective, the V1B section will still operate to furnish a reduced output. In a similar manner, the failure of any single resistor in the plate or grid circuits would *not* be a cause of a no-output condition, because the other half of the circuit would continue operating. However, if common cathode resistors R3, R10, or R11 should become open-circuited or if the plate power supply to either stage (+150 VDC or +400 VDC) should fail, there would be no output.

Reduced Or Unstable Output. Assuming that a satisfactory signal is present at the input to the push-pull direct-coupled amplifier, a number of conditions could contribute to reduced output, which ordinarily would be a cause of a no-output condition in a single-ended amplifier. The failure of a single section

of a twin-triode, or of a single triode where single-triode type tubes are used, would cause a reduced output, as discussed in the previous paragraph. An "open" in any grid or plate circuit would also cause reduced output, because the other half of the circuit would continue to operate. The output, however, would probably be distorted, because either the positive or negative half of the input signal would be cut off. If either balance control R4 or position control R9 should become open-circuited at some point of rotation, an erratic output would be obtained with the control is operated across the point where the "open" exists. A simple misadjustment of R4 or R9, or of bias adjust control R11, with all other components operating normally, would contribute toward an unbalance which might result in reduced or distorted output. If capacitors C2 or C3 should change in value or become shorted, the circuit would become unstable and possibly go into oscillation. In this particular circuit, which is self-biased, a reduced value of plate voltage caused by a defective power supply would, in all probability, only result in a somewhat reduced output, the quality of which may remain acceptable. If, however, a circuit which employs fixed bias should operate with reduced plate voltage, the output might be distorted, in addition to being reduced in value.

DC CHOPPER AMPLIFIER (ELECTRON TUBE)

Application.

The dc chopper amplifier is used mainly in analog computers as a high-gain low-frequency (dc) amplifier.

Characteristics

Uses both direct coupled and dc coupled amplifiers.

Uses a chopper to change the dc signal to an ac signal of proportional amplitude.

Provides essentially drift-free low-frequency amplification.

Is particularly suitable for linear amplification or small dc voltages.

Is normally Class A self-biased, although fixed bias may be employed in some applications.

Circuit Analysis.


General. As has been explained previously in the discussion of the dc amplifier, extraneous circuit and tube noise, as well as temperature-induced gain variations in cascaded stages becomes cumulative, and tends to reduce the amount of amplification available. This occurs because these unwanted, slowly varying low-frequency signals cause a dc drift voltage to be produced. Such action does not occur in a conventional ac coupled amplifier because the coupling network passes only the ac component of the signal. Thus, any dc components resulting from noise, temperature, or other factors are isolated within the stage and are not passed on to the next stage. Consequently, with dc amplifiers used in instrumentation where the signal amplitude indicates a quantity being measured, or where it is used to control a measuring circuit, it has been found that converting the original signal to an ac voltage, amplifying it, and then re-converting it back to a dc voltage, eliminates the drift-voltage problem and permits more stable operation.

Another method of compensating for drift in high-gain dc amplifiers is to employ a compensating circuit in which the drift voltage is changed to an ac voltage, is amplified, and is then fed back as a dc voltage to compensate for the original drift voltage

change. In other texts, the circuit which converts the dc voltage to an ac voltage is called a *modulator*, and the circuit which converts the ac voltage back to dc voltage is called a *demodulator*. In this sense, the chopper amplifier corresponds to the modulator. In this handbook the term *modulator* and *demodulator* are used in the conventional sense, involving the transfer of desired intelligence from one signal to another and the detection or recovery of this signal, respectively.

Prior to the use of the transistor, chopper amplifiers usually employed electromechanical vibrators, photosensitive crystals, and in a few cases, magnetic amplifiers. Because of the appreciable power required to drive the vibrator, coupled with problems of vibration and shock, and relatively short life (about 100 hours), the mechanical chopper is considered inferior when compared with a transistor chopper. The photosensitive devices, likewise, are less desirable because of their complex circuitry. While magnetic amplifiers are still in the developmental stage, their large physical size and relatively large power requirements restrict their use.

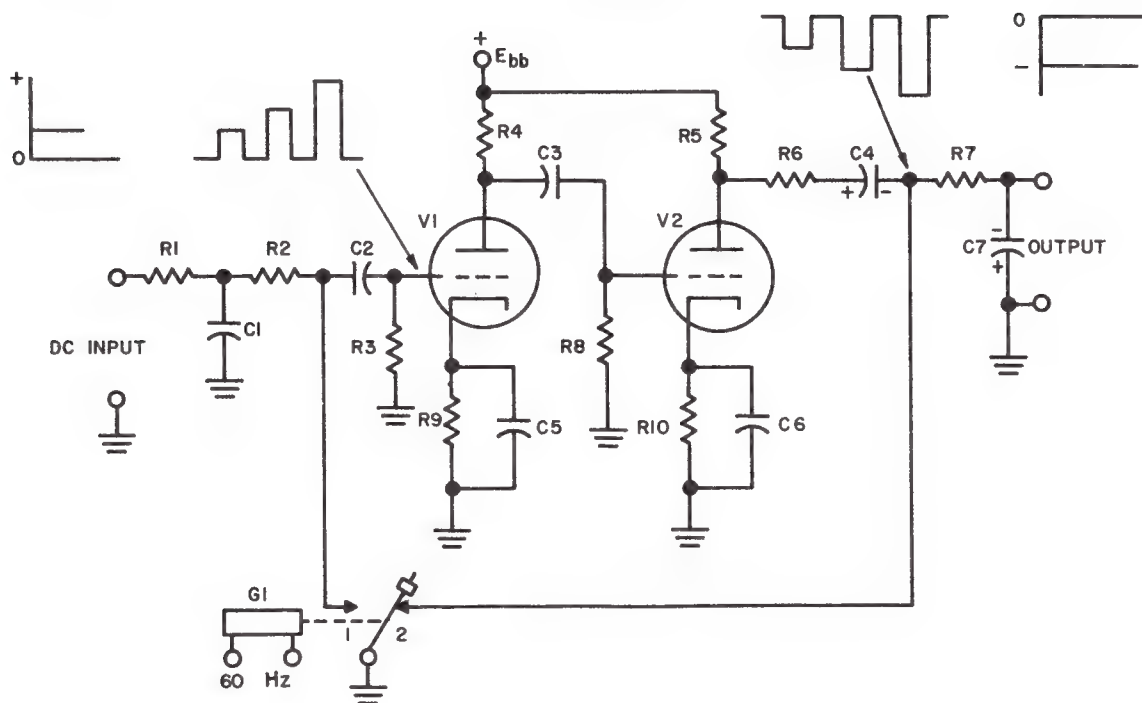Circuit Operation. The accompanying schematic shows a typical mechanical chopper amplifier circuit.



DC Chopper Amplifier

In the schematic R1, R2, and C1 form a low-pass input filter, while C2 is an input coupling capacitor. Tubes V1 and V2 are conventional triode resistance-capacitance coupled ac amplifiers using coupling capacitor C3, and plate resistors R4 and R5. Resistors R3 and R8 are the grid return resistors. Cathode bias is supplied by resistors R9 and R10, bypassed by cathode bypass capacitors C5 and C6, respectively. Cathode bias is obtained by plate current flow through the cathode resistors. (See the introduction to this section of the handbook for a more complete explanation of cathode biasing.) Capacitor C4 is the output coupling capacitor with resistor R6 as its current-limiting resistor (R6 and C4 also form an integrating circuit when grounded). Resistor R7 and capacitor C7 form a low-pass smoothing filter at the output. Synchronous chopper vibrator G1 converts the dc input to ac, and the ac output to dc.


The dc signal to be amplified is applied to the input and C1 bypasses to ground any high frequencies while R1 and R2 form resistive smoothing chokes to ensure that the input is only a slowly changing low-frequency voltage equivalent to dc. With the

synchronous vibrator arm of G1 resting on contact 1, the input to V1 is effectively grounded, and both V1 and V2 rest in the quiescent no conduction condition. Thus, there is effectively no output other than that generated internally by tube noise. With no input signal applied to V1 and the synchronous vibrator arm resting on contact 2, output coupling capacitor C4 is connected to ground, and charges to the quiescent plate voltage of V2. Simultaneously, output capacitor C7 is grounded through R7 and there is effectively no output.

When a positive dc input is applied to V1, the plate of V1 goes negative because of the increase in conduction by V1, thereby causing the plate voltage to decrease. This negative swing is coupled through capacitor C3 to the grid of V2, driving it in a negative direction. The plate current of V2 is thereby reduced, and the plate voltage of V2 rises toward the supply voltage. With the synchronous vibrator arm resting on contact 2, capacitor C4 charges to the high positive plate voltage on V2. When the synchronous vibrator arm on G1 moves to contact 1, the input voltage to tube V1 is removed (shunted to ground) and both

plates V1 and V2 return to their quiescent voltage values and, since C4 is no longer grounded, it discharges through R7 and the load, charging output capacitor C7 negatively. Thus, even though the signal has in effect passed through two stages of amplification, a positive input produces a negative output and effectively inverts the signal, as is required for a dc amplifier for computer use.

If a negative dc input is applied to the V1 grid, the plate voltage rises and drives the grid of V2 positive, drawing more plate current through plate resistor R5, and charges capacitor C4 negatively, provided that it is grounded through contact 2 of vibrator G1. Thus, when the input is grounded by the synchronous contact arm of G1 moving to contact 1, a positive discharge voltage is developed across C7. Again, the signal has been inverted and amplified through a two-stage ac amplifier. The grounding of the input signal through vibrator contact 1 produces an ac signal from the dc input, while the grounding of C4 and the output by contact 2 effectively rectifies the output of the ac amplifier by acting as an integrator and providing a negative output. The action of R7 and C7 as a smoothing filter removes any ripple component and averages out the integrated capacity discharge to provide an essentially smooth dc output. The instantaneous waveforms are shown in the accompanying waveform chart.

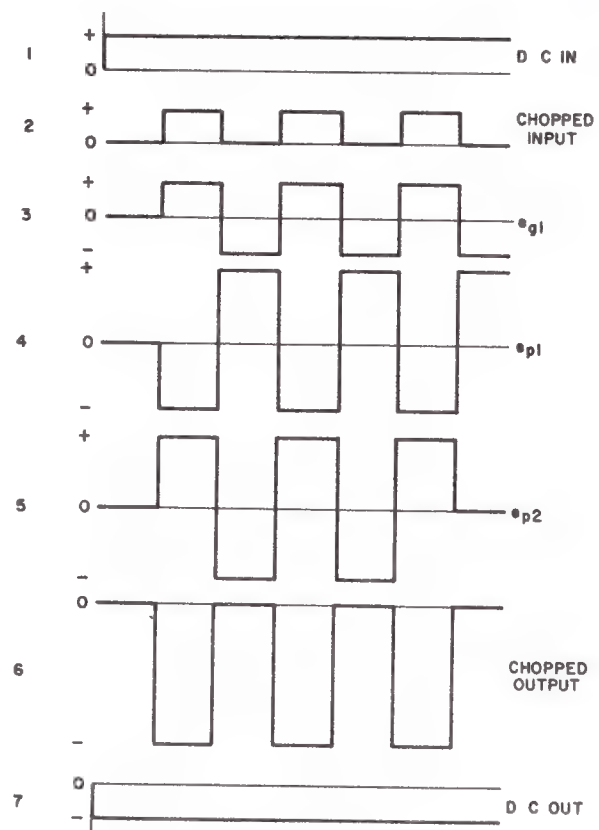

Operating Waveforms

Waveform No. 1 shows the positive dc input to C2, while waveform No. 2 shows the chopped input waveform which is reduced to zero on alternate cycles. The chopped ac waveform averages itself about a new axis on the grille side of capacitor C2, as shown by waveform No. 3. The amplified and inverted plate signal is shown in waveform No. 4 and appears on the grid of V2. The plate output of V2 is shown in waveform No. 5, while waveform No. 6 shows the discharge of C4 as a series of negative pulses. The smoothed pulses appear as a steady average negative dc output voltage, as shown in waveform No. 7. Since the chopping occurs at a constant rate and is equal for both input and output, the ac and dc signals are proportional. Since Class A bias is used in the ac amplifier, the overall amplification is linear.

DC CHOPPER AMPLIFIER (SEMICONDUCTOR)

Application.

The transistor chopper type of dc amplifier is used in analog computers, instrument recorders, and servo-mechanism control systems to convert dc (low-frequency) voltage to ac voltage, for drift-free amplification.

Characteristics.

Uses common-emitter circuit normally, but may also use the inverted form (emitter connected as collector, and collector connected as emitter).

Is free of cumulative dc drift.

Is particularly suitable for linear amplification of small dc voltages.

Uses a rectangular audio-frequency input signal of steady amplitude to provide the chopping action.

Is Class A-biased and normally uses self-bias, although fixed bias may be employed in some applications.

Circuit Analysis.

General. As has been explained previously in the discussion of the dc amplifier, extraneous circuit and transistor noise, as well as temperature-induced gain variations, in cascaded stages becomes cumulative and tends to reduce the amount of amplification available. This occurs because these unwanted signals cause a dc (drift) voltage to be produced. Such action does not occur in a conventional ac-coupled amplifier

because the coupling network passes only the ac component of the signal. Thus, any dc components due to noise, temperature, or other factors are isolated within the stage and are not passed on to the next stage. Consequently, with dc amplifiers used in instrumentation where the signal amplitude indicates a quantity being measured, or is used to control a measuring circuit, it has been found that converting the original signal to an ac voltage, amplifying it, and then reconverting it back to a dc voltage eliminates the drift-voltage problem and permits more stable operation.

Failure Analysis.

No Output. Lack of input voltage or plate supply voltage, open resistor, shorted capacitors, as well as a defective tube can cause loss of output. If R1 or R2 is open, or C1 is shorted, or if vibrator G1 remains on contact 1, no input will be applied to C2 measure the plate voltage and cathode voltage of V1 and V2. If voltage is not present or is abnormal, resistors R4, R5, R9 and R10 may be defective or capacitors C1, C5, and C6 could have shorted to ground. Determine if the 60 Ha voltage is applied to chopper G1 and observe that it operates. If ac voltage is applied and the chopper does not operate, the vibrator is defective. Check that a signal exists on the grid of V1. If no signal appears, check C2 for an open circuit (make certain the chopper arm is not resting on contact 1.) If a signal appears on V1 grid but not on the plate, V1 is probably defective. If a signal appears on the plate of V1 but not on the grid of V2, check C3. Check the resistance of R3 and R8 also to make certain they are not shorted. If an input exists on the grid of V2 but not at the plate, V2 is probably defective. If there is an output at the plate of V2 but not at the output terminal, check the resistance of R6 and R7, and also check C4 and C7, and make certain that the arm of vibrator G1 is not resting on contact 2.

Low Output. Low plate voltage, a defective tube, high bias, a high series resistance, or a leaky shunting capacitor can cause a lower than normal output. Check the plate voltage and bias, if it is normal, tubes V1 and V2 are probably defective. If the plate voltage or bias are abnormal, check the components involved (R4, R5, R9 and R10). Also check C1, C2, C3, C4 and C7 to determine whether they are leaky or have changed value. To determine if any of the series resistors have increased in value, measure the resistance of R1, R2, R6, and R7.


High Output. High plate voltage, low bias or a lowering of series resistance may produce a higher than normal output voltage. Measure the supply voltage to make certain that the power supply is not at fault, and measure the plate voltage. If the plate voltage is high with normal supply voltage, either plate resistors R4 and R5 or cathode resistors R9 and R10 have changed in value. Also check series resistors R1, R2, R6, and R7 for a change of value if the high output persists. It is most likely that a low output condition will be more often encountered than a high output condition.

Another method of compensating for drift in high-gain dc amplifiers is to employ a compensating circuit in which the drift voltage is changed to an ac voltage, is amplified, and is then fed back as a dc voltage to compensate for the original drift voltage change. In other texts, the circuit which converts the dc voltage to an ac voltage is called a *modulator*, and the circuit which converts the ac voltage back to dc voltage is called a *demodulator*. In this sense, the transistor-chopper amplifier corresponds to the modulator. In this handbook, the terms of *modulator* and *demodulator* are used in the conventional sense, involving the transfer of desired intelligence from one signal to another and the detection or recovery of this signal, respectively.

Prior to the use of the transistor, chopper amplifiers usually employed electromechanical vibrators, photo-sensitive crystals, and in a few instances magnetic amplifiers. Because of the appreciable power required to drive the vibrator, coupled with problems of vibration and shock, and relatively short life (about 1000 hours), the mechanical chopper is considered undesirable when compared with the transistor chopper. The photosensitive devices, likewise, are less desirable because of their complex circuitry as compared with the transistor. While magnetic amplifiers are still in the developmental

stage, their large physical size and relatively large power requirements restrict their use. Thus, the transistor-chopper amplifier provides a simple and effective means of converting and amplifying the dc signal.

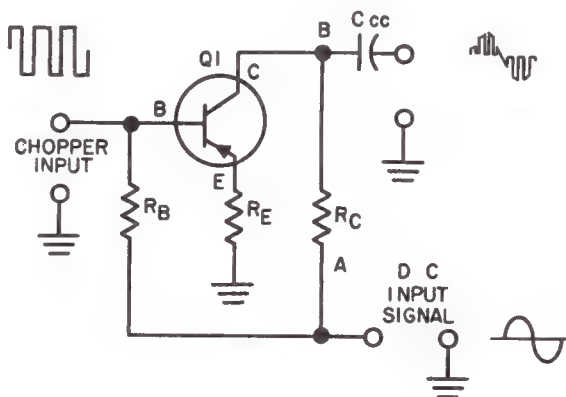Circuit Operation. The following schematic shows a typical transistor chopper using the grounded-emitter configuration.



Transistor Chopper (GE)

Self-bias is used with R_B and the internal base-emitter resistance providing the bias (it acts as a voltage divider connected across the supply). Emitter resistor R_E serves as an emitter swamping resistor provides thermal compensation. (See the introduction to this section of the handbook for a discussion of bias and bias stabilization.) The collector input, which is the signal from the dc amplifier stage, is direct-coupled, while the chopper (sometimes called "carrier") input may be either direct- or ac-coupled. In either instance, the circuit bias voltage must be arranged so that the direct coupling does not bias off

Q1 in an undesirable mode of operation. Note that the direct-coupled collector input is actually the collector supply voltage. Note also that the ac waveform shown as the dc input signal on the schematic represents the signal component produced by increasing the dc input above the level representing zero to produce a positive waveform, and decreasing the dc level below this zero level to produce the negative waveform. It actually is a dc voltage which varies at the signal frequency.

The operation is such that the transistor acts as a switch, being off when de-energized and on when energized. The switching action is obtained from the chopper input signal, which is a rectangular pulse of constant amplitude (usually in the audio range). On the positive peak, the forward base bias is reduced to a value which stops conduction through the transistor. On the negative peak, the forward base bias is increased and the emitter conducts heavily in the saturation region. During the vertical rise and fall times, the bias changes rapidly from one state to the other. It is during this time that the transistor is in its normal operating region, but because of the short duration of the rise and fall time no actual amplification occurs during this period.

Let us consider one cycle of operation. Assume that the transistor is resting in its quiescent state with a small self-bias and with no inputs applied. Transistor Q1 will draw its quiescent value of collector current. Assume that a 1000-Hz rectangular pulse is applied as the chopper input to the base electrode. With equal on and off times the transistor will conduct heavily during the negative chopper-pulse when the forward bias is increased. Assume that the dc input signal is also simultaneously applied to the collector, and that it is positive. This will place a forward bias on the collector (instead of the normal reverse bias), and the transistor will quickly reach a steady saturation current. Note that the dc amplifier input signal is actually acting as the collector supply voltage. At point A on the schematic the input waveform will appear; however, at point B the input voltage is entirely dropped across collector resistor R_C , as a result of the heavy conduction, and no output appears. When the chopper input signal goes positive the forward base bias is opposed, and, since the square-wave input is always of greater amplitude than the bias, the base is reverse-biased and collector

current is effectively reduced to zero. It is not exactly zero because a small reverse current, I_{ce0} , flows through the internal resistance of the base-collector and emitter-base junctions of the transistor. This reverse current produces a voltage drop through collector resistor R_C in opposition to normal collector current flow, from points B to A instead of from points A to B. Therefore, the polarity of this reverse-generated voltage is in opposition to the dc input signal, and thus reduces it a small amount. However, for the present we may ignore this small loss of input voltage and say that during the nonconducting period the full amplitude of input voltage appears at the output. During the entire positive excursion of the dc input signal, the output will consist of a series of pulses having approximately the same amplitude as the input signal at the instant the transistor is turned off. When passed through coupling capacitor C_{cc} , this waveform will look exactly like the input since the dc portion is eliminated and only the varying ac portion appears at the output. As stated previously, this amplitude is slightly less than that of the input because of the reverse drop through R_C . Therefore, although called a "chopper-amplifier," it is clear that the gain is always less than unity and the function is mainly one of converting the dc signal to an ac signal.

Consider now the operation on the opposite half-cycle of the dc input signal. In this instance the collector voltage is always negative, which is the normal reverse-biased collector condition. With the same rectangular chopper input signal, the base bias is alternately reduced and aided. In the reduced condition, effective zero collector current is obtained; during the aiding part of the chopper signal, the forward bias is increased. Thus, the same operating conditions prevail, with the transistor alternately driven to saturation (this time by the chopper signal alone) and to effective cutoff. During saturation (the on period) the collector input signal is dropped to zero through the collector resistor, and during effective cutoff (the off period) the signal appears at the output. In this instance, again, there is also a flow of reverse current, which produces a slight opposing voltage so that the input signal is slightly reduced. The output appears as a negative varying voltage which is identical in shape to the input signal. In the collector circuit it consists of a group of pulses with

an amplitude equal to the input signal amplitude (minus the reverse drop) during the off period.

The unique property of the transistor which permits it to operate with either a forward-biased or reverse-biased collector also serves to switch the functions of these elements. Thus, with forward bias the collector becomes an emitter, and the emitter functions as the collector. This allows the designer the choice of either connecting the transistor as a common emitter, or of reversing the collector and emitter connections and have it operate in the inverted fashion. In either case the operation is identical except that the terms *collector* and *emitter* must be interchanged in the places they appear in the circuit discussion.

In some applications the emitter resistor is not used since its function is for temperature stabilization by small or incremental changes of emitter current, and the large value of saturation current requires R_E to be a small value to prevent interference with circuit operation. By selecting Class A bias for quiescent operation, the transistor is biased in its mid-range of operation, thus permitting the control signal to swing it equally in either direction for cutoff or saturation. This allows the use of a multivibrator type of chopper input signal as the trigger. With some transistors and design, base resistor R_B is also omitted, with contact bias being supplied by the internal base resistance of the transistor. In any event, the chopper-amplifier is always easily recognized because of the dual inputs, with one of them acting as the collector supply.

To be linear in operation, the output signal must be proportional to the input signal. Unfortunately, the transistor is not a perfect switch. When it is closed there is a finite voltage drop across it, and, as stated previously, when it is open there is leakage current through it. The voltage drop across the transistor in the on state is referred to as the "*offset voltage*", and the leakage current is known as the "*offset current*". It is evident that either one reduces the amplitude of the input signal and thus affects the input signal by fixing the lowest limit of signal which may be chopped. These voltages and currents can be reduced by proper selection of transistors (silicon types are preferred) and by use of the inverted emitter-collector (transposed) connection. With the inverted connection a lower offset voltage is obtained because of the effects of the emitter and collector ohmic

spreading resistances. This becomes a design problem since the reverse collector and emitter currents (I_{CO} and I_{EO}) are both dependent upon temperature (they double in value for each 10-degree rise in temperature) and upon voltage (the point of occurrence varies with the voltage). With good design, the output is practically zero when the transistor is conducting, and it is almost equal to the instantaneous value of the input signal when it is non-conducting.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low-voltage ranges of conventional volt ohmmeters. Be careful also to observe proper polarity when checking continuity with the ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No output. If there is no chopper input to trigger the circuit, or if base resistor R_B is open or transistor Q1 is defective, there will be no output. Check the base resistor for continuity with an ohmmeter and the chopper input signal with an oscilloscope. An open collector resistor or emitter resistor will also interrupt the output, and can be located by making a continuity check. If all components check normal and inputs to the base and emitter (or collector) are present, the transistor is defective.

Reduced Output. Any increase in resistance in the collector emitter circuit will reduce the amplitude of the output signal. Likewise, a reduction in chopper amplitude can result in insufficient drive for normal operation and produce a partial output. The circuit resistances can be checked with an ohmmeter, and the chopper signal with an oscilloscope. If coupling capacitor C_{CC} is shorted, the output will also be reduced.

Distorted Output. A nonlinear output in this circuit is equivalent to distortion in conventional amplifiers. Once the circuit is designed, only a change in the value of the components, input signals, or the transistor can cause distortion. The chopper input signal can be checked on an oscilloscope, and the components can be checked with an ohmmeter. A leaky or shorted coupling capacitor (C_{CC}) can cause distortion with reduced output, depending upon the voltages existing in the next stage. The capacitor must be

disconnected to check for leakage, but it can be ohmmeter. If all components check normal, the transistor must be defective.

PART 5-2. AUDIO AMPLIFIERS

AUDIO AMPLIFIERS

General.

The audio amplifier is a circuit arrangement, composed of a tube or tubes and associated components, which is intended to amplify an ac signal whose frequency or composite frequencies fall within the audio range, usually considered to extend from 30 to 15,000 Hz.

This does not mean that all audio amplifiers will amplify all frequencies within this range. Only one particular application—that of the so-called “high-fidelity” audio amplifier—is designed to accommodate the entire range, and amplify all frequencies within the range equally well. Amplifiers in many of the other applications are designed to amplify only portions of the audio range. Specifically, any amplifier that amplifies an input signal whose frequency lies between 30 and 15,000 Hz—whether the input signal consists of only one particular frequency or a multitude of frequencies—may be classed as an audio amplifier. This point should be borne in mind, because in some piece of equipment a circuit may be encountered which is referenced as an audio frequency amplifier, but which actually handles no “audio” intelligence in the sense that it is both within the range of audibility and is intelligible to the human ear. For illustration, the frequency-shift system of transmitting teletype information on a radio-frequency channel utilizes an audio frequency amplifier to raise the audio level of two specific frequencies—one for the “mark” and the other for the “space” in a teletype character—before these frequencies are converted to r-f signals for transmission. In this case the audio amplifier is required to amplify only two frequencies, such as 85 Hz and 170 Hz. Additional circuits may be included to actually restrict the response of the amplifier to a narrow range, such as from 30 to 200 Hz, in order to pass only the two frequencies mentioned above. Yet this amplifier is termed an audio amplifier.

Classifications.

Audio amplifiers may be divided into two general classifications: voltage amplifiers and power amplifiers. In each of these divisions there are several circuit configurations, each of which may utilize one or

more different types of vacuum tubes: triodes, tetrodes, pentodes, or beam power tubes.

The specific characteristics and circuit operation of several configurations in each division are contained in the seven circuits to follow in this section. A brief discussion covering audio amplifiers in general is given in the following paragraphs.

In a voltage amplifier, the primary consideration is the ratio of the alternating output voltage to the alternating input voltage. This ratio is termed the *gain* of the amplifier. The amount of power which is available in the output circuit is both minute and incidental—the increase in signal voltage is the prime concern. In order to produce the largest possible output signal voltage, which is taken across the load, the impedance of this load must be as large as practicable.

In a power amplifier, the primary consideration is the delivery of a large amount of power to the load.

Since power is equal to voltage times current, generally speaking, a power amplifier must develop a sufficient voltage across its load to cause the required current to flow. The value of the load impedance is an important factor, because it will govern, to a large degree, the amount of current which will flow with a given voltage. The value of the load impedance is selected for one of two conditions at a given minimum allowable level of distortion: maximum output circuit efficiency or maximum power output. Output efficiency is the ratio of output power to the dc input power, and it is generally low in an amplifier which is designed for minimum distortion.

The circuit used in both a voltage amplifier and a power amplifier may be one of several types: resistance-capacitance coupled, impedance coupled, transformer coupled, or direct coupled. Each type has certain advantages and disadvantages, which adapt it to specific applications. A resistance-capacitance audio amplifier is probably the most widely used type, with its components relatively inexpensive and their weight relatively light. Its frequency response can be designed to be uniform over the entire audio range.

An impedance-coupled audio amplifier utilizes an inductor in place of the load resistor used in the conventional resistance-capacitance coupled circuit. A large value of inductance is used, to obtain a maximum amount of amplification—particularly at the lower audio frequencies. The amplification is not uniform over the audio range because the load

impedance of the inductor varies with frequency, in accordance with the relationship:

$$Z_L = \sqrt{R^2 + (2\pi f_L)^2}$$

where: Z_L = load impedance (ohms)

R = resistance of inductor (ohms)

f = audio frequency (Hz)

L = inductance of inductor (henries)

The amplification is higher than in the resistance-capacitance coupled circuit with the same plate supply voltage, because the relatively low dc resistance of the inductor contributes to a higher voltage at the output.

A direct-coupled audio amplifier has the distinct advantage of distortionless amplification, when the operating voltages are properly adjusted for Class-A operation. Its response is uniform over a wide frequency range, especially at the low frequencies—and even to zero frequency (direct current). Its practically instantaneous response allows an absolute minimum value of phase distortion, making it especially useful in the amplification of square-wave pulses, such as are used in teletype communications. Its chief disadvantages are the complexity of the resistance network that is required to obtain the proper plate and grid voltages for each stage and the tendency toward instability of operation, as well as the successively higher voltages required to operate the second and any succeeding stages.

Special Transistor Considerations.

The semiconductor type of audio amplifier is similar to its vacuum tube counterpart; however, there are a number of significant differences which must be considered. For example, the electron tube audio amplifier normally operates as a voltage amplifier except for the final output stage, while the transistor audio amplifier operates as a current amplifier in all stages. Thus, the electron tube represents a high-impedance, voltage-sensitive device, while the transistor represents a low-impedance, current-sensitive device.

Since the transistor is basically a low-resistance device, it may draw current from the input source or the preceding stage. (Except in class B audio amplifiers, the drawing of grid current in tube amplifiers represents distortion and is never used. While class C amplifiers do draw grid current in normal operation,

they are never used for audio amplification.) In this respect, each transistor amplifier stage may be considered as a current or power amplifier operating at a current or power level higher than that of the preceding stage, but lower than that of the following stage.

While the types of transistor amplifiers are similar to the types of electron tube amplifiers, such as preamplifiers, driver-amplifiers, and output stages, the power levels employed are much lower. Thus, transistor preamplifiers generally operate in the micro-watt range, amplifiers and driver stages operate in the low milliwatt range, and output stages operate in the high milliwatt or low watt range. At present, power output of 50 to 100 watts for transistor audio amplifiers are normal, whereas power outputs of 1 to 10 watts were considered high until recently. Therefore, any general statements relating to powers applicable to the following circuits must not be taken too literally, since they will change with the state of the art. Actually, except for extremely high-powered transmitter applications, the transistor audio amplifier today compares very favorably in many respects with the electron tube audio amplifier. The small size and reliability of the transistor, plus its long life and low heat-producing ability make its use popular in equipments normally requiring many stages; in addition, the ability to operate at low voltages makes the transistor particularly useful in portable and mobile equipments operating from battery supplies. In larger equipment, power for transistor operation may be obtained from special low-voltage power supplies employing semiconductor diodes and regulators, thus eliminating the need for batteries.


Transistor amplifiers may be operated class A, B, AB, or C, just as with electron tube amplifiers. When operated class A, they are operated on the linear portion of the collector characteristic. The class A biased transistor has a continuous flow of collector current during the entire cycle, whether a signal is present or not, which corresponds with the action in its electron tube counterpart. They may be operated in this manner, in either single-ended or push-pull circuits. Class B amplifiers can be biased either for collector current cutoff or for zero collector voltage. They are always operated push-pull to avoid serious audio distortion. The best power efficiency is obtained when they are biased for collector current cutoff, since collector current will flow only during that half-cycle of the input voltage that aids the forward

bias. When biased for zero collector voltage, a heavy current flows when no signal is present, and practically all the collector voltage is dissipated across the load resistor. Although heavy current flows, the power dissipation in the transistor is very low because power is the product of both *current and voltage*, and the voltage is practically zero (due to the small voltage drop across the very low impedance of the transistor). The collector current varies only during that portion of the cycle when the input voltage opposes the forward bias. Under these conditions low efficiency is obtained and the forward current transfer ratio (α_{ib}) is appreciably reduced. The class AB transistor amplifier is biased for either collector voltage cutoff or current cutoff for less than a half-cycle of operation. In this case the efficiency is somewhat greater than that for class A, but less than that for class B, and the statements just made concerning the class B amplifier also apply to the class AB amplifier. Class C amplifiers are biased so that the collector current or voltage is zero for more than a half-cycle; thus, they are not used for audio amplification because of the series audio distortion produced. However, they can be used single-ended or push-pull (or push-push) for r-f applications.


The most important factors to be considered in an analysis of audio amplifiers are input and output impedances, signal and noise levels, and required frequency response. Since the transistor is basically a low-level current device it is most important that the input and output impedances be matched to obtain maximum power gain. (In the electron tube circuit this is usually only a problem in the output stage.) The ratio of signal-to-noise power at the input to signal-to-noise power at the output gives the noise factor

$$(\text{figure}), F_n = \frac{S_{in}/N_{in}}{S_{out}/N_{out}}.$$

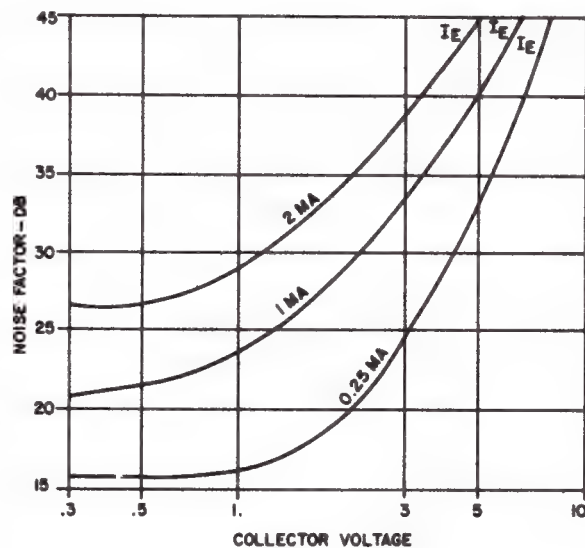The smaller this ratio (F_n), the better the noise quality of the amplifier. The noise factor is affected by the operating point, the signal source resistance, and the frequency of the signal amplified. The accompanying chart shows a typical variation of noise factor with collector voltage and emitter current.



Variation of Noise with Operating Point

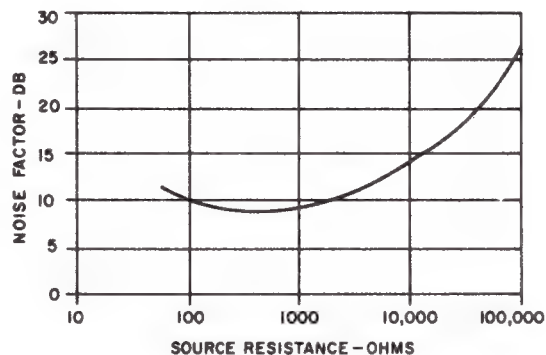


Source Resistance Versus Noise Factor

This figure shows several curves for various values of operating emitter current and collector voltage. As can be seen, the best condition for low noise is operation at emitter currents of less than 1 milliampere and at collector voltages of less than 2 volts. Note that an increase in collector voltage will increase the noise more rapidly than will a similar increase in emitter current. This corresponds to a similar condition in tube amplifiers where high-gain stages are operated at low voltages to reduce noise.

The effect of a change in the signal source resistance upon the noise factor is indicated in the following graph, which indicates that best operation is obtained with an input resistance of 100 to 3000 ohms.

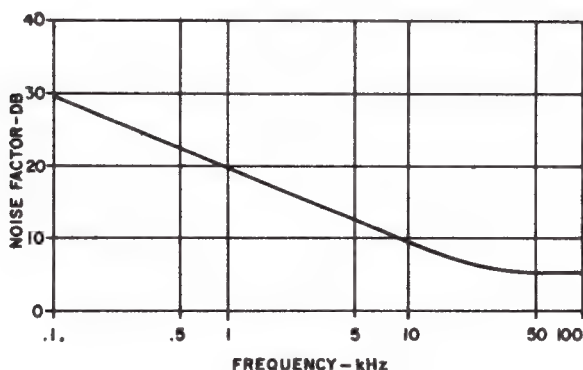
The manner in which the noise varies with frequency is indicated in the following graph. For very low frequencies the noise is high, and for higher and higher frequencies it tends to decrease until at about 50 kHz the curve changes direction and noise again starts to increase. In particular, this illustration predicts that low-noise dc amplifiers are difficult to achieve and design.



Noise Variation with Frequency

The necessity for matching input and output circuits for greatest power gain dictates that particular circuit configurations be used. For example, a low input resistance can be obtained by using the common base (CB) circuit for values of 30 to 150 ohms, and the common emitter (CE) circuit for values of 500 to 1500 ohms. Although a high input resistance produces more noise, its use is necessary when a high-impedance device such as a crystal microphone or a transducer is used. Otherwise, a transformer is required for proper matching.

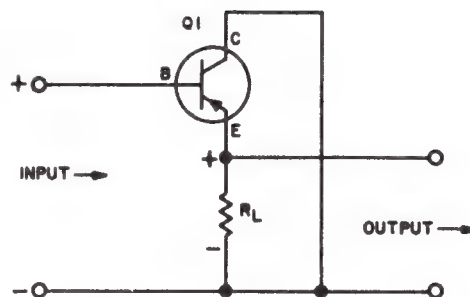The common collector (CC) circuit, which is similar to a cathode follower in electron tube usage, provides a relatively high input impedance, as shown in the following basic circuit.




CC Input Circuit

The high input resistance is produced by the large negative voltage feedback in the base-emitter circuit. As the input voltage rises, the opposing voltage developed across R_L substantially reduces the total voltage across the base-emitter junction, and the current drawn from the signal source remains low. A low current produced by a relatively high voltage indicates low resistance (by Ohm's law); thus, if a 500-ohm resistor is used as R_L , the input resistance for a typical transistor will be approximately 20,000 ohms. Unfortunately, however, small current changes in the circuit, caused by functioning of the following stage, produce large variations in the input resistance value; therefore, this type of input circuit is not very desirable.

A better input circuit can be obtained by use of the CE configuration with series resistance, as shown in the following schematic.


In this figure, r_i represents a typical base-emitter resistance of 2000 ohms with a load resistance of 500 ohms. To achieve the 20,000-ohm input resistance of the circuit previously described, an 18,000 ohm series resistor, R_s , is employed; 18,000 ohms plus the initial 2000 ohms will produce the required value. By use of the series 18,000 ohm resistor the total input resistance can be kept relatively constant at 20,000 ohms, unaffected by variations in transistor parameters or by the current drain of the following stage. The disadvantages of this circuit are a small loss in current

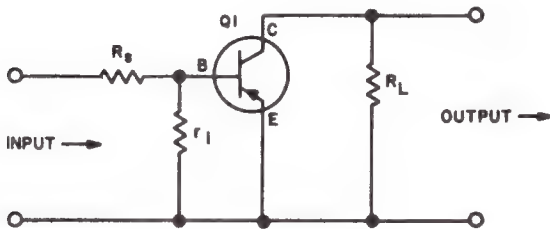gain and the large resistance in the base circuit. The use of a large resistance in the base circuit can lead to bias instability if the bias voltage is fed to the transistor via this resistance.



Series CE Input Circuit

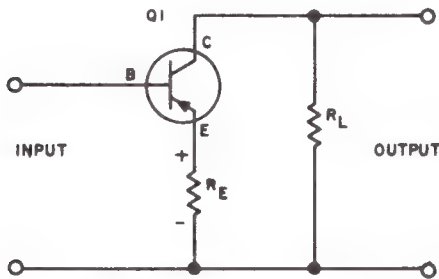The following input circuit represents the best overall compromise.



Degenerative CE Input Circuit

The signal voltage developed across the unby-passed emitter resistor, R_E , develops a voltage in opposition to the input signal. This degenerative (or negative) feedback voltage causes an increase in the input resistance. When a 500-ohm load resistor, R_L , is used with a 500-ohm emitter resistor, R_E , the total input resistance is approximately 20,000 ohms for a typical transistor. In addition, the emitter resistor acts as a swamping resistor, to help stabilize the transistor and minimize thermal variation effects.

Because the common-emitter configuration provides thermal stability (by means of emitter swamping), a relatively high input resistance, and high voltage-and-current gain, it is usually employed to the exclusion of other configurations. Therefore, the circuits to be discussed in later paragraphs will use the common-emitter configuration; the other forms of these circuits will not be mentioned unless considered pertinent to the discussion.

The transistor audio amplifier is usually classified as a *small-signal* amplifier or a *large-signal* amplifier. Actually, the small-signal condition represents excursions of the input signal over only a small range about the operating point (bias level), on the order of fractions of a volt. Small-signal conditions are normally calculated by appropriate formulae, since the values remain relatively linear or mathematically constant over the small range involved. On the other hand, with large-signal conditions, which are associated with the power amplifier (or output stage), there may be considerable departure from the formula for large values; thus, the power amplifier must be analyzed and designed graphically. In this respect, the transistor is somewhat different from the electron tube, with inherent nonlinearities which vary considerably from unit to unit. As a result, matched parts of transistors are used to produce the desired results where the individual parameter variation is too large.

R-C COUPLED TRIODE AUDIO AMPLIFIER (ELECTRON TUBE)

Application.

The R-C coupled triode audio voltage amplifier is used to increase the amplitude of an audio-frequency signal voltage when uniform gain is required over the entire audio spectrum and when a medium value of gain (between 5 and 70) is required. It is generally used to amplify low-level signal inputs, such as those generated by an audio oscillator circuit or by a microphone, vibration pickup, or magnetic tape pickup. It commonly appears in the audio section of communications receivers and transmitters, in sonar equipment, and in applications which utilize signal frequencies in the audio-frequency range instead of aural intelligence.

Characteristics.

Input is normally an audio-frequency signal of extremely small amplitude.

Input impedance is normally very high, ranging from several thousand ohms to several megohms.

Output impedance is usually high, ranging from several thousand ohms to approximately half a megohm.

Voltage gain ranges from 5 to 70, depending upon the application and circuit design.

Operates Class A; no grid current flows under any conditions.

Frequency response is linear over the range of audio frequency for which the amplifier is designed. This may include the entire audio range, or may be restricted to a portion of it, depending upon the intended application of the amplifier.


Output (plate) signal and input (grid) signal are of opposite polarity.

Cathode bias (self-bias) is normally used; fixed bias may be used in some applications.

Circuit Analysis.

General. The R-C coupled triode voltage amplifier circuit is one of the most widely used circuits in audio-frequency amplification. It has the advantages of being the least expensive, having the lightest weight components, having good fidelity over a wide frequency range, and being relatively free from undesirable currents induced by stray fields and ac heater wiring. Probably its only disadvantage is the higher plate supply voltage as compared to that of a transformer-coupled or impedance-coupled circuit; the higher voltage is required to compensate for the voltage drop across the plate load resistor.

Circuit Operation. The R-C coupled triode audio voltage amplifier is used to amplify and reproduce, without distortion, input signal voltages of audio frequency which are applied to the grid of the triode tube. The circuit of a typical amplifier of this type is shown in the following illustration. In this circuit the input signal is applied to the grid of triode V1 through coupling capacitor C1. The grid is returned to ground through grid resistor R1. Cathode bias is furnished by means of cathode resistor R2, which is bypassed by capacitor C2 to maintain the bias at a constant average value and thus prevent degeneration. Plate voltage is furnished from the plate power supply, Ebb through plate load resistor R3. In some circuits, especially where several stages of amplification are utilized, an additional resistor may be used, connected in series between the plate load resistor and Ebb, with a capacitor connected from the junction of the two resistors to ground, to form a decoupling circuit. This addition prevents the possibility of audio feedback (and its result—oscillation) from an output stage or one operated at a high audio level, back to an input or low-level stage through the power supply, Ebb, which could act as a means of common coupling.

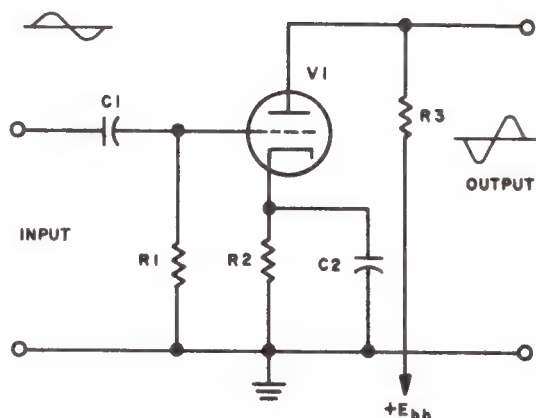


Typical R-C Coupled Triode Audio Voltage Amplifier Circuit

In order to obtain a high value of audio output voltage (a high signal voltage), the resistance value of the plate load resistor should be as high as possible. But this requirement imposes an additional one, because an increase in the resistance of the plate load will cause an increase in the voltage drop across it, resulting in a decrease in the actual voltage at the plate of the triode. In order to obtain the required effective plate voltage, with an increased resistance of the plate load, and only solution is to increase the plate supply voltage, Ebb. However, there is a practical limit to the amount by which the plate voltage may be increased. The maximum voltage obtainable from the plate power supply and the voltage rating of the bypass capacitors in the plate supply circuit both serve to establish this limit.

A frequency response curve for a typical R-C coupled triode audio voltage amplifier is shown in the following illustration. It may be seen, from the illustration, that the amplification decreases at both high and low frequencies. As the frequency increases toward the high end of the response curve, amplification falls off because of the shunting effect of the combination of output capacitance of the stage, the distributed capacitance of the coupling network, and the input capacitance of the following stage. These all act to shunt the higher frequencies to ground. As the frequency decreases toward the low end of the response curve, the amplification also falls off. In this case the reduced gain is caused by the increase in

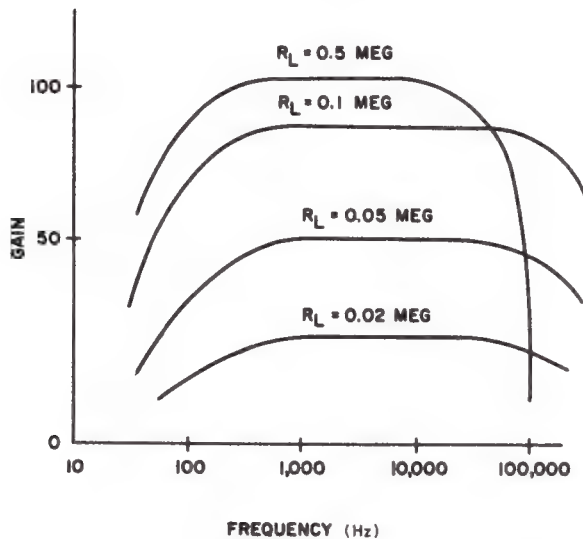reactance of the coupling capacitor as the frequency decreases, and is also caused by the increase in reactance of the cathode bypass capacitor, which introduces degeneration at the lower frequencies.



Frequency Response of an R-C Coupled Triode Audio Voltage Amplifier With Various Values of Plate Load Resistance

An R-C coupled triode audio voltage amplifier can be designed to give a good frequency response for almost any range of audio frequencies. For instance, an amplifier can be built to give uniform amplification for audio frequencies from 100 to 20,000 Hz. By changing the values of the coupling capacitor and the load resistor, the frequency range can be extended to cover the very wide frequency range of the video amplifier. However, this extended range may be obtained only at the cost of reduced amplification, or gain, over the entire range. This may be observed by referring to the previous illustration; it will be seen that the output response is relatively flat from approximately 100 Hz to well over 10,000 Hz when the value of the load resistor, R_L , is 0.02 megohm, but the over-all gain is relatively low compared to that obtained using higher values of plate load resistance. Thus, the R-C coupled triode audio voltage amplifier may be made to give a good frequency response over the entire audio range, at medium values of amplification.

Failure Analysis.

No Output. A no-output condition in an R-C coupled triode audio voltage amplifier may be caused by any one of several defects. First, the presence of an input signal at the input to the amplifier should be verified. The triode tube should be checked to insure that it is capable of operation. The presence of plate voltage at the plate of the triode should be checked; if no voltage or a very low voltage is present, a defective plate load resistor or a defective plate power supply is indicated. If the voltage at the cathode is very high—approximately equal to the plate supply voltage, Ebb—an open cathode resistor may be the cause of no output, assuming that the plate load resistor and the triode have been both found in an operable condition. Finally, an open input coupling capacitor may be the cause of a no-output condition.

Reduced or Unstable Output. Reduced or unstable output from an R-C coupled triode audio voltage amplifier may be due to an aging tube having poor cathode emission, a reduced value of plate voltage due to a defective plate power supply, or an input signal of insufficient amplitude. An open grid resistor would cause severe distortion, greatly reduced output, and possibly intermittent operation due to "grid blocking". If the input coupling capacitor were leaky, distortion would be present in the output signal as a result of the presence of a positive value of voltage at the grid, from the plate of the previous stage supplying the input signal. A reduced value of output, without distortion, may be caused by an open cathode bypass capacitor, which would introduce degeneration in to the circuit. An excessive value of bias, caused by too high a value of cathode resistance (or too high a value of bias voltage if a fixed bias is applied), would also be responsible for an output signal of reduced value.

R-C COUPLED AUDIO AMPLIFIER (SEMICONDUCTOR)

Application.

The r-c-coupled transistor audio amplifier is commonly used where good fidelity over a large range of audio frequencies is desired. For example, it is used in the amplifier stages of receivers and communications equipment where little or no power output is required.

Characteristics.

Uses common-emitter circuit for high gain and better impedance matching.

Operates Class A for linear operation and minimum distortion.

Usually amplifies small signals, but can be designed to handle large signals in cascaded stages.

Is usually fixed-biased from the collector supply, but may be self-biased in some applications.

Emitter swamping is normally used for thermal stabilization.


Gain is fairly uniform over a range of approximately 100 to 20,000 Hz or more.

Both voltage gain and power gain are high.

Circuit Analysis.

General. The r-c-coupled transistor amplifier is similar in general to the r-c-coupled electron tube amplifier previously discussed in this section of the handbook. Use of the common (or grounded)-emitter circuit, permits the analogy that the base is equivalent to the vacuum tube grid, the emitter is equivalent to the tube cathode, and the collector is equivalent to the tube plate. Thus, it is clear from the following schematic that the two r-c-coupled circuits are practically identical. Any differences are due to the internal parameters of the transistor and the matching requirements for maximum output with minimum distortion.

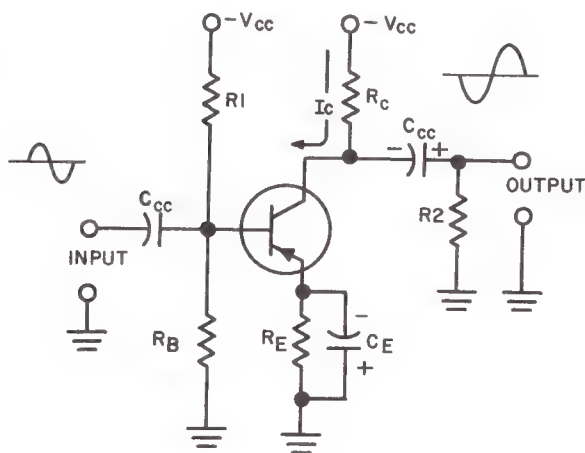Circuit Operation. The following schematic shows a conventional PNP, triode, common-emitter r-c-coupled transistor audio amplifier circuit.



R-C-Coupled Audio Amplifier

The input is shown capacitively coupled, and voltage divider R_1 , R_B provides fixed bias from the collector supply. Emitter swamping is provided by R_E for temperature stabilization; E_E is bypassed by C_E . (See the introduction to this section of the handbook for a discussion of bias arrangements, and bias stabilization methods.) Collector resistor R_C is the load across which the output voltage is developed; this voltage is applied through coupling capacitor C_{cc} to the output circuit. Resistor R_2 is the base-to-ground resistor in the next stage when cascaded amplifiers are used, or is the output load resistor (such as a headset) in single-ended stages.

Normally, the amplifier is a small-signal amplifier, with the bias fixed at the center of the transistor dynamic transfer characteristic. With no input signal a steady collector current, I_C , flows as determined by the base bias voltage. With R_1 and R_B connected across the collector supply as a voltage divider, a forward (negative) bias is developed across R_B ; this bias is sufficient to cause the quiescent value of I_C to flow, even though the collector is reverse-biased. When the input signal goes positive, assuming a sine-wave input, the forward base bias is decreased instantaneously by the amplitude of the input signal, and collector current I_C is reduced. The reduction in collector current causes the voltage across collector resistor R_C to rise toward the supply voltage, which is negative (this is exactly the reverse of vacuum-tube action); thus, a negative-swinging output signal is developed. When the input signal becomes negative, it adds to the forward base bias and causes I_C to increase. The increase in collector current through R_C produces a less negative voltage or positive swing. Therefore, the collector output follows the input signal except that it is reversed in polarity; when the input signal is positive, the output signal is negative, and vice versa. The collector output is developed across R_C between the collector and ground, and is applied through coupling capacitor C_{cc} to the base of the next stage, or to the output load.

In cascaded resistance-coupled stages the base bias resistor and base-to-emitter internal impedance of the next stage transistor offer a shunt path between coupling capacitor C_{cc} and ground. Therefore, the reactance of C_{cc} and the total parallel resistance from base to ground form a voltage divider across the collector resistor of the first stage. If the reactance of the coupling capacitor is large, the output voltage is greatly attenuated, and only a small output appears

between base and ground of the second stage. Since the reactance of C_{cc} varies inversely with frequency, the lower audio frequencies are attenuated more than the higher frequencies. For good low-frequency response the coupling capacitor is made sufficiently large in value that its reactance is very small as compared with the base-to-ground resistance. This is similar to vacuum-tube practice, where relatively small coupling capacitors (such as .001 microfarad) are satisfactory, because the vacuum-tube grid-to-ground impedance is very high. Because the transistor base-to-emitter impedance is fairly low (about 500 ohms), a coupling capacitor of 50 microfarads or more is needed to achieve the low impedance required to pass the signal without excessive attenuation. (A 50-microfarad capacitor has a capacitive reactance of approximately 30 ohms at 100 Hz.) For good low-frequency response the reactance of the coupling capacitor should always be less than one-tenth the effective base input impedance.

At the higher audio frequencies (above 20,000 Hz), the collector-to-emitter capacitance of the first stage and the base-to-emitter shunting capacitance of the second stage tend to bypass the high frequencies to ground, causing a drop in the response. This frequency-attenuating action of the transistor occurs because the width of the internal transistor PN junctions are voltage-sensitive. With higher voltages the transistor region is narrow, corresponding to the closely spaced plates of a capacitor with the associated high capacitance. The reverse bias on the collector also reduces the width of this transistor region, so that transistors are generally characterized by a high inter-electrode capacitance. For example, an audio transistor may have a collector-to-base capacitance on the order of 50 picofarads, as compared with a vacuum-tube plate-to-grid capacitance of one or more picofarads. The collector-to-emitter capacitance is usually 5 to 10 times the value of the collector-to-base capacitance (in the common-emitter circuit), as compared with 8 picofarads or less for vacuum-tube plate-to-cathode capacitance. Thus, it can be seen how the high-frequency response is affected considerably by internal transistor parameters. Of course, any shunt wiring capacitance will also add to the shunting effects of the transistor. Both low- and high-frequency compensating circuits may be used to increase the effective frequency response of the circuit, as discussed in Wideband Video Amplifier Circuits later in this section.

Over the region of 100 to 20,000 Hz, the r-c coupled amplifier has a relatively flat response, and with proper matching will afford high power and voltage gains. Hence, this form of coupling is universally employed where good audio response is required without any appreciable power output (voltage amplification). The common-base configuration is sometimes employed where better high-frequency response is desired than that provided by the common-emitter circuit, since the collector-to-base capacitance is only 1/5th to 1/10 as great.

Transistor audio amplifiers are also characterized by a high inherent noise which is greatest at the lower audio frequencies. Operation with low values of emitter current and low collector voltages, together with low values of input resistance, tends to minimize the noise. In the common-emitter circuit, degenerative effects produced by an unbypassed emitter resistor tend to increase the input resistance. Thus, it is conventional practice to use large emitter bypass capacitors in the r-c-coupled circuit to avoid any possibility of degeneration. As with the electron tube, external feedback circuits provide better response, although emitter degeneration may sometimes be used. Since fixed bias from the collector supply may be easily obtained by a simple voltage divider, it is used in both large- and small-signal applications. Self-bias is generally restricted in use to very small-signal amplifiers; otherwise, distortion and improper operation with a reduction in gain, or blocking, may occur on large signals. In the r-c-coupled amplifier, the emitter resistor functions mainly as a swamping resistor for temperature stabilization, and prevents large changes in amplification with temperature variations.

In considering the operation of the transistor r-c-coupled amplifier as compared with the electron-tube r-c-coupled amplifier, it should be clear from the above discussion that one circuit is an almost exact counterpart (dual) of the other. The difference is that transistor stages operate with low input and output impedances, at low voltages, and at very low levels of amplification, whereas electron-tube stages operate with relatively high input and output impedances, at high voltages, and at high levels of amplification. Thus, the transistor is basically a current amplifier, while the electron tube is a voltage amplifier. Consequently, the transistor requires closer matching (rather than mismatching) of impedances to produce maximum performance.

Failure Analysis.

General. When making voltage checks use a vacuum-tube voltmeter to avoid the low values of multiplier resistance employed on the low-voltage ranges of the standard 20,000 ohms-per-volt meter. Be careful also to observe proper polarity when checking continuity with an ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. A no-output condition may be caused by an open or short circuit, by improper bias or loss of collector voltage, or by a defective transistor. A voltage check will determine whether the bias and collector voltage are normal; also, a VTVM will indicate audio input and output voltages. With the few components involved, simple voltage and resistance checks will usually indicate the source of trouble. If the bias voltage divider is open because return resistor, R_B is defective, the base bias will be sufficient to cut off the transistor. With R_1 open, only contact bias exists and the transistor will very likely conduct heavily in the saturation region. If collector resistor R_C is open, there will be no voltage indication as measured between the collector and ground. If emitter resistor R_E is open, the circuit will not operate; however, if emitter bypass capacitor C_E is shorted, the circuit will operate but it will be temperature-sensitive. Likewise, if the emitter bypass capacitor is open, it may reduce the output because of degenerative feedback, but normally will not cause complete stoppage of operation. If the input coupling capacitor or the output capacitor is open, no output will result. Check the input and output circuits with an oscilloscope; disappearance of the signal will indicate the location of the defective component. If the coupling capacitor is shorted or leaky, it will affect the base bias if located at the input, but will probably not be sufficient to stop operation. On the other hand, if the output capacitor is at fault, the collector reverse bias (which is normally high as compared with the base bias) will be applied as full forward bias to the base of the next stage and will bias it heavily into saturation; thus, no output will result, and the current may be sufficient to destroy the transistor. If the coupling capacitor is leaky, the effect will depend upon the amount of leakage. With slight leakage there may be practically no observable effect, or possibly distortion; with heavy leakage there will probably be no output. Of course, if the transistor is shorted or otherwise defective, a no-output condition will occur.

A rough check of transistor operation can be made (if the transistor can be easily removed from the circuit) by measuring the forward and reverse resistance with an ohmmeter. A high reverse resistance and low forward resistance indicates that the transistor is operable, but does not indicate if the gain is normal. Be certain to observe the correct polarities.

Reduced Output. Improper bias voltage or a change in the value of a component, as well as a defective transistor can cause reduced output. If the transistor gain is low, the output will also be low. If either of the base voltage-divider bias resistors changes in value, the bias will be either too low or too high and the output will be reduced, with accompanying distortion. A simple voltmeter check will determine whether the bias is correct. If the collector resistor is too high in value, the output will be increased because of the extra voltage drop across the resistor; if the resistor is too low, in value, the output will be decreased. If the coupling capacitors are defective, a loss of output at the low-frequency end of the spectrum will result when the coupling capacitance is less than the design value. A leaky capacitor will likewise cause improper bias voltages and reduced output. Capacitors usually must have one end disconnected from the circuit before they can be tested by means of a standard capacitance analyzer (in-circuit capacitance checkers do not require this).

Distorted Output. If the base bias is too high (reduced forward bias), the transistor will operate on the lower portion of its dynamic characteristic, and the negative input peaks will be clipped (positive collector swings). Likewise, if the bias is too low (increased forward bias), the transistor will conduct heavily and operate on the upper portion of its dynamic characteristic, with corresponding clipping of the positive peaks (negative collector swings). In both cases extreme distortion will be caused. If the bias is proper but the collector voltage is not, similar effects may be caused. If the collector voltage is too high, the negative collector swing will be clipped, and if too low the positive collector swing will be clipped; in either instance heavy distortion will result. An open emitter bypass capacitor will permit degenerative feedback to occur, and, depending upon the amount, will show either as distortion or as reduced output. A change in load resistance produced by a defective collector or load resistor or by a leaky coupling capacitor (causing a heavy shunting of the

output load) usually shows as a distorted output with reduced volume because of the mismatching. Use an oscilloscope to follow the signal through the circuit and determine the point at which the waveform departs from normal. In most instances the defective component will then be apparent. Do not overlook the possibility that distortion may be occurring in a previous stage, merely being amplified by the stage under suspicion. Too large an input (overdrive) will cause both positive and negative peak clipping with distortion, just as in an electron-tube amplifier. Apply a square-wave input from a signal generator and observe the output on an oscilloscope. Frequency distortion will be shown by a sloping rise and fall time (poor high-frequency response); a sloping flat top indicates poor low-frequency response. Electron-tube techniques for locating distortion may generally be used for transistor trouble shooting if the proper voltages and polarities are employed.

R-C COUPLED PENTODE AUDIO AMPLIFIER

Application.

The R-C coupled pentode audio voltage amplifier is used to increase the amplitude of an audio-frequency signal voltage when uniform gain is required over the entire audio spectrum and when a high value of gain (up to approximately 350) is required. It is used to amplify extremely low-level signals, where a high gain per stage is required and the number of stages which can be accommodated is limited.

Characteristics.

Same characteristics as electron tube R-C coupled triode audio amplifier, with following exceptions:

Input impedance is very high, usually greater than 0.1 megohm.

Output impedance is high, and as a rule is considerably higher than that of a triode amplifier.

Voltage gain is much higher than that of a triode ampfier, ranging from 100 to 350.


Operates Class A; no grid current flows under any conditions.

Harmonic distortion in the output signal is lower, for the same value of output voltage, than that of a triode amplifier.

Circuit Analysis.

General. The R-C coupled pentode audio voltage amplifier is widely used as the input stage in a high-gain amplifier assembly, where the value of the signal input voltage is extremely low. Because its input impedance is high, it can accommodate inputs from various high-impedance, sources by direct connection, without the necessity of impedance-matching transformers to effect the connection. Such sources include crystal and high-impedance dynamic microphones, crystal vibration pickups (including phonograph pickups), and magnetic tape heads. The gain per stage of a pentode amplifier is much higher than that of a triode, and the pentode amplifier produces an output signal voltage of considerably greater amplitude than that of a triode when operated at the same plate supply voltage, E_{bb} . The total harmonic distortion contained in the output of a pentode audio amplifier is less than that of a triode audio amplifier for a given value of output (signal) voltage.

Circuit Operation. The R-C coupled pentode audio voltage amplifier is used to amplify, to high value, an input signal within the audio-frequency range, and reproduce the original waveform without appreciable distortion. The circuit of a typical amplifier of this type is shown in the following illustration. In this circuit the input signal is applied through coupling capacitor C1 to the grid of the pentode, V1. The grid is returned to ground through grid resistor R1. The pentode is operated with self-bias, with the bias being supplied by means of cathode resistor R2; the resistor is bypassed by capacitor C2 to maintain the bias at a constant average value, thereby avoiding degeneration of the amplified signal. Plate and screen voltages are supplied from the plate power supply, E_{bb} , through decoupling resistor R5 bypassed by capacitor C4, with R3 serving as the screen dropping resistor bypassed by capacitor C3 and with R4 serving as the plate load resistor. The decoupling circuit, composed of R5 and C4, serves to prevent feedback at an audio rate from the output (plate) of V1, back through the low impedance of the power supply to the plate of the previous tube, which furnishes the input signal to the grid of V1.

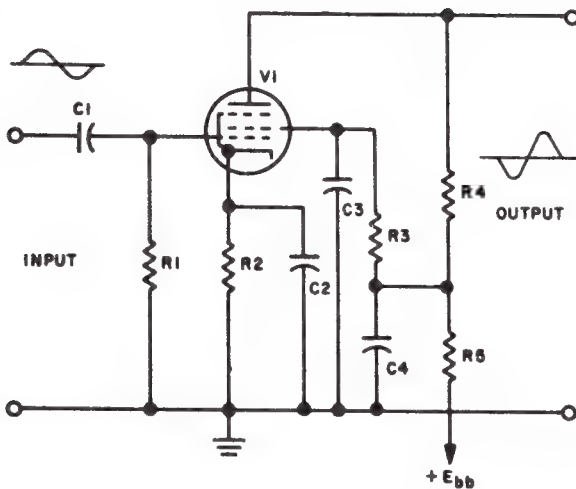

Typical R-C Coupled Pentode Audio Voltage Amplifier Circuit

An example of the use of this circuit is its application as a servo preamplifier. With a type 5840 pentode used for V1, a plate voltage supply E_{bb} of 250 volts dc, and an input signal of 400 Hz, the circuit affords a voltage amplification of 70 when the following component values are used: R1, 1 megohm; R2, 3.3K; R3, 1.5 megohm; R4, 470K; R5, 220K; C1, 0.01 μ f; C2, 30 μ f; C3, 0.1 μ f; and C4, 16 μ f.

The pentode tube used in the R-C coupled pentode audio voltage amplifier has a much higher plate resistance than a triode tube; because of this fact, the resistance value of the plate load resistor has a considerable influence on the amplification of the higher frequencies, especially at the upper frequency limit of the design bandpass. At the lower frequency limit, however, the output coupling capacitor to the following stage may have a somewhat lower capacitance value than in a comparable triode amplifier circuit, and still maintain the same low-frequency response. The effect of the value of the plate load resistor upon the frequency response, or bandpass, of the amplifier may be generalized: with a plate load of 100K, the high-frequency limit is approximately 25,000 Hz, while a plate load of 500K gives a high-frequency cutoff in the neighborhood of 5000 Hz.

Since 25,000 Hz is far beyond the normal response range of an audio-frequency amplifier, a more realistic high-frequency limit of 10,000 Hz may be obtained by using a plate load resistance of 250K.

From the above discussion it appears that, as the plate load resistance is made lower and lower, the high-frequency cutoff limit becomes higher and higher, and that it would therefore be advantageous in any case to use a low value of plate load resistance. While this is true, a low value of plate load resistance has probably a greater disadvantage: the output signal will have a low amplitude. Therefore, in order to obtain sufficient output signal voltage (amplitude), the value of the plate load resistance must be a compromise between output voltage versus high-frequency response.


In connection with the use of a pentode as a voltage amplifier, the equation $I_{load} = e_g g_m$ is often used. This expression, along with an equivalent circuit, can be derived from the equation for output voltage, e_o :

$$e_o = -\mu e_g \frac{R_L}{r_p + R_L}$$

By substituting for μ the relationship $\mu = r_p g_m$, we have:

$$e_o = e_g g_m \frac{(r_p R_L)}{(r_p + R_L)}$$

The terms in parentheses will be recognized as the total resistance of a parallel circuit of r_p and R_L . Hence, the expression suggests the following equivalent circuit. As long as the load is purely resistive, this circuit gives exactly the same results as the original equivalent circuit. If the load is reactive, however, an error is introduced in calculations of phase shift unless the plate resistance r_p is large compared to R_L (with pentode tubes r_p is often very large compared to R_L). When this is true the parallel branch r_p can be neglected, and the load current is equal to $-e_g g_m$. This speeds up calculations and is especially useful for pentode tubes when their values of r_p and μ are not accurately known.

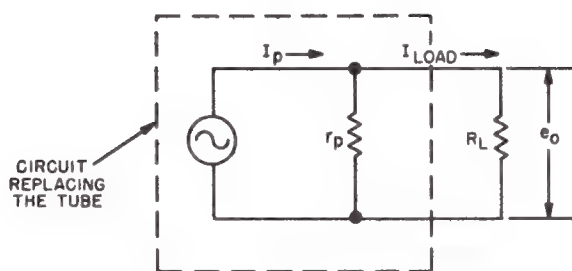

Equivalent Circuit of a Pentode Voltage Amplifier

Failure Analysis.

No Output. If an R-C coupled pentode audio voltage amplifier is defective in that no output is produced, the input signal source should first be checked to see that a signal of proper amplitude is present at the input terminals of the amplifier. The pentode tube should also be checked to insure that it is capable of operation. Plate and screen voltages at the tube socket terminals should then be measured, to determine whether the voltages are of the proper value. If no voltage is present at either the plate or the screen, the plate voltage power supply (E_{bb}) may be defective in that no output is being furnished. Another possible cause may be an open decoupling resistor R5, a shorted capacitor C4, or an open cathode resistor R2. If plate voltage is present but screen voltage is not, screen dropping resistor R3 may be open-circuited or screen bypass capacitor C3 may be shorted. On the other hand, if screen voltage is present without plate voltage, an open plate load resistor R4 is indicated. If, however, both plate and screen voltages are normal and no output is obtained, an open input coupling capacitor C1 could be the cause of the trouble.

Reduced or Unstable Output. If the R-C coupled pentode audio voltage amplifier is defective in that a reduced value of output or instability is evident, the input signal should be checked to see that it is of sufficient amplitude, yet not of excessive amplitude that would overload the amplifier stage. If the input signal is present and has normal amplitude, the trouble may be due to a leaky coupling capacitor C1, which might allow a positive voltage from the preceding stage to be impressed on the grid of V1 thereby

introducing distorting. An open or extremely high resistance grid resistor R1 would tend to cause intermittent operation ("motorboating"); if this condition prevails, the grid resistor should be replaced. A reduced value of output could also be caused by an open cathode bypass capacitor C2 or by an open screen bypass capacitor C3, either of which would cause the circuit to be degenerative. Another cause of low output could be an open screen resistor R3, which would make the tube attempt to operate with plate voltage but without screen voltage. A decreased value of screen voltage, due to a leaky screen bypass capacitor C3, could cause low output. A decreased value of plate and screen voltage, due to a defective power supply E_{bb} , could likewise be responsible for low output. Finally, there is a remote possibility that low heater (filament) voltage, brought about by a loose connection or an overloaded circuit, may be the cause of a low value of output.

IMPEDANCE-COUPLED AUDIO AMPLIFIER (ELECTRON TUBE)

Application.

The impedance-coupled triode audio voltage amplifier is used to increase the amplitude of an audio-frequency signal where wideband response is not desired, and higher gain than that of the wideband amplifier is desired.

Characteristics.

Frequency response is linear over a small band of frequencies, for example from 200 to 10,000 Hz, depending upon the design.

Input is normally an a-f signal of small amplitude.

Input impedance is high, usually more than 50,000 ohms.

Output impedance is high (on the same order as the input), and is suitable for cascaded stages or magnetic output devices requiring little power.

Output signal is inverted in polarity from that of the input signal.

Operates class A biased; no grid current flows under normal conditions.

Cathode (self) bias is normally used, but fixed bias may be used in certain applications.


Requires less plate voltage than that of an equivalent R-C-coupled amplifier to produce an equivalent

output. In this respect it is similar to the transformer-coupled amplifier.

Circuit Analysis.

General. The impedance-coupled triode audio voltage amplifier resembles an R-C-coupled audio amplifier (previously discussed), except that an iron-core inductance (choke), instead of a resistor, is used as the plate load. It is sometimes referred to as a *choke-coupled* amplifier. Because the choke acts as a reactance at ac frequencies, the impedance determines the drop across the plate load. However, since the dc resistance of the choke coil is low, only a small dc voltage drop occurs across the choke. As a result, a much lower plate supply voltage can be used to provide the same effective plate voltage (as compared with an R-C amplifier).

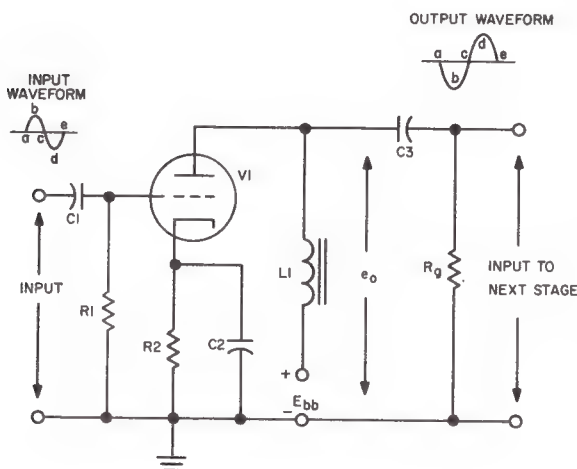Circuit Operation. The schematic of a typical impedance-coupled triode audio voltage amplifier is shown in the following illustration.



Typical Impedance-Coupled Triode Audio Voltage Amplifier

As can be seen, the input signal is capacitively coupled through C1 to the grid of tube V1. Coupling capacitor C1 and grid resistor R1 form an audio voltage divider. The output of this voltage divider is the voltage which appears across R1, and is the

signal voltage applied to the grid of V1. Capacitor C1 also acts as a dc blocking capacitor to prevent the plate voltage of a preceding stage or any dc voltage existing in the input circuit from adversely biasing V1. The reactance of C1 to an audio-frequency signal is much smaller than R1; thus little signal is lost across the capacitor. Resistor R2 provides cathode bias through average plate current flow, and capacitor C2 bypasses the resistor to prevent degenerative effect. Choke coil L1 is the plate load impedance across which the output voltage, e_o , is developed; L1, C3, and Rg form the impedance-coupling network.

With no signal applied, static plate current flows through cathode bias resistor R2, and provides class A bias. A plate voltage drop across choke coil L1 is produced by the dc coil resistance. This drop is constant, regardless of whether a signal is present; thus it produces no output voltage since it cannot pass through coupling capacitor C3. When a positive-going input signal is applied to the grid of tube V1, it reduces the effective grid bias, and the plate current increases instantaneously. Assuming a sine-wave input, as the signal raises, the plate current also increases until the positive peak of the input cycle is reached. During this half of the cycle (from point a to point b on the output waveform), a continuously increasing voltage drop (negative swing) occurs across the load produced by the reactance of L1. This is the audio output voltage which is applied to coupling capacitor C3. With a positive-going input, a negative-going output is developed by the increasing plate current, which drops the voltage across the impedance offered by choke L1. When the grid voltage reaches the positive crest, the plate voltage is at a minimum value (point b on the output waveform). As the grid voltage recedes, plate current decreases. Consequently, the voltage drop across L1 becomes less and less, reaching zero (point c on the waveform) at the completion of the positive half-cycle of the input signal.

As the input signal now swings negative, it adds to the applied bias produced by normal plate current flow, and reduces the plate current instantaneously. During the negative-going half-cycle of input signal, the plate current continuously decreases (point c to point d) until the negative crest is reached at point d on the input waveform. During this portion of the half-cycle, the plate voltage rises toward the source voltage and produces the positive-going portion of the output signal. At the negative crest (point d on the

input waveform), the input signal is equal to the bias, but cutoff is not reached because the initial bias is less than half of the cutoff value to insure that the tube is operated over the linear portion of its grid-voltage plate-current characteristic curve. At this time the plate voltage is equal to the source voltage less the small dc drop in the plate choke. As the negative input signal swings positive and returns to the zero level, the plate current continuously increases (since the effective grid bias is reduced), and the voltage drop produces across L1 increase. Plate voltage decreases from the maximum value to the static level (point d to e on the output waveform).

Since the input signal can never exceed the bias voltage without producing distortion by driving the grid positive, it can be seen that the peak input voltage is only on the order of a few volts or less. On the other hand, the plate swing is over a range of 100 to 200 volts, depending upon tube characteristics, supply voltages available, and bias values. Since the plate voltage swing is actually the output voltage which is applied to the coupling capacitor, it is easy to understand how a voltage gain from input to output of 100 or greater can be obtained. Because the output voltage reaches a negative peak when the input voltage reaches a positive peak, and vice versa, at any particular instant of time they are considered to be 180 degrees out of phase with each other. Actually, they are of opposite polarity and of the same phase because the current and voltage are both in phase (at extremely low frequencies there may be an actual phase shift). Since only a voltage output is desired, it is unnecessary to match the load impedance to the tube impedance. In fact, exactly the opposite approach is used; the load impedance is always selected to be much larger than the plate resistance (for a triode) so that the greatest output voltage is obtained. Because both positive and negative plate current swings are identical, assuming a sine-wave input, the average current remains the same and is not affected by the input signal. Therefore, the cathode current can be used to provide a steady self-bias (fixed bias may be used if desired).

For ease of discussion, the frequency spectrum over which the impedance-coupled amplifier operates can be divided into three convenient ranges: low-, middle- and high-frequency. The gain drops off at the low frequencies because the impedance of the choke coil becomes less as the frequency is reduced. To increase the low-frequency response, a large number

of turns are used to provide a greater inductance. However, the distributed capacitance produced by a coil winding of many turns creates a large shunting capacitive reactance, which causes a drop in the high-frequency response. Over the middle-frequency range the gain is more uniform. It is limited only by the parallel combination of tube plate resistance, plate choke-coil impedance, and the shunting effect of the input resistance (grid resistor) of the following stage. Generally speaking, the plate choke-coil-impedance over the middle-frequency range is very high as compared with either the tube plate resistance or the input resistance of the next stage; thus maximum gain is obtained. The gain of the impedance-coupled amplifier drops over the high-frequency range mainly because of the large distributed capacitance of the choke-coil turns, which effectively shunts the load to ground and offers a low-impedance path to high frequencies.

Failure Analysis.

No Output. A no-output condition could be caused by no input signal, an open-circuited condition, lack of plate or filament voltage, a short-circuited condition, or defective tube. The presence or absence of an input signal can be determined by making an oscilloscope or vacuum-tube voltmeter check at the input. An open-circuited or short-circuited condition can be localized to the defective portion of the circuit by making voltage measurements with a high-resistance voltmeter to determine whether the proper filament, cathode or grid, and plate voltages exist. In many instances open filaments can easily be located by observing that the filament does not light and that the tube feels cold to the touch. Where improper or no voltage exists, check the power supply voltage to determine whether the fault is in the amplifier or in the power supply. If there is normal voltage at the output of the power supply, the trouble is in the amplifier. Lack of plate voltage then indicates a defective plate choke, L1. If the choke is open, there will be no voltage between the plate and ground. If it is shorted, there will be no voltage drop across the choke. If there is a short between the plate and ground, the power supply voltage will be dropped entirely across the choke. Removing the tube will clear the short if the tube is defective; otherwise, it can be assumed that the choke insulation has failed and that there is a dc path through the core to ground. A short-circuit condition is usually indicated

by burning or charring of the parts involved, and sometimes can be easily located by a visual examination. If such an examination does not reveal the trouble, it will be necessary to remove the power, discharge the B+ supply, and then remove the part and make a resistance check on it. A short-circuited condition is indicated by a low resistance between points that normally have a higher resistance.

No output can also be caused by an open coupling (input) capacitor, C1. If the signal is present on the input side (as observed on an oscilloscope) but not on the grid side, either the capacitor is open or the grid side is shorted to ground. Use an in-circuit capacitance tester to determine whether the capacitor is defective. If the trouble is not revealed by this test, it will be necessary to disconnect the capacitor from the circuit and check it with a standard type of capacitance bridge. Output coupling capacitor C3 can also cause a no-output indication if it is open; check it in a similar manner, considering the plate side as the input side and the side connected to R_g as the output side. Unless shorted or open-circuited, a defective electron tube will usually cause reduced or distorted output rather than none at all.

Reduced or Unstable Output. Reduced output is usually caused by lack of proper plate or grid voltages; unstable output is often caused by oscillation and intermittent circuit operation. Use a high-impedance voltmeter to check the grid or cathode bias voltage. A low bias voltage will cause a drop in output because heavy plate current causes peak clipping effects and distortion. A high bias will also cause lower output. If cathode bypass capacitor C2 is open, sufficient degeneration will be produced to appreciably reduce the output. Poor joint (soldering, etc) will create a high-resistance condition; if the poor joint is in the plate circuit, lower output will result. A leaky coupling capacitor (C1) will improperly bias the stage, causing a reduction in output. If coupling capacitor C3 is leaky, it will improperly bias the next stage, draw more than normal plate current, and cause a dc voltage drop in L1; this voltage drop will reduce the effective plate voltage and the output, depending upon the amount of leakage. When normal voltage appears on the tube elements and the output is still below normal, the tube is probably defective. A gassy tube can cause high grid current, thus producing excessive bias with a reduction in output after a short period of operation. Normal output with the set initially operated, followed by a progressively

decreasing output shortly thereafter is indicative of such a condition. Circuit oscillation at r-f frequencies will also cause the output to drop and show up as a fuzzy pattern on the oscilloscope. If the oscillation is at audio frequencies, a howl or squeal will be apparent in the output, and will be indicated on the oscilloscope as a single frequency.

Unstable output can result from an intermittently open bypass capacitor in the cathode or plate circuit. Motor-boating (oscillating at a very low frequency) is sometimes caused by feedback through improper coupling of the grid and plate circuits or through common impedance coupling in the power supply; this is especially true with high-gain cascaded stages. Feedback through the power supply is usually caused by a defective bypass capacitor in the B+ line. This condition commonly occurs when electrolytic capacitors age and dry out, thus losing their capacitance gradually.

Distorted Output. Distorted output may be caused by poor frequency response, the introduction of hum, or improper grid bias. Distorted output due to poor frequency response is obvious when audible monitoring sources are available. To locate the distortion, use an oscilloscope and a sine-wave generator to follow the signal path through the circuit. Observing where the waveform departs from normal will indicate the portions of the circuit involved. A square-wave generator may also be used. With a square-wave signal applied, a sloping leading edge indicates lack of high-frequency response, while a sloping flat top indicates lack of low-frequency response. Since a square wave is made up of many sine-wave frequencies, the application of a 2000 to 3000-Hz square wave will indicate the relative harmonic response over a range up to 5 to 10 times this frequency. Impedance coupling will normally produce a frequency response intermediate between that of resistance-coupled and transformer-coupled stages.

Hum distortion can be observed directly on an oscilloscope. When existing on the power supply leads, it indicates lack of sufficient power supply filtering. If it is not on the power leads, but is evident on the grid, plate, or cathode leads, check for induced hum pickup due to the nearness of grid leads to ac leads.

Improper bias is also a common cause of distortion; coupled with excessive drive, it causes the peaks or troughs of the voice signal to be clipped off. In a very weak tube, leak of sufficient filament emission

can cause distortion on the peaks of amplification because of inability to supply sufficient peak current. While voltage measurements will determine whether the grid and plate voltages are correct, an oscilloscope must be used to observe the waveform. A distortion percentage of from 2 to 5 percent is normally considered acceptable in commercial audio amplifiers.

IMPEDANCE-COUPLED AUDIO AMPLIFIER (SEMICONDUCTOR)

Application.

The impedance-coupled transistor audio amplifier is used where higher gain than the r-c coupled stage is desired with better response than that provided by transformer coupling.

Characteristics.

Uses common emitter circuit for higher gain. Operates Class A for linear operation and minimum distortion.

Usually amplifies small signals, but can be designed to handle large signals in cascaded stages.

Is fixed biased from the collector supply, but may use self bias in some applications.

Emitter swamping is normally used for thermal stabilization.


Gain is fairly uniform over a range of approximately 100 to 15,000 Hz or more.

Both voltage and power gain are high.

Circuit Analysis.

General. The impedance-coupled transistor amplifier is similar in a general sense to the impedance-coupled electron tube amplifier previously discussed in this section of the handbook. Use of the common (grounded) emitter circuit allows use of the analogy that the base of the transistor is equivalent to the electron tube grid, the emitter equivalent to the tube cathode, and the collector equivalent to the tube plate. Thus it is clear from the following schematic that the two impedance coupled circuits are practically identical. Any differences are due to the transistor internal parameters and the matching requirements to obtain maximum output with minimum distortion.

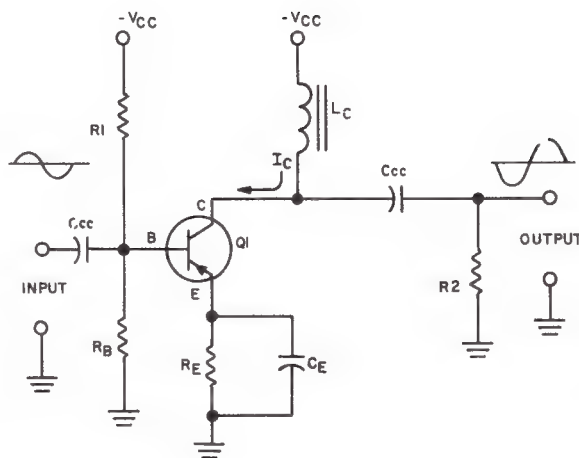Circuit Analysis. The following schematic is that of a conventional PNP, triode, common-emitter impedance-coupled transistor audio amplifier circuit.



Impedance-Coupled Audio Amplifier

The input is shown capacitively coupled, and voltage divider $R1$, R_B provides fixed bias from the collector supply. Emitter swamping is provided by R_E for temperature stabilization; R_E is bypassed by C_E . (See the introduction to this section of the handbook for a discussion of bias arrangements and bias stabilization methods.) Collector impedance L_C is the load across which the output voltage is developed; this voltage is applied through coupling capacitor C_{cc} to the output circuit. Resistor $R2$ is the base-to-ground resistor in the next stage when cascaded amplifiers are used, or is the output load resistor (such as a headset) in single-ended stages. (In some applications $R2$ may be replaced by an iron-cored inductor similar to L_C .)

Normally, the amplifier is a small-signal amplifier with the bias fixed at the center of the transistor dynamic transfer characteristic. With no input signal a steady collector current, I_C , flows as determined by the base bias voltage. With $R1$ and R_B connected across the collector supply as a voltage divider, a forward (negative) bias is developed across R_B ; this bias is sufficient to cause the quiescent value of I_C to flow, even though the collector is reverse-biased.

When the input signal goes positive, assuming a sine wave input, the forward base bias is decreased instantaneously by the amplitude of the input signal, and collector current I_C is reduced. The reduction in collector current causes the voltage across collector impedance L_C to decrease and rise toward the supply voltage, which is negative (this is exactly the reverse

of vacuum-tube action); thus, a negative-swinging output signal is developed. When the input signal becomes negative, it adds to the forward base bias and causes L_C to increase. The increase in collector current through L_C produces a large voltage drop across the impedance, reduces the negative collector voltage and produces a positive swing. Therefore, the collector output follows the input signal except that it is reversed in polarity; when the input signal is positive, the output signal is negative, and vice versa. The collector output is developed across the impedance of L_C between the collector and ground, and is applied through coupling capacitor C_{cc} to the base of the next stage, or to the output load.

In cascaded impedance-coupled stages the base bias resistor and base-to-emitter internal impedance of the next stage transistor offer a shunt path between coupling capacitor C_{cc} and ground. Therefore, the reactance of C_{cc} and the total parallel resistance (or impedance) from base to ground form a voltage divider across the collector resistor of the first stage. If the reactance of the coupling capacitor is large, the output voltage is greatly attenuated, and only a small output appears between base and ground of the second stage. Since the reactance of C_{cc} varies inversely with frequency, the lower audio frequencies are attenuated more than the higher frequencies. For good low-frequency response the coupling capacitor is made sufficiently large in value that its reactance is very small as compared with the base-to-ground resistance or impedance. This is similar to vacuum-tube practice, where relatively small coupling capacitors (such as .001 microfarad) are satisfactory, because the vacuum-tube grid-to-ground impedance is very high. Because the transistor base-to-emitter impedance is fairly low (about 500 ohms), a coupling capacitor of 50 microfarads or more is needed to achieve the low impedance required to pass the signal without excessive attenuation. (A 50-microfarad capacitor has a capacitive reactance of approximately 30 ohms at 100 Hz.) For good low-frequency response the reactance of the coupling capacitor should always be less than one-tenth the effective base input impedance.

In those circuits where an impedance replaces R_2 the coupling capacitor and inductor can be made to series-resonate at a low frequency to provide bass boost.

At the higher audio frequencies (above 15,000 Hz), the collector-to-emitter capacitance of the first stage and the base-to-emitter shunting capacitance of

the second stage together with the large distributed capacitance from turn to turn of the collector-inductance tends to bypass the high frequencies to ground, causing a drop in the response. The frequency-attenuating action produced by the transistor occurs because the width of the internal transistor PN junctions are voltage-sensitive. With high voltage the transition region is narrow, corresponding to the closely spaced plates of a capacitor with the associated high capacitance. The reverse bias on the collector also reduces the width of this transition region, so that transistors are generally characterized by a high interelectrode capacitance. For example, an audio transistor may have a collector-to-base capacitance on the order of 50 picofarads, as compared with a vacuum-tube plate-to-grid capacitance of one or more picofarads. The collector-to-emitter capacitance is usually 5 to 10 times the value of the collector-to-base capacitance (in the common-emitter circuit), as compared with 8 picofarads or less for vacuum-tube plate-to-cathode capacitance. Thus, it can be seen how the high-frequency response is affected considerably by internal transistor parameters. Of course, any shunt wiring capacitance and that of the collector inductance will also add to the shunting effects of the transistor. Both low- and high-frequency compensating circuits may be used to increase the effective frequency response of the circuit, as discussed in Wideband Video Amplifier Circuits later in this section.

Over the region of 100 to 15,000 Hz, the impedance-coupled amplifier has a relatively flat response, and with proper matching will afford high power and voltage gains. Hence, this form of coupling is employed where good audio response is required with a moderate power output (for high output transformer-coupling is used). The common-base configuration is sometimes employed where better high-frequency response is desired than that provided by the common-emitter circuit, since the collector-to-base capacitance is only 1/5 to 1/10 as great.

Transistor audio amplifiers are also characterized by a high inherent noise which is greatest at the lower audio frequencies. Operation with low values of emitter current and low collector voltages, together with low values of input resistance, tends to minimize the noise. By using an inductor in place of the base-to-ground resistor (R_B or R_2 in the schematic) a very low input resistance, and a lower noise figure over that of the r-c coupled amplifier is obtained. In the

common-emitter circuit, degenerative effects produced by an unbypassed emitter resistor tend to increase the input resistance. Thus, it is conventional practice to use large emitter bypass capacitors to avoid any possibility of degeneration. As with the electron tube, external feedback circuits provide better response, although emitter degeneration may sometimes be used. Since fixed bias from the collector supply may be easily obtained by a simple voltage divider, it is used in both large-an-small-signal applications. Self-bias is generally restricted in use to very small-signal amplifiers; otherwise, distortion and improper operation with a reduction in gain, or blocking, may occur on large signals. The emitter resistor functions mainly as a swamping resistor for temperature stabilization, and prevents large changes in amplification with temperature variations.

In considering the operation of the transistor impedance-coupled amplifier as compared with the electron-tube impedance-coupled amplifier, it should be clear from the above discussion that one circuit is an almost exact counterpart (dual) of the other. The difference is that transistor stages operate with low input and output impedances, at low voltages; and at very low levels of amplification, whereas electron-tube stages operate with relatively high input and output impedances, at high voltages, and at high levels of amplification. Thus, the transistor is basically a current amplifier, while the electron tube is a voltage amplifier. Consequently, the transistor requires closer matching (rather than mis-matching) of impedances to maximum performance.

Failure Analysis.

General. When making voltage checks use a vacuum tube voltmeter to avoid the low values of multiplier resistance employed on the low-voltage ranges of the standard 20,000 ohms-per-volt meter. Be careful also to observe proper polarity when checking continuity with an ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. A no-output condition may be caused by an open or short circuit, by improper bias or loss of collector voltage, or by a defective transistor. A voltage check will determine whether the bias and collector voltages are normal; also a VTVM will indicate audio input and output voltages. With the few components involved, simple voltage and resistance checks will usually indicate the source of trouble. If

the bias voltage divider is open because return resistor, R_B is defective, the base bias will be sufficient to cut off the transistor. With $R1$ open, only contact bias exists and the transistor will very likely conduct heavily in the saturation region. If collector inductor L_C is open there will be no voltage measured between the collector and ground. If emitter resistor R_E is open, the circuit will not operate; however, if emitter bypass capacitor C_E is shorted, the circuit will operate but it will be temperature-sensitive. Likewise, if the emitter bypass capacitor is open, it may reduce the output because of degenerative feedback, but normally will not cause complete stoppage of operation. If the input coupling capacitor or the output capacitor is open, no output will be obtained. Check the input and output circuits with an oscilloscope; disappearance of the signal will indicate the location of the defective component. If the coupling capacitor is shorted or leaky, it will affect the base bias if located at the input, but will probably not be sufficient to stop operation. On the other hand, if the output capacitor is at fault, the collector reverse bias (which is normally high as compared with the base bias) will be applied as full forward bias to the base of the next stage and will bias it heavily into saturation; thus, no output will result, and the current may be sufficient to destroy the transistor. If the coupling capacitor is leaky, the effect will depend upon the amount of leakage. With a slight leakage there may be practically no observable effect, or possibly distortion; with heavy leakage there will probably be no output. Of course, if the transistor is shorted or otherwise defective, a no-output condition will occur. A rough check of transistor operation can be made (if the transistor can be easily removed from the circuit) by measuring the forward and reverse resistances with an ohmmeter. A high reverse resistance and low forward resistance indicates that the transistor is operable, but does not indicate if the gain is normal. Be certain to observe the correct polarities.

Reduced Output. Improper bias voltage or a change in the value of a component, as well as a defective transistor can cause reduced output. If the transistor gain is low, the output will also be low. If either of the base voltage-divider bias resistors changes in value, the bias will be either too low or too high and the output will be reduced, with accompanying distortion. A simple voltmeter check will determine whether the bias is correct. If the collector inductor develops a high resistance, the output will be de-

creased because of the extra dc voltage drop across the choke. If the coupling capacitors are defective, a loss of output at the low-frequency end of the spectrum will result when the coupling capacitance is less than the design value. A leaky capacitor will likewise cause improper bias voltages and reduced output. Capacitors usually must have one end disconnected from the circuit before they can be tested by means of a standard capacitance analyzer (in circuit capacitance checkers do not require this).

Distorted Output. If the base bias is too high (reduced forward bias), the transistor will operate on the lower portion of its dynamic transfer characteristic, and the negative input peaks will be clipped (positive collector swings). Likewise, if the bias is too low (increased forward bias), the transistor will conduct heavily and operate on the upper portion of its dynamic transfer characteristic, with corresponding clipping of the positive peaks (negative collector swings). In both cases extreme distortion will be caused. If the bias is proper but the collector voltage is not, similar effects may be caused. If the collector voltage is too high, the negative collector swing will be clipped, and if too low the positive collector swing will be clipped; in either instance heavy distortion will result. An open emitter bypass capacitor will permit degenerative feedback to occur, and, depending upon the amount, will show either as distortion or as reduced output. A change in load resistance produced by a defective collector choke or load resistor, or by a leaky coupling capacitor (causing a heavy shunting of the output load) usually shows as a distorted output with reduced volume because of the mismatching. Use an oscilloscope to follow the signal through the circuit and determine the point at which the waveform departs from normal. In most instances the defective component will then be apparent. Do not overlook the possibility that distortion may be occurring in a previous stage, merely being amplified by the stage under suspicion. Too large an input (overdrive) will cause both positive and negative peak clipping with distortion, just as in a electron-tube amplifier. Apply a square-wave input from a signal generator and observe the output on an oscilloscope. Frequency distortion will be shown by a sloping rise and fall time (poor high-frequency response); a sloping flat top indicates poor low-frequency response. Electron-tube techniques for locating distortion may generally be used for transistor trouble shooting if the proper voltages and polarities are employed.

TRANSFORMER-COUPLED AUDIO AMPLIFIER (ELECTRON TUBE)

Application.

The transformer-coupled triode audio voltage amplifier is used principally for the development of large a-f voltage outputs with a minimum number of amplifier stages and for phase inversion to drive a push-pull amplifier. The limitations of frequency response generally restrict the use of transformer coupling to audio circuits, which do not require an exceptionally wide bandpass or frequency response, but do require large voltage outputs.

Characteristics.

Utilizes low plate-resistance triodes (7500 to 15,000 ohms) with amplification factors of from 8 to 20.

The transformer step-up ratio usually does not exceed 3:1 for good-quality audio. However, much higher ratios are sometimes employed to obtain extreme gain with a sacrifice of frequency response.

Operate Class A; no grid current flows under normal conditions.

Frequency response is linear only over a relatively narrow band of frequencies (approximately 200 to 10,000 Hz).

Cathode bias (self-bias) is normally used, but fixed bias may be used of desired.


Output signal may be phased so that it is of the same polarity and phase as that of the input signal, or opposite as desired.

Circuit Analysis.

General. The transformer-coupled triode audio voltage amplifier utilizes the transformer as a combined plate loading and coupling device. It is the primary of the transformer which serves as the plate load, while the secondary functions as the coupling element. The amplified version of the input signal is developed across the transformer primary. Assuming that the primary impedance is large as compared with the plate resistance of the triode, the voltage developed in the transformer primary is approximately equal to the amplification factor (μ) of the tube multiplied by the input signal. Therefore, the induced signal in the transformer secondary, which is applied to the following stage, is approximately equal to μN , where N represents the step-up turns ratio between the primary and secondary of the transformer.

Transformer coupling has several distinct advantages over either R-C or impedance coupling. A lower value of plate supply voltage can be used, as compared with that of an R-C coupled stage, since the dc resistance of the primary winding is small. The secondary winding of the transformer, when center-tapped, can be used to supply two grid voltages 180 degrees out of phase to a push-pull amplifier, or two in-phase outputs for push-pull operation. The impedance-matching properties of the transformer may also be utilized if needed. Since the primary and secondary of the transformer are not connected together, the following stage (or the output device is isolated from the dc plate voltage of the amplifier stage, eliminating the need for an output network (such as a grid resistor and coupling capacitor), thus effecting a reduction of components. The transformer also has several disadvantages. Its cost is high, and it has large bulk and weight. Additional shielding is also required to prevent the stray fields introduced by the transformer from interfering with the operation of other stages, or causing unwanted feedback within the stage.

Circuit Operation. A schematic diagram of a typical transformer-coupled audio voltage amplifier with a high-impedance input is shown in the accompanying figure. C1 is the input blocking and coupling capacitor, and R_g is the grid return resistance. Resistor R_K is the cathode bias resistor, bypassed by C_K to prevent degeneration. Refer to the introduction to this section of the handbook for a discussion of cathode biasing methods. Transformer T1 is the plate input and output transformer, coupling the output to the next stage or to the load.

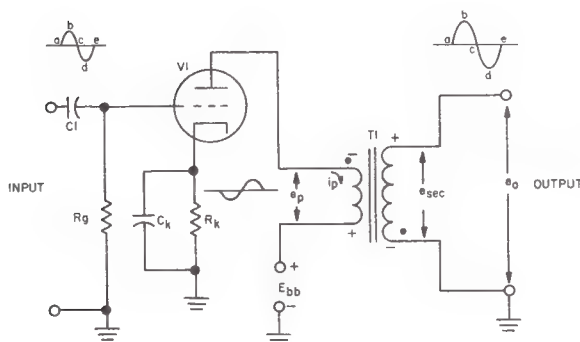

Typical Transformer-Coupled Audio
Voltage Amplifier

As can be seen from the schematic, the input signal is capacitively coupled through C1 to the grid of tube V1. Coupling capacitor, C1, and grid resistor, R_g , form an audio voltage divider. The output of this voltage divider is the signal voltage applied to the grid of V1. Capacitor C1 also acts as a dc blocking capacitor to prevent the plate voltage of a preceding stage, or any dc voltage existing in the input circuit, from adversely biasing V1. The reactance of C1 to an audio frequency signal is much smaller than $R1$; thus little signal is lost across the capacitor.

With no signal applied, static plate current flows through cathode resistor P_k and provides Class A bias. A plate voltage drop (E_p) across the primary of transformer T1 is produced by the dc coil resistance. This small voltage drop is constant, regardless of whether or not a signal is present; and produces no output voltage since it is not connected to the secondary, but does reduce the available plate voltage by a small amount. When a positive-going input signal is applied to the grid of tube V1, it reduces the effective grid bias, and the plate current increases instantaneously. Assuming a sine-wave input, as the signal rises the plate current also increases, until the positive peak of the input cycle is reached. During this half of the cycle (from point a to point b on the output waveform), a continuously increasing voltage drop (negative swing) occurs in the primary as the constantly increasing plate current flows through the load impedance (consisting of the primary reactance plus the reflected load from the secondary). The increasing plate current induces a voltage (e_{sec}) in the secondary of T1 which is the output voltage (e_o). When the secondary is properly connected (phased), the input signal and the output signal are in phase with each other, otherwise they remain out of phase. When the grid input voltage reaches a positive crest at point b on the waveform, the drop across the primary of T1 is at a negative maximum, and is 180 degrees out of phase with the input, causing the effective plate voltage to reach its minimum value (the plate current is now at a maximum). As the grid input voltage now recedes towards zero, the effective bias is continuously reduced (made more negative), causing the plate current also to reduce. The reduction of plate current changes the direction of the magnetic field produced around the transformer primary, and induces an oppositely polarized voltage in the secondary of T1. While the primary voltage is positive-going, the secondary voltage is negative-going. When the

sine-wave signal on the grid reaches point c on the waveform, the positive half-cycle of operation is completed and the tube is again at its quiescent point. Now, the grid signal continues to increase in a negative direction and adds to the cathode bias to make the effective bias still more negative, and reduces plate current flow below quiescent value. This action continues until the negative crest is reached at point d on the waveform. Since the plate voltage is increasing toward the supply value while the plate current is decreasing, at point a the plate voltage is maximum, and the primary voltage drop is positive and maximum also. Because the induced secondary voltage is opposite that of the primary, the output is a maximum negative voltage (it is in-phase with the input). As the grid input signal again reverses direction and falls back towards zero, the effective grid bias once again is decreased and becomes positive-going. Consequently the plate current increases towards quiescent or zero value, and in changing direction it again changes the direction of the field around T1 primary. Thus, a positive-going voltage is again induced in the secondary to complete the negative half-cycle of operation.


For convenience and ease of discussion, the transformer is represented by three equivalent circuits in the accompanying figure. Part A represents the low-frequency range (below 200 Hz), part B represents the middle-frequency range 200 to 8000 Hz, and part C

represents the high-frequency range (8000 to 20,000 Hz).


In part A of the figure, μe_g is considered to be an ac generator which represents the amplified output voltage of triode V1; r_p represents the ac plate resistance of the tube, and L_p represents the inductance of the transformer primary. The dc resistance of the primary winding, which is normally small, can be considered as included in r_p . L_p and r_p form a voltage divider, with the output voltage taken from across L_p . At low signal frequencies, the reactance of L_p becomes small; thus most of the developed voltage appears across r_p , thereby decreasing the voltage dropped across the primary, and hence the output voltage. For a given value of inductance, the lower the frequency the less the output voltage.

In part B of the figure, the reactance of L_p is considered very large as compared with r_p . Consequently the voltage dropped across r_p is much smaller than that developed across L_p by generator μe_g . The magnitude of the output voltage is determined by the tube amplification factor, the plate resistance, the amplitude of the applied signal voltage, and the turns ratio of the transformer. It is over this frequency range that the response is most uniform and the gain is maximum.

In part C of the figure, C_d represents the distributed capacitance between the windings of transformer T1 and interelectrode, stray, and wiring capacitances. The total distributed capacitance, which is appreciably large, shunts the higher frequencies to ground, since its reactance decreases with increasing frequency. L_e represents the equivalent inductance of the transformer (both primary and secondary). The value of L_e depends on the leakage flux and the amount of mutual coupling between the windings. This inductance, together with C_d in the equivalent circuit, forms a series-resonant circuit which resonates at some high audio frequency. At and near resonance, the magnitude of the voltage across C_d is extremely large. If the applied frequency is raised above resonance, the reactance of C_d decreases; hence the output voltage, e_o , decreases. The following figure, a typical response curve, shows a relatively uniform middle-frequency response, a gradual "rolloff" at low frequencies, and a sharper decay at high frequencies (which is preceded by a resonant peak).

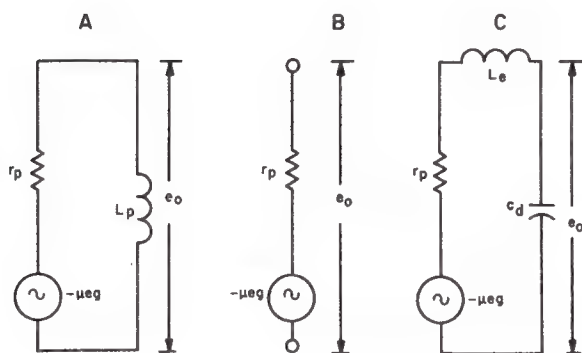

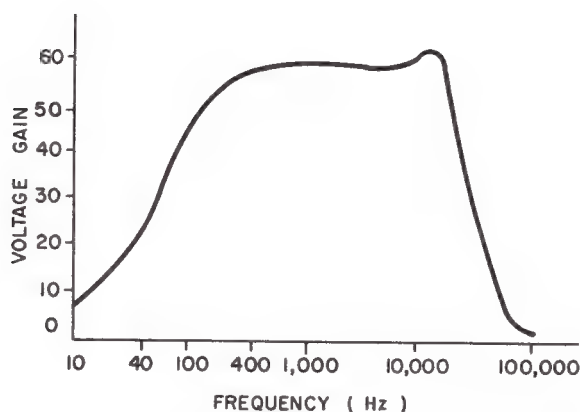Transformer-Coupled Amplifier,
Equivalent Circuits



Typical Response Curve of A Transformer-Coupled Amplifier

In practice, the gain of a so-called "flat response" transformer varies not less than 1 dB and sometimes as much as 3 dB or more over the range of 200 to 10,000 Hz.

Failure Analysis.

No Output. Generally speaking, a no-output condition is caused by the lack of an input signal, an open-circuited condition by the lack of plate or filament voltage, a short-circuited condition, or by a defective tube. The presence of an input signal may be determined by using an oscilloscope or vacuum-tube voltmeter to check the input. An open-circuited condition can be localized to the defective portion of the circuit by using a high-resistance voltmeter to determine whether filament, cathode, grid, and plate voltages exist and are normal. Open filament circuits can sometimes be spotted by noting that the filament does not light and that the tube feels cold to the touch. When a lack of voltage is found, the source (power-supply) voltage should be checked to determine whether the voltage is present; if so, the fault is in the amplifier and not in the power supply. In any case, a lack of voltage indicates either a short-circuit or an open circuit in the associated component. For example, when B+ is present at the supply end of the transformer primary but not at the plate, T1 is open. If the voltage between the primary and ground is equal on both the supply-side and the plate side, there is no voltage drop across the primary coil. Therefore, either the plate current drain is too little

(with the possibility of cutoff bias), or, with normal current drain, a short-circuited primary is indicated. Where the primary resistance is known, as resistance check with the B+ supply off and the filter capacitors discharged will indicate whether the transformer is defective. Usually, a short-circuited condition is evidenced visually by burning or charring of the parts involved.

When all voltages appear normal and an input signal is present, but there is still no output, it is obvious that tube V1 is at fault. Defects in the tube develop with age, and contribute to below-normal circuit operation, in the form of a low or distorted output rather than no output. However, vibration or excessive voltage can cause the tube to become open or shorted; therefore, this possibility must be considered. Indiscriminate replacement of tubes should be avoided.

Reduced or Unstable Output. Reduced output is usually caused by a lack of proper grid and plate voltages, or low filament emission, while unstable output is usually caused by oscillation or intermittent functioning of circuit components. Check the bias voltage on the grid (or cathode) to determine that it is normal. A low fixed bias voltage can cause reduced output due to heavy plate current and peak clipping effects; these symptoms are not applicable to self-bias, because with this circuit arrangement heavy plate current will increase the bias; thus the circuit tends to be self-compensating. A high bias will cause reduced output. An open cathode by-pass capacitor (C_k) can cause sufficient degeneration to reduce the output appreciably. Poor joints (soldering, etc), which create high-resistance conditions in the plate circuit will also produce reduced output. If all voltages are normal and reduced output still exists, the trouble is likely to be in the electron tube. Circuit oscillation may also cause the output to drop, and will show up as fuzzy pattern on the oscilloscope.

Unstable output, erratic operation, or distortion can result from a defective bypass capacitor in the cathode circuit. When in doubt, use an oscilloscope and a sine-wave generator to observe the waveform at the input and output of the tube. In the case of intermittent conditions where oscillation is suspected, the application of a square-wave signal will tend to produce oscillation if instability is the cause of the trouble. Oscillation can result only from feedback caused by improper coupling of the grid and plate circuits, or by common impedance coupling through

the power supply in multistage amplifiers, resulting from aging electrolytic bypass capacitors. This form of oscillation is called "motorboating", since it consists of a very low-frequency signal. Direct feedback usually manifests itself as a squeal or howl in the output.

Distorted Output. Improper bias is a common cause of distortion in the amplifier output. Check for the proper voltages in the grid and plate circuits. (Check the transformer for a dc leakage path between the primary and secondary windings if the bias is positive on the following stage.) Tube performance deteriorates with age, and usually manifests itself in the form of distorted and weak output. In a weak tube, lack of sufficient filament emission can cause distortion on the peaks of amplification because of its inability to pass sufficient current. While voltage measurements will determine whether the grid and plate voltages are correct, it is usually necessary to use an oscilloscope to observe the waveform and determine the cause of the distortion. An oscilloscope and a sine-wave generator should be used to follow the signal path through the circuit; observing where the waveform departs from normal will indicate the defective portion of the circuit. When the observed waveform exhibits a flattening of the negative peak, the current should be checked for abnormal conditions, such as insufficient grid bias, overdrive, and a leaky coupling capacitor. Similarly, excessive bias or grid current flow is evidenced by an oscilloscope waveform pattern with a flattening of the positive peaks. Overloading the amplifier will also produce these same effects; in this case the waveform will show both clipping of the positive and negative peaks.

Oscilloscope waveforms are a valuable aid in failure analysis when poor frequency response is suspected as the cause of distortion. For example, when a wave form which is supposedly a sine wave shows a characteristic "rounded" effect on the positive peak, this is a clear indication of poor low-frequency response of the transformer. In making more precise measurements, a square-wave generator may be used. With a square-wave signal applied, a sloping leading edge indicates a lack of high-frequency response, while a sloping flat top indicates a lack of low-frequency response. Since a square wave is made up of many sine-wave frequencies, the application of a 2000 to 3000-Hz square wave will indicate the relative harmonic response over a range up to 5 to 10 times this frequency.

Hum distortion can be observed directly on an oscilloscope. When it is on the power supply filtering. If it is not on the power leads, but is evident on the grid, plate, or cathode leads, check for induced hum due to the nearness of ac leads in the wiring. Poorly shielded and improperly grounded transformers may also be the cause.

TRANSFORMER-COUPLED AUDIO AMPLIFIER (SEMICONDUCTOR)

Application.

The transformer-coupled transistor audio amplifier is used where higher gain and power output than that provided by an r-f-coupled or impedance-coupled stage are required, and where the reduction in frequency response can be tolerated.

Characteristics.

Uses common emitter circuit for higher gain. Operates Class A for linear operation and minimum distortion.

Usually amplifies small signals, but can be designed to handle large signals in cascaded stages.

Is fixed-biased from the collector supply, but may use self-bias in some applications.

Emitter swamping is normally used for thermal stabilization.

Gain is fairly uniform over a range of approximately 100 to 10,000 Hz or more.


Both voltage and power gain are high.

Circuit Analysis.

General. The transformer-coupled transistor amplifier is similar in general to the transformer-coupled electron-tube amplifier previously discussed in this section of the handbook. Use of the common-emitter (grounded-emitter) circuit permits the assumption that the base of the transistor is equivalent to the electron-tube grid, the emitter is equivalent to the tube cathode, and the collector is equivalent to the tube plate. Thus it is clear from the following schematic that the two transformer-coupled circuits are practically identical. Any differences are due to the transistor internal parameters and the matching requirements to obtain maximum output with minimum distortion.

Circuit Operation. The accompanying schematic is that of a conventional PNP, triode, common-emitter,

transformer-coupled transistor audio amplifier circuit. The input is shown transformer-coupled through T1, and voltage divider R1, R_B provides fixed bias from the collector supply. Emitter swamping is provided by R_E for temperature stabilization; R_E is bypassed by C_E . (See the introduction to this section of the handbook for a discussion of bias arrangements and bias stabilization methods.) The output is transformer coupled through T2.

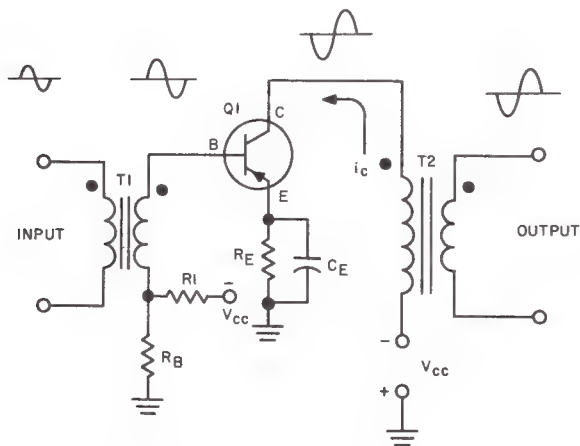

Transformer-Coupled Audio Amplifier

The use of T1 to apply the input signal to the base circuit provides an almost ideal temperature response characteristic. The low transformer winding resistance produces a low base input resistance, and, when used with emitter swamping resistor R_E , any variation in gain with temperature is reduced to a very small value over a large range of temperatures (greater than for any other type of coupling circuit). Normally, transistor Q1 rests in its quiescent condition, with Class A bias provided by voltage divider R1, R_B . The quiescent collector current, I_C , is steady, producing only a small constant voltage drop across the primary resistance of T2. Thus, practically the full value of collector supply, V_{CC} , is available. With a steady collector current no voltage is induced in the secondary of T2, and there is no output (assuming no input signal or noise). When a positive-swinging signal is introduced into the input circuit, current flow through the primary of T1 induces a voltage in the secondary, which is applied to the base of Q1. Assuming that the transformer secondary is connected in-phase with the pri-

mary, a positive increase in voltage appears at the base. This positive voltage swing cancels the forward negative bias, and a reduced flow of collector current occurs. As the instantaneous collector current decreases, the primary voltage drop also decreases, and allows the collector voltage to rise toward the negative supply voltage. Meanwhile, the reducing collector current induces a voltage in the secondary winding. The secondary winding is connected in-phase so that a reducing collector current produces a negative voltage swing in the secondary, and on increasing current produces a positive swing.

The emitter current flowing through R_E is the steady quiescent value, and any change in base bias with input signal is bypassed around the emitter resistor through capacitor C_E . Although the capacitor will not pass the quiescent dc current, it will pass the alternating audio voltage produced by the changing input signal. Thus, only dc current changes flowing through R_E (the thermally induced changes caused by temperature variation) produce an emitter bias. This emitter bias is in a direction which causes a reduced flow of emitter current, since it reduces the forward bias and hence reduces the collector current back to the original value so that it appears unchanged. If the emitter bypass capacitor were not used, the input signal voltage would produce a degenerative effect, since all collector and emitter current would be forced to flow through the emitter resistor.

Consider next the negative swing of the input signal. In this instance, the forward bias on the base element is increased (the two negative voltages add), and a heavy collector current flow occurs. The increasing i_C through the primary of T2 induces a voltage into the secondary. Assuming the same in-phase connection of the primary and secondary, the output voltage is positive.

Note that this action is similar to that of the vacuum tube amplifier, except that it is opposite. That is, a positive input to an electron-tube grid increases the plate current, whereas a positive input to a PNP transistor base element reduces the collector current. In each instance, however, the polarization of the output is opposite that of the input. By changing the connections of the secondary winding of either T1 or T2, the signal can be changed so that it is of the same phase at both the input and the output; this is an advantage of transformer coupling.

Since the secondaries of T1 and T2 are not connected to their primaries, the transformers offer a


convenient method of separating input or output signals from bias or collector voltages. By using the proper turns ratio, the primary and secondary impedances may be matched. In the base circuit the input resistance is matched, giving maximum gain, likewise, in the output circuit the proper turns ratio reflects the secondary load impedance into the primary, which, when added to that of the transformer primary itself, provides a matched load for maximum output.

Normally, the transformer-coupled stage is operated in the middle of its transfer characteristic to produce linear amplification. It is also a small-signal amplifier when used in preamplifier stages. In following cascaded stages it becomes a large-signal amplifier, operating with a larger bias over the linear range of its transfer characteristic. When necessary, bias resistor R_B is bypassed to ground with a large capacitor to prevent audio signal voltages from causing the bias to change with the signal, particularly in high-gain and large-signal amplifiers.

In cascaded transistor amplifiers the load on the secondary of T2 is the base resistance of the next transistor. Since this is resistive rather than reactive, there is less frequency distortion that would occur in an electron tube, where the load is predominately reactive (even in output stages the speaker is a varying reactance). In low-power stages the flow or reverse (leakage) current, I_{ce0} , through the collector-to-base junction becomes important when it is a large percentage of the total operating collector current. Thus, the designer chooses a transistor with as large a beta as is possible, and as small a leakage current as can be obtained, in order to get the most gain with the least leakage current. (The flow of reverse current does not occur in electron tubes.)

The frequency response of the transformer-coupled amplifier is lower than that of the resistance-coupled or impedance-coupled transistor audio amplifier. There is more shunting capacitance than in resistance coupling because of the transformer distributed turn capacitance, and there is a leakage inductance between the primary and secondary which does not exist in the impedance-coupled stage. The accompanying figure shows the equivalent circuit of a transformer-coupled stage and the factors that affect the response

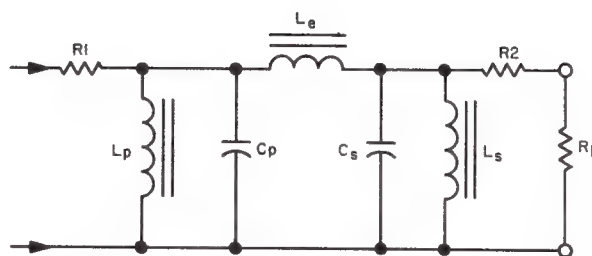In the figure, resistors R_1 and R_2 represent the dc primary and secondary resistance, respectively. These resistances must be kept low since they are ohmic



Transformer Equivalent Circuit

losses: also, the full collector current usually flows through R_1 . Therefore, the slope of R_1 determines the dc load line, and the transformers are designed to have a primary resistance of from 200 to 800 ohms for proper matching of transistors. Inductances L_p and L_s represent the magnetizing inductances of the primary and secondary transformer windings, respectively. The primary inductance is usually made from 2 to 5 times load resistance R_L for good low-frequency response. However, the lower the frequency the less the inductive reactance, so that the response tends to drop at low frequencies. Capacitors C_p and C_s represent the shunting capacitances of the primary and secondary windings, respectively. These include the shunt base-to-ground and collector-to-ground capacitances of the transistor, which are also large. Therefore, the high frequencies tend to be shunted to ground C_p , L_e , and C_s in combination form an effective low-pass filter, so that the high frequencies are attenuated (L_e is the leakage inductance between the primary and secondary). In substance, then, we see that the high-frequency response is primarily determined by the combination of shunting capacitance with load resistance and leakage inductance, while the low-frequency response is determined by the combination of load resistance and magnetizing inductance. In addition, the shunting capacitance and inductance form resonant circuits which produce humps in the response curve. Practically speaking, the response is very similar to that of the electron-tube transformer-coupled audio stage, with somewhat less high-frequency response. Loss of low-frequency response as compared with the electron-tube circuit becomes apparent when miniaturized transformers are used, because of the difficulty of building transformers with a sufficiently

large iron core to provide a high inductance with the limited number of turns available in the space allocated.

Despite the apparent loss of response in the transistor transformer-coupled amplifier as compared with other forms of coupling and the use of electron tubes, relatively good response is obtained by using more stages and low-and-high-frequency peaking circuits where necessary. A maximum efficiency of about 50 percent is obtained as compared with 25 to 30 percent for resistance-coupled stages.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of multiplier resistance employed on the low-voltage ranges of the standard 20,000 ohms-per-volt meter. Be careful also to observe polarity when checking continuity with an ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. A no-output condition may be caused by an open-or-short circuited transformer winding, by improper bias or loss of collector voltage, or by a defective transistor. A voltage check will determine whether the bias and collector voltages are normal; also a VTVM will indicate audio input and output voltages. With the few components involved, simple voltage and resistance checks will usually indicate the source of the trouble. If the bias voltage divider is open because return resistor R_B is defective, the base bias will be sufficient to cut off the transistor. With R_1 open, only contact bias exists and the transistor will very likely conduct heavily in the saturation region. If the primary of T_1 is open, there will be no voltage measured between the collector and ground. If emitter resistor R_E is open, the circuit will not operate; however, if emitter bypass capacitor C_E is shorted, the circuit will operate but it will be temperature-sensitive. Likewise, if the emitter bypass capacitor is open, it may reduce the output because of degenerative feedback, but normally it will not cause complete stoppage of operation. If the input transformer or the output transformer is open, no output will be obtained. Check the input and output circuits with an oscilloscope; disappearance of the signal will indicate the location of the defective winding. If the transistor is shorted or otherwise defective, a no-output condition will occur. A rough check of transistor operation can be made (if the transistor can

be easily removed from the circuit) by measuring the forward and reverse resistance with an ohmmeter. A high reverse resistance and low forward resistance indicates that the transistor is operable, but does not indicate whether the gain is normal. Be certain to observe the correct polarities.

Reduced Output. Improper bias voltage or a change in the value of a component, as well as a defective transistor or transformer, can cause reduced output. If the transistor gain is low, the output will also be low. If either of the base voltage-divider bias resistors changes in value, the bias will be either too low or too high and the output will be reduced, with accompanying distortion. A simple voltmeter check will determine whether the bias is correct. If the collector winding of T_2 develops a high resistance, the output will be decreased because of the extra dc voltage drop.

Distorted Output. If the base bias is too high (reduced forward bias), the transistor will operate on the lower portion of its dynamic transfer characteristic, and the negative input peaks will be clipped (positive collector swings). Likewise, if the bias is too low (increased forward bias), the transistor will conduct heavily and operate on the upper portion of its dynamic transfer characteristic, with corresponding clipping of the positive peaks (negative collector swings). In both cases extreme distortion will be caused. If the bias is proper but the collector voltage is not, similar effects may be caused. If the collector voltage is too high, the negative collector swing will be clipped, and if too low the positive collector swing will be clipped; in either instance heavy distortion will result. An open emitter bypass capacitor will permit degenerative feedback to occur, and, depending upon the amount, will show either as distortion or as reduced output. A change in load resistance produced by a defective output transformer (T_2) or a load resistance change usually shows as a distorted output with reduced volume because of the mismatching. Use an oscilloscope to follow the signal through the circuit and determine the point at which the waveform departs from normal. In most instances the defective component will then be apparent. Do not overlook the possibility that distortion may be occurring in a previous stage, merely being amplified by the stage under suspicion. Too large an input (overdrive) will cause both positive and negative peak clipping with distortion, just as in an electron-tube amplifier. Apply a square-wave input from an audio signal generator

and observe the output on an oscilloscope. Frequency distortion will be shown by a sloping rise and fall time (poor high-frequency response); a sloping flat top indicates poor low-frequency response. Electron-tube techniques for locating distortion may generally be used for transistor trouble shooting if the proper voltages and polarities are employed.

SINGLE-ENDED, R-C-COUPLED TRIODE AUDIO POWER AMPLIFIER (ELECTRON TUBE)

Application.

The use of the single-ended, R-C-coupled triode audio power amplifier is limited to those applications where relatively small amounts (less than 5 watts) of audio power are required, such as an audio output stage with a loudspeaker load.

Characteristics.

Power gain is relatively low (usually not more than 5).

Plate efficiency is low (on the order of 25 percent).

Power sensitivity is low for triode power amplifiers operating under Class A conditions (power sensitivity is the ratio of output power in milliwatts to the square of the rms grid voltage which produces it).

Distortion is relatively low (5 percent maximum).

Operates Class A at all times. no grid current flows under normal conditions.

Cathode bias (self-bias) is usually used, but fixed bias may be used if desired.

frequency response is relatively uniform over a range of 200 to 10,000 Hz.

Circuit Analysis.

General. The primary function of a power amplifier is to deliver sufficient power to a circuit load; any increase of voltage is of secondary importance. In fact, the voltage amplifier uses the same circuit as the power amplifier. The main difference in the two circuits is that the power amplifier is usually the last stage (the output stage). In some instances a power driver may be employed, for example, to supply the driver power for the grids of a Class B high-power modulator. However, this is a special application in which the full output of the stage is usually not used. Since the objective is to obtain as much power output as possible, with as low a plate voltage as practicable,

tubes with a low plate resistance are employed. As a consequence, these tubes are of the low-mu type rather than the high-mu type used in voltage amplifiers. (They are also larger in size, having plates capable of full dissipation of the dc power involved, use higher plate voltage and current, and are generally more rugged than tubes used as voltage amplifiers.) Because of the low mu, a large grid excitation voltage is usually necessary to drive the power amplifier. Therefore, a voltage driver stage is usually associated with the power amplifier. Consequently, at least three stages are necessary to provide audio power output when triodes are used, namely, a high-gain input stage, a driver amplifier, and the output stage. When only one tube is employed in the output stage, it is said to be single-ended. When two tubes are used, they are connected either in push-pull, in push-push, or in parallel. Where power output is considered more important than the distortion products, the parallel connection is generally used to provide about three fourths the rated power of two tubes. For full output and the least distortion, the push-pull connection is used (see the discussion of push-pull Audio Power Amplifiers later in this section). Although pentodes will produce more output than triodes, no further mention of them will be made in this circuit discussion since they are treated separately (see the discussion of Single-Ended, R-C-Coupled Pentode Audio Power Amplifier later in this section.)

Operation under Class A conditions with lack of grid current and an effectively high-impedance R-C coupled input eliminates any possibility of grid losses. This however, does not mean that the effect of the loading of the input circuit on the output of the preceding (driver) stage may be neglected. Thus, the power-amplifier grid input circuit constants determine to a large extent the total amount of undistorted voltage drive available.


The large ac (audio) power output derived from the single-ended circuit is actually obtained from the dc plate supply by converting the dc power to ac power through tube action. Maximum *undistorted* power output is normally obtained when the load resistance is equal to twice the plate resistance of the tube. If the load resistance is made higher than this optimum value, a reduced output will be obtained; however, the distortion will also be greatly reduced. As a result, in those cases where sufficient power output is available, it will be observed that the load

resistance is more than twice the tube plate resistance. For each tube type and given set of circuit conditions, the same set of operating rules does not necessarily apply. Therefore, the preceding discussion is broadly applicable only, and varies considerably with design. It is of interest to note that the distortion present in the single-ended stage consists primarily of second-harmonic signal. While other harmonics are also present, they are of much lower amplitudes and are normally neglected. Output ratings are generally computed for the maximum power output obtained when the second-harmonic distortion does not exceed 5 percent. Thus, the stage may be operated at lower power outputs with appreciably less distortion.

This is usually what is done with so called "hi-fi" (high-fidelity amplifiers systems. For example, a 25-watt output capability is supplied to provide only 2 or 3 watts for normal use. Hence, instead of being 5 percent or more, the distortion is reduced to less than 1 percent. To obtain maximum undistorted power output, the stage must have a properly matched load. This is, the *output load* (usually a loudspeaker) must equal (match) the *desired plate load impedance*. In this case, the output transformer serves as an impedance-matching as well as a coupling device, and must be capable of handling the full input power constantly. Since a speaker output load offers a different impedance to different audio frequencies, it is customary to consider it as offering a purely resistive load, and to assume that it has no reactive components which may be sensitive to various frequencies. Design is accomplished under these ideal conditions; however, practical operation is not quite the same. An explanation of loading and matching effects is given in the following discussion of circuit operation.

Circuit Operation. A typical single-ended audio power amplifier is illustrated in the accompanying figure. The varying input signal is capacitively coupled through capacitor C1 to the grid of triode V1. Capacitor C1 and resistor R1 form a high-impedance input coupling network. The input voltage is impressed across resistor R1 and is applied to the grid of tube V1. The reactance of capacitor C1 to the ac input signal is very small, therefore, the alternating input signal voltage is passed on to the grid with little or no attenuation over the audio-frequency range. Resistor R2 and capacitor C2 make up the cathode-bias circuit. (Refer to the introduction to this section of

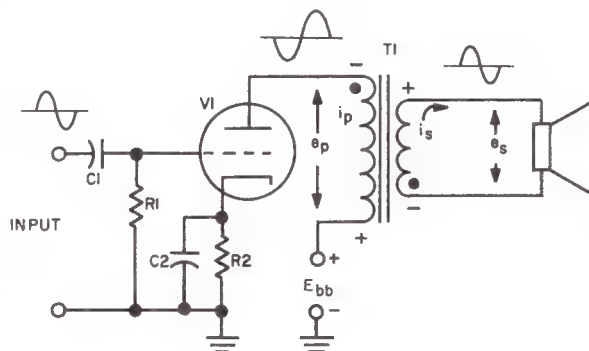the handbook for a detailed discussion of cathode bias.)



Typical Single-Ended Triode Audio Power Amplifier

The varying voltage applied to the grid of tube V1 causes the instantaneous plate current (i_p) to vary through the tube and through the plate-load impedance (primary of transformer T1). The changing current (i_p) through the primary of T1 produces an ac voltage drop (e_p) across the transformer primary, and causes an induced voltage (e_{sec}) to appear in the transformer secondary. This voltage (e_{sec}) causes current to flow in the load circuit. Thus, the transformer forms an output coupling network. It is important to realize that the transformer merely *reflects* into its primary circuit the load which is imposed on the secondary, and (neglecting internal transformer losses) does *not* place a load on the primary circuit unless a load is applied to the secondary. It is the turns ratio between the primary and secondary, not the number of turns in the primary, which governs the reflected impedance.

The current which flows in the transformer secondary will be larger than the primary current by the turns ratio. For example, in an output transformer which employs a step-down ratio of 40:1, the secondary current will be 40 times the primary current. The secondary voltage, however, will be only 1/40th of the primary voltage. Assuming that a primary voltage of 400 volts is generated, the secondary voltage will be only 10 volts. The power transferred will, in the case of an ideal and lossless transformer, be the same in both secondary and primary. For example, assuming a primary current of 20 ma, the secondary current will be 800 ma. Since power equals

$E \times I$, the primary power will be $400 \times .02$, or 8 watts, and the secondary power will be 0.8×10 volts, or 8 watts also. Assume a loudspeaker load of 4 ohms; since $I^2 R$ equals power, a total of 0.64×4 , or 2.56 watts, will be transferred to the speaker voice coil. With 8 watts in the primary, this represents about 32 percent efficiency. In a practical transformer, inherent losses will reduce this figure closer to the previously specified nominal value of 25 percent.


As far as the circuit action is concerned, the power amplifier operates in a manner identical with that of the Transformer Coupled Triode Audio Voltage Amplifier discussed previously in this section. When a positive signal appears at the grid of V1, the plate circuit develops a negative-going output. When this output is coupled from the primary to the secondary it will also be negative if so phased. When the secondary winding is connected in phase, the output will be positive for a positive input and negative for a negative input. Otherwise, the primary and secondary are always out of phase. The ability to connect the secondary for the desired phase is one of the advantages of transformer coupling.

To obtain maximum undistorted power output it is necessary to properly match the load to the tube. Here again the transformer offers a convenient matching method by choice of the proper turns ratio between the primary and the secondary. When used for impedance matching, the impedance ratio of primary to secondary varies as the square of the turns ratio rather than directly, or, stated mathematically: $N_p/N_s = Z_p/Z_s$, or $R_{pri} = (N_p/N_s)^2 R_{sec}$. Thus, assuming a 40:1 turns ratio, a 1600-to-1 impedance transformation is obtained. With a 4-ohm speaker and a step-up ratio of 40:1 (secondary to primary), the reflected load produced in the primary is 4×1600 , or 6400 ohms. Such an impedance would be satisfactory as a load for a 3200-ohm plate resistance stage (the load is twice R_p).

The example of impedance matching given above again illustrates the primary difference between the voltage amplifier and the power amplifier. While the impedance ratio is step-up for the load, it is step-down as far as primary to secondary is concerned. Therefore, only a low-voltage can be obtained, but maximum power output with a minimum of distortion is supplied to the speaker. In the event that the amplitude of the grid voltage is held constant, maximum output can be obtained when the load is equal

to the tube plate resistance; however, such operation in audio amplifiers is encountered only in special cases, usually where only one frequency rather than a range of frequencies is to be amplified.

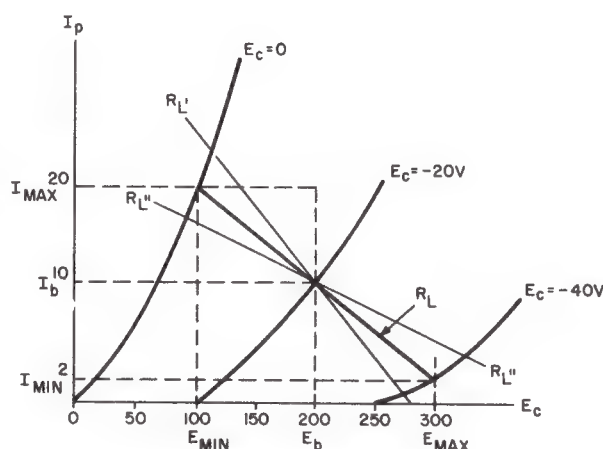The accompanying figure graphically illustrates typical triode plate current and plate voltage characteristics with an assumed load line, from which both power output and harmonic distortion may be determined




Graphic Determination of Power Output and Distortion

Note first that since the I_p - E_p characteristics are not straight lines and are not equidistant, the current and voltage swings will be unequal, and some distortion will exist. The load line R_L is drawn equal to the desired load resistance, and the static bias fixes operation at the intersection of the I_b and E_b lines, where the grid bias is -20 volts. Thus, in the ideal construction, equal positive and negative swings would occur, driving the bias to 0 and to -40 volts, respectively. The resulting plate current and plate voltage swings represented by I_{max} and I_{min} then determine the power output. Neglecting the second-harmonic distortion for the present, it can be shown that $P_o = 1/8 (E_{max} - E_{min})(I_{max} - I_{min})$.

The illustration shows that with lower load resistance (indicated by line R_L) the voltage swings will be smaller and the current swings will be larger than for R_L , and will be unequal; therefore, the power output will be less and the current continuously increases (since the effective grid then higher plate and bias

voltages are needed. In this case, as shown by load line R_L , the plate voltage swings are greater but the current swings are less; thus, the power output is lower, while the distortion is less, since the swings are more nearly equal. For a given tube and plate supply voltage, the desired solution is obtained by adjusting the grid bias. With the proper adjustment, the positive signal peak just takes the total grid voltage to zero, and the negative signal peak just makes the grid sufficiently negative to reduce I_p to its minimum allowable value (without operating on the curved lower portion of the tube characteristics.) The accompanying graph shows the variation of power output and distortion with respect to the ratio of the output resistance and the plate resistance for a triode. It is obvious that the most power is obtained when $R_L = 2 R_p$. On the other hand, if a value of $4 R_p$ is used, the power drops only 25 percent, but the distortion drops from 7 percent to only 2 percent, which is negligible.

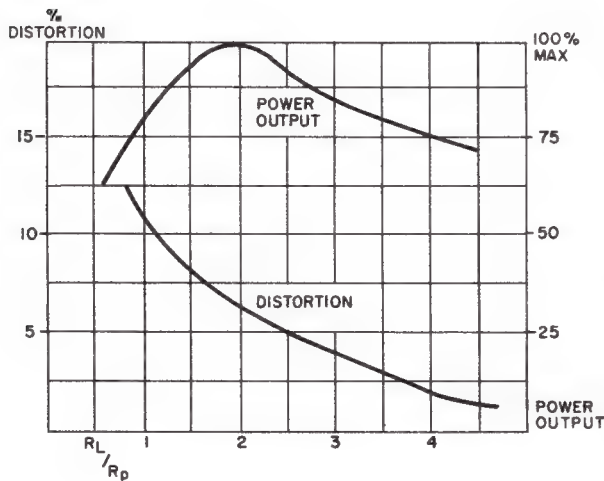


Power Output, Distortion and Load Resistance Relationships

It also can be shown mathematically that $R_L = E_{\max} - E_{\min} / I_{\max} - I_{\min}$. This is a simple Ohm's law relationship, which, by substitution in the proper formulas, becomes:

$$R_L = 2r_p$$

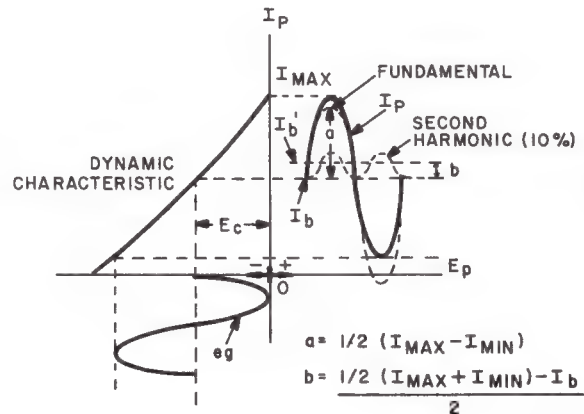The amount of distortion present is determined from the maximum and minimum plate currents, and is illustrated in the following figure.



Development of Harmonic Distortion

In this figure a triode $I_p - E_p$ characteristic is shown; with sine-wave voltage e_g impressed on the grid, the resultant plate current is represented by I_p . Since the maximum and minimum amplitudes are unequal (the curvature of the characteristic causes partial rectification to take place), the average value of I_b rises to I_b' when the signal voltage is applied to the grid. This increase in average current is equal to the amplitude of I_b' , shown by b in the figure. The fundamental component is $a = 1/2 (I_{\max} - I_{\min})$, while the second harmonic component is $b = 1/2 (I_{\max} + I_{\min}) - I_b/2$; the percentage of second harmonic distortion is equal to $100b/a$. The rise in average plate current with distortion shows as a fluctuating plate current, with the plate meter wiggling as the signal fluctuates in intensity.

Assuming that the cutoff voltage of the grid is E_b/μ , the maximum power output of a triode under Class A operating conditions can be estimated roughly in terms of its plate supply voltage and plate resistance by:

$$P_o = E_b^2 / 36 r_p$$

It is evident from the formula, then, that for moderate plate voltages the internal resistance of the

triode *must* be small to obtain relatively large power outputs.

Failure Analysis.

General. Since the circuit of the single-ended power amplifier is identical with that of the triode transformer-coupled amplifier, the failure analysis listed for the Transformer-Coupled Triode Audio Voltage Amplifier, previously discussed in this section, is generally applicable.

The power amplifier ordinarily operates at higher voltage and current than the voltage amplifier. Therefore, visual evidence in the case of flashovers and short circuits is usually more apparent. Excessive heating of a component usually indicates as incipient failure, since prolonged heating accelerates the aging process. Lack of proper bias is usually indicated by increased plate dissipation. Tube plates showing signs of color indicate excessive loading or current drain. Since the tube is generally working at full capability, lack of sufficient emission can usually be observed by a reduction of output, together with distortion. When trouble shooting the circuit, it is important to be certain that the proper load is connected at the output, otherwise, the tube may appear to be operating normally but be incapable of the proper output. To check for proper operation, apply a sustained tone from an audio generator to the amplifier input. Use an oscilloscope to check the waveform from input to output; any distortion will be immediately apparent. Use a vacuum-tube voltmeter to measure the actual ac input voltage, and substitute a resistor equal in value to the proper load impedance at the output. The ac voltage measured across this resistive load will, by use of Ohms' law, indicate the power output ($P_o = E^2/R$).

SINGLE-ENDED, R-C COUPLED PENTODE AUDIO POWER AMPLIFIER

Application.

The single-ended, R-C-coupled pentode power amplifier is used in applications where a relatively large audio power output is desired from a small input voltage, and where some distortion can be tolerated.

Characteristics.

Input impedance is high, usually greater than 0.1 megohm.

Uses an output transformer to match the load to the output device.

Power sensitivity (ratio of output-power to grid voltage producing it) is relatively high.

Power gain is high, on the order of 8 to 20.

Distortion is normally higher than that of the triode (always more than 5 percent and generally on the order of 7 to 10 percent) unless special design considerations or negative feedback is used.

Operates Class A at all times; no grid current flows under normal conditions.

Cathode bias is usually used, but fixed bias may be used in some applications.

Frequency response is relatively uniform and linear over a range of 200 to 10,000 Hz without requiring any special design considerations or compensation.

Circuit Analysis.


General. While the single-ended triode audio amplifier is characterized by low power sensitivity, low plate efficiency, and low distortion, the pentode counterpart is just the opposite; it is characterized by high power sensitivity, high plate efficiency, and high distortion. Because of its basically higher distortion, the pentode power amplifier requires more attention to design. Fortunately, however, the increase in power obtainable with the pentode permits the use of various feedback methods, and what essentially amounts to mismatching to attain power outputs equivalent to or greater than the triode with the same distortion. Usually the use of a pentode output stage eliminates the necessity of a driver stage, since the pentode can be adequately driven by small signals.

The screen element in the pentode requires a dc source of power, which does not contribute materially to the output directly and represents an additional constant loss of power (as compared with a triode). Because the I_p-E_p characteristics are parallel, the amount of second-harmonic distortion is very low, and third-harmonic distortion predominates. Consequently, push-pull operation will not materially help in reducing the distortion. On the other hand, when the load is designed so as to produce more second-harmonic distortion, the use of push-pull operation provides cancellation of this component, and the third-harmonic component is also reduced by the load mismatching. See the discussion of Push-Pull Audio Power Amplifiers later in this section for further details on push-pull operation.

As contrasted with the triode, instead of having a load with twice the plate resistance, the pentode uses a load with only 1/5 to 1/10 the plate resistance. Such mismatching is necessary because of the extremely high plate resistance inherent in the pentode.

This discussion also applies generally to tetrodes and beam power tubes, except that the second-harmonic distortion of these tubes is greater, more like that of the triode. However, like the pentode, they do have a higher plate resistance and greater over-all distortion, which requires negative feedback or other compensation to provide an acceptable output.

Circuit Operation. The schematic of typical single-ended pentode power amplifier is shown in the accompanying figure. The circuit load is a loudspeaker. The varying audio input signal is applied to the grid of pentode V1, through coupling capacitor C1. Capacitor C1 and resistor R1 make up the input coupling network, and the input signal is impressed across resistor R1. The reactance of capacitor C1 to the ac signal is very small; therefore, the alternating signal voltage is readily passed on to the grid without excessive attenuation. The bias circuit consists of cathode resistor R2 and capacitor C2. (See the introduction to this section of the handbook for a discussion of cathode bias.) As is evident from the schematic, the cathode and the suppressor grid are maintained at the same voltage level, being connected together internally or at the socket (depending upon the type of tube used). The varying input voltage applied to the grid of pentode V1 causes the instantaneous plate current (i_p) to vary similarly through the tube and through the plate-load impedance (primary of transformer T1). Capacitor C3 bypasses the screen to ground to prevent the signal voltage from changing the screen voltage at an audio frequency rate. Capacitor C3 is chosen to present a minimum of reactance to the signal voltage; thus, the screen-grid voltage is maintained at a relatively constant dc level. The positive screen-grid voltage is obtained from the plate supply through voltage-dropping resistor R3 to avoid the necessity of providing a separate screen-grid power supply. The changing plate current (i_p) through the primary of T1 produces an audio voltage drop (e_p) across the transformer primary, and also causes an induced voltage (e_{sec}) causes current (i_{sec}) to flow in the load (output) circuit. Thus, the transformer secondary forms an output coupling network.

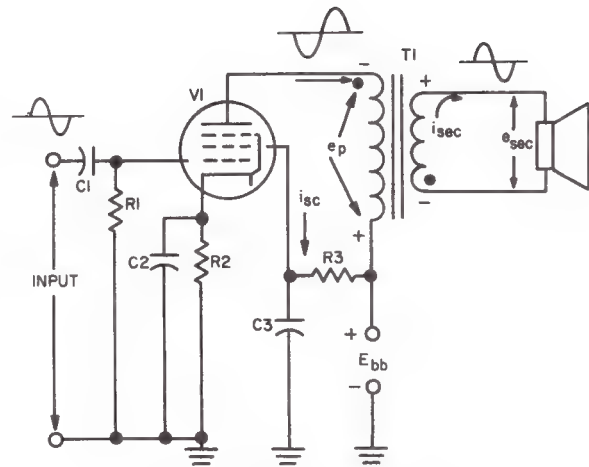


Typical Single-Ended Pentode
Audio Power Amplifier

As far as specific circuit action is concerned, the operation is identical with that of the Transformer-Coupled Audio Voltage Amplifier Circuit and the Single-Ended Triode Audio Power Amplifier Circuits discussed previously. When a positive signal is applied to the grid of V1, a negative-going signal is developed in the plate circuit, and coupled from the primary to the secondary of T1 as a negative-going output signal if T1 is connected in-phase. When a negative signal is applied to the grid, a positive-going amplified signal is developed in the plate circuit, thus inducing a voltage in the secondary of T1. When connected in-phase, the secondary output is positive for a positive input signal and negative for a negative input. Otherwise, the primary and secondary voltages and currents are always out-of-phase.

To obtain maximum undistorted output, it is necessary to properly match the load to the tube. The transformer offers a convenient method of accomplishing load matching since the impedance ratio of primary to secondary varies as the square of the turns ratio, rather than directly. Stated mathematically, $Z_{pr} = (N_p/N_s)^2 Z_{sec}$. Thus, with a transformer having a 50:1 turns ratio and a 4-ohm loudspeaker load, the primary would reflect a load of 2500 times the secondary impedance, or 10,000 ohms. Such a load is

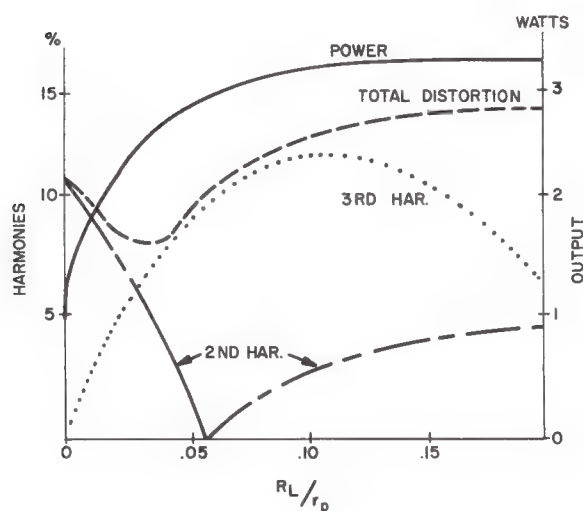suitable for matching pentodes having a plate resistance of 50,000 to 100,000 ohms, with the least distortion being obtained from the higher-plate-resistance tubes. The manner in which the output power varies with the ratio of the load and plate resistance of a typical pentode, together with the amounts of distortion produced, is graphically illustrated in the following figure.




Typical Power Output and Harmonic Distortion Relationships

The large amount of second-harmonic distortion at high load impedances shown in the graph occurs because of the crowding together of the typical pentode plate characteristics at low plate voltages. This causes a greater i_p change during the negative peak than during the positive peak of the output waveform, thus tending to flatten the positive peak. During the interval over which the negative and positive swings are equal, practically no second-harmonic distortion occurs. The large amount of second-harmonic distortion with low load impedance is caused by the unequal spacing of the plate characteristics at low plate currents, which tends to flatten the negative peak of the alternating plate current. Because the load for maximum power output is different from the load for minimum distortion, the choice of the load is a compromise between the amount of power output desired and total distortion that can be tolerated. The load is

usually chosen so as to produce minimum second-harmonic distortion. While it is possible with some tubes and designs that optimum power output may occur at the point of minimum distortion, this is the except rather than the rule. Because of the extreme variations between tube types, simple design formulas like those used for the triode are not obtained; therefore, most of the design must be determined graphically.

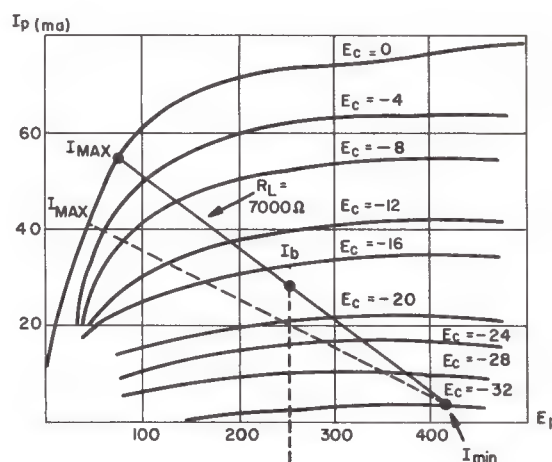The accompanying figure shows the I_p - E_p characteristics for a typical pentode with the proper load line. In this example the plate resistance is 60,000 ohms and the load is 7000 ohms.



Typical Pentode I_p - E_p Characteristics and Load Line

Examination of the plate characteristics reveals that for equal grid swings, equal plate current swings are produced with the 7000-ohm load line. It can easily be seen that if the load line were drawn with less slope (for example, an increased load resistance of 9000 ohms, shown by dotted load line), I_{max} would be less than I_{max} , and if the load were increased further the maximum current would change greatly while the minimum would remain practically the same. As a result, second-harmonic distortion would be increased. It is important with pentodes, therefore, to prevent the load from increasing with frequency, as normally happens when a loudspeaker is the load. To minimize this increase in distortion of

the higher audio frequencies, a capacitor connected in series with a resistor is used in shunt with the transformer primary (in some cases it is in the form of a tone control, and in other cases only a shunting capacitor is used). The variation of the effective loudspeaker impedance with frequency when the RC network is not used is shown by the solid curve (a) in the following graph, and the variation when the RC network is used is shown by the dashed curve (b). Because of the high plate resistance of the pentode, the effective resistance shunting the loudspeaker is less than that for a triode. This reduction of damping on the speaker sometimes causes objectionable "booming" because of resonances which otherwise would be subdued (damped out). It is also of interest to note that the screen grid of a power pentode is not as effective (as compared with a voltage pentode) in shielding the control grid from the plate. As a result, the plate-to-grid capacitance is larger than in the voltage pentode. In addition, because the control-grid connection is made through the base rather than through a tube cap, the grid-to-cathode capacitance is also larger. Therefore, the total effective input capacitance of the power pentode may sometimes be considerably larger than that of the power triode. The result is to produce greater frequency distortion in the preceding amplifier stage. Because of these facts the over-all distortion is so large that negative feedback is practically mandatory to keep the distortion

within acceptable limits if the full power output of the pentode is required.

While it is possible to eliminate the cathode bypass capacitor (C2 in the schematic) and thus obtain degeneration to help reduce the distortion. It is usually easier to use negative feedback. Because of the high gain in the pentode, a larger cathode bypass capacitor is required than in a triode amplifier.


Although the load line as discussed above was considered to be a straight line for convenience, in actual operation the dynamic load line is not straight, but varies in accordance with the reactive component of load impedance in the circuit. The result is to shift the operating point slightly about the bias value assumed for the ideal condition, particularly when self-bias is used. With proper design this is of no consequence, since the circuit is arranged to produce equal shifts for the positive and negative grid swings. If unequal shifts are permitted to occur, however, the effect is to obtain performance entirely different from the assumed values of plate current, voltage, bias and, grid drive, with greater distortion and phase shift. Thus, the gain, output, and response characteristics may sometimes be entirely different from those which are assumed or calculated.

Failure Analysis.

No Output. A no-output condition is normally caused by the lack of an input signal, an open-circuited condition, lack of plate or filament voltage, a short-circuited condition, or a defective tube. The presence of an input signal can be determined by checking the input with an oscilloscope or vacuum-tube voltmeter. An open-circuited condition can be localized to the defective portion of the circuit by making voltage measurements to determine whether the filament, cathode, grid, plate, and screen voltages are present and are normal.

An open cathode circuit will cause a no-output condition. With an open input circuit (C1 or R1 open), the high gain and high impedance of the pentode may permit a slight output; however, for all practical purposes the output will be so low that it can be considered nonexistent.

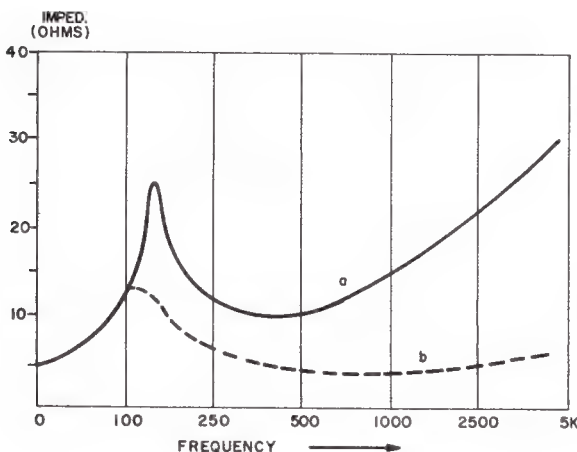If the screen shows color and the plates does not, it usually indicates that the screen is attempting to act as the plate because of an open plate circuit. In this case the plate voltage will be zero.



Variation of Loudspeaker Impedance
with Frequency

An open screen resistor, R3, or shorted screen bypass capacitor, C3, will also cause a no-output condition. In either case no voltage will appear on the screen of the tube. An open screen resistor will be cool. With a short-circuited bypass capacitor, since the screen resistor will be dropping the full voltage from the plate supply to ground, it will be abnormally hot and probably will eventually burn out; a visual inspection will normally show discoloration or even smoke in this instance.

With an input signal present and normal tube voltages, either the tube is defective or the transformer secondary is open. Replace the tube with one known to be good, and check the secondary for continuity with an ohmmeter.

Reduced or Unstable Output. Reduced output is usually caused by improper bias, or low plate or screen voltages. Unstable output is usually caused by oscillation, or by intermittent functioning of circuit components. An open cathode bypass capacitor, C2, will permit sufficient degeneration to reduce the output appreciably, as will an open screen bypass capacitor, C3. If the bias is excessive or if cathode bias resistor R2 has increased in value, the output will also be reduced, depending upon the amount of change. If the screen resistance increases in value or by-pass capacitor C3 becomes leaky, the increased voltage drop across R3 will produce a lower screen voltage and thus reduce the output by reducing the maximum plate swing. If the reflected load impedance is too high, the output will also be reduced. A shorted input coupling capacitor, C1 can place the plate voltage of the preceding stage on the grid of V1, cause increased plate and screen current, increase the cathode bias, and reduce the output. (In some cases it can cause complete cutoff.)

With all voltages normal, the trouble is most likely in the electron tube; reduced emission will cause a loss of output, particularly on the signal peaks when more electrons are needed to increase the plate current.

Unstable output can result from intermittently open or shorted components, and can usually be located by using an oscilloscope to follow the waveform through the circuit. Oscillation can also cause erratic response. If it occurs at radio frequencies, it will show on the oscilloscope as a fuzzy pattern; if the feedback is at an audio frequency, it will be observed as a separate audio frequency. Oscillation will also show in the output as a howl or squeal, or as a

very low-frequency "put-put" (motorboating). Howl or squeal is usually caused by undesired coupling between the plate and grid circuits. Motorboating is usually caused by faulty bypassing (in the power supply or B+ leads), particularly where electrolytic capacitors are used; electrolytic capacitors tend to dry out with age and lose their capacitance.

Distorted Output. Improper bias or improper load matching is a common cause of distortion. Check for proper plate and grid voltages. Lack of sufficient emission in the electron tube will also cause distortion on the signal peaks. Where the voltages are normal and the load is correct, the tube is probably at fault; it should be replaced with a tube known to be good. Use an oscilloscope and audio signal generator to follow the waveform through the circuit. Flattening of both positive and negative signal peaks indicates overdrive (too large an input signal). Flattening of the negative peaks indicates excessive bias or low plate voltage; this symptom can also be caused by low screen voltage. Too low a bias or too high a screen voltage is usually indicated by flattening of the positive peaks. Check the frequency response characteristics. Rounded-off peaks on sine waves or sloping sides or tops on square waves indicates loss of low- and high-frequency response. A 2000- to 3000-Hz square wave applied to the input will provide a signal which can indicate the relative harmonic response over a range of 5 to 10 times this frequency (the square wave is composed of many sine-wave frequencies).

Hum distortion can be observed directly on the oscilloscope. When hum is present on the power leads, lack of sufficient power-supply filtering is indicated. If it is not on the power leads, but is evident on the grid, plate, or cathode leads, check for induced hum due to the nearness of ac leads in the wiring. Additional checks should be made to insure that the transformer is properly grounded and that the shielding is adequate.

PUSH-PULL AUDIO POWER AMPLIFIER (ELECTRON TUBE) (CLASS A, AB, AND B)

Application.

The push-pull audio power amplifier is used where large amounts of undistorted audio power are required. This circuit is commonly employed in receiver output stages, in hi-fi and public address systems, and in AM modulators.

Characteristics.

Power gain is moderately high, on the order of 4 to 10.

Requires twice the drive of a single tube.

Power output is more than twice that of a single tube (about 2-1/2 times).

Second and higher even-order harmonic distortion is cancelled out in the plate circuit.

Distortion varies with the class of operation; it is minimum for Class A operation, and greatest for Class B operation.

Plate efficiency varies with the class of amplifier; it is lower for Class A operation, highest for Class B operation, and intermediate between the two for Class AB operation.

Cathode (self) bias is normally used for Class A or AB operation, but fixed bias is usually used for Class B operation. (Specially designed Class B tubes requiring no bias are sometimes used.)

Cathode bypass capacitor is usually omitted in Class A stages, but is included in Class AB stages.

Circuit Analysis.


General. In push-pull operation, the plate current of one tube is increased, while that of the other tube is simultaneously decreased, and vice versa. As originally conceived, one tube was considered to be pushed while the other tube was pulled; hence the term *push-pull*. While this is true of Class A or Class AB operation, it is not strictly true of Class B operation. Class B amplifiers utilize the push-pull circuit; however, one tube effectively amplifies only the positive portion of the input signal, while the other tube amplifies only the negative portion. This occurs because only one tube conducts at a time, while the other tube is cut off. Push-pull stages require twice the grid drive of single-ended stages; however, each tube may be driven to its full capability, and usually more than twice the output possible with a single-ended stage is supplied. Distortion is reduced because the even-order harmonics are cancelled out. For triodes, this provides a maximum reduction of distortion. For pentodes, since the second-harmonic distortion is small or negligible, only a slight reduction in distortion is obtained. However, with special design in which the pentodes are loaded so that they produce more than normal second-harmonic content, a reduction in both second- and third-harmonic distortion is achieved. With the beam-power tube, distortion is also reduced since this tube

has a large second-harmonic content than the pentode, although not as great as the triode.

Since in a balanced push-pull amplifier the plate currents are equal and opposite, dc saturation effects on the core are eliminated; this permits more efficient transformer design, together with a reduction in both amplitude and frequency distortion. Actually, only 40 percent more turns in the primary (as compared with single-ended stages) are needed to handle two tubes in push-pull. Thus, the transformer design is economical. With a balanced input and output, any hum present in either the input or in the output tends to cancel out. This, together with the reduction in harmonic distortion, provides better audio quality.

With triodes, usually Class A or Class AB operation is employed, and the drive is such that no grid current is drawn. With pentode or beam-power tubes, usually Class B operation is used, and some grid current is drawn. As a result, Class B stages usually require power driver stages, while Class A or AB stages require only voltage driver stages.

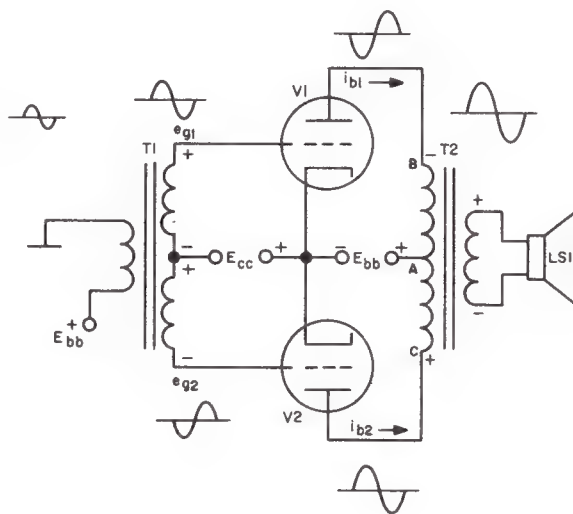Circuit Operation. A typical push-pull circuit using a minimum of components is shown in the accompanying figure. For ease of explanation, fixed bias is assumed. (For a discussion of circuit biasing methods, refer to the introduction to this section of the handbook.) The circuit load is a loudspeaker.




Typical Triode Push-Pull Audio Power Amplifier

It is evident from the schematic that the grids of V1 and V2 are biased equally negative with respect to the respective cathodes. With no input signal applied to T1, the tubes rest in their quiescent (static) state, and equal but opposite dc currents flow in the two halves of the primary of T2. The steady flow of dc current does not induce a voltage in the secondary of T2, since the current in each half of the primary is equal and opposite in direction, and the magnetic flux around the primary cancels. Thus the core is not subjected to a continuous magnetizing force. Consequently, the possibility of dc core saturation is minimized (for a specific core, any dc induced flux adds to the ac induced flux produced by a signal, and thus limits the total amount of flux that can be carried through the iron without saturating). As a direct result, a higher primary inductance is obtained with the same number of turns. On the other hand, when saturation occurs the inductance is reduced just as if the core size were reduced, and this changes the load impedance and creates distortion. The reduction in saturation effects is an inherent advantage of the push-pull circuit. When an input signal is applied to the primary of transformer T1, equal but opposite voltages are induced in the secondary (the schematic shows the instantaneous polarities or one half-cycle of operation; during the other half-cycle they are oppositely polarized). Therefore, when the plate end of T1 is positive the grid of V1 is driven positive, while the grid of V2 is driven negative (assuming that T1 is connected in-phase). The alternating drive voltages, e_{g1} and e_{g2} , are equal and are connected in series with bias voltage E_{cc} . Assume for the moment that the drive voltages are just equal to the bias. It is evident, since they are of opposite polarity, that V1 will conduct heavily (the bias is reduced to zero), and V2 will be biased twice normal, or to zero plate current. The heavy current flow through the primary of T2 to the plate of V1 produces a maximum voltage drop across the load, reducing the plate voltage of V1 to its minimum value. The flux produced by the flow of ac plate current through T2 induces a voltage in the secondary in accordance with the turns ratio of the transformer (the relationship of transformer turns ratio, impedance, and power output will be discussed in more detail in a following paragraph). The secondary of T2 is assumed to be connected out-of-phase with the primary, so that the polarity of the output for the half-cycle discussed above is positive, as shown in the schematic waveforms.

When the plate current of V1 decreases (on the other half of the cycle), the plate current of V2 increases. The alternating currents in the primary of T2 are in phase while the dc currents and their resulting voltage drops are opposing. The net result is that the magnetomotive force produced by the two halves of the primary is zero with no signal impressed. With an input signal applied, the plate current of the two tubes is equal to a current equivalent to the difference in the current flowing in tube V1 and tube V2, both flowing through one half of the primary winding. For example, assume a quiescent current of 30 milliamperes and a drive signal that causes one tube to increase 10 milliamperes instantaneously. Since the grid swings are equal and opposite, the plate current of the other tube is reduced. For ease of discussion also assume that the tube characteristic E_g-I_p curves are exactly identical (in practice they are slightly different). Then, the reduction of plate current in the second tube will be exactly 30 minus 10, or 20 milliamperes. With an upward swing of 10 ma to 40 ma, the difference in current between the two tubes is 40 minus 20, or a total I_p of 20 ma, which is exactly double that of one tube. With a unity turns ratio between each half of the primary and the secondary, equal a-f voltages are induced in the output. Since they occur simultaneously and are in-phase, they are effectively series-connected and the output voltage is doubled. The same effect would be produced by the difference current (20 ma) flowing through one-half of the primary. Consequently, the dynamic characteristic for two tubes operating in push-pull is constructed by subtracting the currents through the two tubes in order to approximate the effect of the transformer.

Class A Operation. The accompanying dynamic characteristic curve illustrates Class A operation. The dotted curve labeled V1 represents the dynamic characteristic of one tube, while the dotted curve labeled V2 represents the dynamic characteristic of the other. Both of these characteristics are assumed to be identical. Although the dynamic characteristics of the individual tubes are curved, the resultant push-pull characteristic is straight. As is evident from the figure, the dynamic characteristic for Class A push-pull operation is extended over that for a single tube, and is even more linear. Thus, greater grid-signal, plate-current, or plate-voltage swings are possible without any noticeable increase in distortion. With a greater swing, greater power output is obtained. By

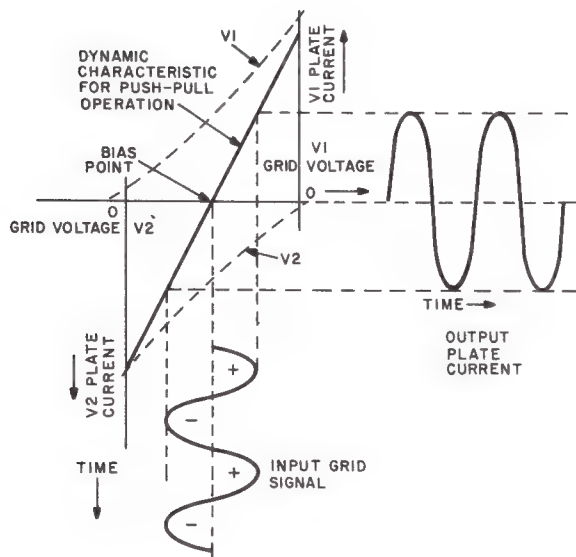projecting the various points of the grid (input) signal to the solid-line, push-pull characteristic shown in the figure, the output waveform is obtained.




Dynamic Characteristic Curve for Class A Operation


The output transformer turns ratio and load impedance relationships in the push-pull amplifier are based upon a unity turns ratio of secondary to one-half of the primary. Thus, when the whole primary-to-secondary turns ratio is considered, that is, the plate-to-plate load, the ratio is 2 to 1. Since the transformer impedance between the primary and secondary varies as the square of the turns ratio, a 4-to-1 impedance transformation is obtained. For example, with a 1000-ohm load across the secondary, the plate-to-plate load is 4000 ohms, and the individual tube load is 1000 ohms. The proper load for a particular tube varies in accordance with the design and class of the amplifier, and is beyond the scope of this handbook. The effectiveness of the push-pull circuit results basically from the elimination of second-harmonic distortion, which permits the tube parameters to be increased much beyond those of the single-ended stage for an equivalent amount of distortion, thus providing a much greater power output. Another reason is that the apparent internal plate resistance of the push-pull combination is much lower than that of a single tube (on the order of $r_p/2$).

Therefore, with the same voltage and bias as that of a single tube, the lower dynamic plate resistance permits much greater output. In addition, the amount of distortion does not increase greatly when the tubes are driven to zero bias or even into the positive region. Therefore, Class B operation becomes feasible, and is used where large amounts of audio power are desired.

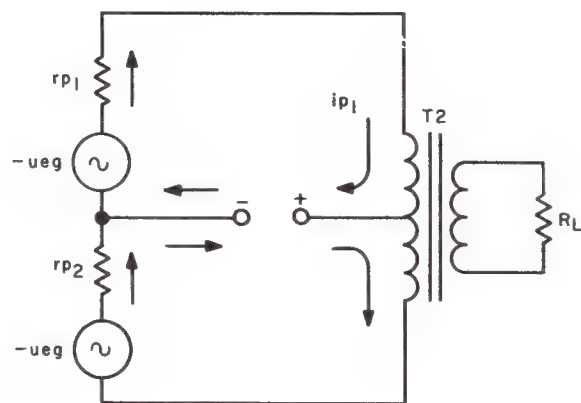The manner in which second-harmonic distortion is eliminated can be more easily visualized if the accompanying equivalent circuits are examined. Part A of the figure shows the fundamental and odd-order




A - ODD - ORDER HARMONICS

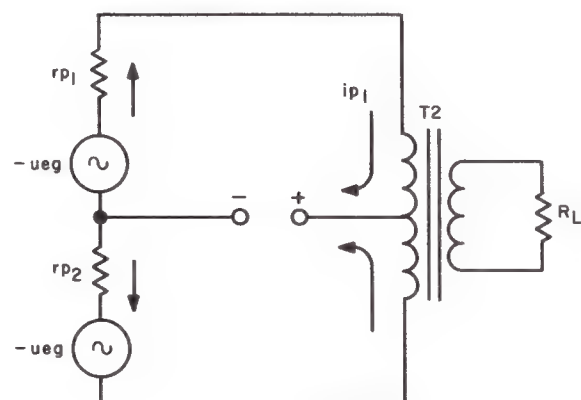

B - EVEN - ORDER HARMONICS

Simplified Push-Pull Equivalent Circuits

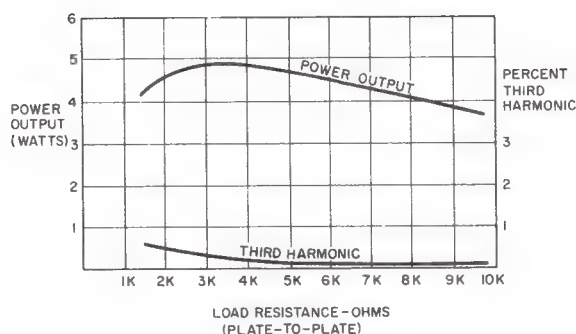

Distortion and Power Output Variation with Load Resistance for a Typical Push-Pull Amplifier


equivalent circuit, while part B shows the second and even-order harmonic circuit. Note that in part A of the figure i_p flows in the same direction through the primary of T2; thus the fundamental and odd-order harmonics induce an output in the secondary and appear across R_L . The current flow is in opposite directions through the power supply, however, so that the fundamental cannot appear as feedback through the common supply impedance; thus oscillation from this cause is prevented. In part B of the figure the flux in the primary developed by i_p cancels, and, while the second-harmonic current does exist in the primary, it does not appear in the secondary as long as the circuit is balanced. Even with an unbalanced current, however, any second-harmonic output is considerably reduced. The reduction of second and even-order harmonics also contributes to a much reduced third and odd-order harmonic content. Since the second and third harmonics produce most of the distortion encountered in the amplifier circuit, the push-pull amplifier automatically provides a much larger undistorted output than that of the single-ended stage. The manner in which the output power and third-harmonic distortion vary in accordance with the plate load for a typical two-tube push-pull amplifier is shown in the accompanying figure. The tube types, plate voltage, bias, and grid drive are the same as those used in a similar graph shown in the discussion of the Transformer-Coupled Triode Audio Power Amplifier, discussed previously in this section of the handbook. Comparison of these charts shows almost a three-time power increase over that of a single tube for the

same load resistance, with a total absence of second-harmonic distortion and very little third-harmonic distortion.

Class AB Operation. In Class AB push-pull operation, sometimes referred to in other texts as Class A prime operation, the grid bias is increased over that of Class A operation, and plate current does not flow during the entire 360 degrees of the cycle. During the peak grid excursions, therefore, some rectification of the grid signal occurs when the plate current is interrupted, causing distortion and high peak plate currents. With self-bias this increases the bias during the peaks and produces nonlinearity, which is the main cause of the increased distortion. With fixed bias the abrupt change which occurs with self-bias is not encountered, and the distortion is less. This occurs because there is no abrupt increase in plate (cathode) current to produce the bias change; instead, the bias at the peaks is determined by the resistance in the grid circuit and any grid current flow so that the change is proportional to the signal increase, it is somewhat more linear, and less amplitude distortion is created. Therefore, self-bias is usually avoided in Class AB operation. Regardless of distortion effects, however, the increase in bias (over that of class A operation) at a particular plate voltage reduces the total operating current and the plate dissipation. Therefore, the efficiency in the plate circuit increases and greater power output is obtained. If desired, the plate voltage (for triodes) may be still further increased to restore the plate dissipation to the full rated value with still greater output. For this reason, Class AB operation is generally referred to Class A operation where power output is the main consideration and a slight increase in distortion can be tolerated. Since the plate current range, and hence the cathode current (in self-biased operation), is greater than that of Class A operation, a slight unbalance between the tubes usually occurs. Therefore, a cathode bypass capacitor is generally used in self-biased Class AB operation to prevent degenerative effects due to this unbalance. Although matched tubes are desirable, whether or not cathode bypassing is used, it is considered to be more economical and practical to provide a current-balancing control in the bias circuit and to use unmatched tubes. Actually, for Class A or AB operation, it is only necessary to match the quiescent value of current to obtain a balance within 10% over the operating range.

The dynamic characteristic of Class AB push-pull operation is obtained in the same manner as that of Class A push-pull operation. A typical characteristic curve would show that the bias is closer to the plate-current cutoff value than is true of the Class A push-pull circuit. In addition, the resultant characteristic is linear over a greater length as compared with Class A operation. This result is less distortion and greater plate efficiency. Maximum efficiency for Class AB operation is on the order of 50 to 55 percent.

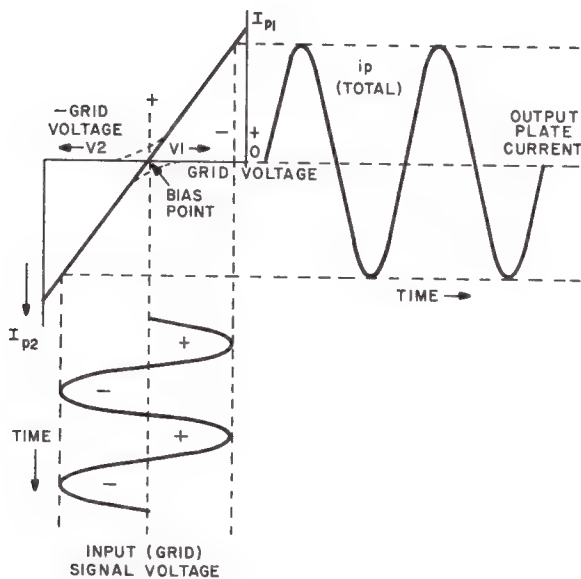Class B Operation. A typical dynamic characteristic curve for Class B operation is shown in the accompanying figure.



Typical Class B Dynamic Characteristic Curve

Note that the bias is higher than that for Class AB operation and is nearer to, but not quite sufficient to cause, plate current cutoff. This, a slight idling (static) current exists with no input signal. With the greater bias, a greater drive signal is required. Since the grids are usually driven positive and grid current is drawn (that is, Class B operation), a power-driver stage is necessary.

Because grid current flows on the peaks of the input signal, a low-impedance grid circuit is necessary, and is usually provided by using a step-down turns ratio from the primary of the input transformer to

the secondary. This also has the effect of reducing the internal plate resistance of the driver tube, and produces better over-all voltage regulation to help diminish distortion on the peak input signal swings. While the circuit operates in a manner similar to that of a Class A or AB push-pull amplifier, it differs in the only one tube is operative at a time. It can be seen, then, with each tube operating separately, that large fluctuations exist in the plate current and voltage, as well as grid current and voltage, and well-regulated power and bias supplies are necessary to avoid distortion. The distortion is caused by flattening of the peaks due to poor regulation. Since the plate current, and hence the cathode current, fluctuates greatly, self-bias is impracticable, and fixed bias is used; in some applications special hi-mu Class B tubes designed to operate at zero bias with very small plate current flow are used. Because only a small static plate current is drawn when no input signal is present, the average plate current is less than that for Class A operation, even though the plate current swing is greater. This is the reason for the higher efficiency produced by the Class B push-pull amplifier. For example, it can be demonstrated that with a plate efficiency of 60%, the power output is 1.5 times the plate dissipation. On the other hand, for a Class A stage operating at 25% efficiency, the power output is only .25 of the plate dissipation. Thus, it is possible to obtain six times as much power output from the same tube in Class B operation as in Class A operation.


Because each tube of the Class B push-pull amplifier operates on alternate half-cycles, the cancellation of the second-harmonic component (a feature of the Class A or AB push-pull amplifier) does not exist (except for the period during which both tubes operate). Harmonic distortion at the input is transmitted in amplified form to the output. Any second-harmonic distortion generated in the stage is also induced in the secondary of the plate transformer. This occurs because the only time that flux exists in the core of the output transformer from both tubes is during the small idling period between signals or during static operation. Class B operation also tends to produce second-harmonic distortion because the dynamic characteristics of each tube is not affected by the other tube's plate current; these currents occur separately during opposite half-cycles (unlike the Class A or AB stage, where one current is coupled to the other by flux produced by simultaneous current

flow in the primary of the plate transformer). Regardless of the tendency toward distortion, the operation of the two tubes "back to back" in the push-pull circuit permits selection of the straight-line portion of the dynamic characteristic for operation. Since operation in this region is linear, second-harmonic distortion is effectively eliminated. However, if operation occurs in the nonlinear region beyond this, or if the tubes are mismatched badly (10% difference in current will produce 5% distortion), then second-harmonic distortion will be produced and the effectiveness of the push-pull connection will be lost. Despite the apparent disadvantages of Class B operation, when careful attention is paid to design much greater output is obtained with not too much additional distortion. Therefore, Class B operation is universally used for high-power audio applications, particularly for transmitter modulator stages. Practically, efficiencies on the order 60 to 66% are obtained, although the theoretical maximum efficiency possible is $\pi/4$, or 78.5 percent.

The accompanying figure shows typical waveforms developed in the Class B amplifier over two cycles of operation, and clearly illustrates the current and voltage relationships. In part A of the figure the input (grid) signal is shown as a sine wave, with an amplitude sufficient to exceed cutoff bias E_c and drive the grid slightly positive. Half-cycles (1) and (3) are identical, as are (2) and (4). However, the odd and even half-cycles are 180 degrees out of phase with each other. As the input signal swings positive, plate voltage E_b is reduced by the drop across load E_L until the peak value of input signal is reached. This corresponds to E_{min} , as shown in part B of the figure. Simultaneously, as shown in part C of the figure, the plate current of tube V1 increases to value I_{max} at the peak of the signal. As the input signal recedes and falls to the cutoff bias value, E_L decreases to zero (supply value of E_b) at cutoff. At this time, the plate voltage is that of the supply, and the drop across the load is zero. Actually, this is the time when idling or static current exists, and is some small value other than zero; it is indicated by the overlap of the current waveforms in part D of the figure. Part D also shows the plate currents for the two tubes, where i_{p1} is that for V1 and i_{p2} is that of V2. Current i_{p2} is shown dotted since it is 180 degrees out of phase with i_{p1} and occurs during the time V1 is cut off. With matched tubes these waveforms are identical,

and with unmatched tubes they vary slightly. (A 100% current difference will produce approximately 5% harmonic distortion.)

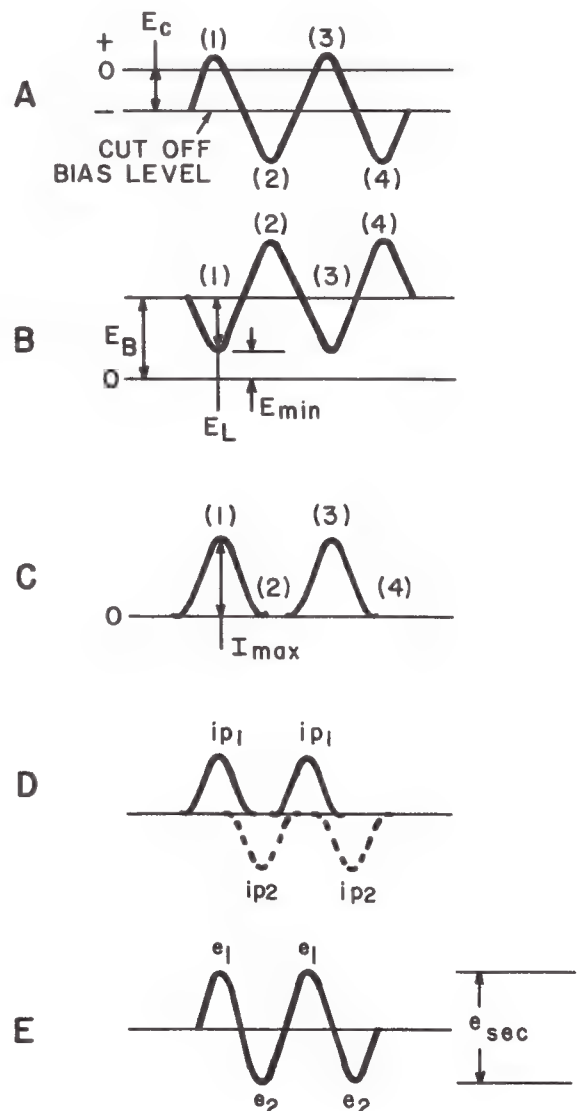The waveform for V2 is produced in exactly the same manner as that for V1 by the even-order half-cycles, (2) and (4) in the figure, while (1) and (3) keep V1 nonconducting. Part E of the figure shows the output voltage in the secondary of the plate trans-



Typical Class B Current and Voltage Waveforms

former. The positive and negative swings are produced through the primary on alternate half-cycles of operation. Thus, the output voltage is similar to the input voltage and is twice that produced by one tube.

For small-amplitude input signals, operation occurs around the point of idling or static (zero) current. In this region the characteristic of each tube is extremely nonlinear and much distortion occurs. However, when large input signals are applied, this area represents only a small fraction of the range; hence its effect is negligible. This nonlinearity at the zero bias point, plus that caused by grid current flow, and unmatched plate currents caused by a difference in tube characteristics, add together to increase the total harmonic distortion. Thus, the Class B amplifier always has more inherent distortion than either the Class A or AB amplifier.

Other Considerations. A special form of Class B operation is that known as Class B *quiescent* operation. In this case the operation is B_1 , that is, the grids are never driven into the positive region. This type of operation is essentially similar to Class AB operation, except that the bias is higher. Because the grids are not driven positive, less distortion is produced and less driving power is required. However, the extremely large output obtained with B_2 operation is not possible; thus it finds rather limited use. Since the theory of operation is similar to those types discussed above, it will not be further explained in this handbook.

Because of the extremely large fluctuations of current and voltage which occur in the typical Class B amplifier, and because some tubes exhibit a negative resistance effect over part of the cycle, transients may be produced and parasitic oscillations sometimes occur in the grid or plate circuits. These undesirable effects are eliminated by placing small bypass capacitors between the cathode and grid or across the primary of the plate transformer. In some instances, in the plate circuit, a series R-C combination may be placed from plate to plate. In such cases, these components act as simple high-pass filters to reduce transient response. They are not essential to the operation of the circuit, and serve only to prevent the possibility of undesired parasitics. The insertion of these components and the determination of their values are design problems not concerned with circuit operation.

Failure Analysis.

No Output. Lack of an input signal, defective input or output transformers, lack of plate or filament voltage, or a defective tube can cause a no-output condition. The presence of plate or filament voltages can be determined by a voltage check. Use an oscilloscope or a vacuum-tube voltmeter to determine whether an input signal exists. Follow the signal through the circuit; when the signal disappears, the trouble will be localized. While an open input winding (T1 primary) will prevent the development of an output signal, either secondary may be open without stopping operation; in this case the circuit will operate on one tube with reduced output. Likewise, in the plate transformer (T2), while an open secondary will prevent any output, an open primary will not (unless both halves are open). Loss of plate voltage on one tube with normal supply voltage indicates that half of the primary is open. One defective tube will not prevent output; however, if both tubes are defective there will be no output. While short circuits across the input can cause loss of output, it is rather unlikely except where capacitors are placed from grid to cathode or from plate to plate in order to prevent transients and parasitics. If such capacitors are used and no output is observed, the capacitors are probably shorted. A resistance check of the windings *with the power off* will indicate continuity; a resistance reading of less than 1 ohm will probably indicate a short circuit.

Reduced Output. Many conditions can cause reduced output. The most common cause is loss of amplification in one tube. This condition can result from a defective tube, loss of filament or plate voltage, or a short circuited condition. Remove one tube and then the other. If one half of the circuit is operative, the output will be reduced considerably or cease entirely when the good tube is removed. If the tube removed is defective, the output will not change; it may even increase. Loss of plate voltage to one tube can be determined by a voltage check. Visual indication such as the plate showing color indicate excessive plate dissipation in the good tube. However, this is only a relative check, since a short circuit can also exist in the tube showing color. An oscilloscope waveform check will show definitely whether one tube is operating normally, but not the other tube. If this is the case, the plate voltage and bias may be

checked on the inoperative tube to determine the fault.

With normal plate, filament, and grid voltages but with reduced output, the trouble is either a tube (or tubes) or a short-circuited (grounded) transformer winding. Check the output load or device, since improper loading will cause reduced output.

Distorted Output. Improper bias, plate voltage, or load impedance, as well as overdrive, will cause distortion. Distortion resulting from poor frequency response may be caused by poor transformer construction, and also by improper loading. If the transformer is defective, replace it. Also, examine the load to make certain that it is of the proper value. Check for the proper bias and plate voltage with a high-resistance voltmeter. Use an oscilloscope to determine the grid drive and observe the waveform. Excessive second-harmonic content in a Class B amplifier indicates distortion in a previous stage, or non-linearity of a tube (or tubes). Check the tube for matched currents, or substitute a pair of tubes known to be matched and note whether the response improves. With matched currents (linear response), very little second-harmonic distortion will be present. With unmatched tubes, a 10% difference in currents can produce as much as 5% distortion. In a Class A or AB push-pull amplifier, second-harmonic distortion indicates that the tubes are improperly loaded or that one tube is defective, since this type of distortion will cancel out in the secondary if the circuit is operating normally. If balanced adjustments for bias and plate current are provided in the equipment, a readjustment will probably return the operation to normal. Operate Class A or AB stages with one tube in the circuit at a time and note on an oscilloscope whether both circuits perform identically, observing the waveform at both the input and the output. The source of distortion should be obvious. When Class B stages are operated with one tube only, the output will be highly distorted; both tubes are necessary to minimize distortion.

PUSH-PULL AUDIO POWER AMPLIFIER (SEMICONDUCTOR) (CLASS A, AB, AND B)

Application.

The push-pull transformer-coupled transistor audio amplifier is used where high power output and good

fidelity are required. For example, it is used in receiver output stages, public address amplifiers, and AM modulators.

Characteristics.

Collector efficiency is high with moderate power gain.

Requires twice the drive of a single transistor stage.

Power output is more than twice that of the single transistor stage.

Second and higher even-order harmonic distortion is cancelled.

Distortion varies with the class of operation; it is least for Class A operation, and greatest for Class B operation.

Collector efficiency varies with the class of amplifier, from 50 percent maximum in Class A to 78 percent maximum in Class B, with an intermediate value for Class AB.

Fixed bias is usually used, but self-bias may be encountered in some Class A applications.

Operates as a large-signal amplifier for all except very small inputs.

Emitter swamping is used for thermal stabilization.


Circuit Analysis.

General. The semiconductor push-pull audio power amplifier is similar to the electron tube version discussed previously in this section of the handbook. Use of the common (grounded) emitter circuit allows use of the analogy that the base of the transistor is equivalent to the electron tube grid, the emitter equivalent to the cathode, and the collector equivalent to the tube plate. Examination of the accompanying schematic reveals that the transistor push-pull circuit is practically identical to the electron tube push-pull circuit. Any differences are due to the transistor internal parameters and the matching requirements to obtain maximum power output with minimum distortion.

Push-pull amplifiers can be operated Class A, Class AB, or Class B, as determined by the amount of forward bias. Like the electron tube push-pull circuit, the least amount of distortion and power output is produced in Class A operation, and the greatest amount of distortion and power output is obtained in Class B operation. Class AB stages operate between these levels of distortion and power output. For a given equipment and type of transistor, selection of

the operating bias, distortion, and power output is a design problem. The following discussion will cover each type of operation; although the different types of operation are similar, there are significant differences among them.

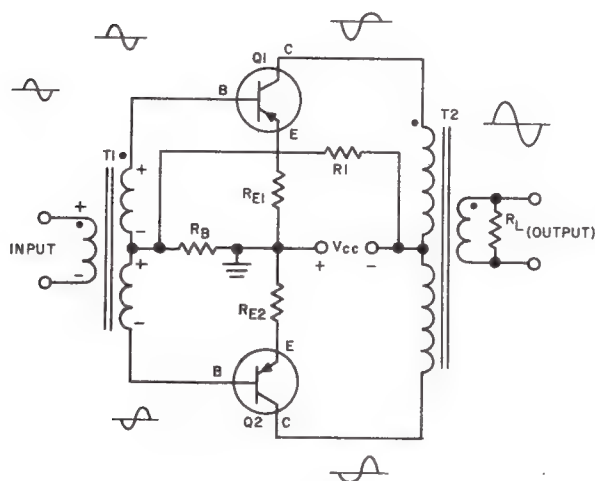Circuit Operation. The following schematic shows a PNP push-pull, transformer-coupled output stage. The load resistance may be a loudspeaker, a Class C r-f stage, or other type of load. The load is considered to be resistive unless stated otherwise in the text.



**Push-Pull Transformer-Coupled Translator
Power Amplifier**

The input signal is applied to the base of both transistors through transformer T1. The polarity for the positive half-cycle of input is shown on the schematic to facilitate proper understanding of the operation. Note that when the top end of the secondary of T1 is positive, the bottom end is negative. Thus, equal and oppositely polarized signals are applied to the base of transistors Q1 and Q2 when an input signal appears in the primary of T1.

The input signal is obtained from a preceding driver power amplifier stage. Very little power is required for Class A operation; increasingly more drive power is required for Class AB and Class B operation. The actual amount of drive power needed depends upon the circuit design and the transistors used; it is on the order of 2 or 3 percent of the output. Transformer input coupling is used to provide maximum drive power and proper matching of the driver stage. Fixed

bias from the collector supply is applied through voltage divider resistors R_1 and R_B . Resistors R_{E1} and R_{E2} are the emitter swamping resistors, which are left unbypassed to provide a slight amount of degeneration. Refer to the introduction to this section of the handbook for a discussion of bias arrangements and bias stabilization methods. The collector load consists of the primary resistance of output transformer T2 plus the resistance reflected from the load connected across the secondary.


Class A Operation. With no input signal, the stage is resting in its quiescent condition, drawing heavy collector current and operating at the point of lowest efficiency. Since no change in collector current occurs, no output voltage is induced in the secondary of T2. Assuming a positive input swing on the base of Q1 and an in-phase connection of T1, the positive voltage of the signal subtracts from the normal forward (negative) bias, effectively reducing the base bias and causing less collector current to flow in Q1. As the collector current is reduced, the changing lines of magnetic flux between the primary and secondary of T2 induce a voltage in the secondary. At the peak of the input signal, the collector current of Q1 is reduced to a small value, and the collector voltage approaches the supply voltage (reaches its most negative value). Thus, the common emitter circuit makes the polarity of the output signal opposite that of the input signal. Simultaneously, the input signal in T1 is applied as a negative voltage swing to the base of Q2 (the ends of the secondary winding are oppositely polarized when a voltage is induced), which adds to the forward bias of Q2. The increase in forward bias causes an increase in the collector current through the primary of T2, and induces an in-phase voltage in the secondary of the output load.

The net result of the input signal is to decrease the signal output of Q1 and to increase the output of Q2. These induced output voltages are combined in the secondary of T2 to produce the effect of a collector current equivalent to twice that of a single transistor. Note that this action is the same as the action that occurs in the electron tube push-pull circuit. In the same manner, the collector-to-collector (plate-to-plate) load impedance is also four times the load, since the primary-to-secondary turns ratio is based on a one-to-one ratio of half the primary to the secondary.

During the negative half-cycle of input signal excursion, the opposite action occurs. The negative

signal adds to the negative forward bias and increases the collector current of Q1. Meanwhile, the base of Q2 is driven positive at the same time Q1 is driven negative. The positive increase in the input signal reduces the forward bias and causes the Q2 collector current to decrease. Again, the net result is the same as if twice the collector current of a single stage were involved in flowing through T2. Note also that the collector current flows in opposite directions through the two halves of the primary of T1, so that any in

phase primary-induced voltage components are cancelled out (second and all even harmonics); thus, the output voltage unduced in the secondary consists of the fundamental component and any odd harmonics. The manner in which the second-harmonic component is cancelled out in the secondary is shown in the following illustration. In part A of the figure, the positive signal is enhanced by the second harmonic, while the negative signal is reduced. In part B, the opposite action is shown for the second half-cycle of operation. The separate resultant waveforms are shown in part C. In part D, they are combined together to form a complete amplified signal with no second-harmonic content.

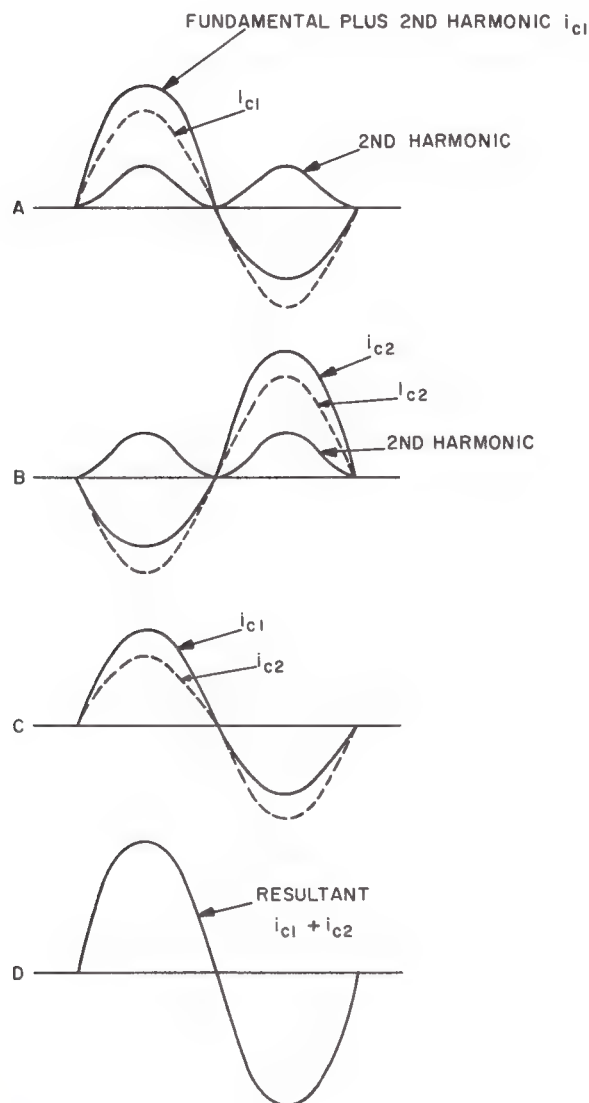

Elimination of 2nd Harmonic


For Class A operation, maximum output efficiency and the least dissipation are obtained with maximum signal swing. To make certain that the power dissipation ratings of the transistor are not exceeded, only half the maximum permissible collector voltage is applied, since the applied voltage tends to double because of the inductive effect of the transformer. For Class A operation, the transistor is biased and operated at the center of the forward transfer characteristic curve, so that equal base current swings will produce approximately equal collector current swings; thus, it functions as a large-signal amplifier. Since a large-signal amplifier operates over a much greater range of current and voltage than a small-signal amplifier, circuit design is accomplished graphically, using the actual transistor currents to determine the range over which minimum distortion and maximum power output can be obtained. Usually, the transistor is slightly less linear than the electron tube, but with good design its operation compares favorably with electron tube operation.

Since much heat is dissipated at the collector for large power outputs, the shell of the power transistor is usually connected firmly to the chassis for direct conduction and reduction of heat (chassis acts as a heat sink). Where the shell must be insulated from the chassis, it is usually separated by a thin wafer of mica (or other suitable material) to prove insulation and yet allow full heat transfer.

Where minimum distortion is required, the transistors are selected in matched pairs, as is true with electron tubes. Because of the high power-handling capability required for Class A operation, transistors are usually operated Class B or Class AB.


Class B Operation. In true Class B operation, the bias is such that no collector current flows for one-half of the cycle. Thus, each transistor reproduces only half of the cycle, and two transistors are required to faithfully reproduce any signal (an exception is the Class B r-f amplifier, discussed later in this section, which uses a tank circuit and amplifies only a single frequency). Since at cutoff a reverse current flows in the transistor, collector current is never completely cut off, and a small quiescent current flows during the inactive half-cycles of transistor operation. (This quiescent reverse current should not be confused with the small forward current which flows in Class AB operation because the bias is not at cut off.)

For two transistors completely biased off, the forward transfer characteristics as shown in the following illustration. The two transfer curves are placed back-to-back to make the complete dynamic operating curve. Note how this curve is rounded off at the beginning and at the end instead of being a straight line. This is typical of the nonlinearity obtainable at cutoff, and illustrates why Class B operation produces the greatest distortion.

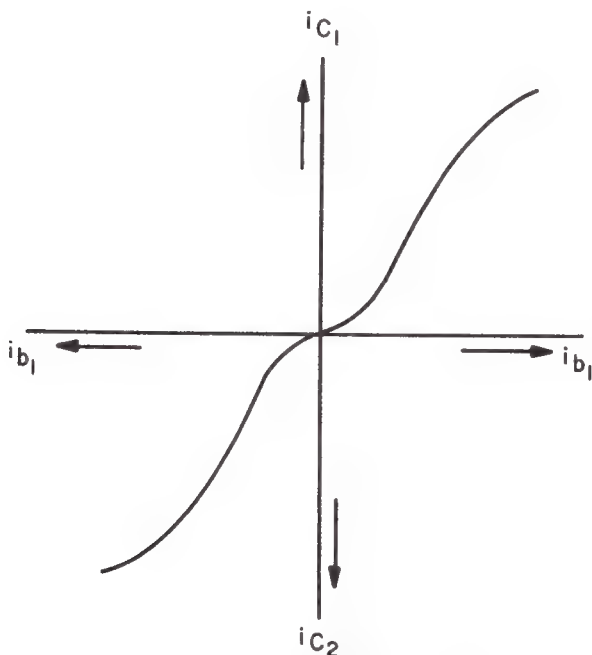

Composite Current Transfer Characteristic,
Class B Operation

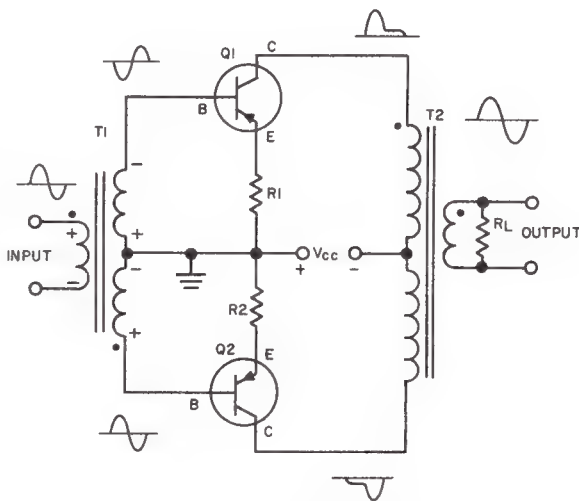The accompanying circuit is that of a typical Class B stage operated with zero bias. Emitter swamping resistors R_1 and R_2 are used for thermal compensation, and are unbypassed to provide a slight amount of degeneration.



Class B Push-Pull Stage

Note here one of the differences between the electron tube and the transistor. At zero bias the conventional electron tube conducts heavily, and it is necessary to apply considerable negative bias to achieve Class B operation. On the other hand, the transistor always has the collector reverse-biased; thus, in the absence of a forward base bias (that is, at zero bias), no collector current can flow. In this respect the transistor is similar to specially constructed Class B (zero bias) electron tubes.


When a signal is applied to input transformer T_1 , a voltage is applied to the base of transistor Q_1 and an oppositely polarized voltage is applied to the base of Q_2 (the polarity for the initial half-cycle is shown on the schematic). With transistors Q_1 and Q_2 at zero bias, only reverse leakage collector current flows in the absence of a signal. When the input signal is applied, the flow of current in the primary of T_1 induces an oppositely polarized signal on the base of Q_1 (transformer connected out-of-phase). Thus, the positively swinging input appears as a negative (forward) bias on the base of Q_1 , causing collector current to flow in the top half of the primary of T_2 , and

induces an output voltage in the secondary. At the same time the input voltage applied to Q2 is opposite in polarity and produces a reverse bias, keeping Q2 cut off. During the entire half-cycle Q1 conducts while Q2 remains cut off. When the input signal reverses polarity, reverse bias is applied to cut off Q1 collector current, and forward bias is applied to Q2. Consequently, Q2 conducts and the increasing collector current through the bottom half of the primary of T2 induces a voltage in the secondary of the output transformer. During this half-cycle Q1 remains cut off while Q2 conducts. Thus, Q1 and Q2 alternately conduct when the input signal produces a forward bias. Since the outputs of Q1 and Q2 are combined in the secondary of the output transformer, the input signal is reproduced in amplified form, but of opposite polarity. If the output transformer is connected in-phase, the same polarity of output exists as in the primary; when it is connected out-of-phase, the opposite polarity exists. This transformer action is identical with that occurring in the electron tube push-pull circuit.

Since there is no heavy flow of quiescent current when no signal is applied, maximum dissipation occurs during the signal (at about 40 percent maximum collector current), and less heat is developed for the same signal as in a Class A amplifier. Hence the transistor can be driven harder to obtain greater efficiency and more power output than is obtained in the Class A stage. The flow of reverse leakage collector current represents a loss of efficiency since no useful action is produced by this current. Such current flow does not exist in the electron tube. To minimize this loss, transistors are selected for a low I_{CEO} . Since audio power is produced, the transistors heat during operation (a maximum of 78 percent efficiency is theoretically obtainable) and the reverse leakage current increases. Emitter swamping resistors R1 and R2 provide a small opposing bias voltage to prevent thermal runaway. They are not bypassed with capacitors as in Class A operation because the capacitors would charge during the operative half-cycle and discharge during the inoperative half-cycle, thus causing a change in bias. Because of the large peak current which flows through these resistors, they are kept to a very low value of resistance to prevent excessive degeneration and loss of amplification. In some applications, by proper selection of transistor types and good design they are not needed. In any event, when used, their main function is to provide

thermal stabilization; any beneficial depeneration which may occur from their use is only a secondary consideration. Otherwise, they have no effect on the operation of the circuit.

Since the transistors operate alternately in Class B operation, there is no basic cancellation of second and even-order harmonics in the output transformer as in Class A operation. There is, however, an increase in third-harmonic distortion produced when the waveform passes through zero (this is known as *crossover distortion*). The development of this type of distortion is shown by projecting a sine-wave input signal on the transfer characteristic curve, as shown in the accompanying illustration. The distortion is greatest for small input signals and least for large input signals. This distortion is eliminated by applying a small forward bias to the base-emitter junction of the transistors, or what amounts to operation as a Class AB amplifier. Class B operation is used only when the large amount of third-harmonic distortion can be tolerated.

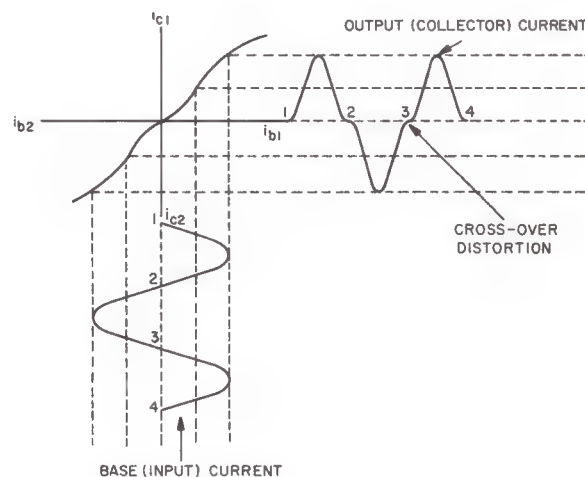

Development of Crossover Distortion


Class AB Operation. The schematic of the Class AB amplifier is basically identical with that of the Class A amplifier shown previously. The only difference is that bias voltage divider resistors R1 and R_B are of different values. Only a slight forward bias is applied, and only a small collector current flows with no signal applied. While this current is essentially wasted, it does eliminate the crossover distortion

which would be produced if the bias were reduced to zero. It is evident, then, that Class AB operation produces slightly less output than Class B operation. Because of the small resting current, the transistor can be driven harder than the Class A stage; consequently, greater output can be obtained than for Class A operation. The efficiency averages about 65 percent for a well designed Class AB stage.

The small resting current, like the average current drawn in Class A operation, cancels out the flux in the primary of the output transformer (each side flows in a different direction), and there is no output produced until a signal is applied. When the input signal is applied, Q1 conducts and Q2 is driven to zero conduction on one half-cycle, while on the other half-cycle Q2 conducts and Q1 is driven to zero. The resultant signal swings are unequal and con-


siderable second-harmonic distortion is produced in the primary of the output transformer; however, it is canceled out in the secondary when both signals are combined (assuming that the transistors are fairly well matched). Thus, only fundamental and third-harmonic distortion can exist in the output. This form of operation is identical with Class A operation except that more odd-harmonic distortion is produced because the transistors operate for less than 360 degrees of the cycle.

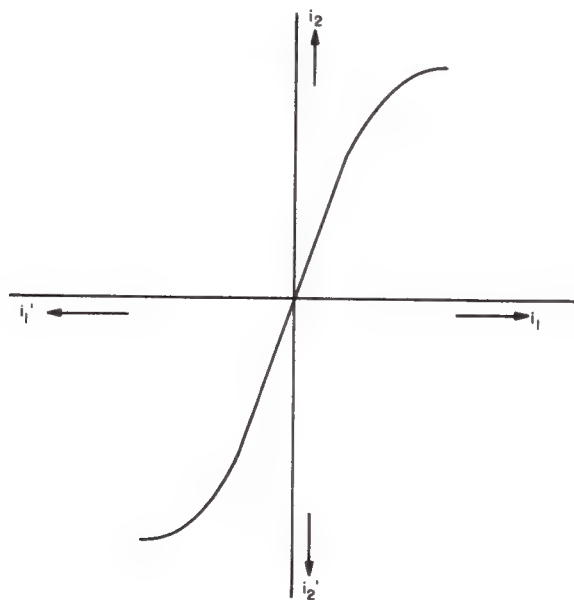The accompanying illustration shows the composite transfer characteristic for a typical Class AB stage. When compared with the transfer curve for the Class B stage shown previously, it is evident that the operation is more linear except for very large signal swings.



Composite Current Transfer Characteristics,
Class AB Operation

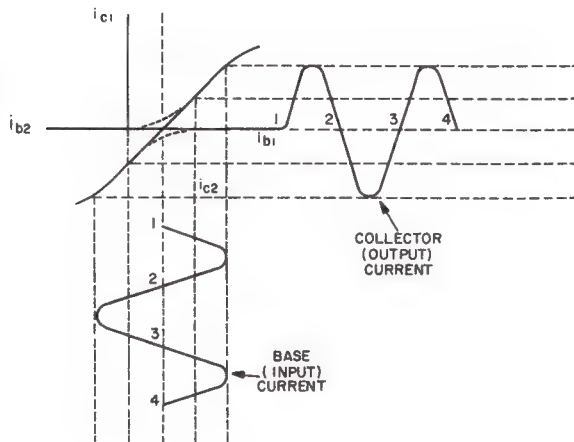Projection of the input signal on the composite transfer curve shows the collector output, which, when compared with that of the Class B stage shown previously, indicates the improvement in fidelity obtained with Class AB operation, and the total elimination of cross-over distortion.



Development of Class AB Signal

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance ordinarily employed on the low-voltage ranges. Be careful also to observe proper polarity when checking continuity with the ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. A no-output condition can be caused by an open circuit in either the input transformer, T1, or output transformer, T2, or in the swamping resistors, R_{E1} and R_{E2} as well as by lack of supply voltage. The supply voltage can be checked with a voltmeter, and lack of collector or base bias voltage can also be determined. Continuity checks of the transformer (WITH THE POWER TURNED OFF) will determine whether one or more of the windings are open, and the resistors can be checked for proper resistance with the ohmmeter. Normally, failure of the transistors will not cause complete loss of output unless both transistors fail completely.

Low Output. Lack of sufficient drive power, low supply voltage, improper bias, or a defective transistor can cause reduced output. The supply voltage and

bias can be checked with a voltmeter. Lack of drive power can be determined by observing the waveform with an oscilloscope and noting whether there is sufficient drive to cause eventual flat-topping or bottoming of the output waveform. A shorted or inoperative transistor can also cause low output. Depending upon conditions, removing the transistor (from a plug-in socket) will either increase or reduce the output. In the case of a shorted transistor, the output will probably increase when it is removed. A transistor with low gain or poor performance, when removed, will probably cause further reduction of the output. If the shorted transistor is left in the circuit and the good one is removed, there will also be a decrease in the output.

Distorted Output. Distorted output may be caused by lack of proper bias or supply voltage, by under-drive or overdrive, or by defective transistors or transformers. If one half of a transformer is open or shorted, one transistor will not operate properly and distortion will occur. Likewise, if the bias is too high, clipping will occur on the peak of the input signal, and if it is too low, collector bottoming will produce the same effect at the troughs of the signal. Transformer resistance and continuity can be checked with an ohmmeter, while the bias and voltage can be checked with a voltmeter. In Class A or Class AB stages, one half of the circuit can be inoperative and the unit will function with reduced output and increased distortion. Use an oscilloscope to observe the waveform, checking from input to output. When the waveform departs from normal, the cause of the trouble will usually be obvious.

PUSH-PULL, SINGLE-ENDED COMPLEMENTARY SYMMETRY AUDIO POWER AMPLIFIER (SEMICONDUCTOR)

Application.

The push-pull, single-ended complementary symmetry audio amplifier is used where high power output and fidelity are required. For example, it is used in receiver output stages, in public address amplifiers, and in AM modulators, where reduced weight and space is a prime requirement.

Characteristics.

Collector efficiency is high with moderate power gain.

Requires only half the drive of the conventional push-pull amplifier.

Power output is twice that of a single transistor stage.

No input or output transformer is used.

Distortion varies with the class of operation.


Usually is Class B biased, but may be biased Class A in some applications.

Fixed bias is usually used, but self-bias may be encountered in some applications.

Circuit Analysis.

General. *Complementary symmetry is unique with transistors, and has no electron-tube counterpart.* Recall from basic theory that a transistor may be either the PNP or NPN type, and that the bias and polarities are opposite. Thus, two different types of transistors may be used back-to-back to provide push-pull operation without the necessity for phase-inverting input and output transforms. An economic advantage is gained in that the cost of the transformers is eliminated, and a more uniform response is obtained since the reactive effects of the transformers are also removed from the circuit.

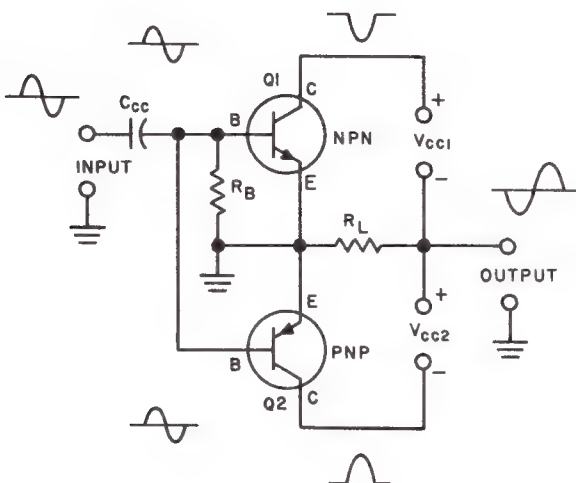Circuit Operation. The accompanying schematic shows a typical single-ended, common-emitter, push-pull complementary symmetry circuit. The operation in Class B at zero bias.



Zero Bias Complementary Symmetry
Push-Pull Circuit

Resistance-capacitance input coupling is used, with C_{cc} acting as the coupling capacitor and R_B as the base return resistance across which the input signal is applied. With both emitters grounded and no bias applied, the bases of the transistors are zero-biased at cutoff. No current flows in the absence of an input signal. When an input is applied, both bases are biased in the same direction. Since Q1 is an NPN transistor, the positive-going input signal produces a forward bias. Q2 is a PNP transistor and requires a negative potential for forward bias; the input signal has no effect other than to reverse-bias Q2 and hold Q2 in a cutoff condition. Thus, during the positive half of the input signal only Q1 conducts. During the negative portion of the input signal Q1 is biased off beyond cutoff by a reverse bias, and a forward bias is applied to Q2, causing collector current to flow for the entire negative half-cycle. Thus, each transistor conducts alternately for half of the cycle, and two transistors are required to reproduce the input signal. Note that the bases are connected in parallel, and, since only one transistor operates at a time, only enough drive for a single stage is required instead of twice the drive as in normal push-pull operation.


Because the transistors are of opposite types, two equal-voltage collector power supplies are required, one negatively polarized and the other positively polarized. (A single supply can be used with proper circuit changes, but twice the collector voltage of a single stage is required.) The load resistor, R_L (which may be the voice coil of a loudspeaker), is connected from the common connection between the power supplies and the emitters. In this instance the emitter end is grounded, so that the power supplies are actually floating above ground. When the input signal is applied and develops an output for each half-cycle, the output is added together in the common load and no transformer is required. To develop maximum power, a low-impedance is needed. Otherwise, if high-impedance loads are used, an output transformer will be required for proper load matching. In this instance, however, the winding need not be center-tapped since the output is single-ended. Because the output is single-ended (taken between the collector and ground), the collector load is calculated on the basis of the full primary-to-secondary turns ratio—not on one-half the primary-to-secondary turns ratio as in the conventional push-pull stage. Thus, the loading is 1/4 the normal push-pull output, which accounts for the low-impedance output.

In most electron tube or transistor circuits it is necessary to separate the dc component in the output from the output from the ac component by capacitive or transformer coupling (except in the special case of the dc amplifier). In the complementary symmetry arrangement such provisions are unnecessary. Both dc power supplies are connected in series with the transistors, and only one transistor is operative at a time; thus, there is no net flow of dc around the circuit. When Q1 conducts, there is a flow of current through R_L , the transistor, and the power supply in one direction. When Q2 conducts, the flow is through R_L , Q2 and the power supply in the opposite direction; thus, there is no circulating current, and the dc is effectively removed from the load circuit since only the continuous flow of dc, since the circuit flows out of the base when Q2 conducts, and into the base when Q1 conducts. Therefore, the charging and discharging of the coupling capacitor and its possible effect on changing the base bias are of no consequence in this circuit.

In the preceding discussion it was assumed that the transistors are balanced (or matched), having identical gain and collector currents. Like the conventional push-pull amplifier, this matching is necessary to obtain maximum output with minimum distortion. Unlike the electron tube circuit, which uses identical plate voltages and matches the plate current, the complementary symmetry circuit has identical collector (plate) currents since the transistors are series-connected and the biasing is adjusted to equalize the collector voltages. In the case of Class A or AB operation, the bias point in the base circuit is affected by drive and base current drain. Thus, keeping the signal from affecting the bias is one of the important design problems. So far as the technician is concerned, the practical effect is that with better design less distortion is obtained, with a maximum of amplification.

Better performance is obtained from the common-collector circuit when complementary symmetry is employed; even though the common-emitter circuit is the more widely used configuration. Although the over-all gain and output are slightly less, the stability of the circuit is improved; the collector supply can be grounded instead of floating (which reduces power supply ripple), and the effect of negative feedback is obtained, thus requiring less closely balanced transistors and improving fidelity and response characteristics. Both circuits are

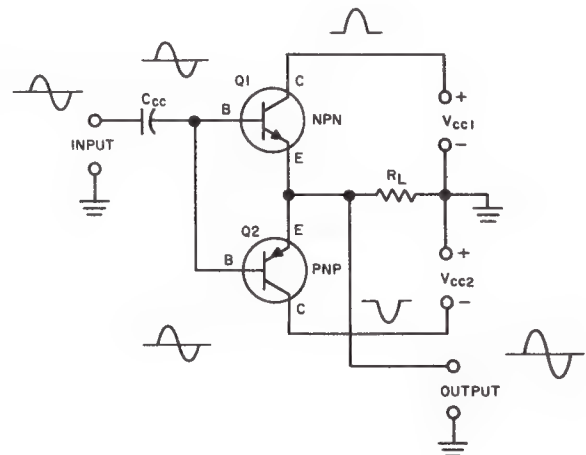identical except that the ground is removed from the emitters and placed on the common power supply connection, as shown in the accompanying schematic.




Common (Grounded) Collector Complementary Symmetry Push-Pull Circuit

As in other common-collector circuits, no polarity inversion of the output signal occurs, so that the inputs and outputs are of the same polarity. In operation, the circuit functions in the same manner as the common-emitter push-pull complementary-symmetry amplifier previously described. Only one transistor operates at a time, zero bias is employed, and the output is taken from the emitters to ground. Collector current flows through Q1, power supply V_{cc1} , and load resistor R_L in one direction, and through V_{cc2} , Q2, and R_L in the opposite direction, as the transistors are alternately forward-biased by the input signal. There is one difference, however, in that more input (drive) voltage is required to obtain full output because of the degenerative effect of connecting the load between the emitters and ground.

The accompanying schematic shows the complementary symmetry push-pull circuit connected for use with a single power supply, and with feedback from collector to base. Connecting capacitor C1 in series with load resistor R_L permits the use of a single power supply. Since no dc normally flows through the load, the insertion of the blocking capacitor has no effect on either ac or dc operation. Since both transistors are connected in series with the power

supply, twice the dc voltage of one supply is necessary. In addition, resistors R_1 and R_2 are employed to provide a fixed base bias and a slight amount of feedback from collector to base. The feedback reduces the matching requirements, and the dc bias is adjusted by selecting the values of R_1 and R_2 so that equal collector voltages are obtained (with the series connection of transistors the same value of current flows throughout the circuit).

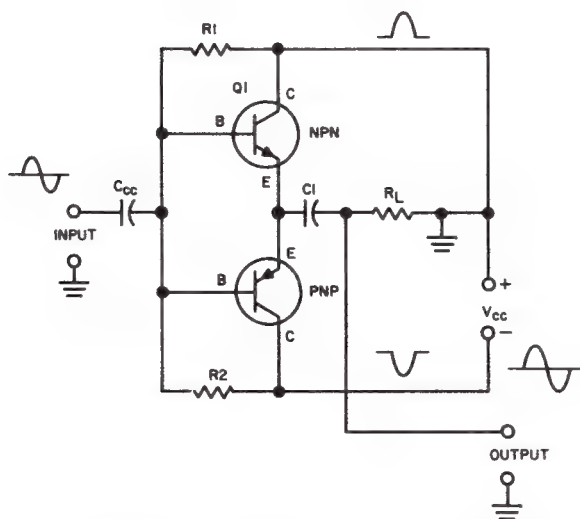

**Complementary Symmetry Push-Pull Amplifier
with Common Power Supply**

As far as dynamic operation is concerned, it is also identical with that of the previously discussed common-emitter complementary symmetry circuit. When a forward bias is applied by the signal, the transistor conducts. With a sine-wave input signal applied, a sine wave of current flows (at audio frequencies) through capacitor C_1 and load R_L to develop the output signal.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low-voltage ranges of most volt-ohm-milliammeter testers. Be careful, also, to observe proper polarity when checking continuity or making resistance measurements with the ohmmeter, since a forward bias through any

of the transistor junctions will cause a false low-resistance reading.

No Output. An open or short circuit in the power supplies or transistors, or an open coupling capacitor or load resistance can cause no output. A voltage check will indicate whether the proper voltage and polarities are applied. Since Class B zero bias operation is normally employed, no base-to-emitter (or ground) voltage exists in the absence of a signal. However, if an attempt is made to measure this voltage with a meter, a false reading may be obtained through the voltmeter shunting resistance. Therefore, only the polarity and supply voltage should be checked, and the input signal should be observed with an oscilloscope. Lack of input signal on the oscilloscope indicates an open coupling capacitor, C_{cc} , or a shorted input circuit caused by a defective transistor. If the supply voltage and polarity are correct and a signal is visible at the input, but not in the load, either the transistor is defective or the load is shorted. A resistance or continuity check will determine whether the load is normal. If it is normal, only the transistors can be at fault. Since only one transistor is operative at a time, both transistors must be defective to cause a loss of output; otherwise, a reduced or distorted output exists.

Reduced Output. If one of the transistors is defective, or if one of the supply voltages is low or the supply is defective, a loss of output will occur. Use an oscilloscope to observe where the input waveform or output waveform departs from normal. Check to make sure that there is sufficient drive in the preceding stages. A leaky coupling capacitor will place a fixed bias on the base circuit, causing conduction in one transistor and rendering the other inoperative. Depending on the amount of bias, the circuit may be such as to very slightly reduce the output or to cause severe distortion. Unbalanced collector voltages, if sufficiently different, will cause loss of amplification and distortion on one side of the circuit, which can be observed on the oscilloscope. Since there are only a few components in the circuit, a resistance and voltage check should quickly indicate whether the components or power supply is defective.

Distorted Output. Improper bias or load resistance can cause a distorted output. Use an oscilloscope to determine where the signal departs from normal. The trouble will then be localized to that portion of the circuit showing the distorted waveform. In the

common-emitter circuit, if the distortion occurs on the negative portion of the waveform, the trouble is in the PNP transistor circuit, if it is on the positive portion of the waveform, the trouble is in the NPN transistor circuit. Since there is no inversion of polarity in the common-collector circuit, the indications will be the opposite. That is, distortion on the positive waveform indicates trouble in the NPN transistor circuit, and distortion on the negative waveform indicates trouble in the PNP circuit.

PUSH-PULL, SINGLE-ENDED, SERIES-CONNECTED AUDIO POWER AMPLIFIER (SEMICONDUCTOR)

Application.

The push-pull, single-ended, series-connected audio amplifier is used where high power output and fidelity are required. For example, it is used in receiver output stages, in public address amplifiers, and in servo amplifiers, where compactness and reduced weight through elimination of the output transformer are desired.

Characteristics.

Collector efficiency is high with moderate power gain.

Requires the same drive as a conventional push-pull amplifier.

Power output is twice that of a single transistor stage.

No output transformer is required, and identical types of transistors are used.

Distortion varies with the class of operation.

Class B bias is normally used, but Class A or AB applications may be encountered.


Fixed or zero bias is normally employed, but self-bias may be used in some applications.

Circuit Analysis.

General. The series-connected, single-ended push-pull amplifiers used two similar-type transistors in the equivalent of the complementary symmetry circuit to provide a transformerless output. It requires fewer components than the conventional push-pull amplifier, but more than that of the complementary symmetry amplifier, since a push-pull input is necessary; it is single-ended in the output only. A compound-connected transistor input circuit may be

used; however, since this circuit requires two additional transistors, an input transformer is usually used instead. Because of the series transistor connection, two separate collector supplies are required, or a center-tapped supply that is twice the value of a single supply is necessary.

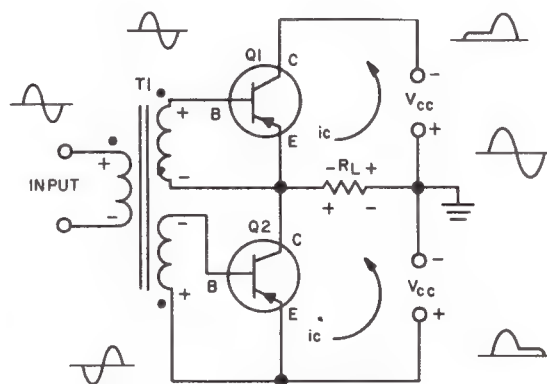Circuit Operation. The schematic of a typical single-ended, series-connected push-pull PNP audio amplifier is shown in the accompanying figure.



Single-Ended, Series-Connected PNP Push-Pull Amplifier Circuit

Note: Read the Direct-Coupled Audio Amplifier circuit discussion earlier in this section for background information.

Transistors Q1 and Q2 are zero-biased and are non-conducting in the absence of a signal. Both transistors are the PNP type. The input transformer has two separate windings rather than the center-tapped arrangement conventionally used in push-pull circuits, to provide out-of-phase (opposite-polarity) input signals to the series-connected common-emitter stages. This provides an input connection which is separate for each transistor; the base of Q1 is driven positive while the base of Q2 is driven negative, and vice versa. With Class B, or zero bias, only one transistor operates at a time. One of the secondaries of T1 is connected so as to invert the signal. Thus, on the positive input signal, Q2 is driven negative and the forward bias causes conduction; meanwhile, the base of Q1 is held at cutoff by a positive input. On the opposite half-cycle, Q2 is held at cutoff while Q1 is driven to

conduction by the negative input signal. In this example the secondary connected to Q1 is connected in-phase, while the secondary connected to Q2 is connected out-of-phase.

The load, R_L is connected from the common point of the two power supplies to the emitter of Q1 and the collector of Q2. Disregarding this load connection for the moment, it is clear from observation of the schematic that the two transistors are connected in series with each other and their separate power supplies. In the absence of an input signal no current flows, and, since each transistor conducts separately, with current flow in opposite directions through R_L there is no net flow of dc through the load in one direction to unbalance it. Therefore, the voice coil of the speaker may be placed directly in this circuit to act as a load, without requiring any dc isolation through coupling capacitors or transformers.

When collector current flows in Q1, the electron path is from the emitter, through R_L and the power supply, back to the collector. When collector current flows in Q2, the electron path is from the emitter of Q2, through the power supply and load R_L , back to the collector. These currents flow in opposite directions through the load resistor, each producing one half-cycle of the signal. There is no continuous flow of dc through the circuit or through the load. In Class A or Class AB stages, a forward bias is supplied to the base, and both transistors conduct continually. DC flows through the series transistors and power supplies, but does not flow through the load resistor. This action occurs because, with a balanced circuit and identical collector current flow in both transistors, equal but opposite voltages are developed across the load resistor; therefore, they cancel, producing an effective zero dc flow through the load.

In Class A operation, any second-harmonic current is canceled out in the load as in conventional push-pull circuits. In Class B operation, there is no cancellation of second-harmonic current, and the predominant distortion is third harmonic. Thus, regardless of the method by which it is obtained, second-harmonic distortion is reduced in this circuit as in the conventional push-pull circuit.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance ordinarily employed on the low-voltage ranges of conventional volt-ohmmeters. Be

careful also to observe proper polarity when checking continuity with the ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. A no-output condition can be caused by an open- or short-circuited input transformer, T1, or load, R_L , as well as by a lack of supply voltage. The supply voltage and the collector or base bias voltage can be checked with a voltmeter. Continuity checks of the input transformer windings (or the load) will locate any open circuits, and short-circuited windings (or load) will be indicated by ohmmeter readings of less than 1 ohm. In Class A or AB stages the bias resistors can be checked for proper values with an ohmmeter. Normally, failure of the transistors will not cause complete loss of output unless both transistors fail completely.

Low Output. Lack of sufficient drive power, low supply voltage, improper bias, or a defective transistor can cause reduced output. The supply voltages and bias can be checked with a voltmeter. Lack of drive power can be determined by observing the waveform with an oscilloscope and noting whether there is sufficient drive to cause eventual flat-topping or bottoming of the output waveform. Either a shorted or otherwise inoperative transistor can cause low output. Depending upon conditions, removing the transistor (from a plug-in socket) will either reduce or increase the output. In the case of a shorted transistor, the output will probably increase when it is removed. Where the transistor has low gain, a slight reduction of output will usually be noted when it is removed. If the defective transistor is left in the circuit and the good one is removed, a decrease in the output will also be observed.

Distorted Output. Distorted output may be caused by lack of proper bias or supply voltage, by underdrive or overdrive, by defective transistors, or by a defective input transformer. If the primary winding of the input transformer is open, either no output will occur or a very low output may be obtained by capacitive coupling between the turns. However, if either one of the secondary windings is open or shorted, one transistor will not operate properly and distortion will occur. Likewise, if the bias is too high, clipping will occur on the peak of the input signal; if it is too low, collector bottoming will produce the same effect at the troughs of the signal. Transformer resistance and continuity can be checked with an ohmmeter, while the bias and collector

voltages can be checked with a voltmeter. In Class A or Class AB stages, one half of the circuit can be inoperative and the unit will still function with reduced output but with increased distortion. Use an oscilloscope to observe the waveform, checking from input to output. When the waveform departs from normal, the cause of the trouble will usually be obvious.

PUSH-PULL, CAPACITANCE-DIODE COUPLED AUDIO POWER AMPLIFIER (SEMICONDUCTOR)

Application.

The push-pull, capacitance-diode-coupled audio amplifier is used where high power and fidelity are required in receiver output stages, public address systems, and modulators. It is usually employed as the power output stage of a resistance-coupled amplifier.

Characteristics.

Collector efficiency is high with moderate power gain.

Requires the same drive as a conventional push-pull amplifier.

Power output is twice that of a single stage.

No input transformer is used, and identical types of transistors are used.

Input circuit is push-pull (oppositely polarized signals from either a phase inverter or a push-pull drive are required).

Distortion varies with the class of operation; operation may be Class A, AB, or B, with Class AB use predominating.


Fixed bias is normally used, but self-bias may be encountered in some applications.

Circuit Analysis.

General. The capacitance-diode-coupled push-pull amplifier differs from the conventional push-pull amplifier only in the input circuit. Diodes are used to prevent the charging or discharging of the coupling capacitor from producing a shift of base bias with signal, and causing distortion. The use of capacitive coupling eliminates the necessity for an input transformer and provides a reduction in weight and space, and an increase in economy. Any improvement in response characteristics through elimination of the

input transformer and its reactive effects are somewhat minimized by the shunting and loading effects of the diodes. Thus, the operation and performance are substantially the same as the conventional transformer-coupled push-pull amplifier, with a slight improvement in the high-frequency response.

Circuit Operation. The accompanying schematic shows a typical push-pull, capacitance-diode-coupled PNP transistor audio amplifier. The operation is considered to be Class B with a slight forward bias to eliminate crossover distortion (actually Class AB), as determined by voltage divider resistors R3 and R4. Because diodes CR1 and CR2 are connected in series opposition across the input, and are isolated by coupling capacitors C1 and C2, conduction through the diodes is necessary to establish a bias on the base of the transistors. With R4 connected between the diodes and ground, a slight negative voltage appears at their cathodes, so that they normally conduct slightly. In the absence of an input signal, conduction through CR1 and CR2 permits a continuous flow of dc base current, which, in turn, permits a small idling collector current to flow through the forward-biased bases. This static (quiescent) current flows in opposite directions through the primary of the push-pull output transformer, T1, and the effective flow is zero. No secondary output occurs because the flux in each half of the primary of T1, produced by dc current flow, cancels (as in conventional push-pull operation).

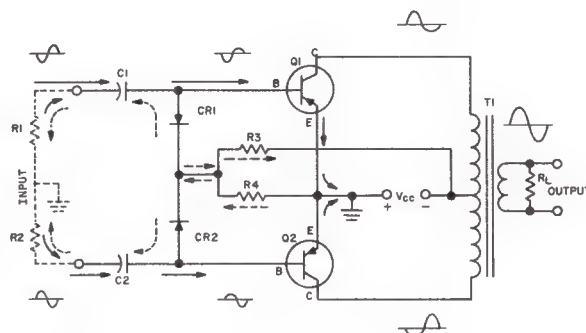

Capacitance-Diode-Coupled Push-Pull Stage

When an input signal is applied, oppositely polarized signals are supplied to coupling capacitors C1

and C2 simultaneously. (Resistors R1 and R2 represent the driver stage output resistance, normally taken between the driver stage collector or emitter and ground.) With a negative-going sine wave signal applied through C1, a forward bias is applied to the base of transistor Q1, causing collector current to flow through the upper half of the primary of T1 into Q1. At the same time, a positive-going input signal is applied through C2 to the base of Q2, producing a reverse bias, and reducing collector current flow through the lower half of the primary of T1 into Q2. Since Q2 is normally producing only a small current flow, this reduction in forward bias drives the transistor nearly to cutoff. Thus, the current in Q2 is reduced while the current in Q1 is increased (this is conventional push-pull action.) When the negative input signal is applied to Q1, it also reverse-biases the anode of CR1, and the diode appears as a very high resistance; therefore, the input signal is not bypassed to ground via R4, and there is no effect on the bias circuit. On the other hand, when the positive input signal is applied to CR2 and the base of Q2, the diode is forward-biased and it conducts heavily. This action permits C2 to discharge rapidly through the low resistance of CR2 and R4 to ground on one side, and from ground through R2 to the other side of C2, as shown by the dotted arrows in the schematic. The electron flow path is from ground through R4, and CR2 to C2 on one side, and from ground through R2 to the other side of C2. Thus, a small instantaneous positive voltage is developed across R4. This voltage further reverse-biases CR1 so that it cannot conduct and affect the operating bias. If CR1 and CR2 were resistor (instead of diodes), the voltage developed through these resistors would appear in series with the bias applied to both transistors and cause a shift in operation. The bias developed would add to the normal bias and place the total bias in the Class C region of operation, thus producing serious distortion and clipping.

With Q1 conducting because of the negative input signal, capacitor C1 charges quickly through the low resistance of the base-emitter junction of Q1 and ground, as shown by the solid arrows in the schematic. When the sine-wave input signal becomes positive-going on the opposite half-cycle, the base of Q1 is reverse-biased and the collector current is reduced. At the same time, CR1 is forward-biased (by the positive input signal) and C1 is quickly discharged through R4 to ground on one side, and through

ground and R1 to the other side of C1. The voltage developed across R4 has no effect on the operating bias, since CR2 is reverse-biased while Q2 is conducting. In addition, it should be noted that the voltage produced across R4 by the discharge of C1 or C2 is polarized in a direction opposite that of the normal bias produced by the voltage divider action of R3 and R4. Since the signal is never allowed to exceed the bias, to prevent distortion, this reverse bias is only a fraction of the operating bias and is thus effectively swamped out of the circuit. Only through failure of one of the diodes can it affect the operation of the circuit.

The operation of the collector and output circuits is exactly the same as previously explained for the conventional push-pull amplifier. Second- and even-harmonic distortion is cancelled in the primary of the output transformer, and the output contains only the fundamental and odd harmonics. The collector-to-collector load resistance is 4 times that of the individual collector-to-ground load, as in the conventional push-pull circuit. Since the input circuit uses the reverse-biased diode resistance as the base-to-ground impedance, the capacitance-diode input circuit offers a high input impedance. Thus, the moderate output impedance of common-emitter phase-inverting driver stages may be conveniently matched.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low-voltage ranges of most volt-ohm-milliammeter testers. Be careful, also, to observe proper polarity when checking continuity or making resistance measurements with the ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. Open coupling capacitors, defective transistors, or a defective output transformer can cause a no-output condition. Observe the signal with an oscilloscope, checking from input to output. Lack of a base signal indicates that coupling capacitors C1 and C2 are open; lack of a collector signal indicates either defective transistors, an open primary on T1, or an open collector supply (check the supply with a voltmeter). Lack of an output across the secondary indicates an open secondary winding. Note that since each transistor will operate separately, a distorted output can be obtained if only one half of the circuit

is defective. Thus, both coupling capacitors, both transistors, or both halves of the primary of T1 must be open simultaneously for a no-output condition. Likewise, in the case of a short circuit, one half of the circuit must be biased off while the other is shorted to cause no output. Only an open circuit or a short circuit of the T1 secondary can produce a no-output condition by failure of a single part.

Low Output. Low output can be caused by a number of conditions. Failure of one half of the circuit, regardless of cause, will result in reduced output. If bias resistor R4 opens, the forward bias will increase and full Class A operation will occur. Where the stage is normally operated Class AB or B, an open R4 will cause a reduction in output. The bias voltage can be checked with an ohmmeter, or R4 can be measured with an ohmmeter. If R3 becomes open, the bias will be removed and the stage will operate Class B, zero-biased. If the drive is insufficient, loss of output will occur. With sufficient drive available, however, it is possible for the output to increase, with an increase in distortion. If R3 is shorted, the increased forward bias will hold the stage in heavy conduction and the input signal will most likely be shunted through CR1 and R4 to ground, resulting in reduced output with distortion. If either CR1 or CR2 is shorted, one half of the input signal will be shunted to ground through R4 and the output will be reduced. If either C1 or C2 is leaky, the bias on Q1 or Q2 will be changed, depending upon the polarity of the voltage on the drive side of the capacitors. A negative supply for a PNP driver stage will cause increased forward bias and reduced output. A positive voltage for an NPN driver stage will produce constant heavy conduction through diode CR1 or CR 2, and cause shunting of the input, loss of drive, and reduced output. Either or both transistors may be defective and cause loss of output. Shorted primary or secondary windings on T1 will also reduce the output. Therefore, it is necessary to use an oscilloscope to observe the waveform and follow the signal through the circuit. When the waveform amplitude decreases, check the parts in that portion of the circuit for proper resistance or continuity as applicable.

Distorted Output. Improper bias, overdrive, or clipping because of too low a collector voltage can cause distortion. Use an oscilloscope to follow the waveform through the circuit; the source of the distortion will usually be easy to locate when the waveform differs from the input. Leaky coupling capaci-

tors will cause improper bias and possible peak clipping. Defective diodes can also cause clipping of the input signal and consequent distortion. Defective transistors can produce distortion through non-linearity or unbalance. For the least distortion, matched transistors are usually used. In some instance poor frequency response in the output transformer may also cause distortion. Poor response can also result from an improperly matched load or from a change in the load resistance. In any event, it is necessary to observe the waveform with an oscilloscope to determine whether the distortion increases or decreases as the signal is followed through the circuit.

COMPOUND-CONNECTED AUDIO POWER AMPLIFIER (SEMICONDUCTOR)

Application.

The compound-connected power amplifier is used as the output stage in receiver, public address amplifiers, and modulators where large audio power outputs are required. It is also used as a direct-coupled control amplifier in transistorized voltage regulators.

Characteristics.

High voltage and power gain are obtained.

Operation is usually Class A.

Fixed bias is normally employed but self-bias may be encountered.

High input resistance is obtained (much greater than for a single CE stage).

Input is series-connected, and output is parallel-connected.

Two or more transistors are required.


Ratio of emitter current to collector current remains constant; there is no drop-off of collector or current high emitter currents.

High current amplification can be obtained with very little distortion (less than ½ percent).

Circuit Analysis.

General. Two compound-connected transistors may be employed as a single transistor and used in other circuit configurations, such as, push-pull audio amplifiers, to obtain greater output and more linear response than can normally be obtained in the circuit. Because the forward current gain does not drop off at


high emitter currents, the operation is linear and since the collector current continues to increase proportionally as the emitter current increases, the transistors can be driven to full output without any increase in distortion. The increase in linearity of the collector current which the compound connection provides can be clearly seen from the accompanying graphic comparison of emitter and collector currents.

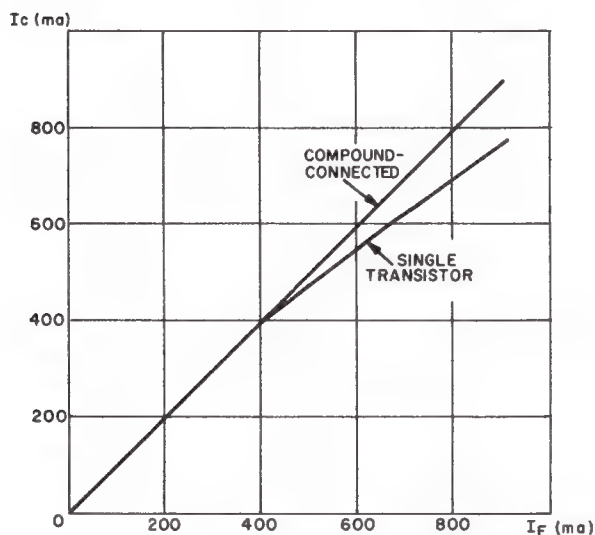

Graph Showing Differences Between Compound-Connected and Single-Transistor Operation

Note that in the graph the ratio of collector current to emitter current for a single transistor remains constant (as indicated by the straight-line portion of the curve) until approximately 400 ma is drawn; then the collector current increases less rapidly as the emitter current increases (as indicated by the curved portion). This is reduction in collector current linearity indicates a loss in forward current amplification, which is most pronounced in power amplifiers that draw heavy emitter current. The variation of the total collector current with input emitter current for compound-connected transistor is also shown in the graph. Observe that the total collector current of the compound-connected transistor does not drop off as the emitter current increases, but varies linearly over the entire range of operation (it is a straight line instead of a curve).

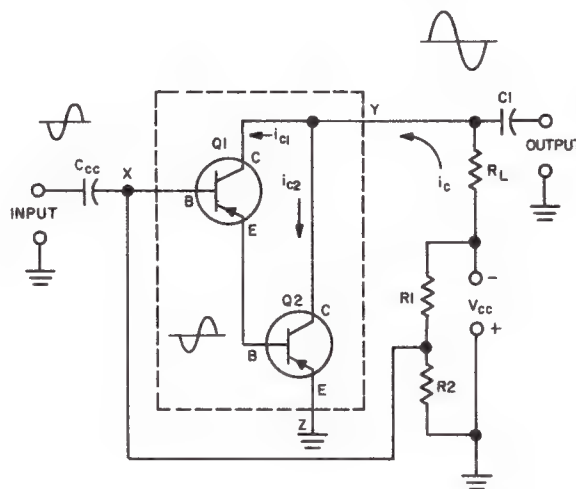Circuit Operation. The basis schematic for a pair of compound-connected transistors used as an audio amplifier is shown in the accompanying illustration. The circuit enclosed by the dashed line can be considered as a single transistor with connection points X, Y, and Z representing the base, collector, and emitter, respectively, of the combined transistors.



Compound-Connected Common-Emitter Audio Amplifier Circuit


Fixed Class A bias is supplied to the base of transistor Q1 through voltage divider resistors R1 and R2 connected across the common power supply. (Refer to the introduction to this section of the handbook for a discussion of the types and methods of biasing.) The bias on Q2 is supplied by emitter current flow through Q1 and Q2 to ground, the actual value being determined by the emitter current of Q1 and the forward gain of Q2. Capacitive input coupling is provided by Ccc. The output load, R_L , is connected in series with both transistors and a common source of power; the collectors are connected in parallel, and thus share a common load. The output is taken through coupling capacitor C1 (in some circuits R_L and C1 are replaced by a transformer for greater power output).

Both transistors are connected in the common-emitter configuration, and, since the base of Q2 is directly connected to the emitter, which is the common leg of Q1, transistor Q2 provides a certain

amount of negative feedback. Because both transistors are series-connected across the input, a much higher input resistance (100 times as large, or more) is offered than with a single CE stage. In the absence of an input signal, both transistors operate in the Class A region, as determined by the fixed voltage divider bias supplied by R_1 and R_2 . The bias on Q_2 is just slightly less than that appearing on the base of Q_1 because of the small voltage drop between the base and emitter of Q_1 .

Assume that a negative input signal appears at the base Q_1 ; this increase in forward bias causes the collector current of Q_1 to increase to a value determined by the forward gain characteristics of Q_1 and the amplitude of the input signal. The flow of i_{C1} (and i_{C2}) through R_L produces the output voltage, which, as in the conventional common-emitter circuit, has a polarity opposite that of the input voltage. At the same time, since the base and emitter of Q_2 are in series with the input, a forward bias is also applied to Q_2 to increase collector current i_{C2} . While the amount of collector current through Q_2 is not as great as that through Q_1 , it adds to the output since it flows in the same direction through R_L . The total collector current flowing through R_L is the sum of the two collector currents ($i_{C1} + i_{C2}$). It is not double that of a single transistor, but varies in accordance with the ratio set by the individual forward gain values and the amount of base current drive applied to Q_1 . It is not necessary that both transistors be matched or have equal forward gain. However, it is convenient to show how the currents are distributed, assuming that the two transistors are identical. In a conventional cascaded stage the gain of two stages would be equal to the gain of the first stage times that of the second. Assuming a value of a $\alpha = 19$, the total gain of two stages would be 361, while for a compound connection a value of 399 is obtained (approximately 10% additional gain). This increase in gain is obtained because the collector current does not fall off at high emitter currents. The accompanying figure shows the two transistors compound-connected in the common-base circuit, for ease of explanation. Assuming a forward gain or α of .95 for both transistors (equivalent to a CE beta of 19), the current relationships through the circuit are as shown in the figure. In this circuit Q_1 handles most of the load current while Q_2 provides additional power during peak conditions. The flow of emitter current in the external circuit is from Q_2 , through the

base of Q_1 , through the input resistance, and back to the collectors of both transistors through the output resistance. The collector current of Q_1 is $0.95 I_E$; therefore, $0.05 I_E$ flows into the base, since the emitter current is the sum of the base and collector currents. Since $0.95 I_E$ flows into Q_1 and the total collector current is $0.9975 I_E$, the collector current of Q_2 is the difference, or $.0475 I_E$. Finally, since $.05 I_E$ flows from the emitter of Q_2 into the base of Q_1 , the base current of Q_2 is the total emitter current of Q_2 less the collector current of Q_2 or $.0025 I_E$. While this might be considered to show little contribution of Q_2 to the operation of the circuit, recall that in the common-base circuit the gain cannot exceed unity, which for all practical purposes is equal to $0.999999 \dots$ etc; thus, a change from 0.95 to 0.9975 represents a considerable increase in gain. Expressed in terms of the common-emitter circuit (as previously mentioned) it is a change of from 19 to 399 in gain, which is a very noticeably increase.

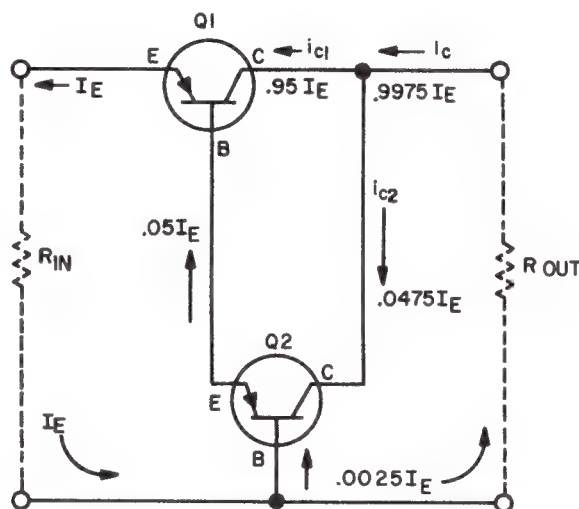

Current Relationships in Compound CB Circuit

Because the transistors are direct-connected in the compound circuit, there is no reactance to deteriorate the frequency response (it extends the low frequency bass response to zero or dc); therefore, although an increase in gain results, no sacrifice in response occurs. With a series-connected input, only sufficient drive for one transistor is required, as the current through a series circuit is uniform. Thus, the addi-

tional gain is achieved without requiring more drive. Although it might be thought that the increased input resistance requires more drive for the same input, it does not, since a smaller current through a higher resistance produces the same voltage drop as a higher current through a smaller resistance. With the collectors connected in parallel, the output resistance is lower than that of a single transistor, but not half as might be expected. It is approximately equal to the ratio of the two collector currents and is not of much significance, because the compound connection produces a larger output mainly by its ability to pass a greater current through the same load. In the basic schematic the output is shown capacitively coupled; where large power outputs are desired, an output transformer is usually used as in the conventional single-ended power amplifier. The compound connection may be used in any of the previously described circuits in this handbook to obtain greater linearity and output, but it requires two transistors for each one used in the conventional circuit.

When the load resistance is connected in series with the emitter of Q2 instead of the collector, this compound circuit becomes the cascaded emitter-follower amplifier, sometimes referred to as the *Darlington circuit*. Because of the large amount of degeneration provided, the operation is slightly different from that of the compound circuit described above. In other publications, the compound connection is also referred to as the *Tandem connection* or the *Super-alpha connection*.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low voltage ranges of most volt-ohm-milliammeter testers. Be careful, also, to observe proper polarity when checking continuity or making resistance measurements with the ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. Lack of supply voltage, either an open or short-circuited input or output or defective transistors, will cause a no-output condition. The supply voltage and the presence of collector and base bias can be checked with a voltmeter. With the proper voltage and polarities existing in the circuit, observe the waveform with an oscilloscope. Loss of signal on the base side of the input indicates either an open

coupling capacitor or a shorted input. Since the emitter of Q1 is connected in series with that of Q2, failure of either transistor will produce loss of output. An open output coupling capacitor (or transformer, if used) will also cause loss of output. Leaky coupling capacitors usually will not cause a complete loss of output. On the other hand, a shorted input capacitor can bias the circuit to cutoff or into heavy saturation depending upon the polarity of the collector supply of the preceding driver stage. Since all short circuits will most likely change the bias and circuit voltages, and open circuits will show normal voltages, a simple voltmeter check will determine the type of trouble. With only a few parts in the circuit, they may be checked separately to determine the defective part.

Reduced Output. Improper bias, low collector voltage, or defective transistors will cause reduced output. A leaky coupling capacitor will produce a larger than normal bias and cause the transistors to operate closer to cutoff or to saturation, depending upon the polarity of the bias. The reduction in output may be slightly noticeably or very evident, depending on the value of the bias change; and may be easily determined by a simple voltage check. If the bias and voltages are correct and the proper load is connected, a reduced output with normal input indicates that either one or both transistors are defective.

Where the wrong load or a short-circuited load is used, the output will be reduced. Check the value of the load with an ohmmeter. Where capacitive output coupling is employed, a leaky or shorted capacitor can cause a steady flow of dc through the output circuit. In the case of a speaker, a steady flow of dc through the voice coil will hold the cone in a steady position and require a large output to move it. Check the output load for a dc voltage to ground using a voltmeter. Where the load has changed in value, reduced output will usually be accompanied by distortion; the same indication will occur for reduced collector voltage, which can be determined by a simple voltage check.

Distorted Output. Audio distortion will be obvious when a monitoring speaker or headphone is provided. Improper bias or low collector voltage, an improper load or defective transistors can cause distortion. Check the bias and collector voltages with a voltmeter. Use an oscilloscope to observe the input waveform and to follow it through the circuit. When it departs from normal; the location of the trouble

will be obvious. Clipping of one side of the signal indicates improper bias or other voltages, while clipping on both sides indicates over-drive, as it does in electron-tube operating. Make certain that the input waveform is not distorted, since subsequent amplification will increase the distortion, making it appear to originate within the stage. With proper bias and other voltages and with a normal load, if distortion appears the transistors are likely to be defective.

BRIDGE-CONNECTED AUDIO POWER AMPLIFIER (SEMICONDUCTOR).

Application.

The bridge-connected power amplifier is used in receiver output stages and public address systems or other equipments where a large audio power output with low distortion is required, and no output transformer is employed.

Characteristics.

Over-all frequency response is improved by direct output coupling.

Operation can be Class A or B, with the least efficiency obtained in Class A, and the most efficiency in Class B operation, as in conventional push-pull stages.

Produces twice the power output of a conventional push-pull stage.

May be operated at twice the normal supply voltage instead of half the voltage as in other circuits.

Each transistor dissipates only half the power of its counterpart in the conventional push-pull stage; therefore, smaller transistors may be used for the same output, or a greater power can be obtained for the same transistors.

A single untapped source of supply voltage may be used.

No dc current passes through the load.


Requires push-pull input (opposite polarity and twice the drive of a single stage).

Circuit Analysis.

General. The bridge circuit is developed from the basic dc bridge, sometimes called the *Wheatstone bridge*, using equal-ratio arms. In the basic two-transistor circuit, two equal power supplies form the other arms. With equal transistors and equal power supplies, the bridge is balanced for dc flow and there is no flow of dc through the load until the bridge becomes unbalanced by application of a signal. The

push-pull, single-ended, series-connected audio power amplifier discussed in this section of the handbook is an example of a simple type of bridge circuit. The full bridge circuit utilizes four identical transistors in a bridge arrangement, or two PNP and two NPN transistors in a complementary symmetry arrangement. The use of four transistors as the bridge arms permits operation with a single (or untapped) power supply, and provides twice the power output of the simple bridge circuit, with less distortion.

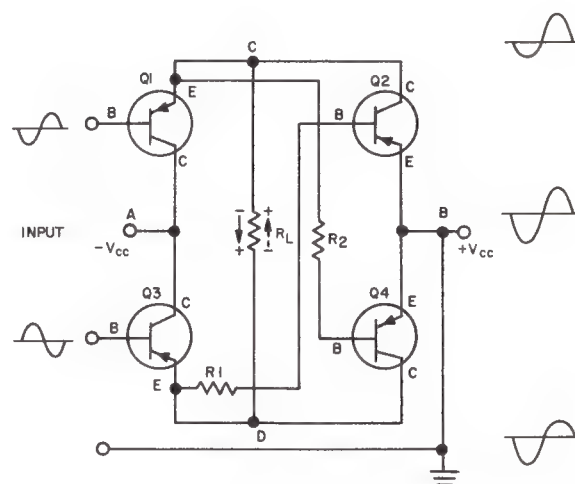Circuit Operation. The schematic of a typical four-transistor PNP bridge amplifier is shown in the accompanying illustration.



Full Bridge Circuit

Note that transistors Q1 and Q3 have the load connected in the emitter circuit, while Q2 and Q4 have the load connected in the collector circuit. Therefore, Q1 and Q3 are common-collector configurations (the output is taken from the emitter) with high input impedances requiring large-voltage input signals. Transistors Q2 and Q4 are common-emitter configurations (the output is taken from the collector) with low input impedances requiring low-voltage input signals, to produce an emitter-collector current equal to that of the common-collector connected transistors, and thus equalize the bridge currents.

The input signal is connected in a push-pull arrangement to the bases of Q1 and Q3; the base input to Q4 is taken from the emitter of Q1 through cur-

rent limiting resistor R_2 , and the base of Q_2 is supplied with a signal from the emitter of Q_3 , taken through current limiting resistor R_1 . In this manner the opposite bridge arms are connected to similarly polarized and smaller inputs (as required for the common-emitter circuit); otherwise, a special transformer or a complementary symmetry arrangement would be necessary to provide proper amplitude inputs. When a negative input signal is applied to Q_1 , the forward bias is increased and both the collector and emitter currents increase. With increased emitter current flowing through R_L , a negative voltage is developed across the load and applied through R_2 to increase the forward bias on Q_4 . Therefore, the collector and emitter currents of Q_4 also increase. The transistors are selected for equal gain, and R_2 for equal I_C , so that the emitter and collector currents of both transistors are equal.

Meanwhile, an oppositely polarized (positive) input signal is applied to the base of Q_3 simultaneously with the input signal applied to Q_1 . The positive input signal reverse-biases the base of Q_3 and reduces any flow of collector and emitter current. Similarly, the emitter voltage of Q_3 developed across load resistor R_L becomes more positive because of the reduction in current flow, and through R_1 places a reverse bias on the base of Q_2 , causing the emitter and collector currents of Q_2 to be reduced also. An increased current through one side of the bridge with a reduced current through the other side of the bridge produces the same effect as in conventional push-pull operation. In Class A operation, the total current flowing through the load is the same as if twice the normal current flow existed. In Class B operation, only two transistors conduct at a time, while the other two remain cut off.

When the input signal changes polarity on the opposite half-cycle (assuming a sine wave input) it becomes positive and a reverse bias is placed on the base of Q_1 . The reverse bias reduces the emitter current Q_1 , producing a positive polarity at the emitter; it is also applied through R_2 to reverse-bias the base of Q_4 . Thus, both Q_1 and Q_4 emitter and collector currents are reduced simultaneously. Meanwhile, the input signal applied to the base of Q_3 also changes, becomes negative, and applies a forward bias to the base of Q_3 , which increases the emitter current. The increased emitter current flows through the load in the opposite direction, as shown by the dashed arrow

on the schematic. The change of current flow creates an opposite polarity across R_L .

Since the voltage developed in the emitter circuit of Q_3 is negative and the base of Q_2 is connected to the emitter of Q_3 through R_1 , a forward bias is also placed on Q_2 . Thus, the emitter-collector current flow of Q_2 is increased simultaneously with that of Q_3 . As a result, the transistors interchange roles; Q_3 and Q_2 become conducting, while Q_1 and Q_4 are driven toward cutoff in Class A operation, or are entirely cut off in Class B operation. Assuming equal transistors, biases, and drives, equal but oppositely polarized voltages are produced across the load resistor by the current flowing in different directions in the bridge arms, so that the effective dc flow is zero. Since the varying (ac) load current flows first in one direction during one half-cycle of input and then in the opposite direction during the remaining half-cycle, the output load can be direct-connected in the bridge, and no output transformer is needed to develop the output signal. While the input resistance of the bridge is high, the output resistance is low, and no impedance transformation is necessary to match loudspeaker or servo loads. (The transistors are usually selected to have an output impedance near that of the load, in which case $R_L = V_c/I_c$.)

Because there are always two transistors across the supply, the collector voltage of each transistor is always less than the supply (usually half). Since no transformer is used, the collector voltage can never exceed that of the supply, so that the designer can apply twice the normal collector voltage to both transistors in order to apply the full rated collector voltage to each transistor. Therefore, a greater output can be obtained than would normally be possible in other amplifier circuits where the maximum collector voltage is never allowed to exceed half the supply voltage. Likewise, since each transistor dissipates only half the power dissipated by each transistor in a conventional push-pull amplifier, a four transistor bridge circuit can produce twice the output of the conventional push-pull circuit. This accounts for the high output power of the bridge circuit. Because the inputs to Q_4 and Q_2 are obtained from the emitters of Q_1 and Q_3 , only enough drive is required to drive the bases of Q_1 and Q_3 . Therefore, no additional drive power is required over that of the conventional push-pull amplifier.

In Class A operation, the quiescent currents of the

transistors are equal, and no dc flows through the load because the bridge is balanced. During operation, the current through one pair of arms increases while the current through the other pair decreases. On the opposite half-cycle the conditions are reversed. On the other hand, in Class B operation all transistors are zero-biased with no signal applied, and no current flows. When an input is applied, one pair of arms conducts while the other pair remains cut off. During the remaining half-cycle the other pair of arms conducts while the first pair remains cut off. Thus, twice the current of a single transistor flows through the load during either type of operation. Because no transformer is used and the transistors are direct-connected, both low-frequency response and high-frequency response are improved. This accounts for the decrease in distortion of the bridge circuit as compared with any of the other push-pull circuits.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low-voltage ranges of most volt-ohm-milliammeter testers. Be careful, also, to observe proper polarity when checking continuity or making resistance measurements with the ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. If the output load or collector supply is open or short-circuited, no output will be obtained. A short-circuited load will be indicated by a resistance reading of less than one ohm, while an open circuit will be indicated by infinity or a very much larger than normal resistance. Check the supply voltage with a voltmeter to determine whether the supply is defective. On the other hand, since the bridge is normally balanced across the points to which the load is connected, a voltage check across the load will usually not pinpoint an open load. Instead, the voltmeter shunt will replace the load, if open, so that a false reading will be obtained. If a transistor is short-circuited, the other portion of the bridge will operate; thus, a single defective transistor will not produce a complete no-output indication. If transistor Q4 or Q2 is shorted, Q1 and Q3 will still operate. On the other hand, if Q1 or Q3 is shorted, the large input signal will probably bias Q2 and Q4 into cutoff and saturation, producing no output (in some instances a slight output may still be obtained, depending upon the

applied bias). If either R1 or R2 is open Q2 or Q4 will not operate and no output will be obtained in Class B operation. Likewise, if Q1 or Q3 is open, the remaining half of the bridge will not operate.

In Class A operation, all four transistors would have to be defective simultaneously to cause no output. Since in Class B operation only two transistors conduct at a time, while the other two are cut off, it will be necessary for two transistors to be defective for no output to occur. When transistors are replaced, they should be replaced in pairs.

Reduced Output. Reduced output may be caused by failure of a single transistor, defective bias resistor R1 or R2, or an open input circuit to one arm of the bridge. The resistors may be checked with an ohmmeter, and the supply voltage may be checked for proper value with a voltmeter. While unbalanced voltages across the separate arms of the bridge may indicate the probable location of the trouble, an oscilloscope check is preferable. Follow the signal from the input and check the output waveform of each transistor. Where the waveform departs from normal, the trouble is in that portion of the bridge. Since the inputs to Q4 and Q2 are taken from the emitters of Q1 and Q3, it will be normal to find the amplitude of Q1 and Q3 larger than that of Q4 and Q2. The emitter outputs of Q1 and Q3 will be of the same phase as their inputs, while the outputs of Q4 and Q2 will be oppositely polarized with respect to their inputs, because of the common-emitter connection.

Distorted Output. Distorted output may be caused by a defective transistor, improper collector voltage, or too large a drive (input signal). The collector voltage may be checked with a voltmeter to determine whether it is normal. Too large an input signal will cause clipping of the signal in the output circuit, as in other amplifier circuits. Too low a collector voltage will produce bottoming, a form of clipping which results when the supply voltage cannot follow the peak signal demands. Hence, it is almost mandatory to use an oscilloscope to check the signal waveform through the circuit. Flattening of the signal at the peaks or troughs of modulation indicates clipping and the resultant distortion. If R1 and R2 and the load are the proper value, and the supply voltage is normal, the transistors are defective.


FEEDBACK AMPLIFIERS

General. Feedback amplifiers are divided into two basic types, those employing positive feedback, and

those employing negative feedback. Positive feedback consists of feeding back a portion of the signal in-phase with the input so that the overall output is increased because of the feedback. If left uncontrolled the additional output, in turn, supplies a proportionately larger input and the overall output is further increased. This cumulative effect of building up the signal amplitude is termed *regeneration*. When the output of an amplifier is fed back into the input in a regenerative manner the final result is to cause the circuit to oscillate at some particular frequency or over a small range of frequencies. Thus the r-f oscillator is basically a regenerative feedback amplifier, which eventually stabilizes at some maximum amplitude. Generally speaking, the use of positive feedback is restricted to oscillators, or special regenerative receivers operating at radio frequencies. It is also used sometimes at lower frequencies (within the audio range) to supply high gain over a single stage of amplification, which is controlled by additional stages with negative feedback.

When the feedback is made 180 degrees out-of-phase with the input signal so that it reduces the overall output of the amplifier, it is considered to be *degenerative* and is known as negative or *inverse* feedback. Although the application of negative feedback reduces the gain of the amplifier below that which would normally be obtained without feedback, it provides many desirable features. In general, it improves the behavior of the system, and increases the bandwidth. It improves the linearity of the system, and consequently produces less intermodulation and harmonic distortion. At the same time, the input impedance is increased and the output impedance is decreased. Any noise generated within the amplifier system itself is reduced, but it has no effect on any externally induced noise. Since a portion of the output is fed back to the input, any change in circuit values is in effect automatically compensated for, so that the circuit gain is stabilized. The following graph shows the overall frequency response and gain for an amplifier without any feedback, an amplifier with 3 dB of negative feedback, and one with 15 dB of negative feedback. Although the overall amplification is decreased by the feedback, the frequency response is increased, and is made flatter over a greater range. The peaks occurring at the extreme low and high frequencies are due to phase shift caused by reactance effects changing the feedback at these frequencies from negative to positive. The loss of amplification

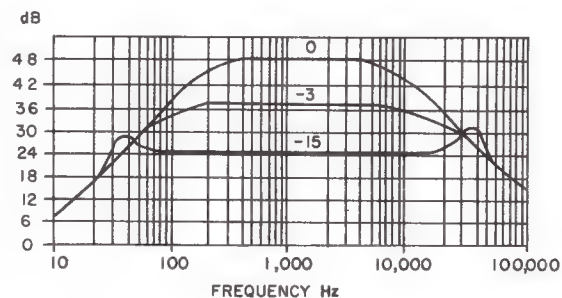when feedback is used can be recovered by employing additional stages of amplification. In fact, with good design it is possible to use a single stage of positive feedback to provide the lost gain, with the remaining amplifier stages using inverse feedback. Typical positive and negative feedback circuits are discussed in the following paragraphs.



Typical Negative Feedback Response Curves

POSITIVE FEEDBACK AMPLIFIER (DIRECT, REGENERATIVE) (ELECTRON TUBE)

Application.

The positive feedback (regenerative) amplifier is used in audio and r-f stages to supply a greater output than is possible through normal gain in a single-tube amplifier.

Characteristics.

Uses self-bias, but fixed bias may also be used if desired.

Provides the amplification of two or three tubes in a single stage.

A portion of the output voltage is fed back (in-phase) with the input signal.

Distortion is increased in proportion to the amount of feedback.

Feedback may be accomplished by resistive, inductive, or capacitive methods.

Usually only one stage of positive feedback is employed.

Oscillation may occur at extremely low or extremely high frequencies because of reactance effects.

Circuit Analysis.


General. Because the electron tube amplifier inverts the signal in the plate circuit, it is necessary either to use a transformer to reverse the phase, or to pass the signal through another stage to obtain positive feedback. The input circuit operates as a mixer and adder, with the output signal being the sum of the input signal and the positive feedback voltage, multiplied by the gain of the stage. In r-f amplifiers, general practice is to couple a portion of the plate output back to the input through an r-f transformer, and to vary the coupling between the two coils mechanically or electrically to control the amount of feedback. Since the design and operation is unique for each application, the following typical circuit shows only one particular arrangement of positive feedback. It will serve, however, to illustrate and describe the basic principles and operation of positive feedback so that they can be applied in the analysis of similar circuits even though the circuits are not identical.

Circuit Operation. A typical cathode feedback arrangement using positive feedback to overcome degeneration provided by unbypassed cathode resistors with improved audio gain and response is shown in the accompanying schematic. The two-stage amplifier consists of a triode cathode-resistance-coupled stage driving a pentode transformer-coupled output stage. Capacitor C1 and resistor R1 form the RC

input circuit to triode V1. Cathode self-bias is provided by cathode resistor R3, and the output is developed across plate resistor R2. Capacitor C2 and resistor R5 are the plate RC coupling circuit for driving pentode V2, with cathode bias supplied by R6. Both cathode resistors R3 and R6 are unbypassed, which normally provides degeneration. However, by connecting the cathode of V2 to the cathode of V1 through feedback resistor R4, the positive feedback voltage cancels the degenerative effects of cathode resistor R3. Thus, the output of V1 is increased by the feedback voltage. Resistor R7 is the screen voltage dropping resistor for V2, bypassed by C3. The output of V2 is transformer coupled through T1 to a loudspeaker or to another amplifier stage, as desired.

Assume a sine-wave input signal applied to C1 and is passed to the grid of V1, appearing across R1. On the positive excursion of the signal, V1 grid is driven in a positive direction. The increasing plate current through plate resistor R2 produces a negative-going output voltage, which is coupled through C2 to drive the grid of pentode V2. The negative driving voltage appears across R5, and causes the plate current of V2 to decrease. The changing plate current through the primary of output transformer T1 induces an output in the secondary. Screen voltage is obtained by dropping the supply voltage through R7, which is held at ground potential for audio voltage changes by screen bypass capacitor C3, so that the screen voltage remains a constant dc and is unaffected by the signal variations. When the plate current of V2 decreases with the negative driving signal, the cathode voltage developed across R6 is negative-going. A portion of this voltage is coupled back through feedback resistor R4 to the cathode of V1. Thus as the increasing plate current of V1 causes an increasing (positive-going) cathode voltage across R3, the negative voltage from V2 cathode cancels it and prevents the input signal from producing a degenerative cathode voltage on V1. Thus instead of the instantaneous bias on V1 increasing, it is held at the same level or even slightly decreased by the negative feedback voltage from V2 cathode. When the feedback is made sufficient to produce a slightly decreasing bias on V1, the output voltage is increased by this positive feedback. The effect is as though the grid input signal were increased.

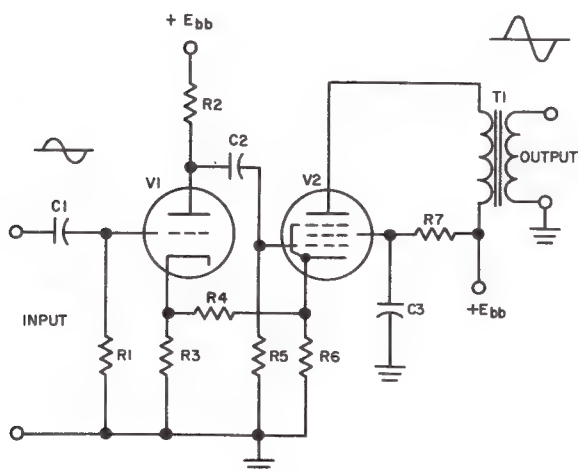On the negative-going portion of the input signal the opposite action occurs. The negative swinging grid




Cathode Coupled Positive Feedback Amplifier

voltage causes V1 plate current to decrease, and produces a smaller bias across cathode resistor R3. At the same time, the plate voltage of V1 becomes positive-going and drives V2 grid in a positive direction. Thus the plate current of V2 is increased, and a higher cathode voltage is developed across V2 cathode resistor R6. This positive voltage, in turn, is fed back through R4 to the cathode of V1, which is the same as increasing the bias, or applying a larger negative-going input signal. The plate output of V1, therefore, is greater. Since R4 is larger than R3 and R6, the cathode voltage developed across R3 has little effect on V2. Because of the feedback arrangement, the output resistance (plate resistance) of V2 is decreased to a lower value and less turns are needed on T1 to produce an appropriate output match, and a large power output is developed. The reduced turns on T1 produces a reduction in total capacitance between turns and increases the effective high frequency response over that which would normally be obtained.

Circuit Variations. A typical positive feedback circuit using a tapped output transformer to supply voltage feedback over a single stage is shown in the accompanying schematic. From an examination of the schematic, it is seen to be a conventional audio amplifier, with a resistance coupled input and transformer coupled output, except for the special feedback provisions. This consists of current limiting resistor R2 in series with V1 grid, and the feedback arrangement of R4 and C5 connected from the secondary of the output transformer back to the grid of V1. While T1 secondary is tapped, a similar arrangement may be produced by using an untapped secondary with a resistive voltage divider across it. The important point to remember about T1 is that the secondary is phased to produce a positive feedback signal. Normally, the primary signal of T1 is inverted from that of the input signal by conventional tube action, thus it is necessary that the secondary winding be phased so as to again invert the signal (otherwise an additional stage of amplification would be necessary to complete the inversion). When the input signal is applied, assuming a positive-going sine wave, the increased positive signal on the grid of V1 causes an increasing plate current. This change of current through the primary of T1 induces a positive-going output in the secondary. The amount of feedback between the tap and ground is applied in shunt with the input signal, and both signals are combined

across R2. Thus the input signal is increased and the output likewise. On the negative-going excursion, the opposite action takes place. The decreasing plate current through the primary of T1 induces a positive-going voltage in the secondary, which is phased by reversing the winding to be a negative-going signal, and a portion of this voltage is fed back through R4 and C5 to enhance the negative swinging input signal and further decrease the output. By using capacitor C5 the feedback becomes phase controlled. The larger the feedback capacitor, the greater the effect on low frequencies, while R4 acts as an attenuator and a phase shifting resistor. With proper proportioning of these parts the feedback is stabilized and prevented from developing into negative feedback (because of excessive phase shift at the low frequencies). However, positive feedback used alone tends to increase distortion, hence it is usually combined with negative feedback in following amplifier stages to accomplish the increase of gain with reduced distortion.

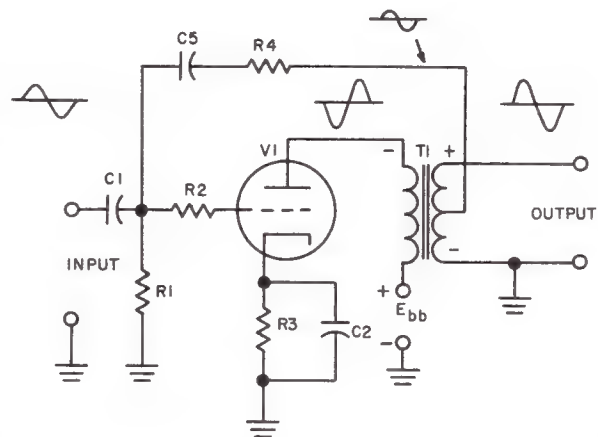

Transformer Coupled Positive Feedback Amplifier

Failure Analysis.

No Output. Lack of plate voltage, improper bias, as well as a defective tube, open coupling capacitors or output transformer can produce a loss of output. Measure the plate and bias voltages with a high resistance coltmeter. If no voltage appears on the plate of V1, R2 is open, while if no voltage appears on V2 plate, the primary of T1 is open or shorted to ground. Use an ohmmeter to check for resistance and shorts to ground. If no signal appears at the input on V1

grid when using an oscilloscope, coupling capacitor C1 is open. Likewise, if a signal appears on V1 plate but not on V2 grid, coupling capacitor C2 is open. If a signal appears on V2 grid but not on V2 plate, either V2 is defective, or screen resistor R7 is shorted by capacitor C3. If screen resistor R7 is open, a small output signal will appear on V2 plate because of the tube acting like a triode. If V2 is considered at fault replace it. When a signal appears on the grid of V1, but does not appear on the plate and the measured cathode bias is normal, replace V1. If cathode resistors R3 or R6 are open no signal can appear on either V1 or V2, respectively.

Low Output. Low screen or plate voltage will produce a low output. Check for proper plate, bias, and screen voltage with a voltmeter. Too high a bias caused by heavy plate current from an external short or defective tube will cause the tube to operate near saturation or cutoff and reduce the output accordingly, usually with noticeable distortion. If feedback resistor R4 opens degeneration will cause a reduced output. If C2 is leaky, the bias on V2 grid will show positive and the tube will be held in heavy saturation producing little or no output.

Distorted Output. With positive feedback it is normal for greater distortion to occur than for the same stage without feedback, unless compensated for by a later stage using negative feedback. Excessive distortion can be caused by low plate or screen voltages or by improper feedback voltage. There may even be oscillation occurring at extremely low or extremely high frequencies because of phase shift effects. Use an oscilloscope to follow the signal through the circuit and note where the distortion appears, then check the associated parts.

NEGATIVE FEEDBACK AMPLIFIER (INVERSE, DEGENERATIVE) (ELECTRON TUBE).

Application.

Negative feedback is used in speech amplifiers, modulators, and high-fidelity sound systems to improve the overall response and stabilize the gain.

Characteristics.

Uses self bias, but fixed bias may also be used, if desired.

Usually requires an additional stage or more of amplification to make up for the loss produced by negative feedback.

A portion of the output voltage is fed back out-of-phase with the input signal.

Distortion is decreased in proportion to the amount of feedback.

Oscillation may occur at extremely low or high frequencies because of adverse phase shifts causing the feedback to change to positive instead of negative.

Noise or distortion generated within the amplifier is always reduced.

Externally induced noise (such as thermal noises generated in preamplifier stages) is not affected.


Bandwidth and linearity of the system is improved, and output impedance is reduced.

Change of circuit values is automatically compensated for so that circuit gain is stabilized and operation is improved.

Circuit Analysis.

General. There are many methods of developing negative or inverse feedback. It may be used over a single stage or over a number of stages (usually not more than three). Since the feedback must always be degenerative, and odd number of stages are usually used. Either voltage or current feedback may be employed. Although the circuit is usually arranged so that the feedback is accomplished in series with the input signal, it may be connected in shunt, if desired.

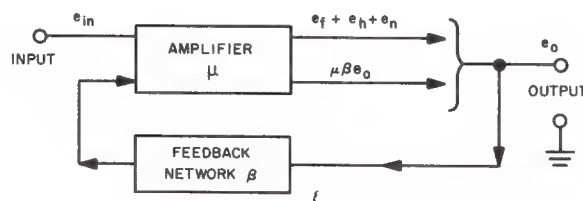The accompanying block diagram shows the manner in which feedback is normally accomplished.




Typical Inverse Feedback Arrangement

The total output voltage is made up of two parts: that resulting from the input voltage e_{in} and that resulting from the feedback input βe_o . The first part consists of fundamental output e_f which is equal to μe_{in} , plus harmonic and intermodulation distortion components e_h , plus any noise e_n generated within the stage. The sum of these components is the

total output e_o , which would normally exist without feedback. With feedback voltage βe_o applied to the input, the second part of the output voltage is $\mu\beta e_o$, which contains a portion of all the three previously mentioned components, plus new harmonic and intermodulation distortion components. Since the feedback opposes the normal signal, the noise and harmonics are reduced by the inverse feedback to a negligible value, and the fundamental output is also reduced. Mathematically it can be demonstrated that both the fundamental, harmonics, and noise are reduced by the factor $1/1-\mu\beta$, where $\mu\beta$ is the feedback factor.

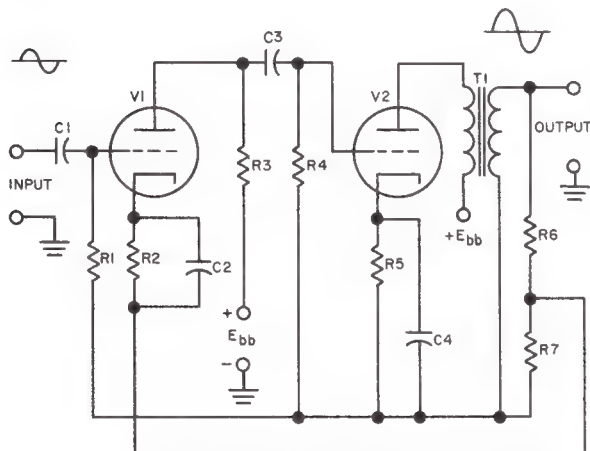Circuit Operation. The accompanying schematic shows a typical two-stage triode inverse feedback amplifier.



Two-Stage Triode Negative Feedback Amplifier

Except for the feedback connection, V1 and V2 form a conventional triode resistance coupled amplifier chain, using an output transformer in the final stage. The negative feedback is inserted in series with the cathode bias resistor of V1 through a voltage divider consisting of R6 and R7 connected across the secondary of the output transformer. When a positive input signal is applied, it passes through C1 and appears across grid resistor R1, driving the grid of V1 in a positive direction and increasing plate current flow. The increased plate current flow through plate resistor R3 causes a voltage drop, which is applied as a

negative-going driving voltage through C3 to the grid of output amplifier V2. For the moment, assume that V1 cathode resistor, R2, is grounded, so that only the dc bias developed by average current flow appears. Since R2 is bypassed by C2, any instantaneous changes in signal current have no effect on the bias and full tube amplification is obtained. With the negative driving voltage from V1 appearing across grid resistor R4, V2 plate current reduces, and the reduction of current through the primary of T1 induces an output voltage into the secondary winding of the output transformer. V2 is also cathode biased, with average plate current flow through R5 developing the dc bias, and is bypassed by C4 so that the signal variations have no effect on bias voltage. With the positive side of the T1 secondary connected to voltage divider R6 and R7, a positive-going portion of the output voltage taken across R7 is applied in series with cathode resistor R2 of tube V1 (R2 is grounded through R7). Thus, this small portion of positive output voltage instantaneously increases the cathode bias, reducing the output accordingly.

When the input signal goes negative the opposite action ensues, a negative output voltage is developed across the feedback voltage divider, and is applied to the V1 cathode to decrease the bias and increase the output. In both instances, the feedback voltage acts in opposition to the normal effect of the input signal, just as if a voltage 180 degrees out-of-phase with the input signal was inserted on the grid of V1. Since the feedback voltage is only a fraction of the input (about one tenth), the input signal is only slightly reduced, but the additional amplification obtained through the gain of the amplifier increases the amount of feedback voltage in the plate of the output stage. Thus, the overall gain is considerably reduced over what it would normally be without feedback. The net effect is to flatten out the amplifier response curve so the gain at low, mid-band, and high frequencies is about the same. Hence with a flatter response greater fidelity is obtained. Any hum produced by the final amplifier supplies a correcting feedback voltage which effectively cancels and reduces the hum, and any harmonic distortion is affected likewise. When the input signal is increased in amplitude, the output also increases but the gain remains relatively constant because of the feedback. Thus the amplifier may be driven harder and still produce better fidelity and less distortion than without feedback. The limit

of drive is reached when grid current flows in the input stage, since the input signal itself becomes distorted and feedback will not correct this condition. With proper design, up to three stages of high gain amplification may be used. Beyond this, excessive phase shift is produced through the feedback, network, so that the feedback changes from negative to slightly positive at the low and high frequency ends of the response curve and usually causes oscillation and distortion, which makes the extra amplification useless.

Failure Analysis.

No Output. An open input, cathode, or plate circuit, lack of plate voltage, or a defective tube can cause a loss of output. Check the plate voltage and cathode bias with a high resistance voltmeter. This will verify that resistors R2, R7, and R5, as well as R3 and the primary of T1 are not open, and that neither C2 or C4 is shorted. Check for an input signal using an oscilloscope, if the signal appears at the input but not on the grid of V1, either C1 is open or V1 has a grid to cathode short. If V1 is good, check the capacitance of C1 with an in-circuit capacitance checker. If the signal appears on the grid but not on the plate, and normal plate voltage exists, V1 is probably defective. If the signal appears on the plate of V1 but not on the grid of V2, capacitor C3 is open or V2 is defective. If the condition persists check the capacitance of C3. If the signal appears on the grid of V2 but not on the plate, either the tube is defective

or T1 primary is shorted. A resistance check will determine if T1 is shorted. If the signal appears on the plate of V2 but not at the output, the secondary of T1 is either open or shorted. Check the resistance and continuity of T1 with an ohmmeter.

Reduced Output. If the plate voltage is low, or the cathode bias is too high, there will be a reduction of output. A defective tube can cause both low plate voltage and high cathode bias, because of heavy conduction due to a shorted condition. Likewise, low emission will also cause a reduced output. Check the plate and bias voltages with a voltmeter if the condition persists, since aging plate or bias resistors may increase in value and cause either a reduction of plate voltage or bias, or both. If either coupling capacitor C1 or C3 is leaky or shorted, the output will be reduced because of improper bias (plate voltage from the preceding stage will be applied the grid). If either the primary or secondary of T1 is partially shorted or develops a low leakage to ground the output will be lower than normal. If an oscilloscope check shows all grid and plate signals normal except that for V2 plate, transformer T1 may be defective.

Distorted Output. Since the negative feedback practically eliminates harmonic distortion, excessive distortion indicates failure of the feedback loop. Check R6 and R7 with an ohmmeter for the proper value. Check to be certain that the input signal itself is not causing the distortion. Any other condition will be revealed by bias and plate voltage checks. Too low or too high a bias or too low a plate voltage can cause distortion.

PART 5-3. PHASE INVERTERS

TRANSFORMER TYPE PHASE INVERTER
(ELECTRON TUBE)**Application.**

The transformer type of phase inverter is used for driving push-pull amplifiers, in public address systems where grid current flow is sufficient to cause distortion in other types of inverter circuits.

Characteristics.

Uses an output transformer with a common secondary center tap.

Uses self bias, although fixed bias may sometimes be used.

Provides maximum output and gain.

Output amplitude is primarily determined by the transformer turns ratio.


Frequency response is uniform over a range of approximately 100 to 5000 Hz.

Two outputs, balanced with respect to ground, are supplied.

Circuit Analysis.

The transformer type of phase inverter is basically a transformer coupled audio amplifier with a center tapped secondary. When the center tap is grounded, two opposite polarity outputs are produced which are essentially out of phase with respect to each other. Thus, a single input signal will provide a dual output with polarity and correct phases for driving a push pull stage. Because the transformer secondary has a low dc resistance, this type of circuit is usually employed where grid current is drawn, such as in Class B push-pull stages. While also classed as a phase splitter and paragraph amplifier, these terms are considered to be more applicable to other types of inverters which use special circuit arrangements to obtain the phase difference and dual output.

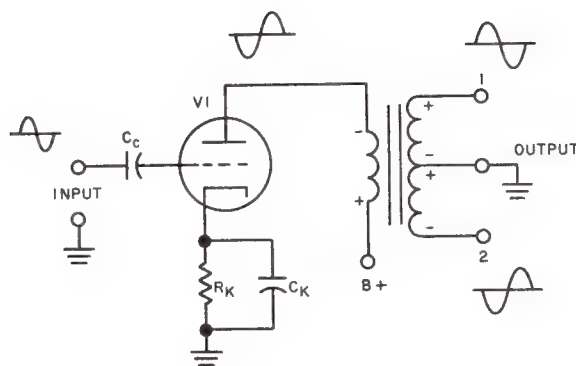Circuit Operation. The schematic of a typical transformer type of phase inverter is shown in the accompanying illustration. A triode tube is employed for simplicity, since it will usually supply sufficient drive (output) for moderate powered push-pull amplifiers. Where greater power or drive voltage is required, a pentode tube may be used, or an additional push-pull driver stage can be added.



Transformer Coupled Phase Inverter

The high impedance resistance coupled input uses C_c as the coupling capacitor and R_g as the triode grid resistor. Cathode bias is supplied through cathode resistor R_k bypassed by C_k . Plate voltage is applied to V1 through the primary of T1. The secondary of T1 is center tapped, and the outputs are obtained between each end of the winding and the center tap.

With no signal applied, tube V1 is resting in the quiescent condition, with the voltage drop across cathode resistor R_k supplying Class A bias (plate current flows continuously for the whole cycle). Cathode bypass capacitor C_k prevents degeneration so that instantaneous plate current variations have no effect on the bias. (Refer to the introduction to this section of the handbook for a discussion of cathode bias.)

When a positive input signal is applied, the grid of V1 is driven positive and increased plate current flows. The increased plate current flow through the primary of transformer T1 produces a greater magnetic field linking the windings and causes a voltage to be induced in the secondary. With a center tap provided at the electrical center of the winding, two outputs can be obtained, as shown by the polarity indicated in the schematic. With opposite polarities, these outputs are of the proper phase for driving a push-pull stage. When the positive half-cycle is completed and the negative half-cycle begins, assuming a sine wave input signal, plate current is reduced. The reduction of plate current flow through the primary of T1 induces a voltage in the opposite direction in the secondary, because the direction of the magnetic

field is now changed. Thus a negative output is produced during the negative half-cycle. The polarity of the secondary winding is now opposite that shown on the schematic. However, because of the grounded center tap, points 1 and 2 on the winding will be of equal amplitude, but of opposite polarity, or phase.

Failure Analysis.

No Output. Lack of plate voltage, improper bias voltage, as well as a defective tube will cause a loss of output. Loss of plate voltage or improper bias, may be determined by making a voltage check with a voltmeter. With plate voltage at the supply but not on the plate of V1, transformer T1 primary is open or V1 is shorted. With V1 shorted there will be a larger than normal voltage drop indicated across the primary resistance of T1. Replace V1, and recheck the plate voltage. With proper plate and cathode-bias voltage, and no output, either grid resistor R_g is open or the secondary of T1 is open. Make a resistance and continuity check of these parts with an ohmmeter to determine which is at fault.

Low Output. Low plate, or high bias voltage, as well as a defective tube can cause a low output. If abnormal plate current is drawn, the plate voltage of V1 will be lower than normal and the cathode bias will be higher than usual and thus less output will be obtained. Use a voltmeter to check plate and bias voltages. If bias and plate voltages are normal, replace V1 with a good tube, since low tube emission can also cause a reduced output. If the low output condition persists after tube replacement, transformer T1 is probably defective. A slight increase in plate voltage with a reduced primary dc resistance, as checked with an ohmmeter, coupled with poor low frequency response is an almost positive indication of a partially shorted primary. Any short or high resistance condition in the secondary will usually show on a resistance check of the secondary, and will probably cause a reduction in one of the output signal amplitudes, if not in both. Use an oscilloscope or VTVM to compare output voltage indications.

Distortion. Use an oscilloscope to observe the input signal waveform and amplitude, then check the output waveforms. If any difference of waveform occurs between the two output signals, the distortion is probably caused by the tube or transformer, particularly when normal plate and bias voltage readings are obtained.

SINGLE-STAGE PARAPHASE INVERTER (ELECTRON TUBE)

Application.

The single-stage paraphase inverter supplies a push-pull output from a single-ended input. It is used mainly to drive audio push-pull power amplifiers in public address systems, or modulators, and in receiver audio-stages.

Characteristics.

Self-bias is usually used although fixed bias may be used, if desired.

Two out-of-phase outputs are provided, one from the plate circuit, and one from the cathode circuit.

Frequency response is relatively uniform from about 100 to 15,000 Hz.


Either triodes or pentodes may be used (pentode provides slightly higher output with improved high frequency response).

Provides less gain than is possible with transformer coupling (output is always less than the input).

Circuit Analysis.

General. The single stage paraphase inverter, also known as a *phase splitter* utilizes the phase inverting property between the grid and plate of the electron tube to supply a 180 degree out-of-phase output. The plate output together with an in-phase output, which is taken from the cathode, provides the desired push-pull output. Since balanced signals are desired, the amplification is limited to that which can be obtained from the cathode, which is always less than unity for a cathode follower. Thus, when plate and cathode outputs are made equal, the output is always less than the input signal. This circuit, however, is more economical to produce and has a better overall response than the transformer coupled circuit. Hence it is usually used in lower priced equipment. For best results two-tube paragraph circuits are preferred, since the overall amplification and response may be arranged to provide better performance with a large output than either the transformer coupled, or the single-tube stage.

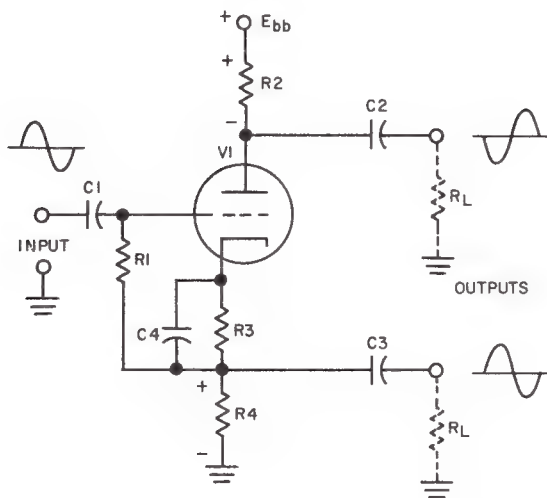Circuit Operation. The schematic of a typical single-stage paraphase inverter is shown in the accompanying illustration.



Single-Tube Paraphase Inverter

The input signal is RC coupled through C1 and R1 to the grid of triode V1. Cathode bias is supplied by R3 bypassed by capacitor C4. The outputs are developed across plate load resistor R2, and cathode load resistor R4, and are capacitively coupled to the push-pull driver or output stage by C2 and C3.

With no signal applied, V1 rests in the quiescent condition with Class A bias supplied by cathode current flow through cathode resistor R3. Since grid coupling resistor R1 is returned to the ground side of R3, any voltage developed across R4 by cathode flow has no effect on the bias between the grid and cathode of V1. Furthermore, since the voltage developed across R4 in the quiescent condition is steady (dc) no output appears from coupling capacitor C3. Likewise, any plate voltage drop developed across plate resistor R2 is also a steady dc and no output appears from C2.

Assume a sine-wave audio input signal is applied to the input terminals. During the positive excursion, the grid of V1 is driven in a positive direction in the conventional manner and an increasing plate current flows. When plate current increases, electrons flow from ground, through R4 and C4 (which bypasses R3), within the electron tube from cathode to plate, and through plate resistor R2 to the voltage supply, creating the polarities shown on the schematic. Note

that the cathode voltage is positive, is in phase with and follows the input signal, while the plate voltage drop is negative and out-of-phase with the input signal. Since these two voltages are constantly varying at an audio frequency they appear as outputs across C2 and C3, and ground. The values of R2 and R4 are made approximately equal so that equal amplitude output signals are produced.

When the input signal reaches its peak positive excursion and swings in a negative direction, the plate and cathode current through V1 is reduced, and the output voltage is reduced, likewise. As the input signal reaches the zero level and swings down into the negative region, the polarities across R2 and R4 are reversed. That of R2 rises towards the plate supply source and becomes positive-going, while that of R4 continues towards zero, drops below the quiescent level and is effectively negative-going because of the reduced cathode current flow. Again, two oppositely polarized (phased) and equal output signals are produced from the single input signal. Thus as the input varies at audio frequency, the cathode and plate outputs do likewise, but oppositely. Since R3 is bypassed for audio frequencies by C4 the bias remains unaffected by the signal current variations. (See explanation of cathode bias given in the introduction to this section of the handbook.)

As long as R2 and R4 are equal, and C2 and C4 together with their coupling (load) resistors (R_L) are equal, the frequency response of both circuits is almost identical. At frequencies about 20 kHz the plate output of V1 tends to drop off because of the effect of the appreciable triode grid-plate capacitance which is usually larger than the grid-cathode inter-electrode capacitance. Therefore, where higher audio frequencies are desired, the pentode tube is used instead of the triode so that its reduced inter-electrode capacitance minimizes this effect.

Failure Analysis.

No Output. Open input or output circuits, a defective tube, improper bias, or lack of plate voltage can result in loss of output. Check the bias and plate voltages with a voltmeter. Use an oscilloscope to observe the input waveform and follow it through the circuit from grid to cathode to plate, and then across the outputs. If an input appears across the input terminals but no signal appears on the grid, coupling capacitor C1 is open. If the grid of V1 reads positive C1 is shorted or leaky. When checking the bias across

R3, measure from grid to cathode using the proper polarity, and then from R4 to cathode. If the grid to cathode reading is zero, grid return resistor R1 is open. If an output appears across R4 but does not appear on the plate of V1, either the tube is defective or R2 is open. With plate voltage present from R2 to ground, V1 is defective (if the voltage is equal to the supply on both sides of R2, the resistor is shorted). When an output appears on the plate of V1 but not at the output load, coupling capacitor C2 is open. If C1 is shorted the plate voltage of the preceding stage will drive V1 into saturation, a constant high voltage will appear across R4, and a constant low voltage across R2 (on the plate of V1) and no output will be obtained.

Low Output. Insufficient bias on V1 due to R3 changing to a low value (or if C4 is shorted) will cause a low plate voltage and a high cathode voltage, and reduce both outputs. If C1 is leaky the grid of V1 will show a positive voltage to ground. If R1 is open the grid of V1 will tend to block or build up a higher than normal bias, operating at or near cutoff with reduced output. If V1 is leaky or gassy, a positive voltage cause by grid current flow will appear between grid and ground. Should normal bias and plate voltage be indicated by a voltmeter but low output still exists, tube V1 may be low in emission and produce a much weaker than normal signal. When operating properly, the cathode and plate outputs will be equal and just slightly less than the input signal amplitude, because of cathode follower action reducing the gain to less than unity.

Distorted Output. Normally, the output signal will be of the same shape and of only slightly less amplitude than the input signal. Use an oscilloscope to observe the input and output waveforms, with a constant sine-wave input signal applied. Flat-topping or rounding off of the positive peaks of the output signal indicate distortion caused by low emission or reduced plate voltage on V1. If the plate voltage is normal and flat topping occurs the tube is defective. If the tube is operated with too high a bias (near cutoff) the peaks will also be clipped when the tube is driven to cutoff. If cathode bypass capacitor C4 is open, the bias on V1 will change with the signal, and amplification will not be linear, some amplitude distortion will occur and degeneration will cause a drop in output at the signal peaks. For small input signals little or no distortion will be observed. However, on large signals the bias may be driven into the

cutoff region causing bursts of distortion. If C4 is open, the cathode bias will vary instantaneously with the input signal variations and show on a voltmeter as a constantly varying (instead of a steady) voltage. With normal plate and bias voltages, distortion can also be caused by overdrive (too large an input signal). When the distortion observed on the oscilloscope at the outputs disappears as the input signal amplitude is reduced overdrive (or improper biasing) is the cause. Since output coupling capacitors C2 and C3, together with the associated load resistance R_L , are in parallel across the plate and cathode resistors, any change in these components or in the load can create some distortion. Such a condition will usually create an imbalance and result in different output amplitudes. Leaky coupling capacitors will show a positive voltage on the load side as well as on the plate or cathode sides and are easily detected by a high resistance voltmeter.

SINGLE-STAGE PARAPHASE INVERTER (SEMICONDUCTOR)

Application.

Same application as electron tube version.

Characteristics.

Requires more drive than for a single-stage amplifier.

Supplies two outputs with one input signal.

The outputs are oppositely polarized and of approximately the same amplitude.

The bias and load resistance are selected to provide equal output signals.

Provides better frequency response than is possible with an input transformer.

Is Class A-biased for equal swings; normally does not use either Class AB or B operation.


Is usually fixed-biased, but self-biased applications may be encountered.

Circuit Analysis.

General. Where a single-ended stage is used to drive a push-pull amplifier, it is necessary to supply two oppositely polarized input signals to the push-pull stage. While a center-tapped transformer may be used, it has been found that RC coupling generally provides better frequency response, with a saving in economy

through elimination of the transformer, plus a reduction in weight and space. The use of the paraphase inverter circuit provides the necessary dual output. The unbalanced paraphase inverter uses a load in the emitter and a load in the collector to develop the oppositely polarized outputs, and is sometimes referred to in other publications as the *split-load* circuit. Actually, the load is not split; identical load resistors are used to obtain equal output amplitudes. A balanced output condition may be obtained in the single-stage paraphase inverter by adding another resistor, as will be explained later.

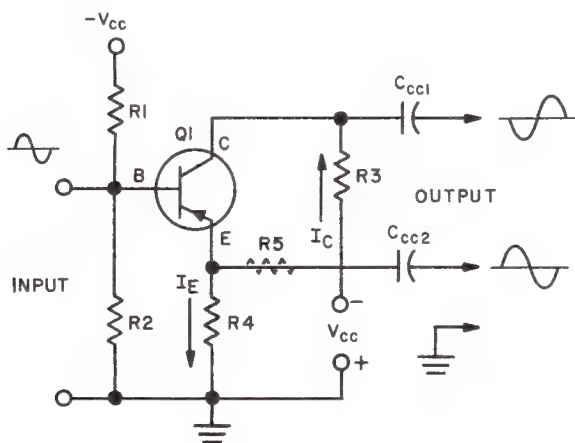Circuit Operation. The accompanying schematic is that of a one-stage unbalanced paraphase inverter.



One-Stage Unbalanced Paraphase Inverter

Fixed voltage-divider bias is supplied by resistors R1 and R2. (See the introduction to this section of the handbook for a discussion of bias arrangements.) The bias is normally Class A with the transistor operating at the center of its dynamic transfer curve. Thus, equal swings about the bias point (with equal loads) will produce equal output signals. R3 is the collector load, and R4 is the emitter load. Both loads are of the same value to produce equal output signals, which are capacitively coupled through Ccc1 and Ccc2 to the push-pull stage.

When a negative input signal is applied to the base of Q1, it adds to the forward bias of Q1 and causes the emitter and collector currents to increase. Electron flow is in the direction indicated by the arrows. The emitter current flowing through R4 produces a

negatively polarized signal, while the collector current flowing through R3 produces a positively polarized signal. Since R3 and R4 are identical in value, and the collector current is practically equal to the emitter current (less the small amount of base current), equal-amplitude output signals of opposite polarity are produced. On the opposite half-cycle of operation, the input signal becomes positive and reduces the forward bias, thus reducing both the emitter and collector currents. In this instance, assuming that the drive is such as to almost stop conduction, the collector output becomes negative and almost equal to the supply voltage. Simultaneously, the emitter current is reduced almost to zero and the emitter becomes positive with respect to the collector. Thus, the emitter and collector outputs change polarity as the input signal changes; the emitter output signal is in-phase and the collector output signal is out-of-phase with the input signal.

Unfortunately, the collector output impedance is higher than the emitter output impedance, and an unbalanced output condition results. Even though equal-amplitude output signals are developed, the push-pull input is basically mismatched for the emitter output and matched for the collector output. As a result, distortion occurs with strong signals.

A balanced output is provided by connecting R5 (shown dotted in the schematic) between the emitter and Ccc2. In this case, the input impedance becomes high for both push-pull transistors, since the impedance of the emitter is now determined by R4 and R5 connected in series, and their total value is chosen to provide an impedance equal to R3. Thus, the distortion produced by strong signals is eliminated. Because a voltage drop occurs across R5, R4 is made larger than R3 to compensate for the loss in output voltage which would otherwise occur.

Since R4 is unbypassed, the voltage developed at the emitter is degenerative, and in effect opposes the input voltage in essentially the same manner as negative feedback; thus, a larger driving voltage must be applied to the base of the phase inverter than would normally be required for an amplifier without feedback. Where this input drive is limited or unavailable, a two-stage paraphase inverter is generally used because of its reduced drive requirements.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of

shunting resistance employed on the low-voltage ranges of most volt-ohm-milliammeter testers. Be careful, also, to observe proper polarity when checking continuity or making resistance measurements with the ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. Lack of supply voltage, no input signal, a defective transistor, or an open collector resistor (R3), emitter resistor (R4), or bias resistor (R2) will produce a no-output condition. The supply voltage can be checked with a voltmeter, and the voltage to ground checked from the emitter, base, and collector, to determine whether normal voltages exist and whether resistor R2, R3, or R4 is open. With an abnormally high voltage between the base and ground, Q1 will be driven into saturation (this indicates that R2 is open). If R2 is shorted, or no input signal is applied, a no-output condition will also exist. If either R3 or R4 is open, emitter and collector current flow will be interrupted and no output will be developed. If either R3 or R4 is shorted, only a single output will be obtained from the portion of the circuit which is not short-circuited. Both resistors would have to be shorted to cause a complete no-output condition. Failure of coupling capacitors C_{cc1} and C_{cc2} will cause loss of output only if they are both either open or shorted to ground; if only one capacitor fails, only one output will be affected. If either capacitor is leaky, a reduced-output condition rather than a no-output condition will occur.

Reduced Output. Low supply voltage, improper bias, changes values of load resistors R4 and R3 (or R5), as well as leaky or defective coupling capacitors, can cause reduced output. The supply voltage and bias may be checked with a voltmeter. However, if R2 were open and a voltage check were made between the base and ground, the voltmeter shunt would replace R2. If the shunt were nearly the same value as R2, a false indication of nearly correct value would be obtained. If the values of R3 and R4 (and R5 if used) increase, then the output signal amplitudes will be less, or unequal at best. With an audio input applied, follow the waveform through the circuit, observing it with an oscilloscope. When the waveform departs from normal, the location of the trouble should be obvious.

Distorted Output. If the bias or supply voltages are incorrect, the load resistance is not of the proper value, or the transistor is defective, a distorted output

will be obtained. Use an oscilloscope to observe the waveform. Since the operation is Class A, equal swings about the bias point should produce equal-amplitude and undistorted outputs of opposite polarity. If overdriven, the tops and bottoms of the waveform will be clipped (a sine wave will appear as a rectangular wave). In the unbalanced circuit (where R5 is not used), strong signals will cause distortion to appear on the collector output but not on the emitter output. In the balanced circuit, strong signals should not cause distortion until they exceed the bias value, and then both outputs should be equally distorted.

TWO-STAGE PARAPHASE INVERTER (ELECTRON TUBE)

Application.

Same application as single-stage version.

Characteristics.

Self bias is usually used, although fixed bias may be used, if desired.

A single-ended input is converted into two out-of-phase outputs.

Amplification may be obtained in addition to the phase inversion.

Either triodes or pentodes may be used, with the pentodes providing higher gain and improved frequency response.

Inherently not self-balancing (usually requires rebalancing if tube is replaced).


Frequency response is relatively uniform from about 100 to 15,000 Hz.

Circuit Analysis.

General. The two-stage paraphase inverter usually employs a single, dual-triode with each half-section connected as a separate amplifier-inverter. Both outputs are taken from the plate circuit, and full amplification can thus be obtained. This type of inverter uses a small portion of the output of one half-section (taken off of a voltage divider across the output) to supply the out-of-phase drive to the second half-section. Balance is primarily determined by the stage gain of the tube. If the gain is different between two tubes (or two half-sections) the voltage divider ratio must be changed (or separate cathode bias resistors are used instead of a common cathode resistor) to

keep the outputs equal. Since such balancing is difficult, the two tube circuit usually is subject to a slight unbalance. However, the large amplification possible permits the stage to be used both as a driver and phase inverter (and sometimes as an output stage) thus economically combining two stages into one.

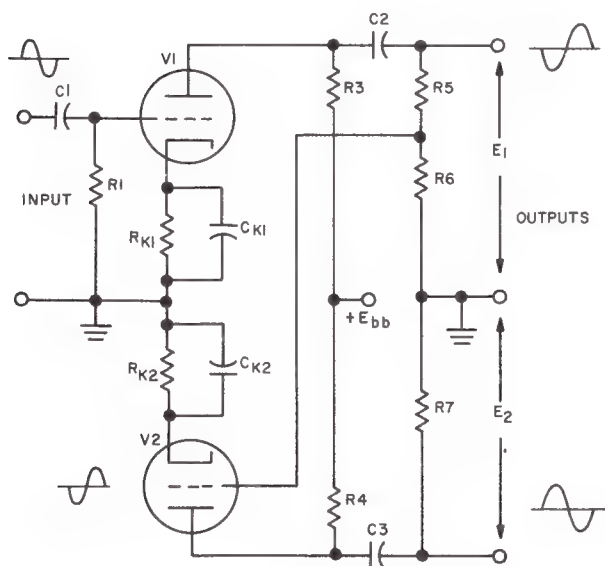Circuit Operation. The following schematic illustrates a typical two-stage triode paraphase inverter. Triodes are used to simplify the discussion.



Triode Two-Stage Paraphase Inverter

Pentodes operate in the same fashion as described below for triode operation, except for considerations of the effect of screen current and voltage (for the same plate voltage a larger swing is possible, and a greater sensitivity and output are obtained with a slight increase in overall frequency response).

The input to triode V1 is RC coupled through C1 and R1, while the inverted input to triode V2 is direct-coupled from voltage divider R5 and R6 connected across the output of V1 (a circuit variation is to employ capacitance coupling and a grid return resistor from V2 to ground). Cathode bias is obtained individually from R_{k1} and R_{k2} bypassed by C_{k1} and C_{k2} , respectively. (In other circuit variations a common cathode resistor, either unbypassed or bypassed,

may be used. Where the single dual-triode is used and separate cathodes are supplied, the circuit shown in the schematic permits closer tube balancing.) Resistors R3 and R4 are the plate load resistors for tubes V1 and V2, respectively, and the outputs are RC coupled through C2, C3, and R5, R6, and R7. Capacitor C2 and voltage divider R5, and R6, provide the output labelled E1 and V1. The inverted input signal for V2 is obtained across R6. Thus R6 also serves as the grid resistor for V2. By direct-coupling from R6 to the grid of V2, any deleterious reactance effects produced by passing the signal through an additional coupling capacitor are avoided (the two coupling capacitors connected in series would reduce the effective low frequency response). Normal operating bias for V1 and V2 is either Class A or Class A prime (AB) operation. Because the input for V2 is taken from across R6, and both R5 and R6 are in series with the grid of the following (output) stage, Class B operation cannot be used (grid current flow on the signal peaks through R6 would produce a distorted input to V2). With no signal applied, the circuit operates in the quiescent condition. Plate current flows through cathode bias resistors R_{k1} and R_{k2} providing normal Class A or AB bias. (See the introduction to this section of the handbook for an explanation of cathode biasing.)

Assume that a sine-wave input signal is applied to the grid of V1. As the signal goes through its positive-going excursion, the grid is driven in a positive direction causing the plate current to increase. The increasing plate current of V1 produces a voltage drop across plate load resistor R3, and reduces the instantaneous plate voltage. Thus a negative-going voltage is developed across R3 (during the positive half-cycle) and is applied to coupling capacitor C2. Since the signal is constantly changing the ac component appears across output resistors R5 and R6, which are connected in series between coupling capacitor C2 and ground. This is the output voltage E1 from tube V1. Resistor R6 is usually one tenth the value of R5, and together they form a voltage divider, so that one tenth of the output of V1 appears as an inverted exciting signal voltage which is applied directly to the grid of V2. This negative-going voltage on V2 grid produces a decreasing plate current in V2, and the voltage across R4 (at the plate of V2) rises towards the source (becomes more positive). The increasing positive-going plate output from V2 is coupled through C3, producing output voltage E2

across R7. Thus the output of V2 is opposite to that of V1 in polarity (out-of-phase) completing the other half of the desired push-pull output. As the plate currents of V1 and V2 rise and fall, the cathode currents do likewise. However, since they are bypassed by capacitors C_{k1} and C_{k2} , they do not affect the steady bias voltage developed by average current flow through the cathode resistors.


When the input signal reaches its positive peak and reverses, conditions, likewise, reverse. The grid of V1 is now driven in a negative direction and the plate current of V1 falls. Output voltage E1 now becomes positive-going and continues to increase until the negative input peak is reached. Meanwhile, the voltage across R6 (which is applied to V2 grid) also rise in a positive direction with the plate voltage of V1, towards the voltage of the supply. Therefore, the grid of V2 is effectively driven positive, causes an increase a plate current and produces a negative voltage drop across plate resistor R4. This negative-going output is coupled through C3 and appears across R7 as output voltage E2. When the input signal reaches the negative peak and swings positive again towards zero level, conditions again revert to that of the initial half-cycle. Thus the positive and negative half-cycle of

input signal control the grids of tubes V1 and V2 to produce relatively identical, but inverted and amplified signals (the relatively large current flow through the large valued plate resistors develops an output voltage much larger than that of the input voltage). Although V2 grid is excited by the output of V1, operation is practically instantaneous so there is no appreciable delay between the input voltage on V1 and that on V2.

A circuit variation of the above described circuit is shown in the accompanying schematic.

In this circuit arrangement, the input to triode V1 is also RC coupled through C1 and R1. However, the inverted input to triode V2 is capacitance coupled by C3 from plate voltage divider R3 and R4 connected across the plate output of V1. The grid of V2 is returned to ground through grid return resistor R5. Cathode bias is obtained individually from R2 and R6 bypassed by C2 and C5, respectively. (In other circuit variations a common cathode resistor, either unbypassed or bypassed, may be used. Where the single dual-triode is used and separate cathodes are supplied, the circuit shown in the schematic permits closer tube balancing). Resistors R3 and R4 are the plate load resistors for tube V1 while R7 is the plate resistor for V2, and the plate outputs are capacity coupled through C4 and C5. Normal operating bias for V1 and V2 is either Class A or Class A prime (AB) operation. With no signal applied, the circuit operates in the quiescent condition. Plate current flows through cathode bias resistors R2 and R6 providing normal Class A or AB bias (see the introduction to this section for an explanation of cathode biasing).

Assume that a sine-wave input signal is applied to the grid of V1. As the signal goes through its positive-going excursion, the grid is driven in a positive direction causing the plate current to increase. The increasing plate current of V1 produces a voltage drop across plate load resistors R3 and R4, and reduces the instantaneous plate voltage. Thus a negative-going voltage is developed across R4 (during the positive half-cycle) and is applied to coupling capacitor C3 to drive V2. Since the signal is constantly changing the ac component appears across plate resistors R3 and R7, which are connected to coupling capacitors C4 and C5. The output voltage from tube V1 is E1. Resistor R4 is usually one tenth the value of R3, and together they form a voltage divider, so that one tenth of the plate output of V1

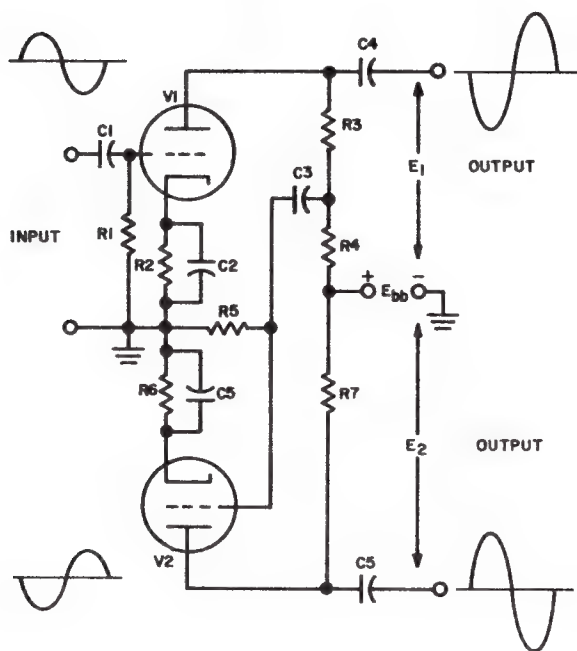

Triode Two-Tube Topped Plate Inverter

appears as an inverted exciting voltage which is applied through C3 to the grid of V2. This negative-going voltage on V2 grid produces a decreasing plate current in V2, and the voltage across R7 (at the plate of V2) rises towards the source (becomes more positive). The increasing positive-going plate output from V2 is coupled through C5, producing output voltage E2. Thus the output of V2 is opposite to that of V1 in polarity (out-of-phase) completing the other half of the desired push-pull output. As the plate currents of V1 and V2 rise and fall, the cathode currents do likewise. However, since they are bypassed by capacitors C2 and C5, they do not affect the steady bias voltage developed by average current flow through the cathode resistors.

When the input signal reaches its positive peak and reverses, conditions, likewise, reverse. The grid of V1 is now driven in a negative direction and the plate current of V1 falls. Output voltage E1 now becomes positive-going and continues to increase until the negative input peak is reached. Meanwhile, the voltage across R4 (which is applied to V2 grid) also rises in a positive direction with the plate voltage of V1, towards the voltage of the supply. Therefore, the grid of V2 is effectively driven positive causing an increase in plate current and producing a negative voltage drop across plate resistor R7. This negative-going output is coupled through C5 and appears as output voltage E2. When the input signal reaches the negative peak and swings positive again towards zero level, conditions again revert to that of the initial half-cycle. Thus the positive and negative half-cycle of input signal control the grids of tubes V1 and V2 to produce relatively identical, but inverted and amplified signals (the relatively large current flow through the large valued plate resistors develops an output voltage much larger than that of the input voltage). Although V2 grid is excited by the output of V1, operation is practically instantaneous so there is no appreciable delay between the input voltage on V1 and that on V2.

In both of the circuits described, the gains of two tubes will vary slightly, and there is a difference in amplitude between the two outputs, unless the bias is changed slightly on one tube. Thus the circuit is seen to be inherently unbalanced, and it does not of itself provide any automatic balancing, as does occur in the cathode-coupled or in the differential types of paraphase circuits. While the circuit values are selected properly by the manufacturer and designer, it

is usually necessary to change cathode and plate resistance values in one tube when a new tube is substituted, to minimize amplitude distortion (this does not authorize any modifications to be made to Navy equipment, since circuit design is presumed to adequately cover such a condition). In most cases the additional distortion produced by tube gain differences is within acceptable limits and is of academic interest only.

When dual-triodes with a single, common-cathode are used in this type of circuit, bias is obtained by a common cathode resistor. In some cases this cathode bias resistor is also bypassed by a capacitor, and a constant unbalance occurs due to the differences in gain between the two half-sections. In other instances, this cathode bias resistor is not bypassed. When unbypassed, the two instantaneous cathode currents flowing in opposite directions tend to cancel out, as in push-pull amplifiers, so that the steady state bias remains substantially constant. Any remaining signal effects which are not balanced out become degenerative, and add to the bias to reduce the total output. When properly designed, this helps to balance the output signals and provide an increase of linearity and a reduction of inherent distortion. Since these circuit variations are only effective to a limited extent, the self-balanced type of paraphase inverter is usually preferred for use where distortion is to be limited to a absolute minimum. Such circuits are discussed later in other paragraphs in this section of the handbook.

Failure Analysis.

No Output. An open input or output circuit, improper bias, or lack of supply voltage, as well as a defective tube can cause loss of output. Check for the proper bias and plate voltage on V1 using a high resistance voltmeter. Too high a bias will almost produce plate current cutoff and reduce the output so low that it is practically no output at all. Measure the bias first from cathode to ground, and then from the grid to ground. If normal bias is obtained from cathode to ground but not from grid to ground, R1 is open. If input capacitor C1 is shorted, tube V1 will be driven into saturation by the plate voltage from the preceding stage driving V1 grid highly positive. If C1 is open, no signal will appear on the grid side but will appear at the input (use an oscilloscope to observe the waveform). If a signal appears at the grid, and in inverted form at the plate of V1 but not at the output, either coupling capacitor C2 (or C4 for the

tapped plate inverter) is open or the output is shorted.

Checking the resistance of R5 and R6 to ground will quickly determine if the output is shorted, if not, then C2 (or C4) is open. Use a capacitance checker to determine if C2 (or C4) is satisfactory. With proper bias and plate voltage, and an input to V1 but still no output, tube V1 is defective. Since the output of V1 is used to supply an input for V2, the output of V1 should always be checked first. When there is an output from V1 but not from V2, either the bias is too high, the plate supply or load is open, the output circuit is open or shorted, or tube V2 is defective. With normal plate voltage and cathode bias on V2 but no signal visible on the plate, tube V2 is defective. Check tube V2; if good, coupling capacitor C3 (or C4) is open, or the output is shorted.

Reduced Output. Improper bias, reduced plate voltage, or a defective tube can cause a reduced output. Check the bias and plate voltage with a high resistance voltmeter. The voltages should be within the limits shown in the instruction book. If the bias is too high on V1, the tube can be driven almost to cutoff on the negative peaks; or if it is too low, V1 may be driven into saturation on the positive peaks. In either case there will be a reduction in output and distortion. Clipping of the waveform can easily be observed with an oscilloscope. If output E_1 is satisfactory, a similar set of conditions can cause a reduction of output in V2. Use the oscilloscope to observe the cathode, grid, and plate of V2. Any signal on the cathode indicates C_{k2} (C5 on the tapped plate inverter) is not properly bypassing or open. Lack of or low grid signal indicates improper voltage division, check R5 and R6 (R3 or R4 on tapped plate inverter) for normal resistance with an ohmmeter.

Distorted Output. Improper bias, low plate voltage, or a defective tube can cause a distorted output. Use an oscilloscope to follow the signal through the circuit from input to V1 grid and plate, to V2 grid and plate, and note when the distortion appears. Too low a bias will cause clipping on the positive peaks, and too high a bias will cause clipping on the negative peaks. Likewise, low plate voltage or low tube emission will also cause peak clipping. If plate voltage reads normal on the voltmeter, and clipping occurs on the positive peaks, the tube emission is low and insufficient to supply the peak current demand.

Since V1 drives V2, any distortion which appears on the output of V1 will also appear on V2 grid, and

will be amplified and appear in V2 output also. With V1 showing no distortion, and V2 distorted, check V2 bias and plate voltage. If these voltages are normal, V2 is probably in need of replacement. Because of the inherent unbalance of this circuit the outputs of V1 and V2 will usually be slightly different, and a slight amount of distortion, say 1 to 2 percent, can be considered as normal operation. Make certain, also, that overdrive is not causing the distortion. Too large an input signal will cause clipping, which can be observed to disappear as the gain is reduced.

TWO-STAGE PARAPHASE INVERTER (SEMICONDUCTOR)

Application.

The two-stage paraphase inverter is used in receivers, public address systems, and modulators to produce sufficient power to drive a high-power push-pull stage from a single-ended input.

Characteristics.

Only a small input signal is necessary to drive the stages to full output.

Supplies two output signals for a single input signal.

The output phase (and polarities) are opposite and suitable for a push-pull input.

Operation is usually Class A, although Class AB or B applications may be encountered.


More than twice the power output of a single-stage phase inverter is obtained.

Distortion is equal to or less than that of the single-stage circuit.

Circuit Analysis.

General. The two-stage paraphase inverter uses two separate transistors operating at their full capabilities in the common-emitter circuit to provide a larger power output than the one-stage phase inverter circuit. Since the output is taken from the collector of each stage, there is no negative feedback in the emitter circuit to overcome (as in the single stage), so that less drive than that required for the single-stage paraphase inverter is required. As a result, more output power is obtained with less drive than for a single stage.

Circuit Operation. The schematic of a typical two-stage PNP transistor paraphase inverter is shown in the accompanying illustration. Transistors Q1 and Q2 are basic common-emitter-connected amplifiers, each supplying a single output. Q2 is connected in cascade with Q1, but has R5 connected in series with the base to limit the current and drop the driving signal to a value equal to that applied to Q1. Thus, with the input signal to Q2 held to the same value as the input to Q1, the output of Q2 is made to equal the output of Q1; also, since the CE circuit produces an inverted output polarity, the two separate output signals are equal and oppositely polarized, and suitable for driving a push-pull stage. Fixed Class A bias is provided for both stages through voltage divider resistors; R1 and R2 bias Q1, while R6 and R7 bias Q2. (See the introduction to this section of the handbook for explanations of types of biasing and stabilization methods.) Resistors R4 and R9 are emitter swamping resistors used for thermal stabilization, and are bypassed by C1 and C2 to prevent degeneration. Since the capacitors bypass any ac component of the signal, they are affected only by dc current variations produced by changing temperature. When a temperature change increases the emitter current, it produces a dc voltage across the swamping resistors which oppose the operating bias and automatically reduces the emitter current to compensate for the temperature-

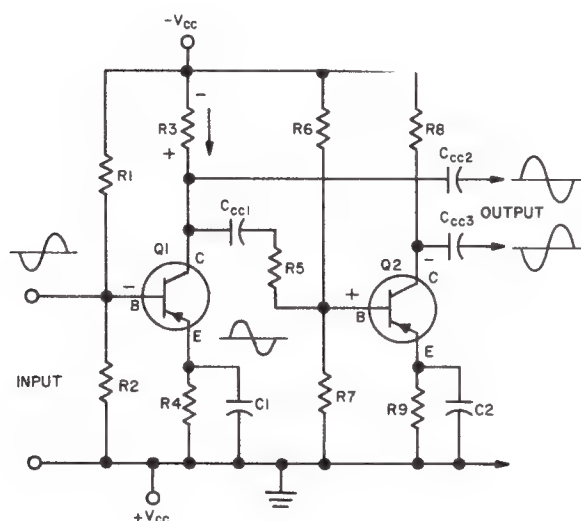

Two-Stage Paraphase Inverter

caused increase. Resistors R3 and R8 are the collector loads of Q1 and Q2, respectively, across which the output voltage is developed. The collector of Q1 is capacitively connected to the base of Q2 by C_{cc1} , and the push-pull outputs are coupled through capacitors C_{cc2} and C_{cc3} .

When a negative input signal is applied to the base of Q1, the forward bias is increased and the emitter and collector currents are increased above the resting (or quiescent) value. Electron flow is from the emitter through C1 to ground, and from the collector supply through R3 to the collector. As shown in the illustration, the collector output of Q1 is positive, and is applied through C_{cc1} to the base of Q2 and through dropping resistor R5 to drive Q2. (The inverted output from the collector of Q1 is supplied to the push-pull circuit by C_{cc2} .) The value of R5 is chosen to supply an input to Q2 just equal to the amplitude of the input signal applied to Q1. With a positive signal applied to the base of Q2, the forward bias is reduced and the emitter and collector currents of Q2 are reduced. Electron flow is from the emitter of Q2 through C2 to ground, and from the collector supply through R8 to the collector. Since Class A bias is used, and assuming that the base voltage applied to Q2 is just equal to the bias, collector current flow is reduced to zero and the collector voltage rises to that of the negative supply (both ends of R8 are negative with respect to ground). Thus, a negative output is obtained from the collector of Q2 and is applied through C_{cc3} as the oppositely polarized (in-phase) push-pull driving signal. Since Q2 operates practically instantaneously (there is no inherent delay), the two outputs appear on the push-pull grids simultaneously. (Note that passage through one stage inverts the signal, while passage through two CE stages returns the signal to the original polarity.)

Assuming a sine-wave input, when the negative half-cycle is completed the signal reverses, and a positive input is now applied to the base of Q1. The positive input reduces the forward bias of Q1 to zero (assuming full swing) and the collector voltage rises to that of the negative supply, thus producing a negative output. The large-amplitude negative collector output is dropped through R5 so that it is approximately equal to the input signal amplitude applied to Q1. This small negative input to the base of Q2 increases the forward bias and causes the collector current flow through R8 to increase. Electron flow is from the supply through R8 to the collector, which produces a

positive voltage drop at the collector (the polarity of this voltage drop is opposite that of the previous half-cycle), so that the output from Q2 is now positive. Since there is no inherent delay in the operation of the transistor, the positive output from Q2 and the negative output from Q1 appear parctically simultaneously at the push-pull inputs.

Dropping resistor R5 acts as a balancing resistor to equalize the output of both stages. The transistors need only be of similar types; matched pairs are not required. The collector resistors are usually made equal so that identical currents will produce equal output voltages. Where little power is required, such as that needed to drive a conventional Class A push-pull stage, swamping resistors R4 and R9 and their associated bypass capacitors C1 and C2 may be eliminated from the circuit, and the emitters connected directly to ground. In applications where distortion becomes critical, the use of feedback from the collector is resorted to by connecting bias resistors R1 and R6 to their collectors. In this instance resistors R2 and R7 could be eliminated by changing the values of both R1 and R6. Thus, it is evident that the basic schematic may vary slightly, according to individual design, using different bias and stabilization methods. However, the operation is essentially the same since two stages of amplification are used to invert one of the outputs and thus provide a push-pull output.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low-voltage ranges of most volt-ohm-milliammeter testers. Be careful, also, to observe proper polarity when checking continuity or making resistance measurements with the ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. Lack of collector voltage, improper bias, or an open R3, R4, or C_{cc1} will prevent Q1 from driving Q2 and there will be no output. The same result will be obtained if Q1 is defective. A defective Q2 or a component in that stage will affect only the output from Q2; the output from Q1 will be unaffected. Measuring the supply voltage, collector voltage, and bias with a voltmeter will usually indicate the portion of the circuit in which the defective part is located. If either R2 or R7 is open,

the bias will be determined by the internal base-to-emitter resistance of the transistors. However, when measured with a voltmeter from base to ground, the meter shunt will act as the lower portion of the bias divider, and cause a false indication. Check also for the presence of an input signal (use an oscilloscope or VTVM probe) since the phase inverter is usually RC-coupled to a preamplifier stage. An open output resistor or coupling capacitor in the preamplifier will not permit any input to appear at the base of Q1. Swamping resistor R4 or collector resistor R3, if open, will prevent the flow of emitter and collector current. If R4 is shorted, the circuit will be temperature-sensitive, but it will operate normally otherwise; with a shorted collector load resistor (R3), no output will be obtained from Q1 and, consequently, Q2 also. A leaky coupling capacitor, C_{cc1} will not produce a no-output condition, but will cause partial clipping of the signal and distortion. If shorted, the increase in bias will drive Q2 into heavy saturation, and, while the output Q2 will be lost, an output will still be supplied from Q1. If R5 is open, no output will be obtained from Q2; if R5 is shorted, the outputs of Q1 and Q2 will be greatly different in amplitude, and distortion will be present. If bias resistor R6 is opwn, contact bias will be placed on Q2; and thus the output will be distorted, and of larger amplitude than normal. If R9 is open, there will be no output from Q2. If collector resistor R8 is open or shorted, no output will be obtained from Q2. If the output coupling capacitors are open, no output will result; if they are otherwise defective, only reduced output will occur.

Reduced Output. Low collector voltage, improper bias, of a defective transistor can cause reduced output. Usually, a voltage check of the supply and bias will determine whether one or more of these voltages are at fault. If either of the swamping resistor bypass capacitors, C1 or C2 is open, the degenerative effect of the swamping resistors will cause reduced output and require greater drive in the stage affected. Since Q1 drives Q2, and open C1 will change both outputs; if only C2 is open; only the output of Q2 will be affected. A leaky coupling capacitor C_{cc1} will improperly bias Q2 and cause a clipped and reduced output. If one or more of the coupling capacitors are completely shorted, the collector voltage will be placed on the following transistor base, cause heavy flow of forward current, and bias the transistor into saturation, thus reducing the output of the stage to a

small value. When normal voltages and bias appear to be present, use an oscilloscope to follow the waveform through the circuit. When the waveform changes amplitude, the location of the trouble should be obvious. If all voltages and resistances check normal and yet the waveform is defective, then the transistor in that portion of the circuit is at fault.

Distorted Output. Improper bias or supply voltage, overdrive, or a defective transistor can cause distortion. Use an oscilloscope to check the waveform, after checking the bias and collector voltages with a voltmeter. Follow the input signal through each stage to the output, checking for proper amplitude and polarity. The signal at the collector of Q1 should be similar to that on the base, but of opposite polarity. The signal on the base of Q2 should be equal in amplitude to that on Q1, but of opposite polarity also. Both collector outputs to ground should be of equal amplitude but of opposite polarity. If the dc bias and collector voltages are normal but a distorted collector output occurs, the transistor is probably defective. Replace the transistor with one known to be good. Make certain that the input signal is undistorted; otherwise, the distortion will be amplified and inverted in passing through the circuit. Clipping of the peaks and troughs of the signal indicate that the input drive is too great.

PARAPHASE, CATHODE-COUPLED INVERTER (ELECTRON TUBE)

Application.

The paraphase cathode-coupled inverter is used to drive a push-pull audio amplifier from a single-ended source. It is used in audio amplifier systems where self-balance together with amplification is desired, and good frequency response and a minimum of distortion is required.

Characteristics.

Self bias is usually used, although fixed bias may be used, if desired.

A single-ended input is converted into two equal and out-of-phase outputs.

Amplification is restricted to about half the maximum value obtainable from a single tube.


Is self-balancing, with a relatively uniform frequency response of approximately 100 to 20,000 Hz.

Either triodes or pentodes may be used, with the pentodes providing higher gain and slightly improved high frequency response.

Circuit Analysis.

General. The cathode coupled inverter is usually used with dual triodes having a common cathode. This circuit offers a saving in space and weight over those of the two tube type of inverters with a slight reduction of components. The inherent self-balancing feature makes it particularly valuable for circuits requiring a minimum of distortion, since a slight amount of degenerative feedback occurs in the cathode circuit and improves the linearity. In addition there is no necessity to rebalance the circuit when tubes are changed, and hum due to cathode-to-heater leakage is kept to a minimum.

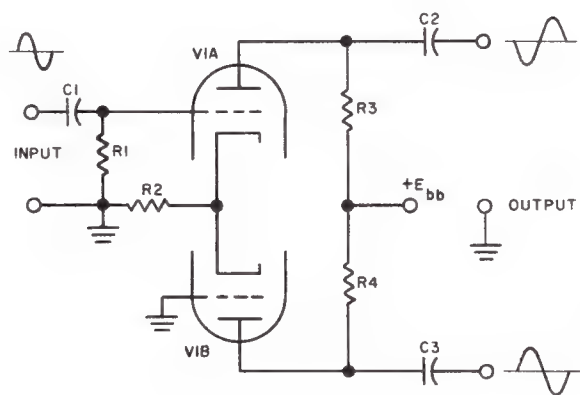Circuit Operation. The following schematic illustrates a typical cathode-coupled paraphase inverter. Although separate cathodes are shown for simplicity and ease of discussion, the tube is actually a dual section triode with a common cathode.




Cathode-Coupled Paraphase Inverter

The input signal is RC coupled through capacitor C1 and grid resistor R1 to the grid of triode V1A, a half-section of dual-triode tube V1. Cathode bias and signal injection for tube V1B, the other half-section of V1, is provided through common cathode resistor R2. The outputs of both half-sections are also RC coupled to the following push-pull stage. Resistor R3 is the plate load resistor for V1A from which the

out-of-phase output is coupled through C2, while resistor R4 is the plate resistor for V1B, and the in-phase output is coupled through C3.

In the quiescent condition with no signal applied, both V1A and V1B conduct and develop cathode bias across R2. The value of R2 is chosen so that the bias is set at the center of the tubes dynamic operating range, with about half normal plate current flowing through each half-section of V1. Since a push-pull output is produced, the cathode and plate current of one half-section increases while that of the other decreases. Thus the average bias remains substantially constant and there is no necessity for bypassing the cathode resistor.

When a sine-wave signal is applied to the input it is effectively passed through capacitor C1 and appears across R1. Assume that the sine-wave is starting its positive half cycle of operation, the grid of V1A is driven in a positive direction, and causes an increased plate current to flow. Electron flow is from ground through cathode resistor R2, tube V1A, and plate resistor R3 to the supply. This electron flow creates an instantaneous polarity as shown in the accompanying simplified drawing.

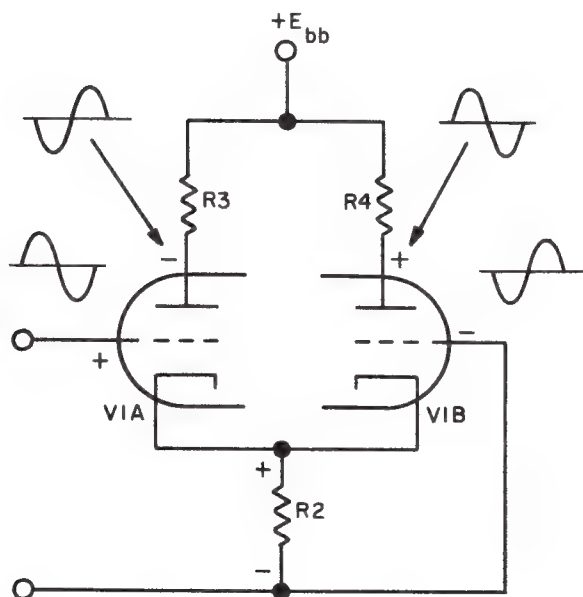

Simplified Polarity Diagram For Positive Half-Cycle of Operation

As can be seen from the drawing, the cathodes of both V1A and V1B become more positive, while the instantaneous plate voltage is decreased by the voltage drop across R3, producing a negative output at the plate. This negative output is coupled through C2 to drive the next stage. The normal grid to plate phase-inverting property of an electron tube is used in this half-section to develop the out-of-phase signal. Meanwhile, with an increasing positive voltage applied to the cathode of V1B, you recall from basic theory that this is the same as applying a negative signal to the grid, and V1B plate current is, therefore, decreased. As the plate current of V1B is decreased, the plate voltage rises towards that of the supply, and a positive output is developed across R4. This positive output is coupled through C3, as the in-phase signal, to drive the following push-pull stage. When the input signal reaches its positive crest, V1A is heavily conducting while V1B is lightly conducting, and opposite and equal output voltages are produced.

As the input signal changes direction and becomes negative-going, operation reverses and the instantaneous polarity becomes opposite that shown on the drawing. Thus tube V1A plate current reduces and V1B plate current increases. The cathode voltage developed across R2 also reduces, which is the same as driving V1B grid positive and causes V1B plate current to increase. A negative output is now produced by the voltage drop across plate resistor R4, and a positive output voltage is developed across R3 as the plate voltage of V1A rises towards the supply voltage with the reducing plate current. Thus the outputs are reversed to produce the negative half-cycle of input signal.

When the negative input signal peak is reached, operation again changes back to the original state with V1A plate current increasing while V1B plate current decreases.

Failure Analysis.

No Output. Too high a bias, lack of supply voltage, an open input or output circuit, or a defective tube can cause loss of output. Check the bias and plate voltage with a high resistance voltmeter. With normal bias and plate voltage and no output, either there is no input signal or coupling capacitor C1 is open, or output coupling capacitors C2 and C3 are open, or the tube is defective. Use an oscilloscope

and check for a signal on both sides of C1. If the signal appears at the input but not on the grid side of the capacitor, it is open. Likewise, if the signal appears on the plate but not at the output, the associated output coupling capacitor (either C2 or C3) is open. If grid resistor R1 is shorted no signal will appear on the grid of V1A also. A simple resistance check from grid to ground will reveal if the input is shorted. If both half-sections of V1 are defective, or if V1A is defective no output will be obtained, but if only half-section V1B is defective an output will be obtained from V1A.

Low Output. Improper bias, low plate voltage, or a defective tube will cause a reduced output. If input capacitor C1 is shorted or leaky, a positive voltage will be applied to the grid of V1A, will cause a heavy flow of plate current and bias off the tube near the cutoff point. If extreme, practically no output will occur, otherwise, a reduced output will be obtained depending upon the amount of bias produced. Usually such a condition will be indicated by a high cathode bias, with a positive grid voltage, and a low plate voltage caused by the large drop through the plate load resistor, produced by the excessive plate current flow. If R2 changes to a lower value, the bias across R2 will tend to remain the same because a larger plate current flows, the increased flow of plate current will, however, cause a larger than normal drop across the plate resistor(s), reduce the plate voltage, and hence the output. If the emission of tube V1 is low, apparently normal grid and plate voltages may be measured on the voltmeter, but the output will be weak and distorted when a signal is applied since the plate current will not be able to follow the signal.

Distorted Output. Due to the common cathode and bias arrangement a decrease in plate current flow on one side will be compensated for by an increase on the other side. Hence distortion is kept to a minimum. Use an oscilloscope and compare the input, grid, and cathode waveforms; they should all be uniform and of the same relative amplitude. Now compare the plate and output waveforms. They should be identical and of larger amplitude. If distortion appears and is eliminated by reducing the input signal, overdriving is indicated. If distortion appears in the plate circuit but not in the grid circuit, either the tube needs replacing or the plate voltage or load is at fault. If either of coupling capacitors C2 or C3 are leaky, a reduced plate voltage may be produced because of voltage division effects across

the next stage input resistors, and cause unbalance and distortion. Check the plate voltage with a voltmeter, if below normal, check the associated plate load resistance with an ohmmeter and check the coupling capacitor with a capacitance checker.

DIFFERENTIAL PARAPHASE INVERTER (ELECTRON TUBE)

Application.

The differential paraphase inverter is used to drive a balanced push-pull audio amplifier from a single-ended (unbalanced) source. It is used in audio amplifier systems where high amplification and good balance is necessary.

Characteristics.

Self bias is usually used, although fixed bias may be used, if desired.

A single-ended (unbalanced) input is converted into two equal and out-of-phase outputs.

Almost full tube amplification is obtainable.

Circuit is self-balancing with a relatively uniform frequency response of 100 to 20,000 Hz or more.


Pentodes are used for high gain and increased high frequency response, but triodes may be used in special instances.

Circuit Analysis.

General. The differential paraphase inverter uses the difference between the two output signals to supply the driving signal for the in-phase output. Pentodes are usually employed, since their high gain permits reducing the difference signal to such a small value that for all practical purposes the outputs can be considered identical. The method of obtaining the difference signal provides an effective negative feedback which stabilizes the gain through the circuit and improved its self regulating properties.

Circuit Operation. The following schematic illustrates a typical differential paraphase inverter.

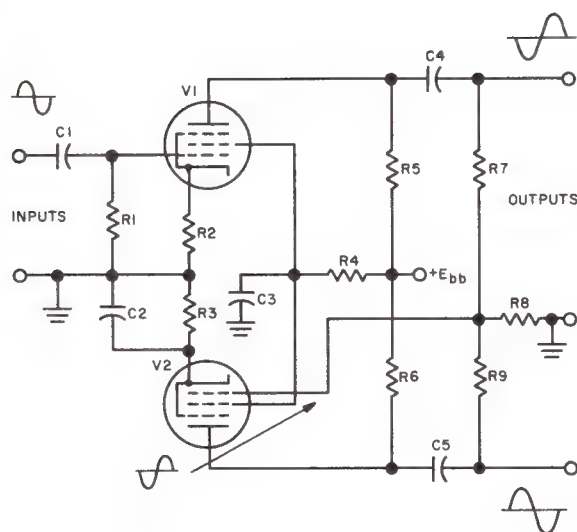The input signal is RC coupled through input coupling capacitor C1 and grid resistor R1 to the grid of V1. Cathode bias for V1 is developed across unby-passed cathode resistor R2, and through R3, bypassed by C2, for tube V2. Screen voltage is obtained from the common plate supply source through series screen voltage dropping resistor R4, and the screens are



Typical Differential Paraphase Inverter Circuit

bypassed to ground by screen capacitor C3. The suppressor elements of the tubes are connected to the cathode. Resistive plate loads and capacitive output coupling is provided. The output is developed across plate resistors R5 and R6, and is applied through C4 and C5 to the output voltage divider consisting of R7 and R9 connected in series with difference resistor R8 to ground. Resistors R7, R8, and R9 also function as grid resistors for the following push-pull stage driven by the inverter.

Tube V1 operates as a conventional resistance coupled amplifier, with the unbypassed cathode resistor providing a slight amount of degenerative feedback to improve the overall response and stabilize the gain. In the quiescent condition, with no signal applied V1, the cathode current consisting of the sum of the screen current and plate current flows through cathode resistor R2 to establish the normal bias level. With a steady screen current flow, a constant voltage drop is produced across screen resistor R4, and together with the screen current of V2, is sufficient to drop the plate supply to the desired screen voltage value. Since R4 is bypassed by C3, the screen voltage remains unaffected by any signal variations when the signal is later applied. Any dc voltage drop across plate resistor R5 reduces the plate supply to the desired quiescent plate voltage value, and no output is

produced. In a similar manner, V2 rests in the quiescent condition with its bias determined by the sum of the screen and plate currents (total cathode current) of V2 through separate cathode bias resistor R3. Since R3 is bypassed by C2, the bias on V2 also will not change with the signal later when it is applied. With both V1 and V2 screens connected in parallel the same screen voltage is applied to both tubes. Although quiescent plate current flow through R6 produces a voltage drop which reduces the supply voltage to that desired for the plate operating value, it is a steady dc and no output appears from C5. From the discussion and an examination of the schematic, it is evident that V2 also operates as a conventional resistance coupled stage similar to V1 except for the source of input voltage. With R7 and R9 connected as a voltage divider in series with R8 across the output of V1 and V2, when a voltage appears across R8 an input is applied to V2 grid. Since the outputs of V1 and V2 drive a push-pull stage they are opposite in polarity and equal, and the effective voltage across R8 is zero. However, the bias network is designed so that the output of V1 is always slightly greater than that of V2, the difference voltage then appears across R8 and is the driving voltage for V2.

With the basic conditions now established, assume that a sine-wave input signal is applied to the grid of V1. During the positive half-cycle of the input signal, the grid of V1 causes an increased plate current flow, and produces a negative-going voltage drop across plate resistor R5, which is applied through C4 to output voltage divider R7 and R8. The portion of negative output voltage appearing across R8 is applied to V2 grid, produces a reduction in plate current, and the plate voltage of V2 rises towards the supply value. Thus, positive-going output is applied across C5 to output voltage divider R9 and R8. The output voltage from V2 appearing across R8 opposes the output developed by V1 across R8, and all but a small fraction of this voltage is cancelled out. This small difference voltage is the actual drive voltage applied V2 grid.

When the input signal on V1 reaches its positive peak and reverses, it becomes negative-going. This negative grid voltage on V1 causes a reduction in the plate current of V1, and the plate voltage rises towards that of the supply. Thus a positive-going output voltage is developed, which is applied through C4 to output voltage divider R7 and R8. The positive

portion of voltage across R8 drives V2 grid in a positive direction, and causes an increased plate current flow through plate resistor R6. The voltage drop across R6 is negative-going and is coupled to output divider R9 and R8 through C5. The negative output voltage from V2 cancels all but a small fraction of the positive voltage across R8. Because the plate output of V2 is also connected back to the grid by voltage divider R9 and R8, a feedback loop exists. Since the output of V2 is always out-of-phase with the grid of V2 the feedback is essentially negative. Thus V2 is stabilized and improved response and linearity are obtained. At the same time, this feedback ensures that the output of V2 is always slightly less than that of V1. Since negative feedback is provided from plate to grid, the cathode of V2 is bypassed by C2 so that full amplification without further degeneration may be obtained.

When the input signal reaches its negative peak and reverses, once again it is positive-going and the initial action discussed above for V1 is repeated. Thus alternate positive and negative half-cycles of input signal produce equal and balanced out-of-phase outputs. The V1 output is always out-of-phase with the input, while the output of V2 is always in-phase with the input.

Failure Analysis.

No Output. An open input or output circuit, lack of supply voltage, input signal, or a defective tube will cause a no-output condition. Check the cathode bias, and plate and screen voltages with a high resistance voltmeter. If the voltages are normal but no output exists, check the input with an oscilloscope. If the signal appears at the input but not on V1 grid, coupling capacitor C1 is open or R1 is shorted. Check the resistance from grid to ground to determine if the input is shorted. If the signal appears on the grid but not on the plate, make certain that proper screen voltage exists. If C3 is shorted the entire screen voltage will be dropped across R4 and no output will appear, likewise, if R4 is open no screen voltage will be applied either V1 or V2. Loss of screen voltage will be detected during the other voltage tests since both plate and bias voltages will be higher and lower than normal, respectively. With normal plate and screen voltage applied, if still no signal appears on the plate, either the tube is defective or plate resistor R5 is shorted.

If a signal appears on the plate but does not appear at the output, either coupling capacitor C4 is open or

R7 and R8 are shorted. Check the capacitor with an in-circuit capacitance checker and the output voltage divider resistors with an ohmmeter.

If an output appears from V1 but not from V2, check with the oscilloscope for a signal on V2 grid. If no signal appears, R8 is either open or shorted. If a signal appears on the grid of V2 but not on the plate, V2 must be at fault. Previous voltage checks were made for bias, screen, and plate voltage so that C2, R3 and R6 cannot be at fault.

Check V2; if no output can be obtained either C5 is open or R9 is shorted. Check the capacitance of C5 with an in-circuit capacitance checker, and measure the resistance of R9. Also measure the resistance from C5 to ground to determine that a short does not exist across the output. Such a condition could be caused by a shorted grid-to-cathode element in the following push-pull stage.

Low or Unbalanced Output. Improper bias, low plate or screen voltage, as well as a defective tube can cause a reduced output. If return resistor R1 is open or becomes high in value with age, the grid of V1 will tend to develop a negative bias and block causing reduced output from both tubes. Check the value of R1 with an ohmmeter. If R4 changes to a higher value, the screen voltage and output will be reduced. Check the screen voltage with a voltmeter and the resistance of R4 with an ohmmeter. If C3 is partially shorted or leaky, the excess current drain through R4 will also lower the screen voltage. If the screen voltage rises when C3 is disconnected from ground, replace the capacitor. If the emission of either tube is low, the voltages may show normal, and signals appear on grids and plate, but a reduced output occurs because of the inability of the tube plate current to follow the signal completely.

If bypass capacitor C2 becomes shorted, the cathode resistor of V2 will be effectively removed from the circuit, and the tube will operate at zero bias. Such operation will cause an unbalanced output with distortion. Checking the resistance of R3 to ground with an ohmmeter will determine if C3 is shorted. If bias resistors R2 or R3 change in value the balance will also be upset, depending upon the amount of change. An ohmmeter check of the resistors will determine whether they are at fault. If either plate resistor R5 or R6 increase in value the output will be above normal, but if they decrease in value the output will be below normal. While the supply voltage drop may be different for each of these cases, the

current will also change and may make the plate voltage reading fall within tolerance values. Therefore, a resistance check of the plate resistors will quickly show if they have changed in value. Changes in voltage divider resistors R7, R8, and R9 will change the gain, drive, and output. Tube V1 output is affected mostly by R9. Defective tubes in the push-pull circuit following this stage can cause a heavy load with a consequently reduced output.

Distorted Output. Improper bias, screen or plate voltage, as well as a defective tube or overdrive can

cause distortion. Check the bias, plate, and screen voltages with a voltmeter. If all voltages are normal but the output is distorted and low the tubes are probably defective, replace them with known good ones. If the distortion reduces when the input signal is reduced, it is the result of too high a drive for the bias used. Poor balance will also cause distortion. Use an oscilloscope and follow the signal from grid to plate through the circuit, and compare outputs. When the distortion appears the cause will be found in the parts associated with that portion of the circuit.

PART 5-4. CATHODE FOLLOWERS

BASIC CATHODE FOLLOWERS
(ELECTRON TUBE)**Application.**

The cathode follower is used for two purposes: To isolate the output of a critical circuit from the loading effects of a circuit to which the output is fed; and to match the output impedance of a signal source to the input impedance of a load circuit. Both purposes are accomplished with an absolute minimum of distortion of the input signal.

Characteristics.

Utilizes a single-stage degenerative amplifier, to furnish an output which appears across an unbypassed cathode resistor.

Input impedance is high; no grid current flows.


Output impedance is low; output signal is in phase with input signal.

Output voltage gain is less than unity; output exhibits a power gain.

Operated Class A to obtain, in the output signal, a faithful reproduction of the input signal.

Circuit Analysis.

General. In the basic circuit shown in the accompanying illustration, a triode tube is used, but a pentode tube may be employed in a similar manner. In the basic circuit the cathode bypass capacitor is absent, and the plate is tied directly to the supply voltage, $+E_{bb}$. The input signal is applied through coupling capacitor C1 to the grid of the tube, V1, and the grid is returned to ground through a relatively high value grid resistor, R1. The output is taken across the cathode resistor, R2, and since this resistor is unbypassed, the output signal voltage is a direct function of the plate current which flows through this resistor. As the input signal rises, or goes in a positive direction, the plate current increases, causing an increased voltage drop across the cathode resistor. As the input signal falls, or goes in a negative direction, the plate current decreases, causing a decrease in voltage drop across the cathode resistor. Thus the output signal *follows* the input signal, both in value and in polarity, although the actual (voltage) value of the output signal is somewhat less than that of the input signal.

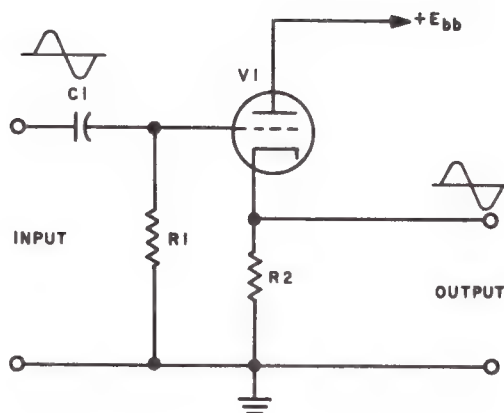

Basic Cathode Follower Circuit

Circuit Operation. In the basic cathode follower circuit, under conditions of no signal input to the grid, a certain amount of plate current flows through the tube because of the positive potential applied to the plate from the plate supply (E_{bb}). This plate current flows through the cathode resistor, R2, and the resultant voltage drop across R2 establishes the no-signal bias level, with the grid effectively at zero (ground) potential, and the cathode at some positive (above ground) potential.

When a positive signal is applied to the grid, the resulting increase in plate current through cathode resistor R2 increases the voltage drop across R2, making the cathode more positive. In like manner, a negative signal applied to the grid causes the plate current flowing through cathode resistor R2 to decrease, making the cathode less positive. Thus the signal variation on the grid produces a variation in plate current through the cathode resistor, and the resulting variation in voltage drop across the resistor develops the bias voltage. This bias voltage, being in phase with the input signal, subtracts from the input signal during the positive half cycle, and adds to the input signal during the negative half cycle. The resulting change in bias in both cases reduces the amplitude of the grid-to-cathode voltage, producing degeneration of the output voltage. For this reason, the voltage gain of a cathode follower is always less than one.

Cathode followers are normally operated with the grid negative with respect to the cathode under conditions of no input signal. The input impedance is

high, and remains high when an input signal is applied. When a positive signal is applied to the grid, the degenerative action increases the grid bias to such an extent that no grid current will flow. This is the same result that would be obtained if the input impedance had been increased. When a negative signal is applied to the grid, no grid current can flow, even though the grid bias is decreased through the degenerative action. Thus the input impedance remains high. As a result of this high constant input impedance, the cathode follower presents a negligible loading effect to the circuit driving it.


The effective input capacitance of a cathode follower is low, compared to that of a conventional amplifier. This results from the fact that the degenerative action reduces the amplitude of the ac component of the grid-to-cathode voltage, and thus causes less current to flow through the tube capacitances.

The output impedance of a cathode follower is low; because of this fact there is a minimum of amplitude distortion of the output signal, under normal operating conditions, even though current is drawn from the output terminals. However, if the amplitude of the input signal is high enough to swing the voltage at the grid too far positive or negative, the tube may be driven to saturation or to cutoff, respectively. When either of these points is reached, limiting action occurs, and any further change in the input signal will not appear in the output waveform. The output signal will thereby be distorted with respect to the input.

Occasionally, a cathode follower circuit may be encountered which is actually designed to operate partially in the region of cutoff. In radar circuitry, video and transmitter trigger pulses, which may be positive pulses, might be applied to a cathode follower which is biased near cutoff. As a result, the cathode follower will pass the signal in normal cathode follower fashion; at the same time it will clip any negative transients which may be present in the input signal, and, in addition, it will eliminate the possibility of any dc loading effects by allowing only the signal voltages to be present across the output cathode resistor. Although this of circuit may be termed a *cathode follower circuit* (because the output is taken from across the cathode resistor), it does not satisfy that definition of a cathode follower where the output signal shall follow the input signal without change in waveform. In this respect such a circuit,

sometimes referred to as a *cutoff cathode follower*, should more properly be termed a *limiter-follower*.

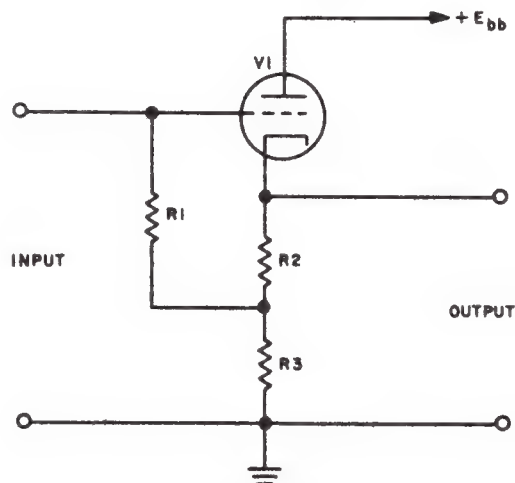If limiting occurs only on the negative peaks of the input signal, i.e., if the input signal drives the tube to cutoff but not to saturation, the circuitry of the cathode follower may be modified as shown in the accompanying illustration.



Modified Cathode Follower Circuit to Prevent Negative Peak Limiting

In this modified cathode follower circuit, the grid resistor, R1, is returned to a positive (above ground) potential at the junction of a two-section cathode resistor composed of resistors R2 and R3. The value of the positive potential (the relative values of R2 and R3) is determined by the anticipated input voltage level. By returning the grid resistor to a tap on the cathode resistor in this manner, the grid bias is reduced by the amount of the voltage drop across resistor R3. Therefore, the input signal can swing to a greater negative value without driving the tube to cutoff, than it could had the grid resistor been returned to ground potential. In addition, the input impedance of the circuit is increased to a very high value.

A further modification of this circuit is frequently used as a wide-band cathode follower. This circuit, shown in the following illustration, contains an input coupling capacitor, C1, and a resistor, R4, of small value in the plate circuit for decoupling purposes. Wide-band cathode followers find extensive use when

application requirements demand power amplification over an extreme range of audio frequencies, from 70 to 20,000 Hz, such as in high-fidelity audio circuits. In the circuit shown below, these requirements may be met by the use of a single triode section of a type 12AT7 twin-triode, with values of $C1 = 0.01 \mu f$, $R1 = 1$ megohm, $R2 = 180$ ohms, $R3 = 820$ ohms, and $R4 = 47$ ohms. Other values would of course be required with other tube types.

The voltage gain (V.G.) of a cathode follower, when a triode-type tube is used, is given by the following equation:


$$V. G. = \frac{\mu R_k}{r_x + (\mu + 1) R_k}$$

When a pentode-type tube is used, μ is large and the term $\mu + 1$ may be reduced to μ . The equation for voltage gain (V.G.) may then be reduced to:

$$V. G. = \frac{R_k}{\frac{1}{g_m} + R_k}$$


The output impedance (Z_{out}) of a cathode follower is given by the following equation:

$$Z_{out} = \frac{R_k}{g_m R_k + 1}$$

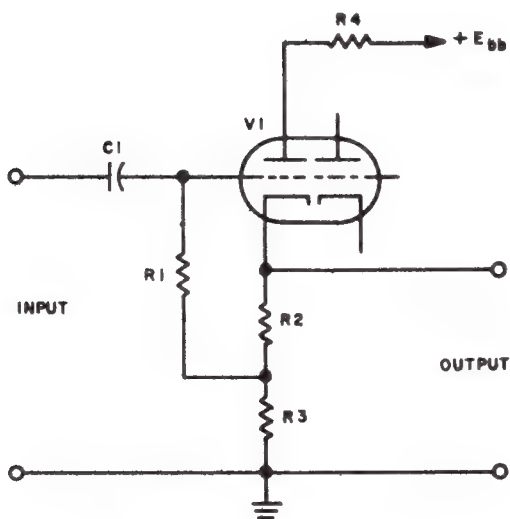

Wide-Band Cathode Follower Circuit


Other modifications of the basic cathode follower circuit are often encountered in radar and communications circuitry. These modifications are included in the following illustrations, which show five circuit variations of cathode followers. In part A, a fixed negative bias is applied, from a power supply, to the grid of a triode at a tap on the grid resistor which is composed of $R1$ and $R2$. The output is taken across the cathode resistor, $R3$. The negative bias applied to the grid, together with the bias developed across the cathode resistor, establishes the initial operating point on the grid voltage-plate current (E_g-I_p) characteristic curve of the particular triode used. The value of negative bias applied depends upon the value of input signal to be handled. This is particularly true in applications where the input signal consists of a series of positive pulses with the interval between each pulse relatively long as compared with the pulse width. For example, if a positive input pulse having an amplitude of 4 volts with instantaneous peak values of +96 volts and +100 volts is applied to the input capacitor of a cathode follower circuit, the pulse which appears at the input grid of the tube would settle down to an average ac value of 0 volts, with most of the pulse appearing above this average value. This is shown in the following "input waveform" illustration, with the input signal shown in part A and the signal voltage which appears at the input grid shown in part B. Fixed biasing is necessary in this situation, in order to place the geometric center of the pulse at the center of the tube's E_g-I_p curve, as shown in part C of the illustration. If, for a given tube, the center of the straight-line portion of the E_g-I_p curve occurs at -5 volts with a given plate voltage, and the input signal is 4 volts peak to peak with the pulse waveform as shown, a total bias of -7 volts on the tube would be necessary in order to displace the average value of the signal so that its geometric center occurs at -5 volts (the center of the E_g-I_p curve), as shown in part D of the illustration. If the value of the cathode resistor is such that, when the tube is operating with -7 volts bias, it produces a 3-volt drop, then the additional amount of fixed bias required is equal to -4 volts.

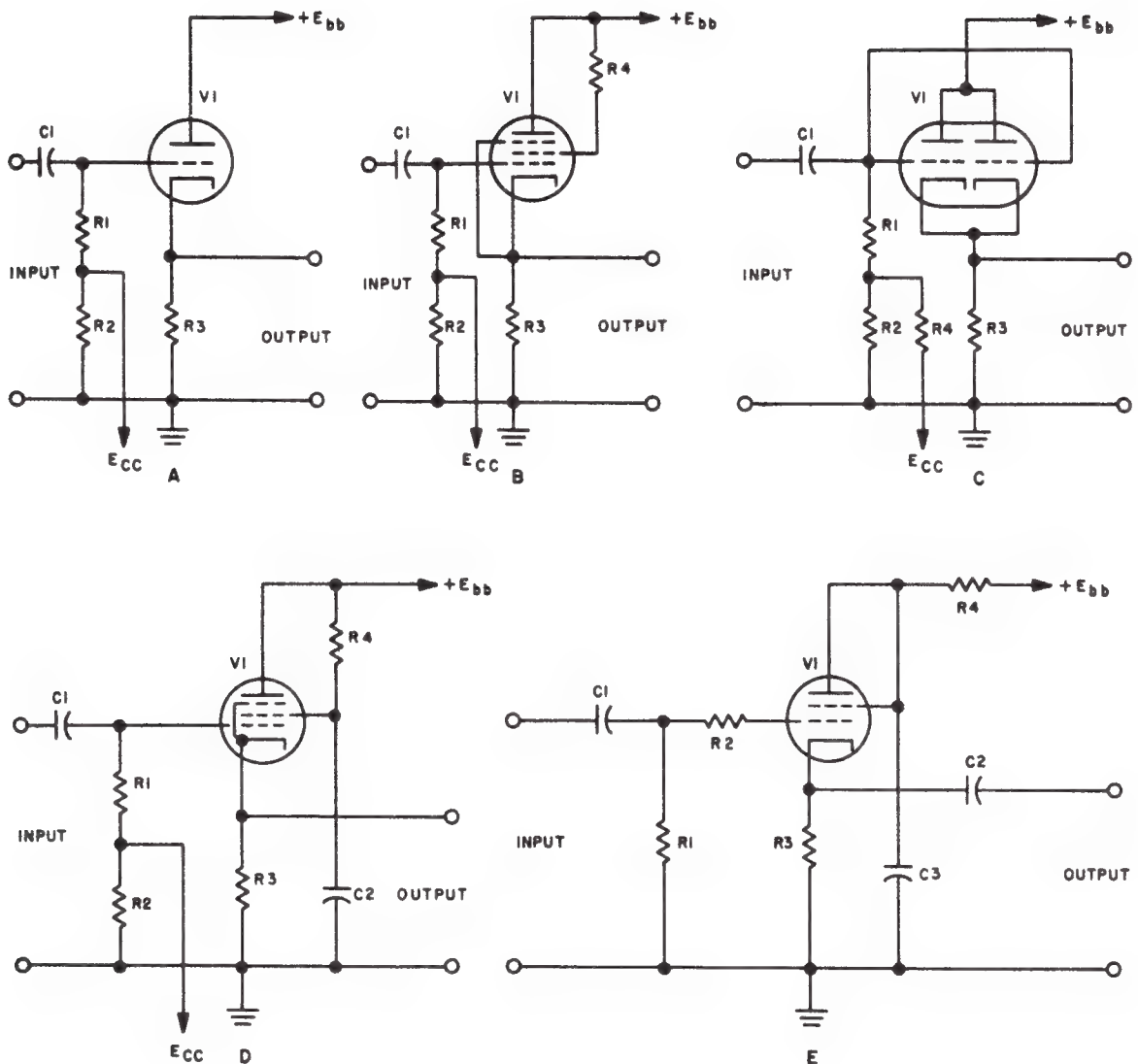

Cathode Follower Circuit Variations

In part B, a triode-connected pentode tube is used, with fixed negative bias applied to the grid in a manner similar to circuit A. Since the power-handling capabilities of pentodes are substantially higher than those of conventional triodes, considerable power output may be obtained from such a circuit. Otherwise, operation of this circuit is generally similar to that of circuit A, with the addition of the screen resistor, R4. This resistor serves to decrease the volt-

age at the screen grid slightly below the plate voltage, in order to keep the screen dissipation within the operating limits of the tube. When certain tubes are used, or when the plate is operated considerably below the maximum rated voltage, this resistor may be omitted. Since no bypass capacitor is used between screen and ground, the plate and screen currents vary with the input signal, and the tube operates as a triode.

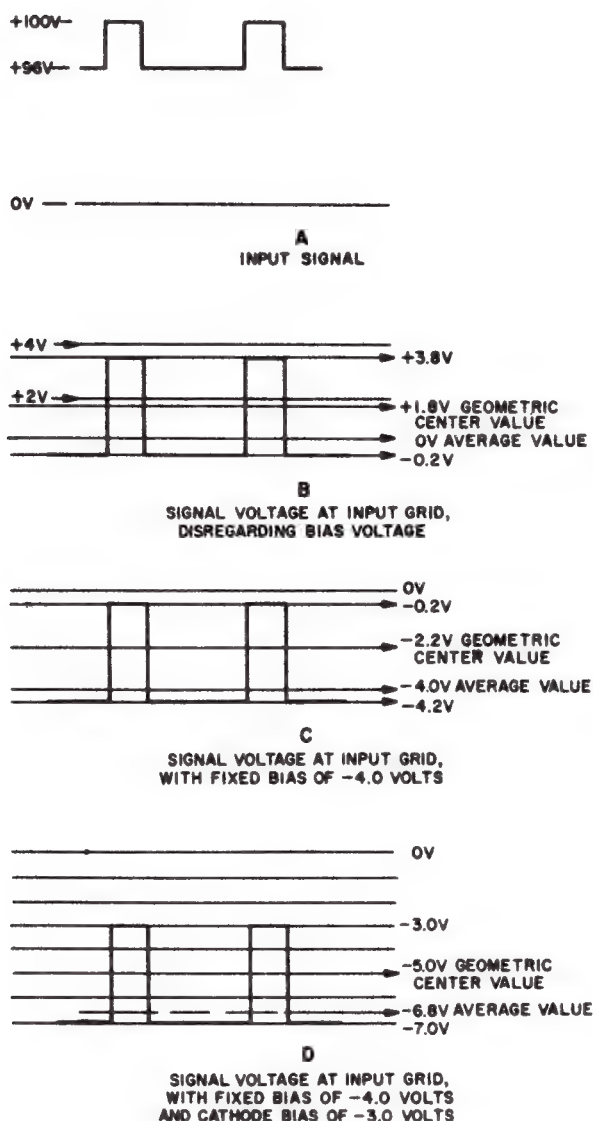

Cathode Follower Input Waveforms

In part C, a twin-triode is used as a cathode follower, with both sections connected directly in parallel. The use of a twin-triode doubles the power output over that of a single tube section, and in addition provides some measure of assurance of continued output, even though reduced in value, in the event of failure of one of the triodes. The operation of this circuit is similar to that of circuit A, with a few exceptions. A fixed negative bias from a power source is applied through resistor R4 to the grids of both triode sections at a tap on the grid resistor

which is composed of R1 and R2. Resistor R4 provides isolation between the grid circuit and the bias voltage supply. The actual bias voltage available at the grid will be somewhat reduced, however, because of the voltage divider effect of R2 and R3. The input signal is applied directly to both grids, which are connected in parallel, although in some cases resistors of low ohmic value, used as parasitic suppressors, are connected between the input and each grid to suppress intermodulation effects between the two tube sections. This effect is a result of slight differences in electrical characteristics, such as cathode emission and transconductance, between the two sections of the tube. The output from the circuit is taken across R3, which is the cathode resistor common to both sections.

In part D, a pentode tube is used. Fixed negative bias is used, as in circuit A. Screen capacitor C2 maintains the dc voltage at the screen relatively constant with variations in input signal. As a result, the power output obtainable across cathode resistor R3 is somewhat greater with this pentode-connected circuit than it is using the triode connection in circuit B.

In part E, a triode-connected tetrode tube is used, although a triode could be connected in an identical manner. In this circuit the grid return is composed of resistors R1 and R2, with R2 providing additional isolation between the input circuit and the tube, and also serving as a grid current limiter. A coupling capacitor, C2, is also employed in the output circuit, to block the dc component when only the ac signal output is desired. Plate supply isolation may be employed, by means of the decoupling filter composed of C3 and R4, which in addition helps to prevent variations in the voltage at the plate and screen during positive peaks of the input signal.

Another variation of the cathode follower circuit may be encountered in some equipments, where the cathode resistor and output coupling capacitor are physically located in another chassis, and are connected by means of interconnecting cables. In order to protect the tube against a possible voltage breakdown between cathode and filament, in the event of an open cathode circuit caused by a disconnected or broken cable, an additional resistor of a substantially higher value of resistance may be employed directly at the cathode connection of the tube. Since this resistor is connected in parallel with the main cathode load resistor, its presence will not affect the output during normal circuit operation.

Failure Analysis.

No Output. If an input signal is being supplied, an open coupling capacitor C1 in the input circuit or an output coupling capacitor, if used, would interrupt the circuit output, as would also an open cathode resistor R3 or a shorted plate capacitor C3. (Refer to Cathode Follower Circuit Variations, circuit E.) Failure of the plate (and screen) power supply, or an open plate decoupling resistor R4, if used, or a defective tube, would also be responsible for a condition of no output.

Reduced or Unstable Output. If a normal input signal is being supplied, a weak or intermittently shorted tube, or leaky input or output coupling capacitors may be the cause of reduced or unstable output. A reduction in the applied plate (and screen) voltage will cause the output to be reduced, while an unstable supply voltage will cause unstable output signal amplitude. A change in grid bias, brought about by a changed value of grid resistors R1 and R2, or of cathode resistor R3, will also affect the output signal, and may distort the signal by biasing the tube nearly to cutoff or to saturation.

LOW-LEVEL VIDEO CATHODE FOLLOWER (ELECTRON TUBE)

Application.

The low-level video cathode follower is used to match the output impedance of a low-level video source, such as a video limiter, to a low-impedance transmission line, without deteriorating the waveform of the video signal.

Characteristics.

Positive output signal is in phase with the positive input signal.

Input impedance is high; no grid current flows within the designed operating range.

Output impedance is low; values shown give an actual output impedance of 100 ohms.

Output voltage gain is less than unity; values shown give an actual gain of approximately 0.5.


Class A output gives undistorted reproduction of input signal within designed operating range.

Circuit Analysis.

General. In the circuit shown in the accompanying illustration, a type 5670 twin-triode is used, with

both sections connected in parallel. Actual values of resistance and capacitance used in this circuit are shown in the illustration; these values govern the input and output limits and the operating level discussed under Circuit Operation. An input capacitor is used in the grid circuit, and the plates are tied directly to the plate supply voltage, $+E_{bb}$. The grids are returned, through grid resistor R1, to a fixed negative bias, $-E_{cc}$, from a voltage divider composed of R2 and R3, which is fed from a $-150V$ bias supply. The output is taken from the paralleled cathodes across cathode resistor R5. Resistor R4 acts as a parasitic suppressor to prevent intermodulation between the two triode sections, due to slight variations between them.

Circuit Operation. This circuit is designed to accept a positive input signal, and reproduce it without distortion in the positive output signal. Under normal operating conditions, the circuit will handle an operating level of 2.2-volt positive input pulses, and produce an output level of approximately 1.0 volt. As a maximum limit, an input signal of 4.2 volts amplitude will produce an output amplitude of 2.0 volts. This output level approaches the grid-current region of the type 5670 tube, and therefore is about the maximum that can be obtained using this tube type. The gain of the circuit is approximately 0.5.

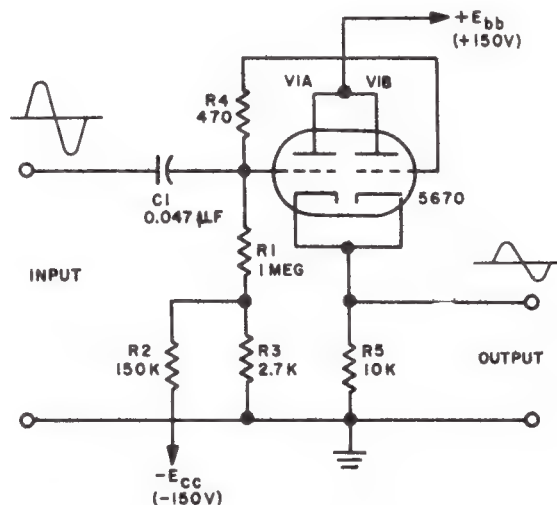

Low-Level Video Cathode Follower Circuit

The input signal is applied through coupling capacitor C1 to the grid of section A of a type 5670 twin-triode, and through suppressor resistor R4 to the

grid of Section B. A fixed value of grid bias is supplied from a negative 150-volt bias supply, to a voltage-divider circuit composed of 150K resistor R2 and 2.7K resistor R3. The junction of the two resistors, at which the voltage is approximately -2.6 volts, furnishes the actual bias to which the grid resistor, R1, is returned. The unbypassed cathode resistor, R5, is common to both triode sections, and the voltage drop appearing across it, which is an exact reproduction of the input signal, constitutes the output of the video cathode follower.

A particular form of distortion of the input signal, known as *droop* or *sag*, is of significance in low-level video cathode followers. Droop is the decay in amplitude, with time, of the flat top portion of a positive square wave input signal. The amount of droop is largely determined by the ratio of the pulse length to the RC time constant of the input coupling circuit. For small values, the percentage of droop is equal to the pulse length divided by the RC time constant:

$$\text{Droop (\%)} = \frac{\text{pulse length (seconds)}}{R_{(\text{OHMS})} \times C_{(\text{FARADS})}}$$

For example, for Values of C1 = .05 μ f and R1 = 1 meg, and a pulse length of 500 μ sec,

$$\text{Droop \%} = \frac{500 \times 10^{-6}}{(1 \times 10^{-6}) \times (.05 \times 10^{-6})} = .01 = 1\%$$

Failure Analysis.

No output. Assuming that a signal of the proper positive value is applied at the input to the video cathode follower, the primary cause of no output may be a defective tube. If the tube is found to be operational, an open coupling capacitor, C1, would interrupt the operation of the circuit. An open resistor R3 in the grid bias voltage-divider circuit would allow the full value of the -150-volt bias voltage to be applied directly to the tube grids, cutting off the tube. Failure of the plate supply voltage would interrupt operation of the circuit, as would also an open-circuited cathode resistor, R5, provided that there is no continuous dc path paralleling R5 in the output circuit.

Reduced or Unstable Output. With a proper positive input signal present at the input to the video

cathode follower, a leaky (partially shorted) grid coupling capacitor, C1, may be responsible for a severely distorted output. This leaky condition, acting as a partial short, would allow any value of dc voltage which is present at the input to be applied to the grid of the tube. This voltage would appear to the tube as a change in grid bias, and shift the operating point on the tube's E_g - I_p characteristic curve into either the cutoff or saturation region. An open grid resistor, R1, may cause the tube to "block", or to "motorboat", or to exhibit no effect other than a distortion of the output waveform. With an open grid resistor the tube may "block" because the grid coupling capacitor, C1, has no readily available discharge path, and may gradually accumulate a negative charge, sufficient to cut off the tube, through grid current on the positive peaks of the input signal. Intermittent conduction of the tube, or "motorboating", may result if leakage through C1 allows C1 to discharge down to the point where the tube is momentarily "unblocked". In some cases of an open grid resistor no immediately discernible symptoms will be evidenced other than a distortion of the output waveform. This may be caused by the grid "floating" at some intermediate value and the input signal continuing to be coupled through by the capacitive voltage divider action of coupling capacitor C1 and the grid to cathode capacitance of the tube. Since the interelectrode capacitance of the tube is very small as compared with the capacitance of C1, most of the input signal will continue to appear across the grid and cathode, and the tube will react in very nearly a normal manner. Should resistor R2 in the voltage divider network be come open-circuited, the fixed negative bias from the -150V power supply would not be applied to the grid. As a result, the input signal may be sufficient to drive the tube to saturation, seriously distorting the output on the positive peaks of the signal. If, on the other hand, resistor R3 became open-circuited, the full value of -150 volts from the bias power supply would be applied to the grid, and the tube would be driven far beyond cutoff. Reduced output may also be traced to an open parasitic suppressor resistor, R4, which would cause one triode section to the tube to be without an applied input signal, reducing the output to half the initial value, with a possibility of distortion on the most positive portion of the input signal due to reduced bias. The reduction in bias would be the result of the "blocked" grid, causing a reduction in current flow

through the common cathode resistor, and hence a lower value of voltage drop across the common cathode resistor. If the cathode resistor should change in value, because of age or overload, the output voltage would be changed accordingly.

PULSE CATHODE FOLLOWER (ELECTRON TUBE)

Application.

The pulse cathode follower is used as an isolation stage between a critical circuit and the circuit which it feeds as a load, while at the same time preventing any loading effects from appearing at the output of the critical circuit. This is accomplished by means of the cathode follower's characteristic of a high input impedance and a low output impedance.

Characteristics.

Output signal is in phase with input signal.

Input impedance is high: no loading effects are reflected at the output of the previous stage.

Output impedance is low: considerable power may be supplied to the output load circuit.

Output voltage regulation is good, due to low output impedance, even through the input signal may have poor voltage regulation due to its high impedance.


Input capacitance is low: approximately 2.5 pf excluding capacitance of circuit wiring.

Rise time response is fast: approximately 0.02 μsec .

Circuit Analysis.

General. In the circuit shown in the accompanying illustration, a single triode section of a typical twin-triode such as a type 5814A, is used. Actual values of resistance and capacitance used in the circuit are determined by the operating characteristics desired, and are therefore not given in the diagram. Typical values used to produce specific operating characteristics, and a discussion of the effects produced, are given under Circuit Operation. An input capacitor, C1, is used in the grid circuit, and the grid is returned to ground through grid resistor R1. Plate voltage is supplied directly from the supply voltage, E_{bb} , and the output is taken across the unbypassed cathode resistor, R2.

Circuit Operation. The pulse cathode follower using an input capacitor (C1) of 0.047 μf and a grid resistor (R1) of 680K, with a type 5814A tube (one triode section), has a very low input capacitance of approximately 2.5 pf, and a fast rise time response of 0.02 μsec . The rise time is in large part dependent upon the transconductance of the tube and its associated interelectrode capacitances. A typical rise time of 0.02 μsec or 0.03 μsec is satisfactory for most radar and other pulse timing applications.

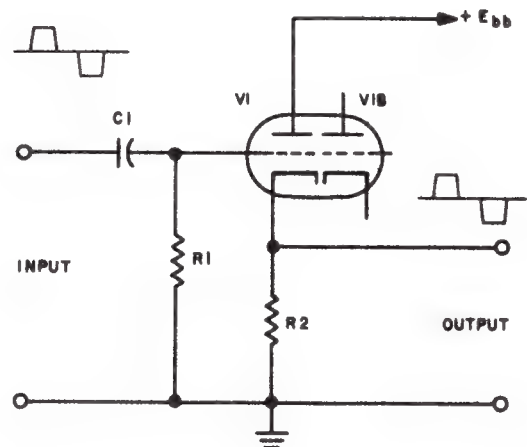


Pulse Cathode Follower Circuit

The transition time of the negative-going edges of pulses, such as the fall time of a positive pulse or the rise time of a negative pulse, is increased by a cathode follower. This transition time depends upon pulse amplitude, while the positive-going edges of pulses are unappreciably affected by pulse amplitude. This is due to the fact that the tube transconductance is of a different value during the fall of the pulse than during the rise of the pulse. The tube is nearer cutoff during the fall of the pulse; transconductance is at a low value and the combination of pulse amplitude, capacitance, and the value of cathode resistor all combine to determine the fall time. The negative transition time may be improved by the use of a negative voltage connected to the cathode resistor, from a negative power supply. If this is done, the tube will draw a higher value of plate current in its quiescent state, compared to a similar tube having its cathode resistor returned to ground. As an alternative, the returned end of the grid resistor may be


connected to a tap on the cathode resistor. Since a higher value of plate current is now drawn by the tube when quiescent, its operating point is appreciably removed from cutoff. The tube's transconductance is hence at a higher value, and the fall time, or negative transition time, is thereby decreased.

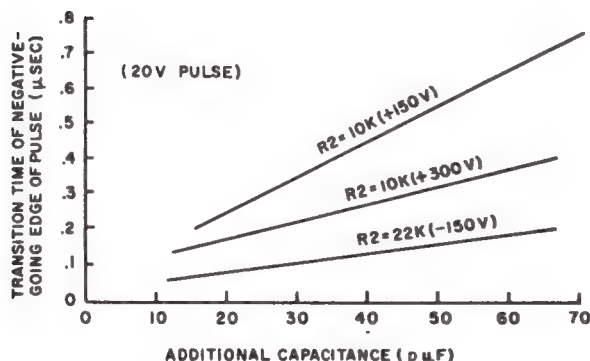Additional capacitance in the output circuit has an effect on the negative transition time, as shown in the following illustration. It can be seen that the capacitance in the output circuit should be kept to a minimum where small values of negative transition time are required.



Effect of Additional Output Circuit Capacitance on Negative Transition Time

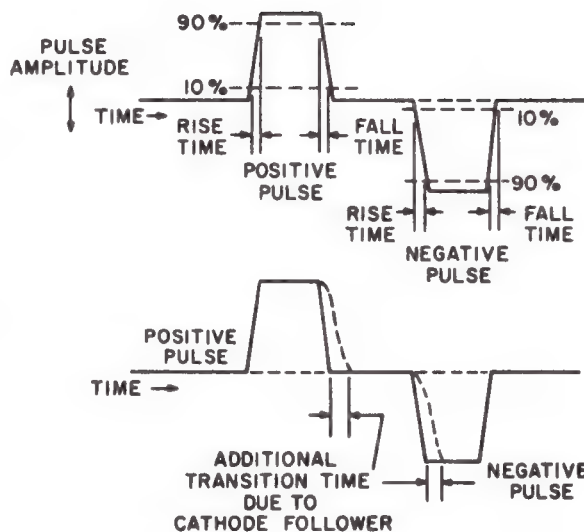The over-all effect of a cathode follower on the transition time of positive and negative pulses, and a visual definition of transition time as applied thereto, may be better understood by referring to the following waveform illustrations.



Effect on Negative-Going Edges of Pulses Due to Cathode Follower

Typical values of gain, input and output limits, output impedance, rise and fall times, for a single triode section of type 5814A twin-triode operated with plate voltages of +150 and +300 volts and cathode resistance of 10K and 22K, are given below.

R_k (ohms)	10K	10K	22K (-150V)
E_{bb} (volts)	150	300	300
Voltage gain	0.87	0.87	0.9
Input limit (volts)	0 to 70	0 to 170	-100 to +180
Output limit (volts)	0 to 61	0 to 148	-90 to +162
Output impedance (ohms) for 20-volt input pulse	300	420	300
Rise time (μ sec)	0.02	0.02	0.02
Fall time (μ sec) for 20-volt input pulse with added 15 pf	0.2	0.15	0.05

The preceding output impedances were measured with a load of such values as to reduce the output voltage to one-half the value of the no-load voltage. The effective output impedance for large values of signal depends upon pulse polarity. As shown above, when a cathode resistance of 22K returned to -150 volts is used, the output impedance is 300 ohms for a positive pulse. For a negative input pulse, however, the output impedance is approximately 1400 ohms. Note the marked improvement in fall time and the increased signal handling capacity gained by returning the cathode-resistor to a negative supply.

Failure Analysis.

No Output. The input circuit should be checked to insure that an input signal is being applied to the pulse cathode follower. The tube should also be checked to insure that it can function properly under normal conditions. If the input signal is present and the tube is good, an open coupling capacitor, C1, would prevent the signal from reaching the tube. If this capacitor were shorted, any value of dc voltage that may be present at the input terminals, from the previous stage, would be applied to the grid of the tube, and would seriously affect its biasing level. Insufficient or no voltage at the plate of the tube, due to failure of the power supply, would obviously result in no output. Another cause may be an open-circuited cathode resistor, R2, assuming that the output circuit has no continuous dc path which could act as a cathode resistor by paralleling R2.

Reduced or Unstable Output. If it has been ascertained that a normal input signal is present at the input to the pulse cathode follower, several conditions could contribute to a faulty output. A leaky coupling capacitor, C1, would effectively lower the input impedance by providing a path of lower resistance in the grid circuit, thus changing the operating characteristics of the tube. Any dc voltage present at the input would appear at the grid, thereby changing the bias. If this voltage is positive and of a sufficient value, the tube may be driven to saturation, resulting in severe distortion of the output signal. An open grid resistor, R1, may cause the tube to "block", or to "motorboat", or to exhibit no effect other than a distortion of the output waveform. (For a more detailed discussion, refer to the Failure Analysis of the Low Level Video Cathode Follower, discussed previously in this section. A change in value of

cathode resistor R2, due to aging and/or excessive current, may be the cause of reduced output. A reduced value of plate voltage, due to partial failure of the power supply or to excessive loading of the supply by some other defective circuit, may also be responsible for a reduced value of output from the pulse cathode follower.

PART 5-5. VIDEO

VIDEO AMPLIFIERS

General. The frequency range covered by the video amplifier is greatly extended over that of the audio amplifier. Video frequencies extend from dc, or a few Hz, to as high as 5 or 6 MHz, depending upon the type of signals. For example, in television applications the picture information requires a uniform bandwidth of from 60 Hz to 4 MHz, whereas in radar applications a band width of from about 30 Hz to 2 MHz is sufficient. In circuits where sawtooths or pulsed waveforms are to be amplified, it is necessary to cover a range of frequencies from about one tenth that of the lowest frequency employed to at least ten times that of the highest frequency. This extended range is necessary because waveshapes which are not sinusoidal contain many harmonics, which must be amplified equally and without any phase delay in order to avoid distortion. The sinusoidal waveform requires only sufficient uniformity of response to pass its second and third harmonics, because any other higher harmonics are of such small amplitude that they can be considered negligible as far as their effect on the shape of the waveform is concerned; on the other hand, the square wave, particularly at the lower frequencies, requires that an infinite number of harmonics be passed for accurate reproduction of the waveshape. In practice, however, it has been found that for square waves, harmonics above the tenth, like those greater than the third for the sinusoidal signal, are actually of negligible amplitude and have little effect on the shape of the final waveform.

Since the video amplifier requires the best possible uniformity of response R-C coupling is used rather than transformer coupling (which has a narrow bandwidth), and cascaded stages are used to supply sufficient gain. This requires that the interstage coupling circuits be modified to obtain the required bandpass, and that inverse feedback be used where possible to flatten out the response. Low-frequency response is improved by using large values of coupling capaci-

tance to lower the series reactance and reduce the voltage drop across the coupling capacitor. The values of the coupling capacitor used between transistor circuits are much higher than the values used between electron-tube circuits (on the order of $10\ \mu\text{f}$). Even so, further compensation is required through partial bypassing of the collector load resistance to improve the low-frequency response and to prevent phase distortion at frequencies lower than 30 Hz. Because the gain is highest at the lower frequencies, it is general practice to reduce the low-frequency gain and boost the high-frequency gain, to obtain uniform response for both low and high frequencies. The high-frequency response is increased by using compensating circuits with inductance in the load circuit. The higher load reactance at the higher video frequencies causes a larger output voltage to be developed (when the output would normally be dropping), and thus extends the frequency response. The series inductance in the load circuit also resonates with the stray (shunt) circuit and transistor capacitance, to produce a high-impedance parallel-resonant circuit which is effective over a large range of frequencies; this is known as *shunt peaking*. Further extension of the response at the highest video frequencies employed is obtained by the use of an additional inductor in series with the coupling capacitor. The series inductor and coupling capacitor form a series-resonant circuit at the very high video frequencies, to boost the response at the upper limits of amplification; this is known as *series peaking*. In the transistor video amplifier, the use of combined shunt- and series-peaking circuits provides the maximum extension of high-frequency response.

In the electron-tube video amplifier, further increase in high-frequency response is obtained by using a lower load resistance than normal and by sacrificing some additional gain. Such compensation is not possible with the transistor video amplifier, however, since maximum gain occurs up to f_{max} , which is the upper limit of usable transistor gain. Above f_{max} the transistor gain drops off to practically nothing, and the transistor no longer amplifies. In the electron tube, however, the gain does not drop off until far past the highest video frequency (actually in the high r-f ranges), so that heavy loading can improve the response. Since the common-emitter circuit produces high gain, cascaded transistor stages can be mismatched so that the low-frequency gain is reduced to equal the high-frequency gain, and still provide uni-

form response with adequate over-all gain. Matching to obtain more gain is usually required only at the transistor cutoff frequency (f_{max}), since excess gain exists at the lower frequencies. Because of the extended frequency range, and since the low-frequency gain and forward amplification vary from transistor to transistor, considerable care is necessary in design to avoid regeneration and circuit instability. Partial bypassing of the emitter resistor is generally used to provide some degeneration and thus stabilize the circuit. Where a number of stages are used, an external negative feedback loop is usually provided to improve the stability and response. However, since the use of external negative feedback is not peculiar to video amplifiers alone (it may be employed in many other circuits), it will not be further discussed in this section.

TRIODE VIDEO AMPLIFIER (ELECTRON TUBE)

Application.

The video amplifier finds extensive use in television circuits, where actual "picture video" signals are amplified; in radar circuits, where wide ranges in frequency must be handled; and in communications where a number of voice-frequency channels are successively "stacked" in frequency, one above the other, to occupy a complete 6-MHz channel.

Characteristics.

Class A operation is utilized to insure an output which is a faithful reproduction of the input signal.

Polarity of output signal is inverted over that of input signal.

Frequency response is broader than that of a standard R-C coupled amplifier.

Input signal may consist of pulses of either positive or negative polarity, or both.

Circuit Analysis.

General. At low frequencies, the gain of an ordinary R-C coupled amplifier decreases rapidly as the frequency decreases, because of the corresponding increase in reactance of the input coupling capacitor with decrease in frequency. The increased reactance causes a greater proportion of the input signal voltage to drop across the capacitor, leaving a smaller proportion of the input signal to appear at the input to the tube, across the grid resistor. In addition, bypassing of the cathode resistor becomes less effective for the same reason, resulting in degenerative effects and

further reducing the gain. This loss of gain at low frequencies may be partially overcome by the use of a larger value of coupling capacitance. If, however, too large a value of coupling capacitance is used, the high-frequency response may be adversely affected.


At high frequencies, the gain of an ordinary R-C coupled amplifier also decreases with an increase in frequency. This is due to the capacitive effects of the wiring, the tube and socket, and interelectrode capacitance itself, all of which effectively add capacitance across the plate load, from the plate of the tube directly to ground. This stray capacitance, C_d , acts as a bypass capacitor in the plate circuit in parallel with the output voltage, bypassing the higher frequencies. As the frequency is further increased the gain continues to fall, eventually reaching a point where the amplifier circuit no longer amplifies.

In order to counteract this action and extend the amplification range in the direction of increasing frequency, the plate load resistance must be decreased. As an approximation, the response may be extended from a given limiting value, such as 10 kHz, to a value ten times as great (1 MHz) by decreasing the value of the plate load resistor in the same proportion, such as from 220K to 22K. However, by so doing, the overall gain of the amplifier, including the middle and lower frequency gain, is considerably reduced. This loss must either be tolerated, if the extended frequency response is required or overcome by using additional stages of amplification.

Circuit Operation. The accompanying schematic illustrates a triode video amplifier circuit. The input signal, composed of video pulses of either positive or negative polarity, is applied to the grid of the triode amplifier through coupling capacitor C1. The grid is returned to ground through grid resistor R1. The combination C1R1 forms an R-C circuit at the input to the tube, and the time constant of this circuit limits the low-frequency response of the amplifier. The time constant must be long, in comparison to the period of the lowest frequency to be amplified. At the middle and high frequencies, the value of C1 is sufficiently large that its reactance is negligible, and the full input voltage appears across grid resistor R1 and is thereby applied to the grid of the tube. But, as the frequency decreases, the reactance of C1 increases according to the formula:

$$X_c \cong \frac{1}{2\pi f C}$$

As a result, the effect of C1 is no longer negligible; its reactance and the resistance of R1 form a voltage divider across which the input voltage is applied. The voltage drop across C1 is lost, for all practical purposes, and only that value which appears across R1 is effective at the grid of the tube. The voltage drop across C1 may be reduced by increasing the capacitance of C1, which will decrease its reactance, but the extent to which C1 can be increased is limited because an increase in physical size results in an increase in stray capacitance. The stray capacitance, in turn, acts in the same manner as a bypass capacitor in the plate circuit, to decrease the gain at the high frequencies.

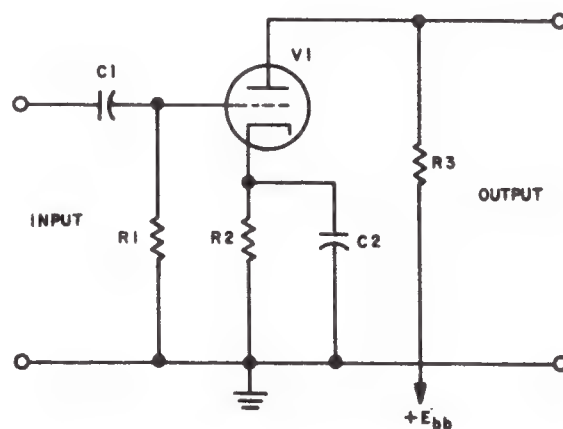


Triode Video Amplifier Circuit

The grid bias, in the triode video amplifier circuit, is obtained by utilizing the voltage drop across resistor R2, connected in series with the cathode of the tube. The total electron current flowing through the tube passes through this resistor. Since the tube current varies with the variations of the applied signal voltage, a corresponding varying voltage is developed across cathode resistor R2. In order to obtain a steady value of grid bias voltage, these signal variations must be bypassed around the bias resistor by means of a filter capacitor, which is the cathode bypass capacitor C2. The reactance of this capacitor must be low, in order to provide a low-impedance path around the resistor for the alternating current components of the signal. This capacitor must have a value of 5 microfarads or greater for audio-frequency amplifiers. For video-frequency amplifiers, which may be required to pass frequencies much lower in

value, the capacitance of the cathode capacitor C_2 must, in many cases, be much greater, such as 100 microfarads or more. As a general rule, the time constant of R_2 and C_2 must be long in comparison to the period of the lowest frequency to be passed by the video amplifier. In order to provide effective bypassing for the ac components of the signal around the cathode resistor, the value of capacitive reactance at the lowest frequency to be amplified is generally accepted to be one-tenth (or less) the resistance value of R_2 .

The value of plate load resistor R_3 has a controlling effect, not only on the gain of the amplifier, but on its frequency response as well. The gain increases with higher values of plate load resistance, but the bandpass of the circuit becomes less. Conversely, lower values of plate load resistance will decrease the gain of the amplifier, but will extend its frequency response. This is illustrated in the following diagram.

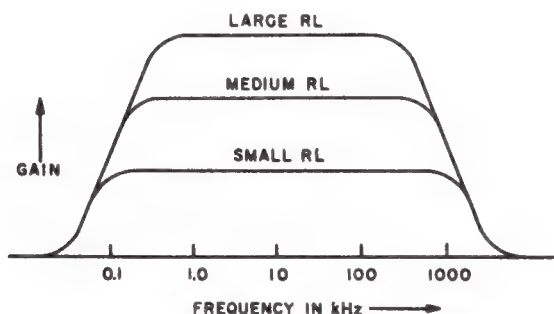


Effect of Value of R_L on Video Amplifier Bandpass

The value of the plate load resistor may be decreased down to approximately 1.5K in some applications. Further extensions of the frequency range require the use of high-frequency and low-frequency compensating networks.

Stray (or distributed) capacitance, due to the capacitance of the circuit wiring and the interelectrode capacitance of the tube, is a cause of poor high-frequency response, and, therefore, distortion. The distortion of the output waveform, as a result of poor high-frequency response, is shown in part C of the following illustration, while the input waveform and the ideal output waveform are shown in parts A and B, respectively. If the parallel combination of the plate resistor, R_3 , and grid resistor R_g of the following stage allows the stray capacitance, C_d , to

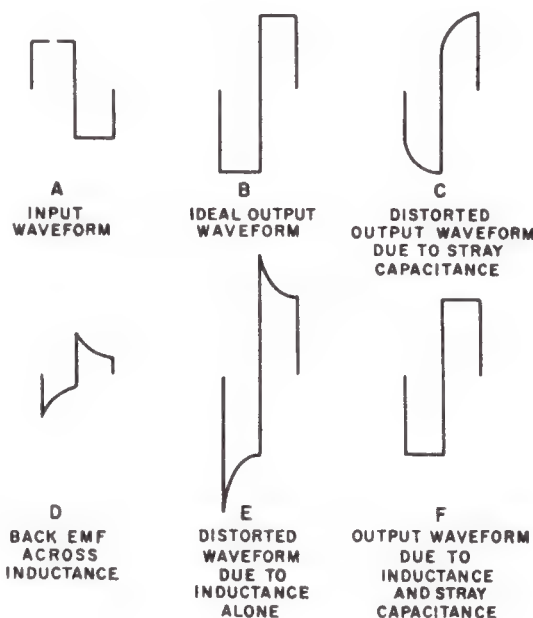charge and discharge quickly, the output will show little or no distortion. If, however, R_3 and R_g are large values of resistance, C_d will require a relatively long time to charge or discharge, and the steep sides of an applied square wave will be distorted, as shown in part C of the illustration.



Intercircuit Waveforms


This condition may be overcome in one of two ways. The first is to reduce the size of C_d by using special amplifier tubes with low values of input and output capacitance between the lead wires and ground. The second is to decrease the time required by C_d to charge or discharge. This can be accomplished by reducing the value of R_3 or R_g . If R_g is reduced, however, the low-frequency response will suffer. If R_3 is reduced, the gain of the stage will be reduced in turn, but this may be overcome by using additional stages of amplification.

The decreased response at high frequencies is caused principally by the shunting effect of the distributed capacitance of the circuit and the interelectrode capacitance of the tube, which together act to reduce the impedance of the plate load. This effect may be compensated for, and the high-frequency range may be extended, by the addition of a small


value of inductance, L_1 , in series with plate resistor R_3 , as shown in part A of the following illustration. This inductance serves to boost the response of the high frequencies, while having practically no effect upon the lower frequencies. The boost in response at high frequencies is due to the high inductive reactance of the inductance, L_1 , which produces a back EMF, resulting in a sharp peak at high frequencies, as shown in D and E of the illustration. This sharp peak, or introduced distortion, will counteract that caused by the stray capacitance, and the resultant output will be almost a pure square wave as shown in F. At low frequencies, the inductive reactance of the inductance is low, and has negligible effect on the circuit. This method, known as shunt compensation, is

effective when the maximum-frequency limit is not too high, and there are only a few stages of amplification.


Another method of compensating for this effect, known as series compensation, is shown in part B of the following illustration. In this method, a small value of inductance, L_2 , is connected in series between the plate and the output to the following stage. This small inductance resonates with the input capacitance of the following stage at high frequencies, and acts to cancel the shunting effect of the input capacitance by the increased impedance of the series resonant circuit. This results in an increased voltage at the input to the following stage, and, therefore, an increase in gain.

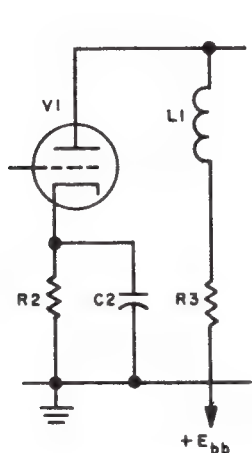

A. SHUNT COMPENSATION

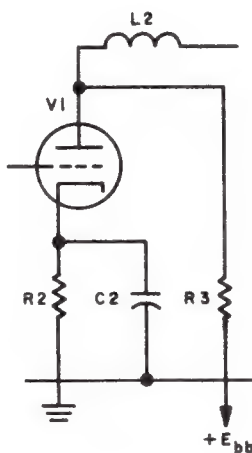

B. SERIES COMPENSATION

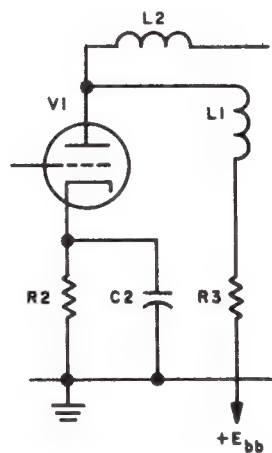

C. SERIES-SHUNT COMPENSATION

Triode Video Amplifier Frequency Compensation Circuits

The advantages of both of the above methods may be combined in a single circuit. This circuit, known as series-shunt compensation, is shown in part C above. This combined method utilizes both the inductance L_1 in series with plate resistor R_3 and the inductance L_2 in series with the plate and the output. The combination gives the high-frequency peaking effect of the shunt-compensation circuit along with the increase in gain at high frequencies due to the resonant effect of the series-compensation circuit.


The decreased response at low frequencies is caused principally by the increased reactance of the input coupling capacitor, which reaches an appreciable

value as the frequency decreases below 200 Hz. This decreased response, or loss of gain, can be counteracted by the addition of a low-frequency compensation network, or filter, in series with the load resistor. This compensation network consists of a capacitor, C_3 , and a resistor, R_4 , connected into a filter circuit as shown in the following schematic. The filter, connected in series with plate load resistor R_3 , accomplishes two purposes:

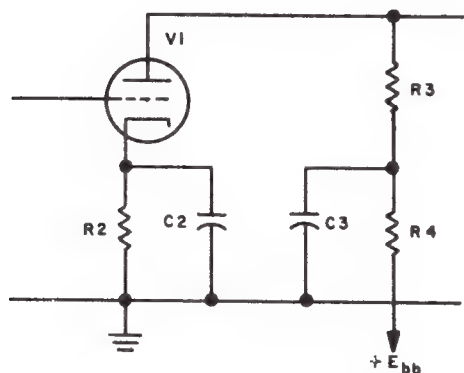
- (1) It introduces a phase shift into the plate circuit which compensates for the phase shift in the output coupling circuit.
- (2) It increases the effective plate

load impedance at low frequencies, and thereby maintains the low-frequency gain. This is explained as follows: At low frequencies R_4 plus R_3 make up the plate load of the circuit. The addition of R_4 will increase the gain of the circuit, and the low-frequency response. The capacitive reactance of C_3 will be high, thereby preventing any shunting effect. At high frequencies the reactance of C_3 is lower, causing the signal to be shunted around R_4 , effectively removing R_4 from the circuit. In this manner the plate load becomes lower at high frequencies, and the high-frequency response will not suffer.

Frequency response is an important consideration in video amplifiers, but it is not the only one. Phase distortion, which can be tolerated in an audio amplifier, is capable of destroying the image on a cathode-ray-tube screen. Phase distortion is produced when the time or angular relationship of electric waves to each other changes as they pass through any electrical system. As an example, consider the wave shown in part B of the following figure.



Low-Frequency Compensation Circuit

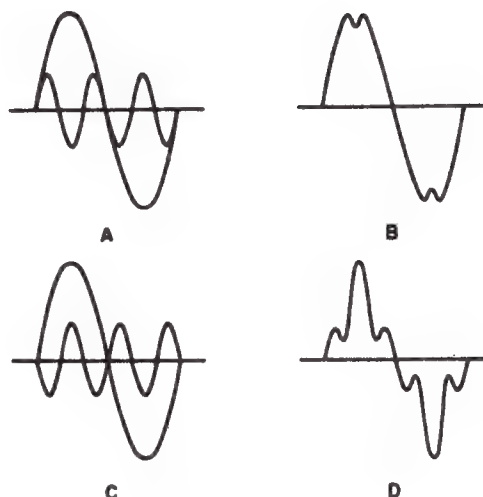


Composite Waveforms of
Fundamental Plus Third Harmonic

This wave is actually composed of a fundamental frequency in combination with its third harmonic, as shown in part A of the illustration. If the effect of the circuit on each of these two waves is different, the two waves may appear as in part C of the illustration, where the third harmonic has changed its position with respect to the fundamental. That is, its phase relationship has changed. The resultant of these two waves will now assume the shape given in part D of the illustration, which is certainly different from the original waveform shown in part B.

At low frequencies, the phase of the voltage at the grid of the amplifier is governed by the amount of opposition offered by the coupling capacitor to the ac waveform passing through the circuit. The coupling capacitor and grid resistor are, in effect, a series circuit. As the applied signal becomes lower and

lower in frequency, the ever-increasing capacitive reactance causes the circuit current to lead the applied (signal) voltage in ever-increasing amounts approaching 90 degrees. The voltage drop across the grid resistor is in phase with the current through it, and would also lead the applied voltage by the same amount. In the middle range of frequencies, from 200 to 2000 Hz, the capacitive reactance of the coupling capacitor becomes small enough with respect to the reactance (resistance) of the grid resistor to have a minimal effect on the passing waveform; therefore, phase shift can be considered negligible in the middle-frequency range. At the high-frequency end of the band, the input capacitance between the grid and the cathode becomes important and must be considered. The input capacitance and the grid resistor form, in effect, a parallel circuit. As the capacitive reactance of the input capacitance becomes less and less with increasing frequency, the current in the parallel combination will become more and more capacitive and will begin to lead the applied voltage by ever-increasing amounts approaching 90 degrees. Another way of expressing this thought is that the voltage across the parallel combination will begin to lag by ever-increasing amounts as the applied frequency is increased. The shift in phase angle at the grid of the tube is opposite to that caused at the low frequencies, but in either case the result is the same: phase distortion. An illustration of the relationship between phase distortion and frequency response in an ordinary amplifier is given in the following figure.

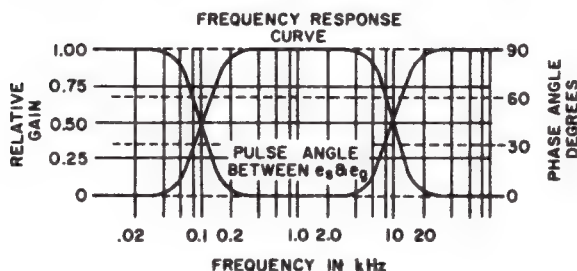The high-frequency and low-frequency compensating networks previously described, in addition to compensating for frequency response, help to correct for phase distortion, as they shift the phase back in an opposite direction to make the circuit appear resistive over a wider frequency range.



Phase Distortion and Frequency Response Characteristics of an Ordinary Amplifier Stage

Failure Analysis.

No Output. With a video signal of sufficient amplitude applied at the input to the video amplifier, a defective tube is the primary cause of no output in the majority of cases. If the tube is found to be operational, an open coupling capacitor C1 would prevent an input signal from reaching the video amplifier grid. An open cathode resistor R2 would interrupt the operation of the circuit, resulting in no output. If a compensation circuit is employed in the plate circuit, a shorted capacitor C3 would prevent the application of plate voltage to the tube, and would probably burn out plate resistor R4. (Refer to Low-Frequency Compensation Circuit diagram.) Failure of the plate supply voltage would interrupt circuit operation in the same manner. Application of plate voltage to the tube would also be interrupted if plate resistors R3 or R4 became open-circuited, again resulting in no output.

Reduced or Unstable Output. Assuming that a video signal of proper amplitude is present at the input to the video amplifier, a partially or completely shorted grid coupling capacitor C1 may be the cause of a reduced or severely distorted output. If the capacitor is partially shorted, any value of a dc voltage which may be present at the input terminals of the circuit would be applied to the grid of the tube. Appearing to the tube as a change in grid bias, this voltage, if positive, may shift the operating point of the tube toward or into the saturation region, causing severe distortion by limiting the positive peaks of the input signal. If grid resistor R1 became open-circuited, grid blocking would result from the accumulation of charges due to the signal voltages on the grid, which could not return to ground. Should cathode capacitor C2 become shorted, the cathode bias would be removed, and the cathode would operate at a fixed ground potential. This would change the operating point on the tube's E_g - I_p characteristic curve, allowing more plate current to flow, and probably operate into the saturation region, with the consequent severe distortion in the output signal. If, on the other hand, cathode capacitor C2 became open-circuited, the cathode voltage would rise and fall with the grid input signal in cathode follower fashion. This would introduce degeneration, which would result in a reduced value of output signal. If the video amplifier circuit contains low-frequency compensation, and capacitor C3 in the compensation network became open-circuited, the compensation characteristics

would be lost, and distortion might result, although this distortion might not be very noticeable.

PENTODE VIDEO AMPLIFIER

Application.

The pentode video amplifier is used to amplify, without attenuation, a band of frequencies between approximately 10 Hz and 6 MHz. This amplifier is normally used to amplify a higher level of input signal than the triode video amplifier, and as a result it can furnish an output signal of considerably higher power than may be realized from a triode amplifier. The pentode video amplifier is used in television and communications applications, and in particular in radar receivers, where it often follows the detector stage.

Characteristics.

Operated as a Class A amplifier to obtain an output signal which reproduces the input signal without distortion.

Output signal is of reverse polarity to that of the input signal.

Input signal may be continuous or pulsed, and of either positive or negative polarity, or both.

Frequency response is more linear throughout the operating range than that of a triode video amplifier.

Over-all gain per stage is higher than that of a triode video amplifier.

Output voltage is higher than that of a triode video amplifier when operated from the same supply voltage as a triode.

Harmonic distortion is less, for the same output voltage, than that of a triode.

Circuit Analysis.

General. Pentode video amplifiers may be classified in four circuit variations, according to the type of bias and the type of screen supply. The bias may be either zero-bias or self-bias, while the screen supply may utilize either a screen resistor or a fixed value of screen voltage. The basic circuits for each of these variations are shown in the accompanying illustration.

The pentode video amplifier has higher plate efficiency and greater power sensitivity than a triode video amplifier, as a general rule, but at the same time it suffers higher odd-harmonic distortion. In order to reduce this type of distortion to a minimum, negative

or degenerative feedback may be used. However, this reduces the over-all gain of the amplifier. The output circuit usually utilizes resistance coupling or resistance-capacitance coupling, although in some applications transformer coupling or inductance-capacitance (choke) coupling may be used. When resistance coupling (or resistance-capacitance coupling) is used, the load resistance for maximum power output is usually within 10 percent of the value obtained by the formula:


$$R_L \approx \frac{0.9 E_{bb}}{I_p}$$

where:


R_L = plate load resistance
 E_{bb} = plate supply voltage (on the source side of R_L)
 I_p = plate current

The power output is less than the value $E_{bb}I_p/2$, because of the power loss in plate resistor R_L . Plate efficiency, for a total harmonic distortion of less than 10 percent, is approximately $35 \pm 7\%$. The overall output circuit efficiency is lower than this value, since the output efficiency is a function of both the plate current and the screen current, and the screen current is wasted insofar as the output is concerned.


Circuit Operation. The following schematics illustrate four basic circuit variations of the pentode video amplifier. In circuit A, the tube is operated at zero bias, with the cathode grounded, and the screen voltage is supplied through screen resistor R_2 , which is bypassed by capacitor C_2 . In circuit B, the tube is operated at zero bias, but the screen is held at a fixed voltage through a direct connection to the screen power supply. In circuit C, the tube is operated with cathode bias obtained through the use of cathode resistor R_2 , which is left unbypassed to provide degeneration, in order to improve the over-all frequency response. The screen voltage is supplied through screen resistor R_3 , which is bypassed by capacitor C_2 . In circuit D, the tube is operated with cathode bias by means of cathode resistor R_2 , which is left unbypassed to provide degeneration. Inductor L_1 is connected in series with plate-load resistor R_3 . Inductor L_1 and resistor R_3 act to extend the response to the higher frequencies.

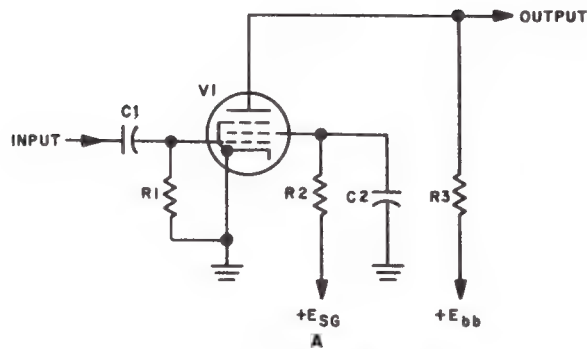


ZERO BIAS, SCREEN RESISTOR

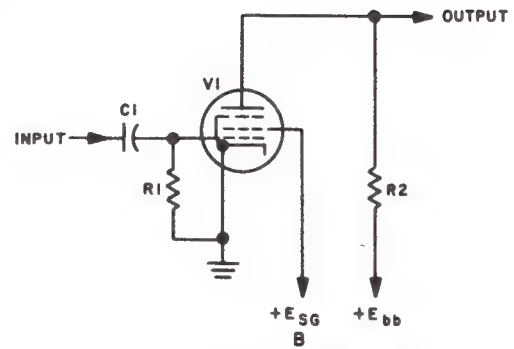

ZERO BIAS, FIXED SCREEN

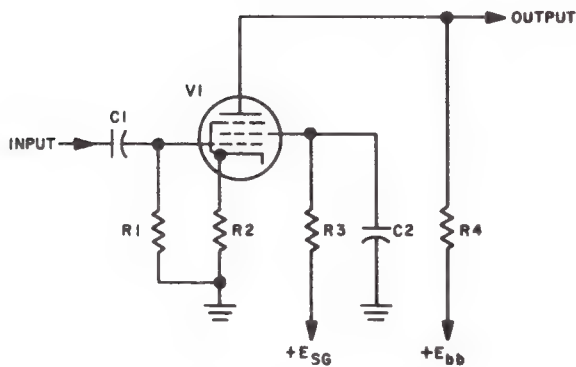

CATHODE BIAS, SCREEN RESISTOR

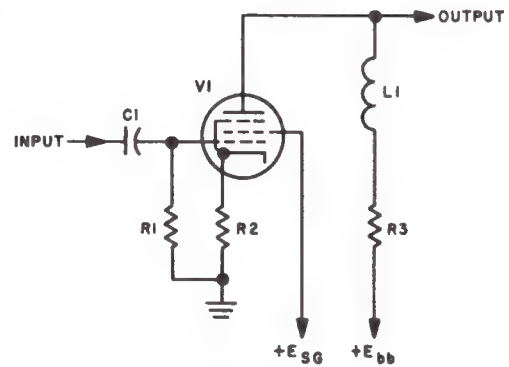

CATHODE BIAS, FIXED SCREEN

Pentode Video Amplifier Basic Circuit Variations

In circuit A, the pentode is operated at zero bias, since no cathode resistor is used, and the grid is returned to the grounded cathode through grid resistor R1. Cathode circuit degeneration at low frequencies, and the resultant loss of gain, is thereby eliminated. This loss of low-frequency gain is evident in circuits using cathode bias, with a bypass capacitor shunting the cathode resistor, because of the increasingly higher capacitive reactance offered by the bypass capacitor as the frequency is decreased below a few hundred Hz. The disadvantage of zero bias, however, is the limitation imposed on the input signal, in that the input signal must not be so great as to drive the grid to saturation and the condition of grid current flow. The screen voltage is supplied, from the power supply, through screen resistor R2, in order to operate the tube at the proper screen potential, which under normal conditions is of a lower value than the

plate voltage. The screen resistor is usually bypassed by a screen capacitor, C2. The R-C circuit which results from the combination of R2 and C2 provides a small amount of degeneration similar to that provided by an unbypassed cathode resistor. Since the normal screen current is only a small percentage of the plate current (10 to 15 percent), the amount of degeneration is proportionally smaller. The degeneration approaches a negligible value when the time constant of the R-C circuit, R2 and C2, is greater than four times that of the lowest frequency which is to be passed by the amplifier.

In circuit B, the pentode is operated at zero bias, similar to that of circuit A. The screen, however, is supplied directly from the power supply, without the use of a screen dropping resistor. By this means the screen voltage is held to a practically constant value, assuming that the impedance of the power supply is


of a relatively low value. As a result, no degeneration is provided by the screen circuit, and the voltage gain of this circuit is slightly higher than that of circuit A.

In circuit C, the pentode is operated with cathode bias, the amount of which is determined by the values of the cathode resistor and the plate and screen currents. The cathode resistor is left unbypassed, in order to provide degeneration, which increases the over-all frequency response of the amplifier and reduces the distortion and/or noise which may be introduced within the amplifier itself. In a number of amplifier circuits, including those designed for audio frequencies, the cathode resistor is bypassed by a capacitor of a relatively large value. The capacitor acts as an extremely low impedance path for all frequencies higher than approximately 200 Hz. As the frequency of the signal to be amplified decreases below this value, the reactance offered by the bypass capacitor increases very rapidly, and as a result the gain at lower frequencies decreases. In order to avoid this decrease in gain in the video amplifier, this bypass capacitor is omitted from the circuit. The gain at the low frequencies is thereby held to approximately the same value as the gain at the medium frequencies, but the over-all gain of the circuit - at all frequencies - suffers a decrease in value, because of the degeneration introduced by the cathode resistor. The screen voltage is dropped, from the power supply potential, through screen resistor R3 to the proper value for pentode operation. The effect of the screen

resistor-capacitor combination is similar to that described for circuit A.

In circuit D, the pentode is operated with cathode bias, in a manner similar to that of circuit C. The screen is supplied by a fixed potential directly from the power supply, and no screen resistor is used. Degeneration due to the screen circuit is thereby avoided, as in circuit B. In this plate circuit, in series with plate load resistor R3. This comprises a shunt peaking circuit, which acts to keep the response flat to a much higher frequency than may be obtained with a simple resistive plate load. A more complete discussion of compensation circuits, including shunt peaking, is given in connection with the triode video amplifier, previously described.

A practical application of some of the circuit variations already discussed is given in the following illustration, which shows the pentode video amplifier circuit used in the AN/SPS-10D Radar Set. In this circuit, the video input signal is applied through coupling capacitor C1 to the grid, which is returned to ground through grid resistor R1. The amplifier tube, a type 6AU6, is operated with cathode bias obtained by means of cathode resistor R2. Partial bypassing is provided by capacitor C2, which, because of its low value of capacitance (130 pf), offers a low impedance only to the higher frequencies. The screen grid is held at a relatively fixed potential from the power supply, through the voltage divider R3 and R4 and its filter.

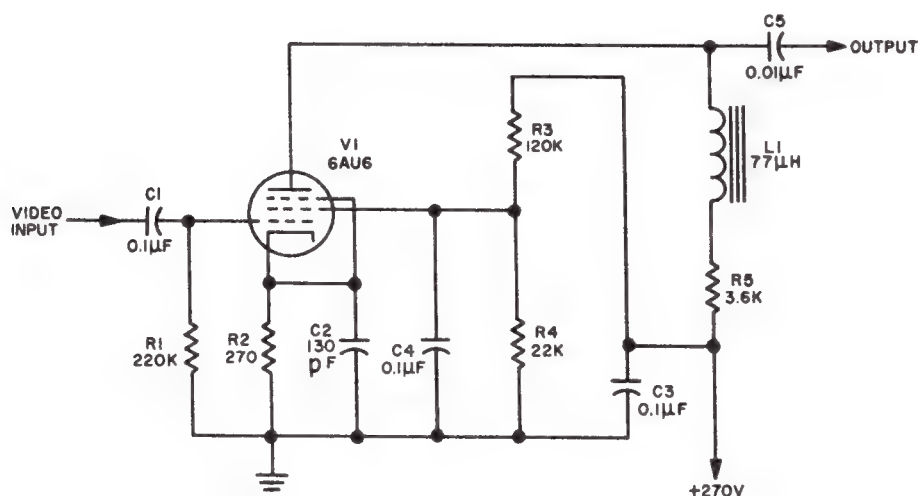

Pentode Video Amplifier Circuit Used in AN/SPS-10D Radar Set

network C3 and C4. In this case, the R-C circuit consisting of R4 and C4 provides negligible screen degeneration, because the junction of R4 and R3 is held at a relatively constant potential by voltage-divider action. A shunt peaking compensation circuit is provided in the plate circuit, by means of inductance L1 in series with plate-load resistor R5. The use of plate shunt peaking maintains the output response flat to a much higher frequency than possible without its use. The output of the video amplifier is taken through C5, the output coupling capacitor.

Failure Analysis.

No Output. Assuming that a signal of sufficient amplitude and proper polarity is applied at the input to the pentode video amplifier and no output is obtained, the tube should be checked for proper operation. An open coupling capacitor C1 or an open cathode resistor, if used, would interrupt the operation of the circuit. An open plate resistor or screen resistor, if used, or failure of the plate or screen power supply would likewise be a cause of no output. If shunt peaking is used in the plate circuit, an open-circuited inductance L1 would interrupt the plate current and result in no output.

Reduced or Unstable Output. With a video signal of proper amplitude and polarity present at the input to the pentode video amplifier, a leaky or shorted input coupling capacitor C1 may be the cause of a reduced or unstable output. A leaky capacitor may allow a dc voltage from the output of the previous stage to be present on the input grid; this would change the value of bias and cause distortion in the output signal, or reduce the output to a low value or even to zero. An open grid resistor R1 would probably cause grid blocking, or audio oscillation at a slow rate. If the cathode bypass capacitor C2 became open-circuited, if one is used, degeneration would be introduced and the output would be considerably reduced in value. If the capacitor became shorted, the cathode would operate at zero bias, and the output would probably be distorted although of a higher value. Should the screen bypass capacitor become shorted, the output would be reduced to an extremely low value, and in addition the screen resistor would probably overheat or burn out, because of excessive current flow. Another cause of reduced output may be traced to a reduced value of plate or screen voltage, due to a faulty power supply. If a

voltage divider is used in the screen voltage supply, similar to that shown in the illustration of the AN/SPS-10D video amplifier circuit, an open resistor at the ground end of the voltage divider would increase the voltage at the screen. This would probably increase the plate current sufficiently to overload or burn out the tube. In either case, the output signal would be severely distorted.

TRIODE VIDEO DRIVER AMPLIFIER (ELECTRON TUBE)

Application.

The video driver amplifier is used to amplify radar or other video signals to the proper level for driving the cathode-ray indicator tube.

Characteristics.

A negative output signal is provided for application to the CRT cathode.

Cathode bias is used, in combination with a fixed negative bias on the grid.

A positive video-input signal is required.

The cathode is partially bypassed at high video frequencies to provide gain stabilization and high-frequency compensation.

The tube elements are connected in parallel to provide increased transconductance.

Shunt or series peaking is not required.

Dc restoration is provided by a separate diode.


Low coupling resistance provides improved frequency response.

Circuit Analysis.

General. A negative video output provides some definite advantages over a positive video output. Since the tube is necessarily biased near cutoff, the quiescent or resting current is much lower than would be required for positive video. As a result, the maximum tube rating for plate dissipation is seldom reached even when the tube is over-driven. By using a dual-triode with low coupling resistance, more gain can be obtained for a given bandwidth than from a single pentode stage. By connecting the triode elements in parallel, the theoretical transconductance is doubled; however, full advantage cannot be taken of this circuit arrangement, because a low value of loading resistance is employed in order to widen the bandwidth. Since the capacitances of both tube elements are in parallel, the effective input capacitance

and output capacitance are greater. The triode driver stage is usually the final (output) stage in a video amplifier chain. This stage always drives the cathode-ray indicator tube, which requires a large voltage drive for intensity modulation of the CRT beam (little power is required); therefore, it is usually spoken of as a "video-driver stage" rather than a "video power-output stage".

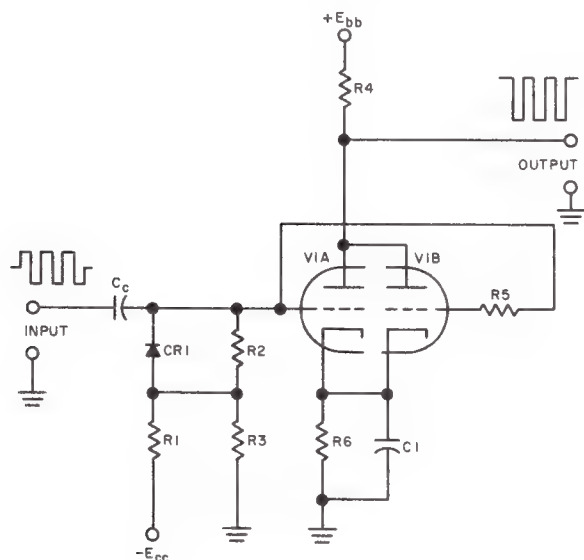Circuit Operation. The accompanying schematic shows a typical dual-triode video driver. The negative output of the driver is usually applied to the cathode of the indicator tube to reduce the cathode bias and illuminate the tube with full beam intensity at the negative peak of the output signal (which occurs at the positive peak of the input signal).



Triode Video-Driver Circuit

Capacitor C_c is the input coupling capacitor; the output of the stage is usually direct-coupled to the CRT cathode. Fixed negative bias is obtained from a voltage divider, consisting of $R1$ and $R3$, to supply a few volts of negative bias to the dual-triode grids through common grid resistor $R2$. Grid resistor $R5$, in series with the grid of $V1B$, is a parasitic suppressor, or "grid stopper", which prevents high-frequency oscillations due to the parallel connection of elements. Diode $CR1$ is a dc restorer which operates as a

biased clamp on the input signal, so that the output signal always produces the same intensity on the CRT for identical input signals. Cathode bias is also supplied by $R6$, which is bypassed by $C1$ so that cathode degeneration occurs, improving the frequency response; thus, special video-frequency compensating circuits are not needed in the plate circuit. A positive input pulse produces an amplified negative output pulse across plate load $R4$.

With no signal applied, the fixed bias prevails and holds both half-sections of $V1$ near cutoff. (The total quiescent current flow is on the order of 0.5 to 1 milliamperes.) The output voltage is zero, and practically the full plate voltage is applied, since the drop across load resistor $R4$ is less than 2 volts. Similarly, the cathode bias developed for the quiescent value of current is only a small fraction of a volt, and thus has practically no effect on the circuit at this time.

Assume that a positive-going video signal is applied through coupling capacitor C_c . The positive input voltage reduces the fixed negative bias, thus increasing the plate current flow. The increased flow of plate current produces a voltage drop across plate load resistor $R4$ and cathode resistor $R6$. The plate voltage drop appears in the output as a negative and amplified output voltage, while the cathode voltage increases the applied fixed bias. Thus, as the amplitude of the input signal increases, the cathode bias also increases, and the effective bias is the total of both the fixed negative bias and the instantaneous cathode bias. The use of combined bias in this fashion provides a more linear input-versus-output voltage relationship. Normally, adequate cathode bypassing prevents instantaneous changes in bias from producing degenerative voltages which oppose the effect of the input voltage. In this circuit, however, the value of the cathode bypass capacitor is selected to be sufficient only for the very high frequencies—not for medium and low frequencies. Thus, at high video frequencies the average cathode voltage remains constant, while at the lower frequencies the instantaneously developed cathode voltage opposes the input signal and reduces its amplitude. As the frequency becomes lower, the reduction is correspondingly greater. Thus, cathode degeneration assumes the form of inverse feedback and attenuates those frequencies which are normally amplified the most. The over-all result is to produce a wider and more uniform band-pass with a slight reduction in gain.

When the video input signal swings in the negative direction, the signal adds to the bias and reduces plate current flow. The voltage drop across the plate load resistor is correspondingly reduced, and the output voltage rises toward zero. The negative-going input signal eventually reaches the fixed bias level, at which time the circuit is again in the quiescent condition. If the negative input signal drops below the bias level, the cathode of clamping diode CR1 becomes negative with respect to the anode and the diode conducts, shunting the signal around grid resistor R2 so that no further reduction in output voltage can occur. The diode conducts until the input voltage equals or becomes more positive than the bias; during this time the output remains at the zero level. When the input signal again goes positive, plate current again flows, producing a voltage drop across R4 and a negative output.

By using a fixed negative bias of the proper value, the tube operates in the Class A1 region and the zero output level is fixed to be almost that of the plate supply voltage. Thus, full advantage can be taken of the large supply swing available; that is sufficient voltage drive can be obtained from a single driver stage without using excessively high plate voltage or large values of quiescent current, as would be required in Class A operation, so that more output voltage is obtained for the same input signal. With the input signal operating on a low duty cycle and consisting of short-duration pulses, the amplitude is usually less than the bias level and the clamping diode will not operate. However, with large input signals greater than the bias level, and operating on a high duty cycle, the clamping diode will operate and hold the output at the same zero level. By properly selecting the value of the cathode bypass capacitor, sufficient cathode degeneration is produced to reduce the rise time to the same value as would normally occur in a properly bypassed driver cathode circuit with shunt peaking employed in the plate circuit. This eliminates the necessity of providing compensating inductance in the plate load, and avoids any adverse affect on the transient response of the amplifier. When properly designed, this circuit will produce a rise time of less than .05 microsecond without excessive overshoot and undershoot.

Failure Analysis.

No Output. Lack of an input signal, improper bias, loss of plate voltage, a defective tube, or an open

cathode circuit can result in no output. If coupling capacitor C_c is open, no signal will appear at the grid and there will be no plate output. Check for an input signal with an oscilloscope or a VTVM. If bias divider resistor R3 is open, full supply bias will be applied to the grid; thus, the tube will be biased far beyond cutoff and will not operate. If R3 is open, the voltage measured from R3 to ground will be the same as the bias supply voltage. If grid resistor R2 is open, no bias will be applied to the V1 grid and the tube will conduct heavily, with cathode bias from R6 biasing it near cutoff. In this case, with very large drive there is a possibility that a small output will be obtained. Ordinarily, however, this output will probably be so small as to be considered no output at all. If bias divider R1 is open, a similar result will occur because of a lack of fixed bias on the grid; if it is shorted, the full bias supply voltage will appear on the grid, thus cutting off the plate current and the output. Use a voltmeter to determine whether the bias appears and, if so, whether it is normal. If cathode resistor R6 is open, the circuit will be incomplete (open) and no output will occur. If R6 is open, shunting the cathode to ground will produce an output, in which case R6 should be checked with an ohmmeter with the power off. (With the power on and R6 open, the voltmeter may act as a high-value return resistor and cause the stage to be biased off; or when used as an ohmmeter and properly polarized the batteries in the meter can furnish an almost normal bias to V1 cathode and cause an erroneous indication.)

If plate resistor R4 is open, no plate voltage will be applied and no output will be obtained. Check the supply, first with a voltmeter to determine that voltage is present, and then check the plate voltage to ground. If plate voltage is normal, and no output can be obtained with proper bias and input signal, V1 is probably defective.

Low Output. Improper bias, low plate voltage, or a defective tube can cause a low output. If the bias is low the diode restorer will clip off part of the input signal and cause a reduced output. Likewise, if the bias becomes too high it will take a larger drive to obtain the same output. Check the bias supply and voltage across R1, R2, and R3 with a voltmeter. If diode CR1 is shorted, grid resistor R2 will be removed from the circuit and the grid signal voltage will be developed across R3 alone. This will lower the grid input impedance and reduce the drive, resulting in a reduced output. Check CR1 for forward and reverse

resistance with an ohmmeter. If R2 is large, which it normally is, the diode need not be disconnected for this check. If there is no difference between forward and reverse indications and a low resistance is measured the diode is shorted. If a high resistance is indicated in both directions, it is open. Check the supply voltage and then the plate voltage with a voltmeter. If the plate voltage is low the output will be reduced. If plate resistor R4 increases in value with age an abnormally low plate voltage will result. Measure the resistance of R4 with plate voltage OFF, when the plate voltage appears to be extremely low, and the supply voltage is normal. A similar symptom can be produced by a defective tube which causes heavy plate current flow, or by low bias. If the tube is good, there is a possibility that the tube is oscillating and that the value of R5 is insufficient to prevent it. Check R5 with an ohmmeter with the plate voltage off. If resistance is normal, connect an oscilloscope across the grid and ground, and then across the plate and ground. If the waveform is found obscured by a broad, light, solid band across it the circuit is oscillating at radio frequencies. Check the wiring, particularly the parallel connections to the tube elements, to be certain they have not been lengthened or changed, substitute another tube, and as a last resort change the value of R5 to a much larger value.

Distorted Output. If the cathode degeneration is changed because bypass capacitor C1 is open or shorted, frequency distortion will occur. The high frequency output (without degeneration) will be lower than the output at medium and low frequencies, and the stage will act like an uncompensated amplifier. Use an oscilloscope and a square wave input. Observe the input and output waveforms; with a positive input, the output signal should be negative, larger in amplitude, and of the same general waveform. A sloping vertical edge on the square wave indicates the rise or fall time is excessive, while a sagging flat top indicates low frequency distortion. C1 can be roughly checked by temporarily shorting it while observing the waveform on the oscilloscope. If the circuit is operating properly the waveform will be more distorted when C1 is shorted. If no change is observed, C1 is either open or shorted. Check C1 with an in-circuit capacitance checker, or disconnect it and check for the proper capacitance value and for leakage. Excessive leakage will cause C1 to act as resistor in parallel with cathode resistor R6. Checks for distortion should be made at frequencies which are not

effectively bypassed by C1. If the check is made at a frequency to which C1 offers little or no reactance, the signal will probably appear slightly distorted whether C1 is working properly or not.

Check the rise and fall of the waveform for overshoot and undershoot. In test equipment applications it should be less than 1%, in TV or Radar applications 5% to 10% is satisfactory, while in Servo-equipment 40% to 50% is acceptable. These tests should be made on a normally operating equipment so that the technician is familiar with the correct waveform appearance and permissible amount of distortion before trouble occurs. Waveforms are not required to be any better than those shown in the appropriate Technical Manual covering the equipment under test.

BEAM-POWER VIDEO DRIVER AMPLIFIER.

Application.

The beam power video driver is widely used in search radars to amplify video signals to the 35- to 60-volt level necessary for intensity modulation of the cathode ray indicator tube.

Characteristics.

Fixed negative bias is employed to provide operation in the Class A1 region.

A negative output is produced for a positive input signal.

Shunt peaking is used to compensate for increased rise time produced by the higher output capacitance of the pentode.

DC restoration is provided by a separate diode.

Provides greater output, more amplification, and better linearity than a single triode driver operating at the same voltages.

Requires more dc power than the triode (screen is added) and plate current is larger.


Circuit Analysis.

General. The beam-power video driver is similar to the triode video driver previously discussed in this section of the handbook. The use of a beam-power pentode tube provides greater amplification than the triode with an increase of linearity. The low input capacitance of the pentode decreases the rise time considerably, however, the large output capacitance greatly increases the rise time, so that the overall result is to increase the rise time to about double the triode value. Consequently, it is necessary to include

a shunt compensating inductance in the plate circuit, since cathode degeneration, as used in the triode, is unable to provide sufficient compensation. The shunt-peaking compensating circuit is designed to reduce the total rise time to from 40 to 50 percent of that obtained without compensation, depending upon the tube type used. Because of the compensating circuit inductance the overshoot is increased to about 3% or about double that of a triode driver. The addition of the screen element in the pentode causes additional dc current to be drawn over that of the triode, which, since it does not directly contribute to useful output, causes a greater dc power loss and a drop in overall efficiency. It is necessary that the screen be bypassed to ground effectively for all frequencies employed. While the screen bypass capacitor is effective for the higher frequencies, it usually offers sufficient impedance at the low frequencies to provide a droop in low frequency output, which does not occur in the triode. The low frequency component of screen current, in effect, produces an inverse feedback voltage across the screen bypass impedance, which lowers the instantaneous screen voltage and reduces output at these frequencies. This action is similar to the degenerative action developed across a lightly bypassed cathode resistor. Unfortunately it is greatest at the very low frequencies near the dc level (1 to 15 Hz) which are normally amplified less than frequencies above this range, unless special low frequency compensation is used. Hence such screen degeneration cannot be used to flatten the overall response since it only further attenuates the low frequencies.

Although the single triode driver lacks the amplification of the beam-power driver, the parallel-connected, dual-triode driver usually provides equivalent performance and amplification without the problem of low frequency droop introduced by the screen element. With proper design, either circuit is effective in driving the indicator tube.

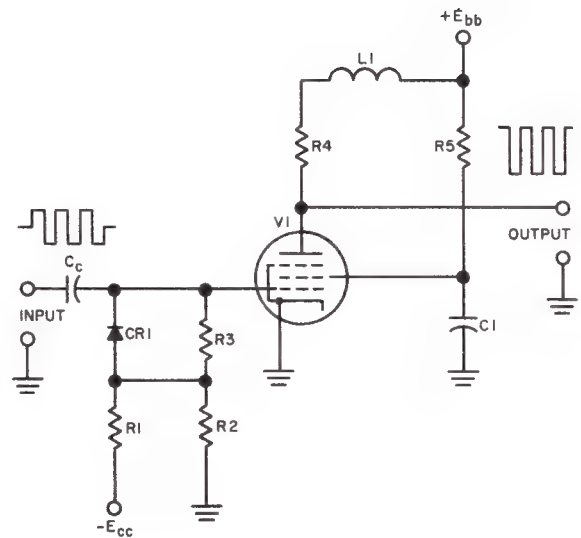Circuit Operation. The schematic of a typical beam-power video driver stage is shown in the accompanying illustration.



Typical Beam-Power Video Driver

Resistance coupling is employed in the input circuit; C_c is the coupling capacitor and R_3 is the grid resistor. The output circuit is usually direct-coupled to the CRT cathode. Diode CR1 is a dc restorer connected across the grid resistor, and fixed bias is obtained from voltage divider R_1 , R_2 connected across the separate negative bias supply. Screen voltage is obtained from the plate supply through series dropping resistor R_5 , bypassed by C_1 . Resistor R_4 is the plate load resistor, and L_1 is the shunt-peaking inductance.

With no input signal, V_1 rests in a quiescent condition with a plate current of approximately 18 milliamperes, as determined by the fixed-bias voltage divider, R_1 and R_2 . The bias is in the Class A1 region and is on the order of 10 volts negative. For small input signals or for short duty cycle signals diode clamp CR1 has no effect, but for large input signals with long duty cycles, it clamps the bias at the fixed value, and prevents the grid from being driven into cutoff. Whenever the input signal makes the cathode of CR1 more negative than the bias value applied to its anode, forward conduction occurs, and the signal

is shunted across grid resistor R3 to ground via R2. Thus the zero output level is maintained at the fixed bias value (see the Clampers section for a discussion of biased clamp operation). When a positive-going input signal appears on the grid of V1, plate current is increased. As the plate current is increased, a voltage drop occurs across plate load resistor R4; this is the negative-going output voltage. When V1 is operating, current flows from the cathode, through the grid wires, through the screen wires, and to the plate. A small dc screen current flow is caused by the positive screen absorbing some electrons as they pass through the screen wires. This screen current flows through screen voltage dropping resistor R5 to the plate supply and ground. The voltage drop across R5 maintains the screen voltage at the desired value. The effective screen voltage is that of the supply less the drop in R5, since screen current flow is in a direction which develops a voltage that opposes the supply voltage. Any instantaneous (ac) variations in screen current are bypassed through C1 to ground. However, at the very low frequencies the impedance of C1 develops an additional instantaneous voltage drop between the screen and ground. This voltage is degenerative and opposes the screen voltage. Since the capacitive reactance of C1 varies inversely with frequency, the screen voltage is reduced at these instants, proportionately to the frequency, and the amplification is, likewise, reduced since the screen voltage controls the plate current. Thus, there is a droop in the waveform at the lower frequencies which are not adequately bypassed by screen capacitor C1.

When the trailing edge of the positive input signal returns towards zero it is negative-going and the plate current is reduced. The reduced voltage drop across R4 produces the positive-going trailing edge on the negative output waveform. Any excessive drive in the negative direction is eliminated by the clamping diode as explained perviously above. When the plate current changes direction, the inductance of L1 tends to continue current flow in the same direction and causes a slight overshoot. Because the overshoot is kept below 3% by proper design and selection of component values, it causes only a slight amount of distortion. Peaking coil L1 is connected in series with plate load R4, and the total drop across this combination load varies in accordance with its impedance. As the frequency is increased, the reactance and hence the impedance of L1 increases as does the high frequency output, thus high frequency compensation is

achieved. For further information on this type of frequency compensation see the previous discussion of the Triode Video Amplifier in this section.

Failure Analysis.

No Output. Improper bias, lack of plate or screen voltage, an open input circuit, or loss of input signal, as well as a defective tube can cause a loss of output. If voltage divider resistor R2 is open, the full negative bias supply voltage will be applied to V1 grid, the plate current will be cut off, and no output can occur. The same condition will occur if R1 is shorted except that, in this instance, the entire bias supply will be dissipated across R2, will cause it to heat, smoke, and eventually burn out. In either case check the voltage across R2 with a voltmeter. If either R1 or R3 is open no bias will be applied to V1, heavy plate current will flow and overload R4 and L1; eventually this will cause the weakest one to burn out. Meanwhile, the output will be held at a constant maximum negative value, causing the CRT to be constantly illuminated, and no signals will appear. Check the bias supply to ground, first with a voltmeter, then from R1 to ground, and finally from the grid of V1 to ground. Lack of voltage indicates that the failure is between the bias supply and the point measured. If the coupling capacitor C_c is open, no signal will appear on the grid, and no output will occur even though normal bias and plate voltage are indicated on the voltmeter. On the other hand, if C_c is shorted the plate voltage of the preceding video amplifier will drive V1 heavily into conduction and cause an indication similar to that of no-bias. In this case, the voltmeter will show a large positive voltage on the grid of V1.

If the plate supply is at fault, no plate or screen voltage will exist on V1, and no output will be obtained. Check the supply with a voltmeter and then check the voltage from screen to ground. If R5 is open, no voltage will appear on the screen, and the plate current will be so small that practically no output will be obtained. A shorted screen capacitor (C1) will also cause a lack of voltage indication at the screen, since the entire supply will be dropped across R5. In this instance, R5 will heat abnormally, and will probably smoke and then burn out. If either R4 or L1 are open, no plate voltage will appear on V1; the screen of V1 would then attempt to function as a plate, and the heavy current flow will cause the screen to heat and glow red, and will also overload

R5, cause it to smoke, and burn out. With normal bias voltage and screen voltage, and a higher than normal plate voltage, if no output voltage exists and an input signal is known to be applied, either tube V1 is defective, or R4 is short circuited.

Low Output. If clamping diode CR1 is shorted, the input signal will be shunted to ground through R2 and a lower than normal output will be obtained. Should R2 increase in resistance the bias will be higher than normal and a reduced output will also occur. In the case of R2 the bias value can be checked with a voltmeter. However, to check the diode, it must either be removed from the circuit, or the plate and the bias supplies must be disconnected and the forward and reverse resistance measured. If the diode resistance is low, and is the same in both directions, it is shorted. If it reads a high resistance in both directions it is open. (It will normally indicate a high resistance in the reverse direction and a low resistance in the forward direction.)

If V1 is low in emission a low output will be obtained. If R5 increases in value, the screen voltage will measure lower than normal with rated supply voltage, and the output will also be low. A similar condition may be caused by a high resistance leak to ground through screen capacitor C1. Check C1 with an in-circuit capacitance checker, or measure R5 with an ohmmeter, with the power OFF. When C1 is disconnected the screen voltage will return to normal if the capacitor is defective.

If the plate supply is low, both the screen and plate voltages will be proportionately lower. If the supply and screen voltages are normal, but the plate voltage is low, V1 may be defective. Check L1 and R4 individually for resistance, with the supply voltage OFF. A poor soldered joint, or an increase in the resistance of L1 or R4 will cause a lower than normal voltage. If L1 measures more than 20 ohms, check its rated dc resistance in the equipment technical manual. Small inductors and chokes showing a higher than normal resistance will usually increase greatly in resistance when loaded, but appear close enough to normal to be within the allowable tolerance of a resistance check (20 percent maximum). In any event, the dc voltage drop when operating should only be a few volts.

Distortion. Usually a simple voltage and resistance check of the circuit will determine defective or off-value parts. To determine distortion, however, it is necessary to observe and compare waveshapes, and

check the input waveform against the output waveform against the output waveform. Also check the waveforms against the specific waveshapes indicated in the equipment technical manual. Use an oscilloscope to observe the operating waveform. The point where it departs from normal indicates roughly the circuit area at fault. Remember, also, that all amplifiers have a slight amount of distortion, but there are tolerances which must not be exceeded. For example, the excessive output capacity of the beam driver circuit and that of the CRT cathode to ground, plus the wiring capacitance, will reduce the rise time. Thus, the leading and trailing edges may have a slight slope rather than being ideally vertical. Likewise, the flat top portion of the pulse can be expected to droop or sag slightly. With inductive parts in the plate circuit there will also be some overshoot and undershoot, caused by the effect of inductance on the transient response. Thus the output waveform will never be identical to that of the input waveform, but they will resemble each other closely. The response of the vertical amplifiers in the test oscilloscope will also affect the apparent waveshape appearing on the screen. When checking waveforms, always make certain that the test equipment is capable of producing the same result as that of the original.

When sloping vertical shapes are observed, look for deteriorated high frequency response caused by an excessive shunting capacitance to ground. For sloping horizontal lines, look for deteriorated low frequency response caused by a defective low frequency compensating circuit, or inadequate cathode and plate, or screen bypassing. By temporarily paralleling the suspected component with a similar part it is usually easy to determine if the suspected part is having the effect on waveshape for which it was designed. Do not make any unauthorized modifications in Navy equipment because it may appear to be better to you, since you may be overcompensating instead.

CHAIN (MIXER, AMPLIFIER, AND DRIVER) VIDEO AMPLIFIER (ELECTRON TUBE)

Application.

The chain video amplifier is used in a radar display system to mix positive radar video with positive marker pulses, to invert the combined signals, and amplify them to a level sufficient to intensity modulate the cathode ray indicator.

Characteristics.

Consists of three basic circuits combined together in cascade.

Uses fixed or self bias, as applicable.

Uses dual triodes to save space and provide adequate amplification.

Requires positive inputs, and supplies a negative output.

Amplification is variable from 30 to 60 times.

Minimum rise time is 80 nanoseconds, with a maximum delay time of 50 nanoseconds.

Droop is not greater than 6% for a 500 microsecond pulse.


Maximum input signal is 1-volt peak, with a maximum duty factor of 0.05.

Maximum output is 60 volts peak.

Circuit Analysis.

General. The chain amplifier consists of three basic circuits: a common cathode type video mixer, a two-stage intermediate amplifier, and a video driver. Each of these basic circuits is described separately in this handbook. For an explanation of the video mixer, see the Common Cathode Video Mixer in the Mixers and Heterodyners Section of this handbook. The intermediate amplifier consists of two identical stages, with the exception that a volume control is added in the cathode of the second stage. See the discussion of the Triode Video Amplifier, and that of the Triode Video Driver Amplifier earlier in this section for a detailed discussion of these two basic circuits.

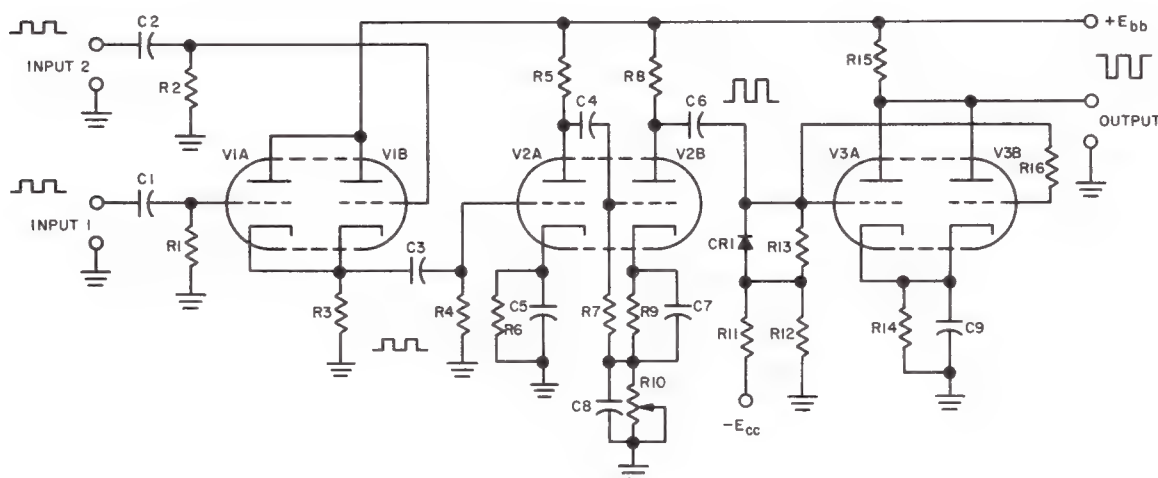Circuit Operation. The accompanying schematic illustrates a typical chain video amplifier.



Chain Video Amplifier

Since each of the basic circuits is fully described elsewhere in this handbook, as stated above, the circuit operation discussion will be limited to a simple functional signal description with characteristics. See the specific basic circuits for any additional information.

Tube V1 is a dual-triode connected as a common cathode video mixer. Resistance coupling is used to supply two identical, high-impedance, grid-input circuits. The plates are paralleled and the output is taken from cathode resistor R3, which is common to both circuits. When a positive input is applied to either grid of V1 a positive output voltage is developed across the cathode output resistor. Because of the cathode follower connection, the circuit is degenerative and no gain is obtained. With approximately 1-volt positive input, about 0.65 volt positive output is developed. For equal amplitude inputs which are in time coincidence, the output is additive and at a maximum. The extent of the adding, primarily, depends upon the value of the cathode resistance and the input signal amplitude. Generally speaking, the largest input signal tends to dominate the output, and the additive factor becomes zero if one of the signals is more than double the amplitude of the other. The low impedance output of V1 is RC coupled to two

opened across the cathode output resistor. Because of the cathode follower connection, the circuit is degenerative and no gain is obtained. With approximately 1-volt positive input, about 0.65 volt positive output is developed. For equal amplitude inputs which are in time coincidence, the output is additive and at a maximum. The extent of the adding, primarily, depends upon the value of the cathode resistance and the input signal amplitude. Generally speaking, the largest input signal tends to dominate the output, and the additive factor becomes zero if one of the signals is more than double the amplitude of the other. The low impedance output of V1 is RC coupled to two

intermediate level, cascaded triode video amplifiers. V2 is a dual triode using each half-section as a separate stage of video amplification. The positive signal from the cathode of V1 is applied to the grid of V2A, which develops a negative output signal across plate load resistor R5. The plate of V2A is RC coupled to the grid of second half-section V2B, so that both stages are cascaded. When the negative driving signal appears on V2B grid, a positive output is developed across plate load resistor R8 for application to the driver stage grid. The cathodes of both stages supply cathode bias through partially bypassed resistor R6 and R9, to provide degeneration at the lower frequencies and thereby improve high frequency response. The fixed cathode resistors of these two stages are identical, however, they are bypassed, with different values of capacitance, because additional resistance in the form of gain control R10 is connected in series with cathode resistor R9 of the second stage and ground. Gain control R10 is only partially bypassed to retain the full degenerative action of these cascaded stages. Overall gain is approximately 15 times, and the gain control permits control of volume over a 2 to 1 range.

The positive output of V2B is also RC coupled to driver stage V3, another dual triode. The elements of V3 are paralleled to provide greater transconductance and more gain. Fixed bias is applied the V3 grids from separate bias source, with partially bypassed cathode resistor R14 supplying degenerative cathode compensation so that plate peaking circuits are not required. The driver stage supplies a gain of approximately 6, and uses a diode dc restorer (CR1) as a biased negative clamp for high level signals. When a positive signal is applied to the grid of V3, a negative output is developed across plate resistor R15 for application to the CRT cathode. A maximum peak voltage drive of 60 volts is obtained for intensity modulation of the CRT indicator. The low output capacitance of the triodes provides good rise time response, and the small quiescent current of 0.5 milliamperes provides efficient operation. The overall pass band is useful from 10 Hz to 1.7 MHz; by changing values and using subminiature tubes, the pass band can be extended to about 3.8 MHz. The high frequency limit is affected slightly by the setting of the gain control, because of the increased degeneration afforded at the low gain settings. Because of the limits permitted by tube specification MIL-E-1, the amplification may be changed by 25% if the tubes

are all selected for high tolerance. A ten percent change in both filament and plate voltage will only vary the amplification 12.5 percent overall. The previously stated values of input, output, and bandpass are made assuming normal plate and filament voltages, and tubes of average tolerance.

Failure Analysis.

General. The detailed failure analysis for the individual stages is discussed at the end of each of the separate circuit discussions referenced at the beginning of this circuit description.

Use an oscilloscope and a square wave generator to isolate the trouble to a basic circuit, then troubleshoot the defective circuit in accordance with the detailed failure analysis for the specific circuit. For example, apply a 400 Hz square wave input signal to one input and observe the output with the oscilloscope. If the output waveform is normal, apply the square wave to the other input and observe that a similar output occurs. Any difference in output indicates trouble in the individual channels of stage V1. Then apply two equal signals simultaneously to both inputs and check for a similar but larger output. If no output, a low output, or a distorted output is obtained during any of these checks connect the oscilloscope successively to the output of each stage. Proceed from the output back towards the input and note when the signal observed on the oscilloscope assumes its normal shape and approximate output level. As an example, assume that with normal input applied both input channels, the driver output is found to be almost normal in amplitude, but distorted. When the oscilloscope is removed and connected to V3 grid, the signal amplitude is reduced, but the distortion is still evident. However, when the oscilloscope is connected to the grid of V2B the distortion disappears. The trouble then exists in tube V2B, its associated circuit, or in the coupling circuit between V2 and V3. Observing the waveform at the plate of V2B will quickly eliminate the coupling circuit. A voltage check of V2 will then reveal if the element voltages are normal, if the voltages are normal tube V2 is probably at fault.

Note that in this case no tubes were replaced or voltages measured until the approximate location of the trouble in this circuit was pin-pointed by the visual waveform check. While the tube could have been replaced and the element voltages measured as soon as the output was seen to be abnormal, it is evident

that a procedure of this sort is basically a waste of time, and even though the trouble might have been eliminated in this manner, three tubes would have been replaced when only one tube actually was defective. Further tests of the tubes would then be necessary to determine which was at fault.

When operation of the circuits is understood and the trouble symptoms are carefully evaluated, much needless testing can be avoided. The cause of the trouble can usually be determined by applying basic circuit theory. In the doubtful cases, a systematic method of testing such as just described will prove superior to any cut-and-try methods, or hit-and-miss guessing.

CATHODE-COUPLED (IN-PHASE) VIDEO AMPLIFIER

Application.

The cathode coupled video amplifier is used as an input matching amplifier, or as an intermediate level video amplifier in cascaded direct-coupled video states.

Characteristics.

Usually is self-biased, although combination fixed- and self-bias can be used.

Usually employs a twin triode for space and economic reasons.

Operates in-phase (a negative output occurs for a negative input and vice-verse).

Provides a high input impedance with a moderate output impedance.

Requires no special frequency compensating circuits.


Inverse feedback from the degenerative cathode produces wideband response.

Circuit Analysis.

General. The cathode-coupled video amplifier can be considered to be a combination of two basic circuits (a cathode follower and a grounded grid amplifier) connected in a cascade arrangement without any coupling elements. The elimination of the necessity for coupling elements through the use of direct-coupling improves the low frequency response. Since most detectors provide a negative output, this circuit may also be conveniently direct-coupled to the detector, and can be either dc or ac coupled at the output.

All the advantages of the cathode-follower input are maintained, while the grounded-grid output circuit provides more gain with greater stability and less tube noise. The output circuit can also be easily matched to the following stage for maximum output by proper choice of load resistor. Since the cathode degeneration is effective for both input and output stages, increased linearity is obtained with better overall frequency response and a wider bandpass than for conventional plate-coupled stages.

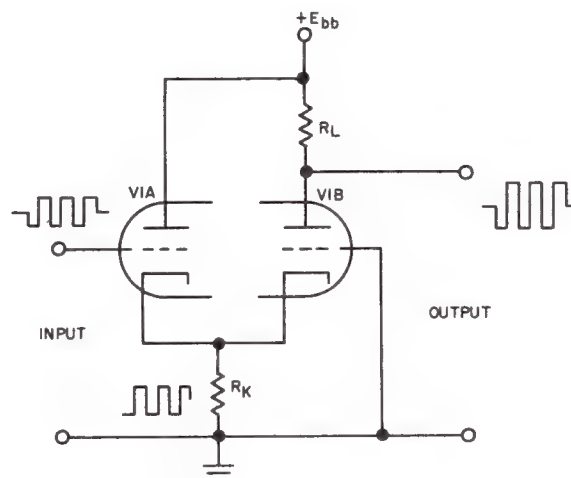Circuit Operation. The accompanying schematic illustrates a typical cathode-coupled circuit with an in-phase output.



Cathode-Coupled (In-Phase) Video Amplifier

A twin-triode tube is used, with one half-section, V1A, operating as a cathode follower, while the second-half-section, V1B, operates as a grounded grid output stage. Cathode resistor R_k functions as a common cathode resistor which supplies bias for both tubes, and as the load across which the input is developed and applied to the output stage. The output voltage is developed across plate resistor R_L in the second half-section of V1.

With no input signal applied, both tubes rest in the quiescent condition, and, since R_k is common to both tubes, the initial bias is determined by the total cathode current of both tubes. When a negative input signal is applied to the grid of V1A the plate current is reduced, and less cathode voltage is developed

across R_k . Since the cathodes of both half-sections are connected together, the instantaneous cathode bias is reduced, and both half-sections tend to draw more plate current. Plate current flow through V1A is determined by the effective bias, which is the difference between the input signal and the developed cathode bias. Current flow through R_k is in a direction which places a positive polarity on the cathodes and a negative polarity at ground. Since the grid of V1B is grounded the reduction of cathode voltage has the same effect as if the grid of V1B were driven less negative, or in a positive direction. Thus plate current flow through load resistor R_L increases and produces a plate voltage drop. The increased drop across the load resistor appears as a negative-going output voltage. Thus the output polarity is the same as the input polarity. The increased plate current flow in V1B, in turn, increases the total cathode current through R_k and produces an increasing positive cathode bias. Thus circuit operation is degenerative and operates with the effect of inverse feedback. Design is such that the common cathode resistor is lower in value than the plate load resistor. Hence, for any change in plate current of V1B the degenerative cathode voltage developed is less than the output voltage. The effective drive voltage for V1B is the difference between the degenerative voltage developed across the cathode resistor and the input signal applied to the grid of V1A. It is less than the input voltage, because the cathode follower stage has less than unity gain; otherwise, the input signal would be cancelled out and no output would occur.

When the input signal swings positive, the opposite action occurs. Plate current in V1A is increased, and produces an increased cathode current and larger bias across R_k . The larger bias is applied as a negative swing to the grid of V1B and reduces the plate current, likewise. Reduction of plate current in V1B causes a reduced cathode current flow through R_k . This inverse or degenerative feedback reduces the total output voltage over what it would normally be without degeneration, but still permits effective amplification of the overall output.

Design is such that the total amplification is about half of that normally obtainable from the same stage, using plate coupling instead of cathode coupling. Although full tube gain is not obtained, cathode degeneration provides an improvement in linearity and prevents any possibility of overdrive and distortion occurring. In addition, the overall response of the

amplifier is broadened by the degenerative feedback. Any tendency of the amplifier to amplify a signal of one frequency more than another frequency is reduced automatically by the increased degeneration produced by the stronger signal. Thus the amplification is made more constant over a wider range than normal, so that the response curve is flattened, resulting in a wider bandpass. The use of direct coupling between the two stages eliminates any problem of phase shift in the coupling capacitor or any reactive effects which would attenuate the lower frequencies. Consequently, shunt- or series-peaking circuits are not required to produce satisfactory video response. In some applications, two twin triodes are cascaded to supply maximum gain.

If a plate load resistor is connected in series with the plate of V1A, operation is substantially the same, except that an out-of-phase output can be obtained. With resistors in both plates, dual and opposite outputs can be obtained with the circuit operating as a phase inverter for push-pull operation.

Failure Analysis.

No Output. Lack of supply voltage, plate voltage, or improper bias will cause loss of output. If either half-section of V1 is defective, or if no signal exists on V1A no output will be obtained. A simple voltage check of the supply, and then from plate to ground will determine if lack of plate voltage is the cause. A check of the bias voltage developed across R_k , with no signal applied, will determine if the proper bias exists; if not, either the tube or resistor is at fault. Loss of input signal can be checked with a VTVM or by observation with an oscilloscope.

Low Output. Improper plate or bias voltage, a defective tube, or a reduced input signal will cause a reduced output. Check the plate and bias voltages with a voltmeter. If the input signal is normal in amplitude as observed on an oscilloscope or VTVM, but the output is low, replace V1 with a known good tube.

Distorted Output. Distortion can best be observed with an oscilloscope and a known input (apply a signal from a signal generator connected to V1A grid, or use a steady input signal to the detector). Observe the waveform on V1A grid, a similar waveform, but reduced in amplitude should appear at the cathode. Then check the waveform at the plate of V1B, a similar but amplified signal should appear. When distortion is visible at any of these points the cause is in the preceding circuit.

WIDE-BAND VIDEO AMPLIFIER (SEMICONDUCTOR)

The wide-band video amplifier is used to provide uniform amplification of video frequencies in radar and television receivers and display amplifiers before application to the cathode-ray-tube indicator or other video output device.

Characteristics.

Common-emitter configuration is used to provide high gain. Transistors used must have an alpha (or beta) cutoff frequency higher than the highest frequency it is desired to amplify.

Class A bias is normally employed to minimize distortion.

Amplifier is specially frequency-compensated to provide wide-band response.

Compensating circuits may be employed in the base, emitter, or collector leads, and even between stages in the coupling circuit, to obtain the desired response curve.


Input impedance is on the order of 10,000 to 15,000 ohms, while the output impedance may be either high or low, depending on the requirements of the output device (high for CRT drive and low for coaxial line drive).

Circuit Analysis.

General. The wide-band amplifier may be either a single stage for light loads, or a number of cascaded stages to supply large driving voltages, where appreci-

able output power is needed. Usually the CRT indicator is driven by the wide-band amplifier since only a little power is required to drive most cathode-ray tubes. The overall response is usually from 30 Hz to 6 MHz, although the response of television stages may be restricted to 4 MHz, and that of radar stages to as low as 2 MHz. When a response greater than 6 MHz is needed, special design techniques are employed, and the overall gain is usually much lower than that of the average wide-band amplifier. The transistors need not be matched, since design is accomplished for each stage individually, and the CE circuit provides better over-all response for mismatched stages. The relatively high-impedance load provided by a CRT is usually considered to be capacitively reactive, whereas the low-impedance load offered by the video (coaxial) line is normally considered to be resistive, since it is usually terminated by a resistor whose value is equivalent to the characteristic impedance of the line to avoid reflections. The types and methods of compensation are standard, but they may be used differently by each designer. It is usually considered more important to obtain the desired gain and response than to effect a savings by the limit use of parts and transistors. Where high power output is required, an external feedback loop is usually employed to provide stability and to improve the over-all response characteristic, in addition to the internal compensating circuits normally used.

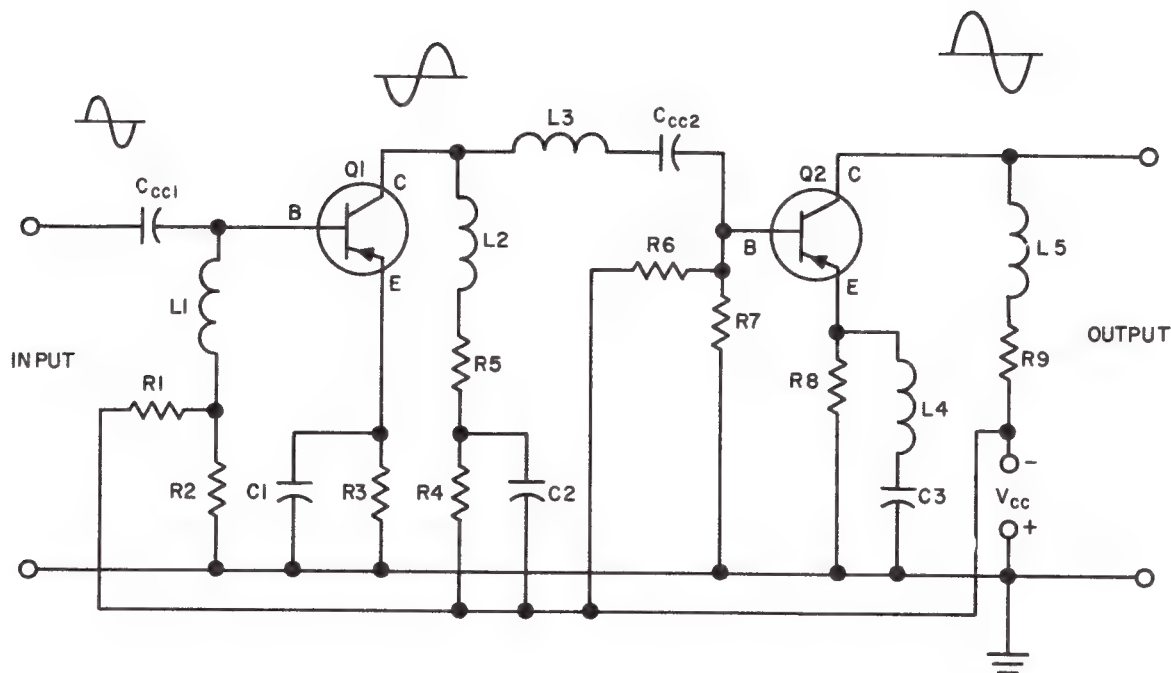Circuit Operation. The following schematic illustrates a typical wide-band amplifier using two transistors in cascade.



Wide-Band Video Amplifier

In the schematic, C_{cc1} couples the base of Q1 to the preceding stage, usually the video detector, and prevents the dc base bias from being shunted through, or affected by, the detector circuit. Resistor R1 and R2 supply fixed voltage-divider bias to Q1, while R6 and R7 perform the same function for Q2. (See the introduction to this section for a discussion of bias arrangements and bias stabilization methods.) R3 and R8 are the emitter swamping resistors for Q1 and Q2, which are bypassed by C1 and C3, respectively. L1, L2, L3, L4, and L5 are compensating inductors inserted to improve the high-frequency response, while R5 and R9 are the collector load resistors. R4 and C2 form a low-frequency boost circuit in the collector circuit of Q1. C_{cc2} is the interstage coupling capacitor. L3, together with the input capacity to Q2 form a series peaking circuit to improve the high-frequency response. The operation of the amplifier is similar to that of any other common-emitter, RC-coupled amplifier except for the effects of the compensating circuits.

When a sine-wave input signal is applied to C_{cc1} , a voltage is developed across the series impedance of L1 and R2, and is applied to the base of Q1. Assume for

the sake of discussion that the sine wave is increasing in a positive direction. This positive swing reduces the negative base bias of Q1 and causes a reduction of emitter current. Since emitter resistor R3 is bypassed by C1 no degeneration is produced. However, as the emitter current reduces, collector current flow through R4, R5, and L2 also reduces. As the collector current reduces, the collector voltage rises towards the negative supply voltage and produces a negative-going output voltage. This output voltage is applied in series with L3 and C_{cc2} , appears across base resistor R7, and is also applied to the base of Q2. The negative-going output of Q1 increases the forward bias on Q2 and causes a greater flow of collector current through R9 and L5. At the same time the emitter current in Q2 also increases, but since it is bypassed by C3 only the high frequency component flowing through L4 changes, and the medium and low frequency components are not affected. Thus, as the input waveform goes positive, a positive going and amplified output waveform is developed in the collector circuit of Q2.

During the negative half of the input signal, the signal adds to the negative forward bias and increases

current flow in the collector of Q1. The increased collector current flow creates a large drop across resistors R4 and R5 and inductance L2, developing a positive-going output voltage. This voltage applied in series with L3 and C_{cc2} appears across R7 and the base of Q2. Since it is positive-going, the forward base bias on Q2 is reduced and causes both the emitter and collector currents to fall also. The collector voltage of Q2, therefore rises towards the supply value and develops a negative-going output signal. Thus the input and output waveforms and voltages are in-phase. Since the transistors operate Class A, a linear and amplified output is produced. The frequency response and bandpass are affected by the compensating networks as follows.

The low-frequency response of the Q1 stage is basically determined by the time constant of C_{cc1} and R2. Although L1 is in series with R2, its effect at low frequencies is negligible since its reactance is very small as compared with the resistance of R2. L1 is used to provide a high reactance (much larger than R2) at the high video frequencies, to avoid shunting them to ground through the relatively low resistance of R2. Since there is more than adequate gain at low frequencies, it is unnecessary to avoid, or to compensate for, any low-frequency shunting at this point. Fixed bias is used so that Q1 may be kept at the center of its operating curve for equal positive and negative swings, as is typical of Class A operation. R3 is affected only by dc changes caused by temperature differentials. When an increased emitter current flows through R3, a positive voltage is produced; this voltage opposes the forward bias, reduces emitter current and returns the operation to normal. Thus, R3 provides conventional emitter swamping action. Since C1 bypasses R3, the ac (signal) variation of emitter current do not pass through R3; hence, R3 has no effect on normal signal operation. As the collector current increases, electron flow is from the supply through R4, R5, and L2 to the collector. At low frequencies the reactance of L2 is very small, and it has practically no effect. Also, at these frequencies the reactance of C2 which bypasses R4 is very large, and can be considered as open. Thus, both R5 and R4 combine to form the collector load at low frequencies. At medium and high frequencies the reactance of C2 becomes very small and can be considered to short-circuit R4. Therefore, as the frequency increases, R4 is shunted out of the circuit, the collector load becomes smaller, and less output voltage is devel-

oped. Note that at the lower frequencies the output voltage is increased over what it would normally be without R4 and C2 in the circuit. Consequently, the combination of R4 and C2 function to extend the low-frequency response. As the high frequencies increase, the shunt output capacitance of Q1 and the shunt input capacitance of Q2 tend to bypass the signals to ground, thus lowering the output voltage at the higher frequencies. To compensate for this effect, L2 offers an increasing reactance (as the frequency increases) and, together with the output capacitance of Q1 (and stray shunt circuit capacitance to ground), forms a parallel-resonant circuit. Since collector resistor R5 is in series with this resonant circuit, it is broadly resonant so that the load impedance is increased over the mid-high-frequency ranges, and the output voltages does not drop over these ranges as it normally would. Thus, the bypassed resistor and the series inductor extend the low-frequency response and the high-frequency response of the circuit, respectively.

The output of the Q1 stage is coupled through capacitor C_{cc2} to the base of Q2. Although L3 is connected in series between the collector of Q1 and coupling capacitor C_{cc2} , it has little reactance at low frequencies and thus has practically no effect on the low-frequency response. C_{cc2} is large and appears as a short circuit to the output signal from Q1, so that the signal is applied to the base of Q2 with practically no attenuation. Although the low value of bias resistance, R7, tends to shunt the input signal to ground, it is not frequency-responsive and does so equally for all frequencies. However, the input capacitance to Q2 is frequency-responsive and shunts the higher video frequencies to ground. To compensate for this loss and to increase the high-frequency response, the value of L3 is chosen to resonate with the input capacitance of Q2 at the higher video frequencies. Thus the high-frequency response is extended by this series peaking circuit to compensate for any input shunting effects. The signal at the base of Q2 is, of course, inverted in polarity by passage through the Q1 stage, and is again inverted in the Q2 stage to provide an output polarity which is identical to that of the input signal.

At the low video frequencies, swamping resistor R8 is shunted by C3, even though L4 is connected in series with C3, since the reactance of L4 is negligible at the low frequencies. As the video frequencies increase, however, the reactance of L4 increases while the reactance of C3 decreases. In effect, L4 acts as a

choke preventing the passage of high-frequency components around R8. Since the high frequencies must now pass through R8, a degenerative voltage is developed by the flow of signal emitter current through R8. This degenerative voltage opposes the normal forward bias and requires a larger input signal to produce the same output. This is the same action that occurs with a partially bypassed emitter resistor, and is equivalent to negative feedback. Thus, the response at the middle and upper video frequencies is kept uniform, and positive feedback through capacitive coupling of the input and output signals is prevented with a slight loss in gain. At the frequency where the reactances of L4 and C3 are equal, series resonance occurs, and R8 is completely shunted (short circuited); there is no degeneration, and a peak response occurs. For all other frequencies L4 and C3 function as a variable-impedance shunt around R8.

Q2, like Q1, is biased Class A, and operates at the center of its transfer characteristic. Therefore, equal input swings develop equal and undistorted outputs across collector resistor R9. Compensating inductor L5 is connected in series with R9 as a shunt peaking circuit, to improve the high-frequency response and correct for the shunting effects of the collector-to-emitter capacitance of Q2, as well as the stray circuit capacitance in shunt to ground. When the output is applied to the control electrode of a CRT, the value of collector resistor R9 is made large in order to develop a large voltage drive. With a low-impedance output, R9 is usually made to match the impedance of the load, being on the order of 50 to 300 ohms, as required.

The schematic circuit just discussed illustrates the standard forms of frequency compensation employed in video amplifiers; however, each wide-band amplifier varies somewhat because of the desired response characteristics and the differences between the transistors. For example, in one amplifier compensating circuits may not be used in the base or emitter loads, but only in the collector and coupling circuits, whereas in another amplifier compensating circuits may be used in the leads of each transistor element. Usually, the greater the number of compensating circuits used, the greater the bandwidth and the better the uniformity of response.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of

shunting resistance employed on the low-voltage ranges of most volt-ohm-milliammeter testers. Be careful, also, to observe proper polarity when checking continuity or making resistance measurements with the ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. Lack of an input signal, improper bias, lack of supply voltage, or a defective transistor can cause a no-output condition. Use a voltmeter to determine the supply voltage and bias. Note that the voltmeter shunt will complete the circuit when you are reading voltages across open components; thus, erroneous indications can be obtained, leading to false conclusions. To avoid errors of this kind, it is better to use an oscilloscope to observe the waveform on the base of Q1, and to follow the signal through the circuit, noting where it disappears. The trouble exists between the points where the signal last appears and where it disappears. If a signal exists on the base of Q1 but not on the collector, either R2, R3, R4, R5, L1, or L2 may be open. Continuity or resistance measurements will determine the defective part. This same condition can also be caused if Q1 is defective. If a signal exists at the collector of Q1 but not at the base of Q2, either L3, C_{cc2}, or R7 may be open, or Q2 may be defective. A resistance check will determine whether L3 or R7 is open; if neither is open, C_{cc2} or Q2 must be at fault. Check the value of the capacitor with an in-circuit capacitance checker. If a signal exists at the base of Q2 but not at the collector, either R8, R9, or L5 is open, or Q2 is defective. If R8, R9, and L5 show continuity and proper resistance when checked with an ohmmeter, Q2 must be defective.

Reduced Output. Reduced output may be caused by improper bias, low collector voltage, a change in the value of the emitter and collector resistors, or defective transistors. The approximate bias and collector voltages can be determined with an ohmmeter. Then use an oscilloscope to follow the waveform through the circuit, noting where the amplitude of the signal changes to localize the trouble to the defective portion of the circuit. If R1 increases in value, the base bias on Q1 will be lowered; if R1 opens, the fixed base bias on Q1 will be effectively zero. Either condition will cause a reduction in output and probably an increase in distortion. If R6 increases in value or opens, it will create a similar condition for Q2. If

either C1 or C3 is open, excessive emitter degeneration will occur and drastically reduce the output. If either R5 or R9 becomes shorted or changes to a lower value, less output voltage will be developed. A similar condition will be caused if Q2 is defective. The resistors can be checked for their proper values with an ohmmeter, and the capacitors can be checked with an in-circuit capacitance checker.

Distorted Output. Improper bias, overdrive, low collector voltage, or defective transistors can cause distortion. The bias and collector voltages can be determined with a voltmeter. Distortion can be most quickly seen and located by the use of an oscilloscope. Apply an undistorted signal and check the waveform through the circuit. The location of the trouble will be evident when the waveform departs from normal. Overdrive will usually be indicated by a flattening of the tops and bottoms of a sinusoidal waveform, indicating that the signal is exceeding the bias voltage at the peaks. In the case of a square wave the amplitude will be reduced, causing amplitude distortion. Since the wide-band amplifier covers a large

range of frequencies, and the low frequencies are particularly susceptible to phase distortion, it is preferable to use a square wave for testing. Because it takes a number of harmonics to produce a square wave properly, the entire audio range may be checked by applying only two different square-wave frequencies, such as 60 and 1000 Mz. The video response can likewise be checked every 5 KHz up to 50 KHz (the usual limit of generator range). A sloping response to the leading or trailing edge of the waveform indicates poor high-frequency response, while a sloping flat top indicates poor low-frequency response. By temporarily short-circuiting a specific compensating circuit, the effectiveness of the portion under suspicion can be gauged. Distortion caused by regeneration (positive feedback) sometimes occurs in high-gain amplifiers, and is shown by a large-amplitude response peak (sometimes by oscillation), usually over a small range of frequencies. In comparison with a wide-band amplifier known to be operating properly, it will show as a hump or peak in what ordinarily would be a flat curve of uniform response.

PART 5-6 RF

R-F AMPLIFIERS

General.

R-F amplifiers are similar in many respects to other forms of electron tube amplifiers, but differ primarily in the frequency spectrum over which they operate. There are two general classes of r-f amplifiers, the untuned amplifier and the tuned amplifier. In the untuned amplifier, response is desired over a large r-f range, and the main function is amplification alone. In the tuned r-f amplifier, very high amplification is desired over only a small range of frequencies, or at a single frequency. Thus, in addition to amplification, selectivity is also desired to separate the wanted from the unwanted signals. The use of the tuned r-f amplifier is generally universal, while that of the untuned r-f amplifier is relegated to a few special cases. Consequently, when r-f amplifiers are mentioned, they are ordinarily assumed to be tuned unless otherwise specified. The tuning element usually consists of a parallel-resonant L-C circuit. It may be inductively tuned by a movable slug, with the tank capacitance fixed in value or consisting of the stray and distributed capacitance existing in the circuit. Or, as is usually the case, a fixed or slightly adjustable inductor determines the high-frequency limit, and a tuning capacitor is used to tune to the desired frequency or over a range of frequencies.

In receiving equipment, the r-f amplifier serves to both amplify the signal and choose the proper frequency; in addition, it serves to fix signal-to-noise ratio. A poor r-f amplifier will make the equipment able to respond only to large input signals, whereas a good r-f amplifier will bring in the weak signals above the minimum noise level (determined by the noise generated in the receiver itself) and thus permit reception which would otherwise be impossible.

In transmitters, the r-f amplifier serves to amplify a single frequency (including any sideband frequencies produced by modulation) to a value suitable for application to the antenna. Basically, the receiver r-f amplifier is a voltage amplifier, while the transmitter r-f amplifier is a power amplifier.

As might be suspected, since the r-f amplifier is employed over the entire r-f spectrum, careful attention to design parameters is necessary to obtain

proper operation. In the medium-, low-, and high-frequency ranges, conventional tubes and components are used. In the UHF, SHF, and microwave ranges, specially designed tubes and components are required to obtain optimum results (for example, the traveling-wave tube and the multi-cavity klystron).

In addition to the design requirements imposed by frequency, other considerations are often involved to obtain less noise and good selectivity with sufficient amplification, such as those involved in cascaded and cascoded stages. In other instances the r-f amplifier not only amplifies, but also serves to multiply the frequency. Each of the various types and classes of r-f amplifiers will be discussed.

The transistors used for r-f amplifiers differ in a number of respects from electron tubes. The forward transfer admittance is roughly 15 to 40 times larger than the corresponding tube transconductance. Both the input admittance and the input capacitance are also correspondingly larger. The base-to-collector capacitance may be equal to, or even less than, the grid-to-plan capacitance of an electron tube. However, because of the lower impedance levels involved in the transistor, this capacitance does not have as much importance as it has in tube circuits. The series resistances of the transistor elements also become higher at radio frequencies and produce a number of effects. For example, the base spreading resistance increases the amount of drive power required and causes instability in the amplifier. The emitter series resistance decreases the amount of drive power required, and also limits the amount of usable amplification because of the additional degeneration produced. The collector series resistance adds to the total output impedance to increase the gain, but also reduces circuit stability because of the possibility of regenerative feedback due to the higher gain. A phase shift is also produced in the output because of this collector resistance. Each of the above items will be discussed in more detail at the appropriate points below.

The tuned r-f amplifier is considered to be a narrow-band amplifier rather than a wide-band amplifier because it passes only a relatively small range of frequencies about the center of its band pass. Whereas the video (wide-band) amplifier passes frequencies from zero to 6 MHz or more, the r-f amplifier used in communications equipment usually does not pass more than 10 to 15 KHz, and in most instances less than this range. On the other hand, it

should be noted that the r-f amplifiers used in television service, or for pulsed modulation, require a much larger bandwidth to accommodate the many side-band frequencies associated with these types of transmissions. Such amplifiers are considered to be special wide-band r-f amplifiers, except when the carrier frequency is so high that the modulation frequency is a small percentage of this figure. For example, a 300-MHz carrier with a 10-MHz modulating frequency would be adequately handled by a narrow-band r-f amplifier, but a 30-MHz carrier containing a 10-MHz modulation frequency would require a wide-band r-f amplifier. Since semiconductor wide-band r-f amplifiers are not yet commonly used, the circuits to be discussed later in this section concern the conventional narrow-band r-f amplifier.

R-F amplifiers are used for both receiving and transmitting. A receiver uses a low-power, small-signal amplifier, while a transmitter uses a high-power, large-signal amplifier. Except for the conditions required by the power consideration, both types of amplifiers are similar and operate identically. Unfortunately, however, the transistor response or power gain is reduced as the frequency is increased. The response curve of a transistor is similar to that of a low-pass filter. That is, up to a certain frequency the gain is fairly uniform, and beyond this cutoff frequency the output drops rapidly toward zero. The limit of this upper cutoff frequency and the rapidity of dropoff depend to a great extent on the type of transistor and its composition. Many different types of transistors have been developed to extend the usable high-frequency range, such as the surface barrier transistor, the drift transistor, and others.

In addition to the loss of gain at the higher frequencies, the action of the transistor becomes complex; the transistor does not operate exactly the same at high frequencies as it does at lower frequencies. The internal resistance changes, and the effects of the junction capacitances become more pronounced. In high-frequency-amplifier applications, the collector-to-base capacitance causes positive feedback that may result in oscillation. The average value of collector-to-base capacitance for high-frequency transistors is on the order of 2 picofarads, as compared with 50 picofarads or more for transistors used at the lower (audio) frequencies. The base spreading resistance (resistance of bulk material of base) of the transistor increases at high frequencies, and the shunting effects of the low-resistance path produced by forward con-


duction of the base emitter junction tend to lower the input resistance, while the forward bias acts to reduce the width of the depletion areas and thus increase the base-to-emitter capacitance. At the same time, the internal flow of emitter current through the base-collector junction also reduces the width of the PN junction and increases the capacitance between the base and collector. It is this capacitance which causes feedback and tendency toward oscillation as the operating frequency is increased. At high frequencies the collector-to-emitter capacitance may be as high as 100 times that of the base-collector junction capacitance. For this reason, the common-base circuit generally gives better high-frequency response than the common-emitter circuit, but lacks the high gain of the common-emitter circuit. Since the common-emitter circuit tends to be more stable at the higher frequencies than either the common-base circuit or the common-collector circuit, the design trend is to use transistors with a high alpha cutoff frequency, and the CE configuration for higher gain. Both CB and CE circuits will be discussed later in this section.

Unilateralization and Neutralization. In electron-tube r-f amplifiers used at the higher radio frequencies, interelectrode capacitance causes positive feedback and oscillation. Neutralizing circuits are usually provided to prevent oscillation and to insure maximum gain with stability. Likewise, in the transistor r-f amplifier, the effect of the base-collector capacitance and the development of negative resistance through a change in internal parameters also causes oscillation. Neutralization circuits are used to prevent this oscillation and to obtain maximum gain. Neutralization represents a special form of unilateralization at a single frequency. When we speak of *unilateralization*, we are talking about the methods of making the transistor a one-way device. In other words, the input circuit is unaffected by the output circuit. Recall from basic theory that there is a reverse current effect and common impedance coupling within the transistor. This means that any change of current in the output circuit also develops a feedback current which affects the input circuit, and vice versa. Thus in tuned amplifiers a change of tuning in the output stage reflects back as a change of capacitance in the input circuit, and also as a change in the amount of output fed back into the input. In cascaded tuned stages such effects would cause alignment problems. As each stage was adjusted the





preceding stages would have to be readjusted, since each adjustment would change the previous adjustment. The result would be that no two alignments would be alike and, likewise, neither would the performance and selectivity of the r-f amplifiers stages be comparable. Unilateralization deals with the method or circuitry whereby both the resistive and reactive portions of the circuit are cancelled so that there is no feedback from output to input, and, power is transferred unilaterally in only one direction, from input to output. Unilateralization of the circuit is not frequency-responsive; it is effective for all frequencies. On the other hand, neutralization is effective for only a single frequency or a relatively small range of frequencies. For example, it is only necessary to neutralize an i-f stage because it operates at a fixed center frequency. However, an r-f amplifier used in a multi-band receiver requires unilateralization to prevent the possibility of feedback or oscillation on any of the frequency ranges over which it operates.

A typical example showing the feedback elements and unilateralization elements involved in a common-base amplifier is illustrated schematically in the accompanying figure. The elements r'_b , r_c , and C_{CB} in the illustration are the internal parameters which cause feedback and oscillation at radio frequencies. Resistor r'_b is the *base spreading resistance*, r_c is the resistance of the collector-base junction, and C_{CB} is the capacitance of the collector-base junction. The resistance of the collector-base junction is very high because of the reverse bias placed on the collector. At very high frequencies C_{CB} effectively shunts r_c . Assume that an input signal adds to the forward bias on the base (the base and collector bias supplies are not shown on the schematic for simplicity) and causes the emitter to be more positive than the base. Collector current i_c increases in the direction shown by the arrow. A portion of the increase in collector current is fed through C_{CB} and r'_b in the direction shown by the arrow, and produces a voltage with the indicated polarity. This internal feedback voltage developed across r'_b is of the same polarity and adds to the input voltage, causing a further increase in i_c ; this action is regenerative and represents positive feedback, which will produce oscillation. The external circuit elements inserted to neutralize this action are R_{N1} , R_{N2} , and C_N ; they correspond respectively, to r'_b , r_c , and C_{CB} . Since at high frequencies C_N shunts R_{N2} , this resistance is necessary

only at the lower radio frequencies. It is clearly seen that when the input signal causes a feedback voltage across r'_b , a portion of increased collector current i_c is also fed back through C_N and R_{N1} to the base. The direction of this external feedback voltage is as indicated on the schematic, and is direct opposition to the voltage developed across r'_b . When the internal and external feedback voltages are made equal, since they are of opposite polarity, they cancel and no positive or negative feedback occurs; thus, the circuit is unilateralized. In the common-emitter circuit, since the polarity of the collector is opposite that of the input, it is necessary to develop an out-of-phase voltage and feed it back to the input. This is done through the use of a transformer, using the secondary winding to invert the feedback voltage, through a tapped tank circuit, or by use of a bridge circuit, as will be shown in some of the following circuit explanations. In some instances an inductance connected in series with a blocking capacitor is used between the collector and the base, with the inductor and the distributed capacitance in the collection circuit operating as a tuned, parallel-resonant circuit. However, inductive arrangements tend to be critical in adjustment since they are resonant only over a small range of frequencies near the center resonance point, and thus are not as frequently used. Partial emitter degeneration is sometimes employed in a similar manner to provide the feedback voltage. The accompanying figure shows some typical feedback circuits used for neutralizing the common-emitter configuration. The parts identifications are identical with these used in the common-base circuit explained

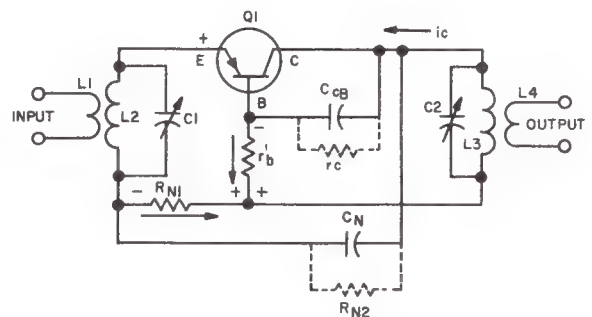

Feedback and Unilateralization Elements

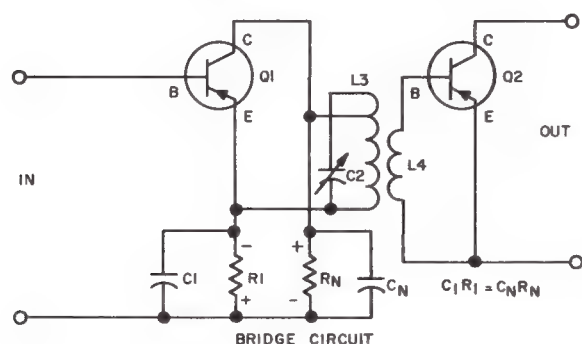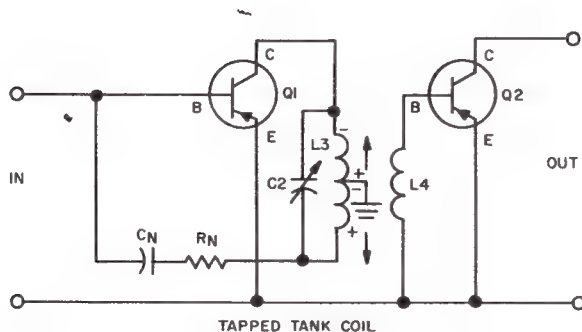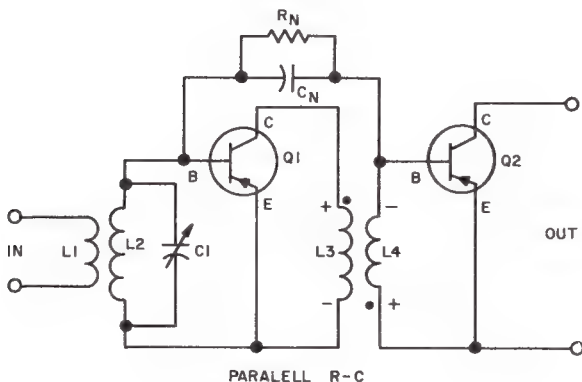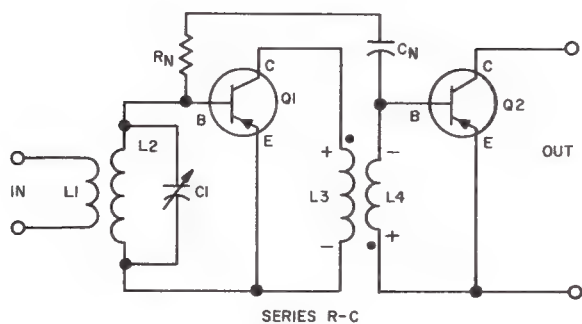


Typical Common-Emitter Neutralizing Circuits

above, and operate in exactly the same manner; therefore, no further explanation is included to supplement the figure.

Selectivity and Impedance Matching. Since the narrow-band amplifier operates to amplify a band of frequencies around the center (carrier) frequency, tuned circuits are always used to obtain the desired selectivity. R-F amplifiers and i-f amplifiers are almost identical. Both are actually r-f amplifiers, but the i-f amplifier operates at a fixed (intermediate) frequency, which is usually lower than the frequency of the r-f amplifier. The amplifier normally consists of only one (or at the very most two) stages, whereas the i-f amplifier uses a number of cascaded stages to obtain high gain with the desired selectivity at the fixed i-f frequency. While the r-f amplifier is tunable over the entire range of reception, the i-f amplifier is fixed-tuned over only a small frequency range about the intermediate frequency. The selectivity is determined by the Q of the tuned circuit; the higher the unloaded Q , the greater the selectivity. When loaded the Q will drop; thus, the design is based upon the unloaded Q , since the loading is usually determined by the circuit configuration and bias. The bandpass of the tuned circuit is considered to be that range of frequencies covered between the half-power points on the selectivity curve (these occur at 70.7 percent of peak amplitude). Thus, a response down 3 dB at 5 kHz on either side of the center (carrier or i-f) frequency covers a range of 10 kHz in bandwidth.

Although matching input and output impedances will provide maximum transistor power gain, this is not always possible. It is sometimes necessary to sacrifice gain to obtain the desired selectivity. In some instances by mismatching stages with individual high gain it becomes unnecessary to unilateralize or neutralize the stages. It is also difficult to obtain a high- Q circuit if the input or output resistance of the transistor which shunts it is low. Therefore, a variety of circuit devices are used to obtain the desired matching impedance while maintaining a high Q for optimum selectivity. Hence we find the simple single-tuned, parallel-resonant tank, so popular with electron tubes, replaced by a tapped tank, or tuned by a capacitance divider for impedance transforming purposes. The following figure shows typical forms of coupling circuits used between cascaded stages of r-f or i-f amplifiers.

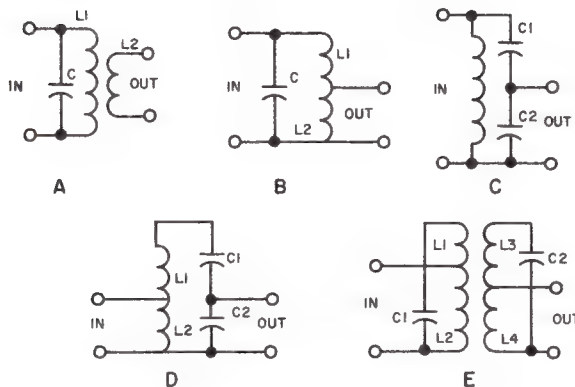

Impedance-Transforming Circuits

In circuit A, the conventional single-tuned, transformer-coupled circuit is shown; the impedance relationships vary as the square of the turns ratio. In circuit B, a tapped auto-transformer is used; L_1 plus L_2 are the primary, while L_2 is the secondary producing a step-down impedance ratio. In circuit C, a capacitance divider is used to reduce the impedance between the input and the output. In circuit D, both the input and output impedances are different, and L_1 helps to improve the over-all Q of the tank circuit. In E, a double-tapped transformer is used to supply high-Q primary and secondary tanks with the proper impedance matching for the input and the output. Since the Q of the circuit depends on the ratio of reactance to resistance in a coil, the lower the resistance and the higher the inductance, the larger the Q. Therefore, to match the low values of input and output resistance in the common-emitter circuit, the large inductance is tapped at an appropriate point along the inductance. The square of the turns ratio between the lower and upper halves of the inductance determines the impedance at the tap. For example, in circuit B of the preceding figure, assume that the collector output impedance is on the order of 10,000 ohms and that the tap is located 1/5 of the distance between L_1 and L_2 ; since L_1 will have 5 times as many turns as L_2 , a 25-to-1 impedance reduction results (impedance varies as square of turns ratio). The output impedance across L_2 then would be roughly 400 ohms, and suitable for matching the input to a common-emitter stage. Naturally, the exact calculation is not as simple as in the example, since the loading effects of circuit capacitance and shunt

internal impedance must be considered; however, the example serves to illustrate the basic principle involved. In practice, the exact location of the tap is made experimentally, using the design equations as a guide.

At the higher frequencies, with a smaller number of secondary turns, unity coupling in r-f or i-f transformers becomes difficult to achieve; thus, capacitive coupling is generally used. Where extreme selectivity is desired, the transformers are usually double-tuned (both primary and secondary are tuned). This produces a sharper response, since two tuned circuits are used instead of one, and a flatter over-all response also results. Cascaded stages are often stagger tuned to provide a wider band pass; this is universally done in television i-f amplifiers.

The receiving r-f amplifier uses Class A bias to avoid distortion, while the transmitting r-f amplifier operates Class B or C for efficient power generation. At the present time, the following circuit discussions are limited to receiving types of r-f or i-f amplifiers.

TRIODE GROUNDED-GRID R-F AMPLIFIER

Application.

The triode grounded-grid r-f amplifier is used in receivers as a tuned voltage amplifier, particularly in the ultra-high-frequency ranges where it is impossible to use pentodes or beam power tubes. It is also used as a Class C linear power amplifier, especially in television transmitters.

Characteristics.

No neutralization circuit is necessary.

Can use either fixed or self-bias.

Has low power gain, but relatively high voltage gain.

Requires more driving power than a grounded-cathode stage.

Grounded grid effectively isolates plate from cathode.

Operates Class A biased for reception, and Class C biased as r-f power amplifier.


Usually used with disc seal or pencil-type, closely spaced triodes at frequencies where coaxial lines are used as tank circuits.

Particularly useful in wideband applications such as TV, because it produces increased output power and efficiency in a particular tube for a given bandwidth.

Circuit Analysis.

General. While the grounded-grid amplifier is most useful at UHF, it is sometimes used on lower frequencies for its inherent stability, and to avoid neutralization. With proper design, it also helps reduce "first stage noise" in receivers. However, the grounded-grid circuit is not generally used at the lower frequencies because of the extremely high gain possible with grounded-cathode pentodes. In transmitting applications it is usually used as a Class C linear amplifier, particularly in those applications where the driver stage has surplus driving power, because only a small amount of power is absorbed by the grid circuit, and the remainder is "passed through" to the plate circuit and adds to the total output because of the grounded-grid connection.

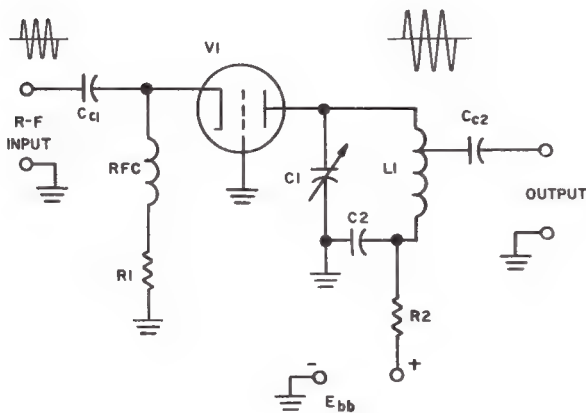Circuit Operation. The accompanying schematic illustrates a typical grounded-grid circuit. For convenience, the tank circuit is shown as a conventional LC parallel-tuned circuit; in actual practice, however, coaxial lines or cavities are used at the high frequencies, where this circuit is usually used.



Typical Grounded-Grid R-F Amplifier Circuit

Input coupling capacitor C_{c1} functions as both a coupling capacitor and a dc blocking capacitor to isolate the input circuit from the antenna or previous stage. Thus, the cathode bias is not affected by the input circuit. Radio-frequency choke RFC keeps the cathode above ground, since the grid is grounded to the chassis. Resistor $R1$ is a conventional but unbypassed cathode bias resistor which supplies Class A bias for $V1$ (see the introduction to this section for

an explanation of cathode bias). The plate of $V1$ is series-fed through voltage-dropping and decoupling resistor $R2$ and tank coil $L1$. Bypass capacitor $C2$ keeps the lower end of tank coil $L1$ at ground potential, and bypasses $R2$ for rf. $C1$ is the tank tuning capacitor, and the rator is grounded to eliminate body capacitance effects when tuning. The output is capacitively coupled through C_{c2} to the next stage.

When an r-f signal appears at the input, the low reactance of C_{c1} allows it to appear on the cathode of $V1$ without any appreciable attenuation. The input signal may be from an antenna or a preceding r-f stage, and in some cases it may be that output of a tuned tank circuit. With the grid at ground potential, $V1$ is biased by the total cathode current flow through $R1$. With a positively biased cathode, the grid is effectively biased negative, and only quiescent Class A plate current flows. With no input signal there is no change in plate current and, consequently, no output.


Assume that an unmodulated r-f signal of constant amplitude appears at the cathode of $V1$. Since this signal appears between the cathode and ground, it can be considered as being supplied by a generator connected in series between the $V1$ cathode and ground. The r-f choke presents a high impedance to ground, and prevents shunting of the input signal to ground through bias resistor $R1$. On the positive r-f half-cycle the cathode is momentarily more positive resulting in the grid becoming more negative, so that a reduction of plate current occurs. In the plate circuit, the tuned parallel tank circuit, $L1$, $C1$, appears as a high impedance to the r-f component of the plate current. With less plate current flowing through the tank impedance, less voltage drop is developed across it and the plate voltage rises toward the source voltage (becomes positive-swinging). Thus, a positive output signal is developed and fed through C_{c2} to the next stage. It is evident that the grounded-grid circuit produces an output signal which is in phase (of the same polarity) with the input signal producing it.

During the negative half-cycle of operation, the cathode becomes less positive (is driven in a negative direction). A negative cathode swing causes the plate current to increase, the produces a large voltage drop across the output load impedance (tank circuit). Since the voltage drop across the tank causes the effective plate voltage to be less, a negative output swing is developed. Again the output signal is in phase with the input signal. (This action is opposite the conventional 180-degree phase shift produced in the

grounded-cathode circuit, and corresponds with the action of the common (grounded)-base circuit in semiconductors). With the grounded-grid amplifier operated Class A, and with equal positive and negative swings, the average value of plate current does not change. The current flow from the cathode remains steady and occurs during the entire cycle; thus, cathode bias can be used, since the plate current is never interrupted. At the same time, the instantaneous signal changes cause larger (amplified) instantaneous r-f pulses of plate current, which produces the voltage drop across the tank impedance and an amplified output voltage. Note that the tank circuit must be tuned to the r-f signal to produce a high impedance and develop an output. Thus, signals with a frequency outside the tuned circuit bandpass are not amplified, or are greatly discriminated against.

From the above description of circuit functioning, it can be seen that the basic functioning of the grounded-grid circuit is similar to that of other types of r-f or audio amplifier circuits. Further consideration is necessary to develop the actions that are peculiar to this circuit alone.

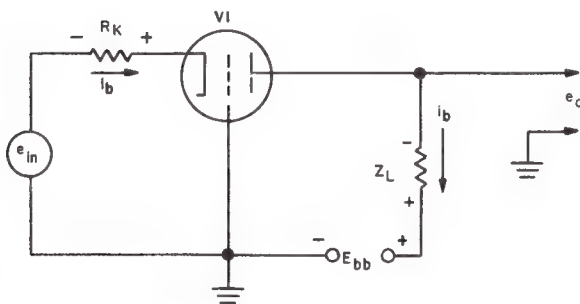Considered the following simplified equivalent of the grounded-grid circuit.



Simplified Equivalent Grounded-grid Circuit

The input signal is shown as an ac generator connected in series with input resistance R_K . Actually, the cathode input impedance is inherently very low, and electron flow is from ground to the cathode, through the grid to the plate, and back into the supply, producing the polarities shown in the simplified circuit. Since the grid is placed between the cathode and the plate, when grounded it acts as a shield which divides the circuit into two parts—an

input circuit and an output circuit, both at above-ground potentials. Hence, any coupling is effectively minimized by the grounded grid. Since electrons flow from cathode to plate, some electrons will be intercepted by the grid and carried to ground. Thus, there will be a greater flow of grid current than in the grounded-cathode circuit, where the grid is isolated from ground by a relatively high impedance. For this reason, the grounded-grid amplifier requires more drive than the conventional grounded-cathode amplifier. Since feedback resulting in oscillation normally occurs from capacitive coupling between the output and input circuits, the good shielding of the grounded grid reduces this effect to a minimum. In addition, the interelectrode capacitances are reduced. The output capacitance is the grid-to-plate capacitance, which is usually the lowest in an electron tube; thus, capacitive shunting effects on the output are reduced at the higher radio frequencies to provide better performance. In addition, the plate-to-cathode capacitance is reduced, since it is the series capacitance produced by the plate-to-grid and grid-to-cathode interelectrode capacitance. Actually, in practical tubes it is reduced to a value on the order of 0.2 picofarad, which is negligible, so that neutralizing is not normally required.

Since signal voltage e_{in} is connected between the cathode and ground, it is effectively in series with the tube plate circuit; thus, in tuned r-f voltage amplifiers the output voltage is produced as though the circuit were driven in the normal manner (grounded cathode), but had an increased amplification amplification factor of $\mu + 1$. Hence, high voltage gain is obtained.

It is important to remember, however, that the matter of gain is relative. A low amplification factor tube will not give as much amplification as a high amplification factor tube. Nor will a triode give as much gain as a pentode at the lower frequencies. Thus, even though we speak of the grounded-grid circuit as providing high gain, it does not mean that the gain is as great as that provided by the grounded-cathode circuit using the same tube and voltages. At the ultra-high frequencies where this circuit is most useful, the performance and gain are better because of the poor performance of the pentode. At the lower radio frequencies, it usually requires two stages of grounded-grid amplification to obtain results equivalent to those obtained with a single grounded-cathode pentode stage.

In power amplifier applications, low power gain is obtained because of the increased drive requirement and the low input impedance. The low input impedance, however, does not absorb all of the input (driving) power and cause a complete loss. Instead, the driving power is fed into the plate circuit (it is connected in series with the plate and cathode circuit), and adds to the total plate power (less the amount needed to drive the tube). The additional plate power supplied by the driver is distributed between the internal tube resistance and the tank circuit, so that only a portion is lost or dissipated in the tube plate. The total output power in watts is equal to $I_p(e_{in} + E_p)$, where e_{in} is equivalent to the rms value of grid voltage (E_g).

In r-f power amplifiers with directly heated filaments, since the filament is also the cathode, it is necessary to use r-f chokes in the filament leads, or provide some other arrangement to keep the filament above ground and balanced. If the filament is not kept above ground, the filament and grid would be short-circuited, and the circuit would not operate.

When employed as a modulated power amplifier, the small portion of drive power which is inserted into the plate circuit remains unmodulated, making it practically impossible to obtain 100 percent modulation when plate modulation alone is used.

Failure Analysis.

No Output. With proper bias and plate voltage, as checked with a voltmeter, only an open input circuit, lack of an input signal, or an open output circuit can result in no output. With input coupling capacitor C_{c1} open, no signal will be applied to the cathode and there will be no output. With output capacitor C_{c2} open, the signal will not appear at the output. Likewise, if the tube is defective, no output signal will appear. If capacitor C2 is shorted or R2 is open, there will be no plate voltage on the tube plate; thus, no output will be obtained. The capacitors can be checked with an in-circuit capacitance checker, while R2 can be checked with an ohmmeter. If the tube is suspected, check it with a tube checker. Do not neglect the possibility that the plate supply fuse may be open. The voltmeter check will usually indicate any abnormal operation. An open plate circuit will be indicated by no voltage at the plate. If the tuned output circuit is shorted, plate voltage will appear to be normal at the supply, but will be entirely dropped across R2 and thus be zero at the tube plate. If the

plate voltage is low, and excessive plate current is the cause, it will also cause a high cathode bias. If the bias is sufficient, the tube will be almost at cutoff and the output will be so low as to be mistaken for no output at all. If the cathode r-f choke is shorted, the bias and plate voltage will appear to be normal, but the input signal will be bypassed to ground through cathode resistor R1, and there will be no output. Where V1 acts as a power amplifier, if C_{c1} is shorted or leaky, the cathode will be biased excessively by the plate voltage of the driving stage; this bias may cause plate current cutoff, and result in no output.

Low Output. If the bias is high, the plate voltage low, or the tube defective, a low output will be obtained. Check the bias and plate voltage with a voltmeter; if the voltage appear to be normal, check the tube with a tube checker. With selective tank circuits, a small amount of detuning of capacitor C1 will attenuate the signal considerably. Likewise, a high resistance in the tank circuit, caused by a poorly soldered connection, may cause sufficient loss of signal because of low circuit Q (and reduced selectivity) to produce a reduced output. An increase in the resistance of R2 due to aging will cause an increased voltage drop, low plate voltage, and low output. A change in the output load can cause a detuning effect on the tank and a reduction of output; the detuning can be compensated for by a slight readjustment of the tuning capacitor. If bypass capacitor C2 opens, the tank circuit, C1, L1, will tune broadly and resonate over a different range of frequencies, and, if R2 is sufficiently small, will cause loss of signal through absorption by the power supply.

Distortion. The grounded-grid amplifier is subject to the same distortion possibilities as other r-f amplifiers. If the bias is too low, large r-f signals will in effect drive the grid positive, causing nonlinearity and saturation effects; thus, the plate waveform will be clipped at the peak of the cycle. If the bias is too high, the negative peaks will drive the tube to cutoff, clipping off the bottom of the signal. In both cases, a distorted output will result. Where modulated signals are amplified, it is important that the bandpass of the tuned circuits be wide enough to avoid sideband cutting, or the missing frequencies will cause distortion. The possibility of increased selectivity due to regeneration is less with the grounded grid than with other circuits; however, the good shielding between the input and output may be nullified if the lead

dress is charged during a repair. Hence, when distortion seems to occur only at certain frequencies or over a narrow portion of the tuning range, or if whistles or squeals occur, neutralization or a lead dress correction may be required.

PENTODE R-F VOLTAGE AMPLIFIER

Application.

The pentode r-f voltage amplifier is universally used as the input stage in receivers or other cascaded r-f amplifier stages to provide a high signal-to-noise ratio with maximum voltage amplification.

Characteristics.

May be either or untuned.

Operates at a specific r-f frequency or is tunable over a range of r-f frequencies.

Provide high gain (100 or better).

Uses impedance coupling at input or output where high gain is not required, and transformer coupling with or without tuning for high gain.

Uses cathode bias, or contact bias for small input signals.

Operates Class A at all times.

Circuit Analysis.


General. The pentode r-f voltage amplifier may be either tuned or untuned. When untuned, the stray wiring and distributed circuit capacitance plus the tube capacitance to ground limit the high-frequency response, and hence the highest r-f frequency at which it can be used. On the other hand, the tuned r-f amplifier uses a parallel-resonant circuit to supply a high impedance across which the load voltage is developed. In this instance, the stray, distributed, and tube capacitances merely add to the value of tuning capacitance so that higher frequencies and greater amplification (as compared with the untuned stage) at these higher frequencies is obtained. Therefore, the tuned r-f amplifier is universally used, and the high gain of the pentode provides amplification not possible with a triode or untuned stage. The tuned r-f amplifier is further subdivided the narrow-band amplifier and the broad-band amplifier into two classes: Narrow-band amplifiers are used to amplify CW or voice-modulated signals (including broadcast signals), whereas broad-band amplifiers are used to amplify television, video, or pulse-modulated signals. Narrow-

band amplifiers accept a maximum of 5 to 10 kHz around the center frequency, whereas broad-band amplifiers cover the range of 5 to 10 MHz around the center frequency. Generally speaking, narrow-band amplifiers used the same types of pentode tubes used with resistance-coupled audio amplifiers, and broad-band amplifiers use the same type of pentode as is used with video amplifiers.

The tuned r-f amplifier may also be subdivided into two other classes: single-tuned and double-tuned. Since the double-tuned type is usually employed in tuned interstage amplifiers and cascaded stages, and these are the subjects of separate discussions later in this section, only single-tuned amplifiers are discussed here.

The use of the pentode, with its high transconductance and amplification factor, results in a high value of voltage amplification. In addition, the low grid-to-plate capacitance of the pentode reduces the tendency toward plate-to-grid feedback and self-oscillation. A lower effective tube input capacitance also increases the high-frequency limit of operation. By the use of coils with a high ratio of inductance to resistance (Hi-Q), the amplification provided by each stage of the tuned r-f amplifier can be made greater than of the amplification factor of the electron tube alone. Since the amplification of the r-f amplifier depends greatly upon the transconductance of the tube, it is also possible to vary the grid bias for the stage in accordance with signal amplitude, and hence automatically control the gain.

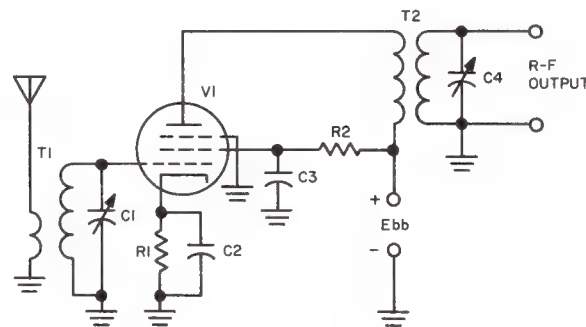Circuit Operation. The accompanying schematic shows a typical pentode signal-tuned r-f voltage amplifier circuit.



Pentode R-F Voltage Amplifier

In the schematic, T1 is an r-f transformer which matches the antenna to the control grid of the pentode. Tuning the secondary of T1 with C1 permits a larger signal to be developed across the Hi-Q tuned circuit, and applied to the grid, than if no tuning at all were employed. Resistor R1 and capacitor C2 form the conventional cathode bias resistor and bypass capacitor. (See the introduction to this section for a discussion of cathode bias.) Resistor R2 is the screen voltage-dropping resistor, and capacitor C3 is the screen bypass capacitor, which stabilizes the screen voltage and prevents it from being affected by the signal. The suppressor element of V1 is grounded directly. In some circuits it is connected externally to the cathode; in certain types of tubes it is connected internally to the cathode. R-F transformer T2 acts as the plate load and couples the output to the next stage. The output winding is tuned by C4 to the desired r-f output frequency. While C4 could be placed across the primary of T2 and the secondary left untuned, the conventional approach is to tune the secondary. With proper design the circuit is effective either way, and the secondary load is reflected into the plate circuit.

When a signal appears on the antenna, it is coupled through the primary of T1 to the tuned secondary (grid input) circuit. With capacitor C1 tuned to the frequency of the incoming signal, a relatively large r-f voltage is developed across the tuned circuit and applied to the grid of V1. The r-f signal, if unmodulated, consists of equal-amplitude positive and negative cycles occurring at the frequency to which the circuit is tuned. For the moment, any fading or noise is considered negligible and the input signal is considered to be of constant amplitude. On the positive half-cycle the grid bias is decreased, causing a plate current increase. On the negative half-cycle the bias is increased, causing a plate current decrease. This changing plate current flowing through the primary of output transformer T2 induces an output in the tuned secondary winding. This operation is practically identical with that of the Transformer-Coupled Audio Voltage Amplifier previously discussed in this section.

For ease of discussion, the signal is considered to be a sine wave with equal-amplitude positive and negative r-f swings. The average plate current flow, therefore, will be constant, and cathode bias may be employed. It is important to note that the r-f amplifier operating as the first stage in the receiver is

usually a small-signal amplifier. That is, the input voltage is on the order of microvolts, except in strong-signal areas; Therefore, a small signal voltage change causes only a very small bias change, and it is necessary to employ high-transconductance electron tubes to produce effective amplification. The pentode tube is well suited for this purpose, since it has both a high amplification factor and a high transconductance. By using a large value of inductance and a small tuning capacitance for the frequency involved, and also as small a coil resistance as is practicable, the tuning circuit exhibits a Hi-Q. Thus, its effective impedance is much larger than that presented by a tuning tank of low Q. Hence, a large input voltage is developed between grid and ground across the tuned circuit. With a step-up turns ratio from transformer primary to secondary, if closely coupled, a still larger input voltage is produced. The step-up of voltage in the transformer and the Hi-Q tuned grid tank increase the small input voltage before it is applied to the tube for further amplification. Normally, Class A bias is used to produce linear swings and to minimize distortion. With very small input signals however, operation occurs over the curved portion of the plate-current grid-voltage characteristic. For example, typical bias values range from 0.5 to 1 or 2 volts maximum. Thus, the tube is clearly operating very close to zero bias, and the E_g-I_p curve in this region is never straight. This results in uneven positive and negative swings, and this produces distortion. For r-f stages, a larger bias and a more linear portion of the curve are used.

When the input signal is modulated, each r-f cycle may be of different amplitude; thus, considering each cycle to be amplified linearly, the modulation is likewise amplified proportionately producing an over-all modulation envelop which is almost identical with that of the original modulation. A slight difference (usually a reduction in modulation factor) exists; this is produced by distortion, which will be discussed in more detail Failure Analysis.

When small values of bias are used in the input stage and large signals are applied, distortion occurs because the signal is partially clipped off in the plate circuit. In addition, grid current flow creates a low-resistance (shunt) path between the grid and the cathode, which effectively lowers the grid tank Q. As a result, the input signal and over-all amplification of the stage are reduced. Therefore, it is common practice to employ a variable cathode resistor for

manual gain control, or to provide some means of automatic bias (gain) control. For a complete discussion of AGC circuits, refer to the Special Circuits Section of this Handbook.

Failure Analysis

No Output. Loss of plate, screen, or filament voltage, or a defective tube, can cause no output. The voltages can be checked with a voltmeter, and an open filament can sometimes be observed by noting that the tube is not illuminated and feels cold to the touch. If the plate, screen, and filament voltages are normal, the tube may be defective. If the tube checks good, check the input transformer by applying a modulated voltage from a signal generator to the input terminal and observe whether there is an input voltage on the grid (use a VTVM or an oscilloscope and r-f probe as the indicator). An open screen resistor (R2) will be indicated by the lack of screen voltage. Similarly a shorted screen capacitor (C3) will drop the screen voltage to zero and cause R2 to heat abnormally. The short circuit condition may be observed visually by smoke from or discoloration of the resistor. An open or shorted cathode bypass capacitor (C2) will not necessarily produce a no-output indication; however, an open bias resistor (R1) usually will. In fact, on very small signals either trouble may not be obvious or may show only as a slight increase in distortion. If tuning capacitor C1 or C4 is defective, depending on whether it is short-circuited or open-circuited, there may be no output or a considerable reduced output, respectively. Since each capacitor is shunted by a coil, it will be necessary to disconnect one end to check for capacitance or a short. Where an open coil is suspected, it can be checked for continuity with an ohmmeter.

Reduced Output. When there is an open circuit in either transformer T1 or T2, if sufficient capacitive coupling exists between the windings (especially at the higher frequencies), the output will be reduced, rather than nonexistent. On the other hand, at the lower r-f frequencies the output may be reduced practically to zero. A check with an ohmmeter will determine whether there is continuity in the coils. A change in the value of screen resistor R2 to a higher value will lower the screen voltage and reduce the output. Likewise, a reduced plate voltage caused by a high-resistance joint or winding will lower the output. Low output can also be caused by a defective tube, that is, a tube with low filament emission or an in-

ternal short. If the tube has an internal short, it will draw a heavy cathode current, thus producing a much greater than normal bias and reducing the output accordingly. A defective antenna or transmission line can cause a weak input signal and an apparent lack of output. In this instance the circuit will check normal in every respect, and changing tubes will make no difference. Substitute another signal from a different antenna, if possible, or apply an input from a signal generator with a calibrated attenuator. If a large value of attenuation is required to reduce the output signal to a low value or zero, the stage is operative and the trouble is external.

Distorted Output. Improper plate or screen voltage will cause a certain amount of distortion. While improper bias will also cause distortion, it will depend to a great extent on the tube used, the input signal amplitude, and the value of bias. Intermodulation between the side (modulation) frequencies of a modulated input signal will create a slight amount of distortion due to the curvature of the tube E_g-I_p characteristic. Normally, special test equipment is required to determine this condition; besides, it is of little consequence except to the designer. Likewise, a change in the modulation factor is caused by the fact that the individual modulated r-f cycles are of different amplitudes. Thus, the larger signals are amplified more than the smaller signals because of the curvature of the tube characteristic; this is also a design problem. Hum distortion may occur because of induced hum on the carrier at low signal levels. This is normally minimized by proper filament bypassing and plate supply filtering, together with screen bypassing. There should be no hum distortion in the equipment as originally supplied, except where the filters or bypass components are defective. The use of an oscilloscope will show where the hum appears and usually localize the source.

Curvature of the tube characteristic can also cause distortion which appears in the form of intermodulation between two strong applied r-f voltages, one of which may be outside the range of the tuning circuit; when sufficient to be annoying in the reception of the desired signal it can be eliminated only by attenuating the undesired frequency. Intermodulation distortion is recognized by the fact that the distortion occurs to the modulation frequencies of signals which are normally loud and clear. It should not be confused with selective fading, which also causes frequency distortion in AM reception.

Another prevalent form of distortion which occurs when two strong modulated signals are nearby is cross modulation. This actually causes modulation of the carrier of the desired signal by that of the undesired signal. Cross modulation is recognized as a form of "monkey chatter" heard in the background of broadcast stations, particularly where strong adjacent-channel signals are present. It is also recognized in voice communication by the clear, undistorted, but weak reception of the undesired station superimposed on the desired station. In the pause between syllables and words, the cross-modulating station can be heard clearly. The interfering signal may not be within the tuning range of the receiver used, although usually it is. Here again, the fault is due to curvature of the tube characteristic, and is eliminated by attenuation of the unwanted signal, either by selectivity or some other means. While usually a design problem, these types of distortion are mentioned here because it is possible in certain instances that design specifications may be overridden by circumstances beyond the control of the technician, such as when the ship is temporarily located close to another station. In this event, needless time might be sent looking for trouble within the circuit.

If too great a selectivity is employed, the sidebands will be partially clipped from a modulated signal, resulting in a form of frequency distortion. This can result from an incorrect setting of a selectivity control or from regeneration within the stage, which will produce sharper tuning. Regeneration can be produced by operating with two low a screen voltage or insufficient screen bypassing, and by improper lead-dress when components in the grid or plate circuit are replaced.

CASCADE R-F AMPLIFIER (ELECTRON TUBE)

The cascade r-f amplifier is generally used in tuned radio frequency receivers to supply high gain and selectivity before detection.

Characteristics.

- Uses a number of stages connected in cascade.

- Operates Class A for linear amplification.

- Usually operated self-biased, although fixed bias may be used.

- Uses a single tuned stage in the grid circuit of each tube, for selectivity.


- Uses pentode tubes for high gain, although any tube type may be used.

Circuit Analysis.

General. The cascade r-f amplifier is a conventional amplifier whose output is connected to the input of a similar stage, which, in turn, is connected to another similar stage. Thus, the outputs are cascaded from one stage to the other, and a number of similar stages are used to provide high amplification. Usually three tuned stages are used, and the amplification varies as the cube of the single stage gain (a gain of 10 per stage produces a total gain of 1000). While it is not necessary that the stage be tuned (untuned stages may also be cascaded), a higher gain is obtained from the tuned stage than from the untuned stage. Hence, the untuned r-f amplifier is generally used only for special, wide-band applications. Likewise, it is apparent that either triodes or pentodes may be employed. However, with triodes less over-all gain is obtained and the high grid-to-plate interelectrode tube capacitance produces inherent instability. Thus, to avoid the problem of neutralization and to achieve high gain per stage, the pentode tube is usually employed.

Circuit Operation. The schematic of a typical cascade r-f amplifier is illustrated in the accompanying figure.

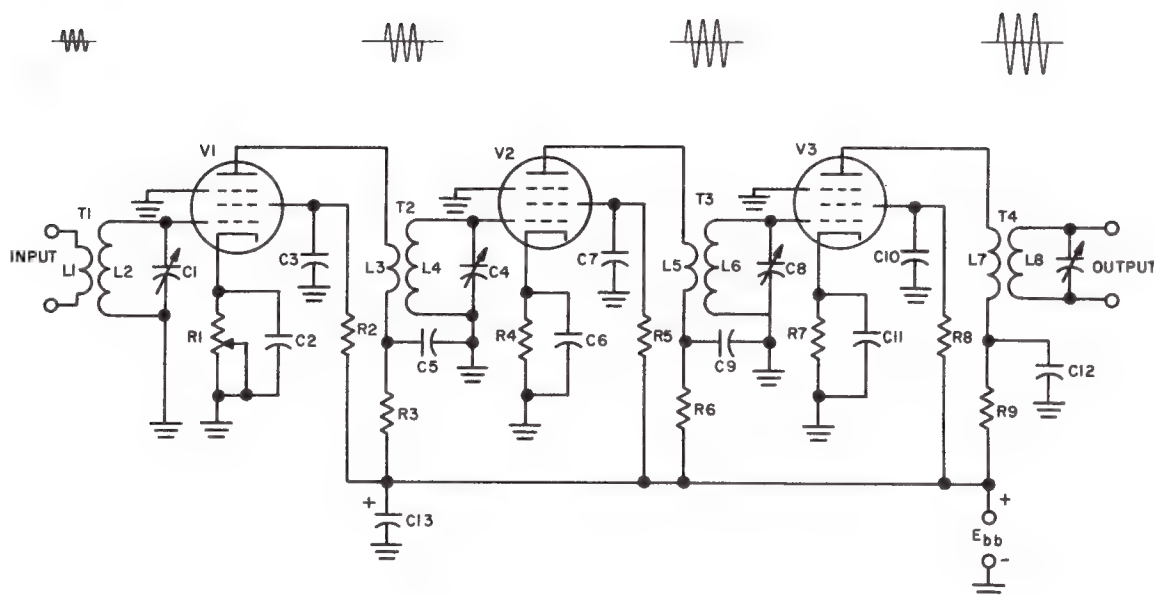Three stages of r-f amplification are provided, using transformer coupling for convenience. While all stages are basically identical, the component values are not always the same. Usually the bias, plate, and



Typical Cascade Three-Stage R-F Amplifier

screen voltages are different in the various stages, or at least they differ between the first and the remaining stages. Since each stage handles the output of the preceding stage, the bias is usually the smallest on the first stage and the largest on the last stage; the large bias on the last stage is necessary for this stage to handle the large output voltage swings developed in the first and second stages. Since the first stage plate swing is the smallest, it can operate with a lower plate voltage and thus produce less "shot noise", to provide a better signal-to-noise ratio without loss of gain. The final stage, of course, has the largest plate voltage. The screen voltage is usually the same for all stages, except perhaps the first stage.

In the schematic, T1, T2, T3, and T4 are tuned radio frequency transformers. T1 is the input transformer, and T4 is the output transformer; T2 and T3 are interstage transformers. The primaries of the r-f transformers are untuned, while the secondaries are tuned by variable capacitors. Although not shown in the schematic, these tuning capacitors are mechanical ganged together for single-knob tuning; otherwise, each of the tuning capacitors would have to be tuned separately for maximum response when a different

frequency is selected. The use of a parallel-tuned circuit provides a high impedance at the grids of V1, V2, and V3, thus producing high gain and good selectivity. Resistors R2, R5, and R8 are screen voltage-dropping and decoupling resistors, which are bypassed to ground for rf by screen bypass capacitors C3, C7, and C10, respectively. Resistors R3, R6, and R9 are plate voltage-dropping and decoupling resistors for tubes V1, V2, and V3, respectively, and are bypassed by capacitors C5, C9, and C12. Cathode (self) bias is supplied by resistors R1, R4, and R7 for V1, V2, and V3, respectively. The cathode bias resistors are bypassed by capacitors C2, C6, and C11. (See the introduction to this section for a discussion of cathode bias.) Capacitor C13 is a large filter capacitor used to minimize hum components in the supply source and possible impedance coupling effects due to the use of a common supply. The input may be from an antenna or other source, and the output can be applied to other r-f stages or to a detector.

When a signal is applied to the primary of the input transformer, signal current variations through L1 produces a varying magnetic field which induces a voltage in secondary L2 by transformer action. When

tuned to resonance by C1, a large voltage is developed between the grid of V1 and ground, across the tuned circuit, and the turns ratio between L1 and L2 determines the impedance presented by the input to the V1 grid. In the case of an antenna input, a step-up turns ratio matches the low antenna impedance to the high impedance of the parallel-tuned circuit, for efficient power transfer. Assume for the moment that the r-f signal is increasing in a positive direction. The instantaneous positive grid swing produces a large instantaneous current flow in the plate circuit. This plate current flowing through the impedance presented by primary coil L3 produces a voltage drop across the T2 primary, and the changing value of plate current also induces a voltage into secondary L4. When L4 is tuned by C4 to the same frequency as the input signal, a large voltage is also developed across this tuned circuit and is applied to the grid of V2. Stage V2 operates in a similar manner and supplies an output to stage V3, which further amplifies the signal and produces a final negative output from T4. (An even number of stages would produce an output of the same phase or polarity as the input.)

When the input signal decreases, the plate current through V1 is reduced, and the reduction in current flow through L3 induces a smaller input voltage in V2, and likewise in V3, with a resultant smaller total output. With each tube operating Class "A", equal positive and negative input signals produce amplified output signals of the same shape, but of larger amplitude and opposite phase. Cathode resistor R1 is variable to provide manual control of the first stage bias, and allow adjustment to prevent strong input signals from driving the tube to saturation and producing distortion.

As can be seen from the above explanation, operation of the cascade r-f amplifier is similar to that of any other pentode r-f amplifier (discussed previously in this section), but with each stage designed to handle the full output of the preceding stage. The cascade r-f amplifier is the counterpart of the tuned interstage (i-f) amplifier, discussed later in this section. It differs principally in the fact that it operates at a higher frequency, is continuously tunable over a large range of frequencies, and has somewhat less selectivity because only single-tuned circuits are used, with slightly less gain (depending upon the operating frequencies and number of stage employed). While simple transformer-coupled stages are shown and dis-

cussed, it is possible to use capacitively coupled stages, or other bandpass arrangements.

The suppressor grid is shown grounded in the schematic to minimize plate-to-grid coupling through the interelectrode tube capacitance, and to provide better shielding between the input and output; thus, at high radio frequencies, the possibility of oscillation due to regeneration is rather remote, so that no neutralizing arrangement is necessary. At the lower radio frequencies, the suppressor may be connected to the cathode without causing undesirable effects, since the r-f feedback is less.

Failure Analysis.

General. The failure analysis for each stage of the cascade r-f amplifier is essentially the same as that for the single-stage pentode r-f amplifier discussed previously. In fact, the first-stage components of the cascade amplifier and the components of the single-stage amplifier are identically symbolized, except that the plate decoupling filter (R3 and C5) was not included in the single-stage amplifier. Therefore, this failure analysis will be confined to generalities concerning multistage circuits.

No Output. Any trouble which produces a no-output condition in a single stage will result in either a similar condition or a considerably reduced output in the multistage circuit. Because of the high gain and the possibility of signal feed-through to a following stage by stray capacitive effects at radio frequencies, it is possible for a single stage to be inoperative and still have a substantial output from cascaded stages. In this special case, the loss in amplification can be observed by inserting an input from a signal generator and noting the output. Then, by successively applying the signal to the following stage inputs (grids) again observing the output produced by the signal generator, it will be noted that the output suddenly increases when the defective stage is passed. Ordinarily, the output would decrease from stage to stage, requiring a constantly increased signal generator output as each stage is passed. If plate decoupling filter R3, C5, or R6, C9, or R9, C12 fails (either the resistor opens or the capacitor shorts), the plate voltage of the affected stage will be zero and no output will be obtained (neglecting the possibility of stray coupling).

Check the plate, screen, and cathode voltages to ground with a voltmeter; any abnormal voltage will localize the trouble to a specific stage and to the parts

associated with that tube element. Be certain to check the supply voltage also; there may be a defect in the power supply. With normal voltages and no output, either an r-f transformer or a tube is defective.

Low Output. High bias, low plate or screen voltage, and a defective r-f transformer or tube can cause the output to be low. First check the plate, screen, and cathode voltages of each tube to verify that the dc bias and operating conditions are normal. Connect an output inductor to the output terminals, and insert a strong signal (within the tuning range) from a signal generator to the grids of V3, V2, and V1, respectively, (use a dc blocking capacitor in series with the generator output). As the generator is moved from stage to stage, adding additional amplification, it should be necessary to decrease the generator output to maintain a constant output indication; otherwise, a lack of gain is indicated. If an oscilloscope and an r-f probe are available, the signal generator can be left connected to the input, and the signal traced from the grid to the plate of each stage with the r-f probe. With the generator set to a specific frequency, tune the tank capacitors about this frequency. An increase in amplitude should be obtained as the signal is peaked; if an increase is not obtained, the tuned circuits are probably defective. Since the screens and cathodes are grounded (for rf) through bypass capacitors, no signal will be observed at the screen or cathode unless one of these capacitors is inoperative. Remember that placing the r-f probe across a circuit adds the probe capacitance, and will cause detuning of the circuit at radio frequencies. Best results are obtained when the signal or output is inserted in the circuit immediately ahead, or taken immediately after the point to be checked. For example, if the output of the first stage is to be checked, the input should be applied to the grid of V1 and the output measured across the T2 secondary. If the signal is applied to the plate of V1 instead, and measured at T2, the loading effects of the signal generator will affect the tuning of T2 and, therefore, the V2 gain. By inserting the signal at the plate of V2, only r-f transformer T2 will be checked, whereas by inserting the signal at the grid of V2, both the amplification of V2 and the operation of T2 will be checked. Loss of gain due to aging of tubes over a long period of time can occur in multistage (cascaded) r-f amplifiers, and may not be apparent until the reduction is severe. In this case all indications and voltages appear normal, except that

the equipment does not seem to be performing satisfactorily and most signals are weak. Where maintenance standards are provided for the equipment, a simple comparison will reveal the deficiency. It should be kept in mind that each stage should produce additional gain; therefore, any stage showing no gain is probably defective.

Distortion or Poor Selectivity. Low bias or plate voltage will cause distortion, as will low screen voltage. Since the screen voltage fixes the range of plate swing, it has more effect in producing distortion than a similar change in plate voltage. Driving the plate voltage below the screen voltage will produce distortion, and in some instances cause a negative resistance condition resulting in unwanted self-oscillation. In multistage amplifiers, the possibility of cross-modulation and intermodulation distortion exists to a greater extent than in single stages; however, the causes are the same.

In tuned radio frequency amplifiers a strong signal tends to block the amplifier and broaden the response curve, so that cross modulation effects are not as noticeable. By adjustment of the manual gain control, the effective amplification can be reduced to prevent overloading on strong signals; thus, the nonlinearity introduced is avoided, and any cross modulation and intermodulation distortion are minimized. Poor tracking of ganged tuning capacitors can also produce either a loss of gain or distortion by cutting off frequencies outside the pass band of the individual stage. However, single-tuned r-f stages are usually so broad in tuning that slight differences (in bandpass or resonance) merely broaden the over-all response curve, so that only poor selectivity results. Proper adjustment of trimmer and padding capacitors will restore the initial selectivity, but cannot compensate for poor design.

CASCADE R-F AMPLIFIER (ELECTRON TUBE)

Application.

The cascode r-f amplifier is employed as a high-gain, low-noise r-f input stage to high-frequency receivers.

Characteristics.

Two triodes provide the equivalent maximum gain of a pentode with reduced noise.

Noise equivalent is equal to that of a single triode stage.

Grounded-grid stage stabilizes the circuit so that neutralization is not normally required.


Uses Class A self-bias, although fixed bias can be used.

Circuit Analysis.

General. The cascode circuit consists of a single, conventional grounded-cathode input amplifier, connected in series with a grounded-grid amplifier stage which contains the output load. In most instances the two tubes are triodes, although they could be triode-connected pentodes or a combination of pentode

input and triode output. To obtain the low-noise feature, the triode output must be used. This circuit, like the grounded-grid circuit discussed previously, is usually employed at frequencies where the effective amplification of pentode and beam power tubes drops off as a result of high-frequency effects. It is seldom used at frequencies lower than 30 MHz, since equivalent or better performance can be obtained with careful design by using a single pentode tube.

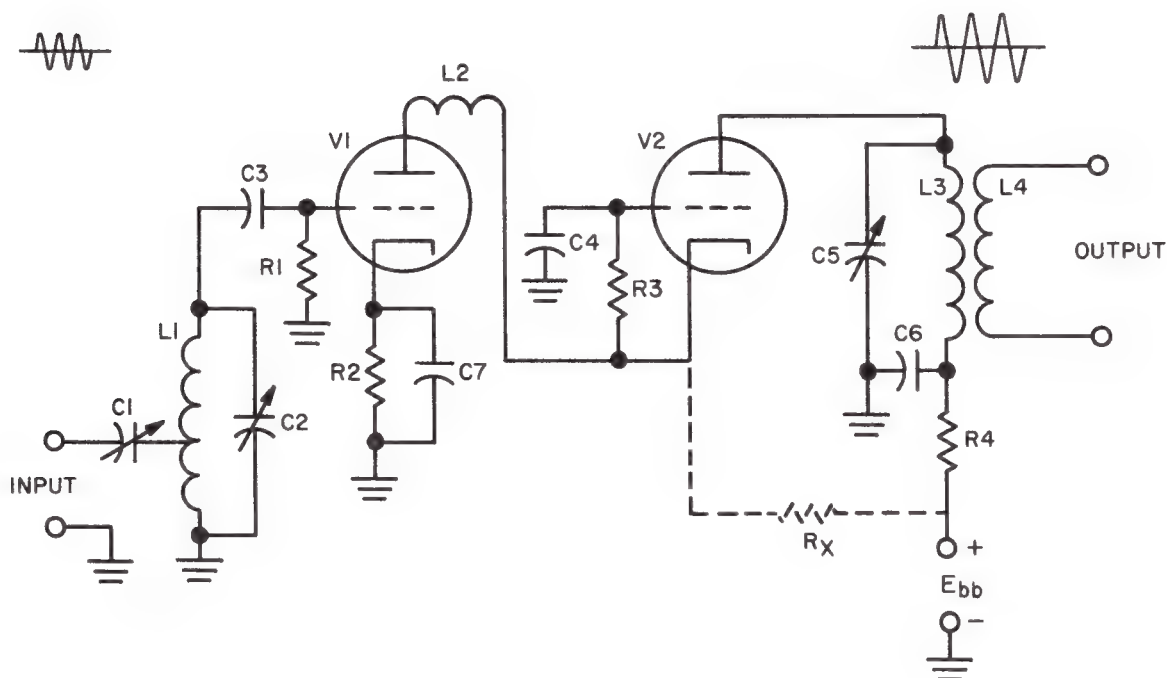Circuit Operation. The accompanying schematic illustrates a typical triode cascode r-f amplifier circuit.



Typical Cascode R-F Amplifier

In the schematic, C1 is a coupling capacitor tapped on the lower end of tank coil L1. It is made variable to provide a slight amount of input tuning. Input tank circuit L1, C2 is coupled through capacitor C3 to the grid of V1. The low reactance of C3 to the r-f signal allows maximum signal (developed across the tank) to appear on the V1 grid and prevents the dc shunting of the grid signal to ground through L1. Cathode bias is provided by R2 bypassed for rf by C7, and R1 is the grid-return resistor. Tube V1 is connected as a conventional grounded-cathode am-

plifier, with V2 acting as the plate load impedance. Inductor L2 helps match the low input impedance of grounded-grid stage V2. The grid of V2 is returned to the cathode by R3, which develops contact bias, and is grounded for rf by C4. The plate load of V2 consists of the parallel-tuned tank, L3, C5, with output winding L4 inductively coupled to it. Resistor R4 is a plate decoupling and voltage dropping resistor, bypassed by C6. This series-feed plate arrangement allows the rotor of C5 to be grounded to avoid body capacitance effects when tuning.

In the absence of a signal, each tube is resting and drawing its static value of screen, plate, and cathode current. Electron flow is from ground through R1, R4, or R7, through the grid and the screen to the plate, through primary coil L3, L5, or L7 and plate resistor R3, R6, or R9, back to the supply. The cathode current is the total space current through the tube, including both the screen and plate current (also including grid current, if allowed to flow), which biases the grid negative because of the voltage drop developed across the cathode resistor. Similarly, screen current flow through the screen resistor produces a voltage drop with a polarity which opposes the source voltage, and thus reduces the screen voltage to the desired value. Screen bypass capacitor C3, C7, or C10 bypasses the r-f current variations to ground (when a signal appears), so only dc current can flow through the screen resistor. The quiescent value of plate current flowing through transformer primary L3, L5, or L7 is steady and this produces no output. However, in flowing through plate resistor R3, R6, or R9, it produces a voltage drop with a polarity which opposes the supply voltage, thus reducing the effective plate voltage to the desired value. Capacitor C5, C9, or C12 bypasses any r-f current variations to ground (when a signal appears) so that only direct current flows through the plate resistor. Thus, any r-f variations cannot change the dc plate voltage. With no signal applied, there is no output from any of the stages (except for slight thermal variations of plate current which produce noise); hence, there is no final output at T4.

Operation of the cascode circuit can be better understood if operation of each tube is considered separately, and then operation of the two tubes combined. V1 represents a conventional triode r-f amplifier using cathode bias and shunt grid feed, with the plate directly connected to the next stage. The plate voltage for V1 is obtained through V2, which acts simply as a dropping resistor. Thus, assuming equal plate currents and plate resistances, the plate voltage of V1 is half that applied to V2 less the cathode bias of V1. Cathode bias is supplied by R2, since the total currents of V1 and V2 flow in series through it. Signal current variations do not affect the bias because R2 is bypassed for rf by C7. (See the introduction to this section for a discussion of cathode bias.) Bias is selected so that plate current flows at all times (Class A), and so that V1 operates over the linear portion of its grid-voltage, plate-

current transfer characteristic curve. The grid of V1 is returned to ground through R1 so that electrons cannot accumulate, bias-off the tube, and block operation. The value of R1 is large enough that none of the input signal is shunted to ground. Thus, when an input signal appears on C1, it is coupled into the tuned tank consisting of L1, C2. By tapping C1 down on tuning coil L1, autotransformer action is obtained to step the low antenna impedance up to the large value of parallel impedance offered by the tuned tank. Thus maximum power transfer is obtained between the antenna and the tank. The input signal appears as an r-f voltage across the tuned input circuit, and is applied to the V1 grid through coupling and blocking capacitor C3. Since C3 is in series with the input, the grid of V1 is isolated from the input circuit as far as dc is concerned, but is connected for rf.

When an input signal is applied, it is coupled through C1 to the tank L1, C2, which at resonance provides an increased signal to C3 and develops a voltage across R1, which, in turn, is applied to the grid of V1. Assuming that the input signal is increasing in a positive direction, the grid bias on V1 is decreased and causes the cathode and plate current to increase. The instantaneous increase of cathode current has no effect on R2 since it is bypassed by C7. However, the increased plate current flow through L2 (and tube V2) drives the cathode of V2 more negative, and since the grid of V2 is held at ground potential the effect is as though a positive voltage were applied to V2 grid. Thus the plate current of V2 also rises and the drop across the plate tank develops a tank current flow in L3, C5 which is inductively coupled to the output by secondary coil L4. With the output winding connected in-phase, an output voltage that is in phase with the input signal is produced.

Conversely, when the input signal to V1 is operating over the negative half-cycle, the bias on V1 is increased by the input signal, and plate current flow in V1 is reduced. The reducing plate current flow in V1 allows the plate voltage to rise towards the supply value, driving the direct-coupled cathode of V2 in a positive direction. When V2 cathode becomes more positive, the plate current of V2 is reduced, while the plate voltage rises and induces an increasing voltage in the tank. When connected in-phase the tank output is negative during a negative input signal to V1. Since both V1 and V2 are connected in series, the output voltage is only half of what it normally


would be with one tube. The noise, however, is only one quarter of that produced by a single high-gain tube. So that a large reduction in tube noise occurs in the amplified output signal. In addition to noise reduction, the circuit is prevented from oscillating (stabilized). This action and the effect of circuit loading are explained in the detailed functioning of portions of the circuit as discussed below.

Assume for the moment that the input signal is again going positive. The bias on the V1 grid is momentarily decreased and an increased plate current momentarily flows. In flowing through L2 the current develops a small emf, which is out-of-phase with the voltage fed back from plate to grid through the plate-grid interelectrode capacitance, and helps prevent self-oscillation of V1. When the input signal goes negative, the bias on V1 is momentarily increased and a decreased plate current flows. Normally, in the conventional amplifier, this change in plate current through the load produces a varying voltage drop which is the output. However, the plate load for V1 consists of V2 and its associated tank circuit, L3, C5. In addition, the reflected load from output winding L4 affects C5 tuning and the value to total impedance presented to the V2 plate. Since V2 is connected in series with V1, the plate resistance of both tubes in series is effectively paralleled with the plate load of V2. The input resistance of V2, the grounded-grid stage, also shunts the output of V1 to ground, but is increased by the series reactance added by L2. Thus, L2 also helps match the V2 grid to the V1 plate. Because V2 is direct-coupled to V1, any signal appearing on the plate of V1 also appears on the cathode of V2, and, since the grid of V2 is grounded, in effect appears as an oppositely polarized signal on the grid. Thus, a positive output on the cathode of V2 appears as a negative signal on the grid of V2, and causes a decrease in the plate current of V2. Conversely, a negative cathode signal appears as a positive grid signal, and causes an increase in the plate current of V2. Since the input and output of the grounded-grid stage are in phase, both tubes operate in the same direction. That is, as the current of V1 increases, so does the current of V2 (both in the same direction). This is necessary since both V1 and V2 are series-connected, and the same current flows through both tubes. When the plate current of V2 increases, a voltage drop appears across tank coil L3, and an output voltage is induced in coupling coil L4 through transformer action. Similarly, when the plate current

decreases, an output voltage of opposite polarity is developed.

The discussion above covers the individual operation of the separate stages of the cascode amplifier without considering the effects of combined operation. To complete the discussion of circuit operation it is now necessary to examine the manner in which these amplifiers operate when connected in series across the plate supply. The normal cascaded amplifier operates in parallel with the supply, and with its grid connected effectively in series. The cascode stage operates in exactly the opposite manner. Both tubes are fed their plate voltage in series, so that the plate resistance of one tube acts as a dropping resistor for the other tube. Although one stage is grounded-cathode and the other is grounded-grid, their grids are effectively connected in parallel.

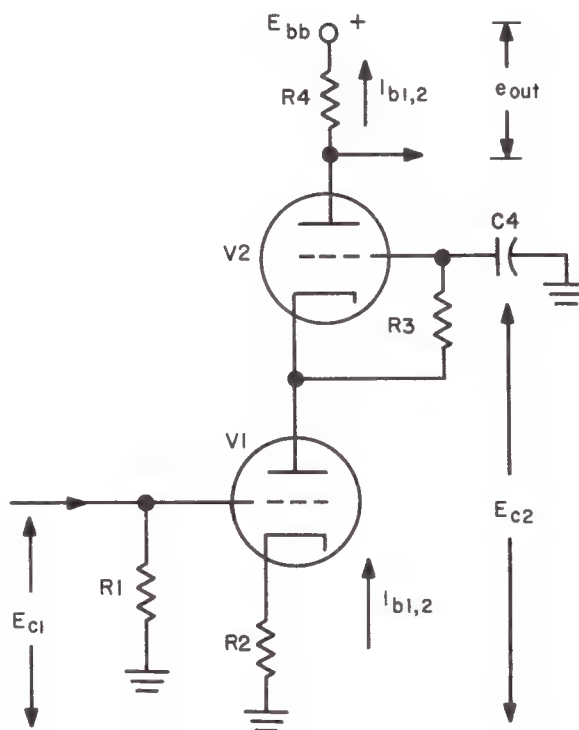The simplified equivalent schematic below shows the dc representation of the circuit. It is clear that there is no dc connection between the grid and ground or between the cathode and grounded of V2 except through V1.



Simplified Equivalent Cascode R-F Amp. Circuit

With no signal applied, the tubes are resting in a quiescent condition, with the same plate current flowing through both V1 and V2. The plate voltage of V1 is determined by the drop across V2 and R4, and is further reduced by the amount of cathode bias developed across R2. As the V1 plate voltage increases (with a signal), the V2 plate voltage decreases, since the total supply voltage does not change. The V1 grid voltage is the cathode voltage drop produced by the total cathode current times cathode resistance R2, plus any signal-excitation voltage. With a practically constant cathode current, this bias voltage changes very little. When the plate current through V1 decreases (because of a negative-swinging input signal), the plate voltage of V1 increases; at the same time the V2 grid voltages increases, since the plate voltage increase of V1 is applied directly to the cathode of V2. Thus, the current through V2 is caused to decrease also to correspond with that of V1. Any increase or decrease in plate current through V1 and V2 (caused by the input signal) produces a corresponding increase or decrease in output voltage across load resistance R4. This load resistance is the impedance offered by the tuned tank at the frequency of the input signal. The result is to provide a relatively constant amplification through V1 and V2, equivalent to that of a single triode tube operated with a reduced plate voltage.

Although maximum gain is obtained, since it is produced at a relatively low plate voltage with a minimum change in plate current, less noise is produced than for an equivalent gain obtained with a large change in plate current. The isolation provided between the input and output circuits by grounded-grid stage V2 minimizes any feedback between the input and output. Therefore, self-oscillation is prevented and neutralization is unnecessary. (Although in some circuit versions V1 is neutralized, this is not done to prevent oscillation, but rather to increase the input admittance so that high gain may be obtained.) by maintaining a relatively constant plate current, the circuit produces a very linear output signal, because the gain is independent of plate resistance and equal to the tube amplification factor at all times. Thus, the normal dropping off in effective amplification at high radio frequencies is overcome by the cascode circuit. The decrease in noise output and the increased gain at high frequencies make this circuit most useful, and provide a much better signal-to-noise ratio than any other circuit combination.

The reason for the decreased noise is not the reduction in shot-effect alone (random variations in the rate of electron emission from the cathode produce a hissing noise called *shot effect*), because of the low plate voltage used. The decreased noise is also due to a reduction in the "induced grid noise" and the "flicker effect". The induced noise is reduced because of the low effect impedance of the grounded-grid circuit. The flicker effect, which occurs because of small temperature changes in oxide-coated cathodes, is reduced by holding the plate current relatively constant. Thus, the space charge within the tube remains relatively large and constant, and any increase caused by flicker effect is swamped out, since any increase in the negative space charge returns the stray electrons to the cathode rather than to the plate.

The combination of a cascaded grounded-cathode and grounded-grid stage is also often used and referred to as a *cascode amplifier*. This change in circuit is accomplished by adding plate voltage dropping resistor R_x , shown in dotted lines in the previous schematic. This circuit is not two series stages with a common plate voltage; it is simply two separate circuits connected in cascade. Although constant gain is not achieved by keeping the plate current in V2 relatively constant, almost identical results are obtained. In fact, the cascaded form of cascode circuit provides additional gain, since each stage operates separately as an amplifier. However, the flicker effect is not eliminated, and as each stage usually operates at a slightly higher plate voltage than each stage in the original cascode circuit, slightly more shot noise is produced. Because of the increased signal gain, however, the increase in the noise figure is not very evident, since the signal tends to override the noise.

Failure Analysis.

General. The failure analysis applicable to the grounded-cathode r-f amplifier and the grounded-grid r-f amplifier may be used as a guide, particularly where the cascaded form of cascode circuit is used. Since the tubes normally have their plates series-connected, the following analysis applies only to the original cascode circuit.

No Output. In the series plate circuit consisting of R4, L3, V2, L2, V1, and R2, any open circuit will prevent operation and thus cause loss of output. Normal plate and cathode voltages will indicate either no signal applied, a defective tube, or an open input or output circuit. Always check the supply voltage

when checking plate and bias voltages, to verify that the supply is operating normally. If the input circuit is defective, placing the antenna (or other input) directly on the grid of V1 should produce an output. A resistance check of L4 will verify continuity, but not necessarily indicate a short circuit since the coil resistance is usually less than 1 ohm in either case. With an oscilloscope and r-f probe, the signal can be checked at the plates of both tubes; if the signal is present, L4 is defective. If R3 opens, the grid of V2 can become blocked by the accumulation of electrons on C4. A resistance check will indicate whether R3 is of the proper value. If either C1 or C3 is open, no signal will be applied to the V1 grid. Use an in-circuit capacitor checker or temporarily add a capacitor equivalent in value to C1 or C3 to determine whether an output can be obtained. If the tubes are suspected, check them in a tube checker. A no-voltage indication on the plate of V2 can be caused by a shorted bypass capacitor C6. If C6 is shorted, the entire plate supply will be dissipated across R4, causing it to overheat, smoke, and possibly burn out.

Low Output. Low plate voltage, high grid bias, or a defective tube will produce a reduced output. The plate and bias voltages can be checked with a voltmeter. If C7 is open, the output will be reduced because of cathode degeneration. Likewise, if either C2 or C5 is detuned or open, the output will be reduced. If C1 or C3 is defective but stray capacitive coupling exists, low output may also be obtained. Use an in-circuit capacitance checker to check the capacitors. If grid return resistor R1 or R3 is open or increases in value with age, it is possible for the associated tube to block or have reduced output after a strong signal. Use an ohmmeter to check the values of R1 and R3 when in doubt. Since the output is an r-f signal, L4 can be open and yet a low output be obtained through stray capacitive coupling.

Distortion or Poor Selectivity. The cascode amplifier is subject to the same causes of distortion and poor selectivity as other types of r-f amplifiers. Low bias or plate voltage will cause clipping and distortion. Use a voltmeter to determine whether the proper bias and plate voltages are present. High resistance in the tuned circuits, caused by poorly soldered joints, will cause board tuning and poor selectivity. Such joints in the antenna or transmission line system can cause rectification of the r-f signal and produce spurious responses or beats which might be misinterpreted as distortion. Changing the antenna will usu-

ally cause this condition to disappear. When in doubt, insert a modulated signal from a signal generator tuned within the range of operation. Use an oscilloscope and r-f probe to follow the signal from input to output. Any distortion will be visible as a change in pattern on the scope. Any cross-modulation effects will be due to overloading by strong local signal, and can be eliminated only by attenuating the signals or by inserting circuits that provide additional selectivity before the input.

TUNED INTERSTAGE (I-F) AMPLIFIER (ELECTRON TUBE)

Application.

The tuned interstage (i-f) amplifier is universally used in superheterodyne receivers to supply high r-f amplification and the desired selectivity.

Characteristics.

Uses pentode-type electron tubes to obtain high voltage gain.

Uses double-tuned tank circuits to obtain sharp selectivity.

Uses radio-frequency transformers to isolate input and output circuits, for voltage step-up and impedance matching.

Operates Class A, self-biased to minimize distortion, although fixed bias can also be used if desired.


Uses a number of similar stages connected in cascade to obtain greater gain and selectivity.

Employs fixed tuning, adjustable over a narrow range, for exact alignment of each stage.

Circuit Analysis.

General. The tuned i-f amplifier may consist of a single stage, or as many as six or more cascaded similar stages to obtain the desired amplification and selectivity. Generally speaking, one to two stages are used for radio broadcast reception, while two to four stages are used in selective communications receivers, and six or more stages are used for radar, television and microwave reception. The intermediate frequency chosen usually determines the number of stages. The lower frequencies, such as 50, 175, and 250 kHz, produce more amplification and better selectivity than 450 kHz; at 21 or 44 MHz (as in TV applications) or at 30 or 60 MHz (as in radar applications), less gain per stage is obtained, and the response curves are broader, so that more stages are


needed. In addition, the bandpass requirement introduces another factor, since a simple 5 to 10 kHz bandpass can be obtained with a few tuned circuits, whereas a broad bandpass of 4 to 5 MHz, with sharp cutoff, which is required in TV and radar receivers, requires a number of stagger-tuned stages. The bandpass is measured at the half-power points of the receiver response curve, that is, at 70.7 percent amplitude each side of the i-f center frequency. For example, if we have an i-f amplifier output of 100 volts at the center intermediate frequency, and it drops to 70.7 volts when the amplifier is detuned 5 kHz each side of resonance, the amplifier bandpass is 10 kHz, as illustrated in the accompanying figure.

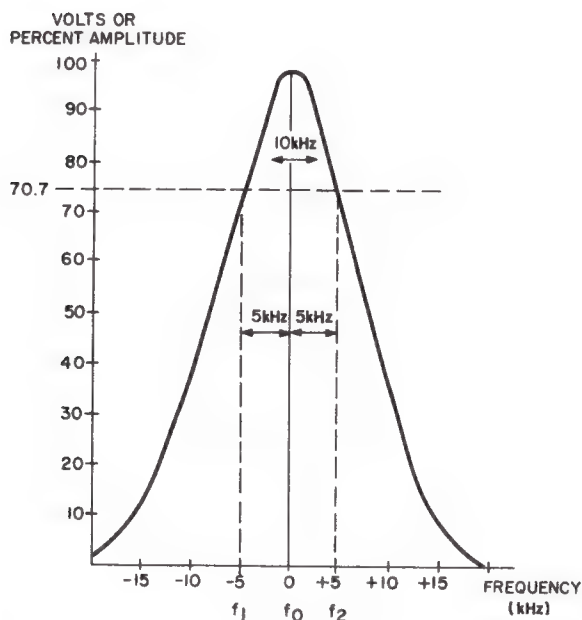

Typical I-F Response Curve


The manner in which the shape of the response curve (selectivity) is changed by stagger-tuning (each tank tuned to separate frequencies) to achieve a broad

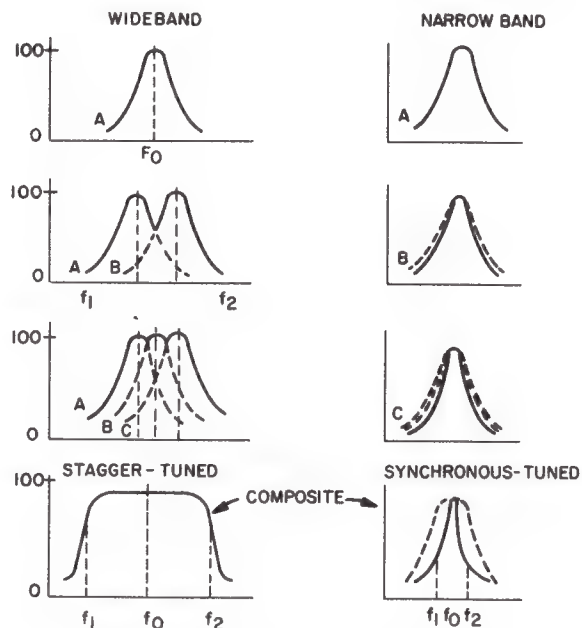bandpass, as compared with synchronous tuning (each tank tuned to the same frequency), assuming optimum coupling between the i-f primary and secondary coils, is shown in the accompanying illustration.



Stagger-Tuning and Synchronous-Tuning Response Curves

Circuit Operation. The schematic of a typical two-stage i-f amplifier is shown in the accompanying illustration. The dashed line divides the circuit into two separate stages. Note that in the inter-stage amplifier T2 is common to both stages. Thus, T2 matches and couples the output of V1 to the input of V2 for efficient signal transfer. Since the stages are operating Class A, no grid current flows and power transfer is not a real concern; however, maximum voltage transfer is important.

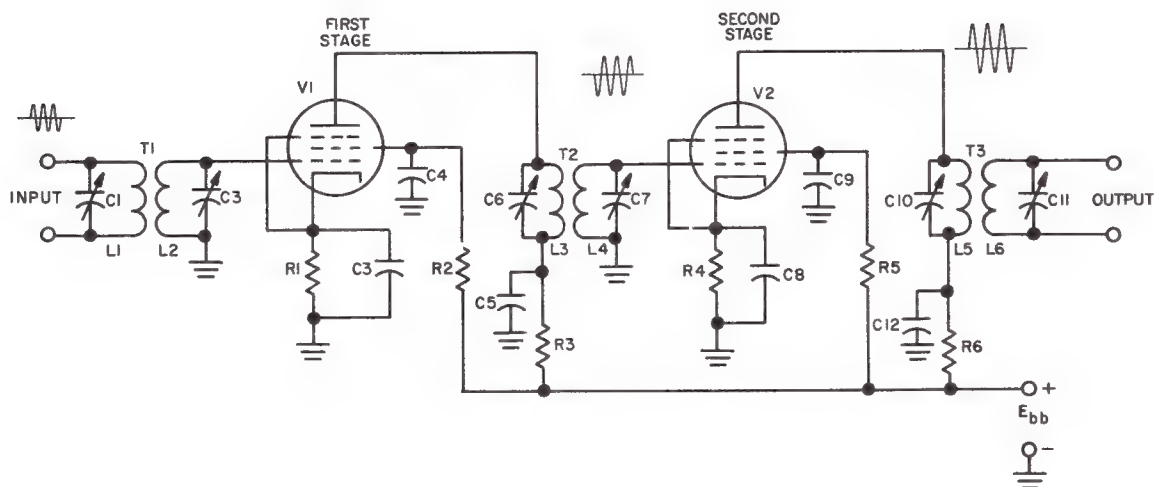

Two-Stage I-F Amplifier Schematic

Transformer T1 couples the grid of V1 to the plate of the preceding mixer or converter stage, while T3 usually supplies the i-f signal to the detector. Any change in impedance between the primary and secondary circuits can be accommodated by changing the turns ratio in the transformers. Normally, a 1-to-1 ratio is used, and any difference in impedance between the plates and grids of the cascaded stages is usually of academic interest only, since the primary and secondary of each i-f transformer are high-Q, parallel-tuned circuits and they both present a high impedance to the circuits in which they are connected. The high impedance produced by the plate circuit tank causes a large voltage drop across the primary, and by transformer action a large voltage is induced in the secondary. At the same time, the secondary presents a high impedance to the following tube grid circuit so that maximum voltage is developed on the grid, and grid losses are kept to a minimum. Thus, it is seen that double-tuning in itself always provides sufficient matching for efficient voltage transfer, provided that the coupling between the primary and secondary is optimum. It is also evident that the largest voltage is developed across either tank at the frequency to which it is tuned, since it presents the highest impedance at resonance. While there are some shunting effects due to grid-to-ground and plate-to-ground capacitance, plus internal leakage in the transformers, this is taken care of in design calculations.

Further examination of the schematic also reveals that the stages are simple pentode r-f voltage amplifiers. Self-bias for the stages is provided by cathode resistors R1 and R4, bypassed for rf by C3 and C8, respectively. Screen voltage is obtained through voltage-dropping resistors R2 and R5, while plate voltage is supplied through R3 and R6. The screen resistors are bypassed to ground for rf by C4 and C9, and the plate resistors are bypassed by C5 and C12, which also form a decoupling network.

With no signal applied, both V1 and V2 are resting in their quiescent condition. Plate and screen currents flow steadily through cathode resistors R1 and R4, and develop a positive bias at the cathode, which is the same as a negative bias on the grid. (See the introduction to this section for a discussion of cathode bias.) Screen resistors R2 and R5 drop the supply voltage to the value of screen voltage necessary to provide sufficient plate current swing. Likewise, plate resistors R3 and R6 drop the plate voltage to the proper operating value. Since each of these resistors is bypassed to ground, any r-f variations of plate current (when a signal is applied) are eliminated so that steady plate and screen currents flow throughout the cycle (with or without signal), and cathode bias can be used.

When an input signal is applied to T1 primary, a high impedance is offered the signal at the resonant frequency to which C1 tunes L1. With secondary L2 tuned to the same frequency by C2, a high impedance

appears between the grid of V1 and ground. When the input signal causes an increase in current through L1, a corresponding increase in voltage is induced in L2 by transformer action, and the increased voltage appears on the V1 grid. As the grid of V1 is made more positive on the first half-cycle of operation, a larger plate current flows through the primary of T2. With tuned circuit L3, C6 tuned to the same frequency as the signal, a high impedance is presented to plate current flow, the plate voltage is reduced toward zero, and a large voltage drop occurs across L3. This voltage drop induces a negative-going signal in the secondary of T2 by transformer action. When tuned circuit L4, C7 is resonant at the signal voltage, a large negative voltage also appears between the grid of V2 and ground.

Since V1 and V2 are biased at the center of their grid-voltage plate-current transfer characteristic curve, large positive or negative swings of voltage can be accommodated without causing any distortion. Thus, the amplified input signal from V1, which appears on the V2 grid, is reproduced in amplified form in the plate circuit of V2. The operation of the tube V2 is similar to that of tube V1 except that the signal is oppositely phased. The negative grid signal from the first stage causes the plate current of V2 to decrease, and the plate voltage of the second stage rises toward the supply voltage (goes positive). At the same time, the primary of T3 offers a high impedance to current flow. The reduction in plate current flow through tuned primary circuit L5, C10 produces a large positive-going voltage and induces a voltage in the secondary of T3. When secondary circuit L6, C11 is tuned to the same frequency as the signal, it produces a high impedance, and a large output voltage is developed across it.

When the input signal at the first stage goes negative, on the remaining half-cycle of operation, the action of V1 and V2 is exactly the opposite of the described above. As the plate current of V1 is reduced by the input signal, a positive-going voltage is produced across the T2 primary, and this voltage is applied to the V2 grid. In turn, the V2 plate current is increased, producing a negative output voltage across T3. Since Class A bias is employed, a sine-wave input produces a larger and amplified sine-wave output. As long as the grid signal does not drive the grid of V1 or V2 to the point where it draws current, and the plate voltage does not fall below zero and cause plate current cutoff, no distortion occurs. The output

waveform of the amplifier is the same as the input waveform, but is much larger in amplitude.

Since the grounded-cathode circuit inverts the input signal, the output of an even number of stages is of the same polarity as the input. Therefore, any feedback from output to input will produce regenerative oscillations. However, the very small plate-to-grid capacitance of the pentode reduces any such feedback to a negligible value, and neutralization is not required. The use of plate decoupling capacitors C5 and C12 prevents feedback through common impedance coupling in the power supply. Thus, a stable, high-gain, and highly selective amplifier is produced by connecting the two double-tuned stages in cascade. From the discussion above it is clear that the operation is identical to that of the single-stage pentode r-f voltage amplifier in all respects, except for the effects of the double-tuned circuits in providing higher gain and selectivity than is possible in a single stage.

Failure Analysis.

General. The discussions of failure analysis for the Pentode R-F Amplifier and the Cascade R-F Amplifier, previously discussed in this section, are generally applicable to the interstage i-f amplifier.

No Output. A defective i-f transformer, and open bias resistor (R1 or R4), loss of screen or plate voltage, or a defective tube can cause loss of output. Check the plate, screen, cathode, and supply voltages with a voltmeter. Lack of plate voltage can result from a defective power supply, an open plate resistor (R3 or R6), a shorted plate bypass capacitor (C5 or C12), or a defective transformer (T2 or T3). If the voltage is zero at the junction of C5 and R3, or C12 and R6, the cause is either an open plate resistor or a shorted plate bypass capacitor. A resistance check, using an ohmmeter (with the power off), will determine which is at fault. With plate voltage of C5 and C12, but not at the plate of one of the tubes, and i-f transformer primary is defective, or the primary and secondary are shorted; in either case, replacement of the transformer is necessary. An open plate circuit in a screen-grid tube can usually be determined quickly by noting that the screen is red, because of an overloaded screen, which tries to take the place of the plate. In this case screen resistor R2 or R5 will be excessively hot; it may smoke, and will eventually burn out. Where voltage exists on the plate of one of the tubes, but not on the screen, bypass capacitor C4

or C9 may be shorted, or screen resistor R2 or R5 may be open. A resistance check from each screen bypass capacitor to ground (with the power off) will indicate zero if the capacitor is shorted, and a resistance check of the screen resistor will reveal the condition of the resistor. Since the screen voltage determines the plate current of a pentode, to a great extent, it is not always necessary for the screen voltage to be zero in order to cause loss of output. Since cathode resistor R1 or R4 is in series with the tube, if the resistor is open the circuit to ground will be incomplete and the tube will not operate. Likewise, if it increases in value sufficiently the tube can be biased off to almost zero plate current, and cause such a small output as to be considered practically no output at all.

If the tube is defective and no emission occurs, the cathode voltage will be zero. With C3 or C8 shorted, there will also be no cathode voltage, but the output will be distorted because of heavy plate and screen current; in this case the plates will get red and the tube may be damaged. Where the indications are otherwise normal, the tube should be suspected. With normal plate, screen, and cathode voltages, and no output, and the tubes are known to be good, it is certain that the secondary of output transformer T3 is open or totally detuned. Usually such a condition will produce a slight output because of stray capacitive coupling between windings, but it could be mistaken for a no-output condition.

Low Output. Low output can be caused by a defective tube, low screen or plate voltage, or too high a bias. First check the tube element voltage with a voltmeter. A low voltage on the plate or screen indicates excessive current drain in that circuit (producing a large voltage drop through the series resistor), an off-value plate or screen resistor, or a leaky bypass capacitor. The resistors can be checked by means of an ohmmeter (with the power off), and the capacitors with an in-circuit capacitance checker. Larger than normal plate and screen current will also cause a corresponding increase in bias voltage, since cathode bias is produced by the sum of all currents flowing in the tube. A leaky screen or plate bypass capacitor will cause reduced plate or screen voltage, reduce the cathode current flow, and hence decrease the bias. Low tube emission is usually indicated by

higher than normal plate and screen voltages, with reduced cathode bias. As the condition becomes worse, the output will continue to decrease progressively until the tube emission is insufficient to produce an output. When all voltages appear normal and the output is low, either a tube may be defective or the alignment may be at fault. If during alignment one of the tuning capacitor (or tuned inductors where inductive tuning is used) does not seem to have any effect, the transformer being tuned is defective; replace it with a good one.

When the set suddenly blocks on receiving a loud signal and becomes almost inoperative, the i-f amplifier is probably oscillating and developing sufficient bias to cause the reduction in the output signal. Sometimes blocking will not occur, but a strong squeal or howl will occur instead. In either case a plate or screen bypass capacitor may be open. In some instances drying out of the last electrolytic capacitor in the power supply will cause loss of filtering ability, produce hum, and through common impedance coupling cause a similar effect.

Distortion. Distorted output can be caused by an improper bias, plate, or screen voltage. When the plate voltage drops below zero, plate current cutoff occurs, and this stoppage of plate current flow causes distortion. If the plate voltage is driven into plate current saturation no further change in plate current can occur, and a similar type of distortion will exist. Excessive bias will cut off the lower portion of the drive signal, reduce the plate current swing, and cause distortion. Likewise, excessive input (drive) voltage will cause the bias to be driven to zero (or above) and cause grid current flow; this will cause plate current saturation on one signal peak, and cutoff on the opposite signal peak. Both distortion and reduced signal output will occur. Usually, a voltage check for this condition will indicate improper or fluctuating voltages on the tube electrodes. However, it is easier to use a scope with an r-f probe and observe the signal. A simulated (signal generator) input with modulation applied also provides a simple signal for observation on a scope. Localization of the trouble to a specific portion of the circuit will usually involve only those components in the circuit where the distortion is observed, so that further simple voltage or resistance checks of the parts involved will locate the defective part.

TUNED INTERSTAGE (I-F) AMPLIFIER (SEMICONDUCTOR)

Application.

The tuned interstage i-f amplifier is used in superheterodyne receivers to produce high gain and the desired selectivity.

Characteristics.

Operates at a fixed frequency and is tunable over a small range for alignment and adjustment of bandpass.

Uses either single- or double-tuned coupling (i-f) transformers.


Uses Class A bias to minimize distortion.

Common-emitter configuration normally used, although common-base circuits may be encountered in some applications.

Usually includes a neutralization circuit to prevent internal feedback from causing self-oscillation.

Circuit Analysis.

General. The i-f amplifier in a superheterodyne receiver determines the selectivity and gain. By using a number of cascaded tuned stages operating at a relatively low radio frequency as compared with the fundamental received frequency, higher gain per stage is obtained than would be possible at the signal frequency. By using a number of tuned circuits, the selectivity is increased over that of a single tuned circuit. The accompanying figure illustrates the manner in which the selectivity and bandpass are affected by a number of tuned circuits.

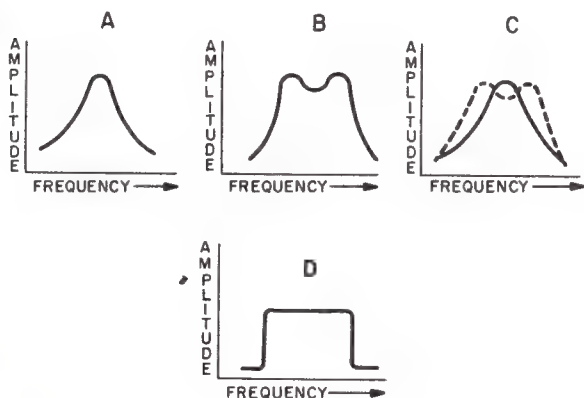


Effect of Tuned Circuits on Bandpass

In part A of the figure, the selectivity curve produced by a single tuned circuit is shown. In part B, the double-humped curve produced by a stagger-tuning two i-f stages is shown (overcoupled circuits also produce a similar response). In part C, the individual response curve are super-imposed on each other. In part D, the idealized response is shown. These coupling circuit techniques are similar to those used in electron tube circuits. Since the tuned circuits in the i-f amplifier form a coupling network matching the output of one stage to the input of the next stage, it is necessary to hold losses in the network to a low value. It is also necessary to match the output and input impedance to obtain maximum gain. At the same time, the unloaded Q of the coupled circuits must be kept as high as possible to retain a good selectivity characteristic. Because of the relatively low input and output impedance of the transistor and the large capacitance between emitter, base, and collector, design problems are created which do not occur in the electron tube circuit. For example, the power transfer efficiency between the primary and secondary of a tuned transformer is maximum when *both* the unloaded Q and the bandpass are large. Thus, a high power transfer and a narrow band pass pose conflicting requirements. Since the bandpass requirement is determined by the amount of selectivity desired, if the input and output impedance are matched, the power transfer can be improved only by raising the unloaded Q.

The common-emitter circuit has a low input resistance together with a high input capacitance, and the output impedance is moderately high with a large shunt capacitance. Therefore, in interstage coupling transformers an impedance step-down (which varies as the square of the turns ratio) is required to match the high output impedance to the low input impedance of the next stage. In addition, the total circuit capacitance must be considered when determining the inductance needed to resonate at the intermediate frequency. Thus, the reflected input (secondary) capacitance (which varies inversely as the square of the turns ratio), plus the primary shunt collector and wiring capacitance, together with the actual primary tuning capacitor, form the total tank tuning capacitance. When calculated for a given set of design considerations, the inductance is often very small and, at an i-f of 455 kHz, requires a very large tuning capacitance to obtain resonance. While the large tuning capacitance has the beneficial effect of swamping out


the comparatively small transistor capacitances, it is difficult to build a small inductance with a high Q . Therefore, it becomes necessary to increase the small value of primary inductance to a larger and more practical coil value. By increasing the inductance (for example 100 times), the tuning capacitance can be reduced to only one one-hundredth of its former value and still resonate at the same intermediate frequency. Although a high- Q circuit, the primary tank now has an impedance of 100 times the original value. To retain the original impedance to match the transistor, the tank is tapped to produce a 10-to-1 turns ratio (the inductance functions as an autotransformer), and the transistor is connected across the lower-impedance portion of the primary winding.

With the primary tank matched for proper power transfer the turns ratio between the entire primary and secondary is selected to produce the proper step-down ratio. Thus, all impedance involved are matched for efficient power transfer. If necessary, the i-f secondary may also be tapped in a similar manner to obtain a high- Q input tank. The following figure illustrates the manner in which the desired selectivity and impedance matching are obtained in a simple single-tuned i-f transformer designed for a 455 kHz i-f.

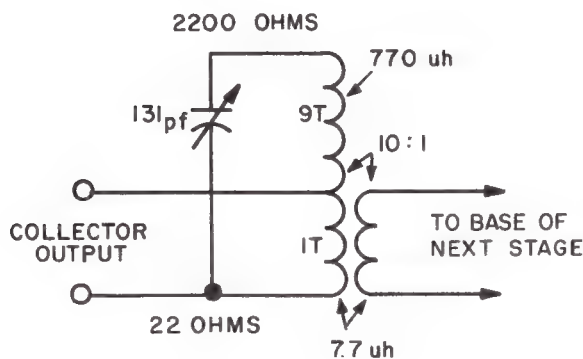

Typical Matching Circuit

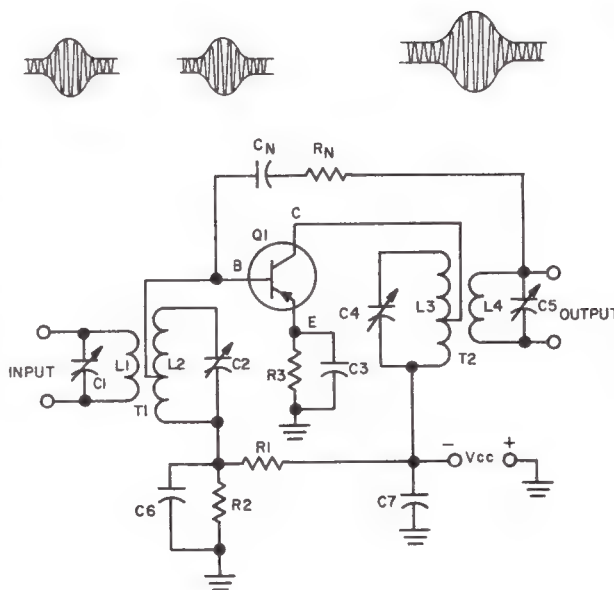Circuit Operation. The schematic of a typical interstage i-f amplifier with neutralization, employing the common-emitter configuration, is shown in the accompanying illustration.



Typical Common-Emitter i-f Stage

The input signal is coupled to the base of Q1 through T1. I-F transformer T1 is double-tuned, with L1, C1 forming the primary tank and L2, C2 forming the secondary tank. The low, base-input impedance is matched for maximum transfer of power by tapping it down on inductance L2, thereby retaining the high Q necessary for good selectivity. Trimmer capacitors C1 and C2 tune the i-f transformer over a small range about the center frequency, permitting exact alignment at the intermediate frequency. Class bias is supplied to the base of Q1 through voltage divider R1 and R2. R2 is bypassed for rf by C6. R3 and C3 are the conventional emitter swamping resistor and bypass capacitor. (See the introduction to this section for discussions of biasing methods and stabilization methods.)

Output transformer T2 couples the collector of Q1 to the base of the following stage. The primary of T2 consists of L3 tuned by C4, and the secondary consists of L4 tuned by C5. L3 is tapped to match the collector output, provide maximum power output, and yet retain the high Q necessary for selectivity. Capacitor C7 is used to bypass the collector supply. Neutralization is provided by RC network C_N , R_N , connected from the secondary of T2 to the

base of Q1. The feedback is taken from the transformer secondary to provide a 180-degree phase shift or polarity inversion, to cancel the internal feedback developed within the transistor.

In the absence of an input signal, the fixed bias determined by the ratio between R1 and R2 causes Q1 to draw its quiescent value of collector current. Q1 operates at the center of its characteristic transfer curve to permit equal positive and negative swings. Since the quiescent current is steady, no output is developed. Assume an input signal within the intermediate frequency bandpass is applied to the T1 primary. Primary tank C1, L1 appears as a high impedance to those frequencies within the bandpass, and, since it is a resonant load for the preceding stage, it develops a large voltage across L1. This primary voltage, in turn, induces a voltage in the L2 secondary. The secondary is tuned by C2, and is resonant at the same intermediate frequencies. Therefore, a large voltage is developed for those frequencies which are within the bandpass, and a portion of this voltage developed between the tap and ground (since C6 provides an r-f shunt around R2, and places the rotor of C2 and the lower end of L2 at ground potential) is applied to the base of Q1. These i-f frequencies are essentially sinusoidal; they consist of the fundamental (or carrier) and modulation which appears as sidebands above and below the center frequency. Assume that a half-cycle of this frequency is negative and adds to the normal forward bias applied to Q1. For the duration of this negative-going half-cycle, the emitter and collector current of Q1 increases sinusoidally, in synchronism with the amplitude of the applied signal.

Since the collector is tapped to L3 any current flow through the tap to the ground end of the coil also induces a voltage in the top portion by autotransformer action. Capacitor C4 tunes L3 to the intermediate frequency, and the tank appears as a high impedance to those frequencies within the i-f bandpass. Thus, a large voltage is developed across the primary of T2 and induces, by transformer action, a voltage in the tuned secondary circuit. The tapped portion of L3 also provides an impedance transformation. With the lower end of L3 supplying an impedance equal to the collector impedance, maximum power transfer occurs through the transistor. The upper portion of L3 (above the tap) provides a higher impedance, which allows a sufficiently high Q to be obtained to provide sharp tuning and selectively

despite the loading effect of collector current flow through the bottom of the coil. Thus, only frequencies within a narrow bandpass around the carrier (i-f) frequency are amplified strongly, and the frequencies outside the bandpass are reduced in amplitude and effectively rejected.

During the remaining (positive) half of the single r-f cycle, the signal opposes the forward bias and causes a reduction in the emitter and collector current. These alternate increases and decreases in current occur at i-f rates, and are equivalent to an ac current flow; thus, the ac signal variations induce an output voltage in the secondary of T2. If the current did not vary with the signal, but rather remained steady, no transformer action could occur.

While the dc emitter current flows through R3, the i-f variations are bypassed by capacitor C3 so they have no effect on emitter resistor R3. Thus only small current changes (induced by temperature changes), consisting of slow, dc variations of emitter current, affect R3. Since electron flow is from emitter current, affect R3. Since electron flow is from emitter to ground, the current changes produce an oppositely polarized voltage which subtracts from the normal forward bias and returns the emitter current to its previous value. This is conventional emitter-swamping action.

The output impedance of the collector is reduced by the step-down turns ratio between the primary and secondary to a value suitable for matching the input impedance of the next i-f stage. Tank circuit L4 and C5 is also tuned to the intermediate frequency and selects only the desired signals for application to the next stage. The use of a number of tank circuits provides a relatively flat but sharp selectivity curve, as explained previously in the introduction to this circuit.

When the intermediate frequency is high enough to cause some of the collector output to be coupled back to the base through the collector-to-base capacitance and develop a feedback voltage through the internal base spreading resistance, oscillation occurs in the i-f stage. Therefore, C_N and R_N are used to feed back a voltage from the secondary of T2, whose phase is opposite that of the collector output, to the base of Q1. With an equal voltage of opposite polarity, the internal feedback voltage is cancelled and oscillation cannot occur. In some circuits R_N is not used; C_N is sufficient. In some circuit designs, mismatching of the stages is used to avoid feedback and

oscillation, with some loss of gain. Usually, only as many stages as are necessary are used to provide satisfactory selectivity, since the more the stages the greater the feedback possibility. Likewise, double-tuned circuits are not used where single-tuned transformers are satisfactory.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low-voltage ranges of most volt-ohm-milliammeter testers. Be careful, also, to observe proper polarity when checking continuity or making resistance measurements with the ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. Lack of an input signal, improper bias, lack of supply voltage, or a defective transistor can cause loss of output. Check the bias and supply voltages with a voltmeter. If R1 is open, the base bias will be zero, which corresponds to Class B operation, and there is a possibility that strong signals may produce a partial output. However, if R2 is open or if the secondary of T1 (L2) is open, the base circuit of Q1 is also open and no output can occur. Should the primary of T1 (L1) be open, there will be no collector voltage applied to the preceding stage, and no transfer of signal to Q1. Since the i-f stage operates at radio frequencies, use an r-f probe in conjunction with a VTVM, or an oscilloscope, to determine whether a signal appears on L1. If R3 is open, the emitter circuit will be incomplete and no output will be obtained. Use an ohmmeter to determine the continuity and resistance of R3. If a voltage exists at the base of Q1 but not at the collector, either T2 is defective or C7 is shorted. A dc voltage reading between the collector and ground with no output indicates that either Q1 is defective or T2 is short-circuited. Check T2 for shorts with an ohmmeter. If neutralizing capacitor C_N is shorted, the base of the following stage will be directly connected to the base of Q1 and will shunt transistor Q1. There will be a loss of amplification, but not necessarily a complete loss of output. However, if the capacitor is open, oscillation will occur and may cause blocking due to a change of bias (the transistor will rectify the oscillation and produce a dc bias). Or, if the oscillation is not strong enough, a partial output may be obtained

(with or without distortion). Check the capacitor with a capacitance checker; also check the value of resistor R_N with an ohmmeter.

Low Output. A number of conditions can cause reduced output. For example, low collector voltage, low bias voltage, loss of transistor gain, an open or high-resistance tuned circuit in the i-f transformers, and short-circuited or changed values of other parts. Check the bias and collector voltages with a voltmeter. Use an oscilloscope and r-f probe and test from point to point throughout the circuit, to determine where the signal drops in amplitude. The signal at the collector of Q1 should be larger in amplitude than the signal at the base of Q1. If the signal appears at the input to T1 and is greatly reduced at the base of Q1, either T1 or Q1 is defective. If C3 is open-circuited, the emitter current flowing through R3 will produce degeneration and oppose the bias. The output will be reduced in proportion to the amount of degeneration. With a collector output equal to or less than the output at the base of Q1, either T2 or Q1 is defective.

Insufficient Selectivity. Lack of selectivity can occur because of poor alignment of tuned circuits, which is usually indicated by loss of gain, together with broad tuning. In most cases, however, special tests are necessary to determine whether realignment is needed, and special procedures and equipment are required for proper alignment. Therefore, readjustment of the i-f trimmers should be attempted only when it is ascertained that the circuit is otherwise operating normally. Where i-f transformer(s) are replaced, it is necessary to make proper adjustments to restore the initial selectivity. A rough approximation of performance may be obtained by observing the detected output on an oscilloscope and tuning an r-f signal generator through the i-f bandpass. The amplitude of the signal observed on the oscilloscope will be nearly uniform for a flat-topped response curve. The 70-percent response points below and the above the i-f center frequency will indicate approximately the low- and high-frequency limits of the bandpass. Where lack of selectivity is suspected, the necessary check can be made by determining the equipment specifications, following the manufacturer's recommended alignment procedure, and comparing results, noting the effect of each adjustment of the response curve.

TRIODE R-F BUFFER AMPLIFIER (ELECTRON TUBE).

Application.

The triode r-f buffer amplifier is employed in receivers, test equipment, and transmitters as an intermediate amplifier stage, between the oscillator and the output stage, to minimize or eliminate the effect of impedance or load changes in the output on the oscillator frequency.

Characteristics.

Operates Class B or C in transmitter applications, and Class A (or AB_1) in test equipment and receiver applications.

Gain and power output are usually low.

Normally operates on the same frequency as the oscillator and output stage.

Plate efficiency varies with the bias; Class A is lowest and Class C is highest, with Class B at some intermediate value.


Requires more grid drive than a pentode buffer.

Usually requires neutralization to prevent feedback and self-oscillation.

Circuit Analysis.

General. In receiver applications, the r-f buffer amplifier is generally used between the local oscillator and the mixer as shown in the accompanying block diagram. Thus, any changes in mixer operation or load, such as might be caused by automatic volume control, affect only the buffer stage, and the oscillator frequency is not pulled or changed. This type of operation is used mostly for single sideband reception, where the oscillator frequency must be kept stable within a few cycles of the desired fundamental or output frequency. In transmitters, the buffer amplifier is used to isolate the high-level modulated r-f output stage from the oscillator, to prevent frequency modulation effects on the carrier and to avoid distortion. It is also used in low-level stages for the same purpose, and in cw operation it prevents sudden changes in load with keying from affecting the oscillator frequency. It is sometimes used as a dual-purpose amplifier to supply additional drive power, plus isolation. When used as a power amplifier, however, its isolating effect is nullified with the larger outputs and loads, so that sometimes more than one power buffer stage may be used. In test equipment, the r-f buffer is not necessarily used only to provide a stable oscillator


frequency, but may be used to prevent the changing of load in one stage from having any other effect on the stage preceding the buffer. Because test equipment and receivers require linear operation with minimum distortion, these buffer stages are always operated Class A (or AB_1). Although the transmitter buffer stage could also be operated Class A, it would result in an unnecessary loss in efficiency; hence the reason for Class B or C operation. Because the Class C stage requires a large drive and this grid current requirement loads the preceding stage, Class C operation is not used when Class B operation will suffice. Since only an r-f carrier is amplified, the tank circuit eliminates any distortion caused by single-tube Class B operation.

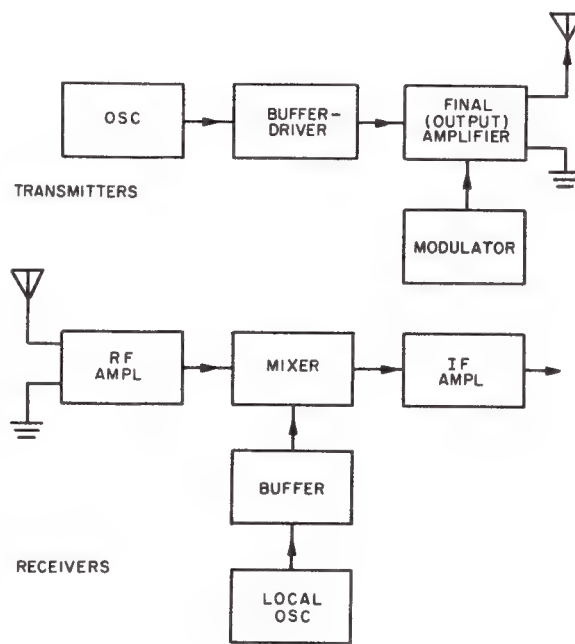

Buffer Locations

Circuit Operation. The schematic of a typical triode r-f buffer amplifier is shown in the accompanying illustration.

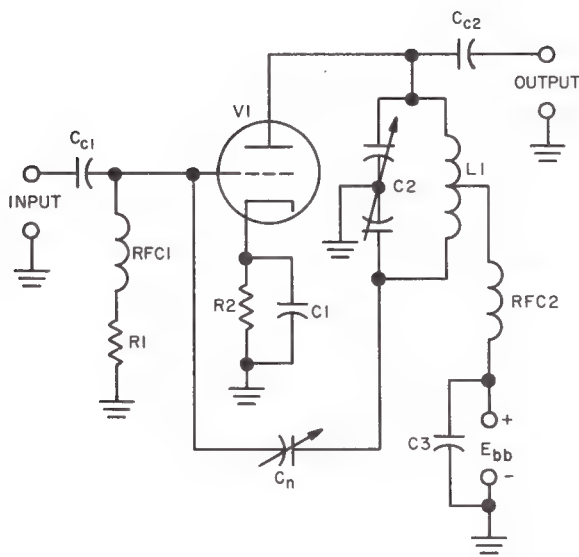Capacitive input and output coupling are provided through C_{c1} and C_{c2} , respectively. Both fixed grid bias and protective cathode bias are employed (although either could be used alone). Resistor R_1 provides the grid bias by means of the grid current



Triode R-F Buffer Amplifier

flow in V1, obtained through grid drive from the oscillator input. Radio-frequency choke RFC1 keeps the input rf from being shunted to ground through the grid return resistor. Protective cathode bias is supplied by R2, bypassed by C1 for rf. The plate tank consists of L1 and C2, with C2 being a split-stator type of variable capacitor. Thus, with the center plate of C2 grounded, the tank is balanced, and opposite polarities exist at the ends of the tank coil. One end of the tank coil is coupled through C_{c2} to the next (output) stage, while the other end of the coil is fed back through C_n to supply a neutralizing connection, and the plate voltage is applied to the center of the coil. RFC2 keeps the rf in the tank out of the power supply, and C3 assures this by bypassing any remaining residual rf around the power supply to ground.


In the absence of an input signal, cathode current flow through R2 develops a protective cathode bias which is sufficient to prevent damage to the tube, but is not sufficient for normal operation. When the oscillator input signal is applied through C_{c1} to V1, grid conduction occurs during the positive half-cycles. Grid current flow from the cathode to the grid, charging the coupling capacitor. During the negative alternation, the grid current is cut off by the negative signal and the bias voltage developed by the charge on

the coupling capacitor discharging to ground through R1. After a few alternations this signal bias develops a steady bias voltage. The total tube current flow through V1 and cathode bias resistor R2 adds a slight amount to the signal bias, and the operating bias is a combination of both. Normally, the tube operates Class B, and plate current is cut off during the negative half-cycle (when operated Class AB only a portion of the negative half-cycle is cut-off). Thus, plate-current pulses flow only during the positive half-cycle, and loss of the negative half-cycle would normally cause distortion. However, the tuned tank circuit, consisting of L1 and C2, acts as a reservoir for rf and supplies the missing negative half-cycles. This action occurs because, once the tank circuit is excited, oscillations do not immediately cease unless there are heavy losses in the tank. Otherwise, once the source of rf is removed, the circuit continues to oscillate with diminishing amplitude each cycle until the rf is dissipated in the resistance of the tank. Since pulses of rf energy are supplied each positive half-cycle, the tank is effectively returned to its initial amplitude once each cycle. Any tank losses are thus supplied by the cycle during which conduction occurs. Therefore, the tank operates as though it were continuously excited, and no distortion in the output exists because of the loss of the negative half-cycle of operation. Single-tube, Class B operation is possible in an r-f amplifier because of the tuned tank circuit. In an audio amplifier, two tubes are necessary, one operated by the positive half-cycle and the other by the negative half-cycle, to provide an undistorted signal.

With the output tank tuned to the same frequency as the input (drive) signal, positive feedback can occur through the large grid-to-plate capacitance of the triode. Although the polarities of the grid and plate are opposite in the common or grounded-cathode circuit, the capacitive feedback voltage leads the predominantly inductive (high-Q) tank voltage, and is, therefore, of the proper phase to combine regeneratively with the input signal. Hence, neutralization is necessary to prevent self-oscillation. Neutralization is accomplished by feeding back an equal but oppositely polarized voltage through C_n from the other side of the tank. Since at any instant the opposite ends of any tank coil are of opposite polarity, taking the feedback voltage off the end of the coil opposite the plate always provides the correct polarity for neutralization. The use of a center-tapped coil

with a split-stator tuning capacitor insures a completely balanced tank. Thus, it is only necessary to adjust C_n to approximately the same value as the grid-to-plate capacitance to obtain neutralization.

The manner in which the neutralizing circuit forms a reactive bridge with equal arms is shown in part A of the following simplified schematic. This plate-to-grid feedback system is known as the *Hazeltine* or *neutrodyne* type of neutralizing circuit. A similar form of feedback from grid to plate is known as the *Rice* system, and is shown in part B of the schematic. While other forms of neutralization are also used, these two types are the most popular and commonly used circuits. In part A of the illustration, Z_g is the input impedance, and coils L_p and L_n together form tank coil L_1 in the plate circuit. The voltage across C_n is equal, and opposite in polarity, to that across C_{gp} ; thus, there is no flow of current from output to input, and complete neutralization results. In part B of the figure, the opposing voltages are developed in the grid tank across L_g and L_n ; otherwise, the operation is the same.

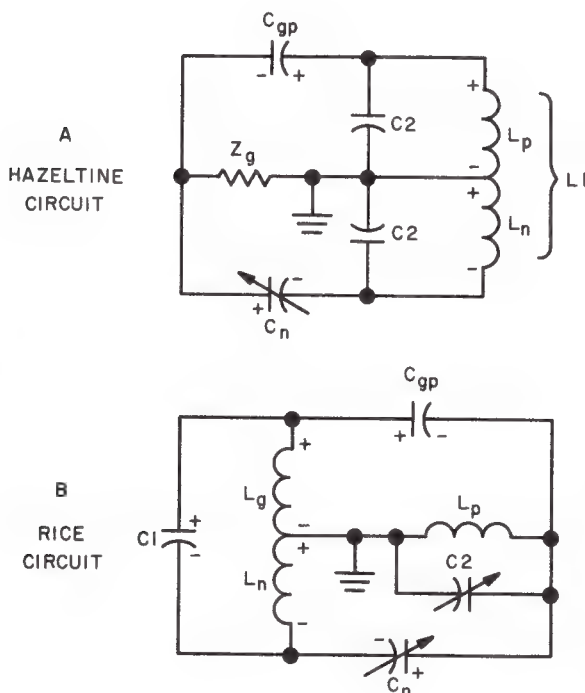

Typical Neutralizing Circuits

Although the triode buffer described above uses capacitive input and output coupling, inductive coupling can be used instead. In this case the grid circuit usually contains a tank, with a coupling coil, and the plate likewise. The operation is the same except for the inductive input and output coupling, which merely transfers the signal into the input tank and out of the output tank. Push-pull stages may also be used as buffer amplifiers, in which case neutralization is easily accomplished by using cross-connected grids and plates, since they are oppositely phased and polarized.

The basic triode r-f buffer amplifier originally consisted primarily of a low-gain voltage amplifier which did not draw grid current and was lightly loaded, since it only supplied the grid current (drive power) necessary for the final output stage. Therefore, it offered no load to the self-excited oscillator, and allowed it to operate at maximum stability. At the same time, the tube was chosen with a power rating which was more than sufficient to supply the grid power needed by the final amplifier. Thus, the buffer stage effectively isolated the oscillator from the output stage, so that it was affected very little by any modulation peaks, or on-off keying of the output stage. For satisfactory performance Class A operation of the buffer was required, and low efficiency was obtained. In later years oscillators of better stability were produced, and Class B operation permitted a more efficient output with slight oscillator loading. Thus, as the state of the art advanced and electron tubes and parts improved; it was found that even Class C operation could be used. Hence, the buffer amplifier is now generally considered to be any amplifier used between the oscillator and output stages and operating on the fundamental frequency. By using Class AB_1 operation, high efficiency with no grid current flow can now be obtained. However, the high gain of the pentode has virtually made the triode buffer obsolete except for special applications.

When operated Class A, the operation is the same as that described previously except that it is not necessary for the tuned tank to supply the negative portion of the waveform.

Failure Analysis.

No Output. Lack of an input signal, loss of plate voltage, a defective tube, or a detuned output tank will cause loss of output. The supply voltage should be checked with a voltmeter to determine whether

the proper voltage is available. The grid drive may be checked by reading the grid voltage developed across R1 (in stages where grid current is drawn). Usually, transmitters are equipped with a milliammeter to read grid and plate current for tuning indications. Plate current indications will usually pinpoint the trouble to a particular location. For example, no plate current indicates an open plate or cathode circuit, a defective tube, or lack of plate voltage. In this case, it is a simple matter to turn off the plate power, *discharge the filter* with a shorting stick, and then make a resistance check of cathode resistor R2, and a continuity check of L1 and RFC2. If plate current is present, tune C2 for minimum dip in plate current. With sufficient drive, there should be a large current off resonance and a small current at resonance. If the drive is lacking, the ratio between the nonresonant and resonant condition will be small. If the ratio is large and the resonant current is lower than normal, there is no load or only a light load on the output, and C_{c2} is a probable open. In this instance, an r-f indicator will show rf on the plate side of the capacitor, but not on the output side; use a small coil connected directly to the vertical plates of an oscilloscope (not through the scope amplifier) to couple to the plate tank and indicate rf. Lack of grid drive will show as a large plate current indication which cannot be dipped to a normal low value, since the bias will be only that provided by R2. If C3 is shorted, the power supply plate fuse or circuit breaker will open, no plate voltage will be applied, and loss of output will occur. Where the plate voltage is normal and the grid drive is sufficient, but the plate current is low (or slowly decreases as the stage operates), the emission of the tube is probably low.

Low Output. Low plate voltage, low grid drive, improper bias, or a defective tube can cause low output. The plate supply voltage and grid bias across R1 and R2 can be checked with a voltmeter. It is important to note the difference between receiving and transmitting r-f amplifier voltage measurements. In the receiver stage, any rf on the grid or plate is usually so small that it will not damage the meter; however, in the transmitter stage, large r-f circulating currents are produced in the grid and plate circuits which can damage the meter when dc measurements are made to ground. Therefore, it is necessary to use a radio-frequency choke in series with the voltmeter, or use a probe which is adequately filtered for rf. A

vacuum-tube voltmeter may be used on receiving equipment, but it is usually unable to withstand the high voltage present in transmitters. As a general rule, therefore, all dc voltages measurements are made in portions of the circuit which are "cold" to rf (no rf exists), and other indications, such as plate current, are used instead. (In special instances, r-f voltmeters can be used.)

With proper plate voltage and bias, low output will be obtained if the r-f grid drive is not sufficient to make the tube draw the proper value of plate current. Likewise, low emission will make it impossible to obtain the proper plate current, and thus the proper output. When all indications other than plate current are normal, the tube is probably at fault.

If cathode capacitor C1 opens, plate current variations occurring at radio-frequency rates will momentarily develop high cathode bias voltages, produce degeneration, and cause reduced output. Temporarily grounding the cathode in this case will restore operation and the output to normal, and prove that C1 is defective. Do not try grounding the cathode unless grid drive is present; otherwise, the tube will operate at zero bias, will be overloaded, and will be damaged if current is allowed to flow for a prolonged period of time. Sometimes low output will be obtained because of parasitic oscillation at a very low frequency. This occurs when a feedback loop occurs through the neutralizing circuit and an associated r-f choke and bypass or tank tuning capacitor(s). The symptoms are high plate current with low r-f output at the desired frequency and larger than normal grid current. Once started, these oscillations will usually continue when the normal grid excitation is removed. If the circuit operates and tunes normally with reduced plate voltage and at a reduced output, but will not do so when full plate voltage is applied, parasitics are probably the cause. Usually, this will not occur in Navy equipment when initially received, but can sometimes be caused by a change in components with age, by a part failure, or by improper bias, or change of lead dress during a repair.

Improper Neutralization. When a stage is incompletely neutralized or misadjusted, operation will become erratic. The tube may operate normally and then suddenly start oscillating when shocked by a transient pulse. To determine whether the stage is properly neutralized, *remove the plate voltage* and tune the plate capacitor through resonance while

observing the grid meter indications. A steady, unchanged meter reading indicates complete neutralization; a slight change or sharp flick of grid current as resonance is passed indicates that neutralization is incomplete. Adjust the neutralizing capacitor while tuning the plate through resonance until the grid meter remains steady.

PENTODE R-F BUFFER AMPLIFIER (ELECTRON TUBE)

Application.

The pentode r-f buffer amplifier is universally used in receivers, test equipment, and transmitters as an isolation stage. It is generally used between an oscillator and an output stage to prevent modulation or load changes from affecting the oscillator frequency.

Characteristics.

Usually operated Class A or AB, self-biased, although Class B or C operation is sometimes employed.

Has relatively high voltage and power gain.

Provides more output than a triode r-f buffer amplifier, with less drive.

Does not normally require neutralization.

Operates on same frequency as input and output stages.


Has greater isolating effect than a triode.

Circuit Analysis.

General. The pentode r-f buffer amplifier is an effective isolation amplifier because of the low grid voltage drive required for full output, which places very little loading on the oscillator (or input) stage. Thus, the oscillator can be designed for maximum stability under a light or idling load. In addition, the effective shielding supplied by the screen and suppressor elements of the pentode reduces the grid-to-plate capacitance to such a small value that feedback is practically eliminated. Therefore, no neutralizing circuits are needed, so that fewer parts are required and the neutralizing adjustment is eliminated. Finally, the high amplification factor of the pentode produces a large output voltage under the control of only a small grid voltage. Since the screen prevents plate current variations from affecting the grid or input circuit to any marked extent, a much larger power can be developed in the pentode plate circuit than in a triode

operating at the same plate voltage. Because of the small drive required, the pentode r-f buffer amplifier may also be used to drive another pentode (or tetrode) output tube without losing its ability to act as an isolation stage. The resultant transmitter output, then, is equivalent to that developed by two or three triodes operating at higher plate voltage and currents.

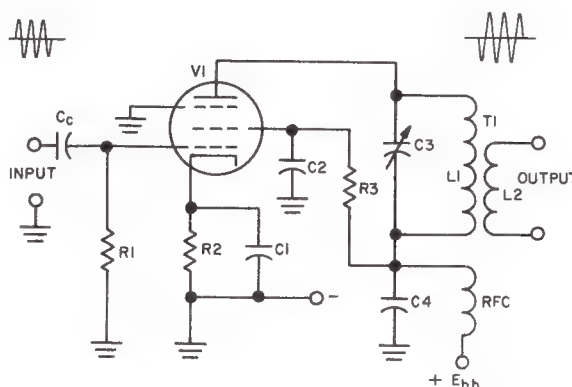Circuit Operation. The accompanying illustration is a schematic of a typical pentode r-f buffer amplifier.



Typical Pentode R-F Buffer Amplifier

The grid of V1 is capacitively coupled through C_c to the oscillator. Resistor R1 is the grid return resistor, across which the input voltage appears. Cathode bias is supplied by R2, which is bypassed for rf by C1. Screen voltage is obtained through dropping resistor R3, which is bypassed to ground for rf by C2. The plate voltage is series-fed through L1 to the plate of V1, and is tuned to resonance by C3. L2 is the output coil, which is inductively coupled to L1 (L1 and L2 form r-f transformer T1). The radio-frequency choke (RFC) prevents any rf from entering the supply and is bypassed to ground for rf by C4.

When the oscillator operates, a signal which is approximately a sine wave is developed in its plate circuit, and is applied through C_c to the V1 grid. The low reactance of C_c ensures that a minimum voltage drop (and very little loss of signal) occurs across the coupling capacitor. Grid resistor R1 provides a high impedance across which the oscillator signal is developed. Since the grid does not normally draw any grid

current, no current flows through R1 at any time (unless Class B or C operation is employed). Cathode resistor R2 provides bias voltage which is developed across it by space charge current flow, that is, the sum of both the screen and plate currents. When plate and screen voltage is applied to V1, current flows from ground through R2, producing a positive cathode bias which is equivalent to a negative bias voltage applied to the grid. Since R2 is bypassed by C1 for rf, no change occurs in bias when an input signal appears across V1 (between grid and ground). Any r-f current variations are bypassed around R2 by C1; hence, the bias is affected only by a steady change in plate or screen current, and not by instantaneous r-f variations. Thus, as the load changes the bias will also change accordingly. It is important that the load be held constant to produce the desired operating bias. When operated Class A (in receivers and test equipment), the operation is over the linear portion of the E_q-I_p curve. In Class AB operation a slightly higher bias is used. (See the introduction to this section for discussions of cathode bias and classes of amplifier operation.)

As the oscillator signal is applied to the grid of V1, assuming a sinusoidal input signal, the positive half-cycle of operation causes the plate current to increase, and the negative half-cycle causes the plate current to decrease. The plate current swing is determined by the screen voltage appearing on the screen of V1, which is controlled by the value of R3. The screen resistor is chosen so that with the proper plate voltage applied, and with no signal, the V1 screen and plate current flowing through cathode bias resistor R2 provides the normal bias. During operation, the screen current flows steadily, producing a voltage drop across R3 of sufficient value to drop the plate supply voltage to the desired screen voltage value. Any electrons striking the screen are bypassed to ground through capacitor C2. Likewise, any change in plate current will not effect the screen voltage, since R3 is always kept at ground potential for r-f variations; hence, only dc current flow determines the screen voltage, and this does not vary with the signal. Since the screen is closer to the grid than to the plate, it exerts a strong control over the plate current; also, since it is grounded for rf through C2, no feedback can exist between the grid and the plate (it acts as a shield). Thus any possibility of feedback and self-oscillation is eliminated, and neutralization is unnecessary. Tank circuit L1, C3 is connected in series with

the plate of V1, and when tuned to resonance offers a high impedance. Thus, as the input voltage swings positive, the plate current of V1 increases, and in flowing through L1 induces a voltage in secondary L2 by transformer action. Meanwhile, the high impedance of the tank produces a large plate voltage drop and the actual plate voltage falls toward zero. The design is such that the plate voltage is not allowed to drop below the actual screen voltage. (Otherwise, the screen of V1 would tend to act as a plate; thus it would be overloaded and cause distortion.)

As the oscillator signal changes its cycle and swings negative, the V1 plate current is reduced, and the reduced value of current through L1 induces an oppositely polarized output voltage in L2 by transformer action (the current now flows in the opposite direction). At the same time, the plate voltage rises toward the supply voltage. The actual plate voltage is almost equal to the supply voltage at the negative peak of the input cycle. The grounded-cathode circuit produces a polarity (or phase) inversion. When the input signal goes negative, the plate output signal is positive and of opposite phase or polarity; conversely, when the input signal goes positive, the plate output signal is negative. The output voltage induced into secondary coil L2 is polarized similarly when it is connected in-phase. If connected out-of-phase, the output signal polarity is the same as that of the input signal.

Capacitor C4 keeps the lower end of tank C3, L1 at r-f ground potential, and the RFC ensures that any residual rf is offered a high impedance, so that it flows to ground through C3 rather than attempting to flow through the low impedance offered by the output filter capacitor of the plate supply.

If tank circuit L1, C3 is not tuned to the oscillator or input frequency, a very small impedance is offered in the plate circuit and little or no output voltage is developed. The unloaded Q of the tank circuit is made high, so that the loaded Q (at resonance) provides sufficient selectivity to pass only a narrow band of frequencies between the half-power points, and the tank is able to discriminate between wanted and unwanted signals. While in Class A operation plate current flows at all times during the cycle, in Class AB or B operation part of the signal is missing (it is beyond cut off). During this period, r-f energy is supplied from the tank circuit so that the operation is the same as if plate current flowed constantly without any interruption of output, and no distortion is

developed. The plate tank is reinforced during each positive half-cycle with sufficient rf to overcome any tank losses, so that the tank is never depleted.

Grounding the suppressor grid provides a shielding action between the screen and plate, and thus prevents secondary emission from the plate. Therefore, coupling between the plate and grid is only through the electron stream, and is at a minimum. In those tubes with suppressors internally connected to the cathode, the operation is identical except there is slightly more coupling between the grid and plate through the electron stream.

Although the input is shown capacitively coupled, it is sometimes inductively coupled, in which case a tuned tank is used in the grid circuit in place of resistor R1. The operation is the same except for the development of a slightly larger grid excitation, since the parallel-tuned tank usually offers a higher impedance than the grid resistor and will cause the input voltage to increase at resonance. Thus, when Class B or C operation is employed, the tank is sometimes added to provide better grid regulation, since grid current tends to shunt the input and lower the grid input impedance.

As is evident from the discussion above, the buffer amplifier operates in paractically the same manner as the pentode r-f voltage amplifier previously discussed as a separate circuit. The only actual difference is in the design considerations, which are based upon light grid and plate loading to provide maximum isolation rather than output voltage or power.

Failure Analysis.

General. The discussion of failure analysis for the Pentode R-F Voltage Amplifier, previously discussed in this section of the handbook, is generally applicable, and is particularly slanted toward receiving application.

No Output. Loss of plate, screen, or filament voltage, a defective tube, defective coupling capacitor C_c , open output coil L2, or shorted grid return resistor R1 can cause no output. Check the tube voltages and supply voltage with a voltmeter. **WARNING:** Voltages dangerous to life usually exist in the plate and screen circuits; be certain to observe all safety precautions when checking these voltages. An open filament can sometimes be observed by noting that the tube is not illuminated and feels cold to the touch. If there is still no output, coupling capacitor C_c is probably open; check for proper capacitance with an in-circuit

capacitance checker. Using a VTVM or voltmeter with an r-f probe (or an oscilloscope), check for voltage between the input and ground. If there is a voltage indication on one side of the coupling capacitor but not on the grid of V1, the capacitor is open or R1 is shorted. (If C_c were shorted, a high positive voltage would appear on the grid from the oscillator plate and cause high cathode bias voltage.) An open screen resistor (R3) will be indicated by lack of screen voltage, although a shorted screen capacitor (C2) will give a similar indication. In the latter case, however, R3 will heat abnormally and drop the screen voltage to zero. This short-circuit condition may be observed visually by smoke from, or discoloration of, the resistor. If the short is prolonged, the resistor will burn out. An open or shorted cathode bypass capacitor (C1) will not necessarily produce a no-output condition; however, if cathode resistor R2 is open, no output will be obtained.

If there is no plate voltage, coil L1 or the RFC may be open (be certain to check the supply voltage to ascertain that the power supply is not defective). If plate bypass capacitor C4 is shorted, the plate supply will be dropped across the RFC, which will heat up and burn out. Coil and RFC continuity can be checked with an ohmmeter *with the power off*.

Usually, a milliammeter is provided in transmitters for measuring the plate current (or a meter can be connected in series between the plate supply and the RFC.) No plate current indicates loss of supply voltage or an open circuit (either in the meter or in the plate circuit). If no dip in plate current can be obtained as C3 is tuned through resonance, either C3 is shorted, there is no drive, or L2 is partially shorted. If the plate current is low and C3 can be dipped properly, but no output exists, output coil L2 is open.

Reduced Output. Excessive bias, insufficient screen or plate voltage, lack of drive, or a defective tube can cause reduced output. Check the bias, plate, screen, and supply voltages with a voltmeter. Low screen voltage will cause insufficient plate and screen current, and will result in low bias and reduced output. Low plate voltage with normal screen voltage will cause the screen to act as a partial plate; the screen may run hot, depending on the value of plate voltage. This can result from a high resistance in the plate circuit caused by a poorly soldered connection, or from a defective tube.

If C3 cannot tune L1 to resonance at the output frequency, a reduced-output condition will be obtained. This can result from a lack of sufficient inductance in L1, caused by a shorted turn, or by a short or open in C3 itself. A check with a grid-dip oscillator, or a wavemeter, will reveal whether the tank circuit is resonant at the wrong frequency.

A leaky or shorted input capacitor (C_c) will place a positive bias on the grid and cause larger than normal plate current to be drawn; at the same time the cathode bias will be increased, so that the effective plate voltage will be reduced. Depending upon the amount of leakage voltage applied to the V1 grid, the output will be reduced, and because the operation is at the bottom of the transfer characteristic curve, the positive signal peaks will be clipped by plate current saturation, causing some distortion in the output. If R1 opens or becomes too high in value with age, coupling capacitor C_c will charge through V1 when the grid is positive with respect to the cathode, but cannot discharge except through existing leakage paths; therefore, the capacitor will tend to accumulate a negative charge and block V1 from operating. Actually, when C_c is charged, no further grid current flows. When the input signal becomes negative-going, C_c discharges through the high shunt leakage paths in the tube and grid circuit, producing a negative bias.

Since the capacitor cannot completely discharge before the next conduction period, it eventually accumulates sufficient charge to hold the grid at cutoff.

Distortion and Other Effects. The buffer amplifier is subject to all forms of distortion common to other r-f amplifiers, except that buffer operation usually implies the amplification of only a single radio frequency. Since tuned tank circuits are used, any tendency toward distortion is usually swamped out by the tank. The tuned tank also minimizes any distortion caused by multiples of the original frequency, or harmonics. Although harmonics exist, they are not selected by the tuned circuit and are greatly attenuated in the output. Clipping and bottoming can cause a tendency toward peak flattening, but the tank circuit tends to supply the energy during the cutoff periods. Thus, the usual effect is to produce a reduction in amplitude and to retain the sinusoidal waveform. When the buffer also acts as a power amplifier, this reduction in distortion may not be obtained to as large an extent. Normally, no neutralization is required; however, it is possible to change the lead dress during repair and cause external feedback because of inductive or capacitive coupling between the relocated leads. Do not change the lead dress of r-f amplifiers unless absolutely necessary.

TUNED COMMON-BASE R-F AMPLIFIER

Application.

The tuned common-base r-f amplifier is used in receiver input stages to provide low noise, and good selectivity rather than high r-f gain, and to eliminate images and spurious signals in superheterodyne receivers.

Characteristics.

Uses common-base configuration.

Uses fixed bias (except when automatic gain control is employed), although self-bias applications may be encountered.

Uses a single-tuned tank circuit to provide selectivity.

Transistor gain is less than unity, but tuned resonant circuits provide some gain.

Does not require thermal compensation.

Because of lower output capacitance, is operable at higher frequencies than any other configuration.

Usually requires neutralization or unilateralization to prevent oscillation.


Circuit Analysis.

General. Because of its lack of gain, the tuned common-base r-f amplifier is generally used as an isolation stage between the antenna and mixed stage, particularly in medium-frequency (broadcast) receivers. While the tuned circuits offer some increase in signal gain, the transistor gain is always less than one. Since images and spurious signals are not discriminated against in receivers having their inputs coupled to the mixer stage, the selectivity and noise reduction effects of the tuned r-f amplifier provide better performance.

Because of the low base-collector capacitance in r-f transistors, the common-base circuit is usually used for very high frequencies (the shunt output capacitance is much lower, and better performance can be expected). With the base grounded, a low base circuit resistance exists, and thermal compensation is usually omitted. The common-base circuit is also considered to be inherently unstable over the entire range of

operation, so that neutralization or unilateralization networks are used to prevent oscillation.


Circuit Operation. The accompanying schematic illustrates a typical common-base r-f amplifier using fixed base bias. For simplicity of circuit discussion, it is assumed that no automatic-gain-control (AGC) voltage is applied. (AGC circuits are discussed in the Mixing, Heterodyning, and Automatic Control Circuits Section.) The tuned input circuit consists of parallel-resonant tank L1, C1, with the antenna tapped at the lower end for proper input matching and maximum power transfer. The circuit is arranged for negative ground, which allows both tuned circuit tanks to be grounded in order to avoid body capacitance effects. The input tank is coupled to the emitter by capacitor C2 thus avoiding shunting of the emitter to ground through the low value of dc coil resistance. The emitter dc return is completed by R1. This is essentially shunt feed bias. While R1 could be replaced with an r-f choke (shown in dotted lines in the figure), it is made resistive to avoid "dead spots" caused by any spurious resonances formed by the stray and element capacitance with the RFC, since the stage usually must be tunable over a wide range of frequencies. Fixed voltage divider bias is provided by R2 and R3. (See the introduction to this section for a discussion of base bias.) C5 places the base at r-f ground and removes the dc bias circuits from the radio-frequency path, so that the initial bias is unaffected by signal variations. Output tank C3, L4 is tuned to obtain maximum selectivity, and the collector output is matched to the base of the next stage through r-f transformer secondary L5. The tuned circuit is placed in the primary rather than the secondary, since tuning the secondary would tend to shift the phase relationships between the primary and secondary. Thus, feedback loop C_N , R_N , provided for neutralization and cancellation of internally developed feedback, remains unaffected by circuit tuning. Transistor Q1 is a high-frequency type of transistor; the case is grounded to provide further shielding and isolation between the input and output circuits. Capacitor C4 bypasses any r-f around the supply, and prevents it from entering the bias circuit.

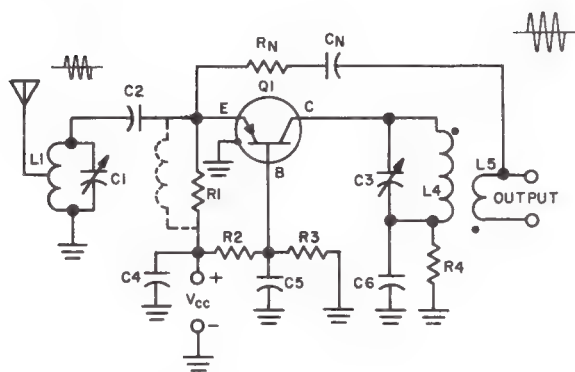

Typical Common-Base R-F Amplifier

The functioning of the r-f amplifier is basically the same as that of an RC-coupled audio amplifier, with tuned tank circuits L1, C1 and L4, C3 acting in place of the emitter and collector resistors, respectively. The difference is that the operation occurs at radio-frequency rates rather than audio-frequency rates. Instead of the amplitude of the audio signal itself causing the emitter and collector currents to vary; it is the amplitude of the r-f envelope at any particular instant which causes these currents to vary. In the case of modulated emissions, the modulation varies the amplitude of the r-f envelope in proportion to the modulation. Thus, the received signal can be considered as an r-f carrier which rises and falls sinusoidally in accordance with the amplitude of the modulation, and is amplified exactly as if it were a single audio frequency, assuming that the input and output circuits are properly tuned and have the required bandwidth. If these conditions are not met, the r-f envelope becomes distorted; that is, a differently shaped signal is formed. The r-f envelope is produced by individual radio-frequency signals varying above and below the zero carrier level. Each cycle produces equal positive and negative alternations, and causes the transistor bias to be increased and decreased equally. The average value over a half-cycle of modulation determines whether the total effect is that of an increased or a decreased signal. Thus, the tips of the r-f pulses trace out a relatively slowly varying signal, which is the audio (or other) modulation, and occurs at an audio (or other) rate—not an r-f rate.

Depending upon the rapidity of rate of change of the audio modulation, a few of the r-f cycles could be lost without significantly affecting the over-all modulation waveshape. The accompanying illustration shows the concept of an r-f envelope and the manner in which it is formed, using a single carrier frequency and a single 400-Hz sinusoidal modulation frequency for ease of explanation. Other more complex waveforms also produce a similar result, which can be demonstrated by a mathematic analysis beyond the scope of this handbook.

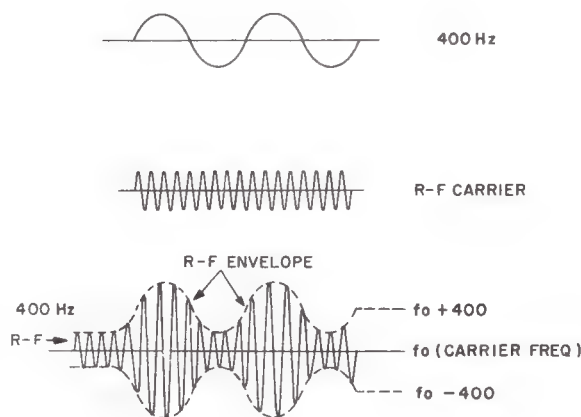

Development of an R-F Envelope

With no signal applied, Q1 rests at its quiescent value of emitter and collector current as determined by base bias divider R2, R3, together with emitter resistor R1 and collector resistor R4. Since the quiescent current is steady, no output is produced. When a signal is applied to L1 from the antenna, a large resonant voltage is developed across tank L1, C1, and is applied through C2 to the emitter of Q1. For ease of discussion, the input tank can be considered as an r-f generator connected between emitter and ground, with an output amplitude equal to the r-f envelope of the signal.

Assume that the input signal amplitude is increasing and becoming more positive, and that the instantaneous value of the signal adds to the emitter bias. As the emitter bias increases in a forward direction, the emitter and collector current increase. Internally in transistor Q1, there is a flow of holes from emitter to collector; externally, the flow consists of

electrons from emitter to collector. A small base current flows from base to emitter (through the base junction), through blocking capacitor C2 and tank L1, C1 to ground, and through C5 to the base. The collector current flow is from ground through R4 and tank L4, C3 to the collector, and through the collector-to-base junction and C5 to ground. Note that in the common base circuit the collector current is always less than the emitter current ($I_C = I_E - I_B$). When the collector current increases with a signal, a large voltage drop is produced across the output tank impedance, thus developing a positive output signal (the common-base input polarities are identical). Since the L5 secondary is coupled to the L4 primary, current flow through the primary induces an output voltage in the secondary by transformer action. The secondary by transformer action. The secondary output may be either in-phase or out-of-phase, depending upon the connections.

Assume now that the input signal amplitude decreases and goes negative. The emitter forward bias is reduced and less collector current flows. As the input signal goes negative, the collector voltage rises toward the supply value. Since the collector is reverse-biased by the negative supply, a negative output signal is produced. Collector resistor R4 prevents large positive swings from dropping the collector voltage past zero, and causing an overshoot which would drive the collector positive and produce a forward collector bias with consequent high current pulse and distortion, by limiting the total available supply voltage. Thus, a large signal can drop the collector voltage to zero, but the supply voltage will still be less than zero by the drop in R4. (This resistor may not be used in some circuits.) Capacitor C6 bypasses the rf around R4 so that it remains unaffected by signal variations, and in effect grounds tank capacitor C3 to avoid body capacitance effects when the capacitor is tuned.

Neutralizing network C_N , R_N is connected between the secondary of the output transformer and the emitter so that it feeds back an out-of-phase voltage to the emitter and prevents oscillation due to internal feedback within Q1. In r-f amplifiers operating over large frequency ranges, this neutralizing network is usually replaced by a more complicated unilateralization network. Thus, the input circuit remains unaffected by any changes in output, or tuning, over the entire range of operation.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low-voltage ranges of volt-ohmmeters. Be careful also to observe proper polarity when checking continuity with the ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

When checking r-f voltages, always, always use a vacuum-tube voltmeter (VTVM) or an electronic voltmeter with an r-f probe. The conventional voltmeter only indicates dc. Therefore, it is necessary to first rectify the r-f before the voltmeter will indicate properly. This is done automatically in the VTVM, and separately by the r-f probe when the electronic voltmeter is used.

No Output. No input signal, a shorted input or output tank, an open emitter circuit or defective transistor, as well as improper bias, can cause no output. If R1 is open, the emitter circuit will be open, and if R4 is open, the collector circuit will be open; in either case there will be no output. If R2 is open, Q1 will operate at approximately zero bias and no output will occur except for extremely strong signals. Check the dc voltages on Q1 to determine the bias. With a normal supply voltage, for a PNP transistor (with negative ground), all voltages will read positive with respect to ground. The emitter will always be a few tenths of a volt more positive than the base, and the collector will read the lowest (sometimes zero). For example, if R4 were shorted, L4 would be connected to ground, the collector would be at ground potential, and the meter would indicate zero, even though full collector voltage would still be applied.

The tank coils can be checked for continuity with an ohmmeter to determine whether they are open; they must be disconnected when the tuning capacitors are checked. If coupling capacitor C2 is defective, there will be no output. If C2 is open, the emitter voltage will be normal, but there will be no output. If C2 is shorted, the emitter voltage will be low (depending on the resistance of R1), and no output will be obtained. In this case R1 will get hot and possibly burn out.

If bypass capacitor C4 is shorted, the supply will be shorted, with consequent loss of output; if the capacitor is open, only a reduced output may occur. If capacitor C5 is open, the base will be connected to

ground through the bias network, and the r-f signal between emitter and base will be attenuated (depending upon the frequency) and will produce either a very weak or practically no output at all. If L5 is open, no output will be obtained (provided that the capacitive coupling between the primary and secondary is very small. Oscillation caused by a defective neutralizing network, if sufficiently strong, can bias off and block the transistor and thus reduce the output to zero. Check the value of R_N with an ohmmeter, and check C_N with a capacitance checker.

Defective r-f tanks can cause a no-output condition. Defective tanks are most easily located in an operating amplifier by observing whether they tune to a specific frequency, particularly when the tuning dial is calibrated, since any change in component values will change the resonant frequency. If the circuit bias voltages appear to be normal and there is no output, connect a modulated r-f signal generator to the antenna, the emitter, the collector, and the output winding, successively. If the input circuit is defective, the signal will appear when the generator is connected to the emitter. If the transistor is defective, the signal will appear after the generator is connected to the collector. With a defective collector tank, the signal will appear when the generator is connected to the output winding. If the signal does not appear, the output coil is open.

It is important to keep in mind that any slight capacitive coupling at radio frequencies will pass a weak signal, so that a weak output is possible under circumstances which at audio frequencies would be impossible. Thus, where more than one r-f stage is used, it is possible to have a "dead" input stage and yet, through stray capacitive coupling, obtain sufficient signal "leak-through" into the following amplifier to produce a weak output.

Low Output. Low output can be caused by improper bias or supply voltage, a defective transistor, high series resistance or impedance, or a low shunting impedance or resistance. The bias and supply voltage can be checked with a voltmeter. If the value of R1 increases, the emitter bias will be increased, and if the value of R4 increases, the collector voltage range will be reduced; both cases will cause reduced output, and can be checked by use of an ohmmeter. If C5 opens, the base return to ground will be through R3, which places it in series with the input signal; thus the input signal will be reduced, as well as the output signal. High resistances produced

by poorly soldered connections can also cause reduced output. Applying a hot iron to the defective joint will usually restore operation to normal. If R1 deteriorates to a very low value, the input signal will be partially shunted to ground and the output will be reduced. No current gain is obtained through transistor in the common-base circuit, since the collector current is always less than the emitter current by the amount of base current. Nevertheless, when low impedance is used in the input and high impedance in the output, a relative voltage gain will be obtained because of the greater voltage drop across the larger impedance.

Distorted Output. Receiver r-f amplifiers are operated Class A to avoid distortion. If the bias is too high the peaks will be clipped, or if the bias is too low a similar effect will be caused by overdriving, and saturation will occur on strong signals; both effects are forms of amplitude distortion. If the selectivity is too sharp, frequencies outside the bandpass will be cut off entirely or partially attenuated. Thus, on modulated signals some of the sideband frequencies will be lost, and frequency distortion will occur because of the loss of some of the audio signals. Normally, deterioration of parts caused by aging, moisture absorption, etc, will produce a reduction in the tuning circuit Q, and thus result in reduced performance and decreased selectivity, but this will not cause distortion. On the other hand, parts value changes can cause regeneration (positive feedback) at certain frequencies or over a range of frequencies. Such feedback increases the sharpness of tuning and can cause distortion due to sideband cutting. The prime cause is failure of the neutralizing or unilateralization network. Such effects can also be caused by a defective transistor. First check the neutralization network for proper component values, and then check the supply and bias bypass capacitors. In multiple-stage receivers, common impedance coupling can occur through deterioration of the power supply bypass capacitor, thus producing unwanted feedback similar to that encountered in electron tube operation.

Distortion caused by "cross modulation" from strong local signals sometimes exists, and is primarily a fault in design (lack of sufficient selectivity) or the result of too close coupling to the antenna, which produces fundamental overload. Thus, saturation occurs, and the nonlinearly produced causes the unwanted signal to appear on the desired signal as cross modulation. This effect is most noticeable when

operating in the immediate vicinity of strong shore or ship stations. It cannot be remedied by normal parts replacement, but rather by external means, such as changing the input and antenna coupling or inserting a loss network at the input.

TUNED COMMON-EMITTER R-F AMPLIFIER

Application.

The tuned common-emitter r-f amplifier is universally used in receivers and test equipment to provide high r-f gain and selectivity, and to eliminate images or other spurious responses.

Characteristics.

Uses common-emitter configuration.

Uses fixed bias (except when automatic gain control is employed), and some self-bias combinations may be encountered.

Transistor provides high gain (100 or better).

Usually requires thermal compensation.

Requires neutralization or unilateralization only at the lower r-f frequencies, since it is inherently stable.


Circuit Analysis.

General. The large collector-to-base capacitance of the transistor tends to shunt the output to ground, when connected in the common-emitter configuration. Therefore, the amplification tends to drop at the higher radio frequencies. On the other hand, a small change in base current causes a very large relative change in collector current. Thus, the small signal input controls a large current which develops the output voltage; this action is similar to electron tube operation using the grounded-cathode configuration. Although the output impedance of the common-emitter circuit is not as high as that of the common-base circuit, the large collector current flow through a moderate output impedance produces a much larger output. Hence, the common-emitter circuit always gives a large gain. Even at the higher radio frequencies where the gain drops off, it may be possible to obtain sufficient gain over that of the common-base circuit to justify use of the common-emitter circuit instead.

The common-emitter circuit also has a higher input impedance than that of the common-base circuit (on the order of a few hundred ohms). Conse-

quently, it is easier to match the input (and the output) circuit for efficient power transfer. As a result, the common-emitter circuit, rather than the common-base circuit, tends to be used universally.

Circuit Operation. The accompanying illustration shows a typical tuned r-f amplifier using the common-emitter configuration. L1 and C1 form the input tuning circuit, with both the antenna and the base tapped onto L1 to provide a proper impedance match. Capacitor C2 bypasses the lower end of L1 to ground for rf, and also bypasses bias resistor R1. Fixed base bias is provided by voltage divider R1, R2. (See the introduction to this section for discussions of bias and bias stabilization.) Thermal stabilization is provided by emitter swamping resistor R3 bypassed by C3. The output tank consists of C4 and L2, with the supply voltage fed at approximately the center of the coil. Thus, an out-of-phase voltage is obtained and fed through C_N for neutralizing the transistor. L2 is also tapped at appropriate points to match the collector and the output circuit. The output is capacitively coupled through C_{cc}. Capacitor C5 functions to bypass rf around collector resistor R4 and the supply, and also to maintain the center of the coil at ground potential, in order to insure the proper phase relationships between the ends of the tank coil. R4 is a voltage-dropping and isolation resistor in the collector circuit (it is not always necessary to use R4).

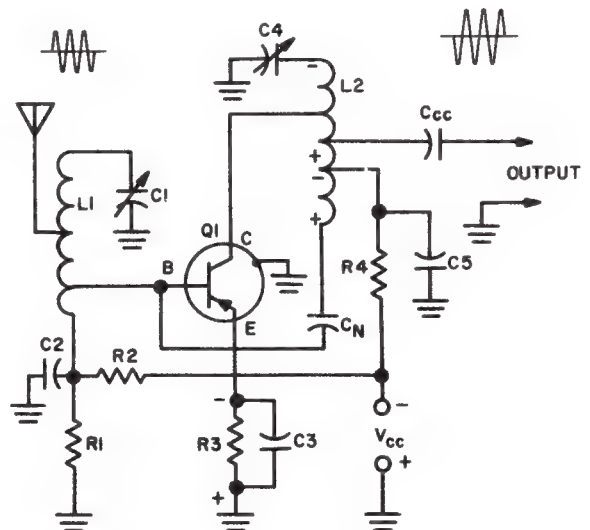

Typical Tuned Common-Emitter R-F Stage

Operation of the tuned common-emitter r-f amplifier is very similar to the previously discussed R-C coupled audio amplifier using the common-emitter circuit, with the tuned tank circuits replaced by resistors. The basic difference is that the audio amplifier operates at low frequencies with relatively slowly varying signals, whereas the r-f amplifier operates at much higher frequencies and follows the relatively slowly varying envelope amplitude when modulated. When not modulated, continuous-wave signals within the bandpass of the tuned circuits are amplified equally on the positive and negative half-cycles and vary in amplitude with the average amplitude of the input signal. Thus, as the signal fades in the output signal is larger, and as it fades out the output signal is smaller. The action, meanwhile, occurs at the r-f rate; for example, a continuous r-f signal of 30 megahertz requires a time of only one thirty-millionth of a second to complete one cycle of operation.

At the start of the cycle of operation the transistor is resting in a quiescent condition, with the collector current determined by the dc base bias, which is fixed for a specific supply voltage by voltage divider resistors R1 and R2. It is usual practice to bias the base negative with respect to the emitter (forward bias). The difference in potential is normally only a few tenths of a volt, and is set at the center of the forward transfer characteristic curve for Class A operation. Since the received signal is normally on the order of microvolts, the low bias value is adequate to prevent overloading (except in the case of strong local signals). Either automatic or manual gain control is usually provided in practical r-f stages to accommodate large signals; this is not shown in the schematic, to avoid circuit complication and for ease of discussion. (See the Mixing, Heterodyning, and Automatic Control Circuits Section for the functioning and operation of semiconductor automatic gain control circuits.)

Assume that an r-f signal within the bandpass of the tuned input (tank) circuit, consisting of L1 and C1, appears at the antenna. With the antenna tapped onto L1 at the proper number of turns to match its impedance, the low-impedance antenna resistance is transformed by autotransformer action to match the large parallel resonant impedance of the tank. Thus, maximum signal transfer from the antenna to the coil is obtained. In turn, the base is also tapped onto L1 for a proper impedance match, to change the low

input resistance offered by the common-emitter circuit to a value that more closely matches the high impedance of the tuned input circuit. With bypass capacitors C2 and C3 effectively grounded the bottom of L1 and the emitter, respectively, as far as rf is concerned, the tuned input circuit is connected between the base and the emitter. Thus, the r-f signal does not flow through the bias voltage divider or the emitter swamping resistor (R3).

Assume, for the moment, that the input signal is swinging negative and adds to the forward base bias, thus producing an increase in collector current, (which is a flow of electrons from the supply through L2 to the collector). Application of the instantaneous negative signal voltage to the base of Q1 causes a flow of holes from emitter to base. This is the same as a flow of electrons from base to emitter, and a circulating base current flow occurs from the emitter through C3 to ground, and through C2 and the lower portion of L1 back to the base. On the positive half of the input signal the forward bias is reduced, and the collector current, likewise, is reduced. Electron flow and base current flow are through the same path as given previously for the negative half-cycle, but is diminished in value. With equal positive and negative swings, an average value of base current flow occurs, and varies in accordance with the signal amplitude. The collector current follows, but it is larger in amplitude since it is approximately equal to beta times the input signal.

Since the input tank circuit is tuned to the frequency of the incoming signal, only r-f signals within the bandpass of the tuned circuit appear at the base and affect the collector current. The amount of selectivity of the tuned circuit depends upon the unloaded Q of the tank. When this Q is high, the tuned circuit is highly selective, and only a narrow band of frequencies is accepted by the tuned circuit. Thus, the base current is controlled by the tuning of the tank circuit. When the tank circuit is resonant to the signal, a base current is injected into the transistor; when it is nonresonant, only the dc (bias) value of base current flow exists.

In the collector circuit, the load impedance across which the output is developed consists of tuned tank circuit L2, C4. Coil L2 is bypassed to ground for rf at the supply voltage tap by C5. Thus, the rotor of tuning capacitor C4 can be grounded to avoid body capacitance effects when tuning. The portion of L2

between the supply and the lower end of L2 forms a neutralizing winding, which furnishes 180-degree phase shift and supplies an out-of-phase voltage back to the base through C_N . Thus, the effect of the tuned input and output circuits being coupled through the transistor collector-to-base capacitance and the internal base spread resistance of Q1, which causes positive feedback and oscillation, are cancelled out. This type of neutralizing circuit is similar to the Hazeltine neutrodyne method used with electron tube operation. Since the output impedance is the low input resistance of a following common-emitter stage; the coupling capacitor is tapped at some intermediate value of turns ratio between the supply and collector taps. Thus, a step-down ratio is provided to match the transistor output for maximum power transfer and gain. The collector is also shown tapped down on L2 for proper matching, assuming that the tuned tank impedance is higher than the collector impedance. This is usually true at low r-f ranges; however, at high radio frequencies, such as in the UHF region, the tank and collector impedances may be of the same order, in which case the collector may be connected to the top of L2. (In some circuit versions a deliberate mismatch may be arranged and the neutralizing arrangement dispensed with.)

Regardless of the impedance-matching or neutralizing methods used, however, the output signal is developed across the impedance provided by the parallel tuned tank circuit. At resonance the impedance is high, and off resonance it is a lower value. Thus, for frequencies within the bandpass of the tuned circuit, the impedance is high, and a large voltage drop occurs across this impedance. With a negative-going input signal the collector current flow causes a drop across the parallel-tuned tank which reduces the collector voltage toward zero. Since the collector is reverse-biased, the output is positive-going. When the input signal swings positive, the forward bias is reduced, which reduces the collector current also. Less voltage drop occurs across the output tank, and the collector voltage increases in a negative direction, thus producing a negative output signal (common-emitter output and input polarities are always opposite). These positive and negative signal excursions occur at an r-f rate. For a constant-amplitude input, a constant, amplified output signal is developed. If the signal is modulated, the output amplitude follows the waveform envelope, and the output amplitude varies in accordance with the modulation. With signal

swings less than the applied base bias, no distortion is produced. If the input signal is greater than the bias, or if the collector voltage is dropped to zero before the peak occurs, then clipping and distortion effects are produced. Resistor R4 is used to drop the collector voltage to the proper value and to act as a decoupling resistor. It also prevents the collector voltage from being driven positive by strong signals, which would forward-bias the collector and cause heavy current flow with distortion. The transistor case is grounded to provide better shielding and prevent r-f feedback.

Normally, swamping resistor R3 is affected only by slow dc variations of emitter current caused by ambient temperature changes. The increased emitter current flow with temperature produces a voltage R3 which opposes the bias voltage and reduces the emitter current back to its original value. Any r-f signal is bypassed across R3 by C3. This is conventional emitter swamping action.

The output is shown capacitively coupled since it is usually more economical than providing a secondary winding to couple out of L2, plus the fact that at high frequencies it is sometimes difficult to obtain optimum coupling between windings because of high-frequency effects. Any of the tapped tanks shown in the schematic can be replaced by tuned transformers without any change in operation, if they have sufficient coupling, if they tune to the same frequencies, and if they tune over the same range. Circuit cost and designer's preference usually determine which are used.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low-voltage ranges of volt-ohmmeters. Be careful also to observe polarity when checking continuity with the ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

When checking r-f voltages, always use a vacuum-tube voltmeter (VTVM) or an electronic voltmeter with an r-f probe. The conventional voltmeter indicates only dc. Therefore, it is necessary first to rectify the rf before the voltmeter will indicate properly. This is done automatically in the VTVM, and separately by the r-f probe when the electronic voltmeter is used.

No Output. Open base, emitter, or collector circuits or short-circuited input or output circuits, as well as lack of supply voltage or a defective transistor, can cause no output. If either L1 is open or C1 is shorted, no output will be obtained. If L1 is disconnected from C1, both the continuity of L1 and the shorting of C1 can be checked with an ohmmeter. Lack of supply voltage as well as bias voltage can be determined by use of a voltmeter. Proper base bias indicates that the bias divider and lower part of L1 are connected to the base. Likewise, proper collector voltage indicates that R4 and L2 are satisfactory and that tuning capacitor C4 is not shorted. If C5 is shorted, the full supply voltage will be dropped across R4, and there will be no output. If coupling capacitor C_{cc} is open, no output will be obtained (although there is a possibility that a strong signal may still feed through as a weak signal by stray capacitive coupling). If emitter resistor R3 is open, there can be no output. If neutralizing capacitor C_N is open and the feedback is sufficient, the transistor may be blocked, with consequent loss of output, although it is more likely that a low output with squeal and distortion will be obtained. However, if C_N is shorted, the base and collector will be shorted through the neutralization coil and no output will be obtained.

Normally, the collector voltage will be lower than the supply voltage because of the drop across R4. A high collector voltage will indicate improper bias on the base, or lack of collector current due to a defective transistor or an open emitter resistor (R3).

Low Output. If the forward bias is too low, if the collector voltage is low, or if the transistor gain has deteriorated, a low output will be obtained. High-resistance soldered connections in the input and output tanks or nonresonance can also cause a reduction of the output. If emitter resistor R3 increases in value or bypass capacitor C3 opens, the output will likewise be reduced by emitter degeneration effects. The bias and collector voltages can be checked with a voltmeter, and R3 can be checked with an ohmmeter. An open bypass capacitor C2, C3, or C5 can cause a reduction of the output through loss of r-f signal in the bias and supply circuits and by emitter degeneration; a bypass capacitor can be quickly checked by temporarily shunting an equivalent capacitor across it. An increase in output when this is done indicates that the original capacitance is insufficient. To determine that the tuned circuits are operating properly, insert a modulated signal from a signal generator

into the antenna, and use an oscilloscope with an r-f probe to determine whether the signal appears at the base and the collector. Tuning the tank circuits will cause the signal to increase in amplitude at the resonant frequency. If the tuning has no effect, the tanks are open or shorted and must be disconnected and checked individually. When the circuit components appear to be operating normally and the output is low, the transistor is probably defective.

When AGC voltage is fed into the base circuit to control the volume automatically, do not neglect the possibility that too great an AGC voltage may be biasing-off the stage. With a properly functioning circuit, the AGC voltage will vary in accordance with the strength of the input signal, or with the tuning, as the desired signal is selected. With delayed AGC it is normal for the AGC bias voltage to be almost zero with weak signals so that full sensitivity is obtained.

Distorted Output or Poor Selectivity. If the bias is too high or too low, the signal may be clipped by operating at or near saturation or cutoff, respectively. If there is excessive regeneration at some frequency, the tuning may be sharpened sufficiently to cause sideband cutoff, and frequency distortion will result from the loss of original frequencies now outside the reduced bandpass. Poor selectivity (broad tuning) is usually caused by high resistance in the tuned circuits due to poorly soldered joints or aging. A lowering of the tuned circuit Q can also cause a broadening of the selectivity curve and reduce the apparent gain. With calibrated dials, reception of the signal at the wrong frequency indicates a change in circuit constants in the tank, or a change in the stray and distributed shunt capacitance in the tuned circuit. Usually, a readjustment of the trimmer capacitors will restore the calibration to normal. It is particularly important while repairing or trouble-shooting r-f circuits not to disturb the lead dress or reroute the wiring; otherwise, a change in stray capacitance (or inductance) will cause improper tracking of the tuned circuit. Moisture absorption in coils and dielectrics plus aging effects can cause a loss of Q, which can be restored only by replacing the tuned circuits or by removing them and baking them in an oven to remove the moisture. A salt spray film can cause a low shunt resistance across a tuned circuit and require washing and drying to provide normal results. In receivers using multigang tuning capacitors, it is common for the oscillator to become detuned and off-calibration enough that the signal is outside the r-f bandpass of

the tuning capacitor in the r-f and mixer stages. A loss of gain, cutting of sidebands, and distortion can result.

SINGLE-ENDED R-F AMPLIFIER (ELECTRON TUBE) (CLASS B OR C)

Application.

The single-ended Class B or C r-f power amplifier is used universally as an intermediate r-f power amplifier (driver) stage, or output (final) amplifier for transmitters, and in special instances for test equipment. (Normally, receivers and test equipment use Class A amplifiers.)

Characteristics.

Uses either Class B or Class C bias.

Output efficiency varies with bias; approximately 50 to 60 percent for Class B operation, and 70 to 75 percent for Class C operation.

Uses a tuned r-f tank circuit to develop the output frequency.

Is neutralized for triodes, but not for pentodes or screen-grid tubes.

Input frequency is usually the same as the output frequency.

Provides high output power and current gain.

Requires grid drive power equivalent to approximately 10 percent of plate output power, or less, depending upon type of tube used.

Normally uses fixed bias, but can also use self (signal) bias and protective cathode bias, or a combination of both.


Circuit Analysis.

General. The alternating component of plate current in a Class B r-f amplifier is proportional to the amplitude of the input (exciting) signal. Therefore, the power output varies as the square of the excitation (drive) voltage. Normally, in CW operation, maximum drive and maximum output are used. When used to amplify a modulated r-f signal, the output must vary linearly with the input so that no distortion is produced; also, the output varies in amplitude in accordance with the modulation. Consequently, for operation as a linear r-f amplifier, more stringent limits must be placed on bias, excitation, and plate voltage than for CW operation. In addition, to allow for the constant load and provide an overload safety

factor, the stage is usually operated at a 20 percent reduction in rated maximum (CW operation) power. (Since the CW stage is keyed, it does not operate at full power continuously, and can therefore be used at the higher ratings without damage.) Other considerations which are applicable to the modulated Class B linear amplifier will be discussed at the end of this article, since slightly different operating conditions are necessary to provide for modulation amplitude increases.

The Class C r-f amplifier is similar to the Class B r-f amplifier, except that it operates at a much higher grid bias, it requires correspondingly greater excitation with more drive power, and it usually operates at a higher plate voltage and current. As a result, greater output and efficiency are obtained. In the Class C stage the alternating component of plate voltage is directly proportional to the plate voltage (not the grid voltage as in Class B operation). Thus, the output power is proportional to the square of the plate voltage. This is why high-level modulators vary the plate voltage of the Class C r-f amplifier stage to produce amplitude modulation.

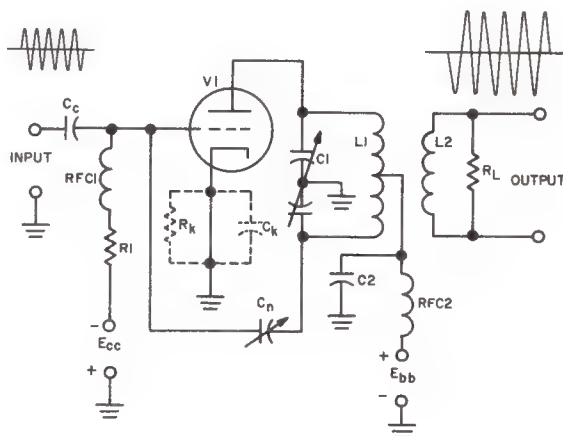Circuit Operation. The schematic of a typical Class B or C triode r-f power amplifier is shown in the accompanying illustration.



Class B or C Triode R-F Power Amplifier

Although pentode, tetrode, or beam-power tubes could have been used in place of the triode, the triode is used here for ease and simplicity of discussion. Considerations involving other types of tubes will be

discussed at the end of this article. The input circuit is shown capacitively coupled by C_c , although any other form of coupling could be used instead. Grid bias (in addition to bias from the fixed supply) is produced by the driving signal, which causes rectified grid current flow through R1; RFC1 prevents shunting of the drive signal to ground via R1. (Protective cathode bias is sometimes provided by cathode resistor R_k bypassed by C_k , and is shown in dotted lines since it may not be used. When it is not used, the cathode is connected directly to ground.) See the introduction to this section for a complete discussion of cathode bias and shunt grid-leak (signal) bias. The tuned plate tank consists of C1 and L1, with output link coil L2 inductively coupled to it (capacitive coupling or another form of coupling such as a Pi-network is sometimes used instead of L2). The plate voltage is series-fed through RFC2, which is bypassed by C2 for rf (shunt plate feed is also often used). This arrangement ensures that any rf at the center tap on L1 is bypassed to ground through the low-impedance path offered by C2 rather than the high-impedance path offered by RFC2 and the power supply filter capacitor. With the center of L1 grounded, both ends of the coil are at opposite and equal potentials. Split-stator tuning capacitor C1 maintains the balanced arrangement, and permits the rotor to be grounded in order to avoid body capacitance tuning effects (shunt plate feed permits the capacitor and coil to be directly grounded). A neutralizing voltage is taken from the end of the tank opposite the plate, and is fed back to the grid through capacitor C_n . In this plate neutralization method, C_n effectively forms part of a bridge circuit which balances out the plate-to-grid interelectrode tube capacitance and prevents feedback and self-oscillation of V1.

As is evident, the schematic is similar to that of a neutralized r-f voltage amplifier, which has been previously discussed in this section of the handbook. The difference in operation is due to the use of cutoff bias, greater drive, and short pulses of plate current conduction, which provide greater power output. Class B and Class C amplifiers are discussed separately in the following paragraphs because of the differences in their operation.

Class B Operation. Normally, V1 conducts for only a portion of a cycle, usually for 180 electrical degrees, but not less than 160 degrees (otherwise, the

operation becomes Class C). The tube is supplied with energy from the tank circuit during the nonconducting portion of the cycle, which provides a so-called "flywheel effect" to keep the circuit oscillating despite the absence of plate current flow for the nonconducting half-cycle of operation. Thus, the r-f output is continuous and a steady output signal is maintained, as long as the key is down. (In Class B audio (untuned amplifier) operation, another tube is needed to supply the energy for the negative half-cycle.)


When the drive signal (r-f excitation) is applied through C_c , the grid of V1 is momentarily driven positive when the positive half-cycle of input signal exceeds the fixed negative bias voltage, and both plate current and grid current flow during this interval. Plate current flow is not continuous throughout the cycle, but is in the form of short pulses of energy, one for each cycle. During this time dc grid current flows from ground to the cathode and charges C_c , when the input goes negative, C_c discharges through R1 back to ground. Electron flow is in the direction which makes the grid end of R1 negative, thus producing a signal bias. Radio-frequency choke RFC1 presents a high impedance to the exciting r-f signal and presents it from being shunted to ground through R1. Thus, only the rectified dc component of grid current flows through R1 to develop the bias. The amount of dc grid flow is averaged over the complete cycle to provide a steady dc bias voltage. This signal bias is in addition to the negative dc fixed bias voltage, which is applied between R1 (or the grid of V1) and ground. The fixed bias automatically provides protection in the event that the grid drive is interrupted, so that complete loss of bias cannot occur. The total bias is the sum of both the fixed bias and the signal bias. Regardless of the type of bias employed, the operation is similar. Tube V1 does not conduct until the exciting voltage drives the grid above cutoff. Once above cutoff, plate current flows and increases as the grid voltage increases. Grid current does not flow until the grid-drive voltage reduces the total bias to nearly zero. From this point on grid current also flows, reaching its peak at the same time as the peak of plate current flow.

When plate current flows, the tuned tank circuit offers a resistive impedance at the frequency of resonance, which drops the effective plate voltage to its minimum value at the peak of the conduction cycle.


At this time the tank circuit absorbs energy from the plate circuit. At the same time the plate is also dissipating some energy; this plate dissipation is at a minimum, since the effective plate voltage is at its minimum also, and maximum efficiency is obtained.

As the amplitude of the grid excitation now decreases toward zero and then swings negative on the following half-cycle, the grid bias is increased and the plate current is decreased. When the plate current decreases, the voltage drop across the load (or tank impedance) also decreases and the plate voltage rises. When plate current cutoff is reached, the plate voltage is just equal to the source. However, the circuit does not cease operation, since the tank circuit contains r-f energy which is now released to the load. From the moment of cutoff until current is again drawn on the next half-cycle of operation, the tank keeps supplying the energy. This is so-called "fly-wheel" action of the tank circuit. During this time (when no plate current flows) the tank circuit is completing its half-cycle of operation, and the instantaneous plate voltage continues to rise until the peak tank voltage is reached. The plate voltage at this point is higher than the source or supply voltage, but, since the tube is biased far below the point of conduction, it has no effect on V1. The tank circuit now swings negative and the plate voltage drops toward the dc supply voltage. At the same time, the peak of negative grid swing is reached and the grid drive signal swings positive, thus reducing the total bias. Eventually, cutoff is passed and the tube is driven into conduction again. As the positive drive voltage increases, the effective bias decreases and plate current flow continues to increase. The plate current flow causes a voltage drop across the impedance of the load (or tank circuit), and the effective plate voltage is again reduced. Near zero bias grid current again flows, increasing to maximum at the peak of the drive signal, which corresponds with point of minimum plate voltage. The cycle now repeats over and over again as long as the circuit is completed (key is held down).

The accompanying illustration shows the manner in which the plate current varies with grid voltage. The grid-plate transfer characteristic curve is assumed to be linear. Actually, there is always a slight amount of curvature near zero bias (the bottom) and near saturation (the top). Therefore, in linear operation the bias for "projected cutoff", which is slightly different than for actual cutoff, is employed, and any curvature near cutoff is neglected (it will produce only a small amount of distortion, which can normally be tolerated). As can be seen from the figure, the plate current is proportional to the drive signal amplitude up to saturation. After the saturation region is reached, the plate current will vary only slightly for a large change in excitation until full saturation is reached, at which point there is practically no change in plate current for any further change in excitation. This is shown more clearly in the following graph, which also indicates how linearity and saturation are affected by different load impedance in the plate tank. Note that in the first curve, produced by a high load impedance, it takes less grid excitation voltage to reach saturation than for moderate and low impedances, as shown in curves 2 and 3. The closer the curve is to saturation, the nearer the output voltage is to the plate voltage. The output voltage never equals or exceeds the plate supply voltage, since the minimum plate voltage is always made greater than the peak value of the grid excitation voltage in order to prevent excessive grid current flow. If the positive grid were allowed to become greater than the effective plate voltage the grid would then act as a plate and tend to carry all the cathode current. Besides causing grid overload and damage to the tube structure, the plate current would actually be interrupted, which is the same as if the plate were driven negative at this time, and distortion would be produced. Recall that at the peak of grid swing the plate current is greatest and rf is being absorbed by the tank circuit; thus, an interruption of current at this point cannot be tolerated.

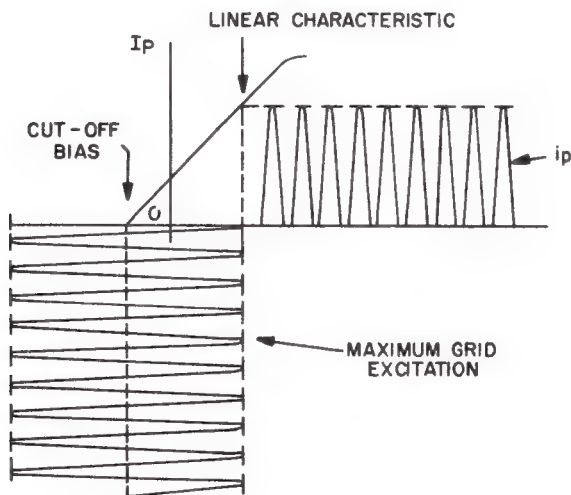

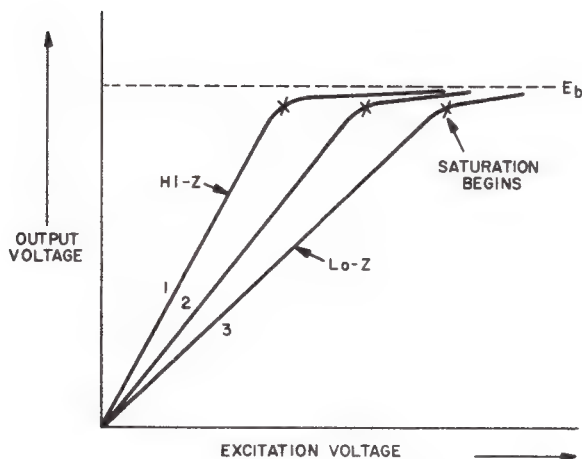Grid Voltage and Plate Current Relationship for Unmodulated Class B Linear Amplifier




Saturation Curves, Showing Effect of Load Impedance

In CW operation it is unimportant whether or not the transfer curve is exactly linear, since no modulation is applied and maximum output with a usable waveform is all that is necessary. Any slight distortion due to nonlinearity is effectively swamped out by the

effect of the tuned tank circuit, so that approximately a sine-wave output is always supplied. Even when driven into heavy saturation the plate waveform will be satisfactory, but more drive power than is needed will be used, and the driver tube may be overloaded. On the other hand, when a modulated signal is to be amplified, it is important that the characteristic curve be linear in order to retain the shape of the modulation without distortion. The following grid-voltage, plate-current curve shows the relationship when modulation is applied. As long as the linear portion is not exceeded (the drive is adjusted correctly), no distortion exists. This is normal Class B linear operation. Should the drive be too low the output will be undistorted, but the full amplified power output will not be obtained and the efficiency will be lower than normal. Since the linear amplifier must provide four times the resting power for full 100 percent modulation capability, the carrier level is normally adjusted for half the maximum current with full excitation and no modulation. When the current doubles on the modulation peaks, the power output will vary as the square of this current, and produce a peak output four times normal. When modulated, the Class B r-f amplifier stage has stricter requirements. The grid bias must not vary with modulation; hence, only fixed bias is used and a constant plate voltage supply is required. Usually, the driver is larger than necessary for CW operation and the grid of the linear amplifier is loaded down with resistance to provide better regulation with a more nearly constant load on the driver. Since maximum plate dissipation occurs in the resting (or quiescent) condition, the efficiency at this point drops to about 33 percent, and reaches maximum efficiency at the peak of the modulating signal of about 65 percent. Since the peaks on voice modulation are of short duration, the total over-all efficiency drops (where in CW operation full power and efficiency are obtained constantly), so that a maximum of 50 to 55 percent is obtained under modulation. To ensure that the tube is not overloaded in the resting (quiescent) condition, lower plate voltage is used than for CW operation. Since Class C operation allows the amplifier to be driven harder and greater efficiency to be obtained, Class B linear operation is used mostly for amplifying low-level AM modulated signals. In the case of single-sideband operation, the linear Class B stage is the only type of amplifier suitable for producing undistorted amplification of the r-f sideband signal

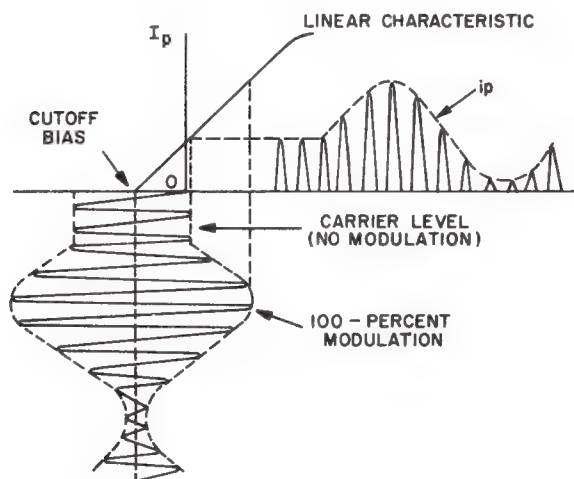(Class C would cause distortion). Where the modulation is developed in the output (high-level modulation), the Class C amplifier is always used.




Grid-Voltage, Plate-Current Relationships for Modulated Class B Linear Amplifier

Class C Operation. The Class C stage is biased far beyond cutoff (2 to 4 times), so that the conduction occurs only over a range of 100 to 120 electrical degrees of the cycle. Since plate current flows for a shorter period of time, greater efficiency is obtained (the losses are less), reaching a maximum of 75 to 80 percent. The circuit is identical with that of the Class B stage, but higher plate voltage and more grid drive are required (the bias is much higher). During the nonconducting portion of the cycle, energy is supplied to the circuit from the tuned tank, just as in the Class B stage. The operation is identical except that the plate conduction period is shorter, and the output is no longer proportional to the amplitude of the excitation signal. Instead, the output is now proportional to the plate voltage. The r-f drive is kept constant at maximum amplitude in order to drive the tube to full saturation. The Class C amplifier is also

linear, but with respect to plate voltage. If the plate voltage is doubled, the plate current is also doubled, and the power output is then four times normal.

In CW operation, maximum drive and maximum plate voltage are used to obtain a greater output. Because of the greater efficiency obtained, the power output of the Class C power amplifier for a given plate voltage is greater than that obtained from a Class B amplifier for the same plate voltage.

When a modulated signal is applied to the grid of a Class C amplifier, the amplifier conducts only while the signal is above cutoff, and a distorted plate output signal appears with part of the modulation cut off. This is shown graphically in the following illustration. On the other hand, if the modulation is applied in the form of an ac plate voltage which alternately adds to and subtracts from the normal dc plate voltage instantaneously in accordance with the modulation, then the modulation envelope will be reproduced without distortion, since the instantaneously varying plate voltage produces a varying output of similar waveform, as shown in the accompanying illustration.

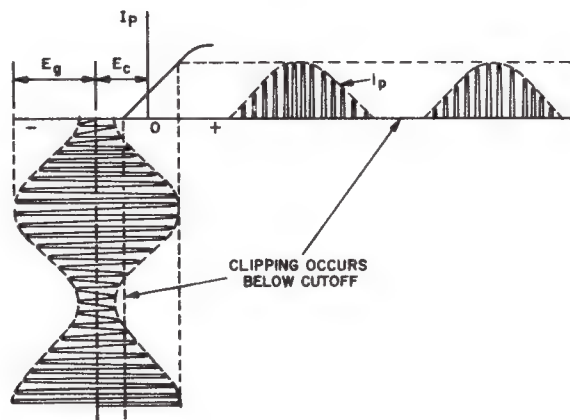

Grid-Voltage, Plate-Current Relationships in a Modulated Class C Amplifier

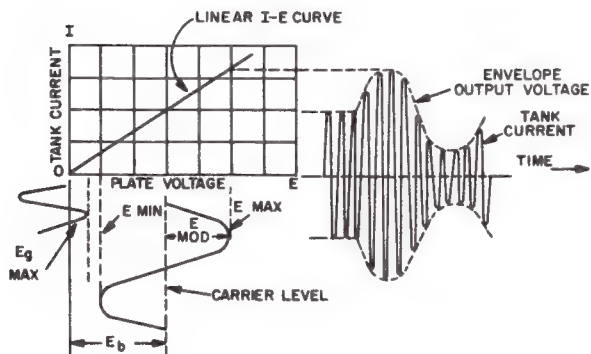


Plate Voltage and Plate-Tank Current Relationships
in a Modulated Class C Amplifier

Note that the tank circuit current variations produce equal positive and negative swings so that a symmetric output envelope is generated, and a minimum plate voltage greater than exciting voltage E_g always occurs. Thus, at no time is the grid voltage more positive than the plate voltage, and excessive grid current cannot flow. The following waveforms show the instantaneous voltage and current relationships in both the grid and plate circuits on the same time basis. Plate voltage variation is shown in part A of the figure, grid current and plate current variations are shown in part B and grid voltage is shown in part C.


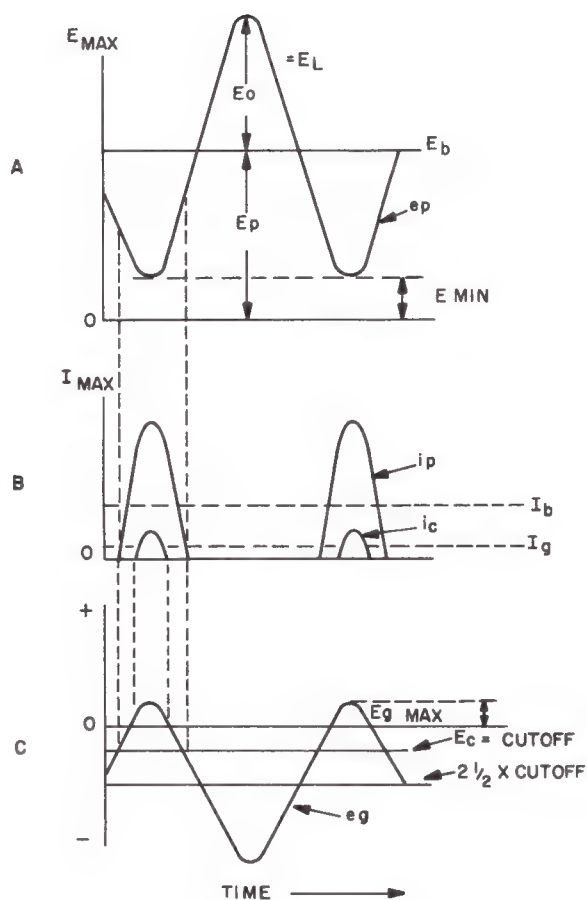
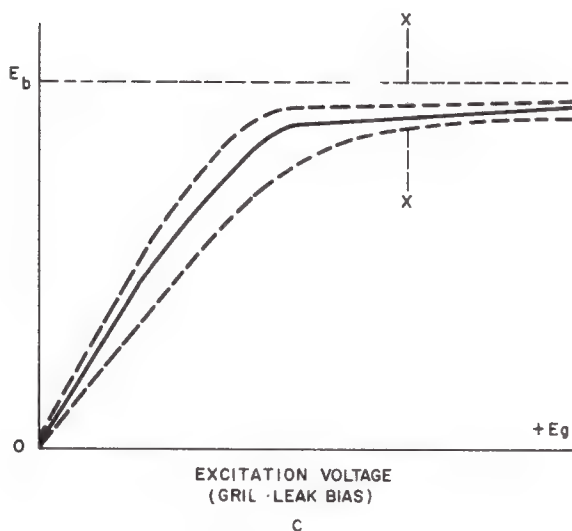
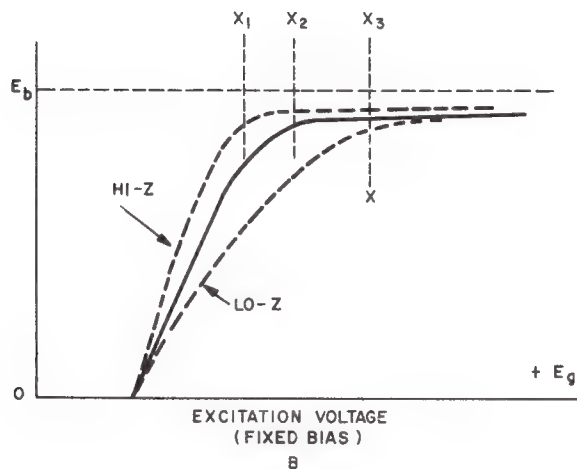


Plate and Grid Waveforms in Class C Operation

The grid bias is shown as E_c and the exciting or drive voltage as E_g . The supply voltage is E_b , and the ac plate voltage drop across the load is E_l , which is also the output voltage, E_o . Note that E_{min} and $E_{g\ max}$ always occur simultaneously, and that all waveforms are sinusoidal since they are developed across tuned tank circuits. (If the grid circuit of V1 does not contain a tuned tank, the effect of the driver stage tank produces the same result.) The plate-current pulse is always much less than half a cycle, and grid current i_g flows only when the grid is positive. The total instantaneous cathode current is the sum of i_p and i_g (in a pentode the screen current is added). The average value of the plate-current pulse over a complete cycle is the direct current, I_b , which is drawn from plate supply E_b . Likewise, the average value of the instantaneous grid current, i_g , is the dc grid current, I_g (averaged over a complete cycle). The plate input power is $I_b \times E_b$. The plate load impedance is connected in series with the plate supply to develop the desired output voltage when plate current pulses flow. The output magnitude is controlled by varying the coupling of the load to the tuned plate circuit. While the plate tank appears as a purely resistive load at resonance, the actual load is the antenna and associated transmission line. When matched, this combination is resistive also, but if not properly matched it may produce a reactive effect (either capacitive or inductive), and require that the plate tank be returned to resonance. This detuning will vary with the degree of coupling to the load. The division of energy between the tuned circuit and the tube is always proportional to the respective voltage drops across them. The drop across the tuned circuit (and reflected load represents useful r-f output, while the drop across the tube resistance represents a loss of energy which is dissipated by the plate as heat. This plate loss is equal to the instantaneous plate current multiplied by the instantaneous plate voltage ($i_p \times e_p$); except for the small amount lost in the resistance of the tank circuit, the plate loss represents the bulk of the inefficiency, which is usually not more than 25 percent.

The accompanying figure shows the saturation characteristics of a typical Class C amplifier for different values of bias and degrees of excitation. In part A the solid curve, "A", represents Class C operation, and the dotted curve, "B", represents Class B operation. The Class B stage is always operated between zero and point 1, where saturation begins. The region is linear; that is, the output varies directly with the input. The Class C stage, however, is always operated to the right of point 1, and usually around point 2, which is in the heavy saturation region. Thus, no current flows until sufficient excitation exists to drive the tube into conduction. As the drive is increased, the current also increases quickly to light saturation at point 1. From point 1 to point 2 there is not much increase in plate current with an increase in drive, and beyond point 2 there is practically no change at all. This is the normal operating point at heavy saturation, and represents the most efficient operation. While below point 1 the output will vary with the input, it is not linear and much distortion will be produced. In part B, the start of saturation is indicated for various values of loading. The high-impedance load at X1 will require less drive than that at X2 for the medium-load impedance, and much more drive is needed to reach X3 with a low-load impedance. In each of these cases the operation is still Class C, but the plate currents, minimum plate voltages, and drive power required are all different. A small tuning capacitance (lo-C) is used to produce the high-impedance condition, while a large tuning capacitance (hi-C) is used for the low-impedance condition. The hi-C tank will also have more losses because of heavier circulating current, and, since the minimum plate voltage is also higher, the output voltage will be less and the efficiency will be at its lowest value. Part C of the figure shows the effect of grid-leak bias on saturation. In this case, the operation is always set at point X to avoid distortion, loss of efficiency, and reduced output. Since the grid bias will vary with the amount of excitation, a low drive current will change the operation into the Class B region, or somewhere between Class B and Class C, with reduced output and distortion.

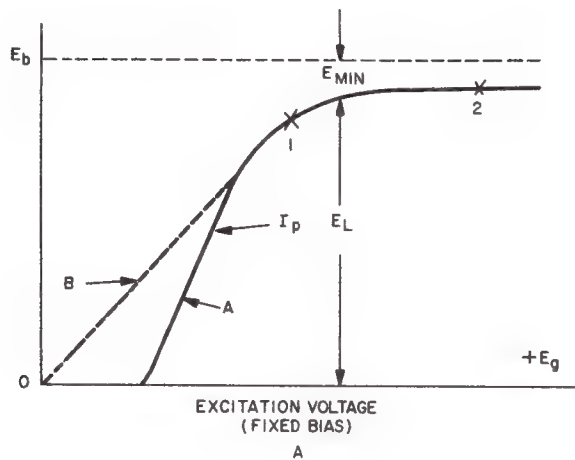

Comparison of Saturation Characteristics of
Class C Amplifier

Thus, it can be seen from the figure that full saturation is always required in a Class C amplifier to prevent any change in drive from affecting the output. With a saturated drive, a larger output can be obtained only by increasing the plate voltage.

Other Considerations. Beam power, pentode, and screen grid tubes are generally used instead of triodes because they require less drive and a larger output can be developed. Also, the screening effect of the screen grid provides reduced grid-plate capacitance and minimizes feedback, so that oscillation will not usually occur, and no provision for neutralization is required. Thus, an over-all saving in parts is obtained. Since the plate is farther from the grid than the screen, it is important to keep the screen voltage higher than the excitation; otherwise, the grid current becomes excessive. However, the minimum plate voltage can now be made lower, and a larger plate obtained. The limiting factor is usually the screen voltage, since if the plate voltage were made much lower than the screen voltage the screen would have a greater attraction for electrons which should go to the plate, and the screen would tend to act as the plate.

At high frequencies, where the transit time becomes an appreciable portion of the cycle, the pulses of plate current are lengthened and distorted, causing reduced output power and lower efficiency. Electrons which are in transit when the negative part of the cycle occurs are driven back to the cathode, and cause a heating effect which can result in damage to the cathode. In addition, extra driving power is required because of power lost in the grid circuit. As a result, different tube designs have been developed to eliminate or at least reduce these effects. As the frequency increases, ubterecktride lead inductance and capacitance limit the highest resonant frequency obtainable with grid or plate tank circuits. Lead losses increase and lower the highest value of impedance which can be obtained with reasonable efficiency. Hence, transmission lines are used instead, and grounded-grid circuits are employed to minimize external coupling between the grid and plate circuits, and to reduce feedback within the tube.

The application of modulation and its effect on amplifier operation and performance have been mentioned at appropriate points throughout this circuit discussion. For further information, the interested reader is referred to the Modulators Section in this Handbook, where the subject is covered in detail.

Failure Analysis.

No Output. An open or shorted input or output circuit, is defective tube, or lack of supply voltage can cause a no-output condition. If coupling capacitor C_c is open, no grid drive will be obtained. No current will be indicated on the grid meter, and the plate meter will also read zero, since the fixed bias will keep the tube beyond cutoff. An open grid choke, RFC1, or grid resistor, R1, will remove the bias from V1; in this case sufficient plate current will be drawn to blow the plate fuse or supply breaker. Such a condition cannot occur where cathode bias is supplied by R_k , since the tube current will be limited by the cathode resistor to a safe value. If either plate choke RFC2 or tank coil L1 is open, or if bypass capacitor C2 is shorted, no plate voltage will be applied to V1 and an output cannot occur. The open-circuit condition will be indicated by no plate meter reading, while the short-circuit condition will be indicated by an off-scale deflection of the meter and the blowing of the plate fuse or supply fuse. If output coil L2 is open, no output can be obtained; the grid meter indication will be normal, with a low plate meter indication. If tank capacitor C1 is shorted, high plate current will be indicated and a blown plate fuse will result; on the other hand, if C1 is open, a minimum plate current dip at the usual resonance position will not be obtained, and the plate current will most likely be high since the circuit is out of resonance. When driven to full saturation, detuning of the tank circuit off-resonance will usually cause excessive plate current (two or three times the normal value). Leaving the tank detuned will probably cause the plate fuse or breaker to open. This is normal, and is due to improper operation rather than a circuit failure. If neutralizing capacitor C_n is shorted, full plate voltage will be applied to the grid of V1, excessive plate current will be indicated, and the fuse or breaker will open.

Where trouble is indicated by high or low meter readings, the bias and plate voltages can be checked with a voltmeter, to be certain they are present and correct. Open circuits indicated by zero current can be checked for continuity, with the POWER OFF and the filter capacitors discharged, using an ohmmeter. Be certain to observe all safety precautions. Since the voltages used in the grid and plate circuits of transmitters are usually very high and extremely dangerous, your first mistake may be your last!

Reduced Output. Low bias or plate voltage, as well as improper drive, will cause reduced output. In modulated amplifiers, lack of sufficient filament emission or inability of the power supply to furnish full peak current will also cause a reduction in the output, with distortion. Bias and plate voltages can be measured with a voltmeter. When measuring dc voltages in r-f circuits, inaccuracies and meter burn-out can occur if sufficient r-f filtering is not employed. It is the usual practice, therefore, to measure the voltages on the dc side of the circuit, and rely on continuity measurements in the r-f circuit, using plate and grid current meters and, when available, r-f tank current meters to indicate when the circuit is operating properly. Usually, low bias should be suspected when both grid and plate currents are larger than normal, and the tube plate shows excessive plate dissipation. Insufficient drive is usually found by noting that the grid current is below normal. With normal grid current, low plate current indicates either low plate voltage, improper load, or a weak tube. Under certain loading conditions where excessive reactance is reflected into the circuit, tuning for minimum dip may reveal that the dip is very broad or hardly noticeable. In this case, the tuning should be adjusted for maximum r-f output as indicated on a thermocouple meter.

When tubes other than triodes are used, the screen voltage becomes important in determining the plate current and hence the output. Make certain that the proper screen voltage is applied, and that normal screen current is obtained. Inserting a meter in the screen circuit (when a meter is not provided) will enable a more certain check on the operation. Normal screen current indicates that the trouble is elsewhere. Low screen current indicates insufficient drive or screen voltage, while high screen current usually indicates high screen voltage or a defective plate circuit. Maximum screen current at the point of minimum plate current is normal, provided that it does not exceed the rated value.

Reduced output is sometimes due to trouble in the antenna or transmission line; therefore, it is always good practice to use a dummy load when checking out the transmitter to make certain that the trouble is not outside the unit. A rough check on tube emission can be made by temporarily detuning the plate tank and immediately returning it back to the proper setting, meanwhile observing that the plate current increases considerably. If held off resonance too long, it

is possible to damage the tube. Where the tube is normally operated so that there is no trace of color, and a reduced output is obtained with color showing on the plate, a loss of efficiency is indicated, most probably involving bias and drive.

In equipment where a C battery is used to supply the fixed bias, the battery voltage should be measured with the equipment inoperative; the battery should be replaced when its voltage drops below 15 percent of the rated value.

In triode amplifiers, improper neutralization can cause reduced output and erratic operation. The neutralization should be checked when reduced output is obtained with greater than normal plate current indication, usually accompanied by increased plate dissipation. The same symptom is also possible when parasitic oscillations exist either at low frequencies or at extremely high frequencies. This should not occur in properly designed and tested Naval equipment, but sometimes will occur in off-the-shelf commercial procurements, or after repair and replacement with a part having a slightly different value. In this case a wavemeter or grid-dip meter will indicate the frequency of the undesired parasitic oscillation. If low-frequency parasitics exist, the bias and plate r-f chokes and bypass capacitors will usually be at fault (they form a tuned tank at that frequency). If high-frequency parasitics exist, they are usually easily eliminated by installing parasitic suppressors in series with the plate lead, between the plate and the tank circuit (the closer to the plate connection at the tube, the better).

Distortion. In CW operation any distortion that exists will be in the form of harmonics; usually, on the 2nd or 3rd harmonics are of great enough amplitude to be of any importance. In this case, besides wasting some useful output, they may radiate at frequencies which may interfere with other services. Placing a low-pass filter between the transmitter and the antenna will eliminate any unwanted harmonic radiation. A reduction of the bias and drive, plus an increase in the tank circuit Q, will also minimize this type of distortion. (This is not to be considered as authorization to make unapproved changes in the equipment, but is discussed in case such conditions are encountered in the field.) When modulated, non-linearity of the transfer characteristic and improper bias or drive will cause a distorted modulation envelope. The waveform may be observed on an oscilloscope (use an r-f probe or connect directly to the

plates); adjust the equipment so that the values used are those which eliminate the distortion. It is also important to determine that the modulation is not distorted before being applied to the amplifier suspected of being at fault. Normal oscilloscope checks will reveal the cause (compare with typical faulty waveforms).

PUSH-PULL R-F AMPLIFIER (CLASS B OR C)

Application.

The push-pull Class B or C r-f power amplifier is used universally at high frequencies as an intermediate (driver) stage, or as the final output stage for transmitters, where a large output with reduced second harmonic distortion is required.

Characteristics.

Uses either Class B or Class C bias. Fixed bias is normally used, but self bias (either signal or cathode bias) may also be used; sometimes a combination of both types of bias are used.

Uses a tuned r-f tank circuit to develop the output frequency.

Output efficiency varies with bias; approximately 50 to 60 percent for Class B operation, and 70 to 80 percent for Class C operation.

Triodes require neutralization, other tube types do not.

Input and output frequencies are usually the same.

Provides high output power and current gain.

Requires approximately twice the grid-drive power of the single-ended stage, and a push-pull input.

Second harmonic output is considerably reduced or eliminated.

Input and output capacitance is half that of the single-ended stage.


Circuit Analysis.

General. In the push-pull configuration, the input and output capacitances of the tubes are effectively connected in series. Therefore, only about half the normal grid and plate tuning capacitance is required for a specific frequency. Consequently, high frequency tanks are easier to construct and use of this type of circuit is more prevalent on the higher frequencies (above 30 MHz) although it can be, and is, used on the lower frequencies. The push-pull grid

input also provides a step up of input impedance of about four times over that of a single tube. Thus it is easier to drive the push-pull amplifier, since the driver stage can be more easily matched. Because two tubes are driven, twice the drive power of a single-ended stage is required. It should be noted that the Class B or C power amplifier although connected in push-pull, does not actually operate in push-pull fashion like the Class A stage. That is, instead of increasing the current of one tube while simultaneously decreasing the current of the other tube (the action from whence the name push-pull was derived), each tube operates separately. Operation occurs only during the positive portion of grid swing when the drive exceeds the bias, and plate current flow is cut off during the negative portion of the cycle as the tank circuit supplies the output. While not operating in true push-pull fashion, this circuit retains most of the advantages of the basic circuit. Since the individual plate load is one quarter the total load, low impedance triodes can be used to develop a high power output. And, although the second and even harmonic content is not cancelled out in the primary of the r-f output transformer, the even harmonics are eliminated in the output circuit (the secondary). The push-pull connection also affords a slight increase in power output; normally, 2-1/2 to 3 times the single tube rating can be obtained, particularly in unmodulated operation (CW). When triode type tubes are used, their large grid-plate capacitance causes feedback, and the circuit tends to operate like a tuned-grid, tuned-plate oscillator; therefore, triodes are always neutralized. The pentode, tetrode, or beam power tube types normally do not require neutralizing because of reduced interelectrode capacitance and better shielding. However, arrangement of components is sometimes such as to permit external coupling (particularly at high power and at high frequencies and neutralization is then necessary).

Although cutoff bias is required, cathode bias may be used since one of the tubes is always conducting (both conduct alternately). However, since the push-pull circuit is a balanced circuit, it is usually easier to apply a fixed negative bias and avoid selecting or matching the tubes to get equal currents. Since grid current is always drawn, a grid leak resistor is usually connected in series between grid and ground to provide some signal bias, and reduce the voltage requirement on the separate C-bias supply.

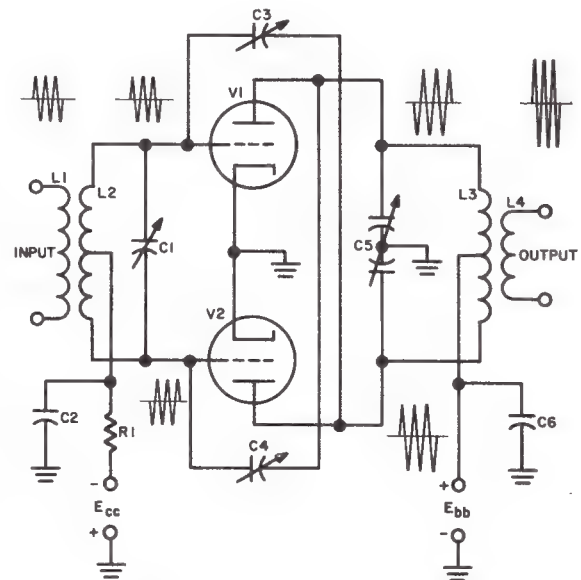Circuit Operation. The schematic of a typical triode push-pull r-f power amplifier is shown in the accompanying illustration. The triode is used for ease of explanation. Considerations for screen grid and other type tubes will be discussed at the end of this article.



Triode Push-Pull R-F Power Amplifier

Coil L1 couples the output of the driver stage to tuned input circuit L2, C1. Grid bias is supplied to a tap on L2 from a fixed bias supply, supplemented by signal bias provided by R1, and bypassed for rf by C2. The cathodes of V1 and V2 are grounded, and the plate tank consists of split stator capacitor C5 and coil L3; the output is inductively coupled through L4. Cross neutralization is provided, with the plate of V1 coupled through neutralizing capacitor C4 to the grid of V2, and the grid of V1 coupled to the plate of V2 by neutralizing capacitor C3. Series plate feed is used with the supply tapped to the center of tank coil L3, and bypassed by rf by C6.

With a fixed negative bias applied to the center tap on L2 from the separate negative bias supply, the grids of tubes V1 and V2 are biased far beyond cutoff (about 2-1/2 times). In the absence of excitation, both tubes are cut off, no current flows and no output is

obtained. When r-f excitation is applied to coil L1 a similar r-f voltage is induced in tank coil L2. Since the center tap of L2 is bypassed to ground for rf it is effectively at r-f ground potential (zero voltage) and the ends of the coil to which the grids of V1 and V2 are attached are at equal and opposite r-f potentials. When a positive voltage appears on the grid of V1, a negative voltage appears at the grid of V2. With a balanced input the voltages are of equal amplitudes and of opposite polarities. Grid tank capacitor C1 tunes the input tank to resonance at the frequency of the drive voltage. The maximum current flows in the closed tank circuit, and maximum drive voltage is developed across the parallel-connected tank and applied to the grids. Assuming a sine wave exciting signal going positive on the grid of V1, the grid of V2 is driven further negative into cutoff and no plate current flows in V2. As long as the signal on V1 grid is below the cutoff level no current flows in V1 also, and both tubes remain cut off. As the positive-going input signal rises above the bias level on V1, the tube is eventually driven into conduction, and plate current flows. Since the tubes are fixed biased beyond cutoff, plate current flows only during the time the grid is above cutoff, or for about 120 degrees of the positive half cycle of excitation signal. As the positive grid voltage increases, plate current increases, reaching its peak at the same time the excitation voltage reaches its crest. At the beginning of the conduction cycle the grid voltage is only sufficiently positive to reduce the fixed bias voltage so that the effective bias is just above cutoff (but still negative). However, as the amplitude of the drive voltage increases, the grid is driven to the zero bias level and then positive. At or near zero bias grid current also begins to flow, increasing to its peak value at the crest of the cycle. Grid current flow is from the cathode of V1 to the grid, through coil L2 and the center tap to grid resistor R1, then to the bias supply and ground. In flowing through R1, a negative voltage is developed across R1 which adds to the instantaneous bias. The value of R1 is chosen so that the maximum desired bias is produced with a specified grid current drive before the crest of the cycle is reached, with light saturation for Class B amplifiers, and with heavy saturation for Class C amplifiers (see Single-Ended (Class B or C) R-F Power Amplifier circuit in this section of the handbook for an explanation of saturation, and the introduction to this section for a discussion of signal bias).


When plate current flows in V1 there is a flow of electrons from the cathode through the grid wires to the plate, and from the plate through the top half of tank coil L3, out the center tap to the plate supply and ground. Current flow through half of L3 produces an electric field around the coil (which acts as the primary of a transformer), and the magnetic lines of force link output coil L4 (which acts as the secondary) inducing an output voltage in it. At the same time, the field around the lower half of L3 induces a voltage which is in a direction to continue current flow through L3. This induced current charges the lower half of split stator capacitor C5 negatively, while the upper half of the capacitor is charged positive. The effect is the same as if the split capacitor were a single capacitor connected across L3 with the upper plate positive and the lower plate negative. Since tank L3 and C5 are parallel resonant at the output frequency, a circulating current is built up within the tank which continues to oscillate back and forth. Reinforced first by V1, and then by V2 as it operates. The resonant tank selects the desired output frequency and discriminates against any harmonics which also tend to develop across the tank impedance. The tank impedance is a maximum at the fundamental output frequency and very low at any of the harmonic frequencies. Thus maximum voltage is developed across the maximum impedance presented at the desired fundamental frequency. The tank coil also acts as a tapped autotransformer with a turns ratio of one half to one (2 to 1). Since transformer impedance always varies as the square of the turns ratio, it presents a load impedance to the single tube of one quarter the plate to plate load impedance. At the positive crest of the drive cycle the voltage drop across the tank impedance is maximum and causes the effective plate voltage to be at a minimum value. At this time the tank is absorbing, or being charged with r-f energy, and only a small amount is applied to the plate for dissipation in the form of heat. This is the most efficient part of the operating cycle.

As the excitation voltage passes the crest and reduces the amplitude it becomes negative going. The effective bias becomes more negative and plate current flow is reduced. This action continues until zero bias is reached and grid current flow, likewise, reduces and ceases. From here until cutoff the plate current continues to reduce, and ceases when cutoff bias is reached. While the plate current is reducing, it induces a tank current flow in the opposite direction

causing the tank capacitor to discharge. This discharge continues beyond cutoff when both V1 and V2 are non-conducting, and is the so-called "fly-wheel" effect of the tank, which continues to supply an r-f output even though neither tube is operating. When the positive half cycle of drive is completed, the negative half cycle starts, the grid of V1 is driven further into cutoff and is held inoperative for the remaining portion of the half cycle.

V2 grid is now being driven positive by the negative half-cycle of input signal. (The input signal is inverted by the push-pull input tank.) During the negative half-cycle, tube V2 is made to operate exactly as described above for V1. The effective bias is reduced until plate current flows, and as the bias decreases grid current flow starts near zero bias, reaching its peak at the negative crest of the drive signal (the grid voltage applied V2 is positive). Plate current flow through V2 and the lower half of the tank coil, now flows in the other direction and charges C5 in the opposite direction to the previous half-cycle of operation. Actually, operation is only over 120 degrees as mentioned before, and the tubes are quiescent over 60 degrees of the 180 degree half-cycle. Thus it can be said that the tank alone supplies energy for a total of 120 degrees, and the tubes for 240 degrees out of a single cycle of operation. Operation of V2 is identical in every respect with that of V1, their currents and voltages are, however, 180 degrees out of phase, but there is no canceling effect since each tube operates separately. The tank circuit, meanwhile, continues to oscillate first in one direction for 180 degrees and then in the other direction for the remaining 180 degrees of the complete cycle, being reinforced each half-cycle by a different tube. Output coil L4 supplies a continuous r-f output to the antenna or transmission line from the tuned tank circuit to which it is inductively coupled. Since the tank is tuned to the fundamental frequency, even harmonic content is almost entirely cancelled in the secondary (L4) since equal and opposite voltages are produced. The closer the circuit is to a balanced condition the more nearly is the even harmonic output reduced to zero. Since the odd harmonics occur in-phase a small amount also appears in the output. The amount is dependent upon the impedance the tank presents to odd harmonics. Usually it is so small as to be considered negligible. However, in extremely high powered stages (megawatts) this output may be on the order of tens of watts (or more) and require extra

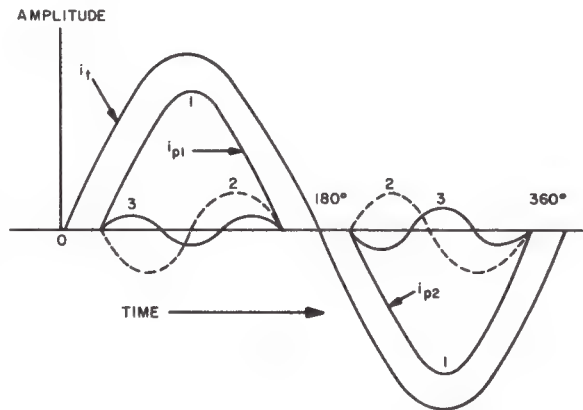filtering to prevent it from being radiated on the undesired harmonic frequency. The manner in which the tank current and the fundamental and harmonic plate current components vary is shown in the accompanying figure to illustrate the manner in which the even harmonics are cancelled.



Tank Current Versus Fundamental and Harmonic Plate Currents

The instantaneous tank current varies continuously throughout the cycle flowing first in one direction (shown as positive) and then flowing in the opposite direction (shown as negative). During a portion of this time i_{p1} and i_{p2} (curve 1) flow alternately as V1 and V2 operate. Any second and third harmonic currents flow as shown in curves 2 and 3, respectively. Since the second harmonic current is always out-of-phase with the fundamental plate current it cancels out. The third harmonic current (curve 3) is in-phase more than it is out-of-phase, therefore, a small amount of odd harmonic distortion remains in the output. The selectivity of the output circuit also helps discriminate against any harmonics, since the impedance it offers to these frequencies determines the output amplitude, and most output circuits are resonant at the fundamental frequency.

With the grid V1 and V2 cross connected to the opposite tube plate through neutralizing capacitors C3 and C4, equal and opposite feedback voltages are applied which cancel out any in-phase plate to grid feedback and prevent the stage from going into self-oscillation. The additional capacitance added by the neutralizing circuit reduces the input impedance,

hence, triodes are only used when necessary, or the push-pull grounded-grid circuit is used instead. The use of a well shielded tetrode or pentode makes neutralization unnecessary, because the plate and grid are shielded from each other by the screen grid and its associated bypass capacitor, which hold the screen at r-f ground potential. The low excitation requirements of the tetrode or pentode makes them especially suitable for use in the intermediate stages of a transmitter. When the power used by the screen grid is considered, however, the overall efficiency of these tubes is not as great as the triode. Because of the easier drive requirement and the lack of neutralization provisions, the tetrode, or beam power tube is generally favored over the triode. Particularly in band-switching transmitters where a neutralizing adjustment is not required for each band.

Failure Analysis.

No Output. Loss of excitation (drive), bias, supply voltage, or defective tube(s) can cause a no-output condition. If input coil L1 is open, no drive will be obtained and the tubes will rest in the cutoff condition. Lack of both grid current and plate current will be indicative of this condition. Check L1 for continuity with the POWER OFF. If drive is present in L1, but L2 is open, or C1 is shorted or nonresonant, a similar condition will exist. If L2 is open the symptoms will be the same as when L1 is open. However, if C1 is shorted no drive will appear on V1 or V2 grid and the fixed bias supply will be grounded through R1. Usually extremely heavy grid current will flow and R1 will heat, may smoke, and will eventually burnout if the condition is prolonged. Meanwhile, the plate current will also be extremely high because of loss of bias and will usually blow the plate fuse or open the plate circuit breaker, if provided. The same symptoms will occur also if grid bypass capacitor C2 is shorted. Check V1 and V2 grids with a voltmeter for the proper negative bias. If L2 is not open and C1 or C2 is not shorted the proper dc bias will appear on both tubes (make this check with driver plate voltage OFF, otherwise, r-f drive may burn out the meter). If C1 is not tuned to resonance, sufficient drive may exist to produce a low output, but normal loading and output will not be obtained. Normal bias voltage also indicates that both neutralizing capacitors C3 or C4 are not shorted. When either C3 or C4 are shorted, plate voltage will be

applied to the grids of both V1 and V2, cause heavy plate current, and blow the fuse or breaker.

When the loss of output is caused by lack of plate voltage it may be due to shorted plate bypass C6, or defective power supply, shorted tank capacitor C5, or defective tube(s). Check the supply voltage first with a voltmeter, be certain to observe all safety precautions since the plate voltage is dangerously high. Make certain that the transmitter plate switch is OFF when checking the supply. If either C5 or C6 is shorted and the supply is good the plate fuse or breaker will operate, and high plate current with normal or slightly higher than normal grid current indication will be obtained momentarily. Usually C5 can be checked visually since arcing will occur as the rotor is varied throughout its range and whenever it touches or moves too close to the stator. If not, make certain the plate voltage is removed, and use a shorting stick to discharge the capacitors in the plate circuit. Disconnect plate bypass capacitor C6 and check continuity to ground with an ohmmeter, no continuity should exist and resistance should be infinite. Then disconnect C5 and L3, and again check for continuity to ground. With the tank disconnected check the plates of V1 and V2 to ground; any resistance other than infinity probably indicates a defective tube. Note: be certain to observe the polarity of the ohmmeter so that a negative potential is applied from plate to ground. Otherwise, if the plate is made positive and the tube filament is operating there will be a flow of current, and a false resistance-to-ground reading will be obtained. Check output coil L4 for continuity at the same time to avoid making a later check.

If proper grid current indication is obtained, but a very low plate reading (or a high plate reading) rapidly tuned C5 back and forth to determine if a minimum dip indicating resonance can be obtained. With a sharp minimum and a reduced plate current either L4 is open, and load is not connected, the drive is too low, or L4 is not coupled sufficiently close to tank coil L3. In the case of heavy plate current and broad dip, usually some output will be obtained, and too large, or an overcoupled load is indicated.

Use of grid and plate meter indications, plus the tuning of C1 and C5, should be made to determine whether normal currents and tuning are obtained, since these offer a quick means of trouble-shooting. In most instances, moderate and high power transmitters and tanks are constructed mechanically and

electrically rugged so that visual observation will locate grounded parts (usually some sign of an arc such as charred insulation or a black spot will mark the point of improper grounding due to the high voltage and currents involved).

In the event of tube trouble, usually both tubes must be defective to cause no output in a push-pull circuit, since the stage is capable of operating at reduced output with only a single tube.

Reduced Output. Low drive, grid bias, or plate voltage, as well as a defective tube can cause a reduced output. Low drive will be indicated by a low grid current reading usually with reduced plate current, and output. Low grid bias will usually cause operation in the Class A or AB region with a higher than normal plate current. Check the bias with a voltmeter from the junction of C2 and R1 to ground; this will indicate the sum of both the fixed bias and the signal bias, and should be made with C1 tuned to resonance and normal grid current. Closer coupling between L1 and L2 will increase the drive if necessary. If the plate current suddenly increases and the output reduces, particularly during voice modulation (or while being keyed off and on), improper neutralization can be suspected. Remove the plate voltage and tune tank capacitor C5 through resonance, the grid current indication should hardly change as resonance is passed. If it flicks sharply, adjust C3 and C4 in small increments, simultaneously, first in one direction and then in the other. No change in grid current will be observed at the point of proper neutralization.

Normal plate voltage and loading accompanied by reduced plate current indicates the possibility of low tube emission. If plate voltage is low with normal load the power supply rectifiers are probably in need of replacing. A dynamic check on the power supply can be made by quickly detuning and resetting C5 to resonance. The heavy off-resonance current should not cause the plate voltage at C6 to drop more than approximately 25 or 30 volts. If it does, the power supply regulation is poor. A poor soldered joint or bad connection can introduce a high resistance in the plate circuit and cause a reduction in applied plate voltage with a low plate current indication. To check this, remove plate voltage from the driver AND finally, discharge the filter capacitor with a shorting stick, and check the resistance between the tap on L3 and the plates of V1 and V2. Indications should be zero or a few tenths of an ohm.

TRAVELING-WAVE TUBE R-F AMPLIFIER

Application.

The traveling-wave tube r-f amplifier is used at super-high frequencies as an untuned r-f amplifier (or mixer) in microwave receivers, as a linear amplifier in transmitters, and in test equipment. Its broad-band characteristics make it particularly useful for high-band television and electronic countermeasures (ECM) applications.

Characteristics.

Range of operating frequencies is from approximately 200 MHz to 15,000 MHz.

Efficiency varies from 10 to 40 percent.

Power handling capabilities vary from as low as 100 microwatts to 1 kilowatt for continuous-wave emissions. Peak power capabilities for pulsed operation extend up to 50 kilowatts.

Power gain in a single tube varies from 20 to 60 dB maximum.

Noise figures from 5 dB to 30 dB can be obtained, depending on the frequency (increases with frequency, but not linearly).

Uses positive bias and high voltage to control emission of an electron gun.

Amplifies by virtue of a distributed interaction between an electron beam and a traveling wave.

Is a nonresonant device inherently capable of enormous bandwidths.


Usually employs magnetic focusing of the electron beam; however, electrostatic focusing is sometimes employed.

Circuit Analysis.

General. Traveling-wave tubes are used for both large and small signal applications; each tube is rated for a specific power-handling capability over a certain frequency range. They supplement the presently available microwave tube types, such as planar triodes, klystrons, and magnetrons. They are particularly useful for wideband applications where a large range of frequencies must be covered. Since the tube is completely self-contained and nonresonant, it has no bulky cavities or large magnets to pose a design problem. Either coaxial or waveguide input and output fittings are provided, depending upon the frequency range in use, so that only filament and collector power are needed in addition to the input and output leads to provide an operating amplifier.

Although the traveling-wave tube has high gain and is easily tuned by changing the collector voltage, it possesses noise characteristics that are somewhat less desirable than those of some of the other types of microwave tubes. Recent improvements along this line have produced noise figures of 6 dB at 3000 MHz and 11 dB at 10,000 MHz or better, as compared with 30 dB for the early versions. The 6-dB figure is approximately the same as that obtained with a crystal mixer. It is well known that crystals are easily damaged by r-f energy. However, the traveling-wave tube is not so easily damaged since an input over-load will merely cause saturation (instead of burnout as in the case of the crystal); hence, with this tube, a simpler duplexing system may be used.


Circuit Operation. The accompanying figure shows the essential elements of a traveling-wave tube. These are a long, narrow electron beam and a circuit capable of sustaining a slow electromagnetic wave with a longitudinal component of electric field, which can travel along in synchronism with the beam. The slow-wave circuit usually consists of a helix or long coil of wire. In such a circuit the wave travels along the wire with approximately the speed of light. If the length of the wire is 13 times as long as the axial length of the coil or helix, the wave will travel along the electron beam at one-thirteenth the speed of light, and the electrons in the beam, passing through the center of the coil, will be in synchronism with this slow traveling wave if they are accelerated by about 1500 volts. The speed of the electron beam is controlled by the potential applied to the accelerating anode. Since the helix is connected to the collector at the end opposite the cathode, the helix also serves as an additional accelerating anode. An axial magnetic field is used to focus the electron beam, to keep the beam from spreading and to guide it through the center of the helix.

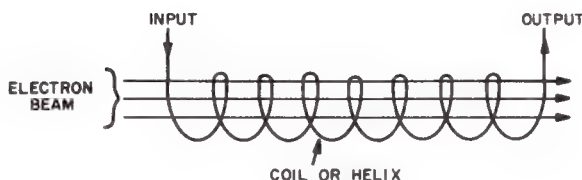

Basic Traveling-Wave Tube Elements

When the electrons travel along in synchronism with the slow wave, there is a cumulative interaction which results in amplification of the traveling wave. At wavelengths of around 10 centimeters, the power gain may be of 1000 to 10,000 times or even greater, in a distance of 10 inches. Because no resonant circuits are involved, the traveling-wave tube is inherently broad-band; substantial gain has been obtained over bands of thousands of megahertz and of several octaves. Waves traveling backward, against the electron stream, are practically unaffected by its presence. To make a stable and useful amplifier, attenuation of the backward wave must be added in the slow-wave circuit. Usually, it is lumped near the center of the tube, and introduces a loss to the backward wave which is much greater than the amount by which it reduces the forward gain. The necessity for the attenuator and its reduction of forward as well as backward gain is a basic limiting parameter, which hinders high-power tube development.

The following figure illustrates a typical traveling-wave tube amplifier using a solenoid type of magnetic focus coil. The electronic beam is obtained from a PIERCE electron gun, which produces a series of essentially parallel-path electrons. The tendency of the parallel electrons to be deflected or to stray from the parallel path is overcome by adding a solenoid on the glass envelope of the tube whose axis is in the longitudinal direction. The focusing field of the solenoid deflects any stray electrons back into the electron stream so that they must travel through the center of the helix.

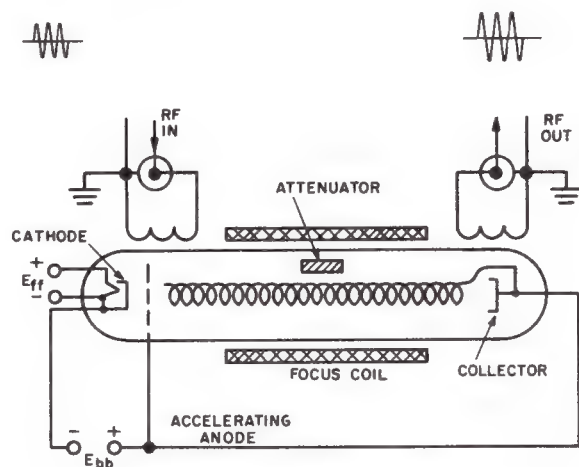


Typical Traveling-Wave Tube Amplifier

The r-f input signal is fed into the helix at the cathode end of the tube, while the r-f output signal is taken from the opposite end of the tube, near the collector (or anode). The accelerating anode creates the initial electric field which attracts the electrons from the cathode, while the collector (or anode) serves to collect the spent electrons after they have passed through the helix, and return them to the power source. The helix is connected to the collector internally, and also acts as an accelerating anode for the electron beam. The r-f signal is coupled to and from the helix inductively. There is no direct connection between the helix and the input and output circuits. The helix consists of a continuous spiral of wire or strap 10 to 12 inches in length, whose natural resonant frequency is much lower than the range of operation so that it acts as a nonresonant device. The purpose of the helix is to provide a path for the input signal in proximity to the electron beam so that interaction can occur between the beam field and the signal field. When the r-f input signal is induced on the helix, a conductive path is provided by the helix from the cathode end to the collector end of the tube, through which the r-f signal current flows. Signal current flow induces a field around the helix which travels with the signal from input to output; thus, a traveling wave is produced along the helix. While the electron beam and r-f signal both travel at the speed of light, the path around the helix is longer. Therefore, the signal field progresses from turn to turn through the helix at a much slower speed than the electron, which travels through the center of the helix and follows the shorter direct path between cathode and collector.

When the input signal field opposes the field of the electrons passing through the center of the helix the electrons are decelerated, and are overtaken by other electrons. During the time the beam electrons are decelerated, they relinquish kinetic energy to the field of the r-f signal, and tend to form in bunches. When the signal field increases, it enhances the electron field and accelerates the electrons, and energy is transferred from the r-f field to the electron field. As the signal field and electron beam progress through the tube, more bunching occurs. Thus, more electrons are available to give up kinetic energy while a particular bunch is passing through a decelerating field. Since more time is spent by an electron in a decelerating field than in an accelerating field, it gives up more energy to the r-f field than it receives. Thus, as the

signal progresses along the helix, it increases in strength, and is amplified.

No energy transfer is possible until electron bunching commences. As bunching increases, the signal amplitude increases and causes even greater deceleration of the electrons (in the following bunch). This causes the signal strength to increase exponentially, as shown in the accompanying illustration. Eventually, a point is reached at which the electrons in the bunches are slowed to the extent that they are no longer in synchronism with the signal field. At this time the forward speed of the beam electrons and that of the signal are no longer near the same value, and the efficiency drops.

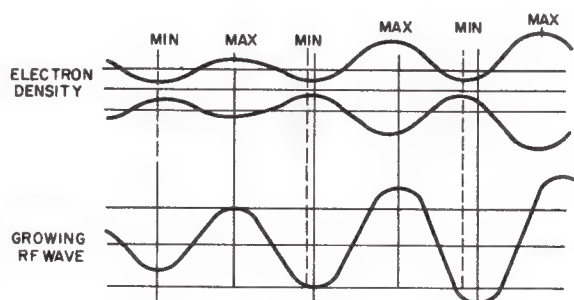

Development of Growing Wave


Operation of the traveling-wave tube is sometimes explained on the basis of a total of four waves existing within the tube, three forward waves and one backward wave. The three forward waves are the result of the division of the input into three components, each with an amplitude of one-third the input strength. The first wave (which is the one we have been discussing) travels more slowly than the electron beam, and increases in strength. Another wave also travels at this same speed and diminishes in strength (as it gives up its energy to the first wave). The third wave travels at the fastest speed, faster than the electrons, and maintains a constant strength. The resultant of these three waves is the constantly growing signal or output.

The gain of the traveling-wave tube is also affected by the input and output coupling circuits. For amplifying a wide frequency band, high gain can be maintained by changing the helix voltage with frequency to maintain the necessary synchronism between the

helix velocity and the beam velocity. In addition, the maximum output power depends upon the input (drive) power, and the power-handling ability of the helix. The amount of power in the beam input power is a factor. Also, since the output end of the helix is heated by r-f currents and electron bombardment, if the beam disperses before passing the output end, the power-handling ability of the helix is another factor. Dispersement of the beam and bombardment by beam electrons can be caused by a maladjustment of the magnetic focusing field. Since a helix mounted in glass has a low heat-dissipating ability, the power output at the present state of the art is limited to values less than 100 watts unless special cooling systems are employed. High-power tubes use either water or forced-air cooling.


The thermal noise of the electrons in the beam affects the noise figure of the traveling-wave tube amplifier, just as it affects the noise figure of other types of amplifiers. The noise signal is induced onto the helix and is amplified in the same manner as any other signal. Lowering the operating voltage will generally result in a slower beam velocity and less thermal noise. If the gain per unit length is low, less noise amplification will also occur; tight focusing of the beam will also produce less noise. Uneven cathode emission, particularly from an aging tube, will produce a nonsymmetrical beam and noise, as will ion movement caused by gases within the tube. When the signal injection point is properly spaced from the end of the electron gun, a reduction in noise occurs because of certain periodic fluctuations in noise current within the tube. Thus, injection of the signal at a point of low noise current results in a greater signal-to-noise ratio.

When the long solenoid focusing coil of the traveling-wave tube is replaced by a series of small coils spaced along the tube, as shown in the accompanying illustration, less energy is required to focus the electron beam, and tighter focusing is achieved. The same effect is produced by using a series of permanent magnets to produce a periodic magnetic field. These types of tubes are called PPM (periodic permanent magnet) traveling-wave tubes. Better over-all efficiency is obtained, since the loss of beam current through dispersion of stray electrons is prevented.

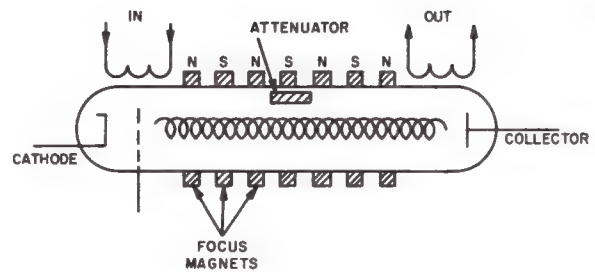

Periodic Electro Magnet Focusing

When a series of opposing electrodes or plates are placed along the tube inside the glass and connected to a dc source as shown in the accompanying illustration, an electrostatic field is produced between the electrodes. This is similar in all respects to the magnetic field produced by the solenoid or the periodic permanent magnets. Focusing in this instance, is done electrostatically, and no change in operation occurs. Because the construction of this tube is more difficult and more expensive, and since the performance is about the same, the electrostatic type of traveling-wave tube is seldom used.

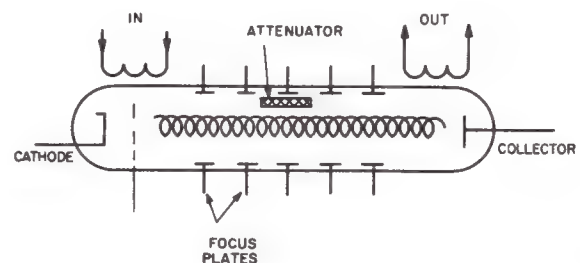

Electrostatic Focusing

The attenuator which prevents the backward wave from causing oscillation and loss of amplification is provided by spraying a resistive film (produced by an aquadag solution) on the helix and tube envelope at

the proper location. In a high-power tube the attenuation is concentrated near the center of the tube, while in a low-power tube it is usually not more than one-third the distance from the cathode.

While more could be said about the various phases of design, the discussion above is sufficient to acquaint the reader with the primary functioning of traveling-wave tubes. Since the tube is a fixed package, there is nothing the electronic technician can do to change its operation. Of course, faulty operation can result from incorrect connections or operating voltage and polarities. Therefore, further discussion at this time is unnecessary. Additional data can be obtained, when desired, by reference to other texts or to manufacturers' information sheets.

Failure Analysis.

No Output. Lack of input signal, an open output circuit, or a lack of filament or plate voltage can cause loss of output. Use a voltmeter to determine whether the filament and plate voltage are correct. **WARNING:** *High plate voltage* exists between the collector and ground; be certain to observe *all safety precautions* when measuring this voltage. Since the cathode is usually connected to one side of the filament, measure the filament voltage *only when the plate voltage is off*.

The input and output circuits can be checked for continuity with an ohmmeter, with the power off. If the external circuits appear to be satisfactory, use a signal generator to supply an input to determine whether there is loss of input signal. Likewise, in the output a dummy load may be substituted. If the input and output circuits are apparently satisfactory and proper electrode voltages are applied, a no-output condition will probably indicate a defective tube.

Low Output. Low output can be caused by improper plate or filament voltage, low drive, or a defective tube. Check the plate and filament voltages, observing all safety precautions. In transmitting applications, insufficient r-f drive will cause reduced output. In the special case where sweep voltages are used to tune automatically over a band of frequencies, it is important that the drive waveform and sweep waveform be of the shapes and amplitudes specified; otherwise, reduced performance will occur. Low tube emission can sometimes be found by noticing that the output fluctuates in amplitude and that a high noise is developed in the output. The beam current in this case will be reduced, and low

output will occur. Unfortunately, other conditions, such as load reflections or a change in accelerating voltage or collector voltage, will also change the beam current. Where solenoid focusing coils are used, lack of sufficient field will also cause a reduction in the beam current, and can be caused by a defective coil, low focusing voltage, or loss of power to the coil. In this case, the focus supply can be checked with a voltmeter and the resistance of the coil determined by means of an ohmmeter, with the power off. Comparison with a good coil will indicate whether the resistance is high, low, or normal.

Because of the few parts involved, usually a voltage check, a waveform check, and a beam current check are the only simple checks possible. In tubes having a low noise figure, disconnecting the antenna from the input in receiving applications will reduce the noise, and serve as a rough indication that the tube is functioning. However, in tubes having high noise figures this change may be masked by the tube noise. Thus, a more positive check is to insert a signal from a known source and determine whether normal amplification is obtained. A change in load should also cause a change in beam current, as should a change in focusing-magnet current.

In the case of overdrive, increased current usually occurs, followed by a reduction in output as the collector is heated by electron bombardment. Once saturation is reached, no further increase in current occurs as the drive is further increased; this indication can sometimes be mistaken for reduced output.

MULTICAVIDITY KLYSTRON R-F AMPLIFIER

Application.

The multicavity klystron r-f amplifier is used to supply high r-f power to the transmitting antenna of television, radar, microwave, and electronic counter-measures equipment operating in the VHF, UHF, SHF, and EHF regions.

Characteristics.

Uses a positive grid voltage.

Uses a number of cavities tuned to the same frequency for narrow-band operation (synchronous tuning), or is stagger-tuned to different frequencies for wide-band operation.

Power gain is on the order of 30 to 50 dB.

Power-handling capabilities range from microwatts

in receiving or test equipment applications, to the tens of megawatts in transmitting applications.

Efficiencies of 40 to 50 percent are possible.

Uses velocity modulation of an electron beam to form electron bunching for amplification.

Each cavity provides additional amplification, and extremely high gain is thus obtained.


External magnetic beam-focusing is usually employed to improve efficiency.

Circuit Analysis.

General. The basic multicavity klystron consists of an electron gun, an input (buncher) cavity, an output (catcher) cavity, and a collector anode. The cavities may be integral within the tube or constructed externally so that the tube can be inserted within them. A focusing coil arrangement is usually included to prevent divergence of the electron beam, loss of electrons, and consequent reduction in efficiency. Any number of cavities can be used by increasing the tube length, as long as the transit time across the lips of the cavity is short as compared with the wavelength of the signal. The high-power klystron operates at voltages of 25 to 100 kilovolts or more, and the current is in terms of amperes or tens of amperes, rather than milliamperes. The unit is usually shielded as a protection against high voltage, and special lead shields minimize the X-radiation produced as a consequence of the high electron voltages used. Since the physical construction of the various tubes available are slightly different for different manufactures, the following discussion applies generally as far as basic theory is concerned. The effects of cavity shape and construction, windows, and apertures or coupling loops are generalized so that the discussion will be applicable to most types of klystrons. Moderate-power tubes use forced-air cooling, while the high-power units use hollow water jackets with forced-water circulation to provide artificial cooling.

Because of the noise produced by the electron beam (noise figure averages 25 dB, the multicavity klystron is normally used for transmitting applications instead of receiving applications. While feedback can be employed between the cavities to provide oscillation, the multicavity klystron is generally used as a linear r-f amplifier, being driven by a lower-power klystron or a traveling-wave tube.

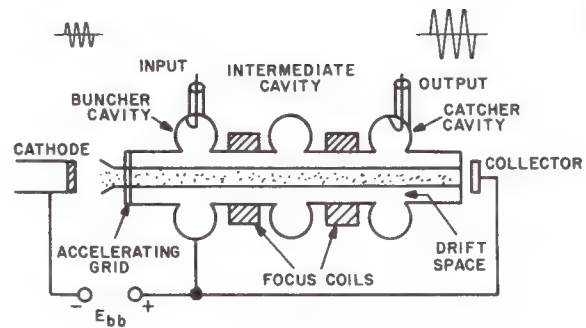Circuit Operation. The simplified schematic of an elementary multicavity klystron is shown in the accompanying illustration.




Simplified Klystron Multicavity Amplifier

At the left is the cathode of the electron gun, from which the long electron beam is accelerated, and at the right is the collector, which finally collects the beam. The electron beam first passes through the input resonator. The input signal produces a longitudinal electric field across the part of the resonator through which the beam passes. This field alternately retards and accelerates the electrons passing through the resonator. The retarded and accelerated electrons all travel along through the drift space between the cavities. There, some of the accelerated electrons catch up with some of the retarded electrons which left the input resonator earlier, so that bunches are formed. These bunches are composed of electrons, which pass through the input resonator while the field was changing from retarding to accelerating. These bunches eventually pass through the output resonator (or catcher) and induce a current from which the output is derived. In the 3-cavity klystron, an intermediate resonator is placed between the input and the output cavities to provide, in effect, a two-stage amplifier in one tube envelope. The bunched electron beam produces a field across the intermediate resonator, and this again retards and accelerates the beam (that is, velocity-modulates it anew). In tubes for very broad-band operation, several intermediate resonators may be used.


The manner in which the electron beam is formed and bunched can be understood by following the action step by step. The initial electron beam is produced by a Pierce-type electron gun. The electrons emanate from a flat cathode under the attraction of a positive accelerating field produced by an accelerating

grid located near the cathode (between it and the input resonator). This electrode is shaped to permit passage of the electrons through a small orifice. In low-power guns the electrode may contain an actual grid structure through which most of the electrons pass without hindrance and from an essentially parallel-path beam of electrons. The tendency of these electrons to expand around the axis of the beam and disperse is corrected by a magnetic field placed along the axis of the tube by a focusing coil (permanent magnets are also used). Any electrons which tend to fly off at a tangent, or in a radial direction, are forced back into the beam path by the parallel flux lines from the coil. In extreme cases they cause the recalcitrant electrons to follow a spiral path back to the axis of the beam. The parallel beam of electrons, all traveling at the same speed, passes through a pair of buncher grids, as shown in the accompanying illustration. Each of the buncher grids is connected to one side of a tuned circuit (cavity). (The tuned circuit and the buncher grids are at the same dc potential as the accelerator grid.) The input signal is usually inductively coupled into the tuned circuit or cavity, and produces an ac field between these grids. Assuming a sine-wave input, when the buncher grid closest to the cathode is positive, the buncher grid farthest away is negative. These voltages add to or subtract from the applied dc accelerating voltage. Therefore, the alternating (signal) voltage between the buncher grids causes the velocity of the electron leaving the buncher grids to differ, depending upon the time at which each electron passes these grids.

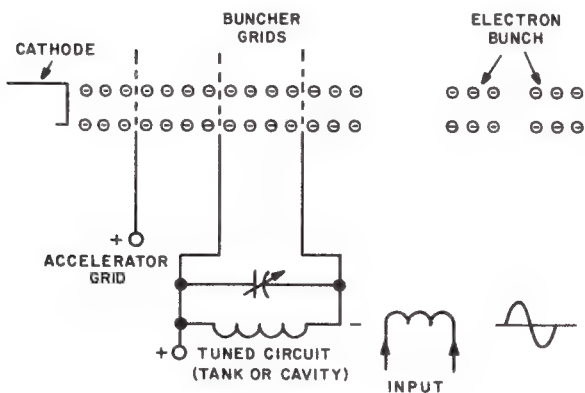

Electron Gun and Buncher Grids

An electron that passes the center of the buncher cavity at the same time the input signal is passing through zero leaves the buncher at the same velocity at which it entered (since no change in accelerating potential occurs). The position of the electrons plotted against time is shown in the following Applegate diagram, which indicates how bunches are formed. The slope of the lines in the figure represents the velocity of the electrons.

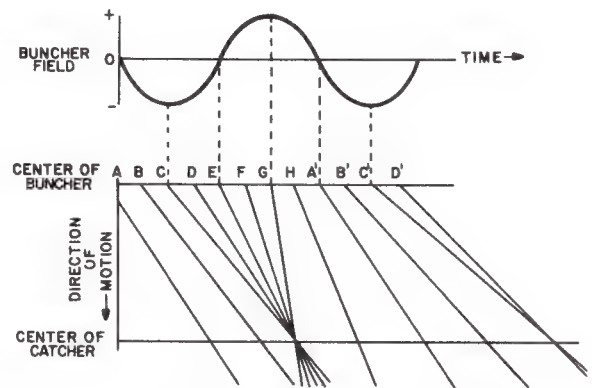


Applegate Diagram of Electron Bunching

Electrons which pass the center of the buncher a few electrical degrees earlier than the point of zero voltage (such as at C and D in the diagram) encounter a negative opposing field, and leave the buncher with reduced velocity, since the decreased voltage of the buncher slows them up. Electrons which pass a few electrical degrees after the instant of zero voltage, as at F and G in the diagram, leave with increased velocity since the buncher voltage is now slightly higher than the voltage of the accelerator grid (positive signal adds to positive electrode voltage). In the field-free drift space between the buncher and the intermediate cavity, faster electrons F and G catch up with electron E, which previously passed the bunch with no change in velocity. Slower electrons C and D lag behind, and hence draw near to E. At some point between the two cavities, electrons C, D, E, F, and G draw close together in a group. Now consider electron A', which leaves the buncher a half-cycle later than E. In this case its neighboring electrons draw away, since H is slightly slower and B' will be slightly faster. Consequently, the electron stream along the tube consists

of electron bunches separated by regions in which there are few electrons. From the diagram, it appears as though bunching occurs in the first half-cycle of operation. Actually, bunching really occurs two or three cycles later in the relatively free drift-space between cavities. Also, bunching occurs twice in the three-cavity klystron (once between the input and center cavities, and once again between the center and output cavities). Since it is less complex and somewhat easier to understand, this diagram is used to emphasize bunching action, although it really is a representation of a two-cavity klystron with the retardation and acceleration of electrons overemphasized by using a much greater electron-line slope than actually occurs.

Since a continuous stream of electrons enters the buncher grids, the number of electrons accelerated by the alternating (signal) field between the buncher grids on one half-cycle of alternation is exactly equaled by the number of electrons which are decelerated on the other half-cycle. Therefore, the net energy exchange between the electron stream and the buncher is zero over a complete cycle (assuming a sinusoidal signal), except for any losses that occur in the tuned circuit or buncher cavity. As the electrons travel down the tube, they pass through the intermediate cavity grids and induce an oscillation into the middle cavity. Thus, an ac potential similar to the input signal is produced between the middle cavity grids. When the middle cavity is tuned to a frequency slightly higher than that of the buncher cavity, it presents an impedance with an inductive component. This provides a phase relationship between the cavity voltage and the electron stream which causes further velocity modulation of the electron stream. In this case, since the cavity is a high-Q resonant circuit, it causes a voltage build-up which is larger than that of the input signal. Therefore, the electrons are again bunched; this time they are formed into denser bunches, and the free electrons between the bunches are still further reduced (some are absorbed into the new bunches). The new bunches of electrons form in the drift space between the middle cavity and the output (or catcher) cavity, pass down the tube, and enter the catcher cavity.


The conditions at the catcher cavity are somewhat different. This cavity is located along the tube so that the passage of the electron stream in bunches through the first grid creates a negative potential upon it. This negative potential retards the electrons, and, in slowing them down absorbs energy from them. The spacing between the two catcher grids is equivalent approximately to a half-wavelength at the frequency of operation. Thus, by the time the first bunch reaches the second catcher grid, the first catcher grid has reversed polarity and becomes positive, while the second catcher grid is now negative, as shown in the accompanying illustration.

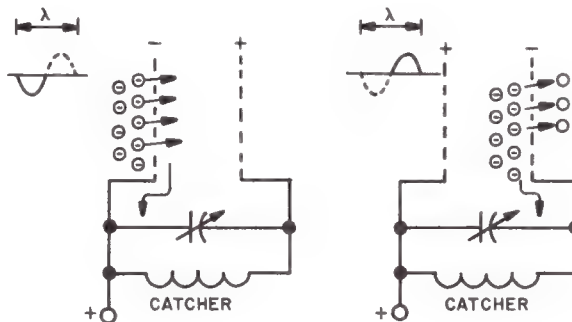

Catcher Grid Polarity

Since the second grid is also negative, it further slows down the electrons and again absorbs energy from them. Thus, in delivering energy to the tuned cavity connected to the catcher grids, the speed of the electrons is greatly reduced. After passing this second set of catcher grids the spent electrons are collected and removed from the tube by the positive collector plate.

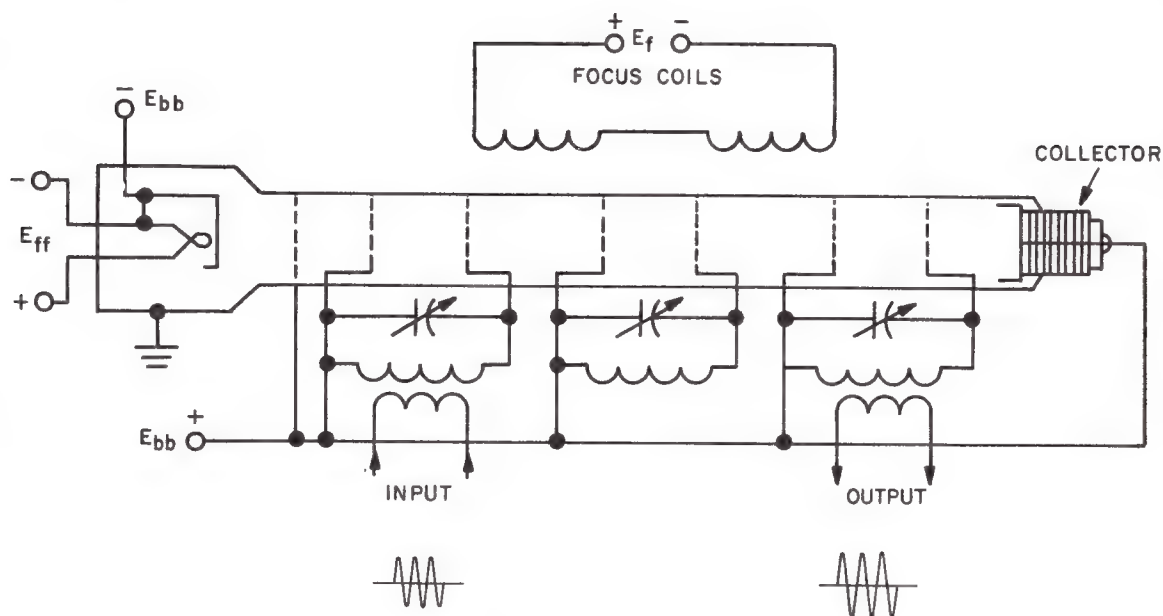A complete multicavity klystron r-f amplifier can be shown schematically as illustrated in the accompanying figure. The operation is exactly as described in the paragraphs above; therefore, it will not be repeated.



Multicavity Klystron R-F Amplifier
Schematic Diagram

Failure Analysis.

No Output. Lack of or improper accelerating voltage, loss of drive power, or improper cavity tuning can result in loss of output. Usually, excessive beam current indicates improper tuning or voltage. A voltage check will indicate whether the voltage is sufficient. **WARNING: Dangerous High Voltage** is present; all safety precautions should be taken to make certain that no shock hazard exists. In practice, the shell of the tube is grounded and a high negative voltage is applied to the cathode. It is particularly important *not to remove any lead shielding* while troubleshooting; otherwise, X-radiation effects will produce a hazard to maintenance personnel. Normally, a no-output condition will be caused by an open circuit (or short circuit) or by a defective tube, rather than by mistuning or low voltage, since in these latter cases some small output normally occurs. When both filament and anode voltages are correct and the proper drive voltage exists, the tube is probably at fault. Substitution of a tube will not immediately restore full output, since the proper tuning and adjustment

procedure must be followed to enable the tube to function properly. Use the manufacturer's recommended procedure for tuning and placing the unit in service, and note any deviations in performance or any abnormal indications as the procedure is followed. Investigate each deviation as it occurs, and make certain that it is cleared up before proceeding further.

Reduced Output. Low filament, drive, or anode voltage, as well as mistuning, can cause reduced output. Check the filament and plate voltages with a voltmeter, observing all safety precautions. An increased beam current can result from improper tuning or improper load. Check the drive, using a dummy load at the input to be certain that sufficient power is available. With sufficient drive established, connect a dummy load to the output and follow the proper tuning procedure. As the tuning procedure is performed, the beam current should reduce, more r-f drive should be required, and a greater output should result. Where focusing coils are used, loss of focus magnetism will show as a reduction in focusing-coil

current and a reduction of beam current (the stray electrons are absorbed before reaching the collector). An increase in beam current can usually be traced to improper cavity tuning. For maximum output, both the input and output cavities should be tuned to the same frequency. In broad-band operation it is necessary that each cavity be tuned to the proper fre-

quency; otherwise, loss of output or of frequency range will occur. As with all other power amplifiers, the proper load must be attached; otherwise, improper impedance relationships will cause unwanted reflections and a loss of power. In receiving applications, low cathode emission will usually cause an increase in noise because of uneven electron emission.

PART 5-7. RF FREQUENCY MULTIPLIERS

RF FREQUENCY MULTIPLIERS

General.

Several applications exist for use of r-f frequency multipliers. For example, a harmonic generator consists merely of a number of frequency-multiplier stages connected in cascade. They are used in receivers, being driven by a stable local oscillator which operates at a low fundamental frequency and is multiplied through several stages to supply an oscillator signal to a VHF or UHF mixer. Likewise, in test equipment, a suitable oscillator has its output frequency multiplied for use as a signal generator or frequency standard, or for other purposes. In a transmitter, the multiplier stage (or stages) allows the use of a single crystal to provide drive for r-f amplifiers operating on harmonically related output frequencies, or it may be used to supply a crystal-controlled output at higher frequencies, where crystal operation at the output frequency is not feasible.

The power output of the multiplier stage varies roughly as the reciprocal of the number of multiplications. Thus, a frequency doubler produces about one-half the output power of a conventional Class C r-f amplifier stage, and a frequency tripler produces about one-third the power; hence, the necessity for cascaded operation at the higher multiples. For example, two doubler stages operated in cascade will deliver twice the power of a single quadrupler stage.

The loaded tank circuit impedance increases roughly in proportion to the number of harmonic multiplications required, since the output power decreases and a greater impedance is necessary to provide the same voltage drop across the tank. This places a practical limit on the number of multiplications possible in a single stage.

Although either triode or pentode tubes may be used as frequency multipliers, the pentode is more commonly used because of the reduced grid drive required for pentode operation, plus the larger power output obtainable for the same plate voltage. Since grid current flows in Class C operation, the multiplier stage requires a slight amount of power from the oscillator to drive it. The reduced drive of the pentode, therefore, allows the oscillator to operate more stably, and permits a lower-rated oscillator tube to be used. Normally, a Class C amplifier is biased at 2 to 2½ times cutoff. The frequency multiplier is

essentially a Class C stage which utilizes its rich harmonic content, or, rather, is operated so as to develop a greater harmonic content than normal. Selection of the desired harmonic by a tuned output circuit produces a relatively large output at that harmonic. To produce the distorted plate current with its rich harmonic content, the stage must be biased higher than for normal Class C operation, and must be driven harder than normal. Thus, plate current flows only during a small fraction of the cycle, roughly from 60 to 120 electrical degrees (depending upon the amount of harmonic multiplication desired). Therefore, the normal grid bias for a multiplier is usually 3 to 4 times cutoff. Because the plate output tank is tuned to a different frequency from that of the input (drive) signal, no plate-to-grid feedback occurs. Therefore, neutralization is never required, regardless of whether triodes or pentodes are used.

PENTODE RF FREQUENCY MULTIPLIER

Application.

The frequency multiplier stage is used to provide an output frequency which is some integral multiple of a fundamental crystal-controlled, or self-excited oscillator frequency. It is universally used in receivers, test equipment, and transmitters.

Characteristics.

Uses Class C operation at all times.

May be self-biased, fixed biased, or a combination of both.

Output frequency is always some multiple of the fundamental.

Normally doubles or triples, but can operate up to about the seventh harmonic.

Efficiency varies inversely with frequency.

Maximum usable efficiency is on the order of 70 percent, and lowest efficiency is about 45 percent.

Grid bias is higher than in the normal Class C amplifier.

Requires more grid drive than would be necessary for operation at the fundamental frequency.


Does not require neutralization.

Circuit Analysis.

General. Schematically, the pentode r-f frequency multiplier appears identical with that of the conventional Pentode R-F Voltage Amplifier or the Pentode R-F Buffer Amplifier previously discussed. However,

there are differences in parts values to provide the correct bias and operation, and the plate tank resonates at a multiple of the fundamental frequency. Detailed differences in operation are discussed below.

Circuit Operation. A typical frequency multiplier circuit is shown in the accompanying illustration. In this configuration, the oscillator output is capacitively coupled through C_c to the grid of V1. Grid bias is obtained through grid current flow in R1, and protective cathode bias is supplied by R2, which is bypassed for rf by C1. The screen voltage is dropped to the proper value by screen resistor R3, bypassed for rf by C2. Variable capacitor C3 and inductance L1 form the output tank circuit, which is inductively coupled to output coil L2. While series plate feed is employed, one end of the tank is bypassed to ground by C4, and the radio-frequency choke (RFC) insures that any residual rf remaining flows to ground by way of C4 rather than through the low impedance of the power-supply filter.

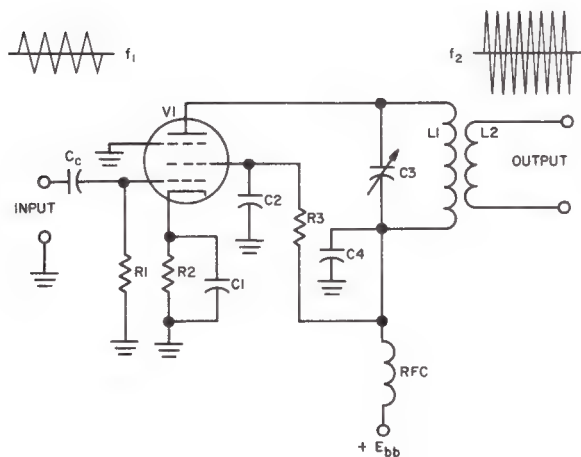

Typical Frequency Multiplier Circuit

With no signal applied no grid bias is developed, and the plate and screen current flow through cathode resistor R2 provides sufficient cathode bias to limit the static current flow to a safe value. When the oscillator signal is applied, the low reactance of coupling capacitor C_c allows practically all of the input to appear across R1 and the V1 grid. On the positive half-cycle of the input signal the plate current increases, and on the negative half-cycle it decreases. During the positive half-cycle C_c charges, and during the negative half-cycle it discharges from the capacitor to ground, a negative bias is developed across R1; this grid bias voltage and the cathode voltage stored in C1 produce a high bias many times the cutoff value. (See the introduction to this section for a further discussion of cathode bias and grid-drive, or signal bias.)

Because of the extremely high bias, the plate current conduction period is reduced to a small fraction of the total cycle. Actually, it is less than a half-cycle and varies with the amount of multiplication desired. For a frequency doubler it is about 120 electrical degrees, and for a quintupler it is about 60 degrees. The short time during which plate current flows produces a very distorted plate pulse which is rich in harmonics. When plate tank C3, L1 is tuned to the desired output frequency, it offers a high impedance at the frequency, so that a large drop in plate voltage occurs across the tank. With an increasing plate current, caused by the positive input signal, the plate voltage is dropped toward zero; during cutoff, produced by the negative portion of the input signal, the plate voltage increases to almost the full value of the supply voltage. A decreasing plate voltage induces a negative output signal in L2 by transformer action, since it is coupled via tank coil L1, while an increasing plate voltage induces a positive output signal in L2.

The instantaneous current and voltage relationships in a frequency doubler are graphically illustrated in the accompanying illustration.

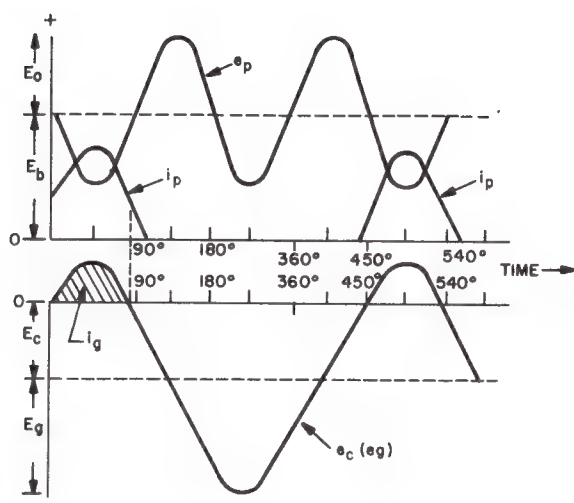


Plate Current and Grid Voltage Relationships

As can be seen from the figure, the plate current flow time is longer than the grid current flow time, but both maximums occur together. Thus, as instantaneous grid voltage e_g starts its positive excursion, no plate current or grid current flows until the grid voltage reaches cutoff. At this time plate current starts to flow. Slightly later, at zero bias, grid current flows also. The grid current flow is supplied from the oscillator or drive source. The increasing plate current (obtained from the power supply) causes a voltage drop across the plate tank impedance (tuned, for example, to twice the frequency of the oscillator). When the plate current is at its maximum, the plate voltage is at its minimum. At this time some plate power is absorbed by the tuned tank circuit. As the drive signal reverses and causes the instantaneous grid voltage to fall toward zero, the plate current decreases and the plate voltage increases. The grid signal continues to swing in the negative direction while the plate voltage rises (in a positive direction). At the static dc level of plate voltage (E_b), the grid drive is approximately equal to the dc bias (zero bias), and as the grid voltage increases toward cutoff, e_p continues to rise. At cutoff, the tank circuit supplies power, and e_p rises, even though the plate current ceases. This is the so called "flywheel" action of the tank circuit,

which continues operation during the time the tube is inactive beyond cutoff. When the instantaneous negative grid voltage reaches the dc bias level (E_c), plate voltage e_p reaches its positive peak and is approximately equal to E_o , the output voltage.

As the instantaneous grid signal continues to decrease beyond the dc bias level, the plate voltage now falls and becomes negative-going, since the tank is operating at twice the grid frequency, and the input signal, being highly negative, has no effect on the plate current. At the negative peak of drive voltage E_g , plate voltage e_p completes its second negative excursion and starts its second positive excursion. The drive voltage also swings positive again and now starts back toward cutoff and zero bias. When the drive is again equal to the dc grid voltage, the second positive peak excursion is reached and the plate voltage starts dropping. As the grid voltage passes cutoff, plate current is again drawn and the plate voltage continues to drop until it reaches the third minimum, when the plate and grid currents are again at a maximum. Once again the plate power is absorbed by the tank to overcome the losses in the tank and to recover the energy supplied to the circuit during the inactive period.

With the tank replenished; it is again ready to supply the flywheel effect of the next cycle of operation. Note that always during the short pulses of plate current flow, the tank is absorbing power from the plate circuit. While on the negative grid swing (where the tube plate current is normally cut off and no output should occur), the tank circuit continues to oscillate and thus supplies the missing portion of the signal. Since the tank oscillations are twice that of the fundamental oscillator frequency, two peaks occur for every fundamental peak (in the tripler three peaks occur). The greater the number of oscillations required between the periods of pulses of plate current, the more the energy required from the tank to sustain these oscillations. Hence, the efficiency and output drop off as the multiplication of frequency is increased. In addition, the flywheel action of the tank maintains an approximately sinusoidal waveform in the output, while the fundamental plate current pulses are greatly distorted. When the grid bias and drive voltage amplitudes, as well as plate voltage, are adjusted for maximum output at a particular frequency, a slightly distorted output may be obtained; however, this can usually be compensated for by a slight adjustment of the tank tuning capacitor.

While push-pull operation can be used to supply more power output, more drive is required and only the odd harmonics are multiplied, since the even harmonics cancel out in the plate circuit. Therefore, push-push operation is employed, as explained in the next circuit discussion.

Failure Analysis.

General. The discussion of failure analysis for the Pentode R-F Voltage Amplifier, and for the Pentode R-F Buffer Amplifier, discussed previously in this section of the handbook, are generally applicable to the frequency multiplier.

No Output. Lack of grid drive, plate, screen, or supply voltage, or a defective tank, output coil, or tube can cause loss of output. Check with a voltmeter to make sure that the supply voltage is normal. If the cathode voltage is also normal, the proper plate and screen currents probably exist, so that either the plate tank is detuned or insufficient drive is indicated. Connecting a milliammeter in series with R1 and ground will indicate the amount of grid current flow; this will show that R1 is not open and serve as a check on C_c . If C_c is open, no drive would be present to cause current flow through R1; if it is shorted, the plate voltage of the preceding oscillator stage will bias the grid heavily positive, cause a large plate current flow, and produce a high cathode bias with practically no output. If cathode bypass capacitor C1 is open, degeneration will reduce the output but not completely eliminate it; if C1 is shorted, a large plate current will flow in the absence of drive voltage, but the plate current will appear normal as long as enough drive is present to produce sufficient signal bias. If screen capacitor C2 is open, self-oscillation and erratic operation (with some output) will probably occur; if C2 is shorted, the supply voltage will be normal but will be entirely dropped across R3. Therefore, R3 will heat, probably discolor or smoke, and eventually burn out. Meanwhile, no plate output will be obtained because of the lack of screen voltage to attract electrons from the cathode. Although a very small plate current may flow because of plate voltage attraction, this output will be practically negligible.

If plate bypass capacitor C4 is shorted, a similar condition will exist, with the entire supply voltage being dropped across the RFC, eventually causing the choke to burn out. Although screen voltage will be present, the plate voltage will be zero and no output

can occur. In addition, the screen will tend to act as the plate and collect all electrons, so that excessive screen current will flow; in this case the screen will be overloaded and heat sufficiently to shown color, and if prolonged the tube may be damaged.

If C3 will not tune L1 to resonance at the desired harmonic, no output will be developed across the tank, since its impedance will be too low to produce an output. The resonant frequency of the tank can be checked with a grid-dip meter or a wavemeter. If all voltages are present, but the screen and plate voltages appear higher than normal while the cathode bias is lower than normal, and with low plate current and no output, either output coil L2 is open or the tube is defective. Check L2 (and the load) for continuity with the power off; if satisfactory, it is likely that tube V1 is defective.

Low Output. With a low screen or plate voltage, a low drive, a high-resistance plate circuit, or a defective tube, a reduced output will be obtained. The plate, screen, and cathode bias voltages can be checked with a voltmeter. Use an r-f choke in series with the meter and check the voltage across R1; this will determine whether grid bias exists and also whether sufficient drive exists. If the bias is low because of lack of drive, the stage will operate Class A, lose efficiency, and result in reduced power output. If screen resistor R3 increases in value with age, the screen voltage will be reduced, as will the output. A similar condition can be caused if screen bypass capacitor C2 is leaky. Check C2 with an in-circuit capacitance checker, or disconnect it from ground and check for a constant voltage between the capacitor and ground by use of a voltmeter. A similar condition can also occur if plate capacitor C4 is leaky. A high resistance in the tank can be caused by a poorly soldered joint. This will usually shown as a broad dip in plate current with tuning, rather than the normal sharp dip. Leaky insulation on C3 can also cause a loss of rf and output. Check the capacitor insulating supports for indications of an r-f burn, or accumulated dirt and moisture, which can produce a shunting resistance to ground (particularly salt deposits from spray). Remove the capacitor, and clean and dry it thoroughly if it appears to be dirty; normal grayish oxidation of plates and metal supports does not indicate the need for cleaning. Do not lubricate the capacitor bearings because of rotor binding (adjust the tension screw instead); otherwise, bad contact will create a high r-f resistance. When the bias and

voltage indications appear normal, but the plate current is low and cannot be increased to a normal value (or if it drops immediately after turn-on, or progressively decreases), low tube emission is probably the trouble.

PUSH-PUSH RF FREQUENCY MULTIPLIER (ELECTRON TUBE)

Application.

The r-f push-push frequency multiplier is used as a frequency doubler in transmitters and test equipments that require a greater output and better efficiency than is possible with the single-tube multiplier.

Characteristics.

Uses Class C bias at all times.

May be self-biased, fixed-biased, or a combination of both.

Provides approximately twice the output of a single-tube multiplier stage.

Provides efficiency almost equivalent to that of a normal Class C amplifier.

Requires a push-pull input connection and a paralleled-plate output.

May use triode or screen-grid tubes.

Operates push-push instead of push-pull (a plate pulse is provided for each cycle of operation).


Does not require neutralization, since output frequency is double the input frequency.

Circuit Analysis.

General. Like the single-stage frequency multiplier, previously discussed in this section of the handbook, pentodes are used in preference to triodes, since the low drive requirement provides less load on the input stage, and a greater output is obtainable than from a triode operating at the same plate voltage. Where the single-stage multiplier may be used to double, triple, or further multiply the input frequency, the push-push stage is usually operated only as a doubler. While it will also operate as a quadrupler (since only even harmonics can be produced with appreciable output), the same output can be more easily obtained with two single-stage doublers, which require slightly less than half the drive power. Thus, push-push operation is more limited in its application than the basic single-stage multiplier. It is mainly used

where a large doubler output is required, since it will produce this output without any loss because of multiplication. This is true because a plate current pulse is provided for each positive half-cycle of the input signal, or one for each output cycle. Thus, the tank circuit requires less replenishing, and greater output and efficiency are obtained. Although a push-pull input is required, this can easily be obtained with a grid tank circuit. In addition, harmonics of odd order, which can sometimes cause a final output on an unwanted frequency, are minimized, and a purer output waveform is supplied than that by the single-tube doubler stage.

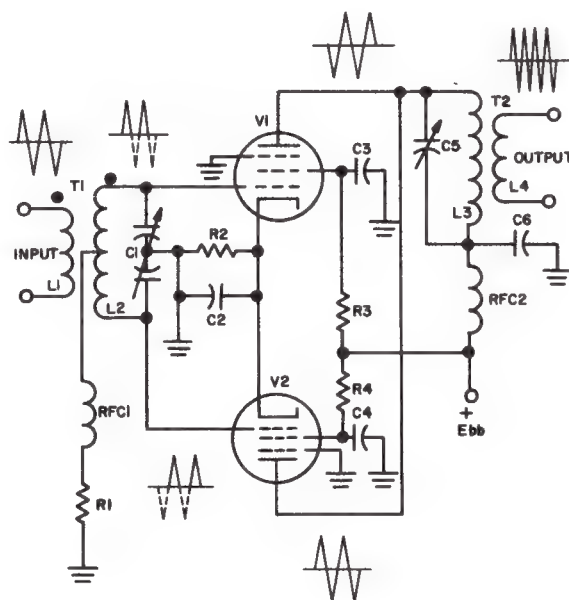Circuit Operation. The accompanying illustration shows a typical push-push doubler stage.



Push-Push Frequency Multiplier Stage

As is evident from the schematic, a push-pull input is provided by r-f transformer T1. L1 is the primary, and L2 is tuned by split-stator capacitor C1 to the fundamental frequency. Signal bias is supplied by grid drive, causing grid current flow through R1, with RFC1 keeping any rf out of the bias circuit. A protective cathode bias is also supplied by R2, which is bypassed for rf by C2. Tubes V1 and V2 are pentodes with their suppressors directly grounded, although tubes having the suppressor connected to the cathode

internally could also be used. Screen voltage for the tubes is dropped to the proper value by R3 and R4, which are bypassed for r-f by C3 and C4, respectively. The plates of V1 and V2 are parallel-connected to plate tank L3, C5. The secondary of r-f transformer T2, winding L4, provides an inductively coupled output, although capacitive coupling could have been used as well. Series plate feed is used, and the dc plate voltage is applied through RFC2 to the bottom end of L3, which is bypassed for rf by C6. Thus, any rf at this point flows to ground through C6 rather than through the power supply filter capacitor, and any body capacitance effects which otherwise would occur when tuning tank capacitor C5 are also eliminated.

When the input signal is applied to input transformer T1, the input voltage in primary winding L1 induces a voltage into secondary winding L2 by transformer action. The center of the L2 secondary is connected to ground through RFC1 and R1. The windings are polarized so that the top end of L2 (connected to the V1 grid) is positive when the top end of L1 is positive. Thus, when the top end of L2 is positive, the bottom end of L2 is negative. Since the bottom end is connected to the grid of V2, V2 is negative when the V1 grid is positive, and vice versa. Thus, a push-pull input connection is provided. Tuning capacitor C1 is a split-stator type which provides a balanced tank arrangement to ground, and also resonates L2 to the operating frequency of the oscillator, or input stage.

In the absence of an input signal, protective cathode bias is provided by plate and screen current flow through R2. The cathode bias and the signal bias are effectively series-aiding, so that the total Class C bias is a combination of both. (See the introduction to this section for a discussion of cathode bias and signal bias.) As the input signal is applied, either the V1 or V2 grid conducts on the positive half-cycle of operation, and grid current flows through R1, producing the signal bias, which is added to the cathode bias. Since only one tube conducts at a time, the cathode bias at any particular instance is produced essentially by only one tube. (When signal bias is absent both tubes will conduct, so the protective bias is produced by both tubes.)

On the positive half-cycle of input signal when V1 conducts, plate current flows for approximately 120 electrical degrees of operation. During the remainder of the cycle, tube V1 is cut off. When the input signal

goes negative, a positive grid voltage is induced in L2 and applied to V2, while V1 is held at plate current cutoff by a negative signal. The positive grid input to V2 causes plate current to flow for a period similar to that of V1. Both plates are parallel-connected, so that a pulse of plate current occurs for each half-cycle of input signal. During current flow, the plate voltage is dropped across the high impedance of output tank L3, C5, which is tuned to twice the input frequency. Each time the plate voltage is reduced to its minimum value, energy is absorbed by the plate tank. Hence, it receives a push to keep it oscillating each negative half-cycle, from which action the term *push-push* was derived. Note that in push-push operation each tube operates alternately while the other tube remains at rest; this should be distinguished from push-pull operation, where the current of one tube increases while the current of the other tube decreases (both simultaneously).

The relationships of the grid voltage and plate current, and grid current and plate voltage waveforms is shown in the accompanying figure.

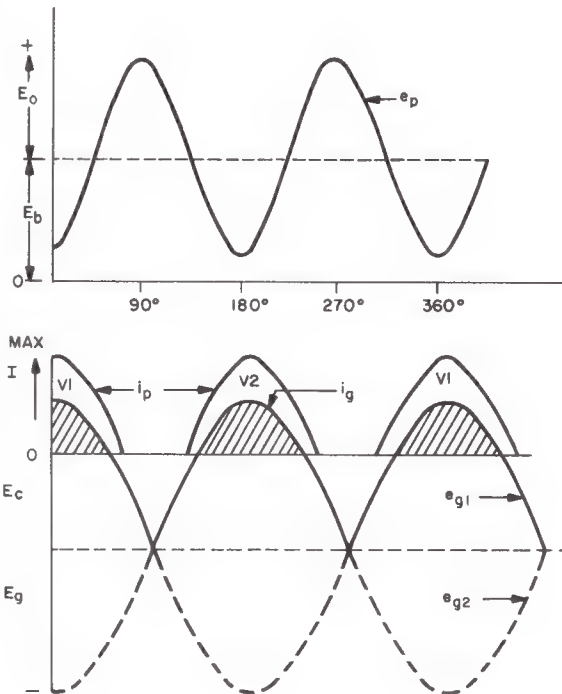


Plate and Grid Waveforms and Their Relationships

As the grid voltage (e_{g1}) to V1 rises in a positive direction, it drives the tube above cutoff, and plate current flows. Plate current i_p , in flowing through the tank impedance at the resonant frequency, produces a voltage drop which opposes the applied plate voltage and reduces it toward zero. As the grid voltage continues to increase grid current flows when zero bias is reached, and develops a bias voltage across R1. RFC1 prevents shunting of the r-f input to ground through R1, so that only the rectified dc bias current flows through R1. The current flow is from ground through cathode bias resistor R2, to the cathode, to the grid, and back through R1 to ground. The cathode bias is increased by the small amount of grid drive current, but this bias remains constant as long as grid current flows, and averages to a somewhat smaller value over the entire cycle. Because of the low value of cathode resistance employed, the over-all bias is enhanced by only a volt or two. Most of the bias voltage is developed across R1, which is a large value of resistance (10K to 50K). As the grid current reaches its peak, so does the plate current of V1. At this time the plate voltage of V1 reaches a minimum value, and power is absorbed by the resonant tank circuit. When the input signal reaches its positive peak and changes direction (assuming a sine wave), it swings negative and falls toward zero. Meanwhile, the plate current and grid current also fall. When the grid voltage drops below zero bias, the grid current stops flowing and the plate current continues to decrease, while the plate voltage increases still further. The plate voltage continues to increase, even at cutoff when the plate current ceases, because of the fly-wheel action of the tank circuit. At this time the tank is supplying energy to the circuit while the tube is inoperative.

When the input signal on the V1 grid reaches zero and continues further in a negative direction (the negative half-cycle), a positive-going signal is induced on the V2 grid through T1. Thus, as the V2 grid rises above cutoff, plate current again flows, but this time in V2. The flow of plate current causes a plate voltage drop across the high tank impedance, and the effective plate voltage of V2 follows. At zero bias, grid current flows in V2 and produces a negative bias equal to that produced by V1 on the opposite half-cycle. When the grid current in V2 is at a maximum, so is the plate current, and the effective plate voltage is again at a minimum. As the input signal reaches its negative maximum and reverses direction it swings

positive, as does the plate voltage. Simultaneously, V2 plate current decreases, first zero bias and then cutoff is reached, and V2 stops conducting. Meanwhile, since the tank circuit is oscillating in synchronism, the plate voltage continues to rise until the positive peak voltage is reached. At this time e_{g1} and e_{g2} are equal to bias voltage E_C and to each other, plate current is completely cut off and the tank is again supplying energy to the circuit. As e_{g2} goes more negative, e_{g1} goes more positive. When cutoff is reached V1 conducts again, and the plate voltage again drops toward its minimum value. At the plate voltage minimum, the plate current is again at its maximum value (as is the grid current), and the tank again absorbs power from the plate circuit. Since the tank oscillates in synchronism, completing one oscillation for each half-cycle of input, the output is twice the input frequency. Because the tank is reinforced for each half-cycle of the input, or once for each cycle of operation, not as much power is expended from the tank as in a single-stage circuit. The plate efficiency, therefore, increases over that of the single stage, since only half as much energy is expended by the tank, and less is absorbed from the plate. As the input signal continues, the action just described is repeated over and over again. Since L4 is inductively coupled to L3, the circulating tank current induces an r-f voltage in L4 by transformer action, and the output is approximately equal to the plate voltage drop developed across one tube. Any other harmonics in the plate circuit are offered a very small impedance, since the tank is not tuned to that frequency; thus, only the desired harmonic frequency exists in the output.

Although the pulses of plate current occur for only 120 degrees and are highly distorted, the fly-wheel action of the tank circuit tends to smooth the output into approximate sine waves at double the frequency. Since frequency multipliers are usually never modulated, any remaining waveform distortion is of little significance.

Failure Analysis.

No Output. Lack of an input (drive) signal, loss of screen or plate voltage, an open output circuit, or defective tubes can cause loss of output. Check the plate, screen, and supply voltages with a voltmeter. For no output it is usually necessary for both tubes to be defective; if one tube is operative, the output will be reduced rather than eliminated entirely. If

cathode bias resistor R2 is open, the circuit will be incomplete and no output can occur. If r-f transformer T1 or T2 is open or shorted, no output can occur. Lack of input (drive) is indicated by no bias voltage, as measured across R1. Likewise, no input will produce high plate and screen current because of the loss of grid bias, and thus cause the protective cathode bias voltage across R2 to be larger than normal. Similarly, if either RFC1 or R1 is open, no grid bias will be obtained, and R2 will produce a larger than normal protective bias with no output. When in doubt, a resistance check of L1, L2, R1, R2, and RFC1 with the power OFF can be quickly and easily made — or either an oscilloscope or a VTVM can be used to check the grids of V1 and V2 for rf. If no drive exists and C2 is shorted, the tubes will show color and be damaged (if the short is prolonged), while no output will be obtained.

If screen resistor R3 or R4 is open, or if capacitor C3 or C4 is open or shorted, there will be a reduction in output, but not complete loss of output; however, if both resistors are open or if both capacitors are shorted, no screen voltage will appear and there will be no output. If either C3 or C4 is shorted, R3 or R4 will heat abnormally, show color, or smoke, and will eventually burn out. If plate choke RFC2 is open, no plate voltage will be applied to either V1 or V2, and there will be no output. A similar condition will result if C6 is shorted; in this case the supply is dropped across the r-f choke, which will probably cause it to smoke and burn out. If C5 does not resonate L3 to the proper frequency, little or no output will be developed. Check L3 for continuity with an ohmmeter, with the plate voltage OFF. Use a grid dip meter or a wavemeter to check the tank resonant frequency. If the condition of C5 is in doubt, coil L3 must be disconnected checking C5 with a capacitance checker. If secondary L4 opens, no load will appear on either V1 or V2 and a lower than normal plate current will be indicated. L4 can be checked for continuity with an ohmmeter.

A milliammeter can be inserted in the grid and plate circuits to facilitate the location of trouble. It will indicate the grid current, which shows whether sufficient drive is present; it will also indicate the plate current, which can be checked for a dip (indicating resonance) and for proper loading. A sharp

dip in the plate current with very low minimum current and no output indicates that the load is not coupled sufficiently or that the output circuit is open.

Low Output. No voltage or low voltage on the screen or plate, insufficient drive, or a defective tube will cause low output. The screen and plate voltages can be checked with a voltmeter; the grid drive can also be checked with a voltmeter by measuring the grid bias voltage developed across R1. If either R3 or R4 is open, no screen voltage will be applied to V1 or V2, respectively, and reduced output will result. Likewise, if either C3 or C4 is shorted, a similar condition will occur. Low screen voltage can be caused by a change in value of resistor R3 or R4, or by a leaky capacitor C3 or C4. A milliammeter inserted into the supply side of each screen resistor will indicate whether proper screen current is obtained. Inability to obtain the rated screen current at the correct voltage indicates a defective tube. If RFC2 is open or if C6 is shorted, no plate voltage will be applied to either V1 or V2. In this case the screen will tend to act as the plate, get hot, and eventually be damaged (if the condition is prolonged). A high resistance due to a poorly soldered joint in the plate circuit of V1 or V2 will cause reduced voltage and output, and will usually be indicated by broad tuning of tank capacitor C5, with low plate current. If the output is low and the voltages appear normal, remove one tube at a time, noting whether the output rises or drops. A partially shorted tube can cause the output to rise when the defective tube is removed. Normally the output should drop to about half value; if no change occurs, the removed tube is probably defective.

Incorrect Output Frequency. If other than the desired output frequency is obtained, one of the tubes is probably inoperative. Since a push-push circuit can produce only even harmonics (2nd, 4th, 6th, etc.), an odd harmonic can be produced only by single-tube operation. In this case the output will usually be reduced. Normally, the tank circuit does not tune through more than one harmonic. However, in multiband equipment using shorting switches to change the inductance, it is possible for a poor or open contact to allow the incorrect value of inductance to be used, and thus cause resonance at some undesired harmonic.

PART 5-8: DEFLECTION

DEFLECTION AMPLIFIERS

General.

A deflection amplifier is intended to accept, as an input, a signal whose waveform may be simple (as in the case of a direct-current waveform) or exceedingly complex (as in the case of several fundamental frequencies in combination with a multitude of their harmonics), amplify it, and furnish an output in which the original waveform remains unchanged. An amplifier intended for use as a horizontal deflection amplifier is required to increase the amplitude of the sawtooth sweep waveform, in order to produce sufficient horizontal deflection. In radar displays of certain types, a triangular type of sawtooth waveform is used for a horizontally swept timebase. An amplifier intended for use as a vertical deflection amplifier is required to increase the amplitude—sometimes to enormous proportions—of almost any type of waveform. Since the requirements of the vertical deflection amplifier are generally more stringent than those of the horizontal deflection amplifier, insofar as gain, bandwidth, and frequency response are concerned, the following discussion will be particularly applicable to the amplifier intended for vertical deflection.

The most complex waveform which may be required to be amplified is a perfect square wave. Such a wave contains a fundamental frequency and an infinite number of odd harmonics. It has zero rise and decay times, and a perfectly flat top and bottom. The voltage changes from a maximum positive value to a maximum negative value instantaneously. In order to amplify a waveform containing an infinite number of harmonics, without distortion, an amplifier having an infinite bandwidth would be required. Such a waveform and such an amplifier do not exist, for the following reasons: Any change in voltage, no matter how abrupt, requires a certain amount of time to occur. The presence of shunt capacitance, which in some amount is always present in a circuit, causes the rate of change of voltage to be further reduced. This results from the fact that the voltage across a capacitor cannot change instantaneously. In addition, every amplifier, no matter how careful the design, introduces some degree of distortion, which deteriorates the (perfect) square wave.

In actuality, the square wave applied to a vertical amplifier contains several hundred (rather than an in-

finite number) odd harmonics. The following illustration shows the output waveforms from amplifiers in which the high-frequency response was purposely restricted. The input to the amplifiers, in each case, was a "perfect" square wave. In A, the output was restricted to the tenth harmonic of the fundamental frequency. In B the output waveform contained frequencies as high as the one-hundredth harmonic of the fundamental, while in C the output contained over five-hundred harmonics. In order to reproduce a square wave with reasonable fidelity the vertical deflection amplifier should have a bandwidth sufficiently wide to pass the tenth odd harmonic of the fundamental frequency. Note that this is a frequency which is 21 times the fundamental. More accurate reproduction of the input waveform requires a bandwidth wide enough to pass the fortieth odd harmonic (81 times the fundamental) of the fundamental frequency.



Output Square Waves Having Restricted Odd-Harmonic Content

A waveform having a very short time duration, such as a timing pulse, requires a different method of calculating the minimum high-frequency response required of the deflection amplifier. The minimum upper limit of response required is inversely proportional to the pulse duration, as follows:

$$f_{\max} = \frac{1}{d}$$

where: $f_{\max}$ = required minimum upper limit of amplifier response, in megahertz

d = pulse duration, in microseconds

As an example, a 1-microsecond rectangular pulse requires a minimum frequency response which is uniform up to 1 megahertz. A 1/4-microsecond rectangular pulse requires a minimum frequency response uniform up to 4 megahertz.

In addition to pulse duration, the high-frequency response requirements of the vertical deflection amplifier also depend upon the rise time of the pulse to be amplified. The rise time is the time required for the pulse to increase from 10 percent to 90 percent of its maximum amplitude. The shorter the rise time required, the higher the frequency response of the vertical deflection amplifier must be to reproduce the waveform.

Finally, in order to accurately reproduce the original waveform in the amplified output, the vertical deflection amplifier must have an absolute minimum of phase shift. That amount of phase shift which is present must be proportional to the frequency of the component frequencies of the input waveform. As an example, suppose a complex waveform which is composed of a fundamental sine wave plus its second harmonic is applied to the vertical deflection amplifier. Suppose, further, that the amplifier delays the fundamental by the interval of time equal to one-quarter cycle. In order to preserve the original waveform, it is necessary that the second harmonic be delayed by an equal interval of time, to maintain the time relationship between the fundamental and the second harmonic. In order to obtain the same interval of time delay, the second harmonic must be delayed by one cycle. A third harmonic, if present in the input waveform, would have to be delayed by three fourths of a cycle. By this means a linear phase shift is produced in which the angular degree of phase shift is directly proportional to the frequency ratio of the harmonic to its fundamental.

BASIC DEFLECTION AMPLIFIER (ELECTRON TUBE)

Application.

The deflection amplifier is used to amplify the signals before they are applied to the deflection plates of an electrostatic-deflection type of cathode-ray tube or to the deflection coils of an electromagnetic-deflection type of cathode-ray tube. Two separate amplifiers are associated with each cathode-ray tube: the horizontal deflection amplifier, which normally amplifies the horizontal sweep signals, and the vertical deflection amplifier, which normally amplifies the input waveform to be displayed on the screen of the cathode-ray tube.

Characteristics.

Horizontal Deflection Amplifier. Input impedance is high; loading of the preceding horizontal generator circuit is thereby prevented.

Input capacitance is low; attenuation of high frequencies is thereby prevented.

High-frequency response is good, but not generally as good as the response of the vertical deflection amplifier.

Bandwidth usually covers 10 Hz to 100 kHz; certain applications may require a range of 1 Hz to 500 kHz; other applications (such as fixed sweeps of radar deflection) may require only a limited range in bandwidth.

Output impedance depends on intended application: impedance is high if amplifier is designed for voltage (electrostatic) deflection; impedance is relatively low to match the impedance of deflection coil if designed for current (electromagnetic) deflection.

Gain of the amplifier depends on application; the gain is usually lower than that of the vertical deflection amplifier, because the sweep generator output normally feeding the horizontal deflection amplifier is ordinarily higher and more constant than the input signal feeding the vertical deflection amplifier.

Balanced output (push-pull) is desirable, to prevent distortion caused by unequal amplification of positive and negative signals.

Vertical Deflection Amplifier. Input impedance is very high; loading of the preceding output circuit, with the consequent waveform distortion, is thereby prevented. (Special applications may require a low input impedance, which must then be matched to the source impedance of the input signal.)

Input capacitance is very low; attenuation of high-frequency components of input signal is thereby prevented.

High-frequency response is very good; application generally demands a better response than that of the horizontal deflection amplifier.

Bandwidth usually covers 10 Hz to 1 MHz; certain applications may require a range of 2 Hz to 10 MHz; other applications may require a range which includes zero hertz (direct current), but at the same time they may require only a limited high-frequency response.

Output impedance depends on the intended application, in the same manner as in the horizontal deflection amplifier. The impedance is high if the

amplifier is designed for voltage (electrostatic) deflection; it is relatively low and must match the impedance of the load (deflection coil) if the amplifier is designed for current (electromagnetic) deflection.

Gain of the amplifier depends on its intended application: it must be sufficient to produce a pattern of acceptable size, on the particular cathode-ray tube used, from the smallest (voltage) input signal required to be displayed on the screen.


Balance output (push-pull) is desirable—more so than in the horizontal—in order to reduce pattern distortion and beam defocusing. Since the input signal to the vertical deflection amplifier is generally much lower in amplitude than that of the horizontal input signal, the amount of gain required of the vertical amplifier is generally higher, and hence the possibility of distortion is also higher.

Circuit Analysis.

General. The circuit discussed here is a basic type of circuit and is given only for the purpose of discussion. More detailed discussion on actual circuits used

as deflection amplifiers will be found in the two amplifier circuits to follow: Voltage Deflection Amplifier and Current Deflection Amplifier.

The following circuit is actually a simple paraphase amplifier, which is used to produce two output voltages, equal in amplitude and opposite in phase (polarity). Since 50 volts per inch is a common deflection sensitivity for cathode-ray tubes, and since the gain of the stage (V1) is less than one, the amplitude of the input signal to this stage should be on the order of 50 volts. The input signal is applied through coupling capacitor C1 to the grid of the deflection amplifier tube, V1. The grid is returned to cathode through grid resistor R1. Plate voltage is applied through plate load resistor R4, and the cathode is biased by means of R2, which is bypassed by C2. The values of R3 and R4 are equal, and the same current passing through them will produce signals which are equal in amplitude but opposite in phase (polarity) at the plate and cathode. These two outputs, which provide push-pull deflection, are coupled through C3 and C4 respectively, to the vertical deflection plates of

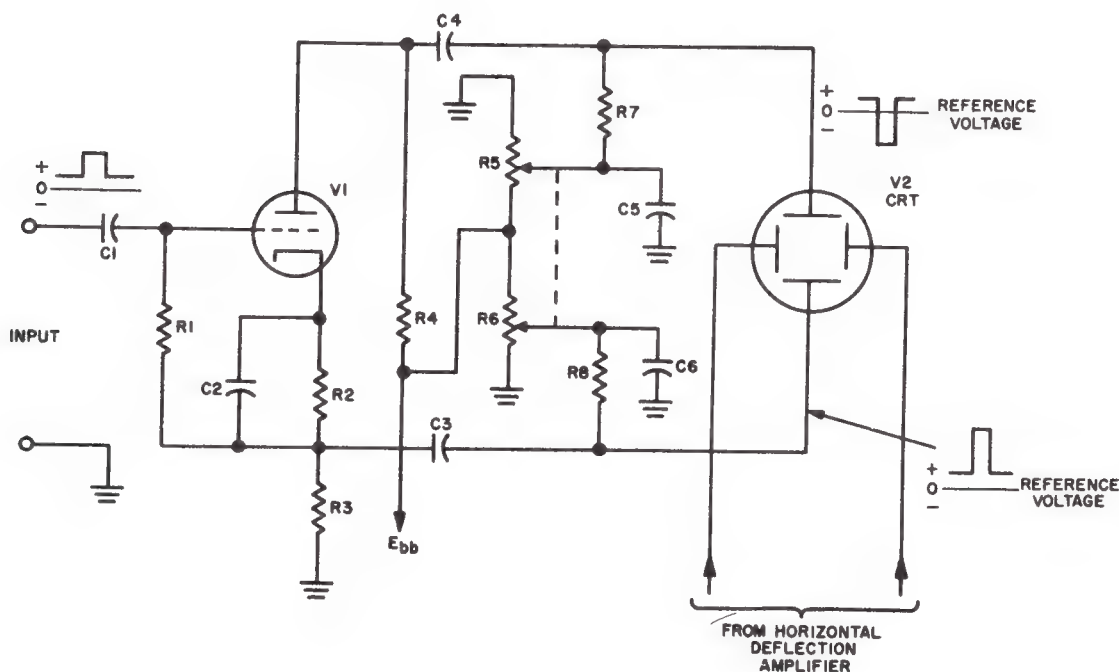

Typical Deflection Amplifier Used for Vertical Deflection

cathode-ray tube V2. Equal deflection above and below a zero-voltage base line is provided by a centering control network consisting of dual control R5/R6, and resistors R7 and R8, which are bypassed by C5 and C6, respectively. Capacitors C5 and C6 insure that any electrons striking the deflection plates will be removed, to prevent a negative charge from building up. If a positive pulse of short time constant is applied at the input to the circuit, to C1, the output at the plate of V1 will be an inverted, or negative pulse, which is shown at the top plate of cathode-ray tube V2 as a pulse below the reference voltage. The output at the cathode of V1 will be an upright, or positive pulse, which is shown at the lower plate of V2 as a pulse above the reference voltage.

Failure Analysis.

No Output. If a signal having an amplitude within the input limits of the deflection amplifier is applied to the input terminals, a defective tube is the most probable cause of a no-output condition. An open coupling capacitor C1, a shorted grid resistor R1, an open cathode resistor R2 or R3, or an open plate resistor R4 would also be responsible for no output, as would also a power supply failure.

Reduced or Unstable Output. In the typical circuit illustrated, the failure of a component is more likely to cause a reduced, distorted, or unstable output, rather than no output whatsoever. A leaky coupling capacitor C1 or a change in value of any resistor would contribute to a reduced or unstable output. If cathode resistor R2 or R3 changed in value, the outputs from the plate and cathode would be shifted from the designed center (which may or may not be at ground potential, depending upon the designed application), and the output would be shifted with respect to the zero reference. If shifted too far, peak distortion may result. A similar condition would occur if resistor R5, R6, R7, or R8 became either open-circuited or changed in value, or if capacitor C3, C4, C5, or C6 became leaky. If capacitor C3 or C4 became open-circuited or if capacitor C5 or C6 became shorted, one half of the normal output signal would be removed from the cathode-ray tube, which would then display only the positive or the negative portion

of the signal, depending upon the half of the circuit which continued to function.

VOLTAGE DEFLECTION AMPLIFIER (FOR ELECTRO-STATIC CRT) (ELECTRON TUBE)

Application.

The voltage deflection amplifier is used to amplify the input signals before they are applied (normally) to the vertical deflection plates of an electrostatic-deflection type of cathode-ray tube. It is also used to amplify the output signals of a sweep generator, before they are applied as a horizontal sweep voltage to the horizontal deflection plates of an electrostatic-deflection CRT.

Characteristics.

Horizontal Deflection Amplifier. Input impedance is high, thereby preventing any loading of the preceding horizontal generator circuit.

Input capacitance is low, thereby preventing the attenuation of high frequencies.

High-frequency response is good, within the design limits of the amplifier (which in many cases are more restricted than those of the vertical deflection amplifier).

Low-frequency response is good, but only in exceptional cases do the requirements demand response down to zero frequency (direct current).

Bandwidth depends on application design: usually covers a range of approximately 10 Hz to 100 kHz; special applications may require a range of 1 Hz to 500 kHz; other applications may require only a limited range, as in the switch-selected fixed sweeps used in radar deflection.

Output impedance is high, since no current need be supplied to the deflection plates of a CRT.

Gain depends on application design: as a rule it is relatively high, but not as high as that of a vertical deflection amplifier, because the input to the horizontal deflection amplifier is usually furnished by a sweep generator having an output level of appreciable value.

Balanced output, furnished by a push-pull type circuit, is desirable, in order to obtain a uniform deflection field, and avoid pattern distortion and defocusing effects inherent in single-ended output.

Vertical Deflection Amplifier. Input impedance is extremely high, thereby preventing any waveform distortion due to loading of the preceding output circuit supplying the signal to be displayed on the CRT. (Special applications may require a low value of input impedance, which must then be matched to the source impedance of the input signal. Normally this would occur only when the deflection amplifier is permanently connected to a signal source. This would not be true in the case of a deflection amplifier used in a test oscilloscope, which must function with widely varying source impedances.)

Input capacitance is very low, thereby preventing the attenuation of the high-frequency components of the input signal.

High-frequency response is very good, generally better than that of the horizontal deflection amplifier.

Bandwidth depends on intended application; usual range is 10 Hz to 1 MHz. Test oscilloscopes of high quality may have a vertical amplifier bandwidth covering 2 Hz to 10 MHz. Other applications, such as oscilloscopes designed for use in teletype and audio work, may require a range which includes zero hertz (direct current), but they may require only a limited range in the higher frequencies.

Output impedance is high, since only a potential difference (no current) is required by the deflection plates of a cathode-ray tube.

Gain is usually high, and a gain control is usually included in the circuit, calibrated both in step and vernier values of voltage gain and/or decibels.

Balanced output (push-pull) is desirable-more so than in the horizontal deflection amplifier, because the gain required of the vertical deflection amplifier is usually much higher than that of the horizontal amplifier, in order to obtain a uniform deflection field and reduce the effects of beam defocusing and pattern distortion.

Circuit Analysis.

General. The most versatile voltage deflection amplifiers are those used in the horizontal and vertical deflection circuits of high-quality test oscilloscopes. For this reason, the discussion that follows will be directed toward this application. In this way, circuitry peculiar to other applications will, in most cases, be included in this discussion as a matter of course.

A horizontal (voltage) deflection amplifier is designed to amplify the signals from a sweep generator, and apply the amplified (sawtooth waveform) signals to the horizontal deflection plates of an electrostatic deflection type of cathode-ray tube. The sawtooth sweep voltage is applied to the grid of the amplifier tube through a potentiometer, which affords control of the amplitude of the signal used as the horizontal time base. This control is normally front-panel mounted and captioned **HORIZONTAL AMPLITUDE**. In order to amplify a sawtooth waveform of voltage whose frequency may be (in a test oscilloscope) switch-selectable to a range which may include 10 Hz and 50 kHz as the low and high limits, respectively, the high frequency response must be maintained up to 350 kHz. The reason such high-frequency response is required is that, in order to reproduce a sawtooth waveform without appreciably distorting it, it is necessary to pass all frequencies up to the seventh harmonic of the fundamental frequency of the sawtooth wave. Thus, to pass a 50-kHz sawtooth wave, a minimum bandpass up to seven times this value is required.

A vertical (voltage) deflection amplifier is designed to amplify the input signals - often extremely minute in value - which are to be displayed on the cathode-ray tube screen. The waveform of the input signal may vary from one extreme - a direct current, or zero frequency - to the other extreme - a square wave whose fundamental frequency in itself is relatively high. In order to pass a signal of zero frequency, a direct-coupled amplifier is the only choice. In order to pass a square wave with reasonable fidelity, a bandpass is required that includes the tenth *odd* harmonic of the fundamental frequency, which is a frequency of 21 times the fundamental. Therefore, the over-all bandpass required of the vertical amplifier has an extremely wide range. High-frequency compensation is usually included in the circuit, in order to extend the high-frequency response to the limits required. The gain is usually adjustable by means of both "coarse" and "fine" controls. The coarse adjustment, when provided, usually consists of a set of resistance-capacitance networks designed to have various degrees of attenuation. The networks of resistors and capacitors are used to maintain the attenuation of any one network constant over a wide range of frequencies. The fine adjustment of vertical gain is usually a potentiometer, located in the grid circuit of some stage of amplification other than the first. Here,


it is isolated from the critical constants of the attenuation networks (which are located in the first stage), and does not vary the input impedance presented by the circuit to the signal source.

In small and inexpensive vertical deflection amplifiers, a single output tube is sometimes used. The output signal is coupled directly from the plate of this tube to one deflection plate of the CRT, while the other deflection plate is grounded. This is an unbalanced output, and has the following disadvantage: Each time the ungrounded deflection plate goes positive, on a peak of signal voltage, the average potential of the two vertical deflection plates rises to a considerable value above that of the second anode. This causes the electrons in the beam to be accelerated to a higher velocity than that imparted to them by the second anode potential. As a result, the trace brightens on positive peaks of the signal, and the beam is not deflected as much by a given increment of signal voltage because of the higher velocity. Negative peaks have an opposite effect, in that they reduce the average potential of the deflection plates, decelerating the beam to a lower velocity. As a result, the trace is reduced in brilliance on the negative peaks, and the sensitivity is increased because the beam is deflected more than it should be by a given increment of signal voltage. These effects may be eliminated by the use of a balanced, or push-pull, type of output circuit.

In both vertical and horizontal deflection amplifiers of better design, balanced or push-pull deflection is always used. In this type of circuit, signals that are equal in amplitude and opposite in polarity are applied to both deflection plates, neither of which is grounded. The positive side of the high-voltage power supply, which is connected to the accelerating anode of the cathode-ray tube, is grounded. These connections produce a minimum difference of potential between the accelerating anode and the deflection plates. As a result, two advantages are realized: First, the effect of the accelerating anode potential in distorting the deflection field is minimized, because of the fact that as one deflection plate is charged to a potential which is positive with respect to the accelerating anode (which is at ground potential), the opposite deflection plate is simultaneously charged to a potential which is an equal amount negative with respect to the accelerating anode. Under these conditions, a line of equal potential midway between the two charged plates is maintained at the same poten-

tial (ground) as that of the accelerating anode. This results in a minimum of beam defocusing and pattern distortion. The second advantage of the positive-grounded connection of the high-voltage power supply is that no high-voltage insulation is required between the accelerating anode and the deflection plates and their associated circuitry. In this respect the problems common to high-voltage circuitry, such as corona and high-voltage breakdown, are eliminated from the region of the cathode-ray tube which includes the neck, the flared portion, and the face (screen), as well as from the output circuits of the deflection amplifiers which feed the signals to the deflection plates. The high (negative) voltage is contained within a small portion of the tube neck at the base, wherein are located the filament and cathode, and the first anode.

Circuit Operation. The following schematics illustrate two common types of deflection amplifiers used for electrostatic deflection. The first shows a phase inverter used to obtain two output voltages, equal in amplitude and opposite in polarity, from a single-ended input signal. In this circuit, the input signal, which is shown as a positive pulse, is applied through a coupling capacitor, C1 to the grid of a triode amplifier, V1. The grid is returned to ground through grid resistor R1. The amplified output, which is a negative pulse due to phase inversion in the tube, is taken from the plate and applied, through coupling capacitor C3, to one of the vertical deflection plates of the cathode-ray tube, V3. The plate voltage is applied through plate load resistor R3 and potentiometer R4. The negative output pulse at the plate of V1 also appears across R3 and R4, which act as a voltage divider. A reduced value of the negative output pulse is taken from a tap on the voltage divider by means of potentiometer R4 and applied, through coupling capacitor C2 and resistor R6, to the grid of the phase inverter tube, V2. Resistor R2 serves as the grid return for this tube. The output at the plate of V2 is a positive pulse, the amplitude of which is exactly equal to (although of opposite polarity) the amplitude of the output of V1, *provided that* potentiometer R4 is properly adjusted to furnish the correct value of signal input voltage to the grid of V2. This positive pulse output of V2 is coupled, through C4, to the other vertical deflection plate of the cathode-ray tube, V3. In this manner, equal and opposite signals are applied to the two deflection plates, to provide a balanced deflection.

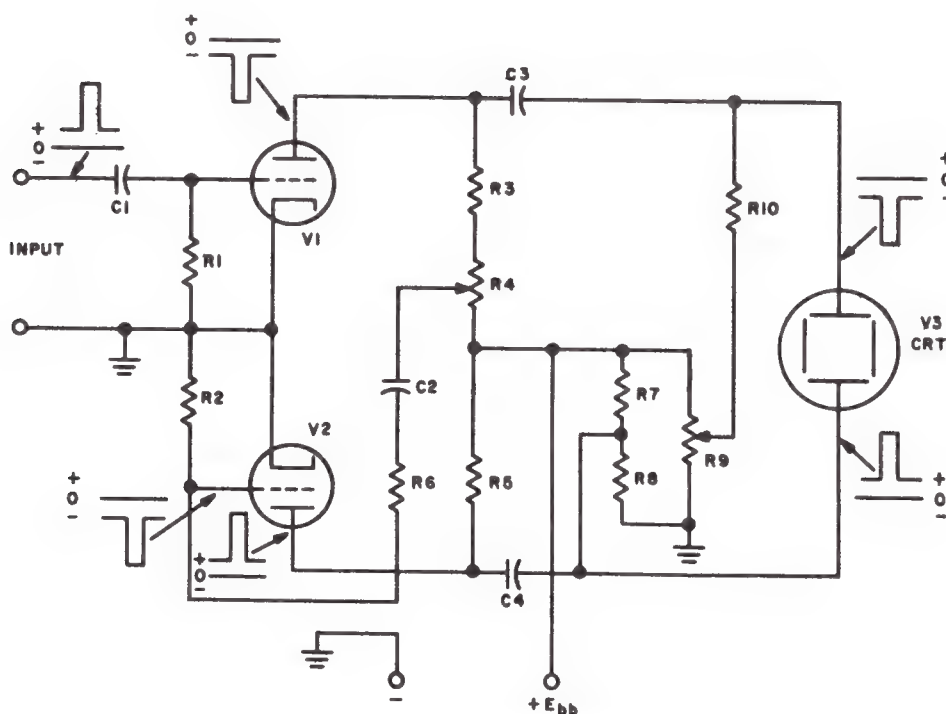


Typical Phase Inverter Used as Voltage
Deflection Amplifier

A shift circuit is usually included as part of a deflection amplifier for electrostatic deflection, by means of which the electron beam of the cathode-ray tube may be positioned in the exact center of the screen, or may be moved to any desired initial position under conditions of no input signal. Although the shift circuit is not, in a strict interpretation, actually part of the deflection amplifier (because the amplifier furnishes its output at the point of coupling to the CRT - at coupling capacitors C3 and C4 in the previous schematic), it is usually shown along with the amplifier circuitry in order to show the complete load circuit. In the illustration shown, the shift circuit is composed of equal resistors R7 and R8, isolation resistor R10, and potentiometer R9. The bottom deflection plate of cathode-ray tube V3 is fixed at a potential half-way between +250 volts and ground, by the voltage-divider action of resistors R7 and R8. When the adjustable arm of potentiometer R9 is set exactly half-way between the two ends of its resistance, the voltage at this point - which is furnished through isolation resistor R10 to the top deflection

plate - will be exactly equal to the voltage at the junction of R7 and R8. Hence, the fixed dc voltages applied to the top and bottom deflection plates will be equal, and the electron beam will be positioned midway between them. By adjusting the movable arm of potentiometer R9 away from its center position, the top plate of the CRT may be made positive or negative with respect to the bottom plate, thereby positioning the beam above or below the center position on the screen.

The second type of deflection amplifier used for electrostatic deflection is the paraphase amplifier, shown in the following illustration. In this type of circuit a balanced output is obtained from a single-ended input signal by means of common coupling in the cathode circuit of both tubes, which accounts for the circuit being known as a cathode-coupled paraphase amplifier. The input signal, again shown as a positive pulse, is applied through coupling capacitor C1 to the grid of triode amplifier V1, with the grid returned to ground through grid resistor R1. Cathode bias is obtained by means of cathode resistor R2,

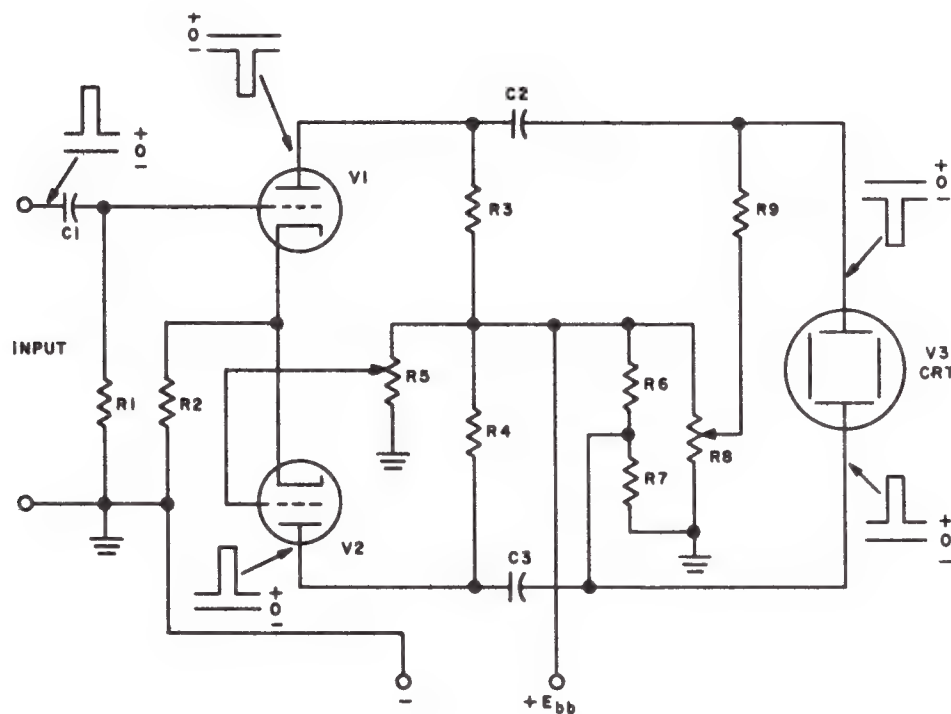

Typical Paraphase Amplifier Used as
Voltage Deflection Amplifier

which is common to both V1 and V2. Since R2 is unbypassed, the input signal at the grid of V1 also appears at the cathode, while the inverted signal appears at the plate as one output of the circuit. The signal at the cathode of V1 is applied, through direct connection, to the cathode of V2. The grid of V2 is connected to a balance potentiometer which acts as a voltage divider between E_{bb} and ground, to furnish the proper bias so that the output signal of V2 can be adjusted to equal that of V1. The positive pulse at the cathode of V2 will increase the bias, decrease the plate current, and produce a positive output at the plate of V2. The output signal at the plate of V2 is reversed in polarity from the input signal, as in any ordinary vacuum-tube amplifier. But, because the input to V2 is the signal voltage developed across cathode resistor R2, and because this signal is applied to the cathode of V2, which has its grid returned to ground through R5 and is thereby at ground potential insofar as the signal is concerned, the output signal at the plate of V2 has the same polarity as the input

signal at the cathode of V2 or the input signal at the grid of V1. In this way, the output signals from the plates of V1 and V2, which are applied to the deflection plates of the CRT, are equal in amplitude but opposite in polarity (phase). Resistors R5, R6, and R7 and potentiometer R8 comprise a shift circuit which allows the electron beam to be positioned on the screen of the cathode-ray tube as desired, in the same manner as described in the preceding typical phase inverter circuit.

The previous circuit operation and schematics have, for simplicity, omitted the additional compensation networks which are often included in specific applications. In order that deflection amplifiers do not restrict the bandwidth of the input signal, they must have wide frequency response, low distortion, and time delay proportional to frequency, similar to the characteristics of video amplifiers. Compensation circuits similar to those discussed under the paragraphs on Video Amplifier Circuits are used in

deflection amplifiers, depending upon the amplifier design and intended application.

Failure Analysis.

No Output. Assuming that a signal of proper amplitude (and polarity if the deflection amplifier is specifically designed for single-polarity pulse operation) is applied to the input terminals, a defective tube should first be suspected as the cause of a no-output condition. An open input coupling capacitor C1, a shorted grid resistor R1, or an open common cathode resistor R2 (refer to paraphase amplifier circuit diagram), or a failure of the power supply would individually be responsible for no output. An open plate resistor on the input side of the circuit (R3 in the illustrations) would also result in no output. Components peculiar to a specific circuit may also be cause of circuit failure. As an example, referring to the second illustration on a typical paraphase amplifier, if plate resistor R4 became shorted, the high value of plate current that would flow through V2 would of course flow through the common cathode resistor, R2. As a result, both cathodes would be at a high positive potential. The grid of V1 would therefore be highly negative with respect to its cathode, and might possibly be biased beyond cut off. No signal output would thereby be obtained.

Reduced or Unstable Output. In both of the typical circuits illustrated, a number of conditions could contribute to a reduced, distorted, or unstable output. The failure of out-of-phase amplifier tube V2, its plate resistor, or its output coupling capacitor, if open, would be responsible for an output of approximately one-half the normal amplitude. An open output coupling capacitor from the plate of V1 would also result in an output signal of one-half normal amplitude. A change in the value of input grid resistor R1 would change the input impedance to the stage; this might affect the amplitude and possibly the waveform of the input signal. An open-circuited positioning potentiometer or its associated resistor (R9, R10 in typical phase inverter circuit; R7, R8 in typical paraphase amplifier circuit) would prevent the positioning of the waveform display on the screen of the CRT in the normal manner. An open resistor in the voltage divider connected across the positioning potentiometer (R7 or R8 in the typical phase inverter circuit; R5 or R6 in the typical paraphase amplifier circuit) would also be responsible for the failure of the positioning potentiometer to properly position the waveform display on the CRT screen.

CURRENT DEFLECTION AMPLIFIER (FOR ELECTROMAGNETIC CRT (ELECTRON TUBE))

Application.

The current deflection amplifier is used to amplify input signals before they are applied (normally) to the vertical deflection coils of the deflection yoke used with an electromagnetic-deflection type of cathode-ray tube. In addition, it is used to amplify the sweep signals which are used as a time base before they are applied (normally) to the horizontal deflection coils of the deflection yoke used with an electromagnetic-deflection CRT.

Characteristics.

Horizontal Deflection Amplifier. Input impedance is high; loading of the preceding horizontal generator circuit is thereby prevented.

Input capacitance is low, attenuation of high frequencies is thereby prevented.

High-frequency response is very good: must be so to avoid the possibility of distorting the trapezoidal input waveform of voltage which is required to produce a sawtooth waveform of current through the horizontal deflection coils.

Low-frequency response is good, but does not include zero frequency.

Bandwidth depends on application design: may cover a range of 10 Hz to 100 kHz, but the range is usually more limited because the specific application normally requires only a few fixed sweep frequencies.

Output impedance is relatively low, and must be matched to the load (deflecting coil) for maximum transfer of current with minimum waveform distortion. This requirement acts to restrict the bandwidth.

Gain depends on application design: the current gain (power gain) is usually high, but the voltage gain may be low—even less than one.

Balanced output, furnished by a push-pull type circuit, is desirable, in order to obtain a uniform deflection field. However, the principal applications of the electromagnetic deflection type of cathode-ray tube, namely, radar and television, do not require the precise duplication of the input waveform that is essential in the principal applications of the electrostatic deflection CRT, namely, waveform analysis and complex wave amplitude measurement.

Vertical Deflection Amplifier. Input impedance is normally extremely high, in order to prevent any

waveform distortion due to loading effects on the circuit supplying the input signal. However, since any particular application of an electromagnetic deflection type of cathode-ray tube normally operates with a permanently connected input circuit, the input impedance of the amplifier may be of a fairly low value, which must be matched to the source impedance of the input signal.

Input capacitance is low, in order to prevent the attenuation of high frequencies.

High-frequency response is very good: must be so in order to respond to extremely sharp input pulses without introducing appreciable time delay.

Low-frequency response is good, but does not include zero frequency.

Bandwidth depends on application design: may cover a range of 10 Hz to 100 kHz, but the range may be more limited when only the leading edge and the length of an input pulse, and not the shape of the top of the pulse, is of consequence, as in pulse display applications (radar).

Output impedance is relatively low, and must be matched to the load (deflecting coil) for maximum current transfer with minimum waveform distortion.

Gain depends on application design: the current gain (power gain) is high, but the voltage gain may be low.

Balanced (push-pull) output is desirable, both from the standpoint of the high power output with minimum distortion required for magnetic deflection, and the need for an absolute minimum of beam defocusing when pinpoint radar target presentation is required.


Circuit Analysis.

General. The deflection of the electron beam in an electromagnetic deflection type of cathode-ray tube is proportional to the strength of the magnetic field set up within the tube, which is in turn proportional to the value of current passing through the deflection coil. Since it is desirable to deflect the electron beam linearly, the current through the coil must increase linearly with time. When the end of the sweep is reached, the electron beam must be returned to its starting point quickly. The current wave required for electromagnetic deflection must therefore be of sawtooth shape if the resultant sweep is to be linear. It should be observed that it is the *current* wave which must be of sawtooth shape for an electromagnetic

tube, not the *voltage* wave as in an electrostatic tube.

The deflection coils, through which the deflection amplifier output current flows, consist of wire wound around either a non-magnetic core or an iron core. The wire used in the coil has, in addition to the desired inductance, some amount of resistance. As a result, the sawtooth current must flow through the equivalent of a series resistive-inductive (R-L) circuit. Since a square wave of voltage will produce a sawtooth wave of current in a pure inductance, while a sawtooth wave of voltage will produce a sawtooth wave of current in a pure resistance, the combination of a square wave and a sawtooth wave of voltage is required to produce a sawtooth wave of current in a circuit containing both resistance and inductance. Such a combined waveform has the shape of a trapezoidal waveform of voltage. This, then, is the waveform which must be amplified by the current deflection amplifier.


Circuit Operation. The accompanying schematic illustrates a simplified typical deflection amplifier for producing a horizontal time base using magnetic deflection. The input signal, which is a trapezoidal waveform of voltage as shown in the illustration, is applied through coupling capacitor C1 to the grid of pentode amplifier V1. The amplifier is operated as a Class A stage, with fixed bias applied from a negative power source. Sufficient bias is applied to the grid, through grid resistor R1, to prevent the grid from going positive with maximum signal input. The amplifier tube, V1, is a pentode or a beam power type, in order to obtain the power amplification that is required to furnish sufficient current to the deflection coil. This coil may require between 50 to 100 milliamperes of current for maximum beam deflection. The output of V1 is applied to the deflection coil, which in the illustration is presented by an inductance, L1, with a resistance, R2, in series with it, shown as a dotted resistance because it is actually a part of L1. The output voltage waveform at the plate of V1 is trapezoidal. When this waveform is applied to the series R-L circuit (deflection coil), the voltage waveform appearing across the resistance is resolved to a sawtooth shape, while that appearing across the inductance is resolved to a square-wave shape. The square wave of voltage across the inductance causes a sawtooth wave of current through it, which is the required waveform for producing a horizontal time base deflection on the screen of the cathode-ray tube.

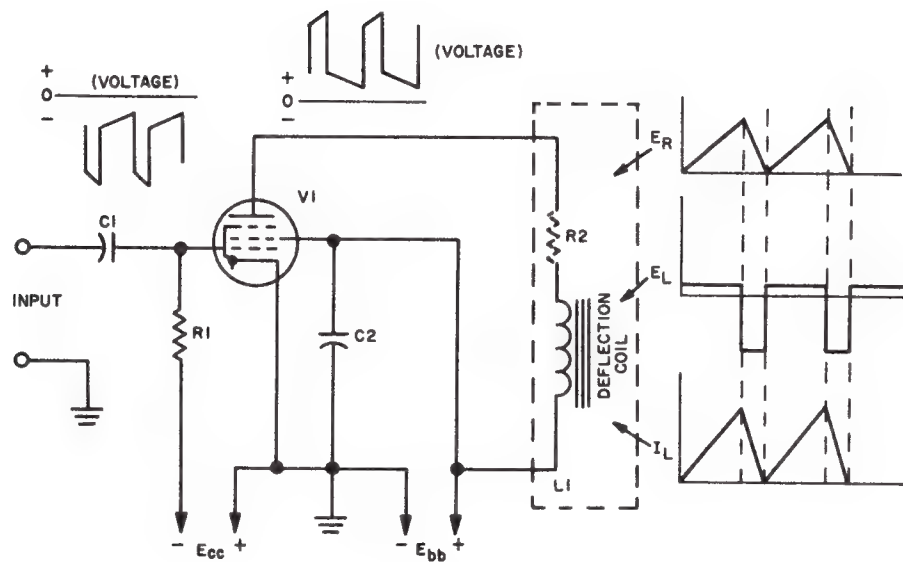

Typical Current (Electromagnetic)
Deflection Amplifier

The development of the sawtooth current waveform from the trapezoidal voltage input waveform is shown in the following illustration. The trapezoidal voltage input waveform to the grid of amplifier V1 is shown at A; differentiated voltage which appears across the

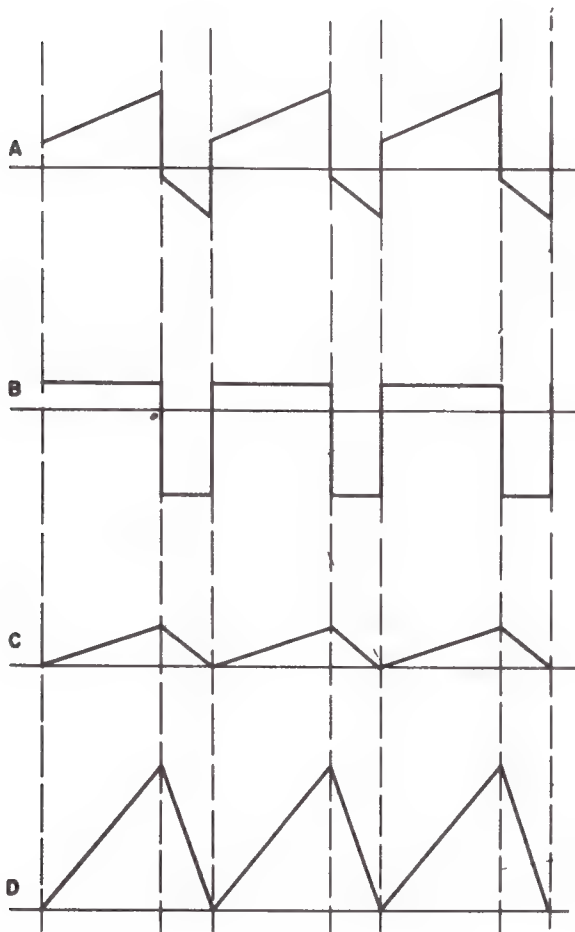
inductance is shown at B; the integrated voltage which appears across the resistance (of the coil) is shown at C; the current through the deflection coil, which is the composite result of waveforms B plus C, is shown at D.



Development of Sawtooth Current Waveform in Deflection Coil from the Trapezoidal Voltage Waveform Input to Amplifier


A second circuit for producing a horizontal time base for magnetic deflection is shown in the following illustration. The input signal to this amplifier is a square wave, instead of the trapezoidal wave required in the previous circuit. This signal is applied, through coupling capacitor C1, to the grid of a pentode or beam power amplifier, V1. The grid is returned to ground through resistor R1. The positive voltage applied to the cathode of V1, from the plate supply by means of the voltage-divider action of resistor R3 and cathode resistor R2, maintains V1 biased to cut-off in the absence of an input signal. When the first positive pulse of the input square wave reaches the

grid, the tube conducts heavily. The resulting plate current, flowing through deflection coil L2 and inductor L1, rises exponentially toward a value which would be limited only by the resistance of the circuit. Before this limiting point is reached, however, conduction of the tube is suddenly interrupted by the negative-going end of the square-wave input pulse. In this way, only a relatively linear portion of the exponentially rising waveform is utilized. When the conduction of the tube is interrupted at the end of the positive square wave, V1 is cut off, and the current decays rapidly to zero. This rapid decay is due to a change in the time constant of the circuit between the rise and fall of the current. During the rise of current, the circuit time constant (which is given as inductance divided by resistance, or L/R) is long, because of the large value of inductive reactance (due to the large inductance) and the small value of resistance in the circuit. The resistance is composed of cathode resistor R2 and the low value of plate resistance of V1. During the decay of current, the time constant is made short, as a result of the increase in the value of plate resistance when V1 stops conducting. With the shortened time constant, the current decays rapidly. The additional value of inductance in the circuit due to inductor L1 increases the time constant, to produce a slow build-up of current. Inductor L1 may be effectively removed from the circuit, by shorting across it, when faster sweep deflection rates are required.

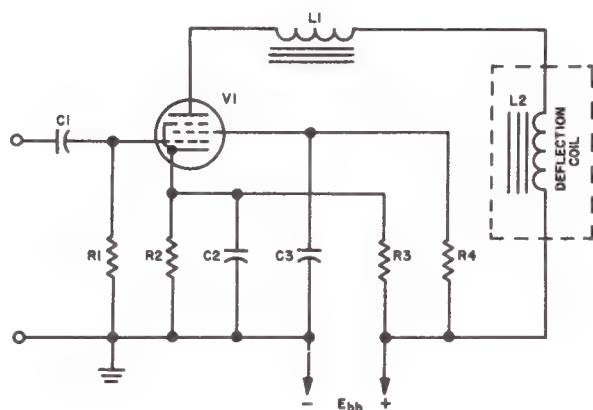

Current (Electromagnetic) Deflection Amplifier Utilizing Square-Wave Input


The sudden decay in current flowing in the deflection coils, when the tube stops conducting, causes a counter e.m.f. to be produced in the coil which opposes the current decay. In addition, the circuit may be shock-excited into oscillation by the sudden change in value of current. Although the oscillations gradually die out, they may continue into the following sweep, especially if the circuit Q is high. This condition may result in a nonlinear start of the build-up of current in the coil, and therefore a nonlinear sweep, as shown in the following illustration.

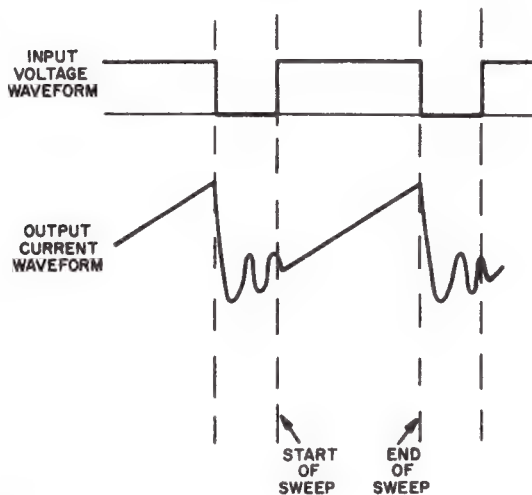

Undamped Oscillations in Deflection Coil Current

These oscillations may be eliminated, or damped out, by lowering the Q of the circuit by means of a resistor shunted across the coil. However, this wastes some of the deflection current; a more satisfactory method incorporates the use of a damping diode shunted across the deflection coil, as shown in the following illustration. In this circuit, diode $V2$ acts to damp out the oscillations in the following manner: When the current through $V1$ is increasing (during the rise of the sawtooth, current wave shown in the illustration above) to provide the sweep deflection, the voltage at the plate of $V1$ is lower than the plate supply voltage by the amount of voltage drop in the deflection coil and inductor. The cathode of damping diode $V2$ is therefore more positive than its plate, and the diode will not conduct. When the current through $V1$ falls to zero (at the end of the sawtooth current wave illustrated), the voltage at the plate tends to rise above the plate supply voltage due to the fact that the counter e.m.f. generated by the inductance adds

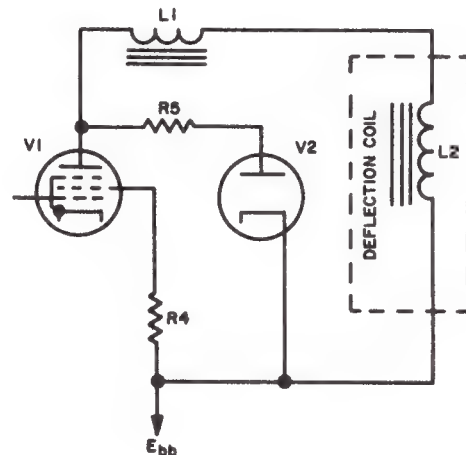to the plate supply voltage. When this condition is reached, damping diode $V2$ conducts, and any oscillations are dissipated in resistor $R5$.



Deflection Amplifier Output Circuit With Damping Diode Added

Balanced output (push-pull) circuits, when used, usually operate by means of a phase inverter circuit fed from a single-ended source, as described in the previous circuit on Voltage Deflection Amplifiers. In some cases in radar deflection circuitry, the two outputs obtained by means of a phase inverter are separately amplified by individual single-ended deflection amplifiers, and then applied to the two separate windings of a split-winding deflection yoke.

Failure Analysis.

No Output. Assuming that a signal of proper amplitude and waveform (square wave or trapezoidal wave, depending on circuit design) is applied to the input terminals, a defective tube would be the most likely cause of a no-output condition. If the tube is found capable of operation, an open input coupling capacitor $C1$ or open grid resistor $R1$, or open cathode or screen resistors, if used, may be the cause of no output. Since a current-deflection amplifier is characterized by a relatively high value of plate-current flow, a common source of trouble is an open deflection coil. If the coil is open-circuited, and the circuit is similar to those previously shown under Circuit Operation, the application of screen voltage to

the tube with no plate voltage present may result in a burned out tube or poor emission, because of excessive screen current. The same condition may prevail if the deflection coil is remotely located from the amplifier, and the interconnecting cable is inadvertently disconnected during operation. No output may also be due to failure of the plate-voltage supply.

Reduced or Unstable Output. A change in value of almost any of the circuit components, due to age or partial failure, may contribute to a reduced output. If the capacitance of input coupling capacitor C1 changed or the resistance of grid resistor R1 changed, the output would be affected. If the cathode bypass

capacitor (if one is used) became either open or shorted, the bias would be changed, resulting in either decreased output due to degeneration (if open) or distortion due to no bias (if shorted). If the circuit incorporates fixed cathode bias obtained through a voltage divider from the E_{bb} line, an open resistor on the E_{bb} side of the cathode (R3 in the second circuit illustrated) would interrupt the fixed bias, and the circuit would operate with self-bias, which may produce distortion under high signal input conditions. A decrease in the voltage of the plate supply, due to faulty operation, would also be responsible for a reduced output.

PART 5-9. OPERATIONAL AMPLIFIERS**OPERATIONAL AMPLIFIERS****General.**

The operational amplifier is a high-gain dc amplifier utilizing negative feedback to establish and control precise gain. An operational amplifier may be used to perform mathematical operations such as addition, subtraction, multiplication, and division, or to provide special waveforms or voltages. This type of amplifier is used especially for analog computation and instrumentation, and in special systems design. Analog computation differs from logic computation in the manner in which it is accomplished. The information applied to a digital computer is separated into and handled in discrete measurable steps (digits), whereas the information applied to an analog computer is usually slowly varying ac or dc voltages. For example, a sawtooth voltage could easily represent the acceleration of an airplane. The slope of the sawtooth could represent the magnitude of the acceleration; the starting level of the slope could represent the initial velocity, and the final level of the slope could represent the final velocity of the airplane. Thus, complex analog problems are solved by operational amplifiers, using resistive input and output networks and high-gain dc amplifiers.

Operational amplifiers are named for their function. For example, the summing amplifier produces an output voltage that is proportional or equal to the sum of the inputs. A difference amplifier acts as a subtractor, producing an output equal to the difference between the input voltages. Similarly, the exponential amplifier produces an exponential output, and the derivative amplifier produces the desired derivative. The logarithmic amplifier, in turn, produces a logarithmic output. Each of these mathematical types of operational amplifiers is fully discussed later in this section. The combining and

coincidence amplifiers are considered as special non-mathematical operational circuits.

COMBINING AMPLIFIER (ELECTRON TUBE)**Application.**

Combining amplifiers are used in transmitter modulation stages, or in combining circuits of television transmitters, where it is necessary to combine two or more signals to obtain an output proportional to each input.

Characteristics.


- Uses a common plate load resistor.
- Has two or more inputs.
- Uses a separate amplifier for each input.
- May be dc coupled or capacitively coupled.
- Uses triode electron tubes.
- Uses cathode bias.

Circuit Analysis.

General. The combining amplifier produces an output which is the result of two or more input signals not necessarily of the same shape, phase, or frequency. Each input signal is applied directly to the grid of a separate electron-tube amplifier through a resistive voltage-divider network. The amplified output of each tube is developed across a common plate-load resistor, resulting in an overall output which is the combination of all input signals.

Circuit Operation. A schematic of a typical combining circuit is shown in the accompanying illustration. Potentiometer R1 and resistor R2 form a voltage driver which couples an input signal to the grid of triode V1. Potentiometer R4 and resistor R5 form a voltage divider which couples an input signal to the grid of triode V2. Resistor R3 is the cathode bias resistor for V1, and capacitor C1 is the cathode bypass capacitor. Resistor R6 is the cathode bias resistor for triode V2 and capacitor C2 is the cathode

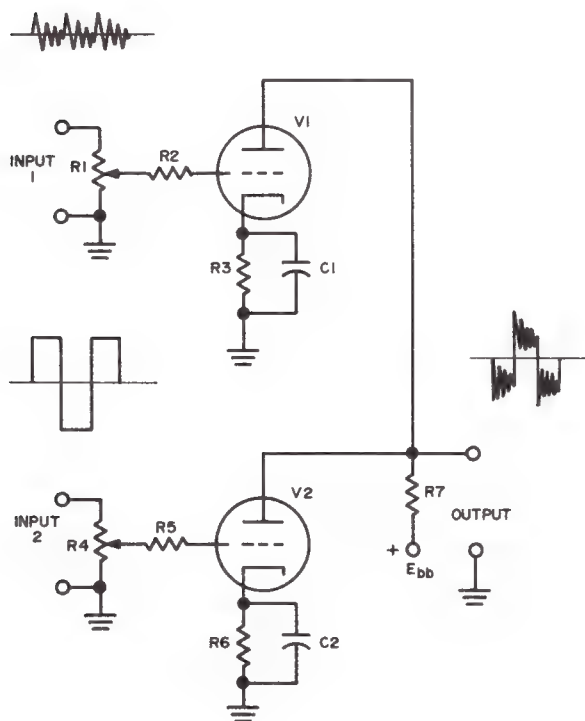bypass capacitor. Resistor R7 is the common plate-load resistor used by both V1 and V2.



Combining Amplifier

The amplitude of the input signal applied to the grid of V1 is determined by the setting of potentiometer R1, and the input signal applied to V2 is, likewise, determined by the setting of potentiometer R4. By using R2 in series with the grid of V1, and R5 in series with the grid of V2, the grid circuits are effectively held at a high impedance, and the shunting effect of R1 and R4 on the respective grid input circuit is minimized. At the same time, overdriving of the grids is limited, since any grid current flow through R2 or R5 will develop an opposing negative bias and reduce the drive.

Normally both tubes are biased so that they are operating at approximately the same plate current. Thus, equal changes of grid voltage produce equal plate current variations and maintain a linear input-output relationship. When the grid of V1 is driven in a positive direction, plate current will increase and produce a negative swing across load resistor R7.

Since R7 is common to both tubes, if the grid of V2 is also driven positive at the same time as V1, the total plate current will be equivalent to the combination of both input signals at that instant. In this example, the circuit is acting as an adder. On the other hand, if one input is decreasing while the other input is increasing, the total plate current and voltage swing across R7 will represent the difference between the two signals.

Since the output voltage is developed by the separate plate currents of V1 and V2 flowing through a common load resistor, the output waveform at any instant is the combination of the two input signals. Hence, applying a sawtooth waveform to one input, and a rectangular waveform to the other input, will produce an output waveform which contains both sawtooth and rectangular signal components, and will be the composite waveform produced by both signals. Because of the normal phase inversion or polarity change produced by the tube amplifier, the combined output will be out-of-phase with respect to the input. Where an output of the same phase or polarity as the input is desired, an additional stage of linear application will be required. The combining circuit is used when it is desired to combine the outputs of two separate channels to control a third channel.

Failure Analysis.

No Output. Loss of output can result from a defective plate supply voltage source, E_{bb} , or if resistor R7 is shorted or open. Loss of output can also occur if a failure exists in each of the individual amplifiers. Both triodes V1 and V2 can be defective, both cathode bias resistors or both grid resistors can be open, or both input potentiometers may be open.

Output voltage can not be developed if plate load resistor R7 is open or shorted. If the plate supply voltage source is defective, triodes V1 and V2 will not be supplied with either plate voltage or plate current to develop an output.

If plate load resistor R7 and the plate supply voltage source are not defective, there must be a defective component in both amplifier circuits. Consider first the circuitry associated with electron tube V1; if the correct signal voltage is present at the grid of V1 and no output is obtained from V1, cathode bias resistor R3 may be open, or tube V1 itself may be defective. If potentiometer R1 is defective, no signal will appear at the grid of V1 and no output will be obtained from this stage. By the same reasoning, if resistor R4 is

open, no signal will appear at the grid of V2, and no output will be obtained from V2.

An open grid resistor R5 or cathode resistor R6 will prevent an output signal from being obtained from V2. If the proper signals and proper voltages are available on the elements of V2, but no output is developed, the electron tube is probably defective.

Low or Distorted Output. A low or distorted output will be developed if the plate supply voltage is not the proper value, or if plate load resistor R7 is not the correct value. If either or both bypass capacitors C1 and C2 are defective, or cathode resistors R3 or R6 are shorted, the output may be distorted. Defective electron tubes may also be at fault.

A lower than normal plate supply voltage or improper bias will cause the triodes to be operated over the nonlinear portion of their plate current-grid voltage characteristic curve. This will result in distortion of the output waveform. Shorted grid resistors R2 or R5 will allow a greater signal amplitude to appear at the grid of V1 or V2. This may drive the tube into saturation.

If one of the tubes is weaker than the other, a low output will be obtained, even though the voltages and parts of each amplifier stage test normal.

COMBINING AMPLIFIER (SEMICONDUCTOR)

Application.

Combining amplifiers are used to provide a single output which is equal to the combination of two or more input signals not necessarily of the same wave-shape or frequency. The combining amplifier is used in transmitter modulator stages or in the combining circuits of television transmitters.

Characteristics.

Two transistor amplifiers are connected provide a common output.

Output signal is developed across a common load resistor.


Two or more simultaneous inputs are necessary.

Circuit Analysis.

General. Two or more input signals not necessarily of the same shape, phase, or frequency, are combined to produce an output which is the result of these signals. Each input signal is applied directly to the base of individually grounded emitter PNP transistor

amplifiers. The output of each amplifier is developed across a common collector resistor. The resulting output is then the combination of all input signals.

Circuit Operation. A typical schematic of a combining amplifier using the common-emitter arrangement is shown in the accompanying illustration. In the circuit, Q1 and Q2 are two identical PNP type transistors. The output impedance of the preceding stage is used to develop forward base bias for Q1 and Q2. The emitters of both transistors are grounded, and the collectors of both transistors are connected to the same end of common load resistor R1.

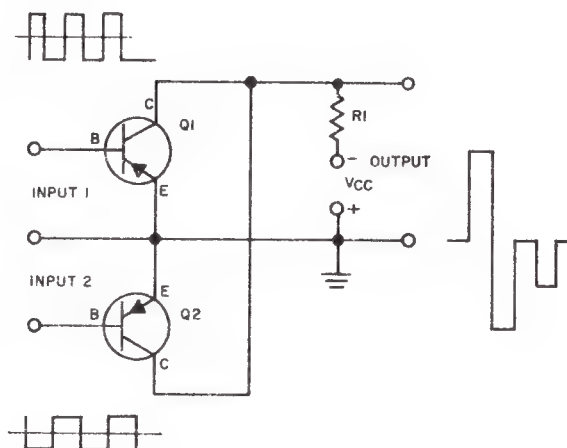


Combining Amplifier

Assume that a positive-going rectangular input waveform is applied to the base of Q1, and a negative rectangular input waveform of one half the frequency, but with the same amplitude as the input to Q1, is applied to the base of Q2. The output which is produced across the collector load resistor contains the amplified resultant voltages of the two waveforms.

For ease of circuit explanation refer to the accompanying input and output waveform chart. At time t_0 , both transistors have equal forward bias and no input voltage applied, and are in their quiescent or resting condition. At this time, the total of both collector currents produces a positive voltage drop across common load resistor R1, and reduces the collector voltage applied to Q1 and Q2 to its normal resting value. At time t_1 , the positive-going leading edge of the pulse applied to the base of Q1 drives it

more positive and reduces the forward bias. The collector current of Q1 is correspondingly reduced, and the collector voltage tries to rise toward the negative supply value. At the same time, the negative leading edge of the input pulse applied to Q2 increases the forward bias, and the collector current of Q2 increases. Assuming equal amplitude inputs and matched transistors, the opposing changes in collector current through common collector resistor R1 balance each other out, so there is no effective change in current flow and voltage across R1. This condition occurs continuously from time t_1 to time t_2 . During this time, the output remains at its normal resting level as shown in the waveform chart.

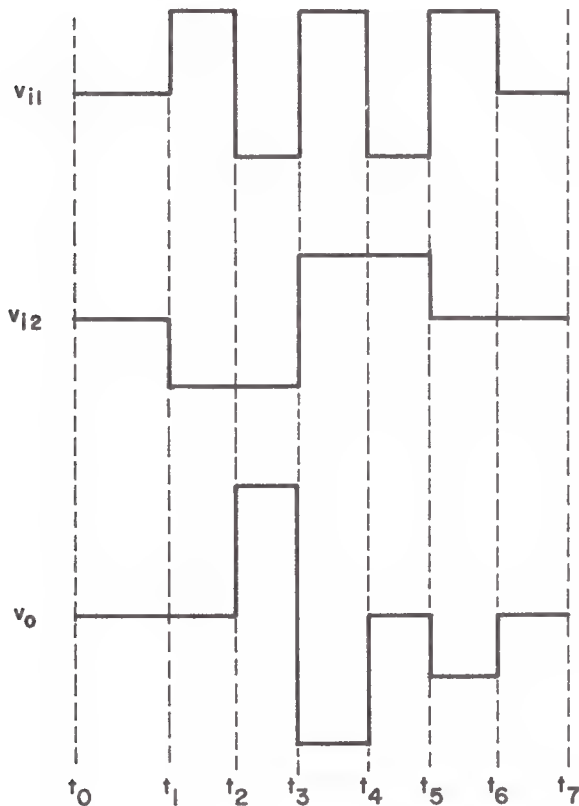

Input and Output Waveform Relationships

At time t_2 , the input pulse on Q1 reaches its trailing edge, driving the base of Q1 in a negative direction and increasing the forward bias. The collector current of Q1 now increases, and adds to the col-

lector current drawn by Q2 which still has a negative pulse (forward bias) applied. With twice the normal collector current flowing through R1, the total collector voltage is decreased, and a positive-going output spike of voltage is produced. This positive output voltage continues for the duration of the negative portion of both input pulses from time t_2 to time t_3 .

At time t_3 , both input pulses end and the trailing edges both drive the bases of Q1 and Q2 positive, reducing the forward bias on both transistors. Consequently, the collector current of Q1 and Q2 flowing through R1 is reduced to twice the normal value, producing a negative-going output voltage swing as the collector voltage rises toward the supply value. This negative output voltage continues during the steady-state condition of the input pulses between times t_3 and t_4 . At time t_4 , the trailing edge of Q1 input pulse drives the base of Q1 negative, increasing the forward bias. The collector current of Q1 increases, and the output voltage tends to rise in a positive direction as the collector voltage of Q1 decreases. However, the positive pulse applied to Q2 base still continues to keep the forward bias reduced, dropping the collector current of Q1. At this time, the increase of collector current through Q1 exactly balances out the decrease of collector current through Q2, and the opposing currents cancel so that no output is produced. Thus, the total output voltage returns to its normal resting value (the zero output level) between times t_4 and t_5 (the input voltages are again canceling each other in the output). At time t_5 , the positive pulse applied to Q2 ends, and the trailing edge of the pulse drives Q2 base in a negative direction until the collector current of Q2 is returned to its normal resting value. At the same time, the leading edge of the input pulse applied to the base of Q1 drives the base positive, reduces forward bias, and reduces Q2 collector current. During the interval from t_5 to t_6 , Q2 collector current remains at the resting value, and Q1 collector current is less than normal. Thus, the collector voltage of Q1 increases negatively toward the supply value. Because Q2 is resting in its quiescent condition and only the current in Q1 is reduced, the negative output voltage is only half the amplitude produced when both transistors are operating. At time t_6 , the positive input pulse on Q1 base ends, and the negative trailing edge of the pulse increases the forward base bias and returns Q1 to its normal forward-biased condition. Hence, normal collector current of Q1 occurs, and, since no

input pulse is applied to Q2, both transistors rest in the quiescent condition, effectively producing no output. At time t_7 , if the pulses are continued, the cycle of operation described above repeats.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of multiplier resistance employed on the low-voltage ranges of conventional volt-ohmmeters. Be careful also to observe proper polarity when checking continuity, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. No output may be the result of defective supply voltage, a defective output resistor, or a defective transistor. With no collector voltage available for either transistor, no output can be produced. This lack of collector voltage may be the result of a faulty collector supply voltage source (V_{CC}), or a shorted or open collector resistor R1. If neither V_{CC} nor R1 is defective, both Q1 and Q2 must be defective in order to produce no output.

Low and Distorted Output. Since there are only four components which make up this circuit, and two of them (R1 and V_{CC}) would not produce an output if either were defective, a low and distorted output will result if either Q1 or Q2 is defective. In this case, the output of the good transistor alone would produce the total output voltage of the circuit, and no combining action would occur.

COINCIDENCE AMPLIFIER (ELECTRON TUBE)

Application.

The coincidence amplifier is mainly used in analog and digital computers. It is used to control the repetition frequency and pulse duration of a given signal by producing an output only when two simultaneous input signals are present.

Characteristics.

Requires a multigrid type of tube such as a pentode.

Simultaneous inputs are applied to the control grid and the suppressor grid.


Tube is normally held at plate current cutoff by a large negative bias voltage.

A clipping circuit within the amplifier clamps the output to a constant amplitude.

Circuit Analysis.

General. The coincidence amplifier uses a pentode operated below plate current cutoff. An input signal applied to the control grid does not drive the tube above cutoff unless another signal is applied to the suppressor grid at the same time. When both signals are present, the tube conducts and the output is held at a constant level by a clipping circuit within the amplifier. In effect, the coincidence amplifier functions as a gated amplifier, which only operates when switched on by simultaneous input signals.

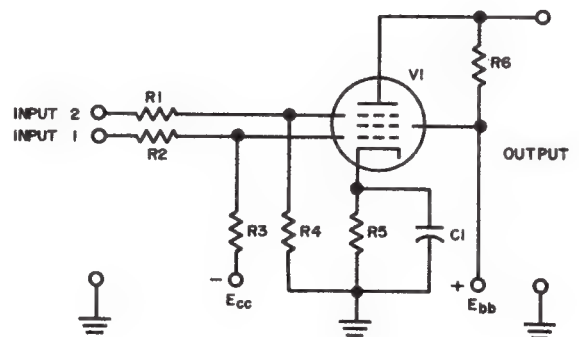Circuit Operation. The schematic of a coincidence amplifier is shown in the accompanying illustration. Input signals are applied to the suppressor and control grids of pentode V1 through resistors R1 and R2. Resistor R5 is the cathode-biasing resistor, and capacitor C1 is the cathode bypass capacitor.




Coincidence Amplifier

Resistor R4 is a clamping resistor, which limits the output to a certain level. The highly negative bias voltage (E_{CC}) is applied to the control grid of V1 through isolating resistor R3. The screen grid and plate of V1 are furnished with positive dc supply voltage from a common source. Plate load resistor R6 drops the plate voltage to a lower positive value than the screen grid supply voltage. The output voltage is obtained between the plate of V1 and ground, developed by plate current flow through R6.

The primary input signal (input-1) is applied to the control grid of V1 through resistor R2. This voltage can not by itself raise the tube grid out of the cutoff

region. The output voltage thus remains at a value slightly less the plate supply voltage. The second input signal (input-2) provides a large positive gating potential on the suppressor grid and overcomes the fixed negative grid bias. When the primary input signal occurs at the same time that the second input signal is applied to the suppressor grid, the pentode conducts.

As shown in the following illustration, an output will be present only at those times when both input no. 1 and input no. 2 are positive at the same time (in coincidence). As the conduction and plate current through R6 increases, the plate voltage decreases by the drop across R6. Plate current is prevented from increasing above a certain level by a suppressor grid-to-cathode feedback voltage. This voltage is developed across resistor R4 when the peak input to the suppressor is large enough to cause the suppressor grid to draw current. (Electron flow from the cathode to the suppressor grid of V1 and ground through R4 develops a negative voltage, which opposes the applied suppressor signal voltage.) The flow of suppressor current also causes the cathode to become more positive, thus increasing the cathode bias voltage and retarding tube conduction. The amplitude of the plate output voltages is then held constant by the combined effect of the retarding suppressor and cathode bias voltages, regardless of the amplitude of the input pulses.

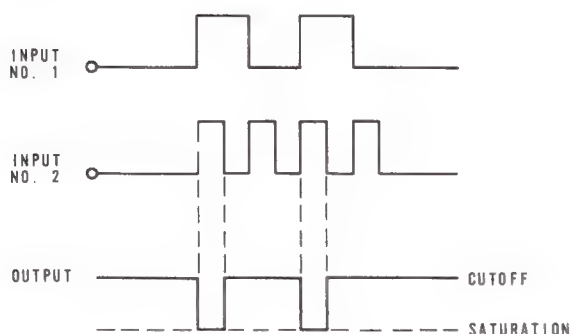

Failure Analysis.

No Output. Lack of filament supply, screen grid or plate supply voltage, a defective electron tube, an open input or output circuit, as well as improper bias, can produce a no-output condition.

A lack of plate voltage, measured between plate and ground, can be caused by open plate load resistor R6. In this case, the screen grid will also glow red, due to an overload, since the electron flow is attracted to the screen. If there is no plate or screen voltage, the plate supply voltage source is probably defective.

When no output exists, but there is a higher than normal plate voltage, plate load resistor R6 may be shorted or tube V1 may be defective.

An open cathode circuit will result if cathode resistor R5 is open. Check the resistance of R5. No filament voltage will also cause a loss of output. This condition can result from a defective filament supply source or defective tube.

An open control gain or screen grid resistor (R1 or R2) will prevent a signal from being applied to the suppressor grid or control grid. Check R1 and R2.

If none of the components is open or shorted and voltages present on the elements of the electron tube are of the proper value, pentode V1 is probably defective.

Low or Distorted Output. Defective grid, bias or plate supply resistors, or an open or shorted cathode capacitor C1 can cause low or distorted output voltage.

An improper voltage on the control grid of V1 indicates that control grid resistor R2 may be open, or that biasing resistor R3 may be open or shorted. A shorted suppressor grid resistor, R1, or an open or shorted clamping resistor, R4, will be indicated by improper voltage on the suppressor grid of V1. If R1 were shorted, only the output would be lowered, but if R4 were shorted, the output would not be clamped at a specific level, and would depend on the input level.

The cathode V1 may measure an incorrect potential because cathode biasing resistor R5 is defective, or because cathode bypass capacitor C1 is open or shorted. A shorted bypass capacitor is indicated by

no voltage at the cathode. An open cathode resistor will usually indicate above normal voltage, since the meter multiplier will act as the cathode resistor.

DERIVATIVE AMPLIFIER (ELECTRON TUBE)

Application.

The derivative or differentiation amplifier is used in analog computers and control circuits to develop an output voltage which varies negatively as the derivative of the amplified input voltage.

Characteristics.

Has a low input and low output impedance.

Uses a capacitive input network.

Uses negative feedback.


Operation of the amplifier is based on resistance-capacitance time constant relationship.

Output is 180° out of phase with input.

Circuit Analysis.

General. The derivative amplifier develops an output which is the differentiated value of the input voltage. This output is developed by the relationship between the input capacitor and a feedback resistor of a triode operational amplifier. The r - c time constant, which determines the exponential decrease of current, is the product of the capacitor and the feedback resistor. The exponentially varying current flows through the capacitor, the triode, and the feedback resistor. This current value times the feedback resistor value equals the output voltage value at any given time. The output voltage, then, varies exponentially as the current varies.


Circuit Operation. The one-line diagram of a derivative amplifier is shown in the accompanying illustration. It shows a derivative amplifier in simplified form. The triangle represents the basic operational amplifier circuitry, so that only a capacitive input and a resistive feedback network are needed to complete the functional diagram of the derivative amplifier. This type of diagram makes it easy to recognize the circuit function, particularly in complex illustrations where many operational amplifiers are used.

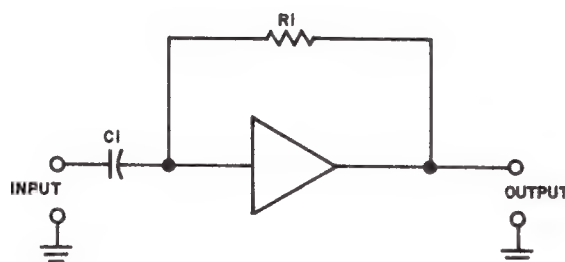

Derivative Amplifier

The schematic of a derivative amplifier is shown in the accompanying illustration. Capacitor C1 is an input capacitor which couples the input signal to the grid of triode V1.

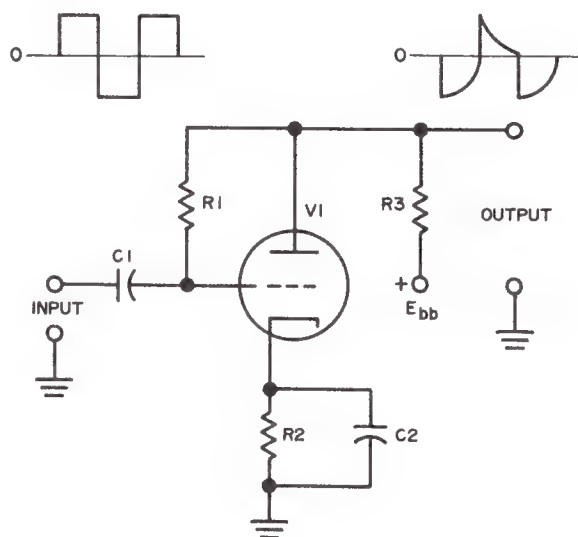Together with feedback resistor R1, C1 forms an R - C time constant network which determines the output waveform at any given time. Resistor R2 and bypass capacitor C2 form the cathode-biasing network for triode V1. Resistor R3 is the plate load resistor from which the output is taken.



Derivate Amplifier Schematic Diagram

When a positive-going pulse input signal is applied to the grid of V1 through capacitor C1, the grid of V1 is driven positive. This causes maximum plate current flow, which develops a maximum negative output, and the current through feedback resistor R1 is also at a maximum. The large feedback current through R1 produces a voltage drop across R1, which slightly decreases the total input voltage. Capacitor C1 charges at a rate determined by the time constant of C1 and R1. The voltage applied to the grid of V1 then decreases at the rate that C1 charges. Plate conduction is decreased by an amount proportional to the decrease in grid signal voltage, and the positive-going output voltage increase is proportional to the decrease in plate current. The resulting output voltage varies directly with the charge on capacitor C1. This output voltage is the negative derivative of the positive input voltage. The charging of C1 during the flat top portion of the input signal continues until the input signal abruptly switches polarity. The negative-going input signal now causes the charge on capacitor C1 to discharge abruptly. The full negative input voltage swing now is applied to the grid of V1 and triode V1 is driven into cutoff. The internal resistance of V1 is now greater than the resistance of R1, permitting the capacitive discharge to flow directly through R1 to the output. At this point, the positive output voltage reaches a maximum positive value. Once discharged, capacitor C1 again charges through resistor R1 at a rate equal to the value of capacitor C1 times resistor R1. As the capacitor charges in a positive direction, the grid of V1 becomes more positive, and rises above cutoff. This causes plate current to flow, and produces a decreased plate output voltage (negative swing), at the rate that capacitor C1 charges. The decreasing positive output voltage represents the negative derivative of the negative input signal.

Failure Analysis.

No Output. A defective electron tube, an open input or output circuit, an open biasing network, or a defective plate supply voltage can result in loss of output voltage.

The input signal can not be applied to the grid of V1 if capacitor C1 is open. If cathode-biasing resistor R2 is open-circuited, the output and tube current flow will be prevented. An open plate load resistor, R3, will prevent plate voltage from being applied to the plate of V1. Similarly, if R3 were short circuited, no output voltage variations could be developed. With

a defective plate supply voltage source, no voltage would be available for the plate of V1. If no output occurs, and the proper potentials appear at the electron tube elements, electron tube V1 is probably defective.

Low or Distorted Output. A shorted input, a defective feedback network, a defective triode V1, or a diminished plate supply voltage value can cause the output to be low or distorted.

A diminished plate supply voltage will cause low plate voltage and the output to be lower than normal. If capacitor C1 is shorted, no charging action will occur, resulting in an output which is not the derivative of the input. A shorted or open feedback resistor R1 will cause the same effect as a shorted input capacitor. If cathode biasing resistor R2 is defective, V1 will be improperly biased and a lower, or higher, than normal plate current will produce an improper output.

If cathode bias capacitor C2 is shorted, it will produce an abnormally large and distorted output. An open capacitor will produce degenerative feedback, and a reduced output will occur.

DERIVATIVE AMPLIFIER (SEMICONDUCTOR)

Application.

Same application as electron tube version.

Characteristics.


Essentially the same characteristics as electron tube version, except it uses a transistor instead of an electron tube.

Circuit Analysis.

General. An output which is the differentiated value of the input voltage is generated by the derivative amplifier. The relationship between the input capacitor and feedback resistor of a PNP transistor operational amplifier develops the differentiated output. The r-c time constant, which determines the exponential decrease of current, is formed by the product of the input capacitor and feedback resistor. The exponentially varying current flows through the capacitor, the transistor, and the feedback resistor. The product of the current and the ohmic value of the feedback resistor equals the output voltage value at any given time. The output voltage, then, varies exponentially as the capacitor current varies.


Circuit Operation. The one line diagram for the semiconductor version of the derivative amplifier is the same as the electron tube version, and therefore is not shown here.

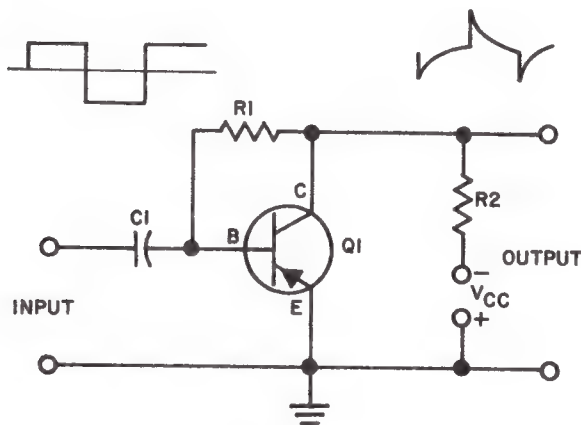The schematic of a derivative amplifier is shown in the accompanying illustration. Capacitor C1 couples the input signal to the base of transistor Q1. Capacitor C1 and resistor R1 form an r-c network which determines the output waveform at any given time. Resistor R1 also provides base bias to transistor Q1. Resistor R2 is the collector load resistor.



Derivative Amplifier

Assuming a square wave signal is applied to the input, and a positive-going input pulse is applied to the base of Q1 through C1, the transistor forward bias is decreased. Emitter and collector currents are decreased because of the decreased forward bias. The collector current decrease produces a more negative voltage at the collector of Q1 as the collector voltage rises toward the supply value (time t_1 on the waveform chart).

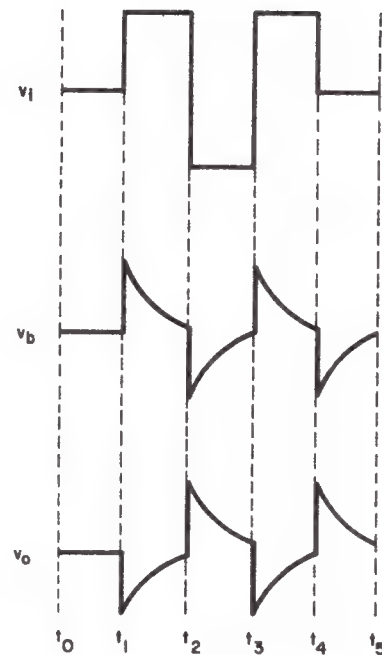

Waveform Chart

Simultaneously, feedback current flows through resistor R1 from collector to base, producing a voltage drop across R1, which slightly reduces negative collector voltage fed back to the base, which simultaneously reduces the input voltage. Capacitor C1 charges at a rate determined by the time constant of C1 times R1. The input voltage at the base of Q1 decreases at the rate that C1 charges (during time t_1 to t_2). This charging action increases the forward bias of Q1, creating increased emitter to collector current. As the collector current is increased toward its quiescent value at t_2 , the voltage at the collector becomes less negative (more positive) at the same rate. The resulting positive-going voltage swing varies directly

with the charge on C1. The negative output voltage spike produced from t_1 to t_2 is the inverted derivative of the applied positive input voltage. The charging of C1, during the flat-top portion of the input signal during time t_1 to t_2 produces the curved trailing edge of the negative output signal, and continues until the input signal changes polarity at time t_2 . The negative-going trailing edge of the input signal causes C1 to discharge abruptly. The full negative input voltage is now applied to the base of Q1 at time t_2 . This produces a large increase in forward bias, which increases the emitter to collector current. The increase of collector current results in a less negative (more positive) voltage at the collector of Q1 (developed by the larger IR drop across collector resistor R2). A feedback current also flows through R1 from collector to base, and develops a feedback voltage which detracts slightly from the input voltage. Capacitor C1 again charges at the rate determined by C1 times R1 during time t_2 to t_3 . The charge is now in a positive direction and the voltage at the base of Q1 again increases during time t_2 to t_3 at the rate that C1 charges. This decreases the forward bias of Q1, creating decreased emitter to collector current. As the collector current is decreased, the voltage at the collector rises towards the supply value and becomes more negative at the same rate, since there is less current flowing through collector resistor R2. The resulting output voltage during time t_2 to t_3 varies directly with the charge on C1. This output voltage is the inverted derivative of the applied negative input. Again C1 charges during the flat portion of the input signal t_2 to t_3). When the signal changes polarity at time t_3 , C1 is immediately discharged and the same action occurs as described above for the first positive-going input pulse at time t_1 .

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of multiplier resistance employed on the low-voltage ranges of conventional volt-ohmmeters. Be careful also to observe proper polarity when checking continuity, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. An open input, a defective collector load, a defective collector supply, or a defective transistor can cause a lack of output to occur.

If capacitor C1 is open, no input will be applied to the base, resulting in no output variations. An open or shorted resistor R2, or a defective collector supply voltage source will prevent voltage from being available at the collector of Q1. If none of these components is found defective, transistor Q1 is probably defective.

Low or Distorted Output. The output may be low or distorted if the input is shorted the feedback resistor is open or shorted, the collector supply is defective, or transistor Q1 is defective.

With input capacitor C1 shorted, no charging time constant can be developed, and the output becomes an inverted form of the input voltage. Likewise, with resistor R1 open, no time constant is developed by which C1 can charge. If R1 is shorted, the transistor effectively becomes a diode and the output is not influenced by the input. A low or high collector supply voltage, produced by a defective collector supply source, results in a distorted output. If none of these faulty conditions exists, but there is a low or distorted output, Q1 is probably defective.

DIFFERENTIAL AMPLIFIER (ELECTRON TUBE)

Application.

The differential amplifier is used in control and analog circuits to provide an output which represents the difference between two input voltages.

Characteristics.

Uses dual triodes with a common cathode resistor.

Degenerative feedback is used.

Output is taken from between the plates instead of between plate and ground.


Symmetrical grid and plate circuits are used.

Circuit Analysis.

General. The differential amplifier (sometimes referred to as a difference amplifier) uses two triodes connected to a common cathode resistor. Plate current flow through the triodes develops a common cathode bias. Since the plate and grid circuits of each tube are symmetrical, equal grid input voltages produce equal plate output voltages. Since the output is taken between the plates of the two tubes, there is no potential difference and, effectively, no output. Hence, the output is the effective difference between

the two input signals. Unequal input voltages produce unequal plate voltages. The output voltage is now the difference between the input signals. If opposite polarity input signals are applied, the output will represent the algebraic difference between the input signals.

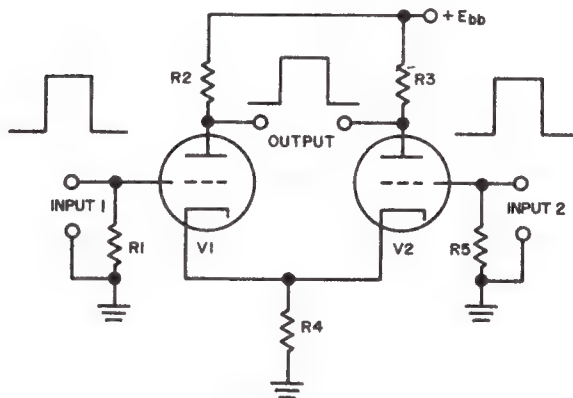Circuit Operation. The schematic of a typical difference amplifier is shown in the accompanying illustration.



Differential Amplifier

Resistors R1 and R5 are the respective grid return resistors for V1 and V2, while R2 and R3 are the respective plate resistors. Cathode resistor R4 is unby-passed, and provides an instantaneous bias which varies with the signal, providing degenerative feedback. The output is taken between the plates of V1 and V2.

For ease of circuit explanation, the operation of each tube will be discussed separately and then the two will be combined. When examined individually, the effect of two simple amplifiers with degenerative feedback in the cathode will be clearly understood. Thus, when V1 grid is driven in a positive direction, increased plate current flows through R2 and produces a negative voltage drop or output. At the same time, the flow of current through cathode resistor R4 develops a cathode bias which determines the grid operating point, plate current flow, and effective amplification factor. The larger the input signal, the greater is the bias developed across the cathode resistor. Thus, a degenerative form of feedback is developed which reduces the range of amplification,

helps to make the operation more linear, and reduces the effects of changes in variation of gain with different tubes. When a negative input signal is applied to V1 grid, plate current flow through R2 is reduced. Consequently, the output voltage increases and produces a positive output swing. At the same time, the cathode bias voltage developed across R4 is less.

If we now consider the operation of V2, it can be seen that it operates identically, except that when the input is applied to the grid of V2, plate current increases or decreases through plate resistor R3. For identical input signals, equal outputs of the same polarity are developed across both plate resistors.

Consider, now, the combined operation of both tubes through the common cathode connection. When the grids of V1 and V2 are both driven equally in a positive direction, equal plate currents flow through R2 and R3, developing equal plate voltage drops. Since the output is taken between both plates, there is no potential difference and zero output. This represents complete subtraction of both input signals. With both plate currents flowing through cathode resistor R4, the grid to cathode potentials are practically identical and the tube currents are balanced.

On the other hand, when one input signal is larger than the other input signal, different plate currents flow through the plate resistors. Similarly, the cathode current flow is less and the total effective bias is reduced. Since the grids are returned to ground through grid resistors R1 and R5, the effective grid-cathode voltage is also changed. If V1 is the more heavily driven tube, the plate current of V2 is reduced, while V1's plate current through R2 is increased. Hence, the voltage drops across R2 and R3 no longer are equal, and an output voltage will appear between the plates of V1 and V2. This output is proportional to the difference between the two input signals.

When opposite polarity input signals are applied to the grids of the tubes, the plate outputs are also opposite in polarity, and the effect is similar to normal push-pull amplifier operation. In this instance, the output represents the algebraic difference between the input signals. It should be realized that, because of the degenerative feedback afforded by the unby-passed cathode resistor, maximum tube gain is not obtained. Hence, push-pull inputs are not normally applied to the difference amplifier, except where the effect of the difference between two different polarity input signals is desired to control another

circuit, motor, relays, or to produce a direct meter indication.

Failure Analysis.

No Output. An open input or output circuit, lack of supply voltage, an open cathode circuit, or a defective tube can cause a loss of output. Since the output is taken between the plate circuits of two tubes, both tubes or circuits must be inoperative to cause a loss of output; otherwise, there will be some kind of output from one of the circuits. Normally, an open cathode bias resistor will prevent an output from either tube, and lack of plate supply voltage due to a blown fuse or defective supply will also inactivate both circuits. If there is supply voltage, but no plate voltage on both tubes V1 and V2, plate load resistors R2 and R3 are probably defective. If both grid resistors R1 and R5 are open, or no input signals are applied, there will probably be a loss of output. In the special case where V1 and V2 grids are connected across a common load resistor, open R1 or R5 grid resistors may not prevent an output. If all resistors are satisfactory and plate voltage is present on both tubes, the tubes may be at fault. In the case where equal input signals are simultaneously supplied, the circuit will be zero-balanced, and although operating normally, no output will be obtained.

Low Output. A low plate or supply voltage, a small difference between input signals, too high a cathode bias, or defective tubes can produce a low output. If the plate supply voltage is normal, but the plate voltage on either or both tubes is not normal (with no grid input applied) plate resistor R2 or R3 may have changed value, or the tube showing abnormal plate voltage may be defective. If the plate voltage of both tubes with no input signal is low, or high, cathode bias resistor R4 may have changed value. If the plate voltage of one tube is lower than that of the other tube, with equal grid input voltages, either the grid or plate resistors are changed in value, or one of the tubes is drawing more plate current than the other. Compare the resistance values of R1 and R4, and R2 and R3, as well as the plate currents of V1 and V2.

Distorted Output. An output which does not vary in accordance with the difference between the input signals is distorted. Usually such a result occurs when

only one of the amplifier circuits is operating properly. In such case, it will be necessary to check each circuit individually for proper resistance and voltage values, and for defective tubes.

DIFFERENTIAL AMPLIFIER (SEMICONDUCTOR)

Application.

Same application as electron tube version.

Characteristics.

Emitters are coupled together.


Output is obtained between the collectors of the transistors rather than between the collector and ground.

Symmetrical base and collector circuits are used.

Circuit Analysis.

General. The differential amplifier uses two transistors connected to a common stabilizing resistor through separate emitter resistors. Current flow through both transistors develops a common bias. Since the collector and base circuits of each transistor are symmetrical, equal input signals produce equal collector output voltages. Since the output is taken between the collectors of the two transistors, with equal input signals, there is no potential difference, and effectively no output. Hence, the output is the difference between two input signals. Unequal input signal voltages produce unequal collector voltages. The output voltage is now the difference between the two collector voltages and represents the difference between the input signals. If opposite polarity input signals are applied, the output represents the algebraic difference (or mathematical sum) between input signals.

Circuit Operation. The schematic of a typical transistor-differential amplifier is shown in the accompanying illustration. Resistors R1 and R7 are equivalent base input resistors. Resistors R3 and R5 are equivalent emitter resistors. Resistors R3 and R5 in conjunction with common emitter resistor R4 help to establish equal bias voltage for Q1 and Q2. Resistors R2 and R6 are equivalent collector load resistors, which are connected to a common collector supply voltage source.

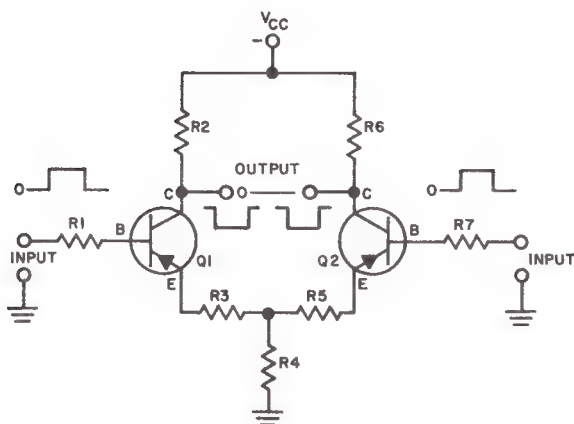

Differential Amplifier

This Circuit is, in effect, two grounded emitter amplifiers using degenerative feedback in the emitter circuit. For ease of explanation, one amplifier will be discussed and then the combined action of both amplifiers will be discussed. When a positive-going voltage is applied to the base of Q1, the forward bias is reduced. The decreased forward bias between the emitter and base of Q1 reduces emitter-to-collector current flow. Consequently, collector current flow through collector load resistor R2 is also reduced. The voltage drop across the collector load resistor is thereby reduced, and the voltage at the collector rises toward the negative collector supply voltage. When a negative-going voltage is applied to the base of Q1, forward bias is increased. The increased forward bias and base of Q1 increases the emitter-to-collector current flow and the collector current through R2. The voltage drop across R2 now increases and makes the collector of Q1 more positive and develops a positive output swing.

Since the amplifier consisting of Q2, R5, R6 and R7 is identical to the amplifier just discussed, with the same input pulses applied to the base, operation is identical. When equal amplitude positive pulses are applied to the bases of both transistors, equal negative voltage drops are produced at the collectors of both transistors. Hence, no output is produced in this case, since the output is the difference between the two collector voltages. When a positive pulse is applied to the base of Q1 and a negative pulse is applied to the base of Q2, a negative voltage is produced on

the collector of Q1 and a positive voltage is produced on the collector of Q2. The output is now the algebraic difference between these voltages or the mathematical sum of these voltages. By the same reasoning, when a negative pulse is applied to the base of Q1 and a positive pulse is applied to the base of Q2, a positive voltage is produced on the collector of Q1 and a negative voltage is produced on the collector of Q2. The output again is the algebraic difference between these voltages, or the mathematical sum of these voltages.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of multiplier shunting resistance employed on the low-voltage ranges of conventional volt-ohmmeters. Be careful, also, to observe proper polarity when checking continuity or making resistance measurements since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. A lack of output can result from an open common cathode circuit, a defective plate supply voltage source, or a defective component in both amplifiers.

With resistor R4 open, current is prevented from flowing through any part of the circuit. If collector supply voltage source V_{CC} is defective, no voltage is supplied to the collector of either transistor.

An output cannot be produced by either amplifier if the input resistor (R1 or R7) is open, the collector load (R2 or R6) is defective, the emitter bias resistor (R3 or R5) is open, or if the transistor (Q1 or Q2) is defective.

When the input resistor (R1 or R7) is open, the input signal can not be applied to the base of the transistor. If the collector load resistor (R2 or R6) is open, no collector voltage will appear on Q1 or Q2. An open emitter resistor (R3 or R5) prevents current flow through the amplifier containing this resistor. If proper voltages are present on the electrodes of the transistor, and the collector voltage does not respond to the signal voltage variations, transistor Q1 or Q2 is probably defective.

Low or Distorted Output. A shorted input, a shorted emitter resistance, a defective collector supply voltage, or a defective transistor may cause, the output to be low or distorted.

If resistors R1, R7 or both R1 and R7 are shorted, the signal voltage applied to the base of Q1 and/or Q2

will not be attenuated, the base bias will be less, and the output will probably be distorted. If resistor R3, R4, or R5 is shorted, the emitter biasing of transistors Q1 or Q2 will be incorrect and a low or distorted output will occur. If the collector supply voltage source is defective the output voltage will be either higher or lower than the required voltage. If none of these conditions exists and the output is low or distorted, either transistor Q1 or Q2 may be defective.

BALANCED DIFFERENTIAL AMPLIFIER (SEMICONDUCTOR)

Application.

The balanced differential amplifier is used in CRT deflection circuits and in instrumentation and control circuitry where a balanced input and output are required.

Characteristics.

Produces an output which is in proportion to the difference between two inputs.

Output and input are balanced with respect to ground.


Output is taken between the collector elements instead of from collector to ground.

May be used as an ac or dc amplifier.

Circuit Analysis.

General. The balanced differential amplifier uses two similar amplifier circuits arranged to be driven by separate base inputs, and the emitters are coupled together through a common emitter-resistor. Identical input signals produce identical output signals. Since the output is taken between the two output loads, instead of to ground, there is no potential difference between identical outputs. Thus, an output exists only when there is difference between input signals. Consequently, common noise inputs tend to cancel each other so that the signal-to-noise ratio is usually improved by the differential amplifier.

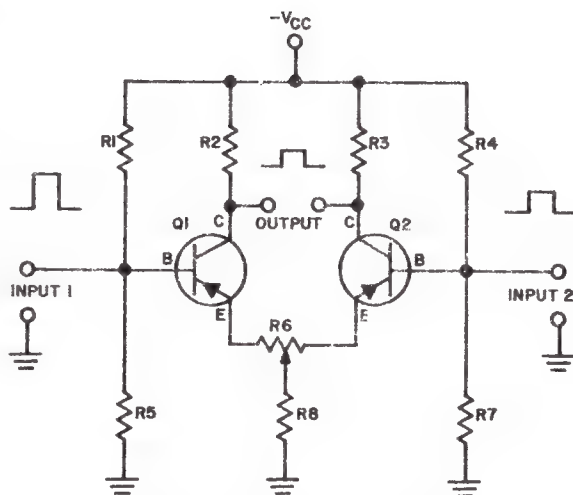Circuit Operation. A schematic diagram of a balanced differential amplifier is shown in the accompanying schematic diagram.



Balanced Differential Amplifier

Fixed base bias is applied to Q1 by bias voltage divider R1 and R5 connected between the negative supply and ground. Resistor R4 together with R7 forms an identical base bias voltage divider for Q2. Resistor R2 is the collector resistor for Q1, and R3 is the collector resistor for Q2; both collector resistors are also the load resistors across which the output is developed. Potentiometer R6 couples the emitter of Q1 to Q2, with the ground return being made through a common-emitter resistor, R8. Potentiometer R6 also permits adjusting Q1 and Q2 for zero balance, and R8 also provides emitter temperature stabilization. Any change in transistor current-flow due to temperature effect produces an opposing bias across R8 which returns the current flow to normal. Emitter stabilization is thus obtained.

Both Q1 and Q2 are symmetrical common-emitter amplifier circuits. When a forward bias is applied to the base of Q1, increased collector current flows through collector load resistor R2, reduces the applied collector voltage to a more positive value, and produces a positive output voltage swing. At the same time that collector current increases, emitter current also increases. The voltage drop produced by current flow through emitter resistors R6 and R8 reduces forward bias slightly, and provides a slight amount of

degenerative feedback which improves output linearity. Since R6 is connected to the emitters of Q1 and Q2, any change appearing on Q1 emitter also appears on Q2. Hence, R6 can be adjusted with equal driving input signals to produce equal conduction through each transistor. This provides an effective zero-balance arrangement to compensate for slight production variations in transistors.

Transistor Q2 operates similarly to Q1. Thus, an increase of forward bias on the base of Q2 produces an increased collector current flow through collector resistor R3, and a positive-going output voltage. With equal amplitude input voltages applied to the base of Q1 and Q2, equal output voltages are produced. Since the output is taken between the collector resistors, instead of to ground, equal output voltages produce no difference of potential between them, and there is no effective output across the output terminals. When one input is larger than the other, an output is produced which is the difference between the two collector outputs.

When the forward bias on either Q1 or Q2 is reduced, less collector current flows through R2 and R3, and the collector voltage increases toward the supply value, producing a negative-going output swing. Again, for equal inputs, no output is produced. For different amplitude signals, the output is proportional to the difference between the applied input signals.

When signals of opposite polarity are applied, the output polarities are opposite, since the collector current of one transistor increases while that of the other transistor decreases. Thus, push-pull operation is obtained, and the output represents the sum, or algebraic difference between the two input signals.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of multiplier resistance employed on the low-voltage ranges of conventional volt-ohmmeters. Be careful also to observe proper polarity when checking continuity with an ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. An open input, output, emitter circuit, or defective transistors, as well as a loss of supply voltage can produce a no-output condition. In most instances, both circuits must be affected, since

if only one of the circuits is operative, some kind of output will be obtained. Lack of supply voltage will cause both circuits to be inoperative. An open emitter resistor, R8, will also prevent both circuits from operating. Two input signals of equal polarity and amplitude will also cause lack of output indication, but in this instance the circuit is operating normally. Where the bias, emitter, and collector voltages appear normal, but there is still no output with unequal input signals, the possibility exists that both transistors Q1 and Q2 are defective.

Low Output. Lower than normal bias, emitter, collector, or supply voltages can cause a loss of output. With a normal supply voltage, low bias can be caused by a change in the value of bias voltage-divider resistors R1 and R5, or R4 and R7. Low collector voltage can be caused by a change in collector resistor values of R2 or R3, or by a change of characteristics in either transistor Q1 and Q2. If emitter resistor R6 or R8 increase in value, a low output will also occur. There is also the possibility that an unbalance caused by a change in values in the parts of one amplifier can be compensated for by readjustment of zero balance potentiometer R6. In most cases, a resistance analysis of the individual parts will indicate the defective component.

Distorted Output. An output which does not vary proportionally with the difference between input signals can be considered as operating in a distorted mode. In most instances of this type, one of the amplifiers will be operating normally while the other amplifier is defective. If the individual outputs are observed against ground with the same input signal applied, the unequal output may be easily determined. Do not neglect the possibility that zero balance control R6 is incorrectly adjusted, since unequal outputs will occur if the circuit is not balanced properly.

SINGLE-ENDED OUTPUT DIFFERENTIAL AMPLIFIER (SEMICONDUCTOR)

Application.

The single-ended output differential amplifier is used in control circuitry and data handling equipment where the difference between two input signals is used to control an output which is not balanced to ground.

Characteristics.

Uses two transistor amplifiers with a common emitter-coupling resistor.

Two inputs are required to produce an output proportional to their difference.


The output is unbalanced with respect to ground.

May be used as a dc or an ac amplifier.

Circuit Analysis.

General. The single-ended output differential amplifier can be considered as an emitter-follower amplifier driving a common-base output amplifier. One input controls the emitter-follower amplifier, which is direct connected to the emitter of the common-base amplifier. The output is thus controlled by the emitter bias. Simultaneously, an input is applied to the base of the output amplifier which also controls the output. When the inputs are of different polarity, the output to ground represents the algebraic difference between the two signals. When the inputs are of the same polarity, the output represents the mathematical difference between these signals. Inputs of equal amplitude and polarity effectively cancel and prevent any change of circuit operation, producing an effective zero output. For unequal amplitude inputs, the larger signal controls operation.

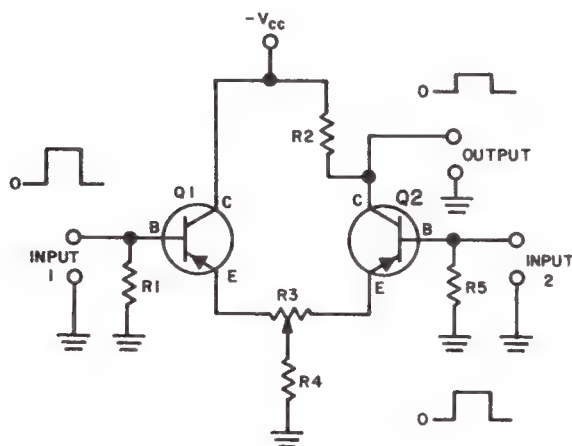Circuit Operation. The schematic of a typical single-ended output differential amplifier is shown in the accompanying illustration.



Single-Ended Output Differential Amplifier

Resistor R1 is the base input and bias resistor for Q1. Potentiometer R3 is the common emitter-coupling resistor and zero-balance control for Q1 and Q2, with R4 acting as the emitter stabilizing resistor. Resistor R2 is the collector load and output resistor for Q2, and R5 is the base input and biasing resistor. The output is taken from the collector of Q2, and the separate inputs are applied to the base of Q1 and Q2.

Since there is no collector resistor for Q1, the collector bias supply filter capacitor effectively grounds the collector for ac. The output is taken from the emitter of Q1 and applied through R3 to the emitter of Q2; therefore, transistor Q1 can be considered an emitter-follower circuit. Likewise, since the inputs of Q2 are between emitter and base of Q1, and between base and emitter for Q2, transistor Q2 can be considered a common-base amplifier. For ease of circuit explanation, each stage is considered separately and their operation combined in a common output.

In the schematic, Q1 and Q2 are fixed-biased by a separate emitter bias supply, so that the base of both transistors are normally forward-biased and the collectors are reverse-biased. When a positive input signal is applied through input-1 to the base of Q1, the forward bias is reduced; thus, the emitter current is reduced. As the emitter current reduces, the output voltage across R4 and R3 increases positively. Thus, a positive increase in emitter voltage is applied directly through R3 to the emitter of Q2, and the emitter current of Q2 tends to increase. When the emitter current of Q2 increases, the collector current also increases, and a positive-going voltage drop is produced across collector resistor R2 of Q2, producing a positive output. However, at the same time that the emitter of Q2 is driven positive, input 2 (which is also positive) is simultaneously applied to the base of Q2. Normally, this will decrease the forward bias on Q2 and cause the collector voltage to rise toward the source and produce a negative output. Since a positive input to the emitter of Q2 effectively cancels the positive input to the base of Q2, the total resultant forward (or decreased) bias depends upon the relative amplitudes of the input voltages. If input 1 predominates, a positive output is produced. If input 2 predominates, a negative output is produced. In either case, the relative output is proportional to the difference between the two input voltages. When both inputs are of the same amplitude, the negative

and positive drops across R2 are equal, and no output results. When inputs of opposite polarity are applied, they bias Q2 in the same direction, so the output actually is the sum of the two signals, or the algebraic difference. Emitter-coupling resistor R3 is a potentiometer, and permits R4 to be connected as a voltage divider to produce an emitter input to Q2 which is equal in amplitude to the base input. Hence, by applying equal input signals and adjusting R3, the output voltage from Q2 may be balanced to zero.

Other circuit variations may be found in other technical manuals, such as using fixed or voltage divider base bias, or even self bias. The circuit arrangement is always such that the output developed by Q1 opposes the input applied to Q2, and results in the difference between the input signals producing the output.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low value of multiplier resistance employed on the low-voltage ranges of conventional volt-ohmmeters. Be careful also to observe the proper polarity when checking continuity with the ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. Open input circuits, open emitter circuits, open output circuits or defective transistors can cause loss of output. If base resistors R1 and R5 open, the base to emitter circuit will be offered a high impedance path through the input signal source, and operation will probably be blocked. If either R3 or R4 opens, the emitter circuits of the transistors will be incomplete and no bias voltage will be measured between emitter and ground. If R2 opens, there will be no collector load for Q2 and no output can be developed. If the emitter, collector, and base voltages are normal, but still no output is obtained, transistors Q1 and Q2 are defective. If no collector voltage appears on both transistors, the supply source is at fault.

Low Output. If any of the resistors change in value, if the supply source is low, or improper bias is applied, or if one or both transistors are not normal, the output will be lower than normal. If the voltage on Q2 collector is normal, and both R2 and the supply source voltage are normal, but the collector voltage of Q2 is low, improper bias can be the cause. Check R3 and R4 and the emitter supply voltage. If

R1 or R5 changes in value, the input signal amplitudes will be affected, and an improper output will be obtained. Similarly, if Q1 or Q2 characteristics change, an improper output will be obtained.

Distorted Output. If the output of Q2 varies other than as the difference between the input signals, one or both transistor circuits are operating improperly, and distortion is occurring. The output of Q1 should produce a waveform identical in shape and polarity to input-1 and of slightly less amplitude. The output of Q2 should always be proportional to the difference between the waveform on the emitter of Q2 and input-2.

BALANCED SUPER-ALPHA DIFFERENTIAL AMPLIFIER (SEMICONDUCTOR)

Application.

The balanced super-alpha differential amplifier is used in analog computers and control circuitry where higher gain than that obtained by the conventional balanced differential amplifier is required.

Characteristics.

Uses super-alpha circuit to provide high gain.

Circuit is balanced with respect to ground.


Output is taken between emitters instead of to ground.

Either self- or fixed-bias can be used.

Circuit Analysis.

General. The super-alpha differential amplifier uses two NPN and two PNP transistors. Through use of the complementary transistors, the same power source may be used for both stages and a super-alpha circuit can be employed. The super-alpha circuit connection uses two direct-coupled transistors in a feedback circuit which is equivalent to a single transistor with superhigh gain. This gain is usually so high that it can never be equalled by a single transistor. Both input and output circuits are balanced, and identical outputs are obtained. Since the output is taken between the emitters instead of to ground, equal outputs effectively cancel; an output is only obtained when the input signals are different in amplitude, resulting in an amplifier which responds only to the difference between the input signals.

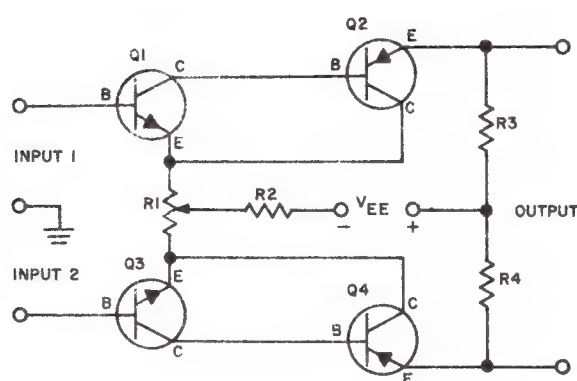Circuit Operation. The accompanying schematic illustrates a typical balanced super-alpha differential amplifier.




Super-Alpha Differential Amplifier

Resistor R1 is the emitter-coupling resistor for transistors Q1 and Q3, while R2 is the common emitter-stabilizing resistor. Resistor R1 also provides a zero-balance arrangement for the circuit. Transistors Q1 and Q3 are the complementary input amplifiers, while Q2 and Q4 are the complementary output amplifiers. Resistors R3 and R4 from the emitter and output loads for Q2 and Q4, respectively.

Since the emitters of Q1 and Q3 are connected to a negative source, forward-emitter bias is produced for these NPN transistors. Since the collectors of Q2 and Q4 are connected to the same negative source, the collectors are reverse-biased, as is usual for PNP transistors.

Basic operation can be more easily understood if the super-alpha circuit is simplified to a single NPN transistor as shown in the accompanying illustration. In this case Q1 and Q2 are replaced with single NPN transistor Q1A, while Q2 and Q4 are also replaced with a single NPN transistor, Q2A. Even though simplified, current flow is the same as in the original circuit, and because of this the emitter and collector elements are drawn reversed. Hence, when a positive input signal is applied to NPN transistor Q1A, the forward bias on the NPN transistor is increased, a larger emitter current flows through R2 and R1, and back through the collector of Q1A and load R3 to the supply. Similarly, when a negative input is applied to the base of Q2A, an increased emitter current flows through R2 and R1, and through the emitter to the collector of Q2A and R4 to the supply source. Thus, negative-going voltage drops are produced across R3 and R4, and the output taken between the

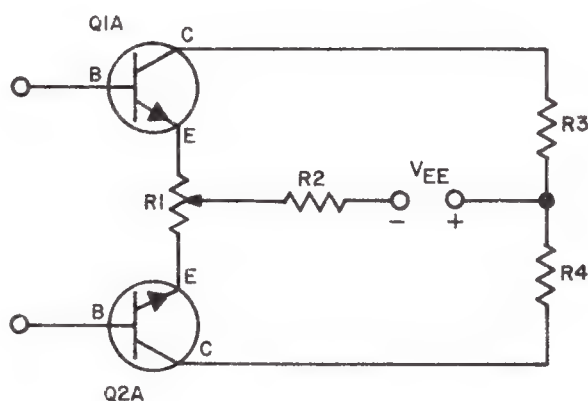

Simplified Super-Alpha Circuit

collectors of Q1A and Q2A is zero (for equal input amplitudes) when R1 is set for zero balance with no inputs. For unequal inputs, the output is the difference between the collector voltages, which is proportional to the difference between the inputs.

Now consider the original super-alpha circuit, remembering that current flow is in the same direction, but that the output emitter and collector elements are reversed in a PNP configuration. When a positive input is applied to the base of Q1, the emitter and collector current of Q1 increases. Current flow is through R2, R1, and the emitter and collector of Q1 to the base of Q2. An increased current flow into the base of Q2 increases the emitter and collector current of Q2, and an increased current flows from the emitter to the collector of Q2 and through emitter-load resistor R3 to the supply. Thus, a negative-going voltage is produced by Q2. In a similar manner, when a positive input is applied to the base of Q3, the emitter and collector current of Q3 increases, and current flows through R2, R1, and from the emitter to the collector of Q3. Since the collector of Q3 is connected to the base of Q4, an increased base current flows. As a result, the emitter and collector current of Q4 increases and an increased current flows through Q4 and back through R4 to the supply source. Thus, a negative-going output voltage is developed across the output of Q4. With equal amplitude inputs, equal negative outputs are developed, and no difference in potential exists across the output when the circuit currents are balanced.

When the input to Q1 or Q2 is changed to a negative input, the reverse action occurs; the PNP

transistor currents are reduced, and the drop across the output load is in a positive direction. Again, with equal inputs and outputs, there is no potential difference across the output and effectively no output occurs. Unequal inputs produce an output proportional to the difference between the input signals.

Since the input emitters of Q1 and Q3 are connected together through R1, it is also possible to apply a single input to Q3 and ground the input to Q1. In this special case, the emitter of Q3 will have an opposing signal applied and a balanced output will still be obtained. If, however, the output is taken against ground, the output of Q4 will be in-phase with the input, while the output of Q2 to ground is out-of-phase with the input. When different polarity inputs are applied, the output will act as a push-pull amplifier and the sum of the input, or algebraic difference, will produce the output.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of multiplier resistance employed on the low-voltage ranges of conventional volt-ohmmeters. Be careful also to observe proper polarity when checking continuity with an ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. Lack of supply voltage, open emitter resistors, or collector resistors, as well as defective transistors can cause a loss of output. If there is no supply voltage, if R2 is open, or if both transistors Q1, Q3, or Q2, Q4 are defective, no output can occur. If potentiometer R1 is open on only one side, or if only Q1 or Q2, or Q3 or Q4 is open, or if output resistor R3 or R4 is open, a partial output will occur. It is necessary for both R3 and R4, Q1 and Q3, or Q2 and Q4, or both sides of R1 to be open to produce no output, since both circuits must be rendered inoperative simultaneously for no output to occur.

Low or Distorted Output. If the supply source is low, if any transistor changes characteristics, if improper bias exists, or if R2, R3, or R4 changes in value, a low or distorted output can occur. If the supply source measures low, low bias and output current will produce a low output. If one half of the circuit operates properly and the other half does not, a distorted and low output will probably occur. A change in the value of currents drawn by the transistors will produce different voltage drops across R1,

R2, R3 and R4, and produce unequal output. If the currents decrease, or the resistor values decrease, a low output will occur. If the currents increase, or the resistor values increase, a higher than normal output will probably occur. Where the waveforms appear normal at the inputs, and the outputs are distorted but voltages appear to be within tolerance, the transistors are probably at fault. A resistance check will usually indicate if any parts are defective.

DIRECT-COUPLED CASCADED DIFFERENTIAL AMPLIFIER (SEMICONDUCTOR)

Application.

The direct-coupled cascaded differential amplifier is used in computers, cathode-ray tube circuits, and in control circuits where a low-drift and high-gain dc amplifier is required.

Characteristics.

Direct coupling is used.

Both amplifiers are balanced with respect to ground.

Output is taken from between the collectors instead of to ground.

Fixed bias is employed.


Circuit Analysis.

General. The direct-coupled cascaded differential amplifier uses two differential amplifier connected in series, that is, the collector output of the input stage is directly connected to drive the base of the output stage. Both input and output stages can also be direct-coupled to the input or output loads, if desired. Since the differential amplifier is balanced, and inherently stabilized by a common-emitter resistor against temperature effects, it has very little drift (output level does not change with temperature). Therefore, with a minimum of drift, direct coupling is used to obtain a relatively stable high-gain amplifier. When an input signal is applied to both input stages, it either increases or decreases the base bias of the output stage. Consequently, either a negative or a positive output swing is developed across the output load. Since both outputs are of the same polarity when similar inputs are applied, the output is produced by the difference between the two input signals. Equal amplitude inputs will produce equal outputs, and there will be no potential difference between them. Thus, the effective output will be zero

if the circuit is correctly balanced. With unequal polarity inputs applied, the circuits will operate as push-pull amplifiers and produce the algebraic dif-

ference or sum of the input signals. Since each stage inverts the input and two stages are used, the output will always be the same polarity as the input.

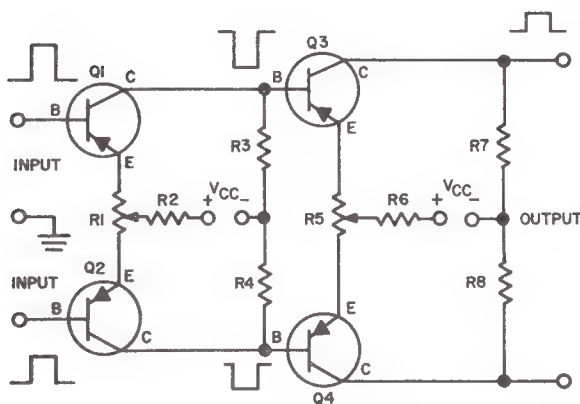Circuit Operation. The schematic of a typical cascaded direct-coupled differential amplifier is shown in the accompanying illustration.



Cascaded Direct-Coupled Differential Amplifier

Resistor R1 couples the emitters of input transistors Q1 and Q2 together, and R2 is an emitter-stabilizing resistor which is common to both input stages. Resistors R3 and R4 are the collector resistors and loads for Q1 and Q2, respectively. They also act as the base input resistors for Q3 and Q4. Potentiometer R5 couples the emitter of Q3 and Q4, and acts as a zero-balance control for the output circuit. Resistor R6 is an emitter-stabilizing resistor which is common to both Q3 and Q4. Resistors R7 and R8 are the collector and load resistors for output transistors Q3 and Q4 respectively. The inputs are applied to the base of Q1 and Q2, while the output is taken between the collectors of Q3 and Q4.

Normally, Q1 and Q2 are base-biased by the input circuit, or by voltage divider bias (not shown in the schematic). The bias is such that equal input swings are possible without biasing the transistors to cutoff (Class A operation). Transistors Q1 and Q3 operate as conventional common-emitter amplifiers. The direct coupling between the collector of Q1 and the base of Q3 places a reverse collector bias on Q1 and a forward base bias on Q3. Operation normally is such that the reverse leakage collector current of Q1 and the collector resistor value produce a bias which places Q3 at the desired operating point. If necessary,

separate bias can be applied to the emitter to obtain the desired operating point. When a positive input is applied to the base of Q1, forward bias is reduced and less collector current flows. The collector voltage on Q1 then increases and a larger negative bias is applied to the base of Q3, producing an increased forward bias. Consequently, Q3 collector current increases, and the increased current flow through collector resistor R7 decreases the collector voltage. Thus, a positive-going output voltage swing is created, and the output is in phase with the input.

In a similar manner, when a positive signal is applied to the base of Q2, reduced collector current flows through R4 and the collector voltage on Q2 increases. This negative increase of voltage is applied to the base of transistor Q4, and causes an increased collector current flow through R8. Hence, the output of Q4 is positive-going, and is in phase with the input. Since the output is taken across the collectors, equal output swings of equal polarity will produce an effective zero output. As long as the output swings are different, there will be a proportionate output which varies as the difference between the outputs. Since a difference in outputs can only be produced (in a balanced circuit) if there is a difference between the input signals, any output represents the difference between the input signals. By connecting the emitters of Q1 and Q2 together with potentiometer R1, emitter-stabilizing resistor R2, which is common to both stages, provides the same temperature compensation for each transistor. Also, the different resistance paths through R1 to both emitters cause an emitter bias to be produced, which compensates for any differences in emitter current resulting from production variations. Thus, R1 is adjusted for zero-balance with no input signal applied, so that approximately equal output currents are developed by equal input signals. Potentiometer R5 connects the emitters of Q3 and Q4 together and operates similarly to zero-balance the output stage, while resistor R6 operates as the common stabilizing emitter-resistor for Q3 and Q4. With both input and output circuits properly zero-balanced, equal outputs are always developed for equal inputs.

In normal design, transistors Q3 and Q4 are usually power-type transistors. Thus, with conventional driving transistors used for Q1 and Q2, a high-current gain can be realized from cascaded direct-coupled stages, and a large output is developed.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of multiplier resistance employed on the low-voltage ranges of conventional volt-ohmmeters. Be careful also to observe proper polarity when checking continuity with an ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. Lack of supply voltage, an open input or output circuit, or defective transistors can result in a loss of output. If emitter-stabilizing resistor R2 or R8 opens, the associated amplifier circuits will not operate. If collector resistors R3 and R4, or R7 and R8 are open, no collector voltage will appear on the collectors of Q1 and Q2, or Q3 and Q4, respectively, and no output will occur. Note that both resistors must be open, or alternate resistors in cascaded stages must be open, to cause a complete loss of output. Likewise, if the transistors are defective, it is necessary that one in each channel be defective; otherwise, a single unbalanced output could occur.

Low or Distorted Output. If the supply voltage is low, if improper bias exists, if the collector resistors change in value, or the emitter resistors change, a low output or a distorted output can occur. If the transistor characteristics change, or if the circuit is not zero-balanced, a low and distorted output can occur. If emitter coupling resistors R1 and R5 open, the circuits cannot be zero-balanced and the output will be somewhat distorted. If collector resistors R3, R4, R7 or R8 change in value sufficiently that zero balance cannot be obtained, unsymmetrical outputs will be obtained, and a low or distorted output will occur.

DIRECT-COUPLED CASCADED, COMPLEMENTARY-SYMMETRY DIFFERENTIAL AMPLIFIER (SEMICONDUCTOR)**Application.**

Same application as direct-coupled cascaded differential amplifier.

Characteristics.

Same characteristics as direct-coupled cascaded differential amplifier.


Circuit Analysis.

General. The direct-coupled cascaded, complementary-symmetry differential amplifier uses two complementary-symmetry differential amplifiers connected in series (cascaded). The output of the input amplifier is directly connected to drive the base of the output amplifier. Both input and output stages can also be direct coupled to the input or output loads, if desired. Since the differential amplifier is balanced, and inherently stabilized by a common emitter resistor against temperature effects, this type of amplifier has very little drift (the output level does not change with temperature). When minimum drift exists, direct coupling can be used to obtain a relatively stable high-gain amplifier. By using cascaded complementary-symmetry stages, the small amount of drift which normally exists is reduced still further, and extremely higher than normal gain may be obtained.

When an input signal is applied to both input stages, it either increases or decreases the base bias of the output stages. Consequently, either a negative or a positive output swing is developed across the output

load. With similar input polarity signals applied, similar output signals are produced. Since the output is taken between the collectors, equal outputs produce no potential difference between them, and for equal inputs there is effectively no output. With unequal inputs, the output represents the difference between the input signals. When the input signals are of opposite polarity, the output operates as a push-pull amplifier and produces different outputs. The result is the sum or algebraic difference between the input signals. Since each stage inverts the input, and two stages are used, the output is always of the same polarity as the input.

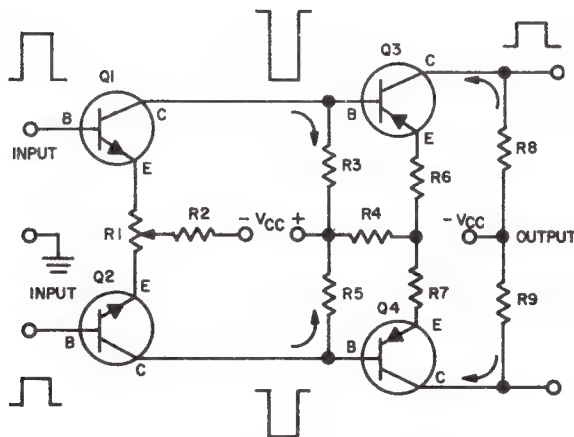Circuit Operation. The schematic of a typical cascaded complementary-symmetry differential amplifier is shown in the accompanying illustration.



Cascaded Direct-Coupled Complementary-Symmetry Differential Amplifier

Potentiometer R1 couples the emitters of NPN input resistors Q1 and Q2 together, and R2 is an emitter stabilizing resistor common to both input stages. By adjusting the emitter bias applied through R1 and R2, the output may be adjusted for zero balance (with no input signals applied) to ensure that both stages are properly balanced. Resistors R3 and R5 are the collector resistors and loads for Q1 and Q2, respectively. They also act as base input resistors for PNP transistors Q3 and Q4. Resistors R6 and R7 couple the emitters of Q3 and Q4, and act as balancing and stabilizing resistors. Resistor R4 is an emitter bias and stabilizing resistor which is common to both

Q3 and Q4. Resistors R8 and R9 are the collector and load resistors for output transistors Q3 and Q4, respectively. The inputs are applied to the bases of Q1 and Q2, while the output is taken between the collectors of Q3 and Q4. Normally Q1 and Q2 are base-biased by the input circuit, or by a voltage divider bias (not shown on the schematic). The bias is such that equal input swings are possible (class A operation). Transistors Q1 and Q3 operate as conventional cascaded common-emitter amplifiers. Transistor Q1 is an NPN type, while Q3 is a PNP type. The direct coupling between the collector of Q1 and the base of Q3 places a reverse collector bias on Q1, and indirectly, a forward bias on the base of Q3. As connected, the emitter of Q3 is forward-biased through R4 and R6 from the same supply which biases the collector of Q1 and the base of Q3. Collector resistor R3 for Q1 is larger in value than emitter resistors R4 and R6 combined. Thus, the drop through R3 by normal (quiescent) collector current flow through Q1 produces a steady negative voltage drop, so that the base of Q3 is always more negative than the emitter. The emitter is more positive than either the base or collector of Q3, since the collector of Q3 is reverse-biased. Thus, Q3 base is effectively forward-biased by the direct coupling circuit, even though a positive voltage exists on the collector of Q1 and the base of Q3. That is, the base of Q3 is less positive (more negative) than the emitter of Q3, and the operating bias is effectively a negative (forward bias) voltage with respect to its emitter. Design is such that the stage operates at the center of its linear Class A range, so that equal positive or negative bias swings are possible without creating excessive distortion.

When a positive input signal is applied to the base of Q1, the forward bias is increased and more collector current flows through R3, driving the base of Q3 negatively and increasing the forward bias on Q3. Hence, the collector current of Q3 increases and the voltage drop produced across the collector resistor R8 is positive-going, producing a positive output (less negative voltage) at the collector.

In a similar manner, when a positive input signal is applied to the base of Q2, forward bias is increased, and the increased collector current flow through R5 produces a negative-going voltage at the base of Q4, and increases the forward bias. With an increased forward bias on Q4, an increased collector current flows through R9, reduces the collector voltage, and produces a positive-going output swing. Since the output

of the total circuit is taken between the collectors, equal amplitude output swings of the same polarity produce an effective zero output. If the output voltage swings are different in amplitudes, there will exist a proportionate output which varies as the difference between the output of Q3 and Q4. A difference in outputs can only be produced in a balanced circuit when there is a difference between the input signals. Since the emitters of Q1 and Q2 are connected together by potentiometer R1, emitter stabilizing resistor R2, which is common to both stages, provides the same temperature compensation for each transistor. By varying the position of R2 along potentiometer R1, different resistance paths are provided through R1 to each emitter, and allow an emitter bias to be produced which compensates for any differences in emitter currents caused by production variations. Thus, R1 is adjusted for zero balance (no output with no input signal applied), so that approximately equal output currents are developed by equal input signals. Resistors R6 and R7 connect the emitters of Q3 and Q4 together, and are temperature-stabilized through common emitter resistor R4, which operates similarly to R2. Since resistors R3 and R5 are equal, as are R6 and R7, and R8 and R9, only the single zero-balance potentiometer R1 is needed for proper adjustment of circuit balance.

When negative inputs are applied to Q1 and Q2, the collector-current flow through R3 and R5 is reduced by the decreased forward bias, and the collector voltage of Q1 and Q2 becomes positive-going, rising toward the source value. In turn, the base bias of Q3 and Q4 is reduced, and less collector current flows through resistors R8 and R9. Thus, the collectors of Q3 and Q4 rise toward the negative source voltage, and produce an effective negative-going output. Again, for equal inputs, equal outputs are produced, and there is no effective difference in potential between them. Hence, the total output is effectively zero. For different amplitude signals, the output is again proportional to the input and the polarity is reversed.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of multiplier resistance employed on the low-voltage ranges of conventional ohmmeters. Be careful, also, to observe proper polarity when checking continuity with an ohmmeter, since a forward bias through any

of the transistor junctions will cause a false low-resistance reading.

No Output. Lack of supply voltage, an open input or output circuit, or defective transistors can result in a loss of output. If emitter-stabilizing resistor R2 or R4 is open, the associated amplifier circuits will not operate. If collector resistors R3 and R5, or R8 and R9 are open, no collector voltage will appear on the collectors of Q1 and Q2, or Q3 and Q4, respectively, and no output will occur. Note that both resistors of balanced stages must be open, or alternate resistors of cascaded stages must be open, to cause a complete loss of output. Likewise, if the transistors are defective, it is necessary that one in each channel be defective, otherwise, a single unbalanced output could occur.

Low or Distorted Output. If the supply voltage is low, if improper bias exists, if the collector resistors change in value, or the emitter resistors change, a low output or a distorted output could occur. If the transistor characteristics change in value, or if the circuit is not zero-balanced, a low or distorted output could occur. If emitter resistors R1, R6, or R7 open, or change to a high value, the circuits cannot be zero-balanced and the output will be somewhat distorted. If collector resistors R3, R5, R8 or R9 change in value sufficiently that zero-balance cannot be obtained, unsymmetrical outputs will occur, and a low or distorted output will result.

EXPONENTIAL AMPLIFIER (ELECTRON TUBE)

Application.

The exponential amplifier is used in analog computers and cathode-ray tube circuits to develop an output voltage proportional to the desired exponential of input voltage.

Characteristics.

Uses a variable- μ pentode.

Unbypassed cathode resistor is used to provide degenerative feedback.


The tube is operated at a non-linear portion of the plate current-grid voltage characteristic curve.

The desired multiple of the input (exponent) to which the output is raised is determined by plate and cathode resistance, and plate voltage.

Circuit Analysis.

General. The exponential amplifier produces an output signal equivalent to an exponentially increased (squared, cubed, etc ...) input signal. This is accomplished by operating only over a selected portion of the tube plate current-grid voltage characteristic curve. The plate current (and output voltage) is, made to vary proportionally with the grid voltage raised to between the $2/2$ power and the $2.5/2$ power. The desired exponent by which the input is to be raised is obtained by the proper selection of plate load resistance, cathode resistance, and plate voltage for a specific value of internal tube plate resistance.

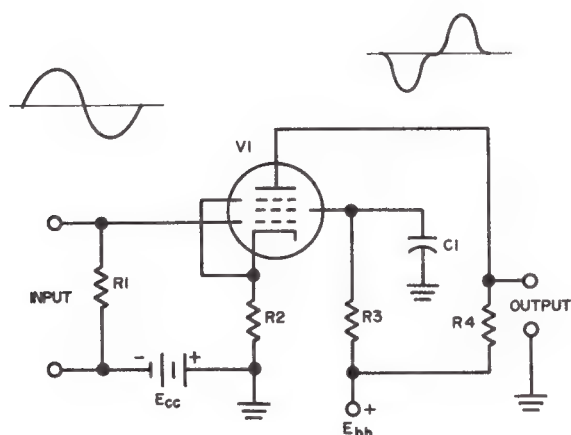Circuit Operation. The schematic of a typical exponential amplifier is shown in the accompanying illustration.



Exponential Amplifier

The input is applied across grid resistor R1. This resistor is also used to apply fixed bias from a separate bias supply voltage (E_{cc}); self-bias is also supplied by unbypassed cathode resistor R2. Electron tube V1 is a variable-mu pentode. Resistor R3 is the screen grid voltage-dropping resistor. Capacitor C1 is the screen grid bypass capacitor. Resistor R4 is the plate load resistor.

The cathode resistance, R2, plate supply voltage, E_{bb} , plate load resistor R4, and the internal resistance of electron tube V1 are chosen to provide an amplified output which varies as the square of the input voltage. By operating variable-mu pentode V1 along a nonlinear portion of the grid voltage-plate

current characteristic curve, the desired exponential relationship between input and output is obtained.

When a positive-going sine wave is applied across resistor R1 to the grid of V1, it effectively decreases the fixed negative bias voltage, and produces increased plate conduction of V1. The plate current rate increase is slight for a small applied grid voltage, and is not proportional to the signal voltage increase. When a positive 1-volt signal is applied, conduction is directly proportional to the input; when the signal increases above 1-volt, the conduction rate becomes proportional to the product of the signal voltage value squared. The increased rate of conduction is enhanced by negative feedback voltage developed at the cathode of V1 through unbypassed resistor R2. The increased plate current of V1 caused by the reduced bias produces a proportional reduction in plate and output voltage.

As the sine wave decreases it causes the grid bias voltage effectively to increase. Plate conduction then decreases at the same rate it increased, until the signal voltage reaches zero. Here the conduction rate of V1 is at a quiescent (static) value. When the input signal voltage swings negative, the plate conduction also decreases at a rate proportional to the square of the input signal voltage. The output voltage developed across plate resistor R4 then increases at a rate proportional to the increase of plate current.

Failure Analysis.

No Output. A loss of output voltage may be caused by an open output circuit, a defective tube, an open cathode resistor, or lack of plate supply voltage.

If plate load resistor R4 is open, no output voltage can be developed since no plate voltage will be applied to V1. A defective plate supply voltage source has the same effect. An open cathode resistor, R2, will produce an open output circuit. If the proper voltages are present on the elements of V1 and there is no output, tube V1 is probably defective.

Low or Distorted Output. A defective input, a defective cathode circuit, a defective screen circuit, or defective supply voltages can result in an output which is low or distorted.

If resistor R1 is defective, improper bias voltage will be applied to the grid of V1, thus providing the incorrect amount of plate conduction for a given signal. A shorted cathode bias resistor, R2, or a defective bias supply voltage E_{cc} will produce the same effect. If screen resistor R3 is defective, improper

screen voltage will be applied to the screen grid of V1. A defective supply voltage source, Ebb, will cause low plate and screen voltages. A defective screen bypass capacitor, C1, will cause output voltage variations to be coupled back to the screen grid of V1, resulting in a distorted output. If none of these conditions exists and proper potentials exist at the elements of V1, the tube is probably defective.

EXPONENTIAL AMPLIFIER (SEMICONDUCTOR)

Application.

The exponential amplifier is used to develop an output voltage proportional to the desired exponential of input voltage. The amplifier is used in analog computers and control circuits.

Characteristics.

Uses common-emitter transistor amplifier configuration.


Uses emitter stabilization for temperature compensation.

Transistor is selected to give an exponential response.

Circuit Analysis.


General. A transistorized exponential amplifier uses a circuit configuration which is essentially the same as a basic transistor amplifier. The distinction between the two types of amplifiers is with the transistor, and, the biasing potentials used. The exponential amplifier uses a transistor and bias combination that produces a collector current variation which is the input voltage raised by a desired exponential. The collector current variation, in turn, produces similar collector and output voltage variations.

Circuit Operation. The circuit of a typical transistorized exponential amplifier is shown in the corresponding illustration. Resistor R1 is a series base resistor. It attenuates the input signal before being applied to the base and reduces base current. Resistors R2 and R4 form a fixed-bias voltage divider for the base of Q1. Resistor R5 is an emitter stabilization resistor, and resistor R3 is the collector load resistor.

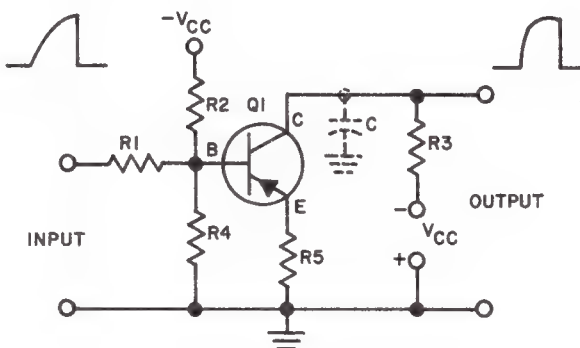

Exponential Amplifier

The positive portion of an input waveform is applied to the input, where it is attenuated by resistor R1 before being applied to the base of Q1. The positive-going input voltage decreases the forward bias of C1. A decrease in base bias causes a decrease in emitter-to-collector current, which, in this case, is proportional to the square of the input signal variation. This is shown in the accompanying illustration of the "Transistor Transfer Characteristic Curve". The decreasing collector current of Q1 causes the IR drop across resistor R3 to decrease at the same rate. The collector, and output voltage then decrease toward the negative collector supply voltage.

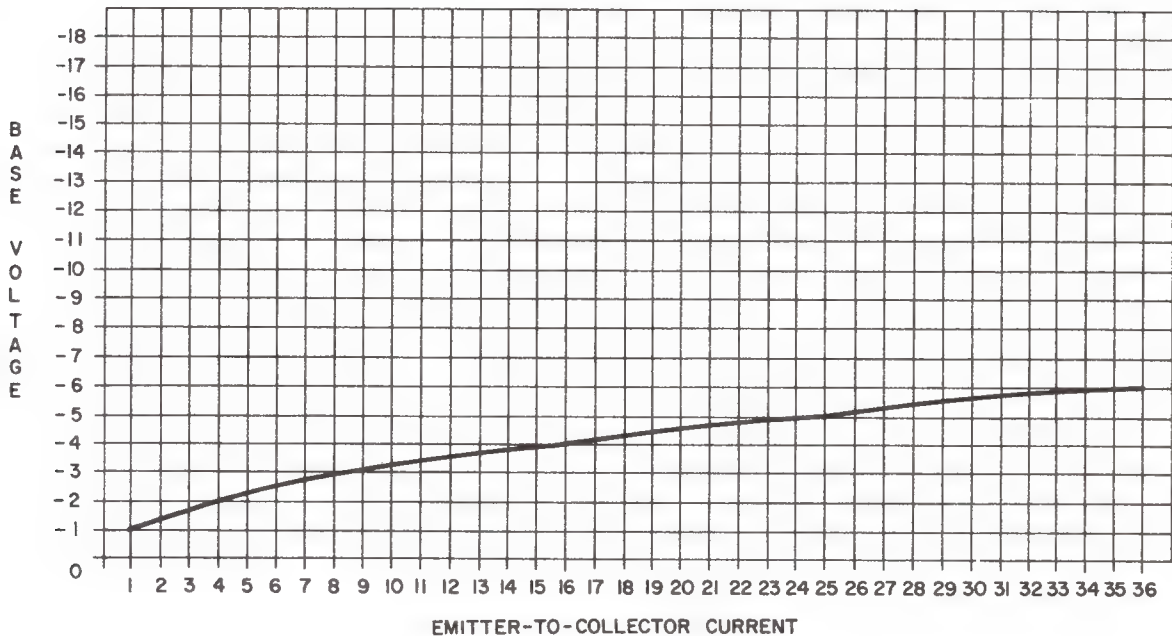

Transistor Transfer Characteristic Curve

As the input waveform passes its positive peak and begins its negative swing, the negative-going input voltage (after being attenuated by R1) is applied to the base of Q1. The forward bias of the transistor is increased by the negative-going input. An increase in bias causes an increase in emitter-to-collector current, which is proportional to the square of the input signal variation. The exponentially increasing collector current of Q1 causes the IR drop across R3 to increase at the same rate. In some circuit variations, a capacitor is placed from the collector to ground to produce an exponential charging waveform.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of multiplier resistance employed on the low-voltage ranges of conventional volt-ohmmeter. Be careful to observe proper polarity when checking continuity, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. There will be no output voltage if the input is open, the collector load is defective, the bias resistor is open, the collector supply source is defective, or transistor Q1 is defective.

An open base resistor, R1, prevents output signal variations from being developed. If R3 were open, no collector supply voltage would be applied to the collector of Q1. No collector supply voltage would be present on Q1 if the collector supply voltage source V_{CC} were defective. An open emitter resistor, R5, prevents any current from flowing in the circuit. If none of these components is defective, and there is no output, transistor Q1 is defective.

Low or Distorted Output. The output becomes low or distorted if the input is shorted, the bias resistor is shorted, the collector supply sources is defective, or if the transistor is defective.

If base input resistor R1 is shorted, the input signals will not be attenuated and a distorted output will occur. A shorted emitter resistor, R5, will slightly lower the output and no temperature compensation

will be produced. A defective collector supply source, V_{CC} may provide a higher or lower collector supply voltage than is necessary. If none of these components is defective and the output is low or distorted, transistor Q1 is probably defective.

INTEGRATING AMPLIFIER (ELECTRON TUBE)

Application.

The integrating operational amplifier is used in analog computer and control circuitry to develop an output voltage that is the integral of the input voltage.

Characteristics.

- Uses a resistive input network.
- Uses a capacitive feedback.
- Uses a triode electron tube.


A square-wave input produces a triangular output waveform.

Usually operated near zero bias.

Circuit Analysis.

General. This integrating operational amplifier, sometimes referred to as a "Miller" integrator, uses a resistive input network and capacitive feedback to produce the integrating effect. The capacitive feedback is essential to circuit operation. The output is developed by the charge and discharge of the capacitive feedback network during the pulse width and the time between pulses of a square wave input. The capacitor also makes the output more linear by controlling plate voltage variations with corresponding smaller and opposite grid voltage (feedback) variations. The output always represents the integral of the input.

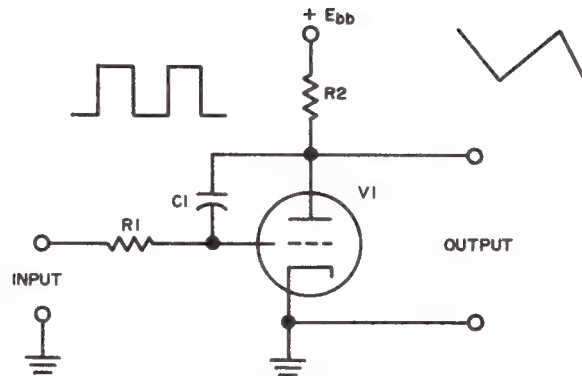Circuit Operation. The schematic of a typical integrating amplifier is shown in the accompanying illustration. Resistor R1 is the grid resistor for electron tube V1. Capacitor C1 is the feedback capacitor, and resistor R2 is the plate load resistor.




Integrating Amplifier

When a positive-going square wave is applied to the grid of V1, it causes increased plate conduction. A corresponding plate voltage decrease (negative swing) is developed across R2. This decrease in voltage (negative swing) is coupled back to the grid through C1. The sum of this voltage and the square wave input pulse results in a decreased grid signal for the moment.

For ease of understanding, refer to the accompanying waveform chart, which shows the grid and plate waveforms and their relationship slightly exaggerated for the purpose of illustration. At time t_0 there is not input, approximately zero bias is applied, and the average plate voltage is 150 volts with no output voltage existing. At time T_1 , the positive-going leading edge of the input signal produces a positive grid bias, which drives the plate into heavy conduction and produces a negative feedback voltage spike. This feedback voltage is applied from plate to grid through C1 and is shown as e_{pg} on the chart. The negative feedback cancels a portion of the positive input signal, and the grid signal is instantaneously reduced to a small value. As a result, plate current decreases and develops a positive feedback voltage, which drives the grid further positive and increases

plate current. The corresponding negative plate feedback signal again cancels a portion of the square wave input, which is constantly applied at full amplitude, for the duration of the input pulse. During time t_1 to t_2 , feedback capacitor C1 is constantly being charged by the effect of negative feedback voltage and the positive input voltage. The addition of these two voltages produces an effectively positive linear grid signal. The positive grid voltage would normally rise exponentially with the charge, as long as the input amplitude remained constant. Since the feedback voltage is constantly affecting the input voltage, the charge occurs nearly linearly. The effect is to produce an average plate current which constantly increases to a maximum at time t_2 , when the trailing edge of the input signal appears. At the same time, the voltage constantly drops, reaching a minimum at 140 volts. Thus, there is a 10-volt negative triangular voltage produced.

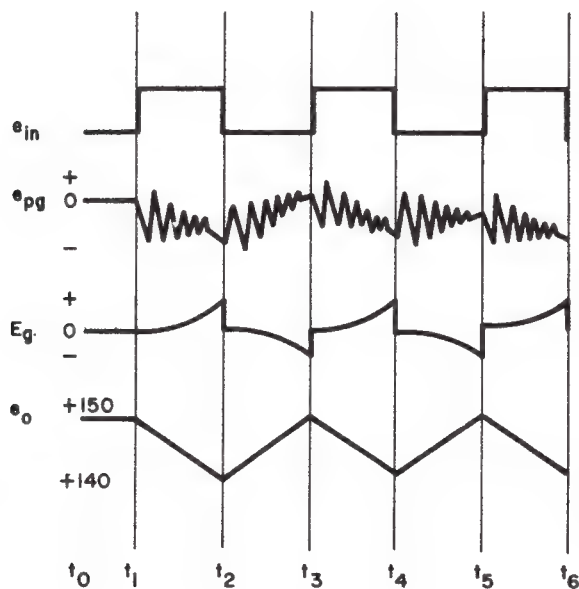

Grid and Plate Waveforms

When the negative trailing edge appears at the input (at t_2), the grid is instantly driven negative, and a large positive plate feedback pulse is created by the decreased plate current. This positive feedback causes an increase in plate current, which produces a negative feedback voltage swing. The negative swing

applied to the grid through C1 reduces the positive voltage on the capacitor, and discharges it a slight amount. Plate current is again decreased, and a positive swing is fed back to the grid. Thus, instead of decreasing exponentially between times t_2 and t_3 , the grid charge voltage on C1 is reduced linearly. As the positive grid bias is reduced to zero between pulses by the discharge of C1, the plate voltage constantly rises. At time t_2 , it again reaches its starting value of 150 volts, the leading edge of the next input pulse arrives, and now drives the grid in a positive direction. From time t_3 to t_4 the cycle of action described above occurs again. The square wave input thus creates a 10-volt triangular output, and represents the integral of the input signal. By selecting the proper time constants and applied voltages, the output voltage and waveshape may be varied for the desired design characteristics. For this reason, the integrator circuit is sometimes used with a switching tube and amplifier to provide a linear sawtooth sweep voltage.

Failure Analysis.

No Output. A defective plate supply source, a defective plate resistance, an open input or a defective electron tube can cause a loss of output.

If no voltage is present on the plate of V1, either the plate supply voltage source or plate load resistor R2 is defective. Check R2 for proper value. If resistor R1 is open, no input will be applied to the grid of V1 and thus no output will be obtained. If all voltages on the electrodes of V1 are proper and no output exists, tube V1 is probably defective.

Low or Distorted Output. The output of this circuit can be made low or distorted by a shorted grid resistor, R1, a defective feedback capacitor, C1, a defective tube, V1, or a defective plate supply voltage source.

If resistor R1 is shorted, the correct charging time constant of C1 will not be obtained, and the output will be something other than the integral of the input. Likewise, if feedback capacitor C1 is open, no charging action will occur, and the output will more closely resemble the input. If C1 were shorted, no charging action would occur and in addition V1 would be connected between grid and plate, acting as a diode. This would produce an output waveform independent of the input voltage. The output will become distorted if the plate supply voltage source provides voltage higher or lower than the desired plate supply voltage. If proper voltages are supplied to all the elements of

V1, and the component parts of this circuit are normal, triode V1 is probably defective.

INTEGRATING AMPLIFIER (SEMICONDUCTOR)

Application.

Same application as electron tube version.


Characteristics.

Same characteristics as electron tube version except it uses transistor with self-bias.

Circuit Analysis.


General. An integrating operational amplifier uses a resistive input network and capacitive feedback to produce the integrating effect. The output is developed by the charge and discharge of the capacitive feedback network during the pulse width and the time between pulses of a square-wave input. The capacitor also makes the output more linear by applying feedback to the base to control collector voltage variations. The output always represents the integral of the input voltage.

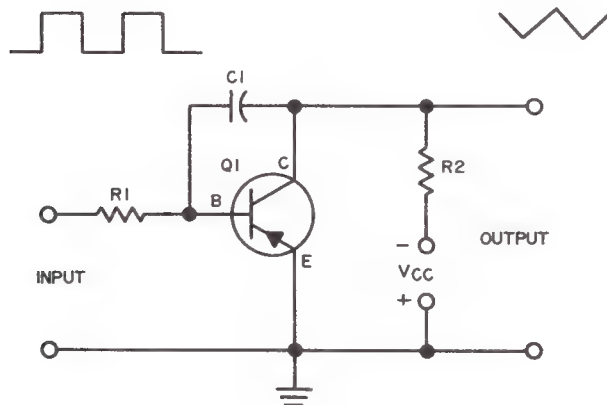Circuit Operation. The schematic of a typical integrating amplifier is shown in the accompanying illustration. Resistor R1 is the base input resistor. Capacitor C1 is the feedback capacitor connected between the collector and base of transistor Q1. Resistor R2 is the collector load resistor.



Integrating Amplifier

The accompanying waveform chart shows the relationship of collector, base, and capacitor feedback waveforms. At time t_0 there is no input and the collector voltage rests at some negative value. At time t_1 a positive-going square wave is applied to the base of Q1, causing a decrease in forward bias. The collector voltage increases negatively and approaches the collector supply voltage, since the current through the collector load resistor is decreased. The negative-going change in collector voltage is capacitively coupled back to the base by C1. This feedback voltage is designated as e_{cb} in the waveform illustration. The base voltage is now lower than the applied input voltage by the amount of the feedback voltage. The forward bias is then increased by this amount resulting in a slight emitter and collector current increase, and a slight drop in voltage across R2 to some more positive value. This positive change in voltage is coupled through C1 to the base of Q1, where it cancels some of the effect of the previously negative-going feedback. The current is decreased slightly between the emitter and collector, and collector voltage again approaches the collector supply voltage, but not nearly as much as it did with the original signal application. This effect continues during the signal pulse

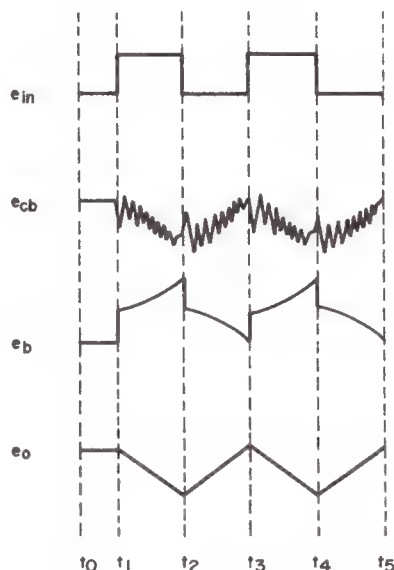

Base and Collector Waveforms

between t_1 and t_2 , but becomes less significant with each feedback pulse. This sawtooth effect is exaggerated in the e_{cb} waveform illustration. During time t_1 to t_2 capacitor C1 is charged by the effect of the negative feedback and the positive input voltage. The addition of these two voltages produces an effectively linear positive base signal. The positive base voltage will normally rise exponentially with the capacitor charge, as long as the input amplitude remains constant. Since the feedback voltage is constantly affecting the input voltage, the charging action occurs nearly linearly. The effect is to produce an average emitter and collector current which constantly decreases to a maximum at time t_2 , when the trailing edge of the input signal appears. At the same time, the collector voltage constantly approaches the negative collector supply voltage. Thus, a nearly linear decreasing negative output is produced.

At time t_2 , the base is instantly driven negative by the negative trailing edge of the input signal. The forward bias is now increased, and produces a larger emitter and collector current, causing greater current flow through R2. The collector current flowing through R2 produces a larger voltage drop across R2, and a more positive (less negative) voltage on the collector of Q1. The increased positive collector voltage is fed back to the base, and causes a decrease in emitter and collector current, producing a negative collector voltage swing. This negative swing is fed back to the base through C1 and reduces the positive voltage on the capacitor, discharging it a slight amount. Emitter and collector current is again increased, and a positive swing is again fed back to the base. Thus, instead of decreasing exponentially between time t_2 and t_3 , the base charge voltage on C1 is reduced linearly. As the forward bias is increased between pulses by the discharge of C1, the collector voltage constantly rises. At time t_3 , it again reaches its initial value, the leading edge of the next input pulse arrives, and applies a positive-going voltage to the base of Q1. From time t_3 to t_4 the cycle of action described above occurs again. The square-wave input thus creates a triangular output, which is the integral of the square-wave input. The output voltage and wave shape may be changed somewhat by selecting the proper time constant and changing the input voltage shape and duration.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of multiplier resistance employed on the low-voltage ranges of conventional volt-ohmmeters. Be careful also to observe proper polarity when checking continuity, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. An output cannot be produced if the collector supply is defective, or transistor Q1 is defective.

If collector load resistor R2 is defective, input variations will not produce output variations. If resistor R1 is open, no signal can be applied to the base of Q1. No collector voltage will be available if collector supply voltage source V_{CC} is defective. If none of these components is defective and there is no output, transistor Q1 is probably defective.

Low or Distorted Output. A low or distorted output may be the result of a shorted base resistor, a defective feedback network, a defective collector supply, or a defective transistor, Q1.

A shorted base resistor will change the r-c time constant so that the base voltage of Q1 will no longer vary linearly and cause an abrupt decrease in output. If feedback capacitor C1 is open, no collector to base feedback will occur and the output variations will duplicate the input variations. If this capacitor (C1) was shorted the collector and base of Q1 will be tied together, causing Q1 to act as a diode. A defective collector supply voltage source may cause the collector voltage to be higher or lower than the required voltage. If none of the previously mentioned components is found defective and the output is low or distorted, transistor Q1 is defective.

LOGARITHMIC AMPLIFIER (ELECTRON TUBE)

Application.

The logarithmic amplifier is used in analog computers and cathode-ray tube circuits to produce an output voltage which varies as the logarithm of the input voltage.

Characteristics.

Circuit uses two electron tubes; a variable-mu pentode and a constant-current pentode.

Plate of the constant-current pentode is connected directly to the cathode of the variable-mu pentode.


Control grid of the variable-mu pentode is maintained at a constant potential by fixed bias.

Output voltage is taken between the cathode and control grid of the variable-mu pentode.

Circuit Analysis.

General. The logarithmic amplifier uses two pentodes in a circuit configuration where the plate of a constant-current pentode is directly connected to the cathode of a variable-mu pentode. The variable-mu pentode has a natural logarithmic relationship from the input to the output, where the output voltage and plate current are normally proportional to the natural logarithm base e raised to a power equal to the input voltage. In this circuit, however, the output is taken from between the cathode and grid instead of the plate, and the input is applied directly to the cathode. Regardless of the output connection, the output voltage still varies proportionally to the tube plate current, and the plate current varies logarithmically with the cathode input voltage. The input voltage applied to the cathode is the plate voltage of the constant-current tube, which varies directly in relation to the signal voltage applied to the grid of the constant-current tube. Thus, the final output voltage varies in relation to the natural logarithm ($\log_e$) of the input voltage.

Circuit Operation. The schematic of a typical logarithmic amplifier is shown in the accompanying illustration. The input signal is applied across resistor R_1 to the grid of V_1 , a constant-current, sharp cutoff pentode. Resistors R_1 and R_2 develop a bias potential between the grid of V_1 , and the cathode. Resistor R_3 is a screen grid voltage-dropping resistor, and capacitor C_1 is the screen grid bypass capacitor. Electron tube V_2 is a variable-mu pentode, which has a constant control grid voltage (E_{CC}) applied.

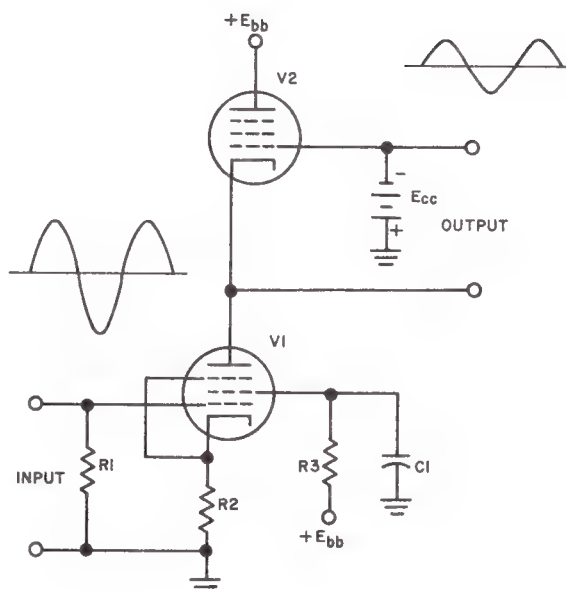

Logarithmic Amplifier

When the positive-going portion of a sinusoidally varying input voltage is applied across resistor R_1 to the control grid of V_1 , it produces a corresponding increase in plate current conduction. Plate voltage is reduced as plate current increases. The reduced plate voltage causes a reduction in the voltage applied to the cathode of V_2 . This reduced cathode voltage is equivalent to a decrease in the grid voltage of V_2 , although the grid voltage is maintained at a fixed negative bias value by a separate supply. As a result, the plate conduction of V_2 is increased and the plate voltage of V_2 is decreased proportionally. Tube V_2 is operated along the nonlinear portion of the (grid voltage-plate voltage) transfer characteristic curve of the variable-mu pentode. The resultant plate voltage

decrease causes the grid-to-cathode bias voltage to be decreased by an amount equal to the natural logarithm of the plate voltage. A bias decrease produces a more positive grid-to-cathode voltage, which is the output voltage. Since the input voltage variations cause corresponding variations in the plate currents and plate voltage of V1 and V2, the relation between the input signal and plate voltage of V2 is linear. However, the grid-to-cathode voltage (output voltage) varies at a rate equal to the natural logarithm of the plate voltage of V2. The positive-going output voltage is then proportional to the natural logarithm of the positive-going input signal.

As the negative-going portion of the signal is applied to the grid of V1, the conduction of V1 is decreased and the plate voltage is increased. The increased plate voltage of V1 results in increased voltage applied at the cathode V2. The higher cathode voltage causes a decreased plate current and a proportional increase in plate voltage of V2. The plate voltage increase causes the grid-to-cathode voltage of V2 to become more negative by an amount equal to the natural logarithm of the plate voltage. The negative-going input voltage then causes a negative-going output proportional to the logarithm of the input signal.

Failure Analysis.

No Output. An open cathode resistor, a defective pentode V1 or V2, or a defective plate supply voltage source can result in a loss of output.

Cathode resistor R2, if open, will prevent any current flow in the circuit. If pentode V1 were defective, no voltage would be applied to the cathode of V2 and thus, no voltage would appear at the output. If the proper voltages appear on the elements of V1 and there is no output, V1 is defective. If the proper voltages are present on the elements of V2 and there is no voltage on the plate of V1, pentode V2 is defective. No voltage on the plate of V2 (and the screen grid of V1) indicates that plate supply voltage source E_{bb} is defective.

Low Output. Low Output can result from low plate supply voltage, low V2 grid bias, or from a defective screen voltage-dropping resistor.

Low plate supply voltage causes the conduction of V1 and V2 to be lower than desirable and makes a lower voltage appear at the cathode of V2. Low bias voltage on the control grid of V2 also lowers the potential existing between the grid and cathode of V2. If screen grid dropping resistor R3 is open, or

larger than it should be, the conduction of V1 will not be sufficient to produce a normal output.

Distorted Output. If grid resistor R1 is defective, cathode resistor R2 is shorted, bypass capacitor C1 is defective, or pentodes V1 or V2 are defective, the output voltage may be distorted.

A shorted or open grid resistor R1, or shorted cathode resistor R2, produces a reduced bias on V1 and causes V1 to be operated on a different portion of the pentode characteristic curve. This, in turn, causes the output to vary improperly with an input signal. An open screen grid bypass capacitor C1 will allow the screen grid voltage to vary with signal current variations in the plate circuit and produce distortion in V1. If none of these conditions exists and proper voltages are available on the elements of V1, pentode V1 is probably defective. If the plate supply voltage of V1 is incorrect and the voltages on the elements of V2 are correct, pentode V2 is probably defective.

LOGARITHMIC AMPLIFIER (SEMICONDUCTOR)

Application.

The logarithmic amplifier produces an output which is proportional to the logarithm of the input. The logarithmic amplifier is used in analog computers and cathode-ray circuits.

Characteristics.

The logarithmic amplifier consists of three stages—a dc amplifier, an emitter follower, and a logarithmic circuit.

Two crystal diodes produce an output proportional to the logarithm of the applied signal.


The amplifier provides low-voltage gain.

Circuit Analysis.

General. This amplifier is especially useful in controlling and maintaining the output of an exponentially increasing input to a linear output. The amplifier, however, can be used to produce an output which is the logarithm of any input. The operation of this circuit is based on the inherent characteristic of silicon semi-conductor diodes to develop a current which is the logarithm of the signal applied to these diodes. The driving circuit for the diodes consists of an operational amplifier and an emitter-follower circuit connected in series with the collector and supply source. The operational amplifier increases signal

strength so that the logarithmic compression of the signal by the diode will not reduce the output to the point where it is unusable. The emitter-follower circuit maintains a high output impedance for the operational amplifier and prevents any load changes from greatly affecting the output impedance of the operational amplifier.

Circuit Operation. The schematic of a typical transistor logarithmic amplifier is shown in the accompanying illustration. In the circuit, resistors R1, R2, and R3 provide voltage divider base bias voltage for transistor Q1. Resistors R2 and R4 also attenuate the input voltage before applying it to the base of transistor Q1. Transistor Q1 and emitter resistor R6 comprise a series load for transistor Q2. Capacitor C1 couples the output of transistor Q1 to the logarithmic output network consisting of the parallel diode combination of CR1 and CR2.

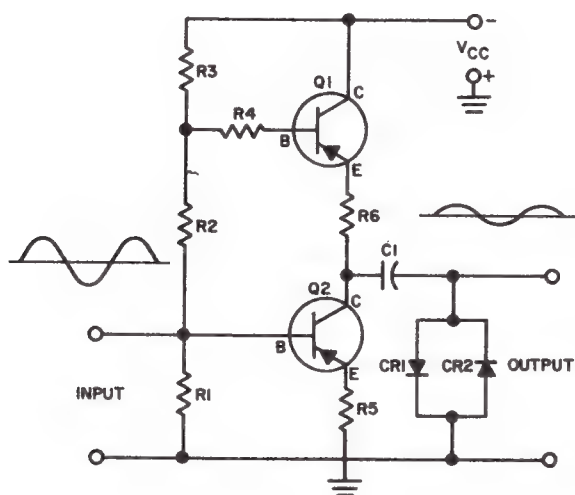

Logarithmic Amplifier

As the positive portion of a sinusoidally varying signal is applied to the input, the bases of both Q1 and Q2 are driven positive. The base of Q1 is driven to a less positive potential than the base of Q2, since the input voltage is attenuated by resistors R2 and R4. The positive-going input voltage decreases the forward bias of both transistors, and the emitter-to-collector current of both transistors decreases. As a result of decreased collector current, the collector voltage of Q2 attempts to increase (rise negatively).

Since the collector voltage of Q1 remains at the negative collector supply voltage value, the decreased emitter current increases the internal resistance of Q2 and causes the emitter of Q1 to become more positive. The voltage at the collector of Q2 then decreases. This, in effect, helps to decrease the total collector voltage swing of Q2 without lowering the supply impedance. The reduced collector current of Q2, however, tends to allow more current to be shunted around Q1 through CR2 without decreasing the supply impedance. The output voltage produced across CR2 is proportional to the natural logarithm of the current flowing through CR2.

As the sine wave reaches its positive peak and swings negative, the input voltage applied to the bases of Q1 and Q2 goes negative. Thus, the forward bias of both transistors increases, and the forward bias of Q1 is somewhat less than the forward bias of Q2 as a result of the attenuation provided by resistors R2 and R4. The current flowing from emitter to collector of each transistor now increases. The current increase of Q2 would normally be much greater than the current increase of Q1. The collector voltage of Q2 becomes more positive by the increased voltage drop across resistor R6. However, the internal impedance of Q1 is lowered, reducing the drop across Q1, and the effective supply voltage at the input to R6 increases. Thus, the collector voltage swing of Q2 is reduced. The collector output voltage swing is coupled through capacitor C1 to the diodes, and since it is positive-going, CR1 now conducts and CR2 ceases to conduct. The output voltage produced across CR1 is proportional to the natural logarithm of the current flowing through it.

Semiconductor diodes provide a good logarithmic range when the current flowing through the diode is larger than the saturation current of the diode. The output voltage is then proportional to the natural logarithm of the quantity formed by the instantaneous forward current through the diode (i_F) plus the saturation current value (I_s), divided by the saturation current. This quantity is added to the diode voltage drop which is the product of the current through the diode (i_F) and the actual resistance of the diode (R_d). This proportionality is expressed mathematically as:

$$V_o = \log_e \frac{(i_F + I_s)}{I_s} + i_F R_d$$

Hence a logarithmic output is produced.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of multiplier resistance employed on the low-voltage ranges of a conventional volt-ohmmeter. Be careful also to observe proper polarity when checking continuity with an ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. An output may not be produced if the collector supply is defective, if either transistor is defective, if the collector load resistor, or emitter bias resistor is open, if the coupling capacitor is open, or if both diodes are defective.

A defective collector supply source (V_{CC}) prevents any voltage from being available on the collectors of either transistor. If either transistor Q1 or Q2 is defective, no current can flow in the circuit. Likewise, current cannot flow in the circuit if the collector load resistor of Q2 (R6) or emitter bias resistor (R5) is open. An open coupling capacitor, C1 prevents current from flowing through either diode. If there is no output developed and if none of the previously mentioned components is defective, both diodes CR1 and CR2 are probably defective.

Low or Distorted Output. A low or distorted output may be produced if any of the biasing resistors is defective, the coupling capacitor C1 is shorted, either diode is defective, or if the collector supply voltage source is defective.

If any of the bias resistors R1, R2, R3, R4 is shorted, the bias voltage available for Q1 and Q2 is incorrect. If resistor R2 or R4 is open, the input signal will not be applied to Q1. A shorted coupling capacitor C1 allows the dc voltage on the collector of Q2 to be applied to the crystal diodes. If either diode CR1 or CR2 is defective, a logarithmic output will only be produced for one half of the input signal. A low supply voltage will prevent the correct supply voltage from being applied to either collector and produce a lower than normal output.

SUMMING AMPLIFIER (ELECTRON TUBE)

Application.

The summing amplifier is an operational amplifier used in analog computer circuitry to develop an output voltage which is the sum of two or more input voltages of the same polarity and phase.

Characteristics.

High stabilized gain.

Negative feedback is employed.

Fixed or self bias may be employed.


Input and output networks are resistive.

Amplifier stages are directly coupled.

Circuit Analysis.

General. A summing amplifier is a direct-coupled amplifier with high stabilized gain. It produces an output voltage that is equal or proportional to the sum of the applied input voltages, which are usually of the same phase and polarity. The input voltages are applied to the grid of an electron tube through equal input resistors forming a summing network. The combined input voltages are inverted and amplified by the tube. A portion of this voltage is fed back to the input of the amplifier through a resistive feedback network. This feedback voltage stabilizes the output and maintains a relatively constant gain.


Circuit Operation. The accompanying illustration shows a summing amplifier in symbolic one-line form. Using this type of circuit representation, the amplifier is indicated by an isosceles triangle. The base of the triangle represents the input of the amplifier and the vertex represents the output of the amplifier. Resistors R1, R2, and R3 form the summing network which provides the input signal to the input of the amplifier. Resistor R4 forms the feedback network for the amplifier. The one-line type of diagram may use a vacuum tube, transistor, or integrated circuit as the amplifier. The symbolic representation is used to show the relation among the input, the output, the feedback network, and the amplifier in simplified form.

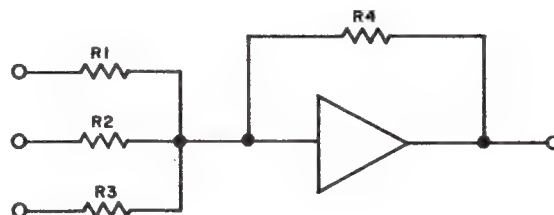

Summing Amplifier Circuit Representation

In the following schematic diagram, the operational amplifier uses triode V1, Resistors R1, R2,

R3, and R6 form a resistive summing network which provides the input signal to the grid of V1. Resistor R8 is a cathode bias resistor bypassed by capacitor C1. Resistor R7 is the plate load resistor from which the output voltage is obtained. Resistor R4 is the feedback resistor which returns a portion of the output voltage to the input to prevent distortion and drift. Fixed negative bias voltage is applied through grid-isolating and voltage-dropping resistor R5. Resistor R6 forms a bias bleeder network with R5 to stabilize the fixed bias voltage on the grid of V1 and completes the summing network path to ground.

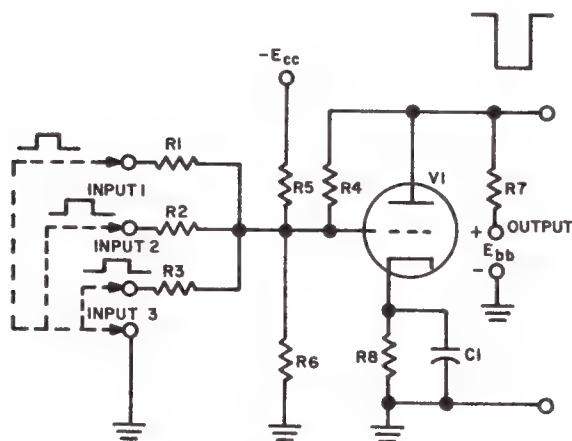

Summing Amplifier Circuit

Voltages of the same polarity and phase are applied to each input simultaneously. The total value of the added input voltages appears at the grid of V1, and produces an increased plate current, which is proportional to the summed input voltage. The plate (and output) voltage decreases in relation to the plate current increase, creating a negative voltage swing. A portion of this negative plate voltage swing is returned to the grid of V1 through feedback resistor R4. This ensures that any distortion or drift existing in the input signal at the grid is canceled by feedback 180° out of phase with the input. The positive plate voltage fed back to the grid of V1 through R4 requires that a fixed negative bias voltage be applied to the grid to prevent the grid from going positive and driving V1 to saturation. A negative voltage source supplies the added bias to the grid of V1 through

resistor R5. Resistor R6 prevents a grid-current initiated voltage drop across R5 from changing the bias voltage at the grid of V1.

When the input voltage swings in a negative direction or reduces, the plate current also decreases. The decrease in plate current causes the plate (output) voltage to rise toward the supply value, creating a positive swing. A portion of the increasing plate voltage swing is fed back to the grid to cancel again any input signal distortion or drift.

The summing amplifier depends upon the feedback network to provide a constant gain despite any variation in tube characteristics. Although a high gain is produced by the tube, the feedback connection reduces the overall gain obtained by the amount of feedback. When an input voltage is applied to either R1, R2, or R3 it will cause a current to flow through the respective resistor and a voltage will be applied to the grid of V1. When this input signal increases, the first small change in voltage is amplified by V1 and appears in the output circuit. In turn, a portion of this output voltage is fed back through R4, and being out of phase with the input, decreases the total input voltage at the grid. The decrease in input is amplified and fed back again to increase the amplitude of the input voltage. This process continues until the amplifier reaches a point of stable operation. If the input resistance is equal to the feedback resistance, the output voltage is equal to the input voltage, except that the output polarity is reversed (provided that an odd number of stages is used). Hence, if the input voltage is doubled, the output voltage will double. The amount of feedback used determines whether or not the output signal will be equal to, greater than, or less than the actual value of input voltage. So, depending upon design, the summing amplifier may not actually amplify the total signal, but it will produce an output which does represent the sum of the applied input voltages.

Failure Analysis.

No Output. Lack of plate voltage, a defective tube, an open input circuit, or lack of input signal can cause a loss of output. If plate load resistor R7 is open, no voltage will appear on the plate of V1. An open cathode resistor, R8, will prevent the tube from operating. Excessive bias caused by a shorted R5 can produce plate current cutoff and no output. Conversely, if R5 is open, a high positive bias voltage will be fed back from the plate of V1 to the grid and

cause heavy plate current flow. In this case, the final value of plate current will be determined by cathode resistor R8, the plate voltage of V1 will be extremely low, and a large voltage drop will occur across plate load resistor R7. In this instance, although an apparent output will be obtained, it will be constant, and the circuit will no longer act as an adder. If bias and plate voltages measure normal and input voltage is present on the grid of V1, but there is no output, the tube is probably defective. For the input circuit to be open, resistors R1, R2, and R3 must simultaneously be open. Check for the proper resistance value and continuity.

Low Output. A low output is an inaccurate output, and can be caused by a defective input circuit, improper bias and plate voltages, as well as a defective tube. Check R1, R2, R3, and R6 for continuity and resistance. Measure the cathode, grid, and plate voltages with no input applied. No cathode voltage indicates the possibility that capacitor C1 is shorted or V1 is defective. Improper grid bias voltage indicates that R4, R5, or R6 are defective, or that the bias supply is at fault. Improper plate voltage indicates that R4, R7, or V1 can be defective.

Distorted Output. In the summing amplifier, an inaccurate output can be considered as a distorted output. Usually a change in feedback resistor R4, or a change in the values of input resistors R1, R2, or R3 are the cause, or the tube is defective. Check the values of the resistors to make certain that they are normal. Also check the bias and plate voltage sources to make certain that the external circuits are not at fault.

SUMMING AMPLIFIER (SEMICONDUCTOR)

Application.

The summing amplifier produces an output voltage which is the sum of two or more input voltages of the same polarity and phase. The summing amplifier is primarily used in analog computers, and in control and instrumentation circuitry.

Characteristics.

A number of input signals are applied to produce a single output.


Resistive input summing networks are used.

Negative feedback is used.

Circuit Analysis.

General. A summing amplifier uses a direct-coupled amplifier with high stabilized gain. It produces an output voltage that is proportional to the sum of the applied input voltages. Each input voltage has the same phase and polarity as the other input. The input voltages are applied to the base of a transistor through a summing network. The combined signals are inverted and amplified across a common load resistor. A portion of this output voltage is fed back to the base of the transistor as negative feedback. The feedback voltage stabilizes the output and maintains a relatively constant gain.

Circuit Operation. The schematic diagram of a typical transistorized summing amplifier is shown in the accompanying illustration. Resistor R1, R2, and R3 together with R6, form a resistive summing network, which provides the total input signal to the base of transistor Q1. Resistor R4 is the collector-to-base feedback resistor and together with R6 supplies base bias to Q1. Resistor R5 is the collector load resistor.

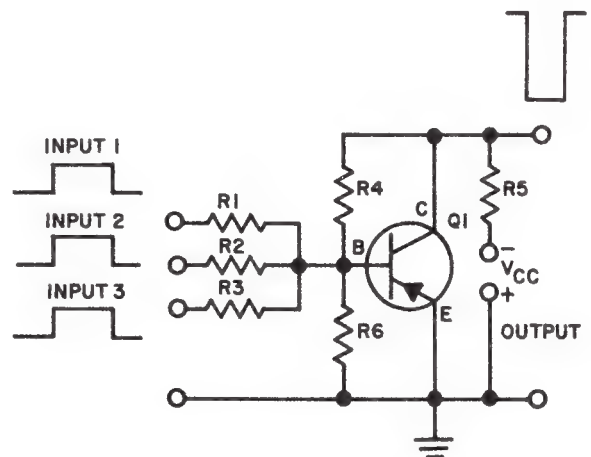

Summing Amplifier

Separate positive signal voltages of the same phase and frequency are applied to resistors R1, R2, and R3. The total sum of these voltages appears across R6 (which completes the path to ground) at the base of Q1, and reduces the normal forward bias of the transistor. The emitter and collector currents are thereby reduced, allowing the collector voltage to rise and

approach the negative supply voltage value. A portion of this negative voltage swing is returned to the base of Q1 through feedback resistor R4. This negative feedback voltage cancels any distortion or drift existing in the combined input voltage since it is 180° out of phase with the input signal.

When the input voltage swings negative, the combined voltages at the base of Q1 develop an increased forward bias. As a result, the emitter and collector currents increase. The increased collector current flow through resistor R5 causes an increased voltage drop across the load. The collector of Q1 is thus driven to a less negative potential (more positive). A portion of this positive collector voltage swing is fed-back to the base of Q1 through R4 where it again cancels any input signal distortion or drift. The output voltage taken between collector and ground is the amplified output which is proportional to the sum of all of the inputs.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of multiplier resistance employed on the low-voltage ranges of conventional volt-ohmmeters. Be careful also to observe proper polarity when checking continuity with an ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. A lack of output may result if all inputs are open, the collector load is defective, the collector supply is defective, or if transistor Q1 is defective or improperly biased.

If input resistors, R1, R2, and R3 are all open, no input voltage can be applied to the base of Q1. An open collector load resistor, R5, will prevent any collector supply voltage from appearing at the collector of Q1. If the collector supply voltage source, V_{CC} is defective, no voltage will appear at the collector of Q1. If none of these components is found to be defective and there is no output, transistor Q1 is probably defective; or R4 may be open, causing loss of forward bias.

Low or Distorted Output. The output of the summing amplifier is low or distorted if any of the inputs is defective, if the feedback network is defective, if the collector supply is defective, or the transistor is defective.

If one or two of the input resistors are open, only the signals applied to the remaining input resistors

will be applied to the base of Q1 across R6. If any or all of these resistors are shorted, the input signals will not be properly summed before being applied to the base of Q1. If feedback resistor R4 is open, any distortion of the input signal will not be corrected before being applied to the base. Transistor Q1 will act as a diode if resistor R4 becomes shorted. The input variations will then be rectified and appear as an average steady output voltage. The collector voltage may be higher or lower than the required voltage, if collector supply voltage source V_{CC} is defective. If the components are not found to be defective with abnormal output, transistor Q1 is probably defective.

RING-BRIDGE AMPLIFIER (SEMICONDUCTOR)

Application.

The ring-bridge amplifier is used to detect and amplify a double-sideband suppressed-carrier signal or a single-sideband signal.

Characteristics.

Requires a ring-bridge detector and a transistor amplifier.

Two stages are needed to provide the dual function of this circuit.

Transformer coupling is used between stages, but the output stage is direct-coupled to the load.


A reference oscillator input is required to produce an output.

Circuit Analysis.

General. The ring-bridge amplifier is a two-state circuit consisting of a ring-type rectifier or detector, transformer-coupled into a dc operational amplifier circuit. The ring-type detector appears in the form of a bridge rectifier, from which the circuit name is derived. A reference oscillator provides a simulated carrier which is transformer-coupled between the center taps of the input and output transformers of the detector bridge, so that an in-phase signal may be coupled to each pair of diodes. No output is obtained as long as the simulated carrier signal alone is applied, since in the balanced bridge circuit equal conduction between opposite diodes occurs, and equal current flowing in opposite directions in the two halves of the same transformer effectively cancels any output. The applied sideband input signal beats with the simulated carrier, and results in the addition to and subtraction

of the input signal from the oscillator signal, causing each diode to conduct alternately on opposite half cycles. The output produced by the bridge diodes is coupled through the output transformer of the detector to the input of the second stage, where the detected signal is inverted and amplified.

Circuit Operation. A typical ring-bridge amplifier schematic is shown in the accompanying illustration. Transformer T1 is the r-f (or subcarrier) input transformer while T2 is the reference oscillator transformer. Transformer T2 is connected between the center taps of T1 and T3. Transformer T3 is the output transformer of the detector stage. Diodes CR1 and CR3 form one group of bridge rectifiers and CR2 and CR4 form the other group. The diode pairs conduct simultaneously for in-phase signals and alternately for push-pull signals. Resistor R1 is an emitter stabilization resistor for Q1. Resistor R2 is the collector load resistor of Q1. The collector supply voltage is V_{CC} and V_{EB} is a separate emitter bias voltage source.

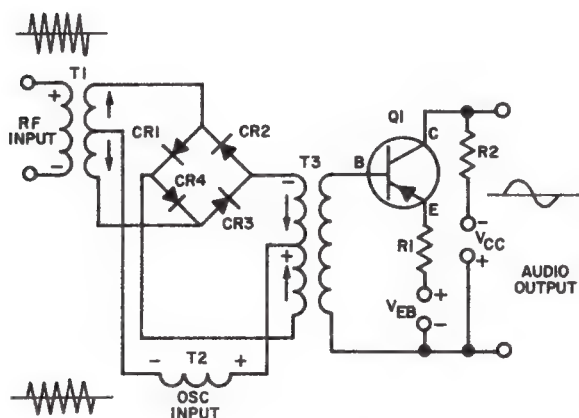

Ring-Bridge Amplifier

When no input signal is applied, except the reference signal from the oscillator, the center tap of T3 is driven positive, and the center tap of T1 is driven negative. Diodes CR2 and CR4 conduct because of the positive voltage applied to the anodes. Electron flow is from the negative terminal of T2 through the lower half of T1 secondary and the cathode to anode of CR4, back through the lower half of T3 primary to the positive terminal of T2. Current also flows through the top half of the secondary of T1 to the

junction of CR2 and CR1. Diode CR2 is forward-biased and conducts, causing current to flow through the top of T3 primary winding back to the positive end of T2. Because of the equal and opposite currents flowing through each half of the secondary of T1 and the primary of T3, the transformer windings cancel, preventing any voltage from being induced into either the primary of T1 or the secondary of T3. As a result, no input is applied to the operational amplifier and no output is produced. When the polarity on the secondary of T2 reverses, a similar situation arises with diodes CR1 and CR3 conducting. In this case, current flows from the center tap of T3 to the cathodes of CR1 and CR3, and to the plates of CR2 and CR4. CR1 and CR3 conduct, causing equal currents to flow through opposite ends of T1 to the center tap. The currents through both halves of the primary of T3 are equal, but opposite in polarity, which again causes the opposing induction fields set up in T3 to cancel, resulting in no output from the detector and no output from the amplifier.

Since the reference oscillator amplitude is stronger than that of the incoming r-f sideband signals, the polarity of the reference oscillator on the diodes controls conduction. Assume that a push-pull r-f signal is applied to the input of T1, developing a voltage across the secondary of T1 which is negative at the top and positive at the bottom. The reference oscillator also assumed to be applying a signal which normally keeps diodes CR2 and CR4 conducting; when both signals add instantaneously, CR2 then conducts more and CR4 conducts less, developing unequal currents flowing from each end of T3 to the center tap. In this case, a greater current flows from the top of T3 to the center tap as a result of the greater conduction of CR2. At the same time, less current flows from the bottom of T3 to the center tap as a result of the lesser conduction of CR4. The result of these unbalanced currents is that the top of T3 becomes more negative with respect to the bottom of T3. The induced voltage in the secondary of T3 is positive at the top of the winding with respect to the bottom. Since the top of the secondary of T3 is connected directly to the base of Q1, the positive input voltage reduces the forward bias of Q1. Q1 conducts less as a result of this reduced forward bias. The smaller emitter-to-collector current of Q1 results in less collector current flowing through R2, producing a smaller IR drop across R2. The smaller IR drop across

R2 causes the voltage on the collector of Q1 to rise toward the collector supply voltage value.

The result of a positive-going input signal riding on a reference carrier input is a negative-going output, which is amplified. The reference carrier is automatically canceled so that it does not appear in the output.

A negative-going input signal riding on a reference carrier input produces the opposite action. Thus, diode CR4 conducts more, while diode CR2 conducts less.

The potential across the primary of T3 now reverses, inducing a voltage across the secondary of T3 which is 180° out of phase with the primary voltage. Hence, a negative voltage is now applied to the base of Q1, producing a greater forward bias; consequently, the greater emitter-to-collector current produces a greater IR drop across R2, and a positive-going collector and output voltage. Again, the reference carrier signal is automatically removed by the cancelling action in T3, previously described.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of multiplier resistance employed on the low-voltage ranges of conventional volt-ohmmeters. Be careful also to observe proper polarity when checking continuity with an ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. The output may be lacking if transformer T1 and T3 is defective, if the collector load resistor is defective, if the emitter stabilizing resistor is open, if the bias voltage source is open, if the collector supply source is defective, if any of the four diodes is defective, or if transistor Q1 is defective.

If transformer T1 is completely open or completely shorted, the input signal will not be

coupled to the detector circuit and no input will be applied to the amplifier circuit. If transformer T3 is completely open or completely shorted, the detected signal can not be applied to the amplifier. A shorted or open collector load resistor, R2 prevents any supply voltage from being applied to the collector of Q1. Collector voltage is prevented from being applied to the collector also, if collector supply voltage source V_{CC} is defective. If emitter stabilization resistor R1 is open, the transistor amplifier circuit sees an open emitter circuit and no current will flow through Q1. An open emitter to base bias voltage source, V_{EB} , will also prevent current flow in the amplifier circuit. If diodes CR1, CR2, CR3, and CR4 are defective, no potential difference can be developed across T3, and thus no input will be applied to the base of Q1. If one of these components is defective, and there still is no output developed, transistor Q1 is probably at fault.

Low or Distorted Output. A low or distorted output can result from a defective reference carrier oscillator transformer T2, a defective diode, a defective transformer T1 or T3, a defective collector supply voltage source, a defective emitter bias source voltage, or a defective transistor.

If reference carrier oscillator transformer T2 is defective, the reference carrier signal will be absent and prevent the detector bridge from being properly balanced. If any of the diodes in the bridge is shorted or open, proper current will not flow through the diode and the proper potential difference will not be developed across the primary of T3. If either transformer T1 or T3 is partially shorted, improper voltage will be applied to the detector bridge circuit or to the amplifier circuit. A defective emitter bias source will cause improper bias to be developed and produce distortion. If collector supply source V_{CC} is defective, improper voltage will be applied to the collector of Q1. If these components are not found to be defective and a low or distorted output is developed, transistor Q1 is probably defective.

SECTION 6

OSCILLATORS

PART 6-1. ELECTRONIC

ARMSTRONG (TICKLER-COIL) OSCILLATOR (ELECTRON TUBE)

Application.

The Armstrong oscillator is used to produce a sine-wave output of constant amplitude and fairly constant frequency within the r-f range. The circuit is generally used as a local oscillator in receivers, as a single source in signal generators, and as a variable-frequency oscillator over the medium- and high-frequency ranges.

Characteristics.

Utilizes an L-C tuned grid circuit to establish the frequency of oscillation. Feedback is accomplished by mutual inductive coupling between the tickler coil and the L-C tuned grid circuit.

Operates Class C with automatic self-bias.

Frequency stability is fair.

Output amplitude is relatively constant.


Circuit Analysis.

General. Oscillations of a tuned circuit will tend to die out at an exponential rate and will finally cease, unless energy is replaced at regular intervals. For oscillations to be sustained, sufficient energy must be supplied to overcome circuit losses. The use of an electron tube as an amplifier provides the additional energy necessary to sustain oscillations. The energy applied to the tuned circuit must be of the correct phase relationship to aid the initial oscillations and of sufficient amplitude to overcome circuit losses in the tuned circuit.

The circuit used to provide this type of feedback is called a *regenerative circuit*, and the energy supplied


is called *positive feedback*. In the accompanying circuit schematic the tuned L-C circuit is designated as L1, C1; the tickler (feedback) coil is designated as L2.

Circuit Operation. The accompanying circuit schematic illustrates a triode electron tube in an L-C Armstrong oscillator circuit. Inductance L1 and capacitor C1 form the resonant grid circuit. Inductance L2 is the plate, or tickler, coil and is mutually coupled to L1, to couple a feedback voltage to inductance L1 by transformer action. Capacitor C2 and resistor R1 form an R-C circuit which is used to develop the operating bias. Capacitor C3 functions as an r-f bypass to place the B+ terminal of tickler coil L2 at signal ground potential. Resistor R2 isolates the B+ line from the r-f signal and also serves to reduce the input voltage applied to the oscillator circuit. Capacitor C_c is the output coupling capacitor.

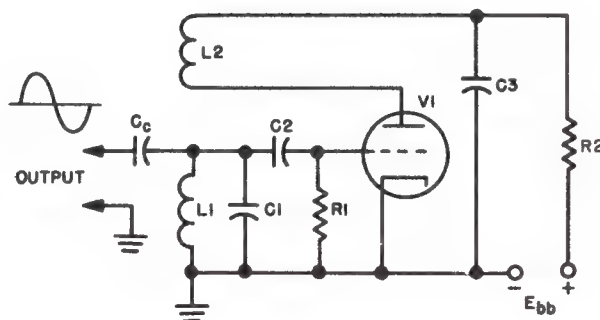

L-C Armstrong (Tickler-Coil) Oscillator

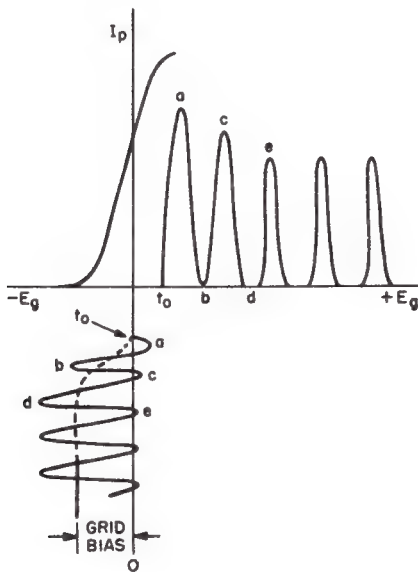For the following discussion of circuit operation, refer to the accompanying illustration of oscillator grid-signal voltage and plate-current waveforms.



Theoretical Grid-Voltage and Plate-Current Waveforms

Initially, the tube is at zero bias (t_0 on waveform illustration) to permit the circuit to be self-starting. When input power is applied to the circuit, the tube conducts because of the lack of operating bias. As the plate current increases through tickler coil L2, an expanding magnetic field is built up around the tickler coil. This expanding field causes an increasing voltage to be induced in inductance L1 of the tuned circuit, and this voltage is of such polarity that the grid of V1 is made positive with respect to the cathode. The positive grid condition increases the flow of plate current, which further increases the field about tickler coil L2; consequently, the voltage induced in inductance L1 increases and the grid is drawn further in the positive direction. This process continues until saturation is reached, at which time no further increase in plate current can take place (point *a* on waveforms).

During the period of time that a charging voltage is induced in inductance L1, capacitor C1 changes to maximum; also, capacitor C2 receives a charge as the result of grid-current flow through the low internal cathode-to-grid resistance of the tube.

When the plate current reaches saturation, a steady (unchanging) magnetic field is produced about tickler coil L2, and, as a result, a voltage is no longer induced

in inductance L1. With no induced voltage present, capacitor C1 begins to discharge through inductance L1, and capacitor C2 begins to discharge through resistor R1 (and L1). The positive voltage on the grid of V1 decreases as capacitor C1 discharges through inductance L1, and this decrease in the grid voltage causes the plate current to decrease below the saturation value. The decrease in plate current through tickler coil L2 causes the magnetic field about the tickler coil to decrease and start to collapse, and thus causes an increasing voltage to be induced in inductance L1. However, the polarity of the induced voltage is reversed from that originally induced in L1 when the magnetic field about tickler coil L2 was expanding. Hence, the induced voltage causes the grid of V1 to be driven negative with respect to the cathode, and the plate current is further decreased, causing the magnetic field about tickler coil L2 to collapse completely. As this occurs, the grid of V1 becomes increasingly negative until a voltage is reached which prevents any further decrease in plate current (point *b* on waveforms). (The voltage induced in L1 during this time also aids the discharge of C1.)

At this instant, capacitor C2 starts to discharge through resistor R1 (and L1), decreasing slightly the negative potential existing between the grid and cathode of V1. Also, capacitor C1 discharges through inductance L1, producing an expanding magnetic field about inductance L1; when capacitor C1 is completely discharged, the magnetic field begins to collapse. The collapsing magnetic field about inductance L1 again produces a voltage across the inductance which charges capacitor C1 and also drives the grid of V1 in a positive direction. As the grid of V1 becomes positive with respect to the cathode, plate current begins to flow through tickler coil L2. The magnetic field produced about tickler coil L2 again increases and induces a voltage in inductance L1, which drives the grid still further into the positive condition. Grid current again flows through the internal cathode-to-grid resistance of the tube to produce a negative charge on capacitor C2. Plate current again rises to maximum, at which time no further increase in plate current can take place (point *c* on waveforms).

The entire process repeats as described above, with the bias voltage continuing to build up across capacitor C2 until a steady value of Class C bias, effectively across resistor R1, is reached. The interchange of

energy at the resonant-frequency rate between inductance L1 and capacitor C1 of the tank circuit maintains the oscillations during the period of time that plate current is cut off and no energy is supplied to the tuned circuit through the tickler-coil feedback circuit.

As oscillations build up, the maximum signal across the resonant circuit becomes increasingly greater. Note that the grid-leak-and-capacitor combination, R1 and C2, is used to develop the operating bias, to permit Class C operation of the tube. When the circuit is placed in operation, a stable operating point is quickly reached where the positive signal peaks are of sufficient amplitude to cause grid current to flow and to charge the grid capacitor, C2. Momentarily, when the signal is less positive, grid current ceases to flow, and capacitor C2 discharges slowly through grid-leak resistor R1. Since the value of R1 is large, only a small amount of charge is lost by capacitor C2 before the signal again is sufficiently positive to cause the grid to again draw current. As a result of this automatic charge-discharge action, an average value of negative bias, approximately the value to which capacitor C2 is being charged, is developed across R1, between the grid and cathode. Whenever the signal amplitude tends to increase, additional grid current flows through the internal cathode-to-grid resistance of the tube, and, therefore, capacitor C2 is charged to a higher value. Consequently, the bias voltage also increases, and the resulting effect is to decrease the gain of the tube. As the gain of the tube decreases, the output-signal level also decreases and returns to approximately its original amplitude. Similarly, when the signal amplitude tends to decrease, there is a decrease in bias voltage and an accompanying increase in the gain of the tube. As the gain of the tube increases, the output-signal level also increases and returns to its original amplitude. Thus, through the regulating action of grid-leak bias, the circuit operation is stabilized, and the amplitude of the output is held essentially constant.

The oscillator output frequency is determined primarily by the values of inductance L1 and capacitance C1 at resonance


$$(f_0 = \frac{1}{2\pi\sqrt{LC}}),$$

although interelectrode capacitances of the electron tube and distributed capacitances and inductances of

the circuit also have an effect upon the oscillator frequency. In most circuits a variable capacitor is used to change the frequency; however a variable inductance can be used with a fixed capacitor to accomplish the same purpose.

The oscillator output, which is taken from the tuned circuit, is generally capacitively coupled (C_c) to the associated load circuit; however, inductive coupling may also be used with the output coupling coil being mutually coupled to L1 near its ground end.

Tuned-Plate Version. The proceeding circuit description covered the basic Armstrong circuit, in which the tank coil is in the grid circuit (tuned grid) and the tickler coil is in the plate circuit. Another circuit version in which these conditions are reversed is called the tuned-plate circuit. In this circuit, the tank is in the plate circuit and the tickler (feedback) coil is in the grid circuit. The operation of this oscillator is identical to that of the tuned-grid circuit, except for limitations imposed by coupling between the plate and grid. This coupling limits the range of oscillation in the tuned-grid version, but not in the tuned-plate version. Actually, the tuned-plate oscillator is considered less susceptible to frequency changes caused by power supply voltage changes than the tuned-grid oscillator. The schematic of the tuned-plate circuit is shown in the following illustration.

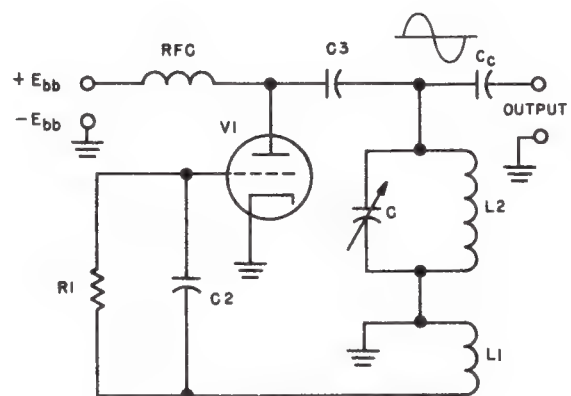


Tuned-Plate Armstrong Oscillator

The parts in the tuned-plate oscillator are labeled the same as in the illustration of the tuned-grid oscillator, for comparison. The differences are the use of shunt plate feed in the tuned-plate circuit instead of

what is essentially series plate feed in the tuned-grid circuit and the use of series grid-leak bias instead of shunt grid-leak bias. Actually, the use of shunt or series feed does not change the method of operation; it merely illustrates possible circuit variations. Grid-leak components R1 and C2 operate in the same manner as described for the tuned-grid version, and C3 is a plate blocking and coupling capacitor instead of an r-f bypass. Note that plate dropping resistor R2 is replaced by radio-frequency choke RFC, which keeps the r-f from being shunted to ground via the power supply filter capacitors. When the circuit is energized, the flow of plate current produces tank circuit variations through L2, and an in-phase voltage is fed back through grid (tickler) coil L1 to sustain feedback exactly as described under L-C circuit operation for the tuned-grid circuit previously discussed. The grid leak formed by R1 and C2 controls the amplitude and grid bias.

Detailed Analysis. Since the oscillator is considered to be a Class C amplifier with a feedback loop, a rigorous mathematic analysis is complex because the circuit operation is inherently non-linear. The analysis can be greatly simplified by using the equivalent plate circuit, together with a few assumptions. This method of analysis is helped in determining the conditions necessary to produce sustained oscillations and in determining the basic frequency of oscillation. With this approach, it is customary to neglect the flow of grid current, but to bear in mind that its effect must be considered and the final results modified to take the grid current into account. Actually, losses due to grid current can be treated as an equivalent loss in the tuned circuit.

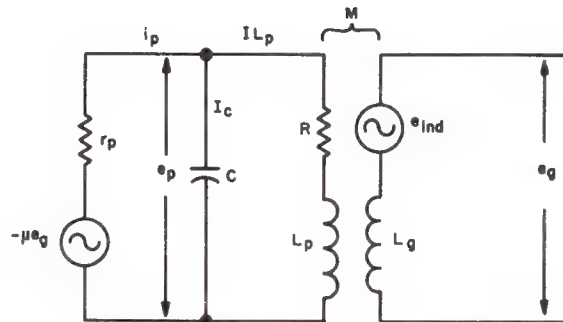The ac equivalent circuit for the tuned plate oscillator is shown in the following illustration. Assuming that the currents are sinusoidal and neglecting grid current flow, Kirchhoff's laws and Thevenin's theorem can be applied to this circuit to obtain the limiting parameters that determine oscillation and frequency.



Tuned Plate Equivalent Circuit

Mathematic analysis of the equivalent circuit for the tuned-plate oscillator shows that the critical value of coupling is:

$$M = \frac{L_p + CRr_p}{\mu} \quad (1)$$

which gives the minimum value that M can have and still allow the circuit to oscillate. To satisfy this condition, M must be possible and:

$$g_m = \frac{RC}{M} + \frac{L_p}{Mr_p} \quad (2)$$

Thus, the coupling between grid and plate coils must exceed the minimum value indicated in equation (1), and must have the sign to produce a positive grid voltage component when I_{Lp} is increasing (this is the condition required for regenerative feedback). The frequency of oscillation is determined by:


$$\omega = \sqrt{\frac{R + r_p}{L_p C r_p}} = \omega_0 \sqrt{1 + \frac{R}{r_p}} \text{ or } f = \frac{1}{2\pi\sqrt{LC}} \cdot \sqrt{\frac{R + r_p}{r_p}}$$

It is evident from (3) that the frequency of oscillation is affected to some extent by the resistance of the load, as well as the plate resistance of the tube. With $r_p \gg R$ to provide better frequency stability (which condition normally exists), we can say that for all practical purposes, or

$$f = \frac{1}{2\pi\sqrt{LC}},$$

where C includes all of the stray and distributed capacitance that tunes L_p .

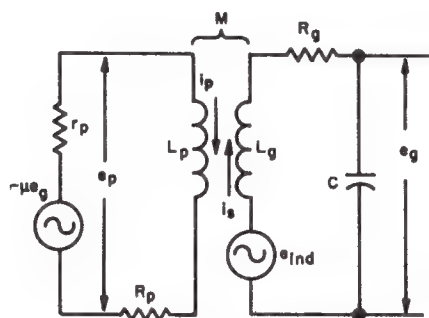A similar analysis of the tuned-grid circuit can also be made by using the following equivalent circuit.



Tuned-Grid Equivalent Circuit

In this instance it can be demonstrated that the requirement for oscillation is:

$$g_m = \frac{RC}{M} + \frac{M}{L_p r_p} \quad (4)$$

Since the quantity M appears in the denominator of one term and in the numerator of the other, the value of g_m is large for both high and low values of M , with a minimum value existing somewhere between. This is to say that in the tuned-plate circuit, while there is a critical value of coupling below which oscillation will not occur, there is no limit to the maximum value of coupling; although plate current and output may be reduced as a consequence, oscillation will still occur. For the tuned-grid circuit there exists both a lower and an upper limit; thus if the value of coupling is too low or too high, the circuit will not oscillate. This upper limit on M could be a practical disadvantage;

however, it appears to be of academic interest, since it is only true for large values of L_p and C . That is, it actually applied only to low r-f or audio frequencies. At the higher radio frequencies the effect of tube capacitance and distributed circuit capacitance makes the value of M required to satisfy this condition so high that it is impractical or impossible to obtain. Thus, although there is a difference between the plate and grid-tuned circuits, theoretically, it is of no practical consequence.

The frequency of oscillation for the tuned-grid oscillator is given as:

$$f = \frac{1}{2\pi\sqrt{C(L_g r_p + L_p R_g)}} \quad (5)$$

From this expression it may be seen that if R_g is very small as compared with r_p , the quantity $(L_g r_p + L_p R_g)$ is nearly identical with $L_g r_p$. Equation (5) may then be rewritten as:

$$f = f_o = \frac{1}{\sqrt{2\pi L_g C}} \quad (6)$$


The tuned-grid circuit is similar to the tuned-plate version in that the ratio r_p/R should be as large as possible for good frequency stability. One other fact may readily be seen if equation (5) is rewritten as:

$$f = \frac{f_o}{\sqrt{1 + \frac{L_p R_g}{L_g r_p}}} \quad (7)$$

where f_o is the same as in equation (6).


Since the operating frequency of the oscillator is equal to the tank resonant frequency divided by a number slightly greater than unity, the operating frequency is slightly less than the natural resonant frequency of the tank circuit. On the other hand, the tuned-plate version has a higher frequency of oscillation than its tank circuit, as shown by equation (3). Thus, at the operating frequency, the tuned-grid tank appears as an inductive reactance, and the tuned-plate tank appears as a capacitive reactance (neglecting the effect of resistance, which is of academic interest only).

Vector Diagram. It is sometimes more helpful to use vectors to show the relationships of the various currents and voltages in the circuit. The following figure shows the vector diagram for the tuned-plate circuit. In this figure, The voltage $-\mu e_g$ is used as a reference. e_g is about 180° out of phase with $-\mu e_g$, as indicated by the negative sign preceding the real quantity $-\mu e_g$. The direction of i_{LP} may be established from the fact that e_g (the voltage induced in L_g) equals $-j\omega M i_{LP}$, and must lag i_{LP} by 90° because of the $-j$ coefficient. Similarly, it can be seen from the ac equivalent circuit, that i_{LP} will lag e_p by something less than 90° because of the resistance R in series with the coil. The amount of phase difference between e_p and i_{LP} will depend on the Q of the coil, being closer to 90° with higher values of Q ($\omega L/R$). This makes e_p lag $-\mu e_g$ by some small angle, which is dependent on the circuit Q . i_c since it is considered purely capacitive, will lead e_p by 90° . The vector sum of $i_p r_p$ and e_p must equal $-\mu e_g$. For this to be true, $i_p r_p$ must lead $-\mu e_g$ by some small amount, and since the current through a resistance is in phase with the voltage drop across it, i_p may be shown as leading $-\mu e_g$. Thus with i_p having a leading phase angle, the tuned plate circuit is shown to be capacitive as was also proven in the mathematical analysis. Note that i_p is the vector sum of i_c and i_{LP} ; therefore, i_c must be the larger quantity.

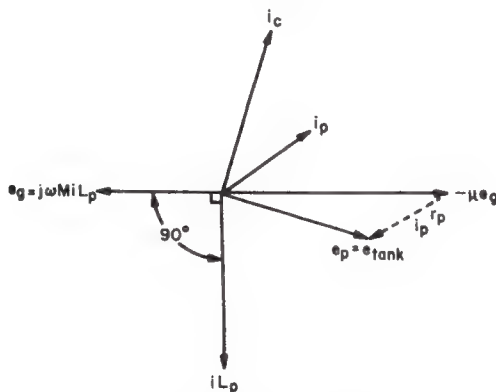

Tuned-Plate Vector Diagram

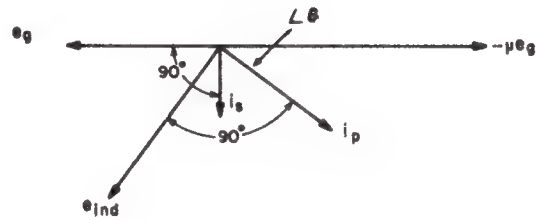The tuned grid circuit may be similarly represented by means of the following vector diagram.



Tuned-Grid Vector Diagram

As with the tuned-plate oscillator, the vector representing the voltage $-\mu e_g$ is used as a reference; e_g is again shown displaced 180° from $-\mu e_g$. Since the plate circuit is inductive and resistive in nature, plate current i_p will lag $-\mu e_g$ by a small angle, θ . This angle will be small because $r_p \gg j\omega L_p$. The voltage induced in the secondary circuit, e_{ind} , will lag i_p by 90° since e_{ind} equals $-j\omega M i_{LP}$. The voltage e_{ind} may be represented by a generator in series with the grid circuit. It was shown in the mathematical analysis that the oscillator operates slightly below the tank frequency; therefore, the capacitive reactance of C will be slightly larger than the inductive reactance of L_p . Viewing the grid circuit as a series circuit in relation to e_{ind} , it is seen that the secondary current (i_s) is slightly capacitive and will lead e_{ind} by a small angle. Since grid voltage e_g is the same as capacitor voltage e_C , it will lag current i_s through the capacitor by 90° . From inspection of the vector diagram, it can be seen that angle θ is the same as the angular difference between e_{ind} and i_s . Higher values of circuit Q will tend to diminish this angular difference, thus diminishing angle $-\theta$ and improving the stability of the oscillator.

Failure Analysis.

No Output. If the circuit is in a non-oscillating condition, negative grid bias will not be developed; as a result, the applied plate voltage will be below normal because of the passage of additional current through the dropping resistor, R_2 . Excessive circuit losses present in the resonant circuit or the tickler (feedback) coil will prevent sustained oscillations. Reduced tube gain will also affect stage regeneration; changing values of the grid-leak bias components, R_1

and C2, will directly affect the operating bias and, hence, the Class C operation and gain of the tube.

Reduced or Unstable Output. A relative indication of oscillator output is provided by the amount of bias voltage developed across R1. This negative bias voltage is normally from 2 to 40 volts, depending upon circuit design and the applied plate voltage.

A reduction in the applied plate voltage will cause the output to be reduced. An unstable voltage source will cause the output to be unstable in amplitude and may also produce some frequency instability. Losses in the tickler (feedback) coil, due to shorted turns or poor soldered connections, can cause reduced output or unstable operation resulting from changes in amplitude of the feedback signal coupled into the resonant circuit (L1, C1).

Incorrect Output Frequency. Normally, a small change in output frequency can be compensated for by realigning or adjusting the variable component of the L-C resonant circuit, assuming that all component parts of the circuit are known to be satisfactory. Since L1 and L2 are mutually coupled, any change in inductance of one coil will have an effect upon the inductance of the other. Thus, if several turns of tickler coil L2 should become shorted, the resonant frequency of L1, C1 will likely be affected and the output frequency will change. This condition is also likely to reduce the oscillator output, since L2 is the means by which feedback or regeneration is accomplished. Furthermore, changes in distributed circuit capacitance, changes in the value of output coupling capacitor C4 and its associated circuit load, or changes in the value of r-f bypass C3 will produce a change in the resonant frequency of L1, C1; thus, the output frequency will depend upon the amount of reactance reflected into the tuned circuit (L1, C1).

ARMSTRONG (TICKLER-COIL) OSCILLATOR (SEMICONDUCTOR)

Application.

Same application as electron tube version.

Characteristics.

Uses an L-C parallel tuned circuit to establish the frequency of oscillation, with feedback being

provided by a separate tickler coil of proper polarity to sustain oscillation.


Operates Class C with stabilized bias for applications where linearity of waveform is not important, and Class A where linearity of waveform is important.

Frequency stability is fair (generally comparable to that of the Armstrong vacuum-tube oscillator).

Circuit Analysis.

General. A sine-wave output may be obtained from an oscillator utilizing a tuned L-C circuit, especially when the transistor is operating over the linear portion of its transfer characteristic curve. The L-C circuit (commonly called a tank circuit) determines the frequency of oscillation. The tank circuit can be located in either the base or the collector circuits to produce two versions of this circuit known as the tuned-base and tuned-collector circuits, respectively; these are similar to the tuned-grid and tuned-plate electron tube oscillators. Although three basic transistor configurations (common base, common emitter, and common collector) can be used, generally, only two, the common emitter and common base, are used in practice. A trend is developing towards the use of the common-emitter arrangement in preference to the others, since it so nearly parallels the electron tube and has input and output impedances that are more easily matched. In the CE circuit, since the input and output are 180 degrees out-of-phase (opposite polarity), it is necessary to provide a 180-degree phase shift (reverse polarity) to bring the output in-phase (of proper polarity) so that oscillation may be sustained. However, in the common-base and common-collector arrangements, the input and output are already in-phase (identically polarized); therefore, no phase shift (polarity reversal) is required (at extremely low frequencies excessive phase shift may prove troublesome). The basic advantage of the Armstrong oscillator, however, is that since the feedback is developed by a separate (tickler) coil, the amount and polarity of the feedback are easily adjusted at the time of manufacture by changing the number of turns or direction of the winding.

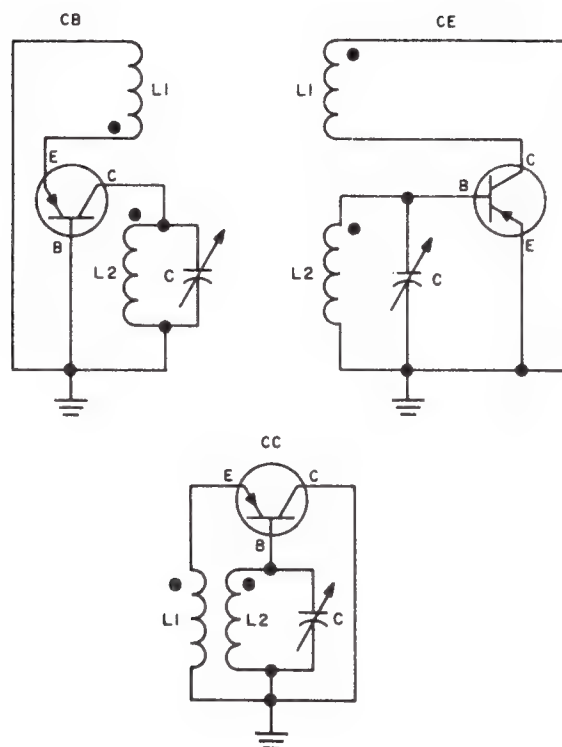Circuit Operation. The three basic transistor configurations of the Armstrong oscillator circuit are shown in the following illustration.



Basic Armstrong Configurations

Bias and plate feed arrangements are omitted for the sake of simplicity, but will be discussed later. It is assumed that forward bias is applied to the emitter-base junction and that reverse bias is applied to the collector-base junction. Only junction transistors are discussed, since point-contact transistors require slightly different considerations and their use is constantly diminishing, except for special applications which will be discussed elsewhere in this technical manual when applicable.

The common-base circuit is usually preferred at the higher frequencies because the collector-emitter capacitance, C_{ce} , helps feed back an in-phase (properly polarized) voltage independently of tickler coil L1, and oscillation is more easily obtained. In the common-emitter circuit this capacitance feeds back an out-of-phase (oppositely polarized) voltage which requires additional feedback from the tickler coil to overcome it. In both the CB and CE circuits, since feedback is primarily provided by voltage induced through the mutual induction between L1 and L2,

and since the voltage gain of these circuits is greater than unity, oscillation is easily sustained. In the common-collector circuit, the voltage gain is always less than unity; therefore, feedback tends to be insufficient for stable oscillation at the lower frequencies, while at the higher frequencies it is assisted by C_{ce} . In some instances, an external capacitor is added between the collector and emitter to provide additional feedback, but when this is done the oscillator can no longer be considered an Armstrong circuit; consequently, the CC circuit is not often employed for this type of oscillator.

The CB circuit with the tuned collector permits convenient matching of input and output impedances, since the low input resistance is easily matched with the tickler coil, and the high output impedance is matched by the tuned parallel-resonant tank circuit. Moreover, the collector-base internal capacitance is swamped by the high-C tank circuit.

In the common-emitter circuit, the moderate input and output impedances are more easily matched, and the tank may be placed in either the base or collector circuits without noticeably affecting the performance.

The operation of the L-C circuit is identical to that of the L-C circuit for the Armstrong electron tube oscillator circuit described in the beginning of this section. The transistor action is as follows: As the oscillator is switched on, current flows through the transistor as determined by the biasing circuit. Internal noise or thermal variations (initial current) produce a feedback voltage between the collector and the emitter which is in-phase with the input circuit. Thus, as the emitter current increases, the collector current also increases, and additional feedback between L1 and L2 further increases the emitter current until it reaches the saturation region, where the emitter current no longer increases. When the current stops changing, the induced feedback voltage is reduced until there is no longer any voltage fed back into the emitter circuit. At this time the collapsing field around the tank and tickler coils induces a reverse voltage into the emitter circuit which causes a decrease in the emitter current, and hence a decrease in the collector current. The decreasing current then induces a greater reverse voltage in the feedback loop, driving the emitter current to zero or cutoff. Although the emitter current is cut off, a small reverse saturation current (I_{CEO}) flows; this current has essentially no effect on the operation of the circuit, but


it does represent a loss which lowers the overall efficiency. In this respect, the transistor differs from the electron tube, which has zero current flow at cutoff.

The discharge of the tank capacitor through L2 will cause the voltage applied to the emitter to rise from a reverse-bias value through zero to a forward-bias value. Emitter and collector current will flow, and the previous described action will repeat itself, resulting in sustained oscillations. Actually, the shunting action of the transistor parameters provides both a resistive and capacitive effect, which causes the frequency of operation to be slightly lower than the tank circuit resonant frequency, but the frequency decrease is so small that the basic frequency of operation is considered, for all practical purposes, to be the tank frequency that is,

$$F_r = \frac{1}{2\pi \sqrt{LC}},$$

where L and C are the values of L2 and C at resonance.

Tuned-Base Oscillator. The tuned-base (tuned-grid) Armstrong oscillator using the common-emitter configuration is shown in the accompanying illustration. One voltage supply is used, with fixed bias being supplied by voltage-dividing resistors R1 and R_B (see the introduction to the amplifier section of this handbook for bias explanation). Emitter swamping resistor R_E bypassed by C1, is used for temperature stabilization.

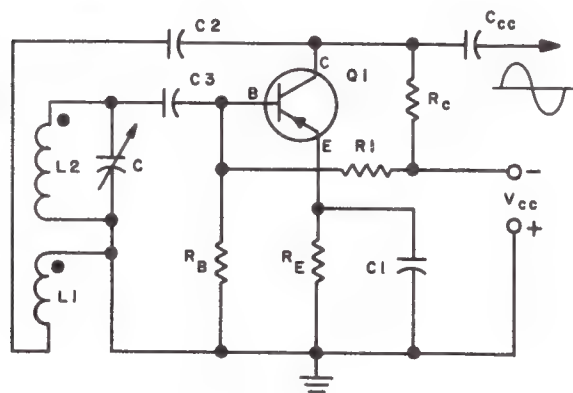


Tuned-Base Armstrong Oscillator

The collector is shunt-fed through R_C, with C2 serving as the coupling (and blocking) capacitor for the tickler coil, to prevent shunting of the dc collector voltage to ground. The tuned tank consists of L2 and tuning capacitor C, coupled to the base of transistor Q1 by capacitor C3, which prevents short-circuiting of the base bias to ground through the tank inductor.

When the circuit is energized, the initial bias is determined by R1 and R_B, and oscillation is built up by feedback from L1 to L2. Besides acting as a thermal stabilizer and swamping resistor, the combination of R_E and C1 acts similarly to a grid leak in an electron tube circuit and builds up a degenerative bias which places operation in the Class C region. That is, while R_B and R1 produce a forward bias, R_E produces a reverse bias, with the algebraic sum of the two biases providing the operating bias. Circuit constants can be adjusted by changing the values of parts to produce practically any of bias between Class A and C. The r-f output is taken from the collector through C_{cc}. The output frequency is determined by the resonant frequency of the tank.

Tuned-Collector Oscillator. The tuned-collector (tuned-plate) Armstrong oscillator using the common-emitter configuration is shown schematically in the accompanying illustration. One voltage supply is used, with fixed base bias being supplied by voltage-dividing resistors R1 and R_B as in the tuned-base oscillator shown previously. The arrangement below uses series base feed, together with series collector feed through the tank inductor, although parallel feed may be used equally well.

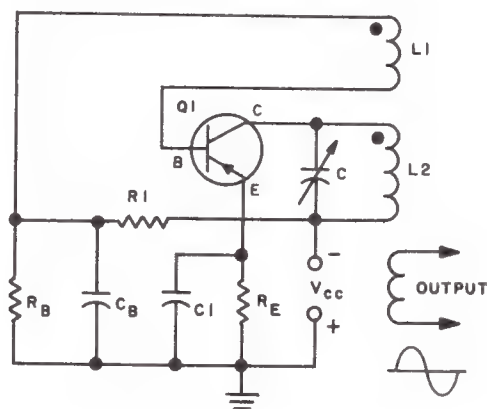

Tuned-Collector Armstrong Oscillator

Since the collector is series fed through L2, tuning capacitor C is above ground and will be subject to hand-capacitance effects. In some circuit variations a radio-frequency choke may be used in series with the tank and bypassed to chassis to shunt any remaining rf around the power supply. Base bias resistor R_B is shunted by C_B , to prevent signal variations from affecting the fixed base bias. Emitter-swamping and base-biasing arrangements operate exactly the same as in the tuned-base oscillator previously discussed. The r-f output, however, is taken through inductive coupling to the tank circuit. Use of series collector and base bias feeds eliminates the need for coupling and blocking capacitors, and thus eliminates any dead spots caused by unwanted resonances of these parts with stray circuit or internal transistor capacitance. The feedback polarity is arranged to provide a 180-degree phase shift, in order to produce positive (regenerative) feedback similar to that obtained in the tuned-base oscillator. Placing the tank in the collector circuit provides an effective swamping capacitance across the collector and emitter, to minimize effects due to the variations of C_{CE} . Although this circuit appears to be more stable from a frequency standpoint than the tuned-base oscillator, it is not so stable thermally. Since the series feed arrangement is used in both the collector and base, there is a dc path of relatively low resistance for reverse saturation current I_{CBO} , which flows during cutoff. The path is from the negative collector supply through the low resistance of L2, through the collector to the base of Q1, and through the low dc resistance of L1, then through the high base bias resistance R_B to the positive supply terminal. Thus the relatively high resistance of collector resistor R_C of the tuned-base oscillator circuit is replaced by the very low dc resistance of the windings of L1 and L2. As a result, the individual transistor I_{CBO} current determines how large a current will flow through the tank and feedback inductances to decrease the effective circuit Q and reduce the over-all efficiency of the oscillator. Where battery power supplies are used, such leakage current will provide a small but constant drain on the battery, an effect not possible with electron tubes.

Failure Analysis.

No Output. As in a vacuum-tube counterpart, loss of gain in the transistor can result in lack of oscillation through loss of feedback. It should be kept in mind that, unlike the electron tube, the transistor

cannot lose gain through loss of emission. Failures of the transistor mostly result in short- or open-circuit conditions rather than deteriorated operation. An excessive time constant in the emitter bias circuit, produced by an increase in the resistance of R_E , could cause blocking effects. A change in the value of emitter bias capacitor C1 will affect the operating bias, will be rather unlikely to completely stop oscillation unless the change is large. Once oscillations have started, loss of forward bias through an open in the base circuit will not necessarily stop oscillations because the feedback signal swinging both positive and negative (on a reference of zero or the established self-bias) will apply on the negative or positive half cycle, depending on the circuit configuration and the type of transistor used, a forward bias and cause emitter collector current to flow (while possible, this condition is not very common). Particular care should be taken not to aggravate troubles by applying potentials greater than the rated voltages (or of the wrong polarity) to the transistor elements when checking the resistance of bias elements and circuit continuity. Failure of the tank and tickler blocking capacitors in the parallel-fed circuit will cause the shorting of bias or supply potentials and stop oscillation; however, at the low voltages used such failure is not very likely. Shorted tickler or tank inductor turns or poorly soldered connections may produce sufficient shunting (or high resistance) to stop feedback, although the tank inductor change would probably be indicated by frequency change rather than loss of oscillation. A short in the tuning capacitor can cause loss of oscillation, and it may be detected by a continuity check unless the tank coil is disconnected.

Reduced or Unstable Output. Instability should be resolved into one of two types—frequency or amplitude. If temperature variations are the cause of frequency instability, the trouble is most likely in the biasing circuit or the emitter swamping circuit. Opening of the bias voltage divider or shorting of one of its resistors will provide less stability, but such a condition is easily found by checking for proper bias with a high-resistance voltmeter, preferably of the electronic type. It is important, in the case of the electronic voltmeter, to make certain that its chassis does not have an above-ground voltage which could be accidentally applied to the transistor under test. Frequency instability can also result from poor connections or changes of L and C values. Mechanical, electrical, and thermal considerations affecting the tank circuit

should be considered. Lack of regulated supply voltage for bias and operation is important. In general, the percentage of regulation in the supply voltage must be better for transistor oscillators than for vacuum tube oscillators. If external to the equipment, power supply regulation effects can sometimes be easily corrected by appropriate use of Zener diodes at the points affected.

Instability in the amplitude can be traced in most cases to variations in the supply voltage or to component failure in limiting diodes placed in the circuit for the sole purposes of maintaining amplitude stability.

While reduced output can result from loss of gain in the transistor, this condition is not as common as it is with electron tubes; therefore, it is more logical to investigate supply and bias voltages first before changing transistors. Excessive bias, rather than lack of bias, is more likely to reduce output.

Incorrect Output Frequency. Normally, a small change in output frequency can be compensated for by realigning or adjusting the variable component of the L-C resonant tank circuit, assuming that all component parts of the circuit are shown to be satisfactory. Changes in distributed capacitance or reflected load reactance will also affect the frequency of operation. Additional capacitance will lower the frequency and less capacitance will increase the frequency; corresponding changes in inductance will produce the same effect. A change in transistor parameters will also affect the frequency; for example, an increase in the collector voltage will reduce the collector-base capacitance, while an increase in the emitter current will increase the collector-base capacitance. Power supply regulation effects can, therefore, be suspected when temporary frequency changes occur. Comparison of actual indications with those of the operational standard will generally indicate the area at fault. It may normally be assumed that major frequency changes will involve the transistor elements and components associated with the tank circuit, since they constitute the major frequency-determining portion of the circuit.

HARTLEY OSCILLATOR (ELECTRON TUBE)

Application.

The Hartley oscillator is used to produce a sine wave output of constant amplitude and fairly constant frequency within the r-f (and sometimes audio) range. The circuit is generally used as a local oscillator in receivers, as a signal source in signal generators and as a variable-frequency oscillator over the medium- and high-frequency ranges.

Characteristics.

Uses an L-C parallel-tuned circuit to establish frequency of oscillation, with the inductance connected as an auto-transformer between grid, cathode, and plate to provide the feedback needed for oscillation.

Operates Class C with automatic self-bias for ordinary, or power, operation and Class A when output waveform linearity is important.


Frequency stability is only fair, but better than that of the Armstrong oscillator.

Circuit Analysis.

General. A sine-wave output may be obtained from an oscillator utilizing a tuned L-C circuit. The L-C circuit (commonly called a tank circuit) determines the frequency at which oscillation will take place. At any particular instant of time, the opposite ends of a tuned inductance are at different polarities, or 180 degrees out of phase. Likewise, the grid and plate of a triode are 180 degrees out of phase. Therefore, connecting the tuned circuit to the grid and plate of the triode will not affect the polarity of operation. When the cathode is tapped to the inductance of the tuned circuit and cathode current flows, a magnetic field will be produced between the cathode-to-plate turns of the inductor. A voltage will be induced in the turns of the inductor connected between the cathode and grid by the cathode current flow, and the polarity of the induced voltage will be in the proper direction to cause an increase of cathode current. Thus, a positive regenerative action is produced by the tapped, tuned-tank circuit connected between

the electron-tube elements. As long as feedback is sufficient to supply the losses in the tuned circuit, continuous, undamped oscillations are produced.

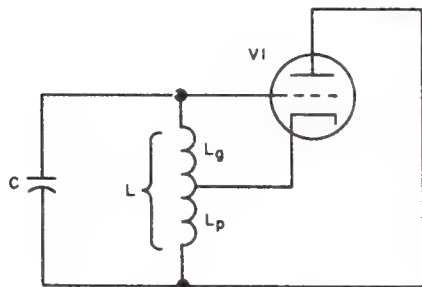
Circuit Operation. The basic Hartley oscillator circuit is shown schematically in the following illustration.



Basic Hartley Circuit

Bias and plate feed arrangements will be discussed later. The tuned (tank) circuit consists of the L_g and L_p portions of inductance L , which is parallel-connected with capacitor C . Feedback is usually accomplished by transformer action between L_p and L_g operating essentially as an autotransformer, with the turns ratio (from about 0.6 to 1) determining the feedback amplitude. (Electrostatic coupling through the tank capacitor can also provide the feedback for oscillation.) Tapping the cathode closer to the plate increases the feedback when the feedback is primarily accomplished by electrostatic coupling through the tank circuit capacitance, with the size of the plate load, L_p , determining the feedback amplitude. Tapping the cathode closer to the plate reduces the plate load and the feedback amplitude. The manner of feedback is determined by the basic construction of the tank circuit inductance.

Shunt-Fed Hartley. The circuit for the shunt-fed Hartley oscillator is shown in the following illustration. Grid bias is developed by R_g and C_g , connected in series between the tuned circuit and the grid of the triode tube. Shunt plate feed is accomplished by connecting the tuned circuit to the plate through C_p , which isolates the tank for dc, but connects it to the plate for r-f current flow. Radio-frequency choke RFC offers a high impedance to the rf, which flows through the tank circuit and not through the power supply, but it permits the dc to flow to the plate.

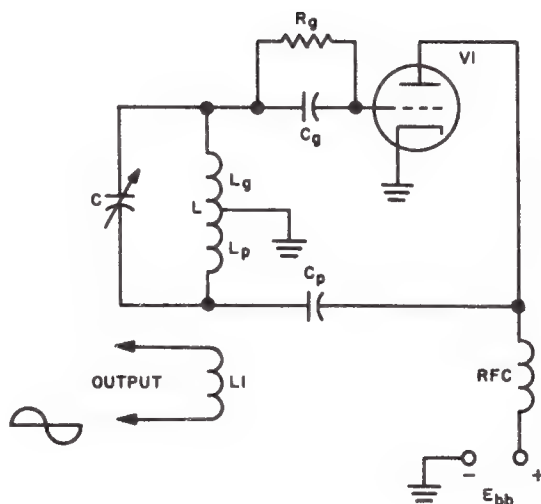

Shunt-Fed Hartley Circuit

The manner in which oscillations occur and the automatic amplitude regulation by grid-leak bias are identical for both the Hartley and the Armstrong oscillators. Refer to the previous discussion of the L-C tickler coil oscillator for an explanation of this action, and assume that the L_p portion of inductor L is the tickler coil.

The use of a high-C tank circuit, consisting of C and L connected between the grid and plate of the electron tube, effectively swamps the tube electrode capacitances and produces better frequency stability. The operating frequency is determined by the values of L and C at resonance

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$


where L is equal to $(L_g + L_p + 2M)$.

Inductive coupling to the load through L_1 at the grouped end of the tank is usually used, but it does not preclude the use of capacitive coupling to the tank circuit where desired.

Series-Fed Hartley. The shunt-fed circuit may be easily modified to a commonly used series plate feed arrangement, by moving the ground connection from the cathode to the bottom end of L_p , and connecting the cathode to the top end of L_p . Thus plate current

will flow directly through L_p . Plate capacitor C_p , in conjunction with radio-frequency choke RFC, then serves only to bypass the rf around the plate voltage supply. The operation of the circuit is otherwise identical to that of the shunt-fed circuit previously described.

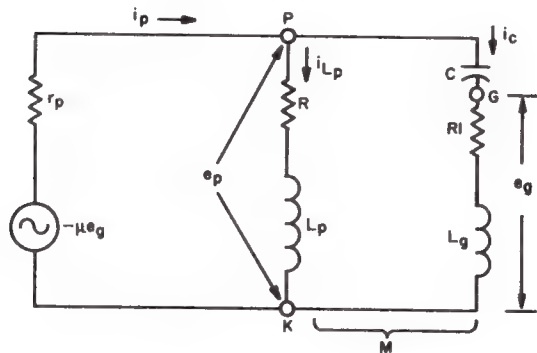Detailed Analysis. The analysis of the Hartley oscillator is similar to that of the tuned-plate Armstrong oscillator previously discussed. The following equivalent circuit is labelled exactly as in the previous example. Since the tank coil is now tapped, the total tank inductance, L , is $L_p + L_g + 2M$. Resistors R and R_1 are equal to the r-f resistance of L_p and L_g , respectively.



Hartley Equivalent Circuit

Analysis of the Hartley circuit shows that the angular frequency is:

$$\omega = \omega_0 \sqrt{\frac{R + r_p}{r_p + R(\mu + 1)}} \quad (1)$$

$$\text{where } \omega_0 = \sqrt{\frac{1}{L_T C}}$$

As in the case of the tuned-plate oscillator, when no power is taken from the circuit, the frequency is practically given by:

$$f = \frac{1}{2\pi \sqrt{L_T C}} \quad (2)$$


where $L_T = L_p + 2M$, or the resonant frequency of the tank circuit. Thus while the oscillation frequency is slightly lower than the tank frequency, if a high r_p and a small R are used, the tank will govern the frequency.

The criteria for oscillation is that:

$$g_m = \frac{\mu(R + R_1) C L_T}{(L_p + M) [\mu(L_g + M) - (L_p + M)]} \quad (3)$$

Examination of equation (3) indicates that even with M at zero the equation will be satisfied; therefore, oscillation can occur even when there is no inductive coupling between the plate and grid circuits, the feedback being capacitively coupled through C . As might be suspected, since the criterion for oscillation is not critical, the Hartley circuit oscillates easily.

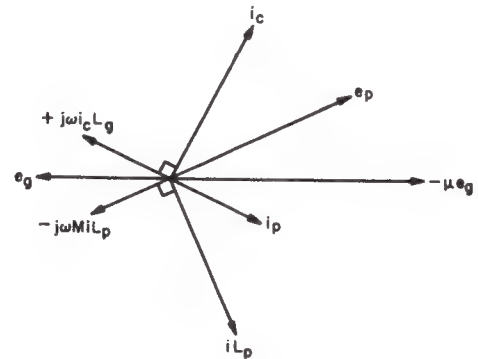Vector Diagram. The relationships between the currents and voltages in the circuit are shown in the following vector diagram. Refer to the equivalent circuit drawing for easier understanding of the development of the vector diagram.



Hartley Vector Diagram

The voltage $-\mu e_g$ is used as a reference vector, and e_g is 180° out of phase. It was pointed out in the mathematical analysis that the Hartley circuit operates slightly below tank resonance; therefore, the tank circuit will appear resistive and inductive, causing i_p to lag $-\mu e_g$ by a small angle, and e_p , the voltage across the tank, to lead by a small angle. The current i_{Lp} will lag e_p by some angle less than 90° dependent on the Q of that branch. The current i_c will lead

e_p by some angle less than 90° since that branch is largely capacitive. The voltage induced in the grid coil, $-j\omega M i_{LP}$, lags i_{LP} by 90° as indicated by its $-j$ coefficient, while the positive component ($+j\omega i_c L_g$), will lead i_c by 90° . Grid voltage e_g is the vector sum of the voltages developed across the grid coil L_g . Note that with higher values of circuit Q the voltages developed across the grid coil will more closely approach in-phase quantities, and the angle between i_p and e_p will also diminish, thereby improving oscillator stability.

Failure Analysis.

No Output. If the circuit is in a non-oscillating condition, negative grid bias cannot be developed; as a result, the applied plate voltage may be below normal because of the additional current drain unless the power supply is well regulated. For this condition, the plate current will be much higher than normal. Excessive circuit losses in the resonant tank circuit will prevent sustained oscillations. Reduced tube gain (if sufficient) will also affect oscillation. Changes in value of the grid-leak bias components, C_g and R_g , will directly affect the operating bias, and hence the class of operation and overall gain of the tube. Such changes, if sufficient, may cause a loss of oscillation. Too high a value of grid leak resistance may cause intermittent operation or "motor-boating". Shorted turns of the oscillator coil (s), in addition to affecting output amplitude and frequency, may cause loss of oscillation because of loading effects. A leaky plate capacitor C_p may also load the oscillator sufficiently to stop operation. In the shunt-fed circuit, a defective radio-frequency choke RFC or coupling capacitor C_c may stop oscillation since the oscillator is dependent on these components for development and application of feed-back voltages.

Reduced or Unstable Output. A relative indication of oscillator output is provided by the amount of bias voltage developed across R_g . Variation from the manufacturer's rated value is indicative of abnormal operation.

A reduction in applied plate voltage will cause a reduced output. Therefore, an unregulated voltage source will produce output amplitude variations and probably frequency changes or instability. Losses in feedback, due to shorted turns or poor soldered connections, can cause reduced output or unstable operation. A leaky plate capacitor, C_p , may cause reduced or unstable output by loading the oscillator or by

reducing plate voltage by adding to the normal current flow through a series resistance. Care should be used in selecting a replacement for a defective r-f choke, since an improper replacement choke may cause unwanted oscillations by resonating with distributed circuit capacitance or with the distributed capacitances of its own windings. Similar care should be exercised in replacing a defective tube in those oscillators operating in the higher frequency ranges where interelectrode capacitances may constitute a considerable portion of the tuned circuits. Variations of this physical capacitance from one tube to another may, in addition to affecting output frequency, cause the oscillator to shift from one mode of operation to another as the oscillator is tuned through its frequency range. For example, a Hartley oscillator could shift to Colpitts operation under the right conditions. This shifting may cause frequency jumps and/or dead spots in the tuning range of the oscillator. At the higher frequencies it is good practice to try more than one replacement tube if the first substitution does not achieve the desired results in frequency of operation and stability. Realignment of circuit components to compensate for a tube substitution should be avoided wherever possible.

Incorrect Output Frequency. Normally, a small change in output frequency can be compensated for by realigning or adjusting the variable component of the L-C resonant tank circuit, assuming that all component parts of the circuit are known to be satisfactory. Changes in distributed circuit capacitance or reflected load reactance will affect the frequency to some extent. Thus, an increase in capacitance will lower the frequency, and a decrease in capacitance will increase the frequency. Therefore, care must be used in the removal and replacement of parts in order not to disturb the distributed capacitance of the circuit which is inherent in the placement of physical parts and the wiring of the circuits. Large changes in ambient temperature may affect the operating frequency of the oscillator. Such changes could come about through failure of an oscillator oven, changes in filament supply voltage, etc. The effects of tube substitution on oscillator frequency were discussed above.

HARTLEY OSCILLATOR (SEMICONDUCTOR)

Application.

Same application as electron tube version.


Characteristics.

Same characteristics as electron tube version, except inductance is connected as an autotransformer between emitter, collector, and base to provide the feedback needed for oscillations.

Circuit Analysis.

General. A sine-wave output may be obtained from an oscillator utilizing a tuned L-C circuit, especially when the transistor is operating over the linear portion of its transfer characteristic curve. The L-C circuit (commonly called a tank circuit) determines the frequency of oscillation. By using a tapped inductor for the tank inductance, a portion of the tank voltage can be fed back to provide positive feedback and sustain oscillation. The tapped inductor tank circuit may be used as either an autotransformer or a phase shifter, depending on the type of feedback needed for the specific circuit configuration. Unlike the Armstrong oscillator where feedback can be shifted in phase 180° by reversing the tickler coil, the Hartley oscillator will operate only in a common-emitter arrangement since the feedback is always shifted in phase 180° .

Circuit Operation. The basic transistor configuration of the Hartley oscillator circuit is shown in the following illustration. Bias and collector feed arrangements are not shown, but will be discussed later. It is assumed that forward bias is initially applied to the emitter-base junction and that reverse bias is applied to the collector junction. This discussion concerns junction transistors only; however, point-contact transistors operate in a somewhat similar manner.

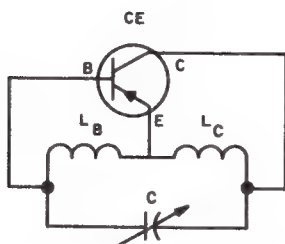


Basic Hartley Configuration

The common-emitter circuit is similar to an electron tube oscillator in that it requires a 180° -degree phase shift from collector to base to produce positive

(regenerative) feedback. Grounding the emitter tap (see following illustration for grounding points) produces the effect of inverting the windings and thus provides the desired 180° -degree Phase shift. The resonant frequency is determined by the tuning of the tank capacitor, C, and is given by the formula:

$$f = \frac{1}{2\pi\sqrt{(L_1 + L_2 + 2M)C}}$$

The figure shows three different arrangements of the common-emitter configuration for grounding the transistor elements. These circuits provide a convenient method for grounding the rotor of the tuning capacitor to eliminate hand-capacitance tuning effects and to obtain proper feedback phasing. Note that the three configurations in the illustration are all *common-emitter* arrangements and that the only difference from the basic schematic is the grounding point. In some texts, these configurations are referred to as *common base*, *common emitter*, and *common collector*, respectively. In all three grounding arrangements of the figure, the feedback is fed from collector to base, and the emitter is the common element.

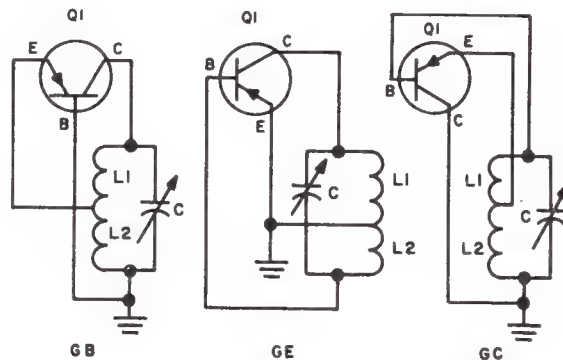


C E Hartley Oscillator Grounding Points

The discussion under the Armstrong circuit concerning the relative merits of the various configurations and the transistor action are applicable to this oscillator. Operation of the L-C circuit is similar to that of the tickler coil electron tube oscillator circuit discussed at the beginning of this Section. In fact, the operation of the Hartley circuit can be considered

exactly the same as that of the Armstrong circuit, with the tickler coil being an integral portion of the tuned tank circuit. The frequency stability of the Hartley oscillator is slightly better than that of the Armstrong oscillator because the tank tuning capacitor tunes the entire coil and feedback loop, and a high C-to-L ratio provides effective capacitance swamping.

Shunt-Fed Hartley. The shunt-fed Hartley oscillator using the common-emitter configuration is shown in the following figure. One voltage supply is used, with fixed base bias being supplied by voltage-dividing resistors R_1 and R_B (see the introduction to the Amplifier Section of this handbook for an explanation of biasing). Emitter swamping resistor R_E , bypassed by C_1 , is used for temperature stabilization.

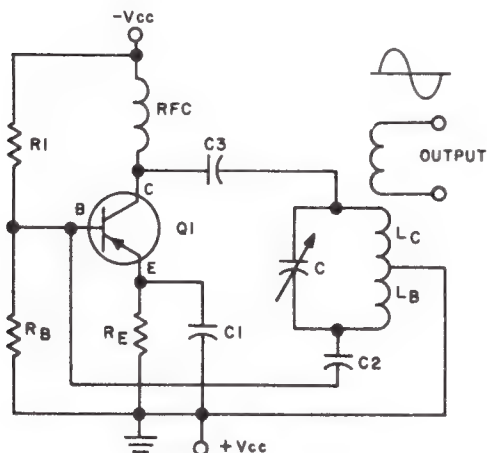


Shunt-Fed Hartley CE Oscillator

The collector is shunt fed through radio-frequency choke RFC, with C_3 serving as the dc blocking and r-f coupling capacitor to keep the tank coil from shorting the collector. Similarly, C_2 serves as the base blocking and coupling capacitor to prevent shorting of the base to ground through the tank inductor.

When the shunt-fed circuit is energized, the initial bias is determined by R_1 and R_B , and oscillation is built up by feedback supplied from the collector to the base through sections L_C and L_B of the tank inductor. Note that an ac path exists from the emitter through the L_C portion of the tank and coupling capacitor C_3 to the collector, and that a similar path exists through L_B and C_2 to the base. As oscillation


occurs, a degenerative bias is developed across R_E (if C_1 is of the correct value) similar to that of the grid-leak-capacitor combination used in electron tube oscillators, and this bias places operation somewhere between Class A and Class C depending on the parts values. Usually the values of voltage divider R_1 and R_B are chosen to provide Class A bias for easy starting, and the values of R_E and C_1 are chosen to provide Class B or C bias for the desired efficiency of operation, with thermal stabilization. The output may be taken from a capacitor connected to the collector or from an inductor coupled to the tank.

Series-Fed Hartley. The series-fed Hartley oscillator is shown in the following illustration. The base circuit is voltage-divider biased and emitter stabilized as in the shunt-fed version. The collector voltage is applied through the tap on the tank inductor, the voltage source being shunted for rf by C_3 . Operation of the series-fed circuit is identical to that of the shunt-fed circuit discussed previously. Since a dc current flows through a portion of the tank circuit, the Q is lowered and the frequency stability is not as great as that of the shunt-fed circuit.

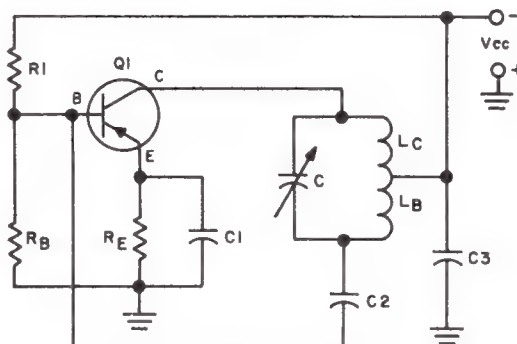


Series-Fed Hartley CE Oscillator

Detailed Analysis. Like the vacuum tube oscillator, the transistor oscillator can be converted to an equivalent circuit and analyzed mathematically to determine the conditions required for oscillation and the frequency of operation, using the h-parameters of the transistor. A typical common-emitter equivalent circuit for the Hartley oscillator is illustrated below. Since the mathematical analysis is complex and beyond the scope of this text, and exact only for low audio frequencies, the interested reader is referred to standard text books for this data.

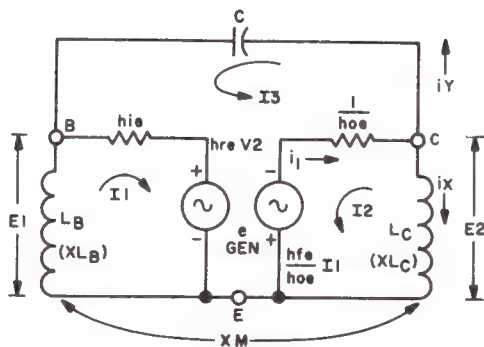

Hartley Semiconductor Equivalent Circuit

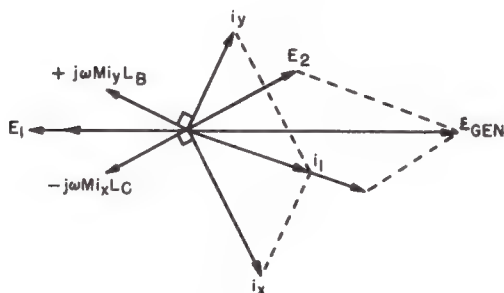The accompanying vector diagram may be more helpful to a better understanding of circuit operation, since it shows the voltage and current relationships. The common-emitter circuit is illustrated.



Hartley Vector Diagram

The voltage e_{gen} is used as a reference vector. Since the Hartley circuit operates slightly below resonance, the tank circuit appears resistive and inductive, causing i_1 to lag e_{gen} , and the voltage across the tank E_2 to lead by a small angle. Current i_y leads E_2 by some angle less than 90 degrees since that branch is largely capacitive. Current i_x lags E_2 by some angle less than 90 degrees, depending upon the Q of that branch. The voltage induced in the base coil $-j_m M i_x L_C$ lags i_x by 90 degrees as indicated by its $-j$ coefficient, while the positive component $+j_m i_y L_B$ leads i_y by 90 degrees. The base voltage, E_1 , is the vector sum of the voltages induced in base coil

L_B . Note that with higher values of circuit Q the voltages developed across the grid coil more closely approach in-phase quantities, and the angle between i_1 and E_2 also diminishes, thereby improving the oscillator stability.

Failure Analysis.

No Output. Lack of oscillation may be due to a shorted or open-circuited transistor. Deterioration with age causing lack of gain may result under high-temperature conditions. Unlike vacuum tubes, however, transistors have operated for years without noticeable deterioration under proper operating conditions. Failure of the collector and base blocking capacitors will short-circuit the biasing arrangement through the tank coil and prevent operation. Open-circuit conditions of the biasing resistors may stop oscillation, though it is more likely that reduced output will result rather than no output. Where radio-frequency chokes are used to keep rf out of the supply or bias circuits, failure of these components may shunt the rf to ground through power supply capacitors. A more likely condition is an open circuit in the RFC caused by poorly soldered connections. A shorted condition of the tuning capacitor will stop oscillation, and it cannot be detected by a continuity check unless the tank coil is disconnected. When trouble-shooting with test equipment containing line filter capacitors, care should be exercised to prevent application of excessive voltage to the transistor by using a common ground on both the transistor and test chassis. Use high-impedance meters to avoid placing a dc shunt or return path in the circuit and causing improper current flow or voltage distribution.

Reduced or Unstable Output. Instability should be resolved into one of two types — frequency or amplitude. Frequency instability will most likely result from poor tank circuit connections, poor insulation between turns, or changes in L and C values. Also, changes in the supply voltage will produce changes in frequency because of changes in the operating point and changes in the internal capacitance of the transistor with different applied voltages. Excessive bias will probably cause a reduction in the output and will most likely be produced by an increase in value of the bias resistor or opening of the bias bypass capacitors with the consequent production of degeneration. Temperature changes are usually evidenced by increased current in the collector circuit and can be caused by a shorted emitter swamping resistor.

Incorrect Output Frequency. Normally, a small change in output frequency can be compensated for by realigning or readjusting the variable component of the L-C resonant tank circuit, assuming that all parts of the circuit are known to be satisfactory. A change of transistor parameters will also affect frequency; for example, increased collector voltages will reduce the collector-base capacitance, and increased emitter current will increase the collector-base capacitance, but these effects are not equal and therefore do not compensate each other. Reflected load reactance can cause a change of frequency depending on the tightness of coupling between the oscillator and the load. Changes in distributed circuit capacitance or in the tank inductor will also cause frequency changes. A comparison of operational indications against operational standard values will generally indicate the area at fault. For example, frequency changes that vary with power supply voltage fluctuations indicate that supply regulation is necessary and trouble is not in the equipment. Major frequency changes will involve the transistor elements and components associated with the tank circuit, since they constitute the major frequency-determining portion of the circuit.

COLPITTS OSCILLATOR (ELECTRON TUBE)

Application.

The Colpitts oscillator is used to produce a sine-wave output of constant amplitude and fairly constant frequency within the r-f range. The circuit is generally used as a local oscillator in receivers, as a signal source in signal generators, and as a variable-frequency oscillator over the low- and very-high-frequency ranges, especially where inductive tuning is desired.

Characteristics.

Uses an L-C parallel tuned circuit to establish frequency of operation.

Features inductive tuning rather than capacitive.

Feedback is obtained through a capacitance-type voltage divider.

Operates Class C where wave form linearity is not important, and Class A where linearity of waveform is important.

Frequency stability is good (considered better than that of the Hartley at the lower and medium frequencies).

Oscillates easily at high frequencies, where inductive feedback types have difficulty securing sufficient feedback.


Circuit Analysis.

General. When a tuned LC (tank) circuit is connected between the grid and plate of an electron tube, the phasing is of the correct polarity to sustain oscillation. The capacitor of a tuned tank circuit may be a single capacitor, or it can be two series-connected capacitors with a total capacitance equivalent to that of the single capacitor. In either case, the frequency of oscillation is the same. The two series-connected capacitors will form a capacitance voltage divider across the tank circuit. Tapping the cathode of the tube to this voltage divider provides a convenient electrical (and mechanical) connection, and a means of controlling feedback between the grid, cathode, and plate elements. The ratio of the capacitances used will determine the amount of feedback, and the total capacitance value will determine the resonant frequency for any particular value of tank inductance. Varying the inductance is a convenient method for tuning the tank over a range of frequencies with a fixed amount of feedback. The use of capacitive tuning involves the simultaneous tuning of both capacitors to maintain the proper ratio of feedback. For tuning over a limited range, capacitive tuning is sometimes employed.

Circuit Operation. The basic Colpitts oscillator circuit is shown schematically in the following illustration. The tuned tank circuit consists of C_g and C_p , in series, and the parallel-connected inductor, L . Feedback is accomplished by the capacitive voltage-divider action of C_g and C_p (or by the use of a variable capacitor shunting C_g and C_p). The feedback ration varies as

$$\frac{C_g}{C_g + C_p}$$

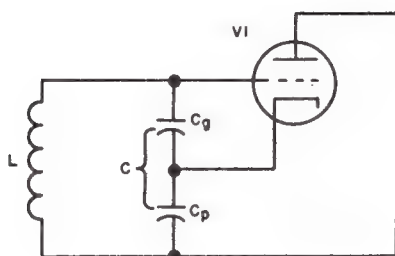thus, increasing the value of C_g decreases the feedback.




Basic Colpitts Circuit

The capacitive ratios vary with circuit design and frequency, from about a 1:1 ratio to a 1:4 ratio, with the larger capacitor being C_p . For high-frequency use, the capacitance voltage divider may consist of only the interelectrode capacitances of the electron tube. The circuit may be arranged for grounded grid, cathode, or plate operation without affecting performance; the grounded-cathode configuration is probably the most frequently used circuit.

For simplicity, biasing and plate-voltage feed methods are not shown in the basic circuit, but are discussed where applicable in the following circuit variations.

Shunt-Fed Colpitts. The circuit for the shunt-fed Colpitts oscillator is shown in the following schematic. Grid bias is developed by R_g and C_g in the shunt grid-leak bias arrangement. Shunt plate feed is also used, with C_c serving as the plate blocking and coupling capacitor, and RFC as the r-f isolating choke. The tank circuit consists of inductor L and capacitor C , which are parallel-connected between the grid and plate of the electron tube. Capacitor C consists of two series-connected capacitors, C_1 and C_2 , which are external to the tube and form a feedback voltage divider to which the cathode is connected.

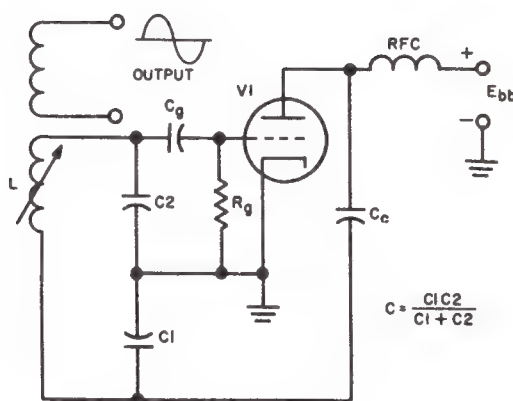

Shunt-Fed Colpitts Oscillator

The manner in which oscillations occur, as well as the automatic regulation of amplitude by grid-leak bias, is the same as explained in the previous discussion of the L-C tickler coil oscillator, except that feedback is obtained from a capacitive voltage divider instead of an inductive voltage divider. Assume that the tank circuit consists of L and C where C represents C_1 and C_2 in series. The tank circuit then is identical with the tuned grid circuit of the tickler-coil oscillator previously described. Since the tank is connected between the plate and grid of the electron tube, and C_1 and C_2 form a capacitive voltage divider, it is evident that there will be a division of feedback voltage in inverse ratio to their capacitance. For a specific frequency the large capacitor will have the lowest impedance, and the smaller capacitor the highest impedance. For equal capacitors, the voltages across the capacitors will be equal. Thus, with the cathode connected to the common connection of the capacitors, the tank voltage will be divided between cathode-and-grid and cathode-and-plate in accordance with the ratio of C_2 and C_1 . Any voltage change in

the plate circuit will appear across C_1 and be fed back through C_2 in the correct phase to drive the grid in that direction to increase the initial change. That is, if the plate voltage is increasing, the grid change will cause a further increase, and if decreasing, a further decrease. This is exactly the same result that is achieved by the plate-grid coils of the Armstrong circuit or the tapped inductor of the Hartley circuit, as discussed previously, and sustained oscillations will occur.

Since the tank capacitance is composed of series-connected capacitors, each capacitor will be larger than the total capacitance that is effective in tuning the circuit. Since these series capacitors are connected in parallel with the grid-to-cathode and plate-to-cathode tube capacitances, they will swamp out the interelectrode capacitance variations and thereby increase the frequency stability. Note, however, that as the capacitance of the feedback capacitors approaches the value of the tube element capacitance, this swamping effect is decreased. Stability therefore, is at a maximum at the lower frequencies. The grid-plate capacitance, which is usually larger than the other element capacitance, remains in shunt with the tank inductor and will not be compensated for. If desired, capacitive tuning can be achieved by using a shunt tuning capacitor across L and leaving the feedback capacitors fixed. The advantage of the Colpitts circuit, however, is in the use of large variable inductors and fixed feedback-tank capacitors for operation in the low- and medium-frequency r-f ranges, where the greatest stability is obtained.

For high-frequency use, the Colpitts can be employed as an oscillator controlled mainly by the capacitance between the tube elements, so that inductance alone is needed to achieve oscillation. This arrangement results in higher frequencies of operation than with other L-C circuits, and is exemplified by the series-fed version of the Colpitts known as the ultraudion circuit, which is discussed as a separate circuit later in this section. The output coupling may be either inductive or capacitive, as desired.

Detailed Analysis. The equivalent plate circuit for the shunt-fed Colpitts oscillator is shown in the following illustration. Assuming that the RFC has infinite reactance, neglecting the grid capacitor react-


ance, and assuming that the circuit has an infinite grid leak with no grid current, it can be seen that:

$$i_p = i_1 + i_2$$

$$e_{gk} = \frac{i_2}{j\omega C_2}$$

$$e_{pk} = \frac{i_1}{j\omega C_1} = i_2 (R + j\omega L) + \frac{i_2}{j\omega C_2}$$
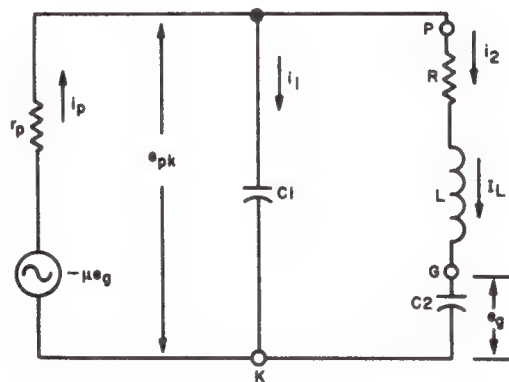
$$-\mu_{egk} = r_p i_p + \frac{i_1}{j\omega C_1}$$



Colpitts Equivalent Circuit

The analysis of the Colpitts oscillator is similar to that of the Hartley, except that the capacitive reactance of capacitors C_1 and C_2 is substituted for L_p and L_g , and the inductive reactance for C . The angular frequency is:

$$\omega = \omega_0 \sqrt{1 + \frac{R}{r_p} \cdot \left(\frac{C_2}{C_1 + C_2} \right)}$$

For all practical purposes, the frequency is:

$$f = \frac{1}{2\pi \sqrt{L \frac{C_1 C_2}{C_1 + C_2}}}$$


The criteria for oscillation is that:

$$\mu = \frac{C_2}{C_1} + \frac{r_p R(C_1 + C_2)}{L}$$

Capacitors C_1 and C_2 form a capacitive voltage divider across L , causing the grid excitation voltage to be proportional to

$$\frac{C_2}{C_1 + C_2}$$

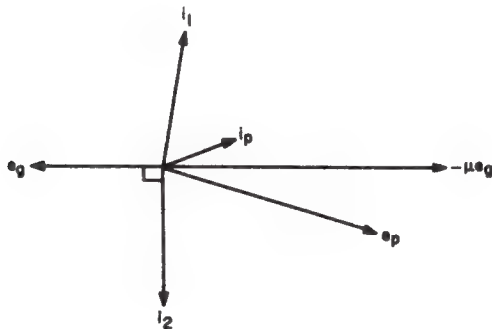Vector Diagram. The relationships between the currents and voltages are shown in the following vector diagram. Refer to the illustration of the equivalent circuit for development of the vector quantities.



Colpitts Vector Diagram

The voltage generator $-\mu e_g$ is the reference voltage, e_g being 180° out of phase. It was shown that the Colpitts oscillator operates above the tank frequency. Therefore, the tank circuit appears slightly capacitive, and i_p leads $-\mu e_g$ by a small angle while e_p lags $-\mu e_g$. The current i_1 through capacitor C_1 will lead e_p by 90° . Current i_2 through the branch containing L and C_2 is primarily inductive and will lag e_p by an angle less than 90° determined largely by the Q of L . The voltage e_g , since it appears across capacitor C_2 , will lag i_2 by 90° , thereby satisfying the conditions for oscillation. It can be seen that with higher values of circuit Q , the phase difference between i_p and e_p will be diminished.

Failure Analysis.

No Output. If the circuit is in a non-oscillating condition, the negative grid bias will be much less

than it is in the oscillating condition, because it will consist of contact-potential bias only, which will allow the tube to operate at approximately zero instead of at cutoff or higher. Thus the plate current will be much higher than normal. Excessive losses present in the resonant tank circuit will prevent sustained oscillations. Reduced tube gain, if sufficient, will also affect oscillation, but will not be as noticeable as in the inductive feedback circuits. Changed values of grid-leak bias components R_g and C_g will directly affect the operating bias and change the amplitude of the oscillations; if the change is large, oscillation may even be prevented; if small, the effect may not be noticeable. A defective radio-frequency choke RFC or coupling capacitor C_c may cause loss of oscillation since the circuit depends on these components for the development and application of the feedback voltage.

Reduced or Unstable Output. A relative indication of oscillator output is provided by the amount of bias voltage developed across R_g . Variation from the standard operating value is an indication of abnormal operation. A reduction of applied plate voltage will cause a reduced output. Therefore, an unregulated voltage source will produce output amplitude variations and probably some frequency change or instability. Losses in feedback due to shorted turns, poor soldered connections, or changing values of feedback capacitance can also cause reduced output or unstable operation. Care should be used in selecting a replacement for a defective r-f choke, since an improper replacement may cause unwanted oscillation by resonating with the capacitance of its own windings or with distributed circuit capacitances.

Incorrect Output Frequency. Normally, a small change in output frequency can be corrected by adjusting the variable component of the L-C resonant tank circuit, provided that all component parts of the circuit are known to be satisfactory. Changes in distributed circuit capacitance or reflected load reactance will affect the frequency of operation to some extent, being most noticeable on the higher-frequency ranges. Changes in stray capacitance which parallels the tank circuit will have a greater effect in changing the frequency than grid-cathode or plate-cathode capacitance changes (provided that they are large enough to overcome the tank swamping effect). Care should be used in replacing a defective tube, particularly in oscillator circuits operating in the higher frequency

ranges. It is good practice to try more than one replacement tube if the first substitution does not achieve the desired results in frequency of operation and stability. Realignment of circuit components to compensate for a tube substitution should be avoided wherever possible. Large changes in ambient temperature may affect the operating frequency of the oscillator. Such changes could come about through failure of an oscillator oven, changes in filament supply voltage, etc.

COLPITTS OSCILLATOR (SEMICONDUCTOR)

Application.

Same application as electron tube version.

Characteristics.


Same characteristics as electron tube version.

Circuit Analysis

General. A sine-wave output may be obtained from a transistor oscillator using a tuned L-C circuit, particularly when the transistor is operating in the linear region of its transfer characteristics. The L-C (tank) circuit determines the frequency of oscillation. The tank circuit consists of two series-connected capacitors in parallel with the inductor. The two series capacitors will act as a capacitance voltage divider across the inductor (in addition to tuning the coil to resonance) with the larger voltage appearing across the smaller capacitor. The capacitance feedback voltage divider may be connected so as to provide either an in-phase voltage or an out-of-phase voltage, to suit the various transistor configurations used. The reactance ratio of the two series capacitors is usually chosen to match the input-output resistances of the transistor used. Mathematical analysis predicts a larger ratio between them than is employed in electron tube practice. The large ratio between capacitor values makes it practical to employ fixed capacitors and tune the inductance over the desired frequency range. The use of capacitance (separate or ganged) tuning over small ranges is occasionally encountered. The frequency of operation is the same as the resonant frequency of the tank circuit, which is given by:

$$f = \frac{1}{2\pi \sqrt{L \frac{C_1 C_2}{C_1 + C_2}}}$$

Circuit Operation. The basic configuration of the Colpitts transistor oscillator is shown in the figure below. For simplicity, bias and collector feed arrangements are not shown, but are discussed later. It is assumed that forward bias is initially applied to the emitter-base junction and that reverse bias is applied to the collector-base junction. Only junction transistors are considered since point-contact transistors operate somewhat differently.

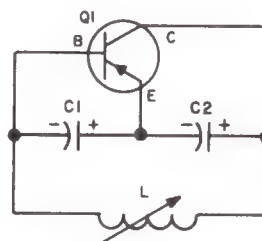


Basic Colpitts CE Configuration

Since in the common-emitter circuit the base and collector elements are out-of-phase, it is necessary to provide a 180-degree phase shift to obtain the positive (regenerative) feedback needed to sustain oscillation. This phase shift is achieved by grounding the common capacitor connection, to make the instantaneous polarity of the capacitor supplying the feedback to the emitter opposite to that of the collector. The discussions of transistor action and the relative merits of the various configurations of L-C oscillators made previously are also generally applicable to this oscillator. The frequency stability is better than that of the Hartley oscillator and the Armstrong oscillator, because the lumped tank capacitors effectively swamp out any slight capacitance changes that occur between the emitter and collector and between the emitter and base of the transistor.


The following simplified schematics of grounding points show three different arrangements of the common-emitter configuration for grounding the transistor elements. These circuits provide a convenient method of grounding the tuning-capacitor rotor to eliminate hand-capacitance tuning effects and to achieve the proper phasing for the feedback. Note that the three grounding point configurations are all *common-emitter* arrangements and that the only difference from the basic oscillator is the grounding

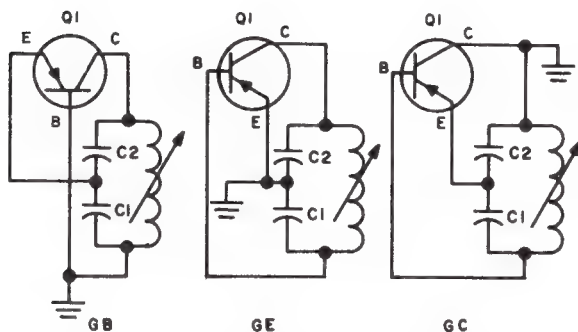point. In some texts these configurations are referred to as *common base*, *common emitter*, and *common collector*, respectively.



CE Colpitts Oscillator Grounding Points

Shunt-Fed Colpitts. The shunt-fed Colpitts oscillator arranged in the common-emitter transistor configuration is shown schematically in the accompanying illustration. One voltage supply is used, with fixed bias being supplied by voltage-dividing resistors R_1 and R_B (see the introduction to the Amplifier Section of this handbook for an explanation of biasing). Emitter swamping resistor R_E , bypassed by C_1 , is used for temperature stabilization.

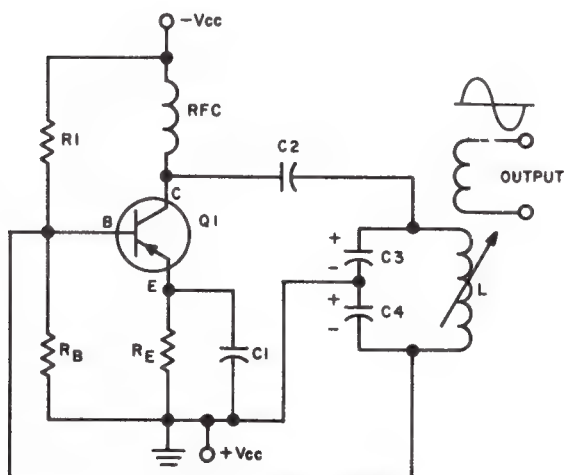


Shunt-Fed Colpitts GE Oscillator

The collector is shunt-fed through radio-frequency choke RFC to keep the rf out of the supply circuit, with capacitor C_2 acting as a coupling capacitor for the tank circuit. Capacitor C_2 also serves as a blocking capacitor, preventing the dc supply from entering the tank circuit and shunting (actually shorting) R_1 through the tank inductance.

When the circuit is energized, the initial bias is determined by R_1 and R_B , and oscillation is built up by feedback from the tank circuit through divider capacitor C_4 . Since the divider is grounded at the common connection, opposite polarities exist across capacitors C_3 and C_4 in respect to ground, with the voltages across these capacitors being determined by the capacitive reactance ratio. Thus a voltage that is out-of-phase with the collector is applied between the emitter and base to supply a positive feedback and sustain oscillation. The combination of R_E and C_1 provides an emitter swamping resistor for thermal stabilization, with sufficient capacitance as a bypass to permit degenerative voltage buildup to occur and bias the transistor into the Class B or C operating region after a few initial oscillations. The values of R_1 and R_B are usually chosen to provide Class A bias for easy starting. The amplitude of oscillation is essentially regulated by driving the transistor to saturation on one portion of the cycle and to cutoff on the other portion. Although such action normally would cause abrupt changes and distort the waveform, the tank circuit effectively smoothes out the pulsations in Class C operation to provide oscillations that are essentially sine waves. In the linear Class A region, the circuit provides satisfactory sine-wave output for test equipment use. The oscillator output is normally taken inductively by a coil coupled to the tank inductor, although a capacitive tap may be used if necessary.

Detailed Analysis. A typical common-emitter equivalent circuit for the Colpitts oscillator is shown in the following illustration. As in the Hartley circuit, the mathematical analysis of the equivalent circuit is too involved for this text, but can be found in standard texts. With both the Hartley and Colpitts equivalent circuits it is possible, with slight modifications, to represent most of the other oscillator circuits now in use. Thus, the interested reader will find these two circuits most useful.

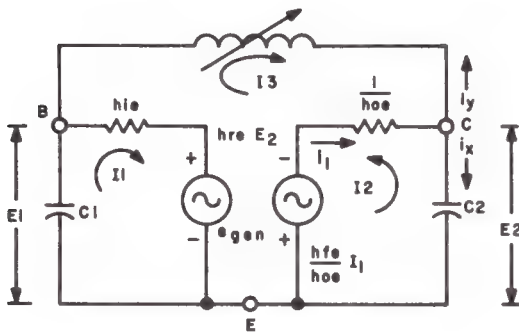

Colpitts Semiconductor Equivalent Circuit


One interesting fact develops from the Colpitts analysis; that is, the starting conditions are found to be:

$$\frac{h_{fe}}{\Delta h_e} = \frac{C_1}{C_2}$$

Where $\Delta h_e = h_{ie} h_{oe} - h_{re} h_{fe}$.

Thus, when h_{fe} is large and Δh_e is small, capacitors C_1 and C_2 will have large differences of values (from 10 to 100 times), which is not the case with the electron tube counterpart.

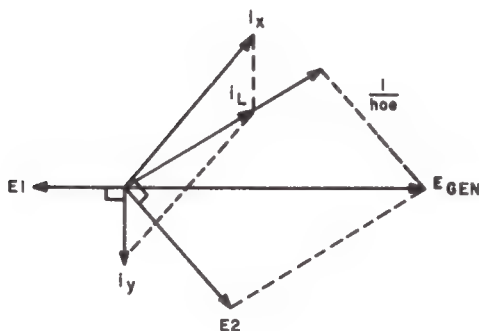The accompanying vector diagram shows the current and voltage relationships for the Colpitts oscillator equivalent circuit above.



Colpitts Vector Diagram

Note that the Colpitts is exactly the inverse of the Hartley. The reference vector is e_{gen} , with the induced base voltage, E_1 , directed 180 degrees out of phase. Since the Colpitts oscillator operates above the tank frequency, the tank circuit appears slightly capacitive. Thus i_1 leads e_{gen} by a small angle, while E_2 lags. Current i_x through capacitor C_2 leads E_2 by 90 degrees. Current i_y through the branch containing the tank inductance and C_1 is primarily inductive and lags E_2 by an angle less than 90 degrees depending largely upon the Q of the tank inductance. Since the induced base voltage, E_1 , appears across capacitor C_1 , it lags i_y by 90 degrees, thereby satisfying the conditions for oscillation. It can be seen that with higher values of circuit Q the phase difference between i_1 and E_2 will diminish.

Failure Analysis.

No Output. Although oscillation may fail because of a shorted or open-circuited transistor, deterioration with age similar to the decrease of emission in electron tubes does not normally occur. High-temperature operation may cause premature failure or drop-off in performance of the transistor; however, this can normally be obviated by proper ventilation of the equipment. Reflected reactance from heavy loading due to tight coupling may occur and prevent oscillation, but it should not occur with proper design. Failure of collector blocking capacitor C_2 will place a dc short circuit across the collector and base of transistor Q_1 through the tank inductance and stop oscillation; it may also ruin the emitter-base junction. Changes in value of the bias resistors will probably reduce the output rather than prevent oscillation completely. Shorting of either of the tuning capacitors will prevent oscillation. In making continuity checks of these tuning capacitors with an ohmmeter, it is important to connect the ohmmeter with the correct polarity because, since the emitter-base junction is in parallel, use of the incorrect polarity would apply a forward bias and possibly damage the transistor.

Reduced or Unstable Output. As in the oscillators discussed previously, it is important to determine whether the instability is associated with frequency or amplitude. If amplitude instability is caused by temperature effects, the bias divider and emitter stabilizing resistors are probably at fault. Reduced output will most likely be due to excessive biasing caused

by changes in value of the bias resistors, or to excessive degeneration caused by an open capacitor (or a reduced value of capacitance) in the emitter bypass circuit. A leaky collector coupling capacitor will cause a change in bias by reflecting, through the tank inductance, a parallel resistance between the base and collector elements of the transistor. Frequency instability will indicate that the tank circuit or supply voltage is at fault. Although this circuit provides capacitance swamping of the elements to minimize transistor capacitance changes with supply voltage changes, it should be noted that a varying supply voltage also changes the transistor operating point and may therefore affect the frequency to some extent. As in the other oscillators, poor mechanical connections and shorted turns or deteriorated insulation in the tank circuit may cause unstable operation.

Incorrect Output Frequency. As in the other oscillators discussed previously, small changes in frequency can be corrected by adjusting the tuning capacitor, assuming that all parts are in good condition. Variations of frequency with supply voltage changes indicate the need for external supply regulation. Major frequency changes will most likely indicate trouble in the tank circuit since it is the primary frequency-determining circuit. Although a change in transistor parameters may change the frequency to some extent, a major parameter change will most likely result in reduced output or unstable operation. Too tight coupling of the load is indicated if the frequency changes noticeably with changes in loading (a slight change is normal).

CLAPP OSCILLATOR (ELECTRON TUBE)

Application.

The Clapp oscillator is used to produce a sine-wave output of constant amplitude and fairly constant frequency within the r-f range. The circuit is used as a beat frequency oscillator in receivers, as a master oscillator in transmitters, and generally as a variable-frequency oscillator over the high- and very-high frequency ranges. It is also employed as a crystal controlled oscillator in frequency meters and in signal generators.

Characteristics.

Uses a separate series tuned L-C circuit to determine the frequency of oscillation, with a capacitance

voltage divider form of feedback to control oscillation.


Operates as Class B or C with automatic self-bias for ordinary or power operation, and as Class A where output waveform linearity is important.

Frequency stability is good. The circuit is considered to have better stability than the Colpitts circuit.

Circuit Analysis.

General. The Clapp circuit is considered to be a variation of the Colpitts circuit discussed previously. It uses the stabilizing effect of a series tuned tank circuit, coupled loosely to the tube feedback loop, to provide better frequency stability. It incorporates capacitive tuning which require the use of only one tuning capacitor. It also offers a convenient method of tuning over a small band of frequencies where band-spread or vernier-type tuning is desired.

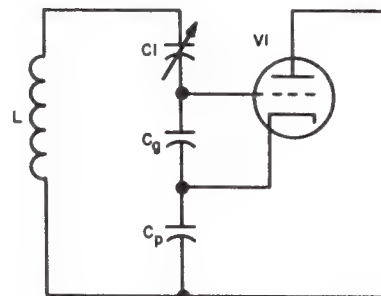Circuit Operation. The basic Clapp oscillator circuit is shown in the following schematic. The tuned tank circuit consists of series-connected components L and C1 in parallel with the basic capacitance feedback voltage divider, C_g and C_p . For simplicity, the biasing and plate feeds are not shown in this basic circuit, but are discussed as necessary in the following circuit discussion.



Basic Clapp Circuit

The capacitance ratio for the voltage divider which provides the basic feedback (as in the Colpitts circuit) may vary with the circuit design and the frequency. Usually it is 1:1 with C1 being smaller (about one-tenth C_g for high-frequency operation).

The circuit may be arranged for grounded grid, cathode, or plate operation without affecting performance; the grounded-plate configuration is the most frequently used.

The frequency of operation is dependent upon the values of the three capacitors and inductor as follows:

$$F = \frac{1}{\sqrt{2\pi L C_1} \sqrt{1 + \frac{C_1}{C_g} + \frac{C_1}{C_p}}}$$

Thus it is evident that when the ratios of C_1/C_g and C_1/C_p are very small, the resonant frequency will be primarily determined by the values of L and C_1 alone. This is the condition usually desired.

Since the resonant frequency is primarily determined by L and C_1 when C_p and C_g are comparatively large, the Clapp circuit may employ much larger values of capacitance in the feedback voltage divider than can the equivalent Colpitts. The larger values of capacitance much more effectively swamp interelectrode capacitances; it has been estimated that as much as a 400 to 1 reduction of change in capacitance by temperature or tube variations may be obtained.


As in the other L-C circuits, the most stable operation is obtained with a high loaded Q , which is produced for a series resonant circuit by a high L to C (not C to L ratio). Thus, for a given frequency, the tank inductance is larger than that used for the previously discussed circuits. Since it is easier to produce a high- Q coil when the inductance is greater than the usual high- C tank affords, the Clapp oscillator benefits from the low- C tank. While the capacitance voltage divider consisting of C_g and C_p does not offer any greater stability in this Clapp circuit than in the Colpitts, the ratio of C_g to C_p is chosen to afford the greatest possible stability in conjunction with the higher Q offered by the series tuned tank. Tuning capacitor C_1 is chosen to have the desired tuning range, with sufficient capacitance to sustain the feedback loop at the higher frequency (feedback increases with decrease of frequency).

Since the basic frequency-determining portion of the Clapp circuit is the tank inductor (C_1 merely tunes over the desired range), which is coupled capacitively through C_1 to the tube, the Clapp tank is generally considered to be more loosely coupled than the tank circuit of the other oscillator configurations. Thus tank circuit changes are normally minimized.

This factor, in combination with the higher circuit Q obtainable, provides the Clapp oscillator with very high stability in the presence of supply voltage variations, the frequency changing only a few parts per million for a supply voltage variation of 15 percent.

Variations of the Clapp oscillator circuit may be encountered. For example, an RFC may be inserted between cathode and ground to keep the cathode at a high impedance above ground, and offer a dc return path to the cathode. Usually this choke is chosen to resonate with its distributed capacitance at the fundamental frequency, and occasionally a trimmer is included to adjust the parallel resonant choke circuit for proper impedance. In special circuit versions, the cathode tank may be used for frequency doubling. These circuit variations, however, are not a part of the basic Clapp oscillator circuit design.

Shunt-Fed Clapp. The complete schematic for a shunt-fed Clapp oscillator is shown in the accompanying illustration. Series plate feed is never used in this circuit and will not be discussed. Shunt grid-leak bias is used (R_g and C_g), with shunt plate feed. Capacitor C_c is the plate blocking and coupling capacitor, and inductor RFC is the r-f choke. The combination of C_c and RFC provide an r-f bypass to isolate the power supply from r-f. The plate is grounded to r-f, and L and C_1 form the tank circuit, which is connected across the feedback divider consisting of C_2 and C_3 . The cathode RFC provides a dc return path to ground for the cathode, and offers a high impedance to r-f to prevent any shunting of divider capacitor C_3 .

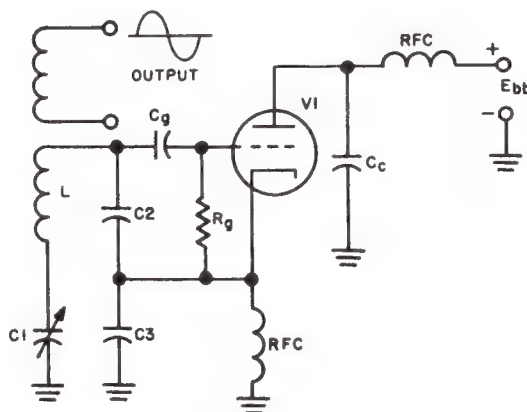

Shunt-Fed Clapp Oscillator

Operation of the circuit and automatic regulation of the amplitude by grid bias are the same as described in previous oscillator discussions. Oscillation is caused by feedback through the capacitance voltage divider, C2-C3, as in the Colpitts oscillator, but the ratio of the capacitors is chosen for the best frequency stability. The output coupling is usually inductive, but it may be capacitive.

Failure Analysis.

No Output. High plate current will be indicative of non-oscillation and consequent loss of operating bias, with the tube operating at essentially zero (contact) bias. Reduced tube gain, if sufficient, will also affect oscillation. Changes in the value of the bias resistor and capacitor will directly affect the operating bias and the amplitude of oscillating — if the changes are large, oscillation may be prevented; if small, the effect may not be noticeable. Shorted turns of oscillator coil, in addition to affecting output amplitude and frequency, may cause loss of oscillation because of loading effects. A defective radio-frequency choke (RFC) or coupling capacitor (C_c) may stop oscillation since the oscillator is dependent on these components for the development and application of feedback voltages.

Reduced or Unstable Output. A relative indication of oscillator output is provided by the amount of bias voltage developed across R_g . Variation from the standard operating value is an indication of abnormal operation. A reduction of plate voltage will decrease the output amplitude. Therefore, an unregulated voltage source will produce output amplitude variations and possibly some frequency change, although the Clapp circuit is considered to be less affected in this manner than the Colpitts (a change of only a few parts in a million for a 15 per cent plate supply fluctuation is claimed). A partially open plate blocking capacitor will reduce the grid-to-plate coupling and feedback and thus affect the output or oscillation. At the higher frequencies it is possible for weak feedback to occur through the grid-to-plate tube capacitance and sustain oscillation even though the plate blocking capacitor is faulty. A leaky plate capacitor may cause reduced or unstable output by loading the oscillator or by reducing plate voltage by adding to the normal current flow through a series resistance. Care should be exercised in selecting a replacement for a defective r-f choke since an improper replacement choke may cause unwanted oscillation by resonating with distri-

buted circuit capacitances or with the distributed capacitances of its own windings.

Incorrect Output Frequency. Changes in distributed circuit capacitance or reflected load reactance will affect the frequency of operation to some extent, although the design of this circuit provides fixed swamping capacitances to eliminate such changes. The largest change will be produced by a change of the tank circuit Q caused by shorted turns or poor soldered connections in the tank circuit. An incorrect output frequency resulting from a change of tube transconductance with age is normally corrected by slight readjustment of the tuning capacitor. Large changes in ambient temperature may affect the operating frequency of the oscillator. Such changes could occur through failure of an oscillator oven, changes in filament supply voltage, etc.

CLAPP OSCILLATOR (SEMICONDUCTOR)

Application.

The Clapp oscillator is used to produce a sine-wave output of constant amplitude and frequency within the r-f range. The circuit is generally used as a signal source in signal generators and as a variable-frequency oscillator for general use over the high- and very-high-frequency ranges.

Characteristics.

Uses a series-resonant L-C circuit to determine the frequency of oscillation.

Feedback is obtained through a capacitance-type voltage divider.

Frequency of operation is relatively independent of transistor parameters.

Operates Class C where wave form linearity is not important, and Class A where a linear waveform is required.

Frequency stability is good (better than that of the Colpitts oscillator).

Circuit Analysis.

General. The Clapp circuit is considered to be a variation of the Colpitts circuit discussed previously. It uses the stabilizing effect of a series-resonant tuned tank circuit, loosely coupled to the feedback loop, to provide good stability relatively independent of transistor parameters. It also offers capacitive tuning, using only one capacitor, without affecting the feedback ratio.

The collector is shunt-fed through radio-frequency choke RFC to keep r-f out of the power supply and avoid power supply shunting effects. Note that series feed cannot be used with the Clapp circuit because tuning capacitor C is in series with tank inductance. Thus a blocking capacitor in either the base or the collector lead is not required for this circuit. When the circuit is energized, Class A bias is supplied for starting by the bias voltage divider consisting of R_1 and R_B , and feedback to the base is applied through feedback divider capacitor C3. Grounding the common connection between the feedback divider capacitors provides the 180-degree phase reversal necessary to provide positive feedback from collector to base. The emitter resistor and capacitor combination acts in the same manner as an electron-tube grid-lead to provide essentially Class C bias after a few oscillations. R_E also acts as a dc thermal stabilizer for collector-current temperature variations. In a properly designed circuit, the proper feedback voltage divider capacitor ratio for stable feedback with the transistor used may be selected, independently of tank circuit design considerations, to provide oscillation over the desired range of operation. The output may be taken capacitively or by inductance coupling to the tuned tank circuit. With loose inductive coupling, the output obtained is very stable and relatively free of the detuning effects of loading, since the tank circuit is loosely coupled to the feedback loop and relatively independent of any change in transistor parameters.

Failure Analysis.

No Output. Since no blocking capacitors are employed and since the tank circuit is essentially unaffected by changes in transistor parameters, lack of output is usually limited to lack of feedback or improper bias voltages. An open or shorted transistor or an open or shorted feedback capacitor will stop oscillation. A shorted tuning capacitor C will also stop oscillator because it will permit the collector voltage on tank coil L to be shorted to the base. Poorly soldered connections may produce circuit losses sufficient to prevent oscillation, while changes in value or open bias resistors will probably reduce rather than stop oscillation completely.

Reduced or Unstable Output. Reduced output would most likely indicate a change in bias resistor values or a defective emitter bypass capacitor. An open or partially open emitter bypass would produce

excessive degeneration and perhaps complete cutoff, though the latter is very unlikely, whereas a shorted emitter bypass would probably be indicated by thermal instability. Frequency instability would be directly traceable to the tank circuit components and connections. An unstable output amplitude could be caused by an intermittent open or short in the bias circuitry or by a poor connection to the transistor or supply voltage. Lack of supply voltage regulation would normally be indicated by amplitude changes rather than by frequency changes.

Incorrect Output Frequency. Changes in distributed circuit capacitance or reflected load reactance will affect the frequency of operation to some extent, but can normally be corrected by resetting or adjusting the tuning capacitor. Large frequency changes will be produced by changes of tank circuit inductance caused by shorted turns or poorly soldered connections. At first glance it might appear that a shorted tuning capacitor would cause the frequency of oscillation to be determined by the inductance of the tank circuit alone (plus some distributed capacitance); however, for this condition oscillation could not occur because the shorted capacitor would short the collector voltage through the tank coil L to the base.

TUNED-PLATE TUNED-GRID OSCILLATOR

Application.

The tuned-plate tuned-grid (TPTG) oscillator is used to produce a sine-wave output of constant amplitude and fairly constant frequency within the r-f range. This circuit is generally used as a variable-frequency oscillator over the high- and very-high-frequency r-f ranges. It is not often encountered in Navy electronic equipment.

Characteristics.

Contains two parallel-tuned L-C circuits—one in the grid circuit and the other in the plate circuit of the electron tube—and uses the internal grid-plate tube capacitance for feedback.


Operates as Class C with automatic self-bias for ordinary, or power, operation and is seldom used for linear waveform applications.

Frequency stability is good when properly adjusted.

Circuit Analysis.

General. When a tuned L-C tank circuit is connected between the grid and cathode of an electron tube and a similar tank circuit is connected between the plate and cathode of the tube with coupling existing between them, sustained oscillation will occur when these tuned circuits are resonated to the same frequency. The amplitude of the oscillation is determined by the amount of feedback from plate to grid, and is also affected by the tuning of the two circuits. To provide the proper phase to sustain oscillation, both the grid tank and the plate tank are tuned to a slightly higher frequency than the resonant frequency at which operation is desired. At the operating frequency both tanks then offer an inductive reactance, and the phase shift through the grid-plate tube capacitance is of the proper polarity to sustain oscillation. The condition for proper phasing is that the inductive reactance of the grid tank circuit be less than the capacitive reactance of the grid-plate interelectrode capacitance at the operating frequency. To sustain oscillation, it is only necessary to supply the losses in the grid circuit, which because of the high-Q grid tank are relatively small. Consequently, only a small capacitance is needed to supply sufficient feedback, and the grid-plate interelectrode capacitance of the triode tube is adequate for this purpose. When a pentode is employed in the circuit, it is usually necessary to supply an external capacitor to provide the feedback, because of the low electrode capacitance inherent in the pentode.

Circuit Operation. The basic tuned-plate tuned-grid oscillator circuit is shown schematically in the following illustration. The grid tank consists of C_1 and L_1 , while the plate tank consists of C_2 and L_2 , no mutual inductance existing between L_1 and L_2 . Feedback occurs through the plate-grid capacitance, C_{gp} (shown in dotted lines), when both tanks are tuned to the same frequency. The feedback amplitude can be controlled by detuning the grid tank with C_1 . Thus, differences in interelectrode capacitance between tubes can be accommodated with no adverse effects.

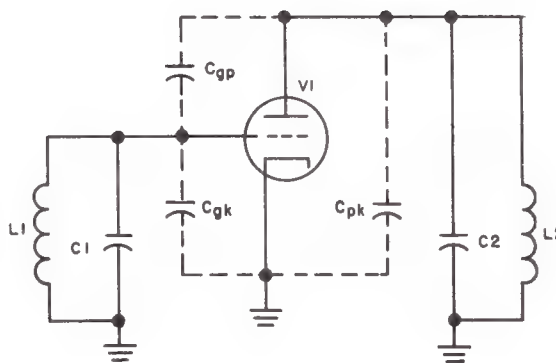


Basic Tuned-Plate Tuned-Grid Oscillator

For simplicity, biasing and plate voltage feeds are not shown in the basic circuit, but are discussed when applicable in the following discussion. Since capacitive feedback determines oscillation, this circuit is a better oscillator at the higher frequencies and is not often used in the low or medium-frequency ranges. Although other configurations may be used, this circuit lends itself conveniently to grounded-cathode operation. The grid tank basically controls the excitation and operating stability, and the grid-cathode tube capacitance is in parallel with the tank, being effectively swamped by the tank capacitance. Likewise, the plate tank capacitor effectively swamps the plate-cathode tube capacitance, and the plate tank is primarily used to determine the operating frequency. Once oscillation occurs near the desired frequency, the plate tank is tuned to set this frequency to the desired value, while the grid tank is adjusted for proper excitation and maximum stability.

Upon examination of the shunt-fed tuned-plate tuned-grid oscillator circuit (following illustration), it is evident that shunt grid-leak bias (C_g, R_g) and shunt plate feed are used, with C_c serving as the plate coupling and blocking capacitor. The radio-frequency choke, RFC, keeps the rf out of the plate supply. L_1 ,


C1 is the grid tank and L2, C2 is the plate tank. The grounded-cathode connection is shown since it permits grounding the tuning-capacitor rotors to eliminate any body capacitance effects on tuning. The use of shunt grid-leak bias isolates the grid tank as far as dc is concerned and reduces circulating grid current, although series grid bias could be used as well. Sometimes a series resistor is included between cathode and ground, to provide protective bias in the event of non-oscillation. Both the plate and grid capacitors are sufficiently large so that the tank circuits are affectively coupled to the grid and plate for r-f, yet isolated as far as dc is concerned. Grid-leak bias action and automatic amplitude regulation are the same as described previously in other oscillator discussions. The feedback action takes place as described above, making use of the coupling between the plate and grid tanks provided by the grid-plate tube capacitance. At radio frequencies which require the use of relatively large inductors and when appreciable power is used, it is important for the tanks to be shielded or turned at right angles to each other, to prevent possible inductive coupling effects which would deteriorate circuit performance.

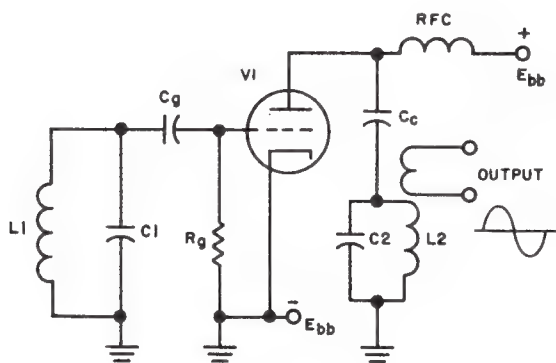Output is obtained by inductive coupling to the plate tank, although a capacitive connection may be made if desired.



Shunt-Fed Tuned-Plate Tuned-Grid Oscillator

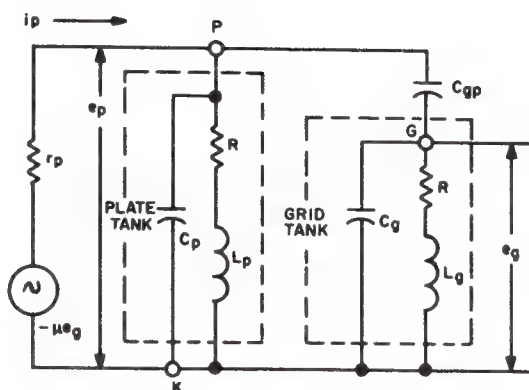
Detailed Analysis. The equivalent circuit of the tuned-plate, tuned-grid oscillator is shown in the following illustration.



Basic TPTG Equivalent Circuit

Since the oscillator operates below the resonant frequency of the tank circuits, both the plate tank and the grid tank will appear resistive and inductive to the signal source $-\mu e_g$.

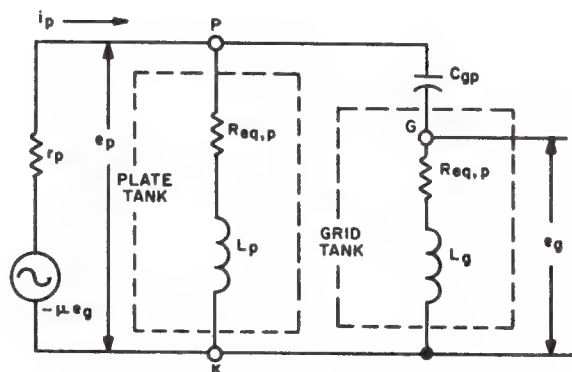The following figure shows the tank circuits replaced by their equivalent values of modified equivalent resistance and inductance at the operating frequency. Notice that this equivalent circuit closely resembles that of the Hartley oscillator which was shown previously.




Modified Tuned-Plate, Tuned-Grid Equivalent Circuit

Therefore, the operation of the TPTG oscillator, at the operating frequency, is basically that of a Hartley

oscillator without the benefit of mutual inductance. However, adjustment of the tuned circuits to meet this condition is rather critical. Note from the equivalent circuits that the basis frequency-determining components are the plate tank and the plate to-grid capacitance of the tube, C_{gp} . The plate tank, therefore, is tuned to establish the frequency of operation, while the grid tank is tuned to establish the proper phasing and amount of feedback voltage for grid excitation.

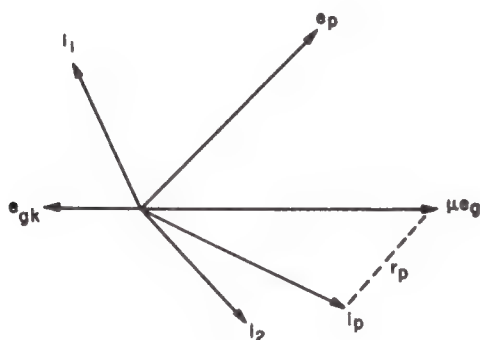Vector Diagram. The relationship between the current and voltages in the circuit is shown by the following vector diagram.



Tuned-Plate Tuned-Grid Vector Diagram

The constant voltage generator output μe_g is the reference voltage. It is assumed that there is no inductive coupling between the plate and grid tank circuits and that the frequency of oscillation is slightly lower than the resonant frequency of the tanks. Since the tank circuits are tuned to a higher frequency than the oscillation frequency, they offer an inductive reactance. Also, since the feedback must occur through the grid-plate inter-electrode capacitance, the grid tank must offer a lower inductive reactance than the capacitive reactance of the electrodes (the grid-cathode and plate-cathode capacitance is assumed to be a part of the tuned circuits). Therefore, the inductive plate tank causes e_p to lead μe_g by some angle dependent on the circuit values, and $i_p r_p$ lags. The inductive plate tank current i_2 also lags e_p somewhat less than 90 degrees. Since the reactance of C_{gp} is greater than the grid tank reactance, i_1 leads e_p by almost 90 degrees. Voltage e_{gk} is developed across the inductive grid coil (tank) and, therefore, leads i_1

by almost 90 degrees. This voltage is exactly 180 degrees out of phase with μe_g , satisfying the requirement for oscillation.

Failure Analysis.

No Output. If something happens to either of the tank circuits so as to cause a large enough shift in that tank's resonant frequency, the circuit will not oscillate, and only contact bias will be developed. Plate current, therefore, will be higher than normal and the standard operating value of grid bias will not be obtained. Excessive losses if present in the tank circuit will prevent sustained oscillation. Changes in the values of grid-bias components R_g and C_g will affect the operating bias and change the amplitude of oscillation. A large change may prevent oscillation, whereas a small change may not have any noticeable effect. Although loss of tube gain will reduce the amount of feedback, the TPTG circuit is a vigorous oscillator when properly adjusted, so that considerable reduction in tube amplification is necessary to reduce oscillation. Too close coupling of the output circuit to the plate tank will produce the same effect as a lossy tank circuit, and reflected reactance may cause sufficient detuning to prevent oscillation. In the shunt-fed circuit, a defective radio-frequency choke RFC or coupling capacitor C_c may cause loss of oscillation since the oscillator depends on these components for isolation from the low a-c impedance of the plate supply and for coupling of the a-c signal to the tuned plate tank.

Reduced or Unstable Output. A relative indication of oscillator output is provided by the amount of bias voltage developed across R_g . Variation from the standard operating value is an indication of abnormal operation. A reduction of applied plate voltage will decrease the output. Therefore, an unregulated voltage source will produce output amplitude variations and probably some frequency change or instability. In this respect, the tuning of the grid tank is important, as is has a great effect on the stability of operation. A leaky coupling capacitor C_c may cause reduced or unstable output by loading the oscillator or by reducing plate voltage by adding to the normal current flow through a series voltage dropping resistance. Care should be used in selecting a replacement part for a defective r-f choke, since an improper replacement may cause unwanted oscillation by resonating with distributed circuit capacitances or with the distributed capacitances of its own windings.

Similar care should be exercised in replacement of a defective tube since the oscillator depends on inter-electrode capacitances as a part of the tuned circuits. Variations of this physical capacitance from one tube to another may be enough to seriously detune the oscillator. It is good practice to try more than one replacement tube if the first substitution does not achieve the desired results in frequency of operation and stability. Realignment of circuit components to compensate for tube substitution should not ordinarily be necessary.

Incorrect Output Frequency. Assuming that all component parts of the circuit are known to be satisfactory, changes in output frequency can be compensated for by realigning or tuning the tank circuits. Detuning effects caused by reflected load reactance will affect the frequency of operation to some extent, being most noticeable on the very-high-frequency ranges. Changes in tank inductance caused by shorted turns, particularly in the grid circuit, will result in a different frequency of operation, if oscillation still occurs. Large changes in ambient temperature, such as may occur through failure of an oscillator oven or changes in filament supply voltage, may affect the operating frequency of the oscillator. Changes in distributed circuit capacitances will also affect the operating frequency. Therefore, care should be used in the removal and replacement of parts, in order not to disturb the distributed capacitance inherent in the physical parts and wiring of the circuit. The effects of tube substitution were discussed above.

Series-Fed Tuned-Plate Tuned-Grid.

Series plate feed is easily accomplished with the tuned-plate tuned-grid circuit by connecting B + and the RFC in place of the ground to L2 (refer to shunt-fed schematic), connecting the plate directly to the top of L2, and bypassing the bottom end of L2 to ground with C_c . Circuit operation and failure analysis are exactly the same as for the shunt-fed circuit with two exceptions: (1) With the series connection, unwanted low-frequency (or high-frequency) parasitic oscillations caused by resonances of RFC and C_c or of RFC and C_{pk} are eliminated. (2) The effect of dc in the tank circuit must be considered; since the capacitor and inductor must withstand both d-c and r-f voltages, their insulation to ground becomes an important factor.

ELECTRON-COUPLED OSCILLATOR (ELECTRON TUBE)

Application.

The electron-coupled oscillator is used to produce an r-f output of constant amplitude and extremely constant frequency, usually within the r-f range. The circuit is generally used in any type of electronic equipment where stability is required, and the output waveform need not be a sine wave, as some distortion of waveform is normal.

Characteristics.

Uses the shielding effect between the plate and screen grid in a tetrode or pentode to isolate the plate load from the oscillator, and employs the electron stream between the screen grid and plate to couple the oscillator output to the plate load.

Operates with practically any circuit configuration of the L-C or R-C type, but is mostly used with L-C circuits.

Frequency stability of circuit is very good—better than that of the previously discussed types of oscillators.

Circuit Analysis.

General. In the triode-type oscillator, variation of the plate supply voltage and reflected load reactance causes slight frequency variations because the plate is involved in the feedback loop. By using the cathode, grid, and screen grid of a tetrode or pentode as the oscillator, the plate is eliminated from the feedback loop. Since the plate current in the tetrode or pentode is relatively independent of plate voltage changes and remains nearly constant for a specific value of screen voltage, variations in the plate load circuit have practically no effect on the other elements. Connecting the screen grid as the plate of the triode oscillator electrostatically shields the plate of the pentode or tetrode, and couples the output of the oscillator to the load through the plate electron stream.

Any of the previously discussed oscillator circuits may be used for the oscillating portion of the electron-coupled oscillator circuit, and the electron tube can be either a tetrode, a pentode, or a beam-power tube.


The tetrode is a four-element tube, which uses a screen grid to accelerate the flow of electrons from the cathode to the plate under control of the control grid. As the electrons pass through the screen grid to the more positive plate, some of them impinge on the screen grid and produce a screen-grid current, which amounts to about one tenth of the plate current. Secondary electrons are emitted by the portion of the electron stream striking the screen grid and by the stream striking the plate. Normally, when the plate voltage is higher than the screen-grid voltage, these secondary electrons are attracted to the nearest element, plate or screen, and merely increase their respective currents. When the plate voltage is near or below the screen-grid voltage, space charge forms a virtual cathode between the screen grid and plate and thus nullifies the effect of electron coupling. Therefore, the screen grid is usually supplied from the plate source through a series voltage-dropping resistor, and it is bypassed to ground with a capacitor to provide an electrostatic shield. The beam-power tetrode uses special construction and beamforming plates connected to its cathode to provide the same effect. The pentode utilizes a fifth element (the suppressor grid), usually connected to the cathode internally and located between the screen grid and plate, to eliminate secondary-emission effects. In some tubes the suppressor grid connection is brought out externally, and may be connected to ground, screen grid, or plate as desired. In the electron-coupled oscillator, it is always connected to provide an effective electrostatic shield between the screen grid and plate, in order to eliminate coupling of load variations back to the oscillator circuit. When a pentode with an internally connected suppressor is used in the electron-coupled circuit, the cathode is always grounded; otherwise, full electron coupling is not obtained and a less stable circuit results.

The electron-coupled plate load may be another tuned tank circuit, a radio-frequency choke, or a resistor. The tuned plate tank may be operated on the same frequency as the grid tank, or it may be tuned to a harmonic, operating as a frequency multiplier. In test-equipment applications, a choke or a resistor (instead of a tank circuit) is usually used with light loading to assure maximum frequency stability. A properly designed electron-coupled oscillator provides the stability of a master oscillator-power amplifier circuit combination with only one tube, and it has the power output of an equivalent triode operating at the

same plate voltage and current.

When a resistor or choke is used in the output circuit, the waveform is not exactly sinusoidal because the plate current does not vary linearly with the screen-grid current. Although the control grid varies the screen-grid current linearly, and these oscillations effectively modulate the electron stream between the screen grid and plate, not all of the current controlled by the grid reaches the plate. Some of the electrons in the screen-plate region are attracted back to the screen grid, while others are shunted to the cathode by the suppressor electrode. Therefore, at any particular instant when the screen-grid current is being slightly increased, the plate current may or may not be increased by the same amount—in fact, it may actually decrease. Hence, the output waveform, which is the result of plate current flow through the load resistance, will not be exactly like the screen-grid waveform; it will be similar, but distorted. If a plate tank or an L-C filter is employed, the distortion will be corrected and a nearly sinusoidal waveform will result.

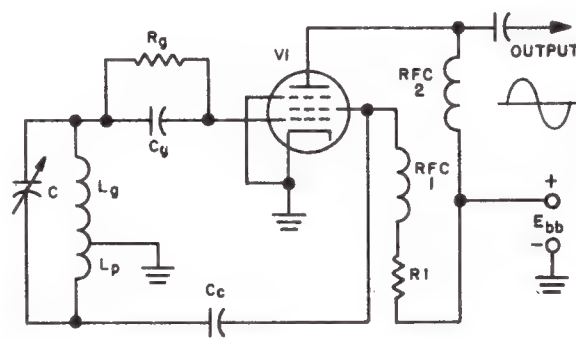Circuit Operation. The schematic of an electron-coupled oscillator using a pentode tube is shown in the following illustration. The oscillator section utilizes the basic Hartley shunt-fed circuit, with a series grid leak as discussed previously in the Hartley oscillator circuit, and with the screen of the pentode acting as the triode plate.




Pentode Electron-Coupled Oscillator

The E.C.O. load is taken from the plate circuit of the pentode. Operation of the oscillator portion is identical to that of the previously discussed Hartley oscillator. In the electron-coupled version, however, plate

voltage is applied to the pentode through RFC2 to keep r-f out of the power supply, and the output is capacitively coupled to the load (usually the next r-f amplifier stage). To insure that the screen of the pentode remains at a lower minimum dc potential than the plate, a dropping resistor, R_1 , is generally used, but may be omitted in some versions of this circuit. Since the screen is above ground at r-f potential, RFC1 is necessary to block the rf from the power supply. If R_1 is a high-value resistor of say 5000 ohms or more, RFC1 may be omitted, because the high resistance of R_1 is comparable to the reactance offered by the r-f choke. Note that the suppressor element is connected to the cathode, which is grounded. If the cathode were above ground, the suppressor could not be connected to the cathode or it would capacitively couple the oscillator into the plate circuit and destroy the shielding effect of electron coupling. Since in this instance the cathode is grounded, the suppressor performs its normal function of eliminating secondary emission and isolating the plate and the screen grid.

The oscillator normally operates Class C, and for each pulse of oscillation a corresponding pulse is produced in the plate circuit through modulation of the electron stream. Thus electron coupling exists between the screen grid and plate. Plate load variations produce plate voltage and current changes, but, since a change of pentode plate voltage has little effect on plate current, these changes have negligible effect on the screen-grid voltage and current. Hence, the stability of the oscillator remains relatively unaffected by load variations. It should be noted that, although the pentode is considered to be unaffected by supply voltage variations, only the tetrode circuit can be designed by selection of proper plate and screen voltages to be completely independent of supply variations. The advantage of the pentode arrangement is that grounded-cathode operation can be used to provide an electrostatic shield between plate and grid or screen, and secondary emission effects need not be considered.

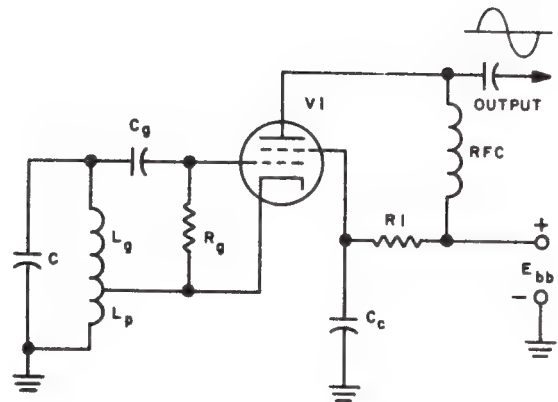The tetrode version of the electron-coupled oscillator which is particularly applicable to beam-power tubes is the grounded-screen circuit shown in the following illustration.



Tetrode Electron-Coupled Oscillator



In this circuit, the shunt-fed Hartley is used; the operation and components of the circuit are the same as just described for the pentode E.C.O. illustrated in the accompanying figures, with the following exceptions.

Since there is no suppressor element in a tetrode tube, secondary emission effects are encountered. Therefore, R_1 is needed to keep the plate voltage always higher than the screen-grid voltage, in order to avoid formation of a virtual cathode within the space-charge region between the screen grid and plate. Because the screen is grounded by C_c , an electrostatic shield is provided between the oscillator and output sections. Since the cathode is above ground and cathode current flows through the L_p portion of the tank, the full current of the tube is utilized to provide feedback through the tank inductor. Actually, this is a series platefed connection. Since the plate current of the tetrode is independent of plate voltage, being controlled by the potentials on the screen and control grids, no undesired coupling results from the flow of cathode current through L_p . The original derivation of this circuit utilized a variable resistor as R_1 , and the screen-grid voltage was adjusted for maximum stability. Since a slight increase of screen voltage (caused by supply or load variations) decreases the frequency,


while a similar change of plate voltage increases the frequency, R_1 can be adjusted for specific screen voltage where a frequency change in one direction will cancel a corresponding change in the other direction and result in freedom from frequency changes due to supply voltage variations.

It should be noted that, if a pentode is used in the tetrode circuit, the suppressor should not be connected to the above-ground cathode, or capacitance coupling will exist between the suppressor and ground and inject an undesired coupling between the oscillator and output sections. Instead, the suppressor grid should be tied to the screen or the plate, making the tube effectively into a tetrode; a pentode with an internally connected suppressor is not usable in this circuit.

A number of electron-coupled-oscillator variations using the oscillators previously discussed are also illustrated. These circuits are drawn in their most usually encountered form; namely, with a plate output tank which may be operated either on the fundamental or a harmonic. Circuit operation is the same as discussed for the basic oscillator with the addition of the electron-coupled circuit theory just completed. The tuned-plate tuned-grid version is not shown because it is usually in the form of a crystal-controlled electron-coupled oscillator, in which the grid tank is replaced by the crystal and the plate tank is the output of the oscillator. This circuit version is discussed later in this section.

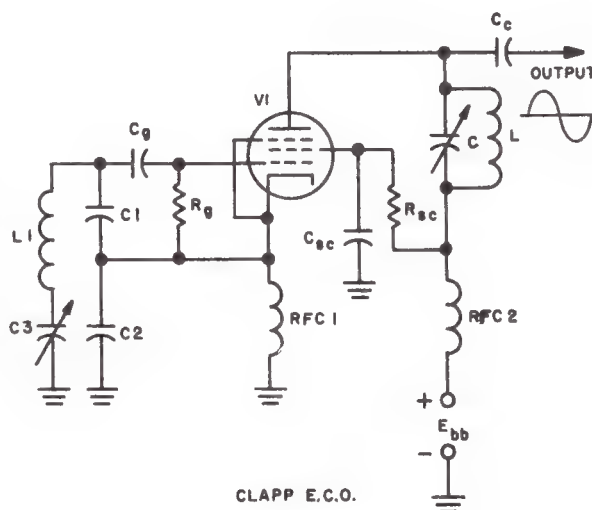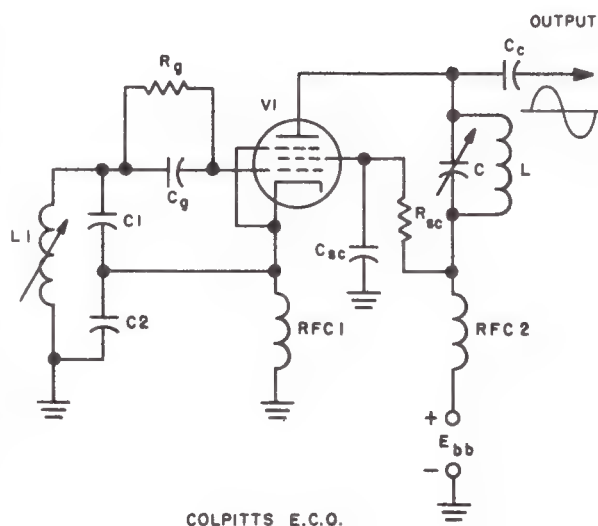

Typical E.C.O. Circuits

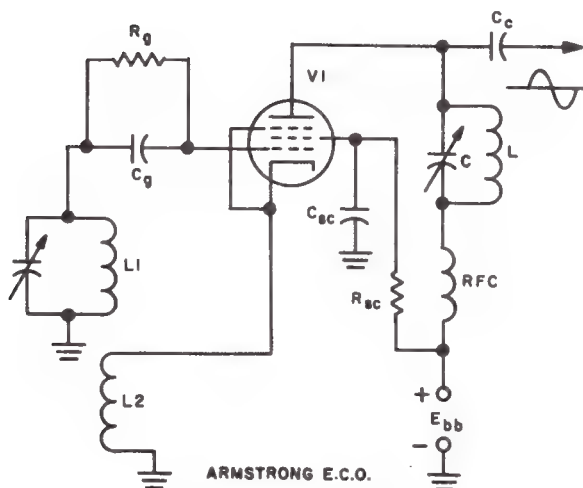

Failure Analysis.

No Output. Failure of oscillation would cause no output, and could result from the same effects described in the failure analysis section of the Hartley oscillator. In addition, lack of supply voltage caused by open components or a short from plate to ground would effectively stop output. Actually, in this type of circuit tube emission could drop to the point where there is sufficient current for the oscillator section, but practically none for the plate. Therefore,

the circuit should be considered as basically a two-section tube, and checked for oscillator output first and then for continuity through the plate circuit. If the plate output circuit is known to be complete with all components in good operating condition, and the oscillator is operating, lack of plate output indicates a faulty tube.

Reduced or Unstable Output. In addition to those causes indicated for the basic oscillator in the Hartley oscillator circuit discussion, the following should be considered: If the basic oscillator is unstable or has a reduced output, then, with all other conditions equal, the plate output will also be unstable or reduced. Thus the oscillator should first be investigated for proper operation. Since the screen voltage determines the amount of plate current drawn by the tube, a reduction of screen voltage would have a more noticeable effect on the output before it dropped below the point where oscillation could be sustained. An increase in resistance of the screen dropping resistor, if used, is a primary cause of reduced output. Where the plate voltage is supplied through a load resistor, it is common for a high resistance to develop, reducing both the plate voltage and the output. This condition can result in instability if the plate voltage becomes lower than the screen voltage. If the output circuit of the plate includes a tuned tank circuit, a normal increase of output is to be expected when the tank is tuned to the same frequency as the oscillator or to a low-order harmonic. Therefore, any effects causing tank detuning will immediately result in a reduced output. When instability is produced by load variations, it can immediately be assumed that the electron coupling is involved; in this case, the circuit should be checked for capacitive coupling between screen and plate or for a change in voltage ratios due to an excessive voltage drop or a short circuit in either the screen or plate. When the screen current increases abnormally, secondary emission effects or a defective (open) plate circuit can be suspected.

Incorrect Output Frequency. Since the output frequency is determined basically by the oscillator portion of the tube, any change in frequency with normal output amplitude indications would indicate that a change of oscillator components or voltages is

the most probable cause. If the oscillator frequency change is not due to components in the oscillator itself, the electrostatic shielding between the plate and screen sections has probably deteriorated because of open or shorted bypass capacitors, changes in tube voltages, or the presence of stray capacitive coupling from other causes.

ULTRAUDION OSCILLATOR (ELECTRON TUBE)

Application.

The ultradudion oscillator is used to produce a sine-wave output of constant amplitude and fairly constant frequency within the r-f range. It is generally used as a variable-frequency oscillator on the very-high and ultra-high-frequency ranges.

Characteristics.

Uses a parallel tuned L-C circuit to determine the frequency of oscillation, with a capacitive voltage divider form of feedback to control oscillation.

Operates Class C with automatic self-bias for ordinary operation.

Frequency stability is fair-similar to that of the Colpitts operating at high frequencies.


Oscillates easily at frequencies which are too high for other types of oscillators, or at which they are very unstable.

Has only one tuning control, and requires only two leads for connections between the tank and the tube.

Circuit Analysis.



General. The ultradudion circuit is essentially a series-fed Colpitts oscillator with a parallel-tuned tank circuit for determining the frequency of operation. The previous discussion of the Colpitts oscillator circuit is generally applicable to the ultradudion oscillator. The following discussion will be limited to pointing out the basic differences of operation between the two circuits and any special considerations necessary for high-frequency operation.

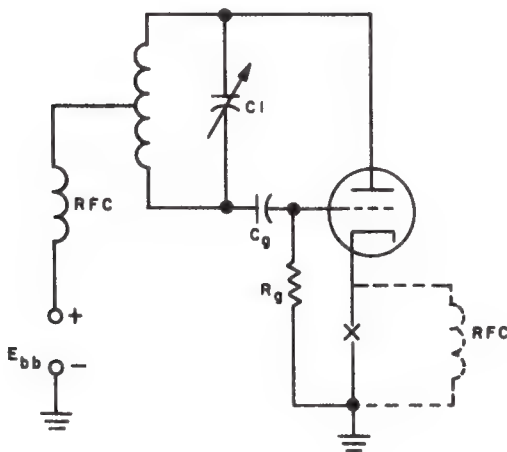Circuit Operation. The ultraudion circuit is shown schematically in the following illustration. The tuned tank circuit consists of L and C₁, connected between the plate and grid of the tube. Shunt grid-leak bias is used (C_g and R_g) because of the series plate feed.



Ultraudion Circuit

The radio-frequency choke shown in dotted lines in the cathode circuit is sometimes inserted (open cathode lead at x), to minimize the effects of stray wiring capacitance; it is usually self-resonant at the frequency of operation. Although the frequency is determined by the tank circuit, the feedback is controlled by the ratio of grid-cathode and plate-cathode electrode capacitance plus any stray wiring capacitance. Operation is exactly the same as previously discussed for the Colpitts oscillator circuit. To visualize the circuit operation and component relationships, refer to the equivalent circuits shown in the illustrations. Figure A shows the basic ultraudion without the cathode RFC, and figure B shows the arrangement when the cathode choke is used; each circuit will be discussed separately.

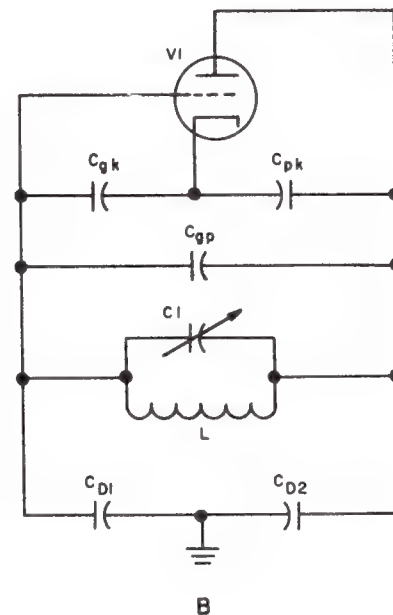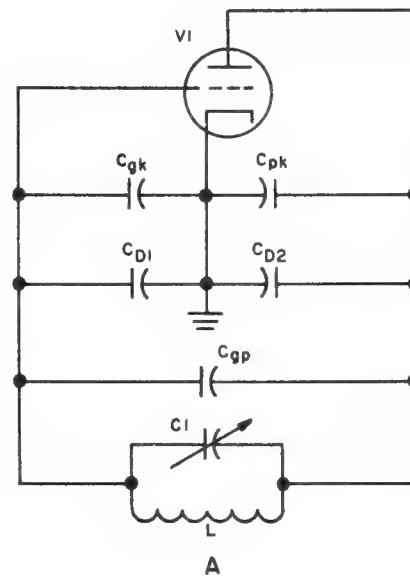

Simplified Equivalent of Ultraudion Circuit

Since this oscillator is designed for extremely high-frequency operation, assume that the tank inductor L is merely a single wire loop of small diameter connected between the grid and plate, so that the inductor includes the leads to the tube as part of the tank. For the moment neglect C_1 ; since the inductor is connected between the plate and grid, it is evident that the grid-plate tube capacitance is in shunt with the inductor and forms a part of the tuned circuit, as shown in A. The grid-cathode and plate-cathode tube capacitances form a voltage divider between grid and plate, with the cathode at ground potential. Likewise, the distributed wiring capacitances C_{d1} and C_{d2} are in parallel with the voltage divider and, since the tube-element capacitances are small, they form a major portion of the capacitance in the voltage divider. Referring to the Colpitts theory, it is seen that C_{gk} and C_{pk} in series form the capacitance across the tank inductor. The tube-element (interelectrode) capacitance is usually small, with the grid-plate capacitance being larger than either C_{gk} or C_{pk} . Therefore, the grid-plate capacitance acts as a swamping capacitor across the tank, being equal to, and in most instances greater than, the total series grid-cathode and plate-cathode capacitances. Thus, when C_1 is added across the tank inductor, the tank circuit is relatively independent of the feedback capacitors and is the primary frequency-determining component. Where the stray wiring capacitance is large, it assumes more control over frequency than the tube capacitance does; therefore, disturbing the wiring may cause extreme detuning of the circuit.

To eliminate this stray capacitance effect and allow the tube capacitance alone to control feedback, the arrangement of B is used. In this case the cathode is above ground, as the RFC is chosen to resonate with its self-capacitance somewhere within the tuning range. Wiring and stray capacitances to ground effectively form a balanced capacitive divider across the tank circuit, but have no effect on the feedback circuit. Thus the stray wiring capacitance affects the frequency of operation to some extent, but it does not affect feedback; consequently, the tube that is most effective for the frequency of operation desired can be used.

Failure Analysis.

No Output. Loss of, or improper, feedback will result in non-oscillation, as evidenced by a lack of grid voltage across grid leak R_g and by a high plate

current because of operation near zero bias. Since the capacitance to ground of the measuring probe will change the feedback capacitance ratio at the frequencies used, a grid voltage measurement to detect non-oscillation is not as effective as at lower frequencies and in other oscillator circuits. High plate current is usually a more positive indication. At extremely critical frequencies, change of lead dress can produce stray-distributed-capacitance swamping in the unbalanced circuit. Loss of tube gain will also reduce output and, if sufficient, will cause a lack of oscillation. Tank circuit losses are more serious at the very high frequencies because the resistance introduced will prevent operation. Thus poor soldering or shorted turns will have a greater effect than at lower frequencies. Changes in the grid-leak resistance or grid blocking capacitor will also affect operation, and small changes will easily stop oscillation at the higher frequencies. An open or high-resistance connection in the cathode RFC (when used) or the plate RFC will also result in a lack of output.

Reduced or Unstable Output. Low plate voltage or too high a value of grid-leak resistance will reduce the output. Poor soldered connections or high-resistance joints will also reduce the output. Unstable operation will occur if the grid-leak time constant changes because of a change in the component values of C_g or R_g . If present in a sufficient amount, stray capacitance which affects the feedback voltage will also produce instability. A reduction of filament emission will affect both the output and stability. Large changes in ambient temperature may affect output, as well as operating frequency. Tube substitutions may be critical, particularly at the higher frequencies, because of minor variations in interelectrode capacitance from one tube to another. More than one replacement tube should be tried if the first substitution does not achieve the desired results in output frequency and stability.

Incorrect Output Frequency. Any change in wiring-to-ground capacitance or lead length will affect the frequency. Changes in the tank circuit will have the greatest effect, and changes in the grid-plate capacitance and the grid- or plate-to-ground stray capacitance will have less effect, with the grid-cathode and plate-cathode variations having the least effect. Changes in the plate voltage will produce a greater frequency change at the higher frequencies than at the lower frequencies. The effects of tube

substitution and ambient temperatures on output frequency were discussed above.

R-C PHASE-SHIFT OSCILLATOR (ELECTRON TUBE)

Application.

The R-C phase-shift oscillator is used to produce a constant-amplitude, constant-frequency, sine-wave output.

Characteristics.

Utilizes a single-stage amplifier with resistance-capacitance network to provide in-phase feedback.

Output frequency in audio range; usually fixed-frequency, but may be variable for certain applications.

Frequency stability good.

Operated Class A to obtain a sinusoidal output.

Circuit Analysis.

General. In the basic circuit shown in the accompanying illustration, a sharp cutoff, pentode-type tube is used as the amplifier tube; however, a triode tube can be employed in a similar circuit. Bias voltage is developed across cathode resistor R_4 . Cathode bypass capacitor C_4 , by virtue of its filtering action, keeps the bias voltage relatively constant and places the cathode at signal-ground potential. The sine-wave voltage is developed across plate-load resistor R_6 ; capacitor C_6 is the output coupling capacitor. Any variation in plate current will cause a corresponding change in plate voltage. These plate voltage variations will also be present at the grid of the tube, since the plate is coupled to grid through the phase-shift network, Z_1 .

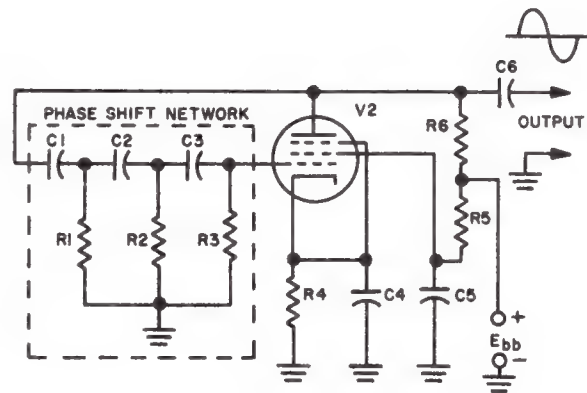



Figure A-465

R-C Oscillator Circuit

The operating condition for oscillation is a function of the amount of bias established by the cathode bias resistor, R_4 . The use of degenerative feedback (cancellation) and regenerative feedback (reinforcement) in the circuit simultaneously for undesired and desired frequencies is made possible by the action of the phase-shift network, Z_1 . The phase-shifting network is comprised of three separate R-C sections; each section is effectively a series R-C circuit. The three R-C sections are designated as C_1, R_1 ; C_2, R_2 ; and C_3, R_3 . The discussion given in the following paragraphs describes the action of only one series R-C circuit, but applies to all three sections.

Phase-Shift Network. It is the property of a capacitor that an a-c voltage applied across the capacitor

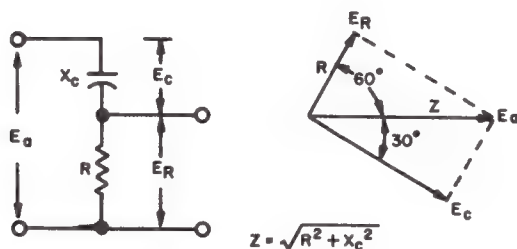lags the current through the capacitor by 90 degrees. In a series circuit containing both resistance and capacitance, however, the voltage lags the current by some angle less than 90 degrees. A series resistance-capacitance circuit is shown in the accompanying illustration, together with its vector diagram.



Vector Analysis of R-C Circuit

The values of capacitive reactance (X_c) and resistance (R), chosen for each section of the phase-shift network, are such as to cause a total impedance (Z). Assuming that this impedance represents the first section of the phase-shift network, it is across this section that plate-voltage variations are applied. The applied voltage is represented in the vector diagram as E_a . The circuit current passes through resistor R and, since this current leads the applied voltage E_a by 60 degrees, the voltage drop E_R across resistor R leads the applied voltage E_a by 60 degrees. The voltage, E_R , developed across resistor R is applied to the second section and is shifted another 60 degrees in phase, so that the output voltage of the second series R-C section leads E_a by 120 degrees. The output voltage of the second R-C section is applied to a third section, and is again shifted an additional 60 degrees to lead the applied voltage E_a by a total of 180 degrees. The output of the third R-C section is applied to the grid of the tube.

Referring to the vector diagram, it is apparent that, since the capacitive reactance (X_c) varies with frequency, the frequencies above or below the frequency for which the circuit is designed will be shifted more or less than 60 degrees by each section of the network, so that the total phase shift contributed by all three sections will be something more or less than exactly 180 degrees. In this manner, the circuit is

caused to oscillate at only one frequency; that is, the frequency which is shifted exactly 180 degrees by the phase-shift network, Z1.

By increasing the number of phase-shift sections comprising the network, the losses of the total network can be decreased; this means that the additional sections will each be required to have a lesser degree of phase shift per section so that the over-all phase shift of the network remains at 180 degrees for the desired frequency of oscillation. Assuming that the values of R and C are equal in all sections, networks consisting of four, five, and six sections are designed to produce phase shifts per section of 45, 36, and 30 degrees, respectively.

Circuit Operation. Oscillations are initially started in this circuit by small changes in the B-supply voltage or by random noise. If it were not for the action of the phase-shift network, Z1, the voltage variations fed from the plate back to the grid of the tube would cancel the plate-current variations, since the tube introduces a polarity inversion between the grid and plate signals. For example, if the plate-voltage variation at any instant of time was positive, the positive variation would be present on the grid. This positive-going grid voltage would then cause the plate current to increase, in turn causing the plate-voltage variation to go negative and, thus, cancelling out the original grid-voltage variation.

Assuming that the plate-voltage variations are applied to the grid 180 degrees out-of-phase with respect to the initial grid-signal voltage, maximum degeneration (or cancellation) will occur. However, if the plate-voltage variations fed back to the grid approach zero-degree phase difference, minimum degeneration will occur. Therefore, if the phase difference between the plate-voltage variations and the initial grid-signal voltage is exactly zero (in phase), the plate-voltage variations will reinforce the grid-signal voltage at any instant of time, causing regeneration; furthermore, these variations will be amplified by the tube and reapplied to the grid, amplified again, and so on, until a point of stage equilibrium is reached and no further amplification takes place. The phase-shift network provides the required phase shift of 180 degrees to bring the voltage fed back to the grid in phase with the initial grid-signal voltage and cause regeneration. The circuit then oscillates under these conditions with relatively constant amplitude.

The phase-shift oscillator is designed primarily for fixed-frequency operation; however, the operating frequency can be made variable by using variable resistors or capacitors in the phase-shift network. An increase in the value of resistance or capacitance will decrease the operating frequency; a decrease in the value of resistance or capacitance will increase the operating frequency. In several practical applications of this circuit, three or more fixed R-C sections are employed together with a variable section to provide a limited range of output frequencies which are determined by the setting of a variable capacitor. In this circuit variation, the fixed R-C sections use values of R and C which will provide a phase shift somewhat less than 180 degrees at the operating frequency desired, and the last (variable) R-C section completes the required phase shift to exactly 180 degrees. The operating frequency is then determined by the setting of the variable capacitor.

Failure Analysis.

No Output. Assuming that the applied voltages are correct, the lack of output results from two possible conditions; either the gain of the tube has decreased to a point where gain is insufficient to overcome the losses inherent in the phase-shift network, or one or more sections of the phase-shift network is possibly defective and does not provide proper phase shift of the plate-to-grid feedback signal.

In some cases, the phase-shift network must be replaced as an assembly if found defective. In cases where the phase-shift network is composed of individual resistors and capacitors, the individual components may be checked and replaced if found defective.

Reduced Output. Reduced output is generally caused by decreased stage gain; however, a small reduction in gain may cause oscillations to cease before any appreciable decrease in output can be detected.

Nonsinusoidal Output. Nonsinusoidal output results when the tube is operating on the nonlinear portion of its characteristic curve. Such operation results from a change in B-supply voltage or bias volt-

age which causes partial or complete clipping of the output waveform.

Output Frequency Incorrect. Since the values of resistance and capacitance that form the phase-shift network determine the operating frequency of the oscillator, any change in component values will be reflected as a change in the frequency of oscillation.

R-C PHASE-SHIFT OSCILLATOR (SEMICONDUCTOR)

Application.

The R-C phase-shift oscillator is used to produce a sine-wave output of relatively constant amplitude and frequency.

Characteristics.


Utilizes R-C network to provide feedback.

Eliminates need for inductors in resonant circuit.

Output frequency is usually fixed within the range of 15 Hz to 200 kHz per second, although the circuit can be arranged to provide an output which can be varied over a wide range of frequencies by changing R or C.

Circuit Analysis.

General. A sine-wave output may be obtained from an oscillator using an R-C network in lieu of an L-C network. The R-C network determines the frequency of oscillation and provides regenerative feedback from the output circuit to the input. In the common-emitter circuit configuration for transistors, the signal between the base and collector is shifted in phase by 180 degrees; therefore, an additional 180-degree phase shift is necessary to provide the correct feedback signal when returned from the output circuit to the input in order to sustain oscillations. The feedback signal of proper phase relationship is obtained using a network consisting of three equal R-C sections; each section produces a 60-degree phase shift at the desired frequency of operation. In the accompanying circuit schematic, the three R-C sections are designated as C1, R1, C2, R2; and C3, R3.

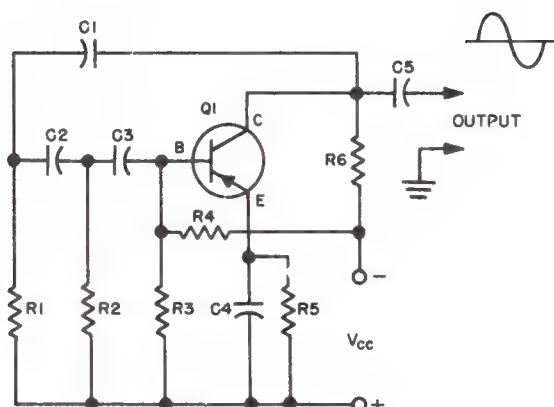

R-C Phase-Shift Oscillator Using PNP Transistor

Phase-Shift Network. The current in a series circuit comprised of resistance and capacitance is determined by the applied voltage divided by the series impedance of the components

$$(I = \frac{E}{Z}).$$

Since a series R-C circuit exhibits capacitive reactance, the current leads the applied voltage by a specific phase angle. The phase angle is determined by the relationship of resistance and capacitance. The voltage drop produced across the resistance is determined by the current through the resistance and therefore leads the applied voltage by a given phase angle.

For a vector analysis of the phase-shift network, refer to the discussion given for the electron tube R-C phase-shift oscillator.

At least three R-C sections are required to provide the 180-degree phase shift needed to produce a positive (in-phase) feedback voltage. The values of resistance and capacitance for a three-section network are chosen so that each section of the network will provide a 60-degree phase shift at the desired frequency.

The R-C phase-shift oscillator is normally fixed in frequency, but the output frequency can be made variable over a range of frequencies by providing ganged variable capacitors or resistors in the phase-shift network. An increase in the value of either R or

C will produce a decrease in the output frequency; conversely, a decrease in the value of either R or C will produce an increase in the output frequency.

By increasing the number of phase-shift sections comprising the network, the losses of the total network can be decreased; this means that the additional sections will each be required to have a lesser degree of phase shift per section so that the over-all phase shift of the network remains at 180 degrees for the desired frequency of oscillation. Since the loss per section is decreased as the amount of phase shift (per section) is reduced, many oscillators employ networks consisting of four, five, and six section; assuming that the values of R and C are equal for each section, the individual sections are designed to produce phase shifts per section of 45, 36, and 30 degrees, respectively.

Circuit Operation. The previous circuit schematic illustrates a PNP transistor in a commonemitter configuration. Resistors R1, R2, and R3 and capacitors C1, C2, and C3 comprise the feedback and phase-shift network. Resistors R3 and R4 establish base bias for the PNP transistor. Resistor R5 is the emitter swamping resistor, which prevents large increases in emitter current and causes the variation of emitter-base junction resistance to be a small percentage of the total emitter circuit resistance. Capacitor C4 bypasses the emitter swamping resistor, R5, and effectively places the emitter at signal ground potential. Resistor R6 is the collector load resistance across which the output signal is developed. Capacitor C5 is the output coupling capacitor.

Oscillations are started by any random noise in the power source or the transistor when input power is first applied to the circuit. A change in the base current results in an amplified change in collector current which is shifted in phase 180 degrees. The output signal developed across the collector load resistance, R6, is returned to the transistor base as an input signal inverted 180 degrees by the action of the feedback and phase-shift network, making the circuit regenerative.

The output waveform is essentially a sine wave; the output frequency is a fixed frequency. When fixed values of resistance and capacitance are used for the feedback network, the 180-degree phase shift occurs at only one frequency. At all other frequencies, the capacitive reactance either increases or decreases, causing a variation in phase relationship;

thus, the feedback is no longer in phase and is therefore degenerative. Note, however, that if the components comprising the phase-shift network should change value, the frequency of oscillation will change to the frequency at which a phase shift of 180 degrees will occur to sustain oscillations.

Failure Analysis.

No Output. All input voltages should be measured with an electronic voltmeter to determine whether the input voltage is present and whether the biasing voltages applied to the transistor are within correct operating limits. If it has been established that all voltages are correct, it is likely that circuit losses are present in the phase-shift network or that degeneration in the emitter circuit is preventing oscillation.

Reduced or Distorted Output. All voltages should be measured with an electronic voltmeter to determine whether the input voltage is present and whether the biasing voltages applied to the transistor are within correct operating limits. A change in base bias or load impedance or degeneration in the emitter circuit will cause reduced output and possible distortion; however, the output frequency will remain substantially correct.

Incorrect Output Frequency. The correct operating frequency of the R-C oscillator is determined by the circuit constants comprising the phase-shift network; therefore, if the output frequency is incorrect, it is likely that the phase-shift network components have changed value in such a manner as to permit a 180-degree phase shift to occur and sustain oscillations at the incorrect output frequency.

WIEN-BRIDGE OSCILLATOR (ELECTRON TUBE)

Application.

The Wien-bridge oscillator is used as a variable-frequency oscillator for test equipment and laboratory equipment to supply a sinusoidal output of practically constant amplitude and exceptional stability over the audio-frequency and low-radio-frequency ranges.

Characteristics.

It uses a bridge circuit to supply positive feedback voltage at the R-C frequency to produce oscillation.

It operates as a Class A linear amplifier and employs negative feedback to produce an almost perfect sine-wave output.

It also uses negative feedback to provide a practically constant output amplitude.

Frequency stability is excellent (2 to 3 parts per million).


Operates over a wide frequency range (10 Hz to 200 kHz or higher).

Circuit Analysis.


General. When the output of a linear amplifier is applied to its input, a feedback loop is produced. If the feedback is out-of-phase with the input, or negative, the amplifier output will be reduced. If the feedback is inphase, or positive, the amplifier will oscillate. The frequency of oscillation for positive feedback can be controlled by using a frequency-selective network in the feedback loop, such as the Wien bridge. When negative feedback is applied to the cathode circuit of an amplifier, it produces a degenerative effect which reduces the output and improves the amplifier response (this is called inverse feedback). By use of the impedance bridge circuit a differential input can be used to provide oscillation at the desired frequency, with amplitude and waveform control.

Circuit Operation. The basic bridge circuit and feedback loop are shown in the accompanying simplified diagram. In the actual circuit, R4 is a small incandescent lamp with a tungsten filament, and is normally operated at a temperature that produces a dull red or orange glow to give automatic control of amplitude (thermistors are also used). Resistors R1 and R2 are of equal value, as are capacitors C1 and C2, with R3 having twice the resistance of lamp R4 at the operating temperature. The bridge is balanced and the circuit oscillates at a frequency given by:

$$f_0 = \frac{1}{2\pi R1 C1}$$

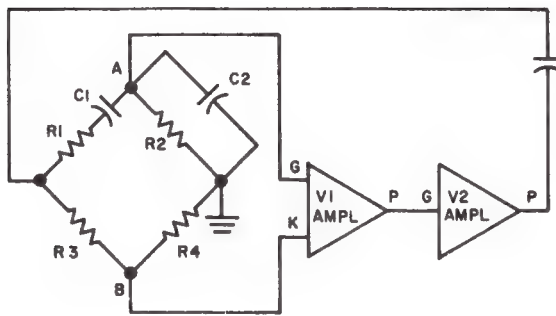

Simplified Wien Bridge Oscillator

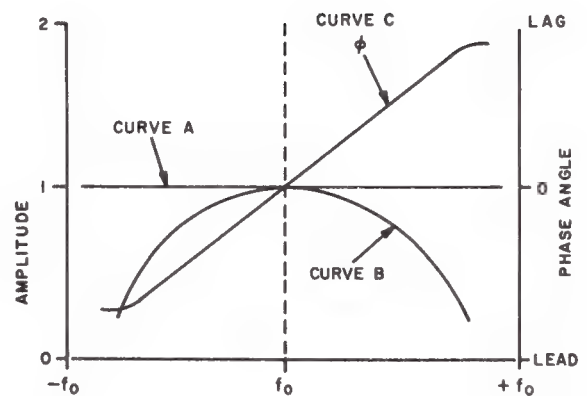

Phasing Diagram

It can be seen by inspection that resistors R3 and R4 form a resistive voltage divider across which the output voltage of V_2 is applied. Since these resistors are not frequency-responsive, the voltage at any instant from point B (and the cathode of V1) of the bridge with respect to ground is dependent upon the ratio of R3 to R4 for any frequency which the amplifier produces at its output. Components R1, C1, and R2, form a reactive voltage divider, between the output of V2 and ground, which is frequency-responsive, with the grid of V1 connected at point A. Thus the voltage across R2 is applied to the input of the amplifier, between grid and ground. When the voltage between point A and ground is in phase with the output voltage of V2, maximum voltage will appear between the grid and ground; therefore, maximum amplification occurs and a large output voltage is produced by V2. Two amplifier stages, V1 and V2, are used to produce a total phase shift of $180^\circ \times 2$, or 360° , to insure that the voltage at the output is in phase with the input. Thus reactive networks R1, C1, and R2, C2, are not required to shift the phase to produce oscillation, but are used to control the frequency at which oscillation takes place.


The manner in which these various feedback voltages vary in amplitude and phase are best shown by the following graphic representation. The center (dotted) vertical line (ordinate) represents the frequency at which the oscillator operates. The left and right vertical lines represent a frequency much lower than the operating frequency, and a frequency much higher than the operating frequency, respectively.

Curve A represents the negative feedback between point B of the simplified schematic and ground. Since it is the same at all frequencies, it is represented by the horizontal line covering the middle of the graph. Curve B represents the positive feedback voltage existing between the grid (point A) of V1 and ground, or the voltage across R2. At frequencies below the operating frequency (f_0), the series reactance of C1 is large, and the voltage across R2 is reduced. As the operating frequency is approached, the reactance diminishes, and the voltage across R2 reaches a maximum at f_0 . As the frequency is increased above f_0 , the parallel reactance of C2 shunts R2, effectively reducing the voltage across R2. Thus, both above and below f_0 the voltage across R2 is reduced, and only at the operating frequency is it a maximum. At this frequency, the positive feedback voltage (at the grid) is exactly equal to (or very slightly greater than) the negative feedback voltage (at the cathode), amplification is at a maximum for V1 and V2. Now consider the phase of the output voltage which is fed back to the input of V1; this is shown by curve C. Because of the phase shift produced by R1, C1, a phase shift occurs above or below the operating frequency; at the operating frequency, however, the phase change is zero, and the output of V2 is exactly 360° from the input voltage, because of the phase inversion through two stages of amplification. Thus, below f_0 the phase angle leads and above f_0 it lags. The out-of-phase voltage above and below f_0 , together with the

decrease in the regenerative feedback voltage applied to the grid as compared with the degenerative feedback voltage applied to the cathode of V1 effectively stops oscillation at all frequencies except the operating frequency, where R_1C_1 equals R_2C_2 .

The schematic of the Wien bridge oscillator is shown in the accompanying illustration. Operation is the same as previously discussed. Amplitude regulation is provided by the use of resistor R4, which is an incandescent lamp (DS1) with a tungsten filament. The current through this lamp consists of the cathode current of V1 plus the ac current at the oscillating frequency through R3 and R4. The design is such that the lamp is operated at a temperature-sensitive point (where the resistance of the lamp changes rapidly with temperature). When the amplitude of oscillation tends to increase, the ac component of the current through the cathode and through the lamp increases. The resistance of R4 (DS1) increases in value because of its higher temperature, and, being in the inverse feedback circuit causes an increase of degenerative feedback. Thus, the amplitude of oscillation is automatically reduced back toward the original level.

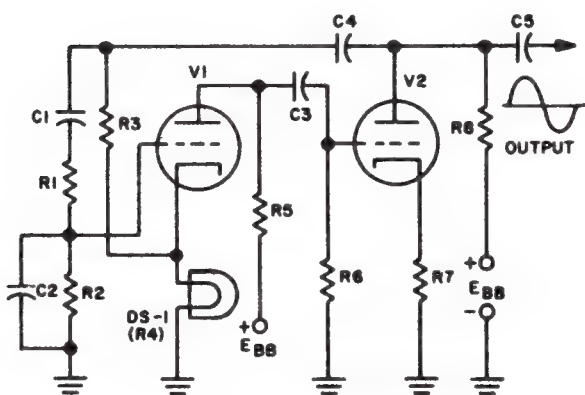In the schematic, resistors R1, R2, R3, and DS1 and capacitors C1 and C2 from the arms of the Wien bridge.



Wien Bridge Oscillator

Tube V1 is R-C-coupled through C3 to the grid of V2. R5 is the plate resistor of V1, which produces a 180-degree phase inversion. Resistor R6 is the grid resistor for V2 across which the output of V1 is applied. The circuit design is such that the phase shift

through the coupling network consisting of R5, C3, and R6 is kept to a minimum. The cathode of V2 is biased by R7, which is left unbypassed to provide degeneration and help keep the output waveform linear. The sinusoidal output waveform is developed across R8 and applied through C4 from the plate of V2 to the input of the Wien bridge as a 360-degree phase-shifted signal, which is now in-phase with the original signal. An output is also taken from the plate of V2 through capacitor C5 for external use. The values R8, C4, and C5 are also chosen to provide an absolute minimum of phase shift, so that the bridge circuit alone determines the feedback frequency. The operation of this circuit is similar to that of the basic circuit described above, with the oscillation frequency being at the frequency where R_1C_1 equals R_2C_2 and with waveform linearity retained by inverse feedback through R3 and R4. Biasing is a combination of cathode and contact bias, with a larger amount of degeneration (inverse feedback) being provided by the unbypassed cathode bias circuits; the output waveform is extremely linear. The output amplitude is small because of the large amount of degeneration employed, and circuit stability is excellent with a minimum of phase shift or frequency variation.

Failure Analysis.

No Output. Since the feedback loop involves two tubes and a bridge network, it is apparent that an open circuit in the coupling capacitors or bias resistors will stop oscillation immediately. An excessive phase shift caused by the change of coupling network values due to aging may also cause stopping of oscillation at the lower frequencies. It is rather improbable that changes due to the aging of tubes would result in the stoppage of oscillation, although failure of one tube due to lack of emission or loss of gain could prevent operation. A defective lamp would produce an open cathode circuit in V1 and stop oscillation. Usually a resistance check will quickly isolate the trouble in this circuit.

Reduced or Unstable Output. The principal components to suspect in the case of reduced output are the electron tubes and the degenerative feedback components. An increase of cathode bias resistance with age or leaky capacitors which place improper bias on the grids not only will reduce the output, but will probably distort the waveform. Poor connections and soldered joints will also cause either condition.

Following the signal path from grid to plate with an oscilloscope will quickly show lack of amplitude and any waveform distortion. Motorboating at low frequencies may occur through common impedance coupling in the power supply, and should be suspected if oscillations are produced at more than one frequency simultaneously.

Incorrect Frequency. Since the frequency is primarily under control of the reactive portion of the bridge network, these components should be suspected when the frequency is incorrect. Where band switching and tuning arrangements are included in the design, faulty switches, poor contacts, and bad connections would be the primary causes of frequency shift.

WIEN-BRIDGE OSCILLATOR (SEMICONDUCTOR)

Application.

Same application as electron tube version.

Characteristics.


Same characteristics as electron tube version.

Circuit Analysis.

General. The Wien-bridge circuit consists of a resistive element and a reactive element arranged in a bridge. The resistive element supplies an inverse (negative) feedback voltage to the emitter, and the reactive network supplies a regenerative (positive) feedback voltage to the base of the same transistor. When the bridge is balanced (at the operating frequency), the positive feedback is slightly greater than the negative feedback and oscillation occurs. The operating frequency is determined by the R-C networks employed in the reactive bridge arm. To obtain the feedback, two transistor amplifiers are used, each producing a 180-degree phase shift, or the total 360-degree phase shift necessary for positive feedback to the base circuit. The negative feedback is obtained by inserting a portion of the feedback into the emitter circuit of the input transistor to produce an out-of-phase or negative feedback. The operation of the bridge circuit and the development of the positive and negative feedback voltages are the same as described for the electron tube counterpart.

Circuit Operation. The semiconductor Wien-bridge oscillator is shown schematically in the following

figure. Except for bias arrangement, it is practically identical to the electron-tube Wien-bridge oscillator.

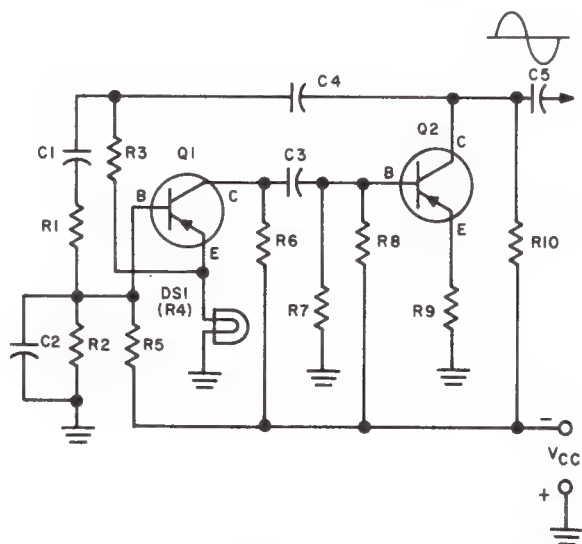

Wien Bridge Oscillator Using PNP Transistor

Voltage divider base bias is used, with R2 and R5 biasing Q1, and R7 and R8 biasing Q2. Temperature stabilization is provided by series emitter (swamping) resistors R4 and R9 (see Section 3, paragraph 3.4, for an explanation of this action).

Resistors R3 and R4 form the resistive arm of the bridge across which the output of Q2 is applied; a portion of this voltage appears across R4 (DS-1) as a negative feedback, being in-phase with the emitter voltage. Resistor R4 (or DS-1 or RT-1) is either an incandescent lamp or a thermistor with a positive temperature coefficient. When a lamp is used, it is operated at a current which produces a temperature-sensitive point (where resistance varies rapidly with temperature); when a thermistor is used, it is selected to have the desired temperature-current characteristic. In either case, the bias developed across this resistor is in opposition to the normal (forward) bias, and produces a degenerative effect. The feedback voltage is of the same polarity as the degenerative bias and increases the degeneration. However, since the output of the voltage divider is not frequency-sensitive, the feedback voltage is always constant

regardless of the frequency of operation. At frequencies other than the frequency of operation the degenerative feedback predominates and prevents oscillation. At the frequency of operation, which is controlled by the bridge reactive arms consisting of R1, C1, and R2, C2, the positive feedback is a maximum. This in-phase feedback signal is applied to the base and is slightly greater than the negative feedback at the balance point or frequency of operation which is given by:

$$f_o = \frac{1}{2\pi R_1 C_1}$$

where R1 is equal to R2, C2 is equal to C1, and R3 is slightly greater than twice R4.

The amplified output of Q1 is developed across collector resistor R6, and it is applied by capacitor C3 and base resistor R7 which form a conventional resistance coupling network (designed for minimum phase shift), to the input (base) of transistor Q2. The signal is further amplified by Q2, and the voltage developed across collector resistor R10 is supplied as an output through capacitor C5, and, as a positive feedback through C4 to the bridge network. Note that the Q2 emitter resistor, R9, is not bypassed and that the circuit of Q2 is therefore degenerative. Note also that R10, C4, and C5 are designed to provide a minimum amount of phase shift. Thus, with a highly degenerative two-stage amplifier and Class A bias, the output signal is essentially a pure sine wave. Since the coupling networks are arranged for minimum phase shift, the phase shift required for regeneration is obtained from the inverting action of the common-emitter configuration, with each amplifier stage providing a 180-degree shift. The feedback input signal is thus shifted 360 degrees in phase to produce a regenerative (positive) feedback independent of circuit parameters. The reactive portion of the bridge (C1, C2 and R1, R2) determines the frequency at which maximum amplification (and feedback) occurs. Resistor R4 (DS-1) controls the degenerative feedback and also the output amplitude; that is, when the input signal to Q1 increases, more emitter current flows through R4 (DS-1), and the lamp or thermistor resistance increases, producing a degenerative voltage which opposes the input signal, and tends to restore it to the original operating value by reducing the amount of amplification through the feedback loop.

This oscillator then, with amplitude stability, temperature stabilization, and degenerative feedback to control the waveform, and with an R-C frequency-selective circuit to determine the frequency of operation provides a signal of excellent stability and pure waveshape for test applications. In order to control the frequency, either resistors R1 and R2 or capacitors C1 and C2 are changed in value or made variable. With a two-gang variable capacitor and a selector switch (or fixed and variable resistors), a continuous range of frequencies over a number of bands may be obtained.

Failure Analysis.

No Output. If the feedback loop or the coupling network between stages is open because of a defective (open) component or if the supply voltage is too low the circuit will not oscillate. Also, if the coupling capacitors are short circuited, the circuit will not oscillate because the bias circuits will apply an abnormal bias to Q1 and Q2. For example, with C4 shorted the emitter of Q1 will be negatively biased and stop oscillation; with C3 shorted the bias will be provided by the parallel combination of R6 and R8 in series with R7 and most likely will be too large to permit operation. If the R4 bridge arm opens, the emitter will be disconnected from the circuit and the transistor will not operate. A resistance analysis and continuity check of the circuit with a high-impedance volt ohmmeter should quickly determine the defective component.

Reduced or Unstable Output. An intermittent open or short in any of the bridge reactive network parts will change the frequency of operation and cause instability. Poor contacts in band switches will also cause instability. When the output is reduced, it is logical to suspect that a defective component in the positive feedback loop is permitting the degenerative action to predominate. Since some positive feedback is required to maintain even a weak oscillation, the reduced output would most likely be caused by increased series resistance in the positive feedback loop, because an open in this loop would stop oscillation. Failure of the transistors with age or reduced output because of lack of emission as in an electron tube would be the least likely cause of reduced output. Normal aging of the transistor will have little effect on oscillation since operation is over only a small

range of amplitude and only small currents are involved. In the event of damage to the transistor, by the application of improper bias or by the application of ohmmeter voltages and polarities that exceed the transistor rating (through poor testing techniques) reduced or no output will occur, but this type of trouble is due to factors external to the circuit and normally should not happen. The supply voltage should be checked for the rated output voltage because a low supply voltage could readily affect the oscillator output.

Incorrect Frequency. Where the frequency of operation differs from the original calibration, the cause might be the aging of circuit parts such as changes in value of R and C in the reactive arm of the bridge or possibly poor switch contacts. Any large change of frequency which cannot be compensated for by retrimming or recalibration is most likely due to defective parts in the frequency arm of the bridge (C1, C2, R1, R2). If the frequency change is linear, the resistive parts should be suspected; if it is non-linear, the capacitive parts should be suspected. The circuits of Q1 and Q2 would not effect any frequency changes.

MAGNETOSTRICTION OSCILLATORS

Application.

The magnetostriction type oscillator is usually used at audio, supersonic, or low radio frequencies to provide an extremely stable sine-wave output. This circuit is employed in preference to the crystal type of oscillator at the very low frequencies because of its simplicity, ease of construction, and economy due to the lack of suitable quartz crystals. It finds particular application in laboratory test equipment and low-frequency standards.

Characteristics.

Uses a nickel-steel alloy rod to control the frequency of oscillation.

Feedback is through magnetostriction effects and not through externally coupled inductors.

Provides frequency stability of less than one Hertz at audio frequencies.

Produces an approximate sine wave of relatively constant amplitude.

Circuit Analysis.

General. The magnetostriction effect is similar to the piezoelectric effect found in crystal oscillators.

Instead of using electric charges, however, it operates by the effect of a changing magnetic field. When an iron-alloy rod is placed within a magnetic field, there is a change in length due to the strain placed on the rod by the magnetic field. This compressional strain, in effect, squeezes the rod and makes it longer; when the field is removed, the rod returns to nearly its former length. Similarly, when a rod located within a magnetic field changes its length, it also includes a change in the magnetic field, increasing or decreasing the field. The induced change is dependent upon the original direction of the magnetic field and the polarization of the metal rod and its composition. When the change in length of the bar is performed at the resonant (mechanical) frequency of the bar, and the induced change is properly phased to enhance the field that produces the strain, mechanical oscillations are set up at the fundamental frequency of the bar. When clamped in a fixed position at the middle, the bar will vibrate with a flexural motion similar to a tuning fork. The metal composition of the bar determines its efficiency and effectiveness as a resonator. A pure iron rod will oscillate very feebly if at all, and a nickel rod will vibrate strongly, but has poor stability. A combination of nickel and iron, such as Invar or Stoic metal, oscillates strongly but has a poor temperature coefficient. With the addition of a small amount of chromium to the nickel alloy, one of the strongest vibrators and most readily available metals (Nichrome) is produced. A copper-nickel alloy (Monel) has too little residual magnetism to operate without an external field, but when a permanent magnet is held nearby it oscillates strongly. Temperature effects will cause changes in the bar length and thus affect the frequency of operation; hence, for extreme stability, the alloy must have a small temperature coefficient or temperature control must be used. Operation in this respect is similar to the operation of crystal oscillators.

The change in length at fundamental longitudinal (mechanical) vibrations is on the order of one part in one million (of an inch) for a field of one gauss, using a nickel rod as an example, but when the rod is resonant, the change in length is multiplied one hundred times or more. Thus, at the resonant frequency the mechanical change in length is sufficient to produce a substantial change of field, and control the operation of the oscillator. At the lower audio frequencies, it is desirable to use an oscillator phased to oscillate very feebly, if at all, without the rod. At


supersonic and low r-f frequencies of from 25 to 300 kHz, the oscillator is not very greatly affected if the basic electronic circuit oscillates strongly without the bar. The stability of the bar prevails in either case. By utilizing nickel tubing with a negative temperature coefficient and filling the tubing with Stoic metal which has a positive temperature coefficient, temperature compensation may be achieved to produce a nearly zero-temperature-coefficient bar.

Although operation is possible at 2 MHz and higher, the oscillation is usually feeble and not nearly so strong as that of the conventional quartz crystal; therefore, operation of this type of oscillator is usually restricted to the lower frequencies.

Circuit Operation. The basic circuit of the magnetostriction oscillator is shown in the accompanying illustration. Grid bias is obtained conventionally through gridleak operation ($C_g R_g$), and series plate feed is used. The coils are wound so as to produce the same flux at the plate end of the bar for an increasing plate current or an increasing grid current (they are in-phase). This condition, which is opposite to that of the normal feedback oscillator, produces degenerative feedback, rather than regenerative feedback. In addition, these plate and grid coils have no coupling or only very loose coupling. Thus, the oscillator will normally not oscillate at all, or oscillate only feebly, as a result of feedback between the interelectrode capacitances. Capacitor C_1 is the tuning capacitor, and is connected so as to tune both the plate and grid coils (either one along may be tuned if desired). For a single frequency or frequencies within a narrow range of operation, C_1 may be fixed and different lengths

of rod may be inserted in the coils (similar to crystal plug-in operation) for the different frequencies.

Assume that plate voltage is applied and that the plate current is producing a steady strain on the rod. If a noise pulse occurs and produces an increase of flux in the plate coil, a compressional wave will be started at the plate end of the bar and will travel to the left toward the grid end. This compressional wave due to magnetostriction will travel through the bar in a manner similar to the propagation of sound waves through a metal bar. When the compressional wave reaches the grid coil, L_g , the lengthening of the bar induces a positive voltage in the grid coil, which is applied to the grid and causes the plate current to increase. The increased plate current induces a stronger field around the plate coil, inducing another compressional wave into the bar. The compressional waves in the bar are reflected from the grid end and travel back to the plate end, where they again are reflected back toward the grid end. When the compressional wave which is reflected from the grid or left end of the bar reaches the right or plate end, a voltage is induced in plate coil L_p by the lengthening of the bar. This voltage, by induction, creates a stronger field around the plate coil. Consequently, the motion of the plate end of the bar is further reinforced, causing it to vibrate more strongly. As a result, another compressional wave is started and the cycle repeats. When the induced and reflected are in phase, the grid-reflected wave arriving at the plate end will always reinforce the induced wave at the plate end, producing at stronger oscillation. Therefore, the length of time it takes for the wave to travel from one end of the bar to the other and return will determine the phasing of the reflected and induced waves. For each length of bar, there will be a specific time taken for a wave to travel to the end and return; if the length is made equivalent to an electrical half-wave-length, each wave will reinforce the other. When the frequency of the tuned circuit (as adjusted by C_1) is approximately the same as the resonant frequency of the bar, maximum reinforcement will occur and maximum mechanical vibration will be produced. With the bar initially unpolarized, operation will occur at the second harmonic. Therefore, the bar is usually permanently magnetized and inserted into the coils so that the field of the plate coil increases the polarization. Operation then takes place at the fundamental frequency ($f = v/2l$ where v is the velocity of sound and l is the length of the bar). Adjusting

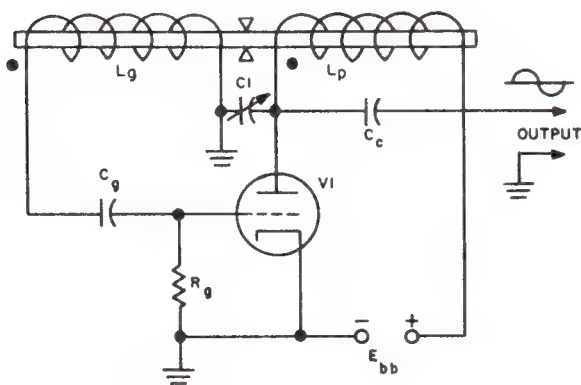

Magnetostriction Oscillator

tuning capacitor C1 for maximum plate current tunes the oscillator to the bar frequency, and feedback is provided mainly through magnetostriction action. Even though there may be some coupling to produce oscillation without the bar, with the bar in place oscillation is strengthened and maintained, being controlled by the mechanical vibration of the bar.

When the bar vibrates at an audio frequency, the sound is audible close to the bar. The operation is similar to the operation of an ac driven tuning fork. The difference is that the tuning fork is actually driven by an ac signal (audio) from an oscillator operating at the frequency of the tuning fork. The tuning fork vibrations induce a magnetic change in a pickup coil around one leg of the fork, thus inducing a stable mechanically controlled signal back into the driving oscillator. The output of the magnetostriction oscillator is usually capacitively coupled from the plate circuit into an amplifier, operating as a buffer on either the fundamental or the desired harmonic frequency.

Failure Analysis.

No Output. If the bar (or tube) is mechanically defective or the tuned circuit is not adjusted to the bar frequency, no output will result. A plate milliammeter connected in the plate circuit will abruptly indicate a two or three times increase of current when tuning capacitor C1 is adjusted to the bar frequency. Otherwise, the circuit is probably open and should be checked with an ohmmeter.

Low Output. A low supply voltage or poor soldered connections which introduce high resistance into the circuit can cause a reduction of developed signal. Excessive bias developed by an RC grid-leak combination which has too large a time constant can cause blocking of the grid and motorboating. Normal resistance and voltage checks will quickly isolate the defective portion of the circuit.

Incorrect Frequency. Since feedback occurs at the bar frequency and is practically independent of the tuned circuit, only a free-running oscillator operating considerably away from the fundamental bar frequency can produce an incorrect frequency. Actually, once the bar starts oscillating the tuned circuit can be varied over quite a noticeable tuning range before oscillations cease. Thus, small changes in the LC circuit will affect only the output amplitude. The usefulness of this circuit as a frequency stabilizer stems from the fact that only the mechanical vibration of

the bar determines the frequency of oscillation. Therefore, at low audio frequencies it will be practically impossible to obtain a different frequency. At r-f frequencies, however, it is possible for spurious oscillations to occur at a frequency not related to the bar frequency because of operation of the electron tube circuit as another form of self-excited oscillator. The frequency of operation should indicate the relative values of components involved, so that the circuit can be examined for lumped capacitance and inductance which could resonate at the undesired oscillating frequency.

NEGATIVE RESISTANCE OSCILLATORS

General.

The negative resistance type of oscillator includes the dynatron, which operates by virtue of secondary emission effects in a screen grid tube, the negative transconductance pentode (or transitron) circuit, and the push-pull (or kallitron) circuit. There is also a possible fourth class, that is, the negative grid resistance type (better known as the tuned grid oscillator with capacitive feedback inherent within the tube); however, this oscillator is not used very much at present. Since it is sometimes included in the negative resistance group, however, it is mentioned here; the interested reader is referred to standard texts for this data.

Negative resistance is a somewhat vague term, which is not very well understood by the layman, or even by many engineers. Actually, it is a term used to describe an imaginary property dealt with in the mathematical analysis of oscillators (and also in amplifiers to a limited extent). It is often erroneously defined as the opposite of positive resistance, which is considered as conventional, or real, resistance. This definition is based on the fact that positive resistance manifests itself by an increasing voltage drop as the current is increased. Negative resistance, on the other hand, manifests itself by a decreasing current as the voltage applied to the device exhibiting the negative resistance is increased, or by a decrease in voltage as the current is increased. While these physical effects are real, the derivation and meaning of the term is purely artificial.

In the mathematical analysis of oscillators, a series of terms have been developed to describe the properties of the circuit; they are then added and equated


to zero. One of these terms is always positive resistance, which is real; it exists in the dc and ac resistance of the coils and leads, and is always assigned a positive value. Therefore, to be equated to zero, the series must contain certain other terms that are of equal, but negative, value. It is this negative resistance which, when it equals the positive resistance mathematically, permits oscillation. With any type of oscillator, both the positive and negative resistance concepts apply. In the oscillators considered previously, the negative resistance is created by an external circuit, such as an inductive or capacitive feedback arrangement. In the true negative resistance type of oscillator, however, the negative resistance is an inherent property within the tube or device which exhibits it. There is no circuitry involved other than the requirements to supply a tank circuit or inductor in parallel (or sometimes in series) with the negative resistance. The basic simplicity of this type of circuit makes it useful if its inherent defects do not nullify the advantage of its simplicity.

A more effective way to understand *negative resistance* is to visualize it as a generator of energy. In contrast to positive resistance, which *dissipates* energy at a rate proportional to the square of the impressed voltage or current, negative resistance *generates* energy at a rate proportional to the square of the impressed voltage or current.


Negative resistance may be either voltage-controlled or current-controlled; the accompanying figure illustrates the volt-ampere characteristics of these two types of control. As can be seen, each type is the exact inverse of the other. In the voltage-controlled device, as the voltage is increased the current rises to a peak, and then drops to a low value from A to B (this is the negative resistance region) and then increases to a new peak value thus the volt-

age is a single-valued function of the current. In the current-controlled type, the voltage varies similarly as the current is increased, and the current is a single-valued function of the voltage. Note the characteristic "lazy S" pattern of these curves, which makes them easily identifiable. The oscillators described in the following discussions are all of the voltage-controlled type.

When either a parallel resonant or a series resonant tank circuit is connected across a negative resistance device, it can be mathematically demonstrated that oscillation will occur if certain conditions are satisfied. The basic equivalent circuit of a negative resistance oscillator is shown in the accompanying illustration. L, C and r in the figure represent the tank inductor, capacitor, and tank resistance respectively, and p represents the negative resistance.

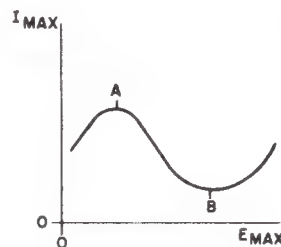


Voltage-Controlled

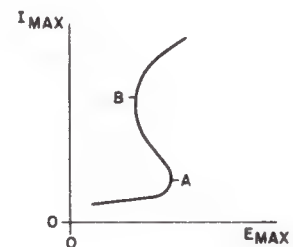

Current-Controlled

Voltage-Controlled

Current-Controlled

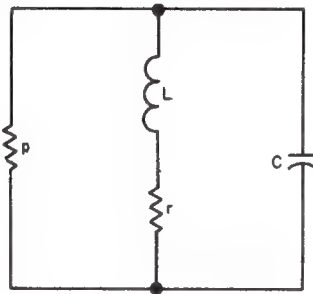

**Basic Negative Resistance Oscillator
Equivalent Circuit**

It can be shown mathematically that when p is smaller than the ratio L/rC the amplitude of oscillations will build up. On the other hand, when p is greater than the ratio of L/rC , the oscillations will diminish in amplitude and eventually cease. The criterion for constant oscillation with no change in amplitude is that p be just equal to L/rC . Thus for oscillation to occur, p must be less than, or equal to, L/rC .

If a generator is substituted for p in the basic figure, it can be understood how the basic concept of negative resistance applies. The region where the device exhibits a negative resistance normally covers a limited range, and is never associated with positive resistance. That is to say, when the device is operated as a conventional feedback oscillator, the operating region is beyond that portion associated with the negative resistance properties. Thus, devices which exhibit negative resistance can also be employed in circuits involving the positive resistance region of operation without any conflict with their negative resistance characteristics. For example, the same type of tube which is particularly useful in the dynatron oscillator (because of its inherent secondary emission at plate voltages lower than the screen voltage) may also be used in conventional LC feedback oscillator circuits operating at higher plate and screen voltages in the so-called positive region. For good waveform, it is important that large capacitance values be used in the tank circuit of the negative resistance oscillator, as small capacitance will cause distorted output waveform.

DYNATRON OSCILLATOR

Application.

The dynatron oscillator is used to produce a stable sinsonidal output over the low, medium, and high-frequency r-f ranges (and sometimes the audio-frequency ranges). It is used mostly as a signal generator for laboratory or test equipment purposes or as a bent-frequency oscillator in receivers.

Characteristics.

Uses the negative resistance of a screen-grid tube to produce oscillation.

Provides very good stability, but at a low output amplitude.

Uses a two-terminal tuned circuit to determine the frequency of operation.

Circuit Analysis.

General. The dynatron circuit was originally based upon the use of the type 24 screen-grid tube, which exhibited considerable negative resistance at low plate voltages. The negative resistance was due to secondary emission from the tube plate. Present day tube manufacturing and design methods have minimized the undesired secondary emission, but it still exists at very low plate voltages in most tetrodes. Secondary emission occurs when the plate is much lower than the screen voltage, because of bombardment of the plate by electrons which have passed the screen grid. With high or normal plate voltage these electrons are attracted back to the plate and have no effect. With low plate voltage, however, the field of the grid extends into the plate region and attracts the secondary emitted electrons knocked out of the plate. Thus, the plate current is reduced by the amount of secondary electrons captured by the screen grid, and the screen current is increased. The accompanying figure illustrates typical plate and screen currents for a type 24 tube. These curves have the distorted "lazy S" shape characteristics of negative resistance as explained previously in the general discussion. When the tube is operated in the region of negative slope with a tank circuit connected to either the screen or the plate, oscillation will occur. Maximum screen current flows when the plate current is minimum (point B on the curve). Useful oscillation is

possible between points A and B, with the oscillator adjusted to work at the midpoint of this negative resistance region. From points B to C and beyond is the positive resistance region, which cannot be used for dynatron operation. It can be clearly seen that the plate of the dynatron must be operated at extremely low voltages; therefore, the amplitude of oscillation is limited and the circuit is capable of only a small output. The output amplitude is controlled by adjusting the grid voltage, which varies the slope of the negative resistance region.


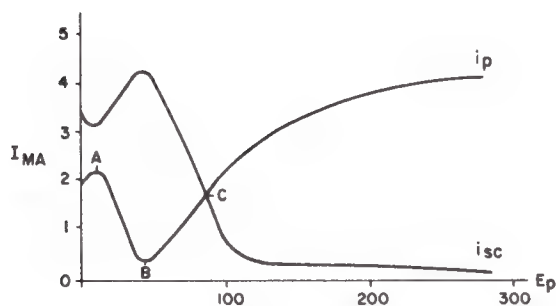


Plate and Screen Current Relationships

One of the advantages of this type of oscillator is that it requires only a single coil with tuning capacitor, instead of a tapped coil or an additional tickler winding. Thus its extreme simplicity made it popular. On the other hand, since secondary emission varies with the age and emission of the tube, and since tubes of the same type and manufacture have widely different secondary emissions, it is necessary to have a plate voltage control to permit adjustment for stability with tube aging and the use of different tubes. Because of the low output and the variation of secondary emission from tube, this circuit is not very widely used today.

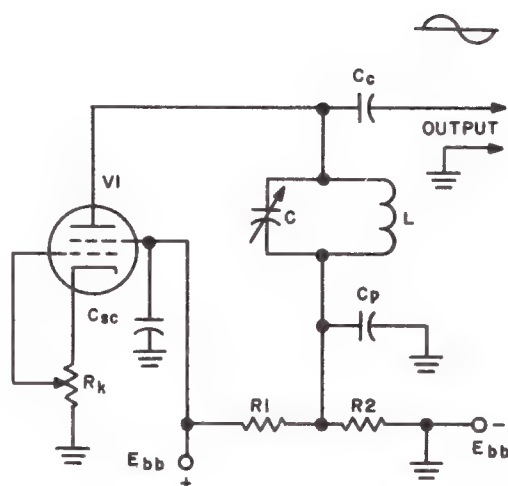

Dynatron Oscillator

The grid is biased by means of potentiometer R_k when cathode current flows. Adjustment of the grid arm of the potentiometer effectively places the grid at a more negative potential with respect to the cathode in one direction of rotation, and at a less negative potential in the other direction of rotation. The screen is connected to the high side of the plate supply and bypassed by C_{sc}, and the plate is connected to a voltage divider consisting of R1 and R2. Thus, the plate voltage is reduced below the screen voltage. Capacitor C_p is the conventional series-feed bypass. The tuned tank, consisting of L and C, is placed in the plate circuit, although it could also be placed in the screen circuit. The output is taken capacitively from the plate by C_c.

The inherent stability in this type of oscillator is based upon the action of the tank circuit primarily, as in other types of the LC oscillator. Although operation at a low plate voltage limits the output to a low value, it also contributes some stability, because

load changes are a smaller percentage variation than in other self-excited power type oscillators. Since the feedback is inherent in the tube, rather than being provided by an external circuit, changes in tube element capacitances are not as effective in causing frequency changes, thus contributing to the stability of this type of oscillator. Therefore, a dynatron which is properly adjusted for the correct operating point and plate voltage is practically equivalent to the electron-coupled LC oscillator, as far as frequency stability is concerned.

Operation at a low amplitude insures better linearity and less harmonic content in the output, accounting for the relatively pure output waveform of this type of oscillator. Variation of the grid voltage changes the slope of the negative resistance characteristic and thus governs the operating amplitude.

Detailed Analysis. Mathematically it can be demonstrated that when an LC tank circuit is connected to a negative resistance element oscillations will start and continue, with the negative resistance supplying the losses caused by the positive resistance of the tank. In the conventional external feedback oscillator, this same action is obtained by the feeding back of output voltage in-phase with the input voltage. In the dynatron it is inherent within the electron tube. Thus, in the conventional feedback oscillator, as the plate voltage is increased, the plate current is also increased and the amplitude of oscillation is primarily limited by the power supply voltage. In the dynatron, with the plate operating at a lower voltage than the screen, as the plate voltage increases the plate current decreases. As the plate current decreases, since the supply voltage remains substantially the same (considering a regulated supply), there is more voltage available for the load. Thus, as the tube current becomes smaller, the voltage across the load builds up. In effect, the tube is releasing energy from the power supply instead of absorbing it. Therefore, the tube can be considered as a generator which supplies power to the tank circuit. The generated energy is used to overcome the losses in the tank circuit, and the oscillation builds up until an amplitude is reached where a state of equilibrium is obtained, and continuous oscillations are produced without any external feedback circuitry. All that is required is to shock excite the tank circuit into oscillation, and once started the action continues. Starting is produced by turning the circuit on. The initial rush of current to the plate produces a transient oscillation in

the tank circuit, at the approximate frequency to which it is tuned. In the absence of negative resistance, this oscillation would quickly die out, being damped by the positive resistance of the tank. The inherent negative resistance of the tube, however, provides an effective in-phase feedback. Consider the tank circuit and its operation. In an oscillator condition, the coil and capacitor are interchanging energy. First the capacitor tends to charge as the transient increases, and the charging current flows through the inductor in a direction which increases its magnetic field. As the transient reaches its peak and drops, the magnetic field about the coil collapses and induces a reverse voltage in the coil, which is in the direction of capacitor discharge. Consider now the instantaneous ac component of plate voltage. As the transient increases in amplitude, the total effective plate voltage is increased and the instantaneous plate current is reduced. With a lowered current the plate voltage tends to rise, and this constitutes a higher effective plate voltage. Thus, the action within the tube is such as to aid the transient, and the tube is quickly driven to its saturation region (point B on the plate and screen curves shown previously). At saturation the plate current does not change, so the inductor field collapses and the reverse cycle occurs. Since the voltage is decreasing, the plate current increases; this in turn, reduces the available plate voltage, and the tube absorbs the power. The transient is now falling and effectively subtracts from the total applied plate voltage. Thus the plate voltage is driven in a negative direction (a peculiarity of the dynatron region), whereupon the plate current change reverses itself. At this time the capacitor, which is discharged, proceeds to charge again and the cycle is repeated. The limits of operation are set by the applied grid bias, which determines the operating point, and the static plate voltage.

Unfortunately, the effects of secondary emission are not completely controllable, and the setting for optimum amplitude and efficiency for each tube of the same type varies. The negative resistance oscillator circuits which follow are considered to be better from the standpoint of stability and criticalness of adjustment than the dynatron circuit. When the tank tuning capacitance is reduced to that of the tube elements and leads, the output waveform is considerably distorted, and operation approaches that of the relaxation oscillator with the frequency of operation being set by the time constant of the resistance

and capacitance in the circuit. With the tuned tank, however, the angular frequency of oscillation is approximately

$$\omega = \sqrt{\frac{r+p}{p} \frac{1}{LC}}$$

Since r , which represents the ac resistance of the coil and leads, is usually only a few ohms, whereas the negative resistance p is seldom less than two or three thousand ohms, the frequency of oscillation is practically equal to

$$f_o = \frac{1}{2\pi \sqrt{LC}}$$

As a result, small changes in p which result from changes in the supply voltage have negligible effect on the frequency of oscillation at the threshold value, where p is equal to or less than L/rC .

Failure Analysis.

No Output. A no output indication will be caused by lack of supply voltage, or by a plate voltage which exceeds the screen voltage and places operation in the positive resistance region, producing a non-oscillatory condition. An increase in coil resistance due to poor contacts or soldered joints can place operation in the non-starting region; such resistance will be so high that it will be revealed by a resistance analysis. With normal voltages applied and no oscillation, either the tank circuit is short circuited, or the secondary emission has changed and requires an adjustment of plate, screen, and grid voltages or a change of tubes. A change of load can change the negative resistance values and place the circuit in the nonoperative region. In this case, removing the load will restore normal operation and indicate the source of trouble.

Reduced Output. A primary cause of reduced output, which is common in this circuit, is for a change to occur in secondary emission, requiring a readjustment of operating voltages or the selection of another tube. A change in grid voltage to an operating region of small slope will also cause an amplitude change and reduced output. Such a condition will be evident by a grid voltage check. The reduction of applied plate voltage through a defective voltage divider can also cause the same condition. Thus, voltage and resistance checks should quickly reveal any defective components.

Incorrect Frequency. Changes in load or changes in applied screen and plate voltages will change the frequency slightly, but the effect is usually negligible. Since the tank circuit is the primary frequency-determining portion of the circuit, any large frequency change will be due to a change in tank circuit parameters. Usually the tuning range is sufficient to adjust the circuit to the desired frequency. Once properly set, any noticeable frequency change indicates either ambient temperature effects or poor contact resistances (soldered joints) in the tank circuit.

TRANSITRON (NEGATIVE GM) OSCILLATOR

Application.

The transitron, or negative transconductance (g_m), oscillator is used to supply a stable sinusoidal waveform at audio and low or medium radio frequencies. It is used mainly in test equipment, receivers, and laboratory instruments that require a simple band-switching oscillator.

Characteristics.

Uses the negative transconductance effects of a pentode to provide negative resistance type of oscillation.


Uses an external capacitor coupled between the suppressor and screen to obtain negative transconductance.

Utilizes a two-terminal tank circuit to determine the frequency of operation.

Circuit Analysis.

General. When a negative voltage is applied to the suppressor grid of a pentode, it will cause electrons that have passed through the screen grid to return to the screen grid. If the negative suppressor voltage is decreased (made more positive), more electrons will be attracted to the plate, and the screen-grid current will be reduced. Thus, the screen-to-suppressor transconductance is negative. With proper voltages and circuit arrangements, the screen current will decrease with a small positive voltage increases on the suppressor, even when the screen voltage is also increased an equal amount. The accompanying figure shows a typical screen current versus screen voltage characteristic curve of a pentode which has its suppressor coupled to the screen through a capacitor. The

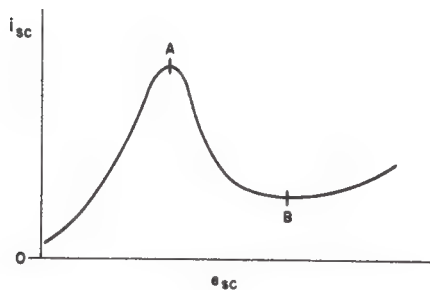
typical distorted "lazy S" pattern indicates that there is a negative slope. There, oscillation will occur if an LC tank circuit is connected in the screen circuit.



Negative Transconductance Characteristic

If the control grid is biased negatively, the bias may be adjusted to control the amount of negative resistance developed. With the negative transconductance arrangement, the control and development of the negative resistance effect is by electrode voltages and circuit parameters. Thus, the transitron oscillator does not depend upon secondary emission for its operation; therefore, it does not have the undesirable features of the dynatron oscillator, although the circuit is somewhat more complicated.

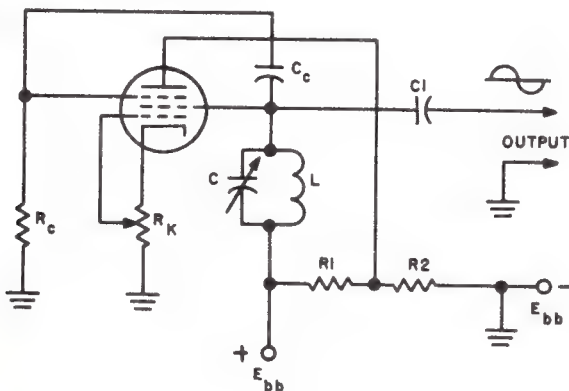Circuit Operation. The schematic of the basic transitron oscillator is shown in the accompanying figure. In this circuit, the LC tank is inserted in the screen grid circuit, and the screen is capacitively



Basic Transitron Oscillator

coupled to the suppressor through capacitor C_c . The output is taken capacitively from the screen circuit through C_1 .

Cathode bias is employed, and the grid is returned to potentiometer R_K . Variation of the negative grid bias permits the slope of the negative transconductance region to be controlled. Thus, both output and linearity control are effected. Note that the plate is placed at a reduced potential with respect to the screen grid by means of the voltage divider consisting of R_1 and R_2 . The basic arrangement is the same as in the dynatron oscillator, except that the pentode has an additional element, the suppressor. Since the suppressor is located between the screen and plate, it will control the current between these elements when properly biased. To produce the negative transconductance, the screen is capacitively coupled through C_c to the suppressor, and the suppressor is returned to ground through R_c . As a result of these connections, instantaneous ac variations of the screen voltages are effectively applied to the suppressor, and dc variations are effected through the RC network in accordance with the time constant. For proper operation, it is imperative that the reactance of C_c at the operating frequency be very small as compared with the resistance of R_c . This is necessary to ensure that practically all of the feedback voltage appears across R_c and that very little voltage divider action occurs, as when C_c has a large value of reactance. The effect of the voltage divider action is to reduce the feedback and produce a higher negative resistance, which is not desired.

In a pentode, the movement of electrons from the cathode to the screen and plate constitutes the screen (i_{sc}) and plate currents (i_p), respectively. Variations in suppressor voltage (e_{su}) have negligible effect on the total number of electrons leaving the cathode because of the shielding effect of the screen and control grids. The suppressor grid voltage, however, does control the division of the space current between the screen and plate. Making the suppressor voltage less negative results in a greater number of electrons passing through to the plate; consequently, the plate current, i_p , increases while the screen current, i_{sc} , decreases. On the other hand, making the suppressor voltage more negative results in fewer electrons being passed through to the plate, and a decrease of i_p , with an increase in i_{sc} . Typical variations of the screen and plate currents with changes in the suppressor voltage are shown in the accompanying graph. A decrease of

i_{sc} with an increase of e_{su} indicates the existence of a negative transconductance between the screen suppressor grids. Since the reactance of C_c is negligible at the frequency of oscillation, the alternating components of the screen voltage and the suppressor voltage are of the same polarity. Therefore, an increase in screen voltage instantaneously increases the suppressor voltage and, because of the negative transconductance, decreases the screen current. Thus, the negative transconductance of the tube produces, in effect, a negative resistance between the screen grid and cathode.

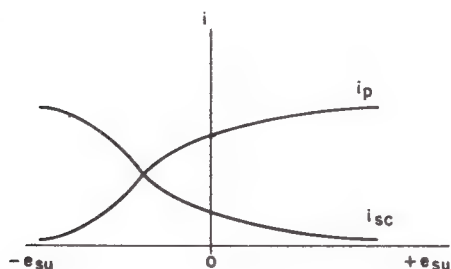


Plate and Screen Currents vs. Suppressor Voltage


When the transitron oscillator is adjusted so that the negative resistance is smaller than the value needed to produce continuous oscillations, any brief oscillation or transient caused by closing of the plate switch is amplified. As a result, the operating range on the screen current versus suppressor voltage characteristic curve is increased, and, because of the curvature of the characteristic, the average slope of the part used is decreased. Since this is the same as increasing the value of the negative resistance, the amplitude of oscillation increases until the value of the negative resistance is such that it maintains a constant amplitude of oscillation.

Detailed Analysis. For oscillations to be sustained, the losses in the tuned circuit must be replaced by energy supplied from the electron tube. The losses produced by the circuit resistances are best illustrated in the accompanying transitron equivalent circuit.

The negative resistance presented by the tube to the tuned circuit is represented by R_N , and the tank circuit losses by R_t in parallel with the LC tank. The shunt resistance of suppressor return resistor R_{su} and load resistor R_L are effectively in parallel with the

negative resistance and the tank loss resistance. The sum of R_L , R_{su} , and R_t is the effective positive resistance. The current in R_N must be equal and opposite to the total current through this positive resistance. If R_N is larger than the positive resistance, the current through R_N is too small and the oscillations die out. If R_N is smaller, the current is too large and the oscillations increase in amplitude. When the current through R_N is just sufficient to sustain oscillations, the circuit is the equivalent of a simple LC combination, and the frequency of operation is:

$$f = \frac{1}{2\pi\sqrt{LC}}$$

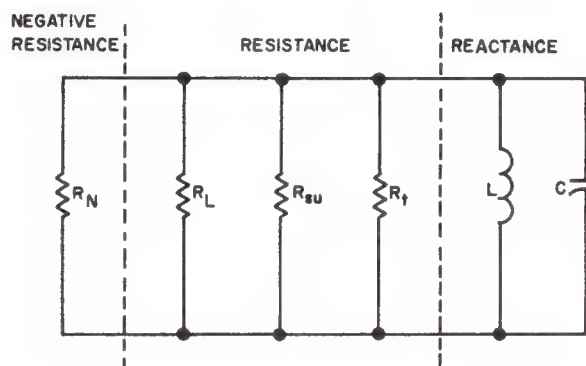

Transitron Equivalent Circuit

Failure Analysis.

No Output. The loss of plate voltage due to defective divider resistors, the lack of screen voltage due to an open tank coil or a defective supply source, or a defective tube will cause loss of output. A change in the value of the feedback capacitor can reduce the feedback below the amount required for oscillation, depending upon the frequency of operation. High resistance coil contacts (poor solder joints) will also cause circuit losses high enough to stop operation. Since there are relatively few components, trouble should easily be isolated by a voltage check to determine proper operating conditions, and by a resistance analysis if the voltage are apparently correct. It should not be necessary to select tubes to produce oscillation, because, unlike the dynatron, the circuit is operable regardless of secondary emission.

Restoring oscillation by the selection of tubes indicates insufficient feedback between the screen and suppressor due to incorrect or changed values of R_c or C_c .

Reduced Output. Excessive reactance in the suppressor-screen feedback circuit can change the negative resistance value and reduce the amplitude of oscillation. However, reduction of output is more likely to be caused by excessive bias on the control grid, which will restrict operation to a very limited range of negative slope. Also, excessively low screen and plate voltages will cause a reduction in over-all amplitude, even though the tank circuit at resonance will provide an increase of output. In oscillators covering a wide frequency range where the feedback capacitor value is changed by a switching arrangement to produce optimum feedback, difficulties with switch contacts may cause loss of amplitude on some of the ranges.

Incorrect Frequency or Instability. Since the tank circuit is the primary frequency-determining element, normal variations of frequency due to aging of components should be easily compensated for by adjustment of the tuning capacitor. After the capacitor is adjusted, if the frequency varies it is probably due to the effect of ambient temperature changes or r-f heating on the tank inductance and distributed capacitance.

KALLITRON (PUSH-PULL) OSCILLATOR (ELECTRON TUBE)

Application.

The push-pull negative resistance type of oscillator, known as the *Kallitron*, is used to produce pure audio-frequency waveforms, with low harmonic content. Its use is mostly confined to laboratory type audio generators and test equipment.

Characteristics.

- Uses two tubes in a push-pull feedback arrangement.


- Uses a tuned LC tank to determine frequency of operation.

- Produces a sinusoidal output waveform, with low harmonic content.

Circuit Analysis.

General. In a balanced push-pull circuit with no input voltage applied, the quiescent plate currents

and voltages are equal. When an input is applied, first one tube conducts, and then the other conducts. Assuming a sine wave input, as tube 1 goes through a positive grid excursion, it develops an inverted polarity output across its plate load resistor. If this inverted output is applied to the grid of tube 2, a positive output will be developed in the plate load of tube 2. If the plate output of tube 2 is fed back to the grid of tube 1, the positive input excursion will be enhanced, and the tubes will be driven in opposite directions equally. As the input waveform changes polarity the opposite action occurs, with grid 2 now being driven positive and grid 1 negative. If a tank circuit is connected between the plates of these tubes, oscillation will occur because of current flow in the external circuit, and the frequency will be determined mainly by the tank circuit resonant frequency. The accompanying figure shows an elementary oscillator circuit of this type, with the tank connected between points A and B (bias voltage is not shown for simplicity).

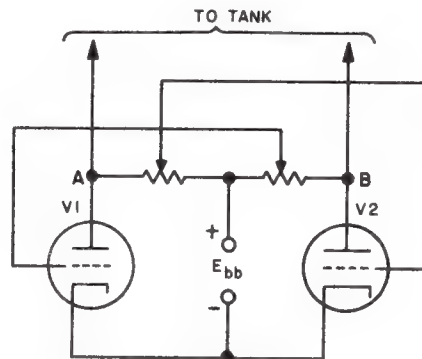


Elementary Push-Pull Oscillator

As can be seen, the circuit is basically a simple multivibrator. However, in a multivibrator the current (and voltage) changes abruptly from one value to another and is determined mainly by the values of R and C in the circuit. In the Kallitron oscillator, however, the oscillation is controlled by the tuned tank circuit, and there are no abrupt changes, the transition from one state to another or conduction being smoothly sinusoidal. Because the plate voltage of each tube increases when the plate current decreases, there is in effect a negative resistance between the

two plates. The second harmonic output is effectively reduced by the push-pull action, and the third harmonic content is reduced by the tuned circuit. Therefore, the output waveform is relatively pure, having a minimal amount of harmonic distortion.

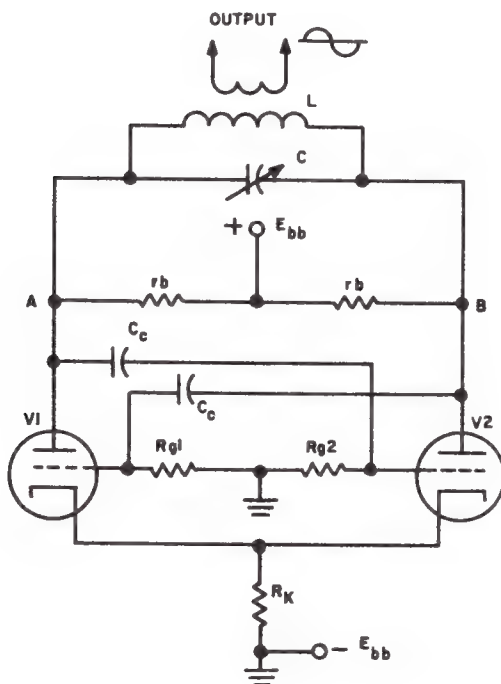Circuit Operation. The schematic of a typical Kallitron oscillator is shown in the accompanying illustration. Usually a dual triode in one envelope with its accompanying circuitry is used to provide, in effect, a single tube oscillator. To keep the push-pull relationships in balance, the output is generally taken inductively, but it may be taken capacitively.




Kallitron (Push-Pull) Oscillator

Cathode bias is provided by R_K . Since the tubes operate in push-pull through a common cathode bias resistor, it can be seen that as the plate current of tube 1 increases the bias also increases, and, being applied to the V2 cathode, it reduces the plate current of tube 2. On the other half cycle, the operation is reversed, with the V1 current decreasing and the V2 current increasing. The net result is a negligible change in cathode current. Feedback is obtained by cross-connecting the grids and plates through C_c .

Thus as the grid of V1 rises, the plate current increases, causing the voltage on V2 grid to fall, which increases the plate voltage of V2 and feeds back a rising grid voltage to V1 grid. Likewise, on the opposite cycle the conditions reverse. The output amplitude is controlled by proportioning the grid resistors, R_g , and the grid coupling capacitors, C_c . The amplitude is also affected to some extent by the applied plate voltage and the values of the plate load resistors. However, the most effective method is to adjust the bias by means of R_K to obtain the desired amplitude. Actually, C_c and R_g operate essentially as grid leaks. When the reactance of the grid coupling capacitor is small in comparison with the grid leak resistance at the lowest operating frequency, the feedback is at a maximum, and the tank circuit can be connected in either the grid or plate circuits.

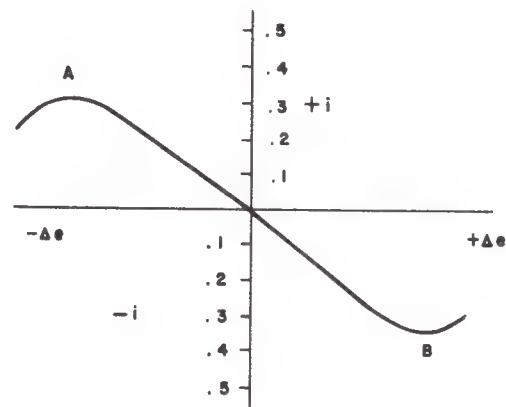A typical curve showing plate voltage change versus external current flow between points A and B exhibits a continuous negative slope over most of its range, indicating typical negative resistance characteristics, as illustrated in the accompanying figure.



Typical Current-Voltage Characteristics

With the feedback action now understood, it can be clearly seen that when the LC tank is connected between points A and B it is alternately charged and discharged at its natural resonant frequency. Since the voltage on one plate is increasing when the voltage on the other tube plate is decreasing, points A and B are always of opposite potential. With a low-resistance tank circuit in place, the negative resistance action, produced by the tube operating at reduced

conduction, effectively supplies energy to the tank circuit to overcome its positive resistance losses, so that continuous oscillation is maintained.

Failure Analysis.

No Output. Lack of plate voltage due to an increase in external load resistance or short-circuiting of the supply will cause lack of output. Since the negative resistance primarily depends on the amplifying action of the tube, insufficient amplification may also result in no output. Any change in the feedback circuit which reduces the feedback below the critical point can also stop oscillation. Since these conditions are generally produced only by an open- or short-circuited component, resistance and voltage checks should quickly isolate the defective component. Tank circuit losses resulting from shorted turns or from increased resistance due to poor contacts (poor solder joints) can also be a contributing cause. Shorted turns will show up as a change in frequency if the circuit oscillates at all, and excessive resistance will cause reduced amplitude if it does not entirely stop oscillation.

Reduced Output. Excessive bias resistance will cause a reduction of amplitude. A reduction of applied plate voltage will also reduce the amplitude, but it can easily be detected by a voltage check. Changes in the feedback capacitors or the grid-leak resistors will also reduce the amplitude. Checking the capacitor with an in-circuit capacitor analyzer will quickly determine whether the capacitance is correct, and a resistance analysis will determine whether a grid-leak resistor has changed value. A decrease in the amplification factor of the tube with aging can also reduce the output.

Incorrect Frequency or Instability. Since the tank circuit is the primary frequency-determining element, major frequency change would indicate the possibility of shorted turns or a reduction of capacitance. The nature of the trouble is indicated by the direction of the frequency change. That is, an increase in frequency indicates shorted turns or a reduction of capacitance, and a decrease in frequency indicates an increase of capacitance, since the number of turns cannot increase.

Usually minor frequency changes, which may be produced by slight changes in plate voltage with changes in load or line voltage, can be compensated for by retuning the tank circuit. Since the stability of this circuit is normally better than that of either the


dynatron or transitron, small frequency changes will require the use of a reliable secondary frequency standard to determine them. At the frequencies used, changes in tube element capacitance with temperature is rather unlikely to affect the frequency. Unstable operation might possibly be caused by a reduction of the tank capacitance to a minimal value, due to such trouble as defective bearing contacts in the tuning capacitor. This could produce a distorted waveshape and possibly result in the relaxation type of oscillation. Such operation would be evidenced by abrupt changes in current and voltage from one value to another, and the frequency would, no doubt, be out of the frequency range for which the circuit was designed.

PART 6-2. CRYSTAL OSCILLATORS

CRYSTAL OSCILLATORS

General.


The crystal type of oscillator uses natural or synthetic nonconducting crystals excited by the piezoelectric effect and vibrating at or near their natural frequency to control the frequency of oscillation. The electrical excitation of the mechanical device at or near its fundamental, harmonic, or sub-harmonic frequency produces stable mechanical oscillations; these are converted into electrical impulses of the same frequency are fed back into the oscillation circuit to sustain highly stable oscillations at the desired frequency of operation. The most popular, economical, and plentiful kind is the quartz crystal (shown in the following illustration), which in its natural (alpha) state only requires cutting, grinding, and polishing to size. The frequency of oscillation is determined mainly by the thickness (or length for very low frequencies) of the crystal slab. The crystal cannot be made to vibrate too strongly or it will shatter. Tourmaline crystals were once popular for the higher frequencies since they are more rugged and thicker for a given frequency. Because of the expense and scarcity of large-sized crystal prisms, and since tourmaline has a negative temperature coefficient which prevents a zero-temperature-coefficient cut from being obtained, tourmaline crystals are not in common use today, although they may occasionally be encountered.

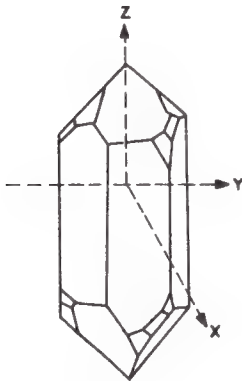

Natural Quartz Crystal, Showing the X, Y, and Z Axes

A quartz prism has three basic axes, X, Y, and Z. The Z axis is the optical axis, the Y axis is considered the mechanical axis, and the X axis is considered the electrical axis (see quartz crystal previously illustrated). No piezoelectric effects are directly associated with the Z axis; an electric field applied in this direction produces no piezoelectric effect on the crystal, nor will a mechanical stress along the Z axis produce a difference of potential. A simple compressional or tensional mechanical stress applied along the Y axes will cause a change of polarization of the X axis, but not the Y axis; however, if a shearing or flexural strain is applied along the Y axis a change of polarization will occur. When the crystal is stretched along the X axis, a positive charge will appear on one end of the crystal, and when the crystal is compressed along the X axis, a negative charge will appear. Thus, piezoelectric effects are produced for either X- or Y-cut crystals, as shown in the accompanying illustration.

The piezoelectric effect is defined as that effect which produces a potential across the parallel faces of a crystal-line dielectric substance when pressure or torsional forces are applied between the faces, or, conversely, that effect which causes the crystal to distort itself when a voltage is applied between the faces. Thus, when alternating voltages are applied between the crystal faces, it will oscillate (vibrate mechanically) at a specific frequency, which is determined mainly by the thickness of the crystal.

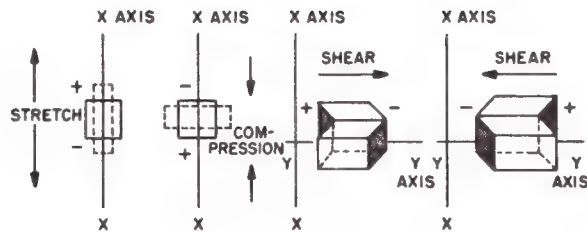


Piezoelectric Action

When loosely coupled to a suitable oscillator circuit and excited at the proper frequency, the crystal will stabilize the frequency of oscillation. If the circuit is arranged to provide self-oscillation at the natural frequency of vibration of the crystal and will not oscillate without the crystal, it is a crystal-controlled oscillator. Normally, a crystal has two frequencies or modes of operation: the *resonant* (fundamental) frequency, or *series* mode, and the *anti-resonant* frequency, or *parallel* mode. The series and parallel modes are similar to the equivalent types of resonance. In the series mode, the crystal presents a low impedance and provides a maximum of stability. In the parallel mode, it presents a high impedance (usually considered infinite), since the crystal is used as a high-Q inductor which is resonated with the crystal circuit shunt capacitance (including crystal and holder capacitances), to form a highly stable *parallel-resonant circuit* operating at the antiresonant frequency of the crystal. The antiresonant crystal frequency is always slightly higher than the natural, or series-resonant, frequency.

The variation with frequency of the series reactance (X_s) of a typical quartz crystal is shown qualitatively in the accompanying figure. The solid line represents the condition where the resistance R is equal to zero (which is only theoretically possible); the dotted line represents the true conditions where R has some finite value. Thus, where R is equal to zero, the series reactance is equal to zero at

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

and changes from + infinity to - infinity at the frequency f_{po} (the solid line on the graph). When R is greater than zero, the dotted line indicates that the series crystal reactance has a finite maximum and minimum, and that it actually has a zero value at both f_s and f_p , the series- and parallel-resonance frequencies. For a reasonably small R , the frequency difference between f_s and f_p is approximately the same as that between f_o and f_{po} (they are quite close). In practice, the frequency difference between series and parallel resonance varies with the type of crystal and its cut. For example, a GT-cut quartz crystal can have a difference as low as 0.08 percent of the resonant frequency, and an AT-cut crystal can be as great as 2 percent.

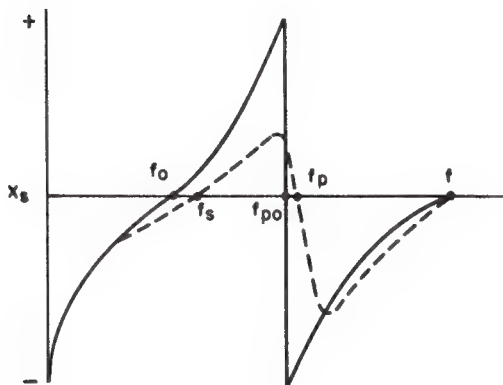


Variation of Series Reactance
of Crystal With Frequency

The series mode of operation is usually used for wave-filter circuits where a specific frequency is to be absorbed, or for *overtone* oscillators operating at high frequencies. A brief discussion of the basic principles of an overtone crystal is given in the next paragraph. The parallel mode is usually used in oscillator circuits where it is extremely high Q produces stable operation not normally possible with the ordinary inductor or LC tank circuit. As issued, the antiresonant (parallel-resonant) frequency is marked on the holder unless otherwise specified on the nameplate (overtone crystals are stamped at the overtone frequency). Crystal calibration and rating are for a specified shunt capacitance and holder, and for

operation in a *standard* circuit. For MIL STD crystals the circuit is that specified in the Standard. For commercial crystals the schematic of the circuit used for calibration is generally supplied with the unit, or is otherwise specified. When used in a *nonstandard* circuit, the crystal will operate at a slightly different frequency from the calibration obtained in the standard circuit (± 3 MHz maximum), depending upon the tolerance to which it is ground, the holder capacitance, and stray inductance and capacitance effects of wiring.

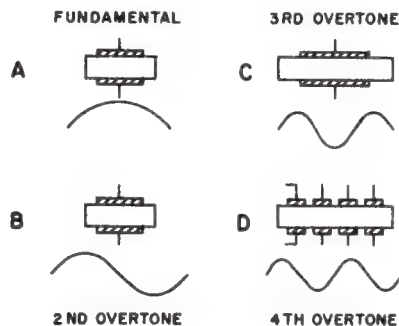The following figure shows the basic flexural vibration modes for fundamental, second overtone, third overtone, and fourth overtone operation of a crystal bar. These modes are used at low frequencies, where a bar producing lengthwise vibrations instead of a plate is used.




Crystal Flexural Vibration Diagrams for Lengthwise
Vibrations

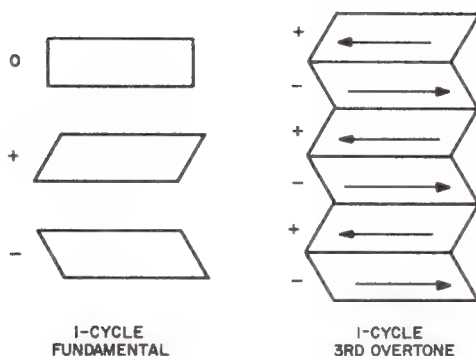Part A of the figure shows the basic mode of operation as the fundamental frequency with the bar bending in the middle, and parts B, C, and D show second, third, and fourth overtone operation. In part B, note that the second harmonic flexing is of opposite direction, or phase, and that with a single plate extending the length of the crystal the bar cannot easily oscillate. On the other hand, the third overtone has the same motion or phase at both ends with the middle free to flex. In practice, the output on the third overtone is strong with a single plate, but the output of the second overtone, if not completely canceled, is so weak that it is unusable (the bar has practically no piezoelectric effect). By plating a single

electrode and then dissolving the plating between nodes, it is possible to get free flexing and piezoelectric effect from even overtones, either separately through each set of plates, or by using one or the other of the end plates for excitation as shown in part D of the figure.

In the high-frequency crystal a different condition exists. Here the thickness shear mode is the mode of interest, and it is illustrated in the following figure. It is clearly seen that the vibrations in this mode are as if the crystal were squeezed with a shearing motion, distorting it somewhat as shown. Since this motion is essentially lateral, the crystal may be clamped at the edges, without being appreciably affected by the spring pressure between the plates; that is, the mechanical friction is negligible. When operating on an overtone, the high-frequency crystal appears to be formed of layers with the motions occurring in opposite directions. It should be understood, of course, that the illustrations are exaggerated to convey the idea. Basically, a crystal does not oscillate on one frequency; it has numerous nodes and modes, which can be affected by changes in temperature and excitation. For example, it is possible to heat the crystal by overexcitation, and cause it to change from a mode of operation at one temperature to another mode of operation at a higher temperature. It is also possible to cut and grind it so that it oscillates most vigorously on a particular frequency for *fundamental* crystals, and overtone frequency for *overtone* crystals.



Thickness Shear Vibration Diagrams

Overtone operation is normally restricted to the odd harmonics on high-frequency thickness shear type crystals. In the circuit to be discussed, the crystal will operate only at the overtone frequency if ground for overtone operation. The circuit, however, will also operate at an overtone of a fundamental type crystal (which is some odd multiple of the fundamental frequency), but it will not operate at the fundamental frequency unless the tank is tuned to the fundamental frequency. It is possible to operate up to the third or fifth overtone with fundamental crystals and up to the ninth or higher overtone with overtone crystals.

As a matter of academic interest, it should be noted that crystals have been made which will operate on even harmonics, but this is the exception rather than the rule; only crystals which operate on odd overtones are of practical interest.

Since the overtone crystal is usually very thin, its mounting is very important. Therefore, it is usually plated and connected to wire electrodes in a sealed container. It is also very sensitive to surface imperfections; for example, scratches that would not affect the operation of the fundamental crystal can prevent operation of the overtone crystal. Therefore, extra care should be observed in handling and cleaning operations.

Generally speaking, the series-resonant crystal oscillator has greater frequency stability and can generate higher frequencies, whereas the parallel-resonant type oscillator is more economical to construct, can operate over a wider frequency range (by substitution of different crystals), and can generate greater output. However, there are a number of exceptions to this general rule. The *parallel-resonant oscillator* is primarily used with fundamental-mode crystals at frequencies below 20 MHz. In conventional circuits of this type, the crystal must operate between its resonant (series-resonant) and anti-resonant (parallel-resonant) frequencies, thereby behaving as an inductor. Under these conditions, the circuit will not oscillate if the crystal becomes defective and the oscillator is a true crystal-controlled type. Maximum stability is achieved with a low crystal drive and with operation in the class A to class B range. For maximum power output, the oscillator is operated class C. With normal voltages the electro-mechanical coupling in the parallel mode of operation tends to become too weak to sustain oscillation at the


higher frequencies. This reduction in coupling, plus the shunting effects of tube and crystal capacitances, makes increased drive and plate voltage necessary to produce oscillation, thus leading to crystal fracture or instability; hence, it is impractical to use the parallel mode at the higher frequencies. It is possible though, by frequency multiplication in a number of subsequent stages, to obtain high-frequency operation with a parallel mode basic crystal.

The *series-resonant oscillator* is almost always used with *overtone* crystals. Because the output is lower than that of the parallel-resonant type, the operating range is restricted, and more parts are required. The series-resonant crystal oscillator is usually used only for high frequencies, or for low and medium frequencies where special design considerations make its use justifiable (mostly for frequency standards and laboratory and test equipment).

The inertia of the mechanical equivalent of the crystal oscillator provides a stable oscillatory action that is little affected by the varying parameters of the electron tube circuit (and for which crystal-controlled oscillators are noted) so that changes of tube capacitance or line voltage have little effect on the frequency of operation. In fact, the change of crystal dimensions with temperature usually has a greater effect. In this respect, the X-cut crystal has a *negative* temperature coefficient of 20 to 25 parts per million per degree centigrade (a 10°C rise in temperature of a 5000-kHz crystal produces a lowering in frequency of 1000 to 1250 Hz), and the Y-cut crystal has a *positive* temperature coefficient of 75 to 125 parts per million per degree centigrade. Thus, it can be understood that various crystal cuts provide different temperature coefficients, each suitable for different ranges of operation, with each different cut designed for zero temperature coefficient (see previous illustrations for typical cuts and typical temperature-frequency variations) or as near thereto as possible. (The GT cut is the only one which covers a large range of temperatures.) For exact frequency operation, as needed in frequency standards or for special uses, temperature compensation is utilized, with the crystal ground and cut for a zero temperature coefficient over a temperature range easily sustained by the thermostatically controlled oven.

The effect of the crystal holder and the shape of the crystal have a slight effect on the resonant frequency, which varies with the cut. For example, a Y-cut crystal may be clamped at the edges without


affecting operation (see accompanying illustration), whereas an X-cut crystal will oscillate only if all edges are free. Since the crystal is mounted between two metal plates and is a dielectric, there is an equivalent capacitance for the crystal determined by its dimensions, plus a capacitive effect due to the plates of the holder. Thus air gap holders, provided with a variable top plate adjustment, are sometimes used. Changing the effective capacitance by adjusting the gap changes the frequency of operation slightly (from 500 Hz to 3000 Hz maximum).

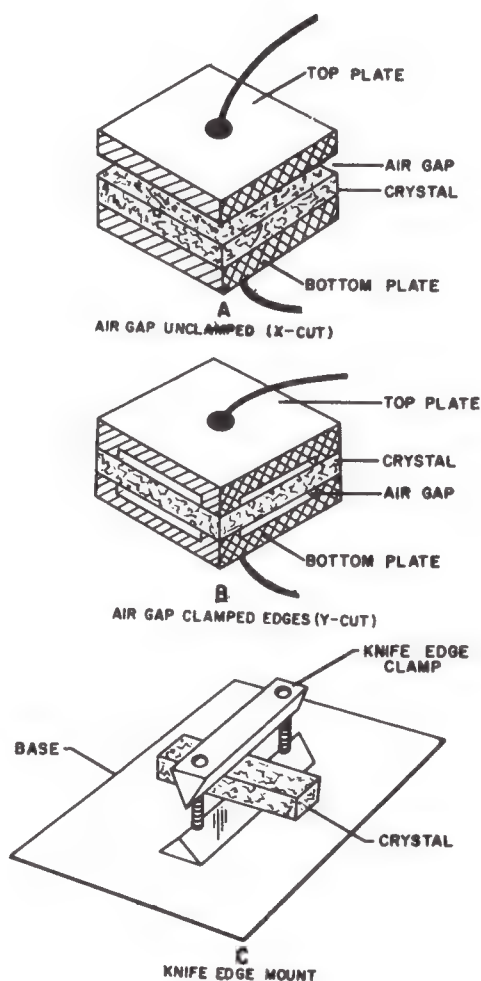

Typical Mountings

The electrical equivalent circuit of the crystal and holder is illustrated in the following figure, to show

the parameters and components needed to stimulate a single quartz crystal. The inductance, L , is on the order of henries (for low-frequency crystals) with a Q of 100,000 or better. The series resistance, R , varies from unit to unit but is usually less than 500 ohms (the lower the better since it represents a loss of power). The capacitance of the crystal without a holder is represented by C and is on the order of a few picofarad. Where an air gap holder is used, the capacitance of the holder air gap is in series with the crystal, as indicated by C_g . The holder capacitance (with no air gap) appears in shunt with the crystal and also includes any wiring, stray, and distributed capacitance plus the grid interelectrode capacitance of the tube, all of which are lumped together as C_d . For the parallel-resonant mode of crystal operation, this capacitance is fixed at 32 picofarads for Military Standard crystals.

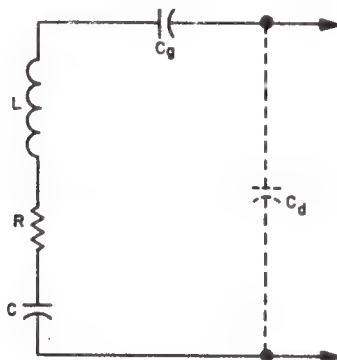

Crystal Equivalent Circuit

The discussion of electron-tube crystal oscillators is also generally applicable to semiconductor crystal oscillators. However, the basic semiconductor is less frequency stable than an electron tube, mostly because of its inherent ability to act as a variable capacitor with a change of collector voltage. In an LC oscillator the *tank circuit* is the frequency-determining and stabilizing element, but in the crystal oscillator, it is the *crystal* itself, because the crystal operates essentially as a parallel tuned tank or series tuned tank depending on the mode of operation. Therefore, whether semiconductors or electron tubes are used, the basic principles of operation of the resulting crystal oscillators are identical. The chief

differences in operation are the effects on feedback and the circuitry used for the effective feedback control.

Like the self-excited semiconductor oscillator, the crystal-controlled semiconductor oscillator also has circuit configurations similar to those in the electron-tube field, but none so well known by name as the Miller and Pierce circuits. Therefore, the circuit discussions are identified primarily from a functional standpoint rather than by name. By the principle of *duality*, most of the electron-tube circuit configurations have duals in the semiconductor field. Since there are numerous circuit variations now in use and the state of the art in such that changes occur constantly, the circuits have been classified into three arbitrary groups and a circuit typical of each group will be discussed.

The first group, known as the *transformer-coupled group*, includes those oscillators using mutually coupled separate coils to provide feedback. The oscillators in this group have the advantage of extreme flexibility. They can be used in either CB, CE, or CC configurations, since polarities and impedances can be completely controlled by the number of turns and directions of the windings. The second group uses a capacitive voltage divider and is called the *Colpitts-type crystal oscillator*. The third group is the *overtone group*, which generally uses a tuned tank with a tapped coil in a Hartley type feedback arrangement operating at a desired harmonic or overtone. In any of these circuits, series or parallel resonance of the crystal may be employed. However, since the transistor is a low-impedance device, operating with relatively low voltage and high current, it conveniently lends itself to the use of series mode crystal operation, using only one stage instead of two stages as is necessary in the electron-tube circuit.

Because the transistor is basically a low-power device, it minimizes problems of heating and over excitation, which often cause crystal shattering in the power-tube oscillator. Thus, frequency changes due to thermal effects within the crystal are usually negligible, and ambient temperature changes are more important. For extreme stability, temperature compensation is necessary, particularly since the transistor itself is temperature sensitive and generally requires compensation. At normal room temperatures (or lower), and with average low-temperature or zero-temperature coefficient crystals, the transistor


crystal oscillator is stable enough for average use without compensation. At higher temperatures, compensation of the transistor, if not the crystal, is necessary in most cases.

Dc stabilization (biasing) methods as discussed in the Amplifier Section of this handbook are used in crystal oscillators, as well as self-excited oscillators, to insure that variations of emitter and collector voltages and currents do not cause parameter changes. The use of the form of stabilization generally results in more power being consumed in the biasing circuits than in the basic oscillator.


In considering output requirements, the load is generally in shunt with the crystal or the tuned tank circuit; as a result, increased power output usually affects the frequency stability by degrading the Q of the resonator or increasing the effective coupling impedance between crystal and feedback circuit. Or, as in self-excited oscillators, the less the output required, the more stable the frequency, and the less load changes affect the circuit. For all ordinary purposes, the good mechanical stability of the crystal resonator makes it almost free from the effects of load changes, particularly if the collector voltage is regulated.

Good crystal oscillator design requires the use of low impedance coupling between the oscillator and resonator, the use of either resistance stabilization (in the form of series resistance in the emitter and collector circuits) or reactance stabilization, regulation of supply and bias voltages through the use of Zener diodes, the temperature control of both the transistor and the crystal.

In the following circuit discussions, the external feedback type of oscillator is discussed. However, it is possible to use the inherent negative resistance of a transistor to provide oscillation. In this case, a tuned or high-impedance circuit is employed in the base-emitter circuit, and the crystal provides a low-impedance (series) feedback connection resembling the Miller and Pierce electron-tube circuits, as shown in the accompanying illustration. These types of oscillators (primarily used with point-contact transistors), however, are dependent entirely upon the transistor parameters since the feedback is entirely within the transistor and varies with each one. Such circuits are considered undesirable, except for special applications; they have been mentioned only for general information and will not be discussed further.

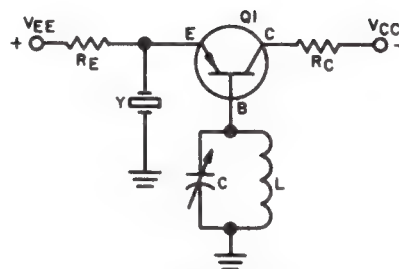

EMITTER-BASE CRYSTAL

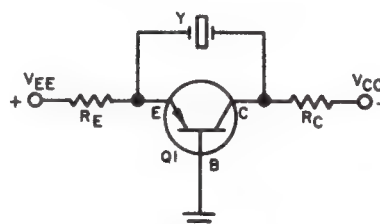

EMITTER-COLLECTOR CRYSTAL

Basic Negative-Resistance Type Oscillators

GRID-CATHODE (MILLER) CRYSTAL OSCILLATOR. (ELECTRON TUBE)

Application.

The Miller crystal oscillator circuit is used to supply a constant-frequency sine-wave output at a relatively constant amplitude, usually within the r-f range. This circuit is used wherever a highly stable specific frequency is needed, such as the basic oscillator in a transmitter, receiver, frequency standard, or test equipment.

Characteristics.

Utilizes piezoelectric effect of a natural or synthetic crystal to control frequency of oscillation.

Crystal is connected between grid and cathode of an electron tube.

R-F feedback occurs only through grid-to-plate inter-electrode tube capacitance.

Operates normally with class B or C automatic self-bias, but may be operated class A or with combination fixed and self-bias for special designs.


Frequency stability is excellent, with or without temperature compensation.

Output amplitude is relatively constant.

Circuit Analysis.

General. The Miller-type crystal oscillator uses the crystal connected between the grid and cathode tube elements. Because of its popular usage, it is sometimes considered the basic crystal oscillator. However, the Pierce-type crystal oscillator which uses the crystal connected between the grid and anode tube elements, and is discussed later in this section, is also a basic type of crystal oscillator. In some other texts the Miller oscillator may be called the Pierce-Miller oscillator. However, to avoid confusion in this Handbook, the grid-cathode-connected crystal is called the Miller oscillator, while the grid-plate-connected crystal is called the Pierce oscillator. The Miller circuit is popularly used because, for a given amount of crystal excitation, it provides a greater output than any other circuit arrangement; the output is greater because the basic feedback occurs between the grid and plate of the electron tube, and not through the crystal. This also prevents the crystal from being subjected to sufficient strain to cause fracture of the crystal, and the tube may be driven harder.

Circuit Operation. The basic Miller oscillator is shown in the accompanying illustration. The crystal is located between the grid and cathode, and grid-leak bias is obtained through R1, with the shunt capacitance of the crystal, together with that of the holder, acting as the grid-leak capacitor. The tuned tank circuit, LC, is located in the plate-to-cathode circuit. As shown, the rfc and C1 form a conventional series plate-feed decoupling circuit, but the tank may be shunt-fed, if desired.

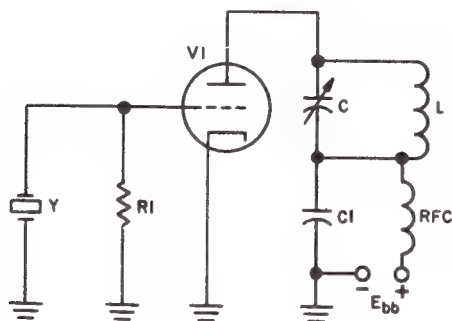

Basic Crystal (Miller) Oscillator

Crystal action in controlling oscillation can be explained as follows: Assume that the tank circuit in the basic oscillator is tuned to a higher frequency than the anti-resonant (parallel-resonant) crystal frequency, so that the plate circuit appears inductive. Assume also that filament and plate potentials are applied and the crystal is not vibrating. A positive voltage is present between plate and ground, and a negative voltage is present between grid and ground (due to contact potential). By piezoelectric action, the negative grid voltage will cause the crystal to be deformed slightly. Assume that a noise pulse occurs and causes the grid to go more negative, thus further deforming the crystal. The deforming of the crystal produces a piezoelectric action, increasing the charge on the grid in the same direction, and drives it further negative. When plate current cutoff is reached, the feedback becomes zero, and the accumulated grid voltage discharges through grid leak resistor R1. As the grid voltage is reduced, the deformation of the crystal is reduced, and the negative piezoelectric charge on the grid is also reduced by a corresponding positive induced piezoelectric voltage until plate current again flows. This cumulative action causes the crystal to vibrate mechanically near its parallel-resonant frequency. Once started the vibrations continue and induce in the grid circuit an ac voltage of a frequency almost equal to the vibration frequency of the crystal. As long as the plate tank is tuned to present an inductive reactance, the proper phase for feedback is maintained. When the tank is tuned on the capacitive side of the frequency of oscillation (to a lower frequency), the phase of the crystal oscillation opposes the plate-to-grid feedback, and oscillation is reduced and eventually stopped. Tuning the tank circuit allows the feedback to be controlled from minimum to maximum with a corresponding output. To produce the proper phase relationship, tuning is approached from the high capacitance side of resonance. Plate current varies in a similar manner from a high value to a low value at the optimum point, then suddenly increases and abruptly reaches its normal static (non-oscillating) value as the series-resonant frequency is approached. The action described, although slightly exaggerated for ease of understanding, happens very quickly. That is, the tube reaches its class B or C operating condition in one or two cycles of operation.

Since the crystal is essentially the equivalent of a high-Q circuit, it resonates only over a very narrow range of frequencies (tuning is very sharp). Therefore, slight changes in tube parameters and supply voltages have a minimal effect, about 100 to 200 times less than in the conventional LC oscillator.

Biasing Considerations. In the basic Miller oscillator shown above, the bias is supplied by means of grid-leak action, as in the conventional LC feedback oscillator. Since the crystal represents a very high-Q circuit (a Q of 100 times or more than that of the conventional LC tank), it is evident that grid leak resistor R1 effectively acts as a shunt for the voltage generated by the vibrating crystal. Therefore, an r-f choke is sometimes placed in series with the grid leak to reduce the load on the crystal and help it start oscillating more easily. When a bias battery replaces the grid leak and the series-connected r-f choke is also used, the grid operating point is fixed by the battery bias, and the circuit can be adjusted for maximum power output, with minimum crystal excitation and good output waveform. The combination of battery bias and r-f choke, however, does not make for easy starting. The use of cathode bias, together with the r-f choke and with or without the grid resistor, normally provides the most effective starting, and is used where keyed oscillator operation is required (maximum stability dictates that keyed operation be avoided).

As the bias is increased, the crystal current increases, because more excitation is needed to swing the operation into the cutoff region and overcome the bias. The increased bias also increases the mechanical distortion of the crystal and causes it to vibrate harder. If driven excessively, the crystal will shatter.


Other Considerations. The plate voltage applied to the crystal oscillator is limited to a value lower than that applied to the standard LC oscillator, because as the power increases with an increase of plate voltage, so does the feedback voltage, which in turn increases the current through the crystal. The increase of crystal current has two effects: (1) it may exceed the value where it causes the crystal to vibrate so strongly that it shatters; (2) since the temperature of the crystal depends upon the current flow through it among other things, unless the crystal has a zero

temperature coefficient over a wide enough range, the frequency of operation will vary, either increasing or decreasing, depending upon whether the temperature coefficient is positive or negative.

Temperature changes external to the crystal will change the grid-to-plate interelectrode capacitance of the tube, and supply voltage changes will change the plate impedance and affect the frequency of operation. This frequency change occurs in parallel-resonant crystal operation because either a change in the feedback capacitance or the plate load impedance will affect the phase shift in the feedback loop, and cause the crystal to operate at a frequency somewhat nearer to or farther from the antiresonant frequency, to satisfy the conditions for sustaining oscillation.

The Miller oscillator provides an average frequency deviation of approximately 1.5 times that of the Pierce oscillator (to be discussed later) and is therefore less stable than the latter circuit. On the other hand, it will give the same output (or slightly more) with only half the grid excitation and crystal current. Thus, with the same excitation, the Miller oscillator can supply twice the power of the Pierce oscillator and effectively obviate the need for an additional stage of amplification to bring its output up to the value needed to drive a following power amplifier. (The high output power largely accounts for the popularity of the Miller circuit and its almost universal use.) When used with a pentode, the Miller circuit provides maximum output with minimum crystal strain and excitation, and also greater stability (see the Electron-Coupled Crystal Oscillator circuit discussion given later in this section).

Detailed Analysis. The basic Miller oscillator is considered to be a variation of the tuned-grid, tuned-plate oscillator, in which the feedback occurs solely through the grid-plate interelectrode capacitance. The equivalent circuit of the Miller oscillator is shown below with bias and plate voltages omitted for simplicity. The crystal tank (tuned-grid) circuit is represented by L_1 , R_1 , C_3 , tuned by interelectrode capacitance C_{gk} , and the plate tank by L_2 , R_2 , tuned by variable capacitor C_2 . The two circuits are coupled by the internal plate-grid capacitance, C_{pg} , for feedback purposes.

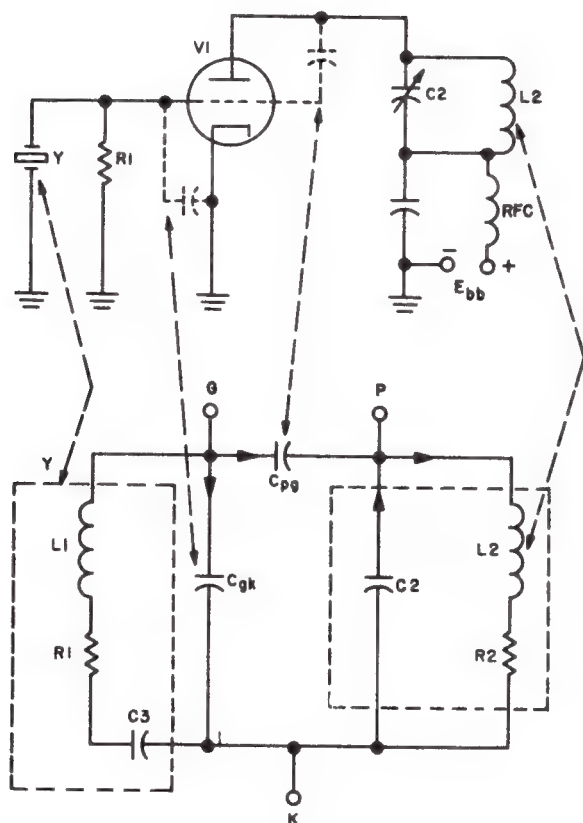


Basic Miller Equivalent Circuit

The plate circuit must appear inductive so that the correct phase shift will be produced in the developed r-f plate voltage to compensate for the effect of the resistance in the feedback loop; this resistance prevents the necessary 180-degree phase rotation of the equivalent generator voltage of the amplifier from occurring entirely in the feedback circuit. Since the load capacitance is a function of frequency, the Miller oscillator cannot be operated at more than one frequency and still present the same load capacitance to each crystal unit, unless provision is made for adjustment of the circuit parameters. Hence, the tuned tank circuit is required so that the plate circuit will appear inductive when the tank is tuned to the high-frequency side of crystal resonance.

Now examine the means by which the proper phase relationships between the grid and plate voltages are maintained to produce oscillation. In the

conventional electron tube, the grid and plate voltages are always 180 degrees out of phase. When the grid voltage is positive, it causes the plate current to increase. Consequently, the voltage drop across the plate load impedance produces a negative-going output voltage. If this output were fed back to the grid, it would oppose the grid voltage and reduce or prevent any possible oscillation. To produce oscillation it is necessary to shift this phase another 180 degrees. Thus, a positive-going grid voltage must be reinforced and enhanced by a positive-going (feedback) voltage from the plate circuit. If the feedback voltage is sufficient to replace any losses in the feedback circuit, continuous oscillation will occur. Now consider the crystal oscillator equivalent circuit which follows:

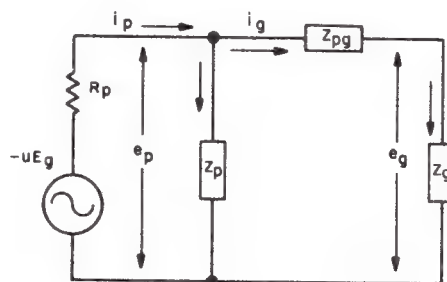


Crystal Oscillator Equivalent Circuit

The equivalent generator voltage is $-\mu E_g$, where μ is the amplification factor of the tube and E_g is the excitation voltage on the grid. R_p is the plate resistance of the tube, and Z_p is the plate impedance from plate to cathode, with Z_g as the grid impedance from grid to cathode. These impedances are reactive, and must always have the same sign for oscillation to be produced. Considering an ideal circuit with no feedback losses, the plate-to-grid impedance, Z_{pg} , is the dominant impedance in the feedback circuit, and is always opposite in sign to Z_p and Z_g . If Z_p and Z_g are positive, Z_{pg} is negative; thus the current, i_g , leads e_p and $-\mu E_g$ by 90 degrees. If Z_p and Z_g are negative, Z_{pg} is positive; thus i_g lags e_p 90 degrees. The voltage across Z_{pg} , of course, is in phase with e_p in both instances. Since Z_g is opposite in sign to Z_{pg} , e_g is thus opposite in sign to e_p , and the required phase reversal takes place. Note that i_g is first rotated in phase with respect to e_p ; next, e_g is rotated in the same direction with respect to i_g .

In a practical circuit, the feedback losses cannot be zero; thus an exact 180-degree reversal cannot be obtained in the feedback circuit alone. This means that e_p must first be rotated by an amount exactly sufficient to make up the losses in the feedback circuit. To do this, the plate tank is tuned to a higher frequency than the antiresonant crystal frequency. Therefore, Z_p appears as an inductive reactance, and e_p is rotated in a leading direction. The smaller the value of R_p , the more nearly will Z_p control the phase of i_p , and the more detuned must the tank circuit become in order to produce the necessary rotation of e_p . If practically all the resistance in the feedback arm is between the grid and the cathode, as is normally the case when e_g is developed directly across the crystal unit, e_p must be rotated through a larger angle than otherwise, thereby requiring the tank circuit to be detuned to a greater degree.

In a conventional parallel-resonant crystal oscillator having an ideal feedback arm, the frequency would be entirely determined by the resonance of the tank circuit; thus fluctuations in R_p , although effective in changing the activity, would not affect the frequency. In practical circuits, changes in both R_p and Z_p will slightly shift the phase of E_p and, consequently, the frequency. The basic amount of frequency shift is fixed by the crystal used, varying directly with the Q and the shunt capacitance of the crystal. This is the reason for using a standard value of 32 picofarads for crystal capacitance; the Q depends upon crystal processing and composition, and thus varies somewhat.

In the Miller circuit, the maximum permissible voltage across the crystal unit is $(k + 1)$ times the maximum voltage, where k is the gain of the stage and is equal to e_p/e_g , as shown in the crystal equivalent circuit. Theoretically, this gain can approach the μ of the tube as a limit when the load impedance, Z_L , is large as compared with the plate resistance, r_p (as shown by the following simple electron tube amplifier equivalent circuit); this explains the large output obtainable from this circuit when used with hi- μ tubes.

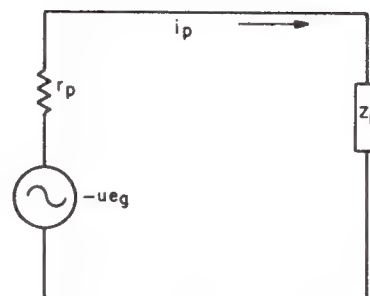

Electron Tube Amplifier Equivalent Circuit

When a pentode, instead of a triode, is used as the oscillator tube, it is usually necessary to insert a small feedback capacitance between plate and grid, because of the small value of interelectrode capacitance present in the pentode. The output waveform is also improved by using a tuned tank circuit with a low L/C ratio. Since the tuning must be such that the tank impedance appears inductive, the tank circuit provides an effectively high- Q plate load when the tank capacitor is set for the proper load capacitance.

Failure Analysis.

No Output. Since the crystal controls oscillation, the crystal will not oscillate and no output will be obtained if the crystal is removed, if poor or loose holder connections cause an open or high-resistance circuit, if the plate circuit is detuned sufficiently, or if no plate voltage is present because of open- or short-circuit conditions. When sustained arcing (caused by too high a crystal r-f excitation current) produces burnt spots on the holder or crystal, it will not oscillate until cleaned (this condition normally does not occur in pressure type holders, but may occur in unloaded or air gap holders). Navy policy is to return defective crystals to the crystal laboratory for repair. Do not attempt to clean crystals. An open r-f choke or a short-circuited plate bypass capacitor will remove plate voltage from the tube, and the

crystal will not oscillate. Poor soldered connections on the tank coil in a series-fed circuit will produce a similar result. An open-circuited grid RFC in a circuit using no grid or cathode bias resistor will open the grid circuit and prevent oscillation unless the crystal is defective and has a low resistance. Insufficient feedback capacitance between tube elements (most likely to be associated with pentodes) will cause the crystal to stop oscillating (This condition will not occur in an oscillator which has previously oscillated unless the tube becomes defective).

Reduced Output. Low plate voltage, a detuned plate tank circuit, or a crystal of low activity will result in reduced output. An open-circuited tank capacitor will allow the circuit to act as an untuned plate oscillator and, if the feedback is not too greatly out-of-phase, may permit weak oscillation; this trouble may be easily located because the tuning of the tank will not affect the plate current, and the plate current will be high, near its normal non-oscillating value. Increased resistance in the feedback arm due to poorly soldered connections will cause less phase rotation and, if excessive, will result in weak oscillation or entirely prevent operation.

Unstable Output. Any instability as far as oscillation is concerned would be associated with the feedback circuit and the crystal. A defective crystal, due to a partial fracture, may cause instability of amplitude and frequency. A defect causing the output to change from one mode of crystal operation to another could also cause instability, but in most instances it would be easily discovered because it would also change the operating frequency. An intermittent open, short-circuited, or partially open bypass capacitor may also cause a similar condition, although it is more likely to result in either no output or reduced output.

Incorrect Frequency. Since frequency is primarily determined by the crystal and tank circuit tuning, either a defective crystal or tank circuit may cause a change of frequency. The most probable trouble would be a defective, burnt, dirty, or fractured crystal. Changes of frequency on the order of only a few cycles per second may be due to tank detuning or temperature effects; changes greater than a few cycles per second indicate a change of crystal parameters. Temperature variations are generally indicated by a slow change of frequency in one direction with an increase of temperatures; such variations may occur if the ambient temperature is above the range of

thermal compensation provided. A slight change in frequency, due to aging or a change in drive level, can normally be compensated for by a slight change or tank tuning; otherwise, the crystal must be replaced.

GRID-PLATE (PIERCE) CRYSTAL OSCILLATOR (ELECTRON TUBE)

Application.

The Pierce crystal oscillator circuit is used to supply approximately a sine-wave output of relatively constant frequency, usually within (although not restricted to) the r-f range. This circuit is used wherever a specific frequency of extreme stability and of moderate power output is needed, such as the basic oscillator in multistage transmitters, test equipment, receiver-converters, etc. It is usually interchangeable with the Miller oscillator in low- and medium-frequency applications, but it is not often used in high-frequency applications, mostly because of its low output.

Characteristics.

Utilizes piezoelectric effect of a natural or synthetic crystal to control frequency of oscillation.

Crystal is connected between grid and plate (or any other element acting as an anode) of an electron tube.

Does not require an LC tank circuit for fundamental mode operation.

R-F feedback occurs only through crystal.

Operates normally with class B or C automatic self-bias, but may be operated class A or with combination fixed and self-bias for special design.

Frequency stability is excellent, with or without temperature compensation.


Output amplitude is relatively constant.

Circuit Analysis.

General. The generalities applicable to the basic crystal oscillator in the discussion of the Miller circuit are also applicable to the Pierce circuit. The simplicity of the Pierce oscillator, with its lack of tuned plate tank and its ability to oscillate easily over a broad range of frequencies with different crystals, makes it popular for use in crystal calibrators, receivers, and test equipment, and in transmitters not requiring much drive. The Pierce circuit is sometimes considered as the inverse of the Miller circuit since it exhibits opposite effects. Thus, instead of operating

as an inductive reactance as the Miller circuit does, the Pierce circuit operates as a capacitive reactance (when a tank circuit is employed, it is always tuned for a lower frequency). The crystal excitation voltage for the Pierce is approximately half that permissible with the Miller circuit. The plate load of the Pierce oscillator is resistive and is usually large enough in value that minor fluctuations in the tube plate resistance have much less effect on the frequency of operation than in the Miller circuit. This is used to best advantage when a pentode is employed, since its inherently high plate resistance and low grid-plate capacitance permit a greater range of plate load with the use of an external capacitor to fix the amount of excitation.

Circuit Operation. The basic Pierce oscillator circuit is shown in the accompanying illustration. Conventional grid-leak bias is obtained through C_g and R_g , which operate as described previously in the Amplifier Section of this handbook, and in the LC Tickler Coil Oscillator Circuit discussion given previously in this section. The crystal, which is connected between grid and plate, offers a high Q . The inductive reactance of the crystal, together with the capacitive reactance of $C1$ (which consists of tube and stray wiring capacitance), provides the final phase rotation required to produce the 180-degree shift in the feedback voltage in order to sustain oscillation. The plate load is resistor $R1$. $C2$ is the conventional plate bypass capacitor used in series plate feed arrangements. The use of resistor $R1$ in the plate circuit provides a relatively flat response over a wide range of frequencies, so that various crystals may be substituted for operation on other frequencies without any tuning being required. In some instances, however, when it is desired to operate on a single frequency or over a narrow range of frequencies, with increased output, an r-f choke is substituted for $R1$. This choke eliminates the dc power loss in the resistor and provides a high r-f impedance for proper operation; since the plate voltage is increased, the (resistor voltage drop is eliminated) output is also increased.

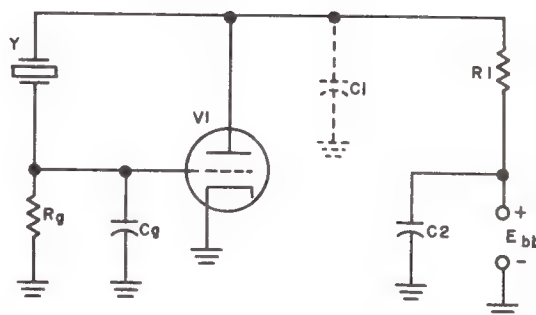

Pierce Crystal Oscillator Circuits

Now consider one cycle of operation. Assume that crystal Y is at rest and that the circuit as illustrated above is inoperative, with no plate voltage applied. At rest, the crystal is unstressed and there is no charge on either plate. When the plate voltage is applied, since no bias exists initially, heavy plate and grid current flows. Simultaneously, the crystal is stressed by this plate potential, and a piezoelectric charge appears across the crystal. The sudden shock of applied plate voltage causes the crystal to start oscillating at its parallel-resonant frequency. Assume also that the plate voltage stress induces a positive piezoelectric charge on the grid, which tends to increase plate current and grid current flow. The plate current quickly reaches saturation at some low plate voltage, caused by the drop through plate resistor $R1$. Meanwhile, grid current flow is producing a negative voltage drop across R_g , thus charging C_g . As the crystal vibrates in the opposite direction, it induces a negative charge which adds to the negative grid voltage produced by the charging of C_g . As a result, plate current is now reduced by the increasing grid bias, and the plate voltage rises. The rising plate voltage again induces a positive charge on the grid. The crystal now flexes in the opposite direction, and the plate voltage again induces a positive charge on the grid by piezoelectric effect. Grid current flow again tends to charge C_g , and the cycle is repeated.

For oscillations to occur, the crystal must be effectively synchronized in its vibration, so that the piezoelectric effect does not oppose oscillation by reducing the feedback between grid and plate. The proper phasing is accomplished by connection of the crystal between grid and plate. The inherently high Q of the crystal makes it act as a large inductor to shift the phase of the feedback voltage in the proper direction to cause oscillation. Capacitance C_1 provides additional phase shift to complete the 180-degree rotation needed.

Bias Considerations. As in the conventional LC oscillator, grid-leak bias may be employed for self-bias and amplitude stabilization, but unlike the grid-leak circuit in the Miller oscillator previously discussed, it usually employs a grid capacitor (C_g) because the crystal is connected between grid and plate and cannot provide the necessary grid-leak capacitance.


During operation, grid bias is produced by the grid leak and capacitor combination of R_g , C_g . As grid current is drawn the capacitor charges, and in the absence of grid current it discharges. After a few cycles of operation an equilibrium state is reached where the slight amount that leaks off during the negative cycle just equals the amount of charge during the positive cycle; thus a steady bias is maintained. This action is similar in all respects to that of the conventional grid leak in other forms of oscillator circuits.

Since the excitation in a Pierce oscillator is low, it is common to use a higher value of grid-leak resistance than in the Miller oscillator (grid bias is equal to $I_g R_g$). Fixed bias can be used in place of grid-leak bias to stabilize the operating point; however, fixed-bias operation normally requires that starting provisions be made, particularly if the bias voltage is at or below cutoff. When a power-type oscillator is required, a combination of cathode bias and grid-leak bias is sometimes employed. Use of the cathode bias provides a protective bias voltage in the absence of excitation and allows the use of a lower value of grid-leak resistance. However, the use of the combination bias also reduces the starting sensitivity and may be objectionable for keyed oscillators.

Other Considerations. Although the Pierce oscillator is normally used without a plate tank circuit, this is not always so. Where the output waveform is important, use of a selective tuned circuit in the plate circuit minimizes the harmonic content in the output

and thus provides a purer waveform than is produced by a resistive plate load, which is not frequency responsive and provides a high harmonic content. Selection of the circuit with a resistor plate load for use in a crystal calibrator to supply harmonics of 200 to 300 times that of the fundamental proves particularly advantageous. On the other hand, when overtone operation is desired, the Pierce circuit *must* use a tuned tank circuit to select the desired overtone if a useful and practical output is to be obtained.

Since this circuit is a vigorous oscillator, it lends itself to use as a multifrequency oscillator which permits numerous crystals to be switched into the circuit to obtain operation over a wide range of frequencies, as shown in the following illustration. A particular advantage of the Pierce oscillator is that, since crystal activity varies considerably from crystal to crystal, it will operate with a weak crystal as well as a strong one. Since the Pierce oscillator is normally operated at a low output than that of the Miller oscillator, an additional amplifier stage can bring the output up to the same level. Such operation can be accomplished conveniently by using a single dual-triode tube as oscillator and amplifier.

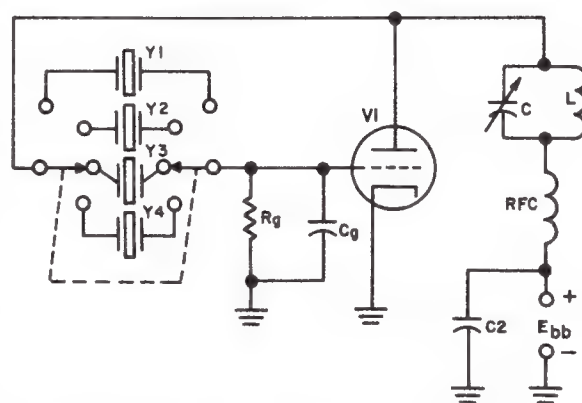


Multifrequency Crystal Oscillator with Plate Tank

Lack of a tuned output circuit sometimes causes difficulty when a crystal is used which has a strong overtone activity as compared with the fundamental, because the Pierce circuit tends to respond at the frequency of strongest activity. However, this is a fault of the crystal rather than the circuit, as a fundamental-ground crystal has its greatest activity at the fundamental frequency.

Because the plate impedance is resistive and of a high order, fluctuations in the plate resistance of the tube (which are only a small percentage of the total plate resistance) because of varying supply voltages or loads have less effect on the output frequency, so that this circuit is basically more stable than the Miller type oscillator.

Because the crystal is in series with the feedback from plate to grid and has full plate voltage across it, caution must always be observed to keep the fixed plate voltage below that which could cause excessive feedback and produce shattering of the crystal, or a frequency change due to heating of the crystal.

Circuit Modifications. Some typical circuit modifications made to improve the operation of the Pierce circuit or to overcome an inherent defect as shown in the following illustrations and are accompanied by a brief explanation. There are many variations of the basic Pierce circuit, because as long as the crystal is connected between the grid and any element other than the cathode, the resulting oscillator is basically a Pierce circuit.

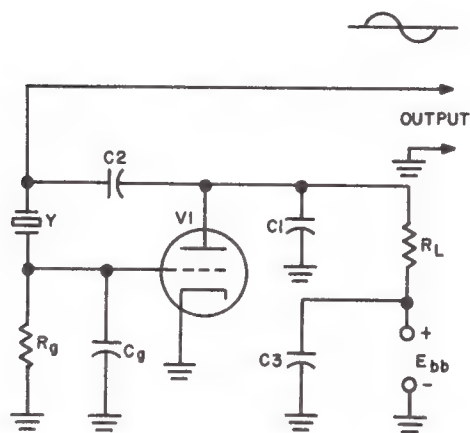


Grounded-Plate Pierce Circuit

The grounded-plate version of the Pierce circuit uses a capacitor, C2, to block the plate supply from the crystal and thus minimize the electrostatic strain on the crystal. Sometimes an r-f choke is placed in series with the cathode to reduce the shunting effect of C1; however, this choke is unnecessary if the other components are properly chosen. The plate load resistor, R_L , may or may not be used (when it is not

used, C3 is also eliminated). It might appear that, with no cathode choke and no plate load, the shunting effects of C1 and the power supply capacitor would effectively short-circuit the crystal output; however, since the output is taken directly between the crystal and ground, the shunting has little effect, and maximum crystal output is obtained.

The operation of this circuit is practically identical with that of the basic Pierce oscillator. Even though the schematic of the grounded-plate Pierce circuit shows that C2 prevents the dc plate voltage from straining the crystal, it does not prevent the plate voltage changes from appearing on the crystal. Furthermore, C2 is charged and discharged through the crystal capacitance. Therefore, the crystal is initially shocked into oscillation by the ac or r-f voltage changes occurring in the plate and grid circuits. Once oscillations are started, the operation is identical with that previously described for the basic circuit.

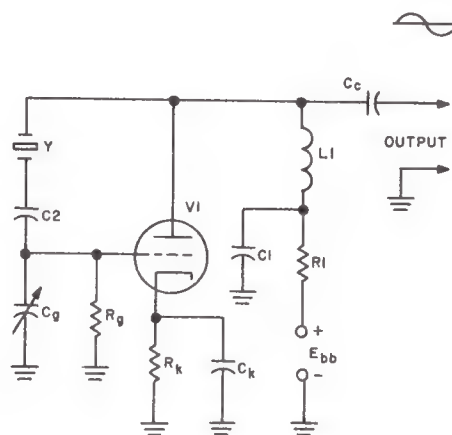Another variation, using combination cathode and grid-leak bias, is shown in the following figure.




Combination Bias Arrangement

In the circuit above, R_k is a low-value resistor (say 200 ohms) and furnishes cathode bias, being bypassed by C_k . Grid-leak bias is supplied by R_g (resistance on the order of 100,000 ohms) and C_g . The grid capacitor is made variable to provide a slight amount of tuning for the crystal, in order to permit operation with crystals of different frequencies. Actually, it has the same effect as C_1 in the basic Pierce circuit,

shown previously; that is, it provides the proper phasing for the predominantly inductive crystal to ensure oscillation. Capacitor C2 effectively reduces the strain on the crystal though it does not isolate it from the plate supply. In this respect, both this circuit and the preceding circuit show two variations of using a blocking capacitor in series with the crystal to reduce the crystal strain. This is done to protect the crystal; with a constant d-c potential applied to the crystal, it would be permanently strained in one direction, and could be shattered by the excessive strain produced when the oscillations are in the same direction as the applied plate voltage, causing it to vibrate greater in one direction than the other. In the circuit above, the plate load resistor is replaced by inductor L1 to avoid the d-c losses in a resistive load. The inductor also makes it desirable to have C_g variable to compensate for the phase-shifting of L1 (it is assumed that the distributed capacitance of L1 in this case does not tune the inductor to the frequency of oscillation). Resistor R1 is a voltage-dropping resistor which is used to reduce the plate supply voltage to the desired plate voltage level; it is not required if the correct voltage is provided by the power supply. Capacitor C1 is the conventional series-feed decoupling capacitor.

Another method of connecting the crystal to avoid the strain produced by the plate voltage is to ground the crystal directly and to ground the plate through a capacitor, as shown in the following illustration. With this arrangement, the cathode must operate above ground, and an r-f choke is used to provide the necessary isolation. Capacitor C3 effectively grounds the plate so that the crystal is connected between grid and plate, but is unstrained by the d-c supply potential. Resistor R_g , and capacitor C2, together with RFC and R_k , provide combination grid-leak and cathode bias, and C1 and C2 form a typical Colpitts type capacitive feedback voltage divider. Capacitor C_t represents the total grid tuning capacitance (both the interelectrode and stray wiring) which is the effective tuning capacitance across the crystal (32 picofarads with MIL-STD types). In this case, it is clearly seen that the crystal acts as the tank circuit (see Ultraudion Oscillator equivalent circuit shown in the following illustration), but that it is shunted by the grid leak, which effectively reduces its Q. The output is taken from across the crystal through coupling capacitor C_c .

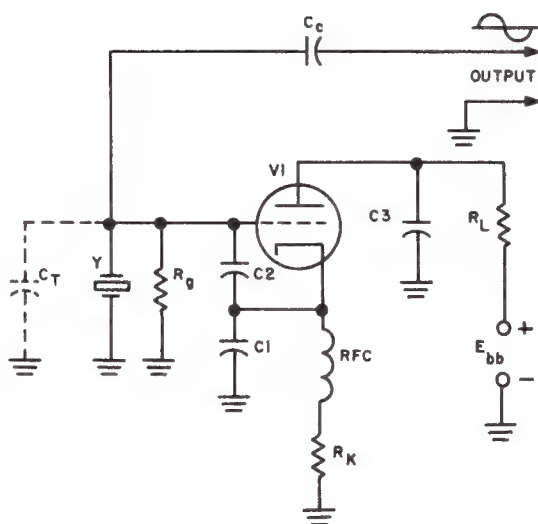


Grounded-Crystal Circuit Variation

Again, the circuit operation of the grounded-crystal stage illustrated above is practically identical with that of the basic Pierce oscillator previously described. The crystal is shocked-excited into vibration by the a-c plate and grid voltage changes. In addition, the capacitive voltage divider formed by C1 and C2 provides additional feedback to overcome the shunting effect on the crystal caused by grid leak R_g . Their value is such that the circuit will not oscillate with the crystal removed. Their use makes the circuit easier to start, and permits the use of crystals with much weaker activity than normal.


Detailed Analysis. The Pierce oscillator is considered to be the ultraudion version of the Colpitts type of L-C oscillator circuit, with the crystal taking the place of the plate tank as illustrated in the accompanying illustrations.

The Pierce circuit operates at a frequency which places it on the inductive side of parallel resonance in the crystal. When a plate tank circuit is used, it is always tuned to a lower frequency to make it appear as a capacitive reactance. Thus, the crystal operates somewhere between its series- and parallel-resonant frequencies. The tube grid-plate interelectrode capacitance, C_{gp} , is in shunt with the crystal, and the effective tank tuning capacitance of the inductive crystal is

the electrostatic crystal capacitance (represented by C in the Ultraudion equivalent illustration) in parallel with grid-plate tube capacitance C_{gk} , together with the series-parallel combination of grid-cathode capacitance, C_{gk} , and plate-cathode capacitance, C_{pk} (which includes the distributed wiring capacitances). For Military Standard crystals, this capacitance is always held to 32 picofarads total. Since the plate circuit is predominantly resistive, consisting of R_L only, as shown in the Pierce equivalent circuit above, any small fluctuation in any of these capacitances is minimized; as a result, the circuit has a more stable frequency of operation than the Miller oscillator. Capacitor C_1 , previously illustrated in the basic Pierce oscillator circuit, is usually inserted to ensure that the circuit will oscillate with many different types of crystals. Although the crystal (tank circuit L, R, C in the illustration) is connected between plate and grid, and feedback occurs through the crystal, it is the basic piezoelectric charge applied to the grid-cathode interelectrode capacitance, C_{gk} , that couples the crystal into the circuit electrically, as is evident from examination of the Pierce equivalent circuit shown previously. Because the plate circuit is predominantly resistive, small fluctuations in tube plate resistance due to changes in operating voltages are a smaller percentage of the over-all total plate resistance; therefore, greater frequency stability is obtained than in the tuned plate oscillator, in which plate resistance changes are a much greater percentage of the total load resistance. The higher plate resistance and lower grid-plate capacitance of the screen grid tube are particularly advantageous in the Pierce oscillator. Since the crystal is effectively the tank circuit and represents the highest impedance in the circuit, it is evident that the largest voltage is developed across the crystal, but it is limited by the maximum voltage and power dissipation that the crystal can withstand without shattering. Thus, the maximum output from this type of circuit is limited by the crystal power-handling capability (area), rather than by circuit components. (Modern, 1/2-inch-square, crystals have only 1/4 the power-handling ability of the old 1-inch-square type.)

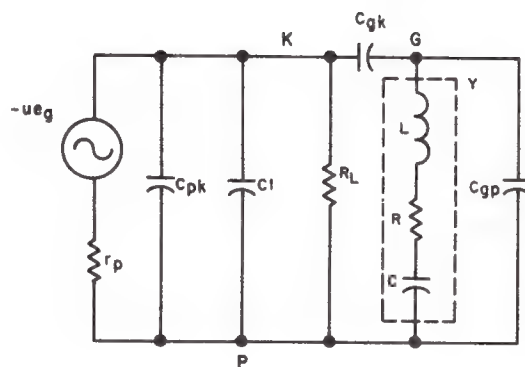

Pierce Equivalent Circuit

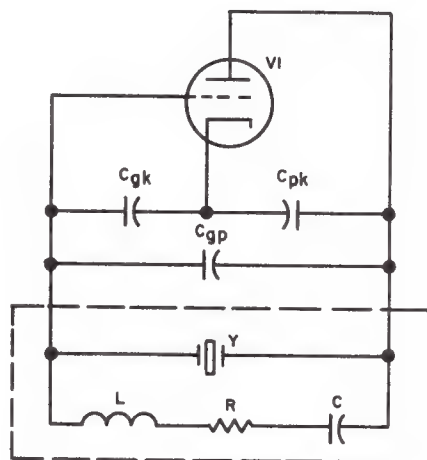

Ultraudion Equivalent Circuit

Pierce Equivalent Circuit

Ultraudion Equivalent Circuit

Ultraudion as Compared with Pierce Crystal
Equivalent Circuit

Failure Analysis.

No Output. If the crystal is removed or if poor or defective holder connections cause an open (or high-resistance) circuit, the crystal will not oscillate, and no output will be obtained. Also, if the plate load resistor is open or if a short circuit lowers the plate voltage sufficiently, the crystal will not oscillate. In the case of over-excitation when unloaded or air gap holders are used, the crystal may be burnt because of r-f arcs between the crystal and mounting plates, and it will not operate until cleaned. (Return crystal to repair center; do not attempt to clean it yourself.) In a poorly sealed holder, dust accumulation or moisture from condensation may also make crystal cleaning necessary. Normally, with the sealed, pressure-type holder, cleaning is unnecessary. An open series blocking capacitor will disconnect the crystal and stop operation.

Insufficient feedback capacitance between electron tube elements (most likely with pentodes) will prevent the crystal from oscillating, but this condition will not occur with a tube which has previously oscillated unless the tube becomes defective. An open grid resistor or capacitor will probably prevent operation, but may result in reduced output. Usually, only open-circuited or short-circuited conditions will prevent the circuit from operating. In the case of over-tone operation, excessive detuning of the plate tank can cause a stoppage of oscillation, which will resume after the circuit is properly tuned.

Reduced Output. Since the Pierce crystal oscillator operates vigorously when excited, any reduction in output will result from lack of excitation or low plate voltage, rather than from high resistance or poorly soldered contacts. An open or shorted grid capacitor or grid-leak resistor will change the bias conditions and result in either reduced output or no output. When the grid-leak bias is combined with cathode bias, failure of the grid-leak bias will cause reduced output and perhaps hard starting. A dirty crystal may not oscillate at all or only weakly, and could be the cause of reduced output. With unsealed crystal holders a reduction in output, hard starting, or stoppage of oscillation was a signal for possible cleaning; however, with modern sealed holders the possibility of crystal contamination is not very likely, but should be kept in mind. (Return crystal to repair center; do not attempt to clean it yourself.)

Unstable Output. Instability may be due to an intermittent or poor (high-resistance) connection in the feedback circuit, but it is more likely to be due to a defective crystal which has been partially fractured by over-excitation. A crystal which normally operates satisfactorily in a tuned Miller oscillator may be defective and have a spurious frequency which is produced alternately with the desired frequency, when the crystal is used in a Pierce circuit, and thus cause an unstable output. Such a condition is evidenced by changes in frequency, due to erratic jumping from one frequency to the other.

Incorrect Frequency. Since the crystal frequency is primarily determined by its own constants, an incorrect frequency is probably the result of a change in the crystal itself or in the holder and associated wiring capacitances. Normally these changes are very small. If the crystal is not temperature-controlled, over-excitation can cause sufficient heating of the crystal to change the frequency; this condition is normally indicated by a continuous drift in one direction as the crystal is heated. A zero-temperature-coefficient crystal operating within its range of compensation will not be affected by minor temperature changes. Since a tuning adjustment is usually not provided, a noticeable change in crystal frequency indicates a circuit or crystal parameter change which should be checked. With the few parts concerned in this type of oscillator, it should not be too difficult to determine the defective component. Crystal or tube aging effects may also cause a change in frequency, which would be indicated by a slow change over a long time. Any decrease in grid circuit resistance may cause an increase in frequency, and an increase in the grid resistance due to high-resistance contacts may decrease the frequency. Cleaning the crystal sometimes restores it to its normal frequency of operation. However, do not attempt this yourself. Return it to the repair center. Actual aging of the crystal may cause a change of frequency, which is not correctable except by grinding or plating (at the repair center) to restore the proper thickness. Such aging usually does not occur quickly, but is cumulative over a long period of time. It should be noted that frequency is based upon time and that time is controlled astronomically and does vary in very minute parts. Thus, primary frequency standards are only accurate to 2 or 3 parts per 100 million for short

time operation, but this accuracy decreases as the time interval is lengthened. Therefore, crystal frequencies should not be expected to be absolutely accurate. However, they should be as accurate as their rated tolerance, and should normally require a stable secondary frequency standard to determine their error. Where crystal-controlled receiving and transmitting frequencies are involved, it may sometimes be suspected that either one or the other is in error when, in fact, both could be in error.

ELECTRON-COUPLED CRYSTAL OSCILLATOR (ELECTRON TUBE)

Application.

The electron-coupled crystal oscillator is used almost universally to provide an approximate sine wave rf output over the low-, medium, and high-frequency rf ranges. It utilizes a screen grid or pentode tube to provide extreme stability and greater output than is possible with a basic triode-crystal oscillator, and is widely used in transmitters, receivers, test equipment, and other equipments which require crystal frequency control. Its widest application is for frequency multiplication in the plate circuit.

Characteristics.

Utilizes piezoelectric effect of a natural or synthetic crystal to control frequency of oscillation.

Uses electron coupling to the load to reduce strain on crystal, to minimize load variations, and to provide extra stability.

Normally operates with automatic self-bias and class C, but may be operated with combination fixed and self-bias and class A or B for special design purposes.

Frequency stability is better than frequency stability of triode crystal oscillator, and power output is also greater.

Output waveform is a relatively constant amplitude sine wave, but if output is primary consideration it may be a distorted sine wave.

Uses a tuned plate tank for harmonic operation.

Circuit Analysis.

General. The discussion on the Electron-Coupled LC Oscillator given earlier in this Section is generally applicable to this circuit. The basic crystal-controlled

circuit employs either a Miller or Pierce oscillator which utilizes the screen grid of a tetrode or pentode tube as the anode. Either grounded-cathode or grounded-plate circuits may be used, with the grounded cathode being used mostly with a basic Miller oscillator, and the grounded plate being used mostly with the basic Pierce oscillator. The basic Miller oscillator is usually used for single-frequency operation, and always incorporates a tuned tank circuit. The Pierce oscillator is used where a number of frequencies are to be covered by changing of crystals, with no tuning adjustment being provided; however, plate tuning is required if harmonic operation (frequency multiplication) is desired.

Circuit Operation. A typical electron-coupled Pierce type oscillator is shown schematically in the following illustration. The grounded-plate version of the basic circuit is used to minimize the electrostatic strain on the crystal. The illustration shows a pentode tube rather than a tetrode because better electron coupling, or looser coupling, between load and crystal oscillator is possible because of the effect of the suppressor element. The looser coupling results from the fact that the screen grid completely surrounds the control grid and effectively isolates it from the plate circuit, and from the fact that the suppressor, if grounded or properly biased, minimized capacitance coupling between screen and plate. Thus, the coupling between oscillator and load circuit is provided by the electron stream alone, and any reflected load changes have negligible effects. Although the circuit shown may at first glance appear to be a Miller oscillator, it can be seen that the cathode is effectively above ground and that the oscillator plate (the screen grid) is grounded for ac by capacitor C4; hence, the crystal is connected (as in the typical Pierce circuit) between grid and plate (screen). This type of connection prevents the supply voltage from placing permanent electrostatic strain on the crystal, and is preferred for that reason.


In the schematic, the suppressor is shown grounded through C5, and it is held effectively at zero bias with respect to the plate by its connection to B+ through R2 (an internally connected suppressor type tube should *not* be used in this circuit). Thus, by construction, the grid is effectively shielded from the plate, and the coupling effects of plate-cathode capacitance are therefore reduced. Since the oscillator plate (the screen) is grounded, the RFC is used to keep the cathode above ground for rf. The output is

taken from across plate load resistor R_L through capacitive coupling. Actually, the plate load can be an r-f choke or a tuned LC circuit when the circuit is operating on the fundamental frequency. When it is desired to double or triple the frequency, it is necessary to tune the plate circuit to the desired harmonic, or overtone, for maximum output. Combination fixed-bias (from voltage divider R_1 and R_k) and self-bias (from R_k) is used to stabilize the circuit against frequency changes caused by bias variations because the excitation changes for various crystals and frequencies of operation. Therefore, with a fixed oscillator anode (screen) voltage which is relatively unaffected by load variations caused by supply changes or tuning, plus a stable operating point established by the fixed bias, usually only temperature effects need be considered with evaluating the short-time frequency stability of the circuit. In a typical circuit of this type, changes in resistor values of 20% result in a frequency change of only 1 part per million (ppm), and capacitance changes of up to 10% produce frequency changes of less than 8 ppm, whereas changes in temperature of the crystal and other circuit parts produce frequency changes as high as 35 ppm per degree centigrade above ambient room temperature.

Use of a crystal with a better temperature coefficient and with temperature control can reduce this to a short-time frequency variation of only 2 to 3 ppm.

Electron coupling also affords greater output because the circuit employs the equivalent of two tubes, the triode section operating as a low-voltage oscillator with low grid excitation and low crystal strain, and the pentode section operating as an amplifier loosely coupled to the oscillator by the electron stream between screen and plate. Thus, the amplifier portion may be operated at high voltages, which if used in the basic oscillator would normally shatter the crystal; consequently, the power output from the amplifier plate is greater than that from the basic unit. The over-all result is a stable crystal oscillator operating with crystal excitation on the order of a few milliwatts and providing a power output on the order of watts. In most cases, the output is equal to or greater than the output available from the basic Miller type power oscillator, and has a greater frequency stability.

Now consider one cycle of operation. When $B+$ voltage is applied, the fixed cathode bias produced by voltage divider R_1 and R_k permits a heavy flow of screen and plate current. Since the plate is isolated from the oscillator portion of the circuit by the zero-biased suppressor grid, and is coupled only through the electron stream in the tube, plate current flow has no effect on oscillator operation. Since the grid is located between cathode and screen, electrons will be intercepted from the space current, causing a small grid current to flow. Grid current flow through R_g develops a negative bias on the grid, which tends to charge C_1 . Thus R_g and C_1 act as a grid leak and grid capacitor, respectively. Simultaneously, the crystal is shock-excited into oscillation by the changing grid and screen voltages. The crystal vibrations produce a piezoelectric voltage across the crystal, and between grid and ground (the screen is bypassed by C_4 , and acts as the oscillator anode). The crystal oscillates in synchronism with the grid and plate voltage changes. On the negative swing, the crystal-generated voltage adds to increase the bias and reduce the anode (screen) current. On the positive half-cycle, the total bias is decreased. Consequently, the screen current (and thus the electron stream through the tube from cathode to plate) is caused to alternately decrease and increase at the oscillator frequency. The capacitive voltage divider (C_2 and C_3), connected between grid

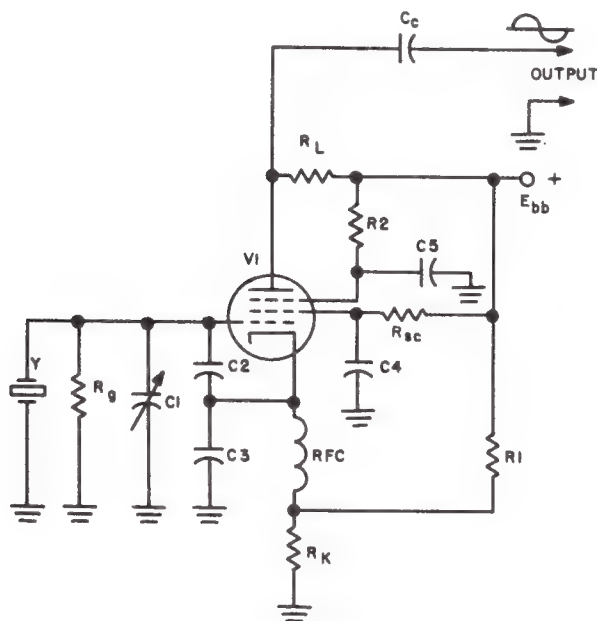


Grounded-Plate Pierce Electron-Coupled Oscillator

and cathode, and plate and cathode, fixes the minimum amount of feedback. Thus it helps stabilize the circuit and overcome any tendency toward hard starting because of the initial fixed cathode bias. The cathode is kept above ground potential by the rfc; otherwise, oscillation would not occur (screen and cathode would be short-circuited for r-f).

The electron stream between screen and plate varies in accordance with the crystal oscillation frequency. Since the plate voltage and current are greater than the screen voltage and current, the r-f output voltage developed across load resistor R_L is larger than the voltage developed across the crystal. Since the plate is isolated from the screen and oscillator section of the tube by the zero suppressor bias, any load variations or supply voltage changes have little or no effect on the oscillator. Thus, a more stable and higher-powered output is taken from the plate circuit of the electron-coupled crystal oscillator. The dc power dissipated in R_L , of course, appears as a loss of efficiency, since it is wasted in heating the resistor.

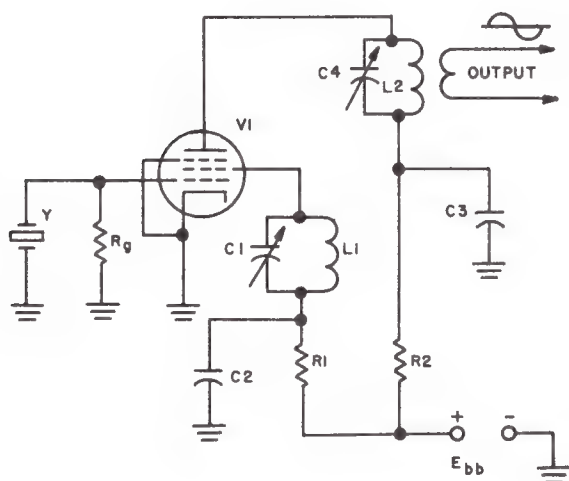The accompanying circuit schematic shows the Miller version of the electron-coupled crystal oscillator. Although this circuit requires two tank circuits, it has the advantage that doubling (or tripling) can be accomplished in the final tank, while the basic stability of the fundamental frequency is retained.



Miller Electron-Coupled Oscillator

Note that in this circuit the cathode is grounded; hence, even though the suppressor is shown externally connected, an internally connected suppressor type of tube could be used without impairing the electron coupling. Actually the second tank circuit ($C4$, $L2$) need not be used; a resistor or RFC could be used in its place, but tuning the plate circuit ensures that the proper output frequency is selected and reduces the harmonic content to a minimum. From the illustration it is evident that the basic oscillator circuit is connected between the cathode, grid, and screen (anode) tube elements, just as in the Pierce electron-coupled oscillator. However, the crystal is connected between grid and cathode, and the operation of the oscillator is as described previously (see Grid-Cathode (Miller) Crystal Oscillator discussion at the beginning of this section of the Handbook). Electrostatic isolation of the plate by means of the grounded suppressor limits the coupling to the electron stream alone, thus providing increased stability because of freedom from the effects of load variations on the oscillator.

Failure Analysis.

No Output. Lack of output from this type of oscillator may be due to a fault in either the oscillator portion or the amplifier portion of the circuit. Thus, it should first be determined whether the crystal oscillator is oscillating, using the failure analysis discussion of the basic oscillator as a guide. If the oscillator is operating, then lack of output is caused by lack of plate voltage due to an open or short-circuited condition. An open suppressor bypass capacitor may cause a virtual cathode to be formed between screen and plate and reduce the output almost completely. A defective electron tube may oscillate, but have insufficient emission to supply any appreciable output in the plate circuit. Usually, the cause of a no output condition can be quickly localized to a particular part by a resistance check of the few components involved.

Reduced Output. This condition is more likely than no output and may be caused by low plate voltage, by the presence of a high resistance in the plate load circuit due to poor connections, particularly in tuned tank circuits, and by excessive bias. Short-circuiting of the cathode bias voltage-dropping resistor connected to the supply source (R_1 in Pierce circuit) would produce cutoff-bias conditions and the

tube would not operate; an increase in this resistance would minimize the fixed bias and allow the cathode bias alone to prevail, causing class A operation of the plate section, so that reduced output and a reduction of harmonic content would occur.

Incorrect Frequency. Since the frequency is determined by crystal operation, any basic frequency changes will occur solely in the oscillator section, except when the circuit employs a plate output tank. If this tank becomes tuned (either accidentally or by component failure) to the wrong harmonic of the crystal frequency, the circuit will produce an output of incorrect frequency. Any changes caused by load fluctuations or supply voltage fluctuations will be so small that they may go unnoticed unless precision measuring equipment is available.

OVERTONE CATHODE-COUPLED (BUTLER) CRYSTAL OSCILLATOR (ELECTRON TUBE)

Application.

The cathode-coupled (Butler) crystal oscillator is used primarily for overtone crystal operation on high or very high radio frequencies. It is used in receivers, transmitters, test equipment, and other equipment which requires the use of a stable crystal-controlled high-frequency oscillator.

Characteristics.

Uses an overtone crystal to provide operation on frequencies which are not integral harmonics of the fundamental crystal frequency.

Employs two triodes coupled by the crystal operating all series resonance.

Normally operates class A, but may be operated class C for greater power output.

Provides an approximate sine-wave output of relatively constant amplitude.

Circuit Analysis.


General. The Butler cathode-coupled two-stage oscillator is one of the most widely used of the *series mode* oscillators because of its simplicity, versatility, frequency stability, and comparatively high reliability. This circuit seems to be the least critical to

design and adjust for operation at a given harmonic with any type crystal. The balanced circuit, plus the fact that twin triodes within a single envelope can be used, contributes to a saving in space and cost and provides for short leads. The cathode-coupled circuit can also be used for operation on the lower radio frequencies, provided that the resistance of the crystal unit is not greater than a few hundred ohms. However, the power output is less than that of the Miller circuit for the same crystal power, and the broad bandwidth of operation without tuning as provided by the Pierce circuit is not possible.

At series resonance, the crystal element appears as a resistance, so that in the normal circuit it can be short-circuited or replaced with a comparable resistor without stopping oscillations. Although circuit operation of the series-mode oscillator is less complicated than that of the parallel-mode oscillator, the circuit design becomes increasingly critical at the high frequencies and higher overtones. It is vitally important to keep stray capacitance at a minimum, and all leads must be as short as possible to eliminate unwanted resonances. It is sometimes necessary to nullify the shunt crystal capacitance by paralleling the crystal with an inductor which is antiresonant with the shunt crystal capacitance at the operating frequency. It may also be desirable to connect a capacitor in series with the crystal to tune out the stray inductance of the crystal leads, and tuned output circuits must be provided to select the proper overtone. For maximum frequency stability, the effective resistance of the circuit facing the crystal unit should be as small as possible. At the higher frequencies, stray capacitances limit the impedances obtainable with tuned circuits, making them more selective, and more effective in influencing the frequency and increasing instability.

Usually, the output is taken from the plate or cathode of either tube. Sometimes the cathode follower is a pentode tube utilizing the cathode, screen, and grid elements as the basic oscillator, which is electron-coupled to the plate load. This provides greater stability and affords the possibility of tuning the plate circuit to a higher harmonic.

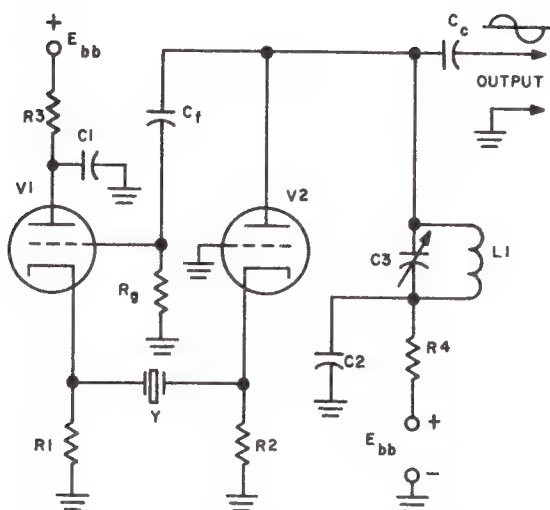Circuit Operation. The accompanying illustration shows the basic cathode-coupled circuit using triodes.



Basic Cathode-Coupled Crystal Oscillator

Tube V2 is a grounded-grid amplifier whose output is fed back to the cathode (input circuit) through cathode follower V1 and the series-connected crystal. Cathode bias is supplied through R1 and R2, and V1 normally conducts more heavily than V2 (both tubes are identical triodes). The feedback voltage is coupled capacitively through C_f to the grid of V1, and grid resistor R_g provides conventional grid-drive bias which varies with the excitation supplied. When operated class A, no grid current is drawn, and there is no grid-drive bias produced across R_g . In this instance R_g acts solely as the grid-return resistor in a conventional R-C coupling network, and the bias is produced by R1 alone. In class C operation, grid current is drawn, and grid drive bias is produced exactly as in the conventional r-f driven amplifier. In this case, the total bias consists of the self-bias produced through cathode resistor R1, plus the drive bias in the grid circuit. The tuned tank circuit (L_1 and C_3) in the plate of V2 offers maximum impedance at the frequency to which it is tuned. The maximum output voltage (and feedback) occurs at this point, neglecting crystal operation. The crystal is normally an overtone type, and is ground for maximum activity at the overtone frequency (fundamental frequency crystals are occasionally used with this circuit, but this fact does not materially affect the theory of operation of the circuit). Usually the circuit will oscillate when the

crystal is short-circuited or replaced with an equivalent resistance, operating at the frequency of the tank circuit. Resistor R4 and capacitor C2 are a conventional plate voltage dropping and decoupling network provided for series plate feed of V2. Resistor R3 and C1 perform a similar function for V1 with sufficient capacitance to effectively ground the plate of V1 for rf at the frequency of operation. The output is taken from the plate of V2 through coupling capacitor C_c , but it could also be taken from V1 or from the cathode without materially changing operation.

Off resonance, the crystal exhibits a high resistance, which effectively reduces the feedback and prevents oscillation. At the series resonant frequency, the crystal exhibits a low resistance and the circuit oscillates vigorously. Since the gain of the cathode follower tube cannot exceed unity, there is partial control of excitation because V1 cannot amplify the feedback from V2; as a result, greater feedback is provided for a weak crystal than for a strong crystal. This action enhances overtone operation, since the strongest oscillations are at the fundamental frequency, with successively weaker oscillations being obtained as the numerical value of the overtone increases.

Now consider one cycle of operation. When plate voltage is applied to V1 and V2, since no initial bias exists there is a heavy flow of plate current. The flow of plate current through R1 and R2 produces a cathode bias on each tube which reduces the plate current flow. At the same time, the flow of plate current in V1 through plate resistor R3 drops the supply voltage to the proper value. Any a-c variations in voltage produced by changing plate current through R3 are bypassed to ground by C1, and tube V1 operates as a cathode follower. The initial flow of current shock-excites the crystal so that it vibrates at its series-resonant frequency. At resonance the crystal appears as a low value of resistance, while on either side of resonance it appears as a large resistance. In the off-resonance, high-resistance state, the crystal attenuates any feedback from the plate of V2 through V1 and thus prevents oscillation. In the series-resonant state, the low crystal resistance permits practically all the feedback to be applied across R2. (The crystal resistance, R, and the cathode bias resistor, R2, form a voltage divider connected in parallel with R1.)


With the crystal oscillating on the positive half-cycle, assume that a positive voltage produced by

piezoelectric effect is applied to R2, and increases the bias. The plate current of V2, therefore, is reduced. Since the output voltage is developed across the impedance of the plate tank circuit, a reduction in plate current produces less drop across the tank, and the plate voltage approaches the source (goes positive). Thus, a positive-going voltage is fed through coupling capacitor C_f to the grid of V1. The positive-swinging grid voltage produces an increase of plate current in V1 and a positive increase across cathode bias resistor R1. Since the gain through cathode follower V1 is less than unity, no amplification of the signal occurs through V1. Sufficient feedback occurs, however, to replace the small circuit losses; thus oscillation is sustained.

On the negative half-cycle of operation the crystal develops a negative voltage which is applied to R2. The bias on V2 is thus reduced, and the plate current increases. The output voltage produced across the tank circuit is now negative-going, and is fed back to the grid of V1 to reduce plate current flow. Consequently, the voltage drop across cathode resistor R1 is decreased, and a negative-going voltage is applied through the crystal to maintain oscillation.

Although it might appear that the feedback voltage is such as to oppose crystal oscillation, it must be realized that this circuit will operate with the crystal removed if the equivalent resistance (or an ohmic connection) is placed across the crystal terminals. Operation without the crystal, however, is never as stable as with the crystal.

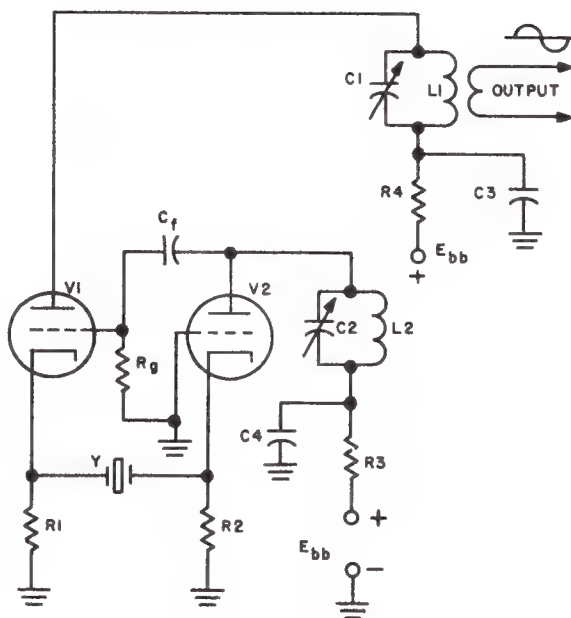Circuit Modifications. As with all other oscillator circuits, there are numerous variations of the basic circuit. A typical variation is shown in the accompanying illustration.




Frequency Multiplying Overtone Oscillator

This circuit is essentially identical with the basic Butler overtone oscillator, except for the insertion of a tuned tank in the plate circuit of the cathode follower. Thus, the cathode follower stage becomes a cathode-coupled stage. The effect on over-all operation is to make available an output which can be tuned to a harmonic of the overtone frequency (instead of being bypassed to ground as in the basic circuit) and provide effective frequency multiplication.

As far as the basic oscillator is concerned, the operation is the same as described for the basic circuit. Although amplification occurs in the plate circuit, since the plate load of V1 is tuned to a different frequency, any coupling effects through the plate-grid capacitance do not affect the basic frequency.

An electron-coupled version is formed by connecting V1 as a conventional pentode amplifier which is resistance-capacitance coupled to V2, with the frequency multiplying tank in the plate circuit of V1, shown in the following illustration. This version is identical with the basic Butler circuit except that the screen of V1 acts as the anode of the cathode-follower stage. With the screen ac grounded through C2 and the suppressor tied back to the cathode, the plate is coupled solely through the electron stream between screen and plate. The rfc and C3 form a conventional series plate feed decoupling network, and R_{sc} is the screen resistor. All other components function as in the basic oscillator. In this circuit V1 is usually operated class C, and has a high applied plate voltage. Thus, the plate output is considerably higher than in the previous triode type of frequency-multiplying circuit, and the tank L_1 and C_1 may be tuned to either the second or third harmonic of the oscillator frequency. The basic tank C_4L_2 is tuned to the fundamental frequency.

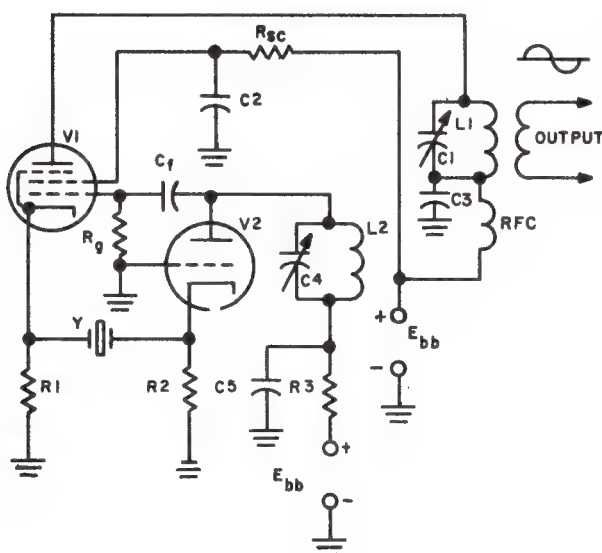

Electron-Coupled Overtone Oscillator

Although other versions of the Butler circuit exist, they are similar to the versions described above. The identifying feature of the Butler oscillator is the connection of the crystal as a series feedback arm between two cathode-coupled stages. Overtone oscillators with grid-cathode or grid-plate connected crystals are special versions of the Miller and Pierce circuits.

Failure Analysis.

No Output. A primary cause of inoperation is a defective crystal or poor holder connections; the crystal and holder resistance should not exceed 500 ohms for proper operation. Since two tubes are involved, a defective tube is also a possible cause of no output. An open circuit in the feedback path, either in the coupling capacitor or crystal holder, will also stop operation. In addition, short-circuited components will cause the affected tube to draw greater than normal current and stop oscillation. A short circuit across the crystal will not stop oscillation; depending on the design, it is possible for oscillation to continue at the tank frequency. Lack of supply voltage will also stop operation, but low supply voltage will primarily affect only the output amplitude. Because of the few components involved, a quick voltage and resistance check should isolate the defective part. If all parts and voltages appear normal, the cause of trouble is in the crystal, or the tank tuning capacitor is shorted or tuned to the wrong frequency. If other crystals oscillate in the circuit, cleaning the defective crystal may restore activity. (Return crystal to repair activity for cleaning.)

Low or Unstable Output. Excessive bias on one or both tubes will reduce the output. Such bias could be caused by heavy current through the cathode bias resistors due to defective tubes or short-circuited components in the plate circuits. A change in the grid-leak resistor and in the coupling capacitor constants may cause blocking and motorboating or intermittent operation. A weak or dirty crystal may also produce low output. (Replace the crystal.) Too low or too high a plate voltage can cause instability.

Incorrect Frequency. The series-resonant crystal oscillator is the most stable kind. Therefore, a change in frequency will probably be due to crystal caused effects. Cleaning the crystal should restore proper operation (cleaning to be done only at repair activity); if not, there is a possibility that changes in stray capacitance between cathode and ground (perhaps

from a change of lead dress) have caused a slight detuning. Though operation at a frequency above the series frequency can occur, it is rather unlikely because the limits of series resonance do not permit as much detuning as those of parallel resonance.

OVERTONE CRYSTAL OSCILLATOR (SEMICONDUCTOR)

Application.

The overtone type oscillator is used as an oscillator in receivers, converters, frequency synthesizers, and test equipment, and as an exciter in low-power transmitters. Its use is restricted to the high-frequency ranges (above 20 mc) where fundamental mode crystal operation is not practicable.

Characteristics.

Uses piezoelectric effect of a quartz crystal operating on an odd overtone to provide stable high-frequency oscillations.

Has at least one tuned circuit at overtone frequency and may have two; it is never untuned.

Operates class C to help produce harmonic operation.

Regenerative feedback is usually provided through a tapped coil (Hartley principle).

Always operates as a crystal-controlled oscillator to avoid spurious frequencies.

Circuit Analysis.

General. Overtone circuits are basically of two types: one type uses a crystal which is ground for fundamental frequency operation, and the other uses an overtone ground crystal. Since the circuits that use overtone crystals are usually designed for specific types of crystals, this discussion will be restricted to circuits which can use either type of crystal.


Basically, the overtone crystal oscillator uses an inductive form of feedback, but it is not necessarily limited to that type. It just happens that at the present state of the art the inductive type is more popular. Although the tapped coil is primarily a Hartley feedback arrangement, it is closely similar to the tickler coil feedback arrangement. At the frequencies used, the tighter coupling of the Hartley arrangement and the ease of construction make it a more natural choice.

For operation of an overtone circuit, regenerative feedback must be provided to assist in the starting of

oscillations, but the feedback must not be strong enough to cause free-running oscillations. Most circuits of this type are first designed to operate as free-running oscillators, and the amount of feedback is then reduced by the manufacturer until only the crystal controls the oscillation. Oscillation is usually vigorous, and the output at the third and fifth overtones (using a fundamental crystal) is almost as large as that at the fundamental; at higher overtones, the output falls off quickly. The output depends so much upon the processing and manufacture of the crystal, however, that the highest overtone at which practical operation is possible is rather indefinite. Designers have produced satisfactory outputs on overtones above the 11th, but mostly with patented circuits and special components. In the transistor crystal oscillator, for example, overtone operation has been improved by the use of special transistors designed to minimize phase shift at very high frequencies. When this type of transistor is combined with an overtone crystal or a specially processed crystal, the results equal or surpass similar electron-circuit tube achievements, but the power output is less.


Circuit Operation. A simplified schematic of the basic overtone semiconductor oscillator, using the common-emitter configuration, is shown in the accompanying illustration. It can be seen at a glance that this is the basic Hartley Oscillator circuit with a crystal in series with the emitter feedback connection. For simplicity, bias and supply arrangements are not shown. It is assumed that the collector is reverse-biased and the base forward-biased, and that PNP junction transistors are used. The crystal can be either a fundamental or an overtone type. The tank circuit, consisting of L and C, is tuned to the overtone frequency desired. The principle of operation is exactly the same as the principle of operation of the basic Hartley oscillator, with proper polarity of feedback between the oppositely polarized collector and base being obtained by means of the tapped-coil arrangement. The difference in operation is primarily in the amount of feedback, with the portion of the coil between emitter and base producing just enough feedback for easy starting with the crystal in place. In the self-excited Hartley, the tap on the inductor is normally at or near the center of the coil, the number of turns between emitter and base being selected for strong and stable feedback. In the overtone oscillator the feedback coil usually consists of a few turns (no more than 3 or 4), approximately 10% of the total

number of tank coil turns. This corresponds very closely to the tickler coil oscillator arrangement used in regenerative receivers, where it is possible to just produce oscillation with the regeneration control all the way on. The overtone oscillator regeneration, however, is adjusted so that the circuit will not quite oscillate with the crystal out of the circuit, but will produce, strong stable oscillation at the crystal frequency only (no spurious self-oscillation) with the crystal in the circuit.

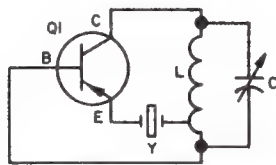

Simplified Overtone Circuit

A typical overtone circuit with bias and supply connections is shown in the accompanying figure. The common-emitter circuit is used, and the crystal is in series with the feedback loop as in the basic schematic. Voltage divider bias is obtained through R_1 and R_B , and the base resistor is bypassed for rf by C_B . An unbypassed emitter swamping resistor (R_E) is used for stabilization. Actually, at the high frequencies used, it is probable that the distributed capacitance (shown in dotted lines in the schematic) across R_E and the resistor itself form a grid-leak bias arrangement for amplitude control, and that some designs may use a bypassed emitter. In the circuit shown, the collector supply is bypassed by C_2 , with the RFC connected in series between the negative collector supply terminal and L_1 , as a conventional series-feed arrangement.

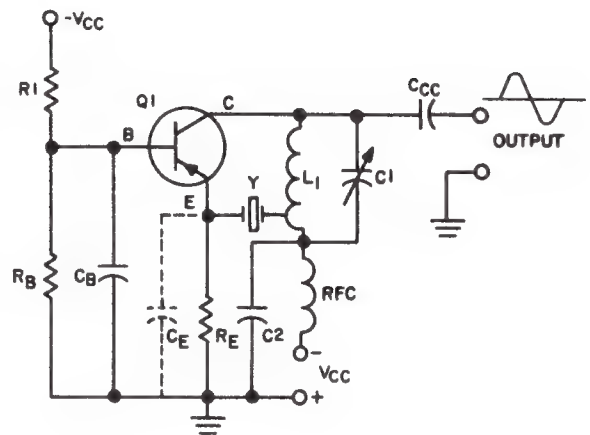

Overtone Crystal Oscillator


Now consider one cycle of operation. When collector voltage is applied, bias divider R_1 R_B supplies class A bias to the base, and collector current flows as in a conventional amplifier circuit. Assume that a noise pulse causes the collector current to increase and that a voltage is developed across the tank circuit ($L_1 C_1$), which offers a high impedance at the resonant frequency. The voltage developed across the tank is positive with respect to the supply end. The crystal offers a low-impedance path to the emitter at series resonance. With the crystal connected near the supply end, that electrode is negative, and the electrode connected to the emitter is positive. Therefore, a voltage exists across the crystal, causing it to deform in one direction. The base of the transistor is connected for rf through C_B and C_2 to the supply end of the tank coil. Thus the tank is essentially connected between collector and base, with the emitter

tapped to the tank. This is equivalent to a typical Hartley-type of grounded-base feedback oscillator, which is effective only for the series-resonant frequency of the crystal. On either side of resonance the increasing crystal impedance quickly stops any feedback, and the circuit will not oscillate.

As the noise pulse causes the collector current to increase, the feedback to the emitter is positive and the base end of the coil becomes more negative. Both the more negative base and the more positive emitter cause an increase in forward bias and a greater I_C . The collector current increases until the supply voltage bottoms (cannot go any lower). During this time the tank capacitor, C_1 , is charging. The tank circuit now discharges and the polarity of the base and emitter feedback voltages change to produce a reduced forward bias and a lowering of I_C . This causes the collector voltage to rise toward the supply voltage and become more negative. At the same time, since the polarity across the crystal changes, the crystal flexes in the opposite direction as a result of piezoelectric action. This state of operation continues until the collector current cutoff point is reached; at this time a small flow of I_{CEO} (reverse current) occurs, but it has no effect on operation other than to cause a lowering of efficiency. When the feedback ceases, the crystal flexes back toward its original resting condition and generates a piezoelectric charge that starts collector current flowing again, and the cycle repeats. Emitter resistor R_E is affected only by the dc current flow, and operates as a simple swamping resistor for thermal compensation and stabilization. In some circuits the distributed capacitance across R_E is considered to cause it to operate in a manner similar to that of the electron-tube grid leak. That is, the charge across this capacitance holds the circuit inoperative until the charge leaks off; too large a capacitance will effectively short the crystal. The capacitance is shown in dotted lines in the above illustration because it is not considered necessary for operation. The output is taken capacitively through C_{cc} between collector and ground, or, if desired, by inductive coupling to the tank circuit. The tank circuit is tuned to the overtone

frequency, and the crystal also operates at the overtone frequency.

Circuit Variations. A typical practical operating design used in a satellite transmitter is shown in the following figure. The grounded-base arrangement is employed. The tank circuit is connected between base and collector, and the emitter is connected to the tap on the tank coil through the series crystal and capacitor C_4 . Separate bias supplies are shown because their use provides almost perfect stabilization; however, voltage divider bias can be used if only one supply is available. RFC1, in the emitter circuit, is used to keep the emitter above ground, and R_E , which is bypassed by C_1 , provides emitter swamping (and also controls output). Forward bias is applied between the emitter and base by battery supply V_{EE} . Conventional series collector feed is provided through RFC2, which is bypassed for rf by C_6 . The output is taken capacitively from the collector through C_7 , which is adjustable to match of 50-ohm load. Capacitor C_3 is a base blocking and coupling capacitor (it also affords a reduced tuning range for C_2); it connects the base to the tank circuit for rf and isolates it from the dc collector supply; otherwise, the supply would be short-circuited. Capacitor C_5 is a trimmer across the tank, and variable capacitor C_2 is the tank tuning capacitor. Feedback is obtained from the tap on L_2 , and applied through C_4 and the series crystal to the emitter. In this circuit, C_4 adjusts the phasing to ensure feedback of the proper polarity and to compensate for the phase lag in the transistor at high frequencies. It acts as a variable regeneration control to permit the use of various types of crystals and replacement transistors. Inductor L_1 is used to resonate out the effects of excessive crystal holder shunt capacitance at the frequency of operation. At the series resonant overtone the crystal offers minimum impedance and supplies maximum feedback from collector to emitter. Although the emitter and collector are of the same polarity, or phase, L_2 and C_4 provide the necessary phase rotation to insure oscillation, since the feedback is taken from the end of the tank coil opposite the collector.

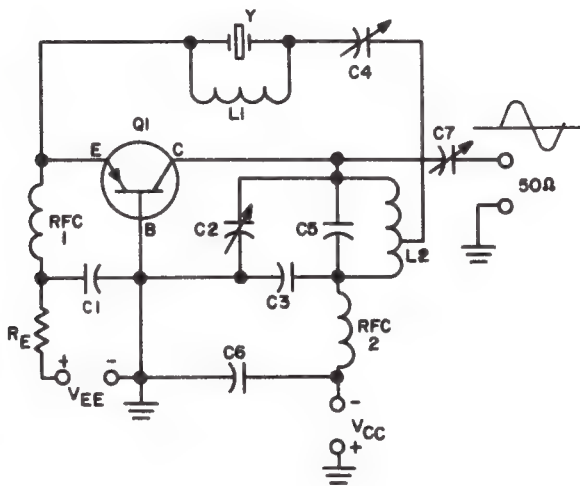

Grounded-Base Overtone Oscillator

Now consider one cycle of operation. When voltage is applied, the fixed bias, which is less than cut-off, permits collector current to flow. Assume a noise pulse which causes an increased I_C . Since the tank is connected between collector and base, with the emitter tapped onto the coil, it is basically a Hartley-type oscillator. In this circuit L_2 acts as an autoformer, with the emitter-base turns coupled to the emitter-collector turns. However, the emitter is not directly connected to the coil; it is connected through crystal Y and capacitor C_4 in series. The capacitor offers only a small capacitive reactance to the oscillator frequency; the crystal offers a high impedance off-frequency, and a low impedance at its series-resonant frequency. Thus, feedback is permitted at the series-resonant frequency, but is stopped on either side of resonance.

The increased collector current induces a feedback pulse in the emitter-base portion of L2 in a direction which increases the forward bias, and, hence, the collector current. Capacitor C4 provides a phase-delay adjustment which can reduce the amount of feedback (or increase it, as desired) so that various types of crystals and transistors may be used. For the purpose of this discussion it can be considered as short-circuited, since it is only a production type or compensator, and is not necessary to basic operation. Since the feedback action is regenerative, the collector current continues to increase until the collector saturates and no further change can occur. At this

time the crystal, which was initially deformed by the feedback potential between the emitter and collector, flexes in the opposite direction. The polarity across the crystal produced by piezoelectric action also reverses, and the flow of emitter current is reduced; since the collector current is also reduced, and the feedback is regenerative, the collector is driven to cutoff. At this time a small I_{CEO} (reverse current) flows, but it has no effect on operation except to lower the over-all efficiency. At this time C1, which was charging during the conduction period, now discharges through R_E . When the bias drops below cutoff, current again flows and the cycle repeats. During the reducing collector current period, the crystal is flexed in a direction opposite the initially caused deformation, and at cutoff it again flexes oppositely and resumes its original shape. Thus, the crystal is caused to oscillate, and in oscillating it provides a low-impedance path for the feedback. Because of its inherent stability, the crystal controls the frequency by permitting operation to occur at only one frequency. The basic tank circuit (L2, C2) functions in the conventional manner to supply energy during the non-conducting half-cycle, so that the negative output alternation may be completed. This flywheel effect provides a sine-wave output through coupling capacitor C7, instead of the distorted pulse which otherwise would occur.

The circuit described above is capable of providing an output of 15 to 30 milliwatts at an efficiency of 30 to 35% to a 50-ohm load, and a maximum output of 100 milliwatts at an efficiency of 40 to 45%. Under constant loading and controlled temperature, the short time frequency stability is plus or minus one part in one hundred million. The circuit uses a fifth overtone crystal operating on 108 MHz and a diffused base transistor.

Failure Analysis.

No Output. Loss of output will result from the loss of bias or supply voltage due to an open- or short-circuited component; this condition is easily determined by checking for the presence of voltage. An incorrectly tuned tank circuit will prevent the crystal from operating and could result from shorted turns or a shorted tuning capacitor, but at low voltages used, troubles of this kind are rather unlikely with ordinary components. In miniaturized circuits where the current-carrying capacity is low, there is the possibility that an overload can cause the induc-

tor or leads to open. It is important, therefore, to use a meter having a very low full-scale current requirement, preferably in the microampere region. A VTVM is preferable to the standard 20,000-ohms-per-volt meter, although with care both can be used interchangeably. A check of the forward and reverse resistances of the transistor will quickly determine whether it is at fault. Because of the low potentials involved, a high resistance or poor soldered joint can introduce excessive resistance and stop the circuit from oscillating. A defective, partially fractured, or dirty crystal can also prevent oscillation.

Reduced Output. Since the output amplitude is primarily controlled by the emitter swamping resistor and bias voltage, changes in these parameters can cause reduced output. Opening of the bias ground return resistor will place a higher bias voltage on the transistor, and, depending upon the internal base-to-emitter resistance of the transistor, oscillations may be blocked entirely or hard starting may result. Hard starting is usually a clear indication of a dirty or defective crystal. The value of the emitter resistance and its bypass capacitor will determine the output amplitude to a great extent; therefore, a partially shorted capacitor or increased resistance in the emitter circuit will reduce the amplitude. Such troubles can be easily located by making a resistance check of the few components in the circuit. A reduction of output may also be caused by short circuiting of the transistor elements or by mismatching of the transistor due to a change in the circuit values. This too is easily checked by making a resistance analysis and by measuring the forward and reverse resistances of the transistor. A combination of low forward resistance and high reverse resistance indicates a satisfactory transistor. If the forward resistance is high or nearly the same value as the reverse resistance, the transistor is defective. If both resistances are zero, the transistor is short-circuited.

Incorrect Frequency. Since the crystal is the frequency-determining component, an appreciable change in frequency indicates a defect or a change in the crystal, except where the tuned circuit is actually tuned to another overtone. Under normal conditions it is practically impossible to tune the tank to resonance at a different overtone unless the tank circuit components are defective. Although a fundamental type crystal will operate within the tolerances marked on the holder, it must be kept in mind that for overtone generation of the crystal the tolerances will be

multiplied by the overtone number (1, 2, 3, etc); hence, the tolerance range at the overtone will be much larger. Oscillation will occur, not over the entire range of tolerances, but at a specific frequency within the range. On the other hand, overtone crystals are rated for their actual tolerance at the overtone frequency; therefore, operation outside this range indicates a defective crystal or spurious oscillations. As a result of changes in circuit components and transistor parameters with age, excessive feedback may occur at certain resonant frequencies and produce free-running oscillations. Usually these signals have a much rougher or more raspy sound and are less stable than the controlled oscillations. In the case where calibration capacitors or feedback controls are provided, it is normal for them to control the frequency slightly so as to permit the crystal to be operated on its exact frequency. When no controls are provided, a change in ambient temperature can place the crystal in another class of temperature compensation and change the actual overtone frequency. The temperature tolerance is shown on the crystal holder and is standard for a MIL type crystal. Minute imperfections or partial fractures can also cause the crystal to operate at another frequency. Return defective or dirty crystals to the crystal repair activity for servicing.

TICKER COIL FEEDBACK CRYSTAL OSCILLATOR (SEMICONDUCTOR)

Application.

This oscillator is used to provide an approximate sine-wave r-f output that is extremely stable under crystal control, and operable over the low-, medium-, and high-frequency r-f ranges. It is universally used where a transistor oscillator is required; typical applications are local oscillators in receivers and heterodyne converters and oscillators in test equipment.

Characteristics.

Uses piezoelectric effect of a quartz crystal to control oscillator frequency.

Uses a feedback (tickler) coil to provide the proper phasing for oscillation and control of regeneration.

Usually has the primary coil tuned to the crystal fundamental frequency, with the secondary (tickler) coil being untuned. Not restricted to a particular configuration; may be CE, CB, or CC as desired.

Can operate on a fundamental, harmonic, or overtone frequency if proper tuned circuit and crystal are selected.

Circuit Analysis.


General. The semiconductor tickler coil crystal oscillator is basically a transformer-coupled oscillator. It may be either tuned or untuned, or partially tuned by stray and distributed capacitance. When the circuit is tuned, it is possible to operate the crystal on a fundamental frequency and tune the tank circuit to a harmonic, thus obtaining frequency multiplication, or to use overtone crystals for the same result. Like the electron-tube crystal oscillator, it may be crystal-stabilized or crystal-controlled. However, this circuit discussion will be restricted to the crystal-controlled type of oscillator. The ease of obtaining the feedback and controlling it makes the tickler coil feedback circuit popular. Since the polarity of each coil with respect to the other is easily changed by reversing the windings (at the time of manufacture), and since the coupling may be made tight by spacing the coils close together, or loose by spacing them apart, it is easy to obtain the proper amount and polarity (or phasing) of feedback. With the use of inductors to provide a low dc resistance, the dc resistance losses are minimized, and more output is obtained from the circuit with better efficiency. Since the transistor requires a certain amount of stabilization against bias and temperature changes, it is usually necessary to add stabilization resistors or reactances.

The use of a crystal operating in the series-resonant mode is more common with transistor oscillators because the crystal serves as a convenient means of permitting feedback at the resonant frequency by virtue of its low impedance series resonant circuit, but offers a high impedance to feedback at all other frequencies. When placed in series with the feedback loop, the crystal effectively controls the feedback. Use of the parallel-resonant mode is not obviated, however, since sufficient flexibility exists in the placement of the crystal in either the collector, base, or emitter circuit to match circuit conditions. For example, since the common-base circuit has a high output impedance, the crystal could be placed in the collector-to-base (or ground) loop and operated effectively as a parallel resonator. Actually, the possibility of three different basic circuit configurations,

together with placement of the crystal in either the input or output circuits, poses a problem in the circuit discussion because of the numerous circuit variations that can be formed. The discussion will, therefore, be limited to a typical circuit considered most likely to represent present day use. It is assumed that placement of the crystal or choice of circuit configuration does not materially change the basic stability, but that it does affect the power output and efficiency of operation to some extent.

Since the crystal power oscillator practically does not exist in the semiconductor field (most outputs are on the order of milliwatts), the crystal is not restricted in its placement by power requirements or heat dissipation, but it may be placed so as to produce the best performance.

Circuit Operation. The basic common-emitter circuit configuration for the tickler coil crystal oscillator is shown in the accompanying illustration. For the sake of simplicity, bias and collector supply voltages are not shown and will be discussed later. It is assumed that forward bias is applied to the emitter-base junction and that reverse bias is applied to the collector junction. The discussion is based upon the use of PNP junction transistors, although the basic principles also apply to point-contact transistors. From the discussion of basic transistor operation in the Amplifier Section of this Handbook, it will be recalled that the inputs and outputs of the common-collector and common-base circuits are of the same polarity, or in-phase, and that those of the common-emitter circuit are oppositely polarized, or out-of-phase. Thus, to obtain the desired polarity (phase) of feedback in the common-emitter circuit, the two coils are oppositely phased. In the illustration the feedback is from collector to base, with the input being considered from base to emitter. Since the polarity is reversed in the transistor collector circuit, the tickler coil, L₂, is connected so that it also reversed the polarity, and feedback through the crystal (series-mode operation) arrives at the base properly polarized (or phased) to produce regeneration. Removal of the crystal, which is in series with the feedback loop, will prevent the occurrence of feedback; therefore, the circuit will not oscillate with the crystal removed. However, the circuit is normally designed to operate as a self-excited oscillator with the crystal short-circuited.

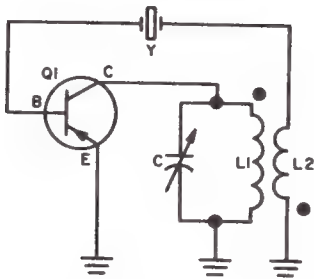

**Basic Tickler Coil Crystal Oscillator,
Common-Emitter Circuit**

The operation of the circuit is similar to the operation of the electron-tube Tickler Coil LC Oscillator described earlier in this section. When the oscillator is switched on, current flows through the transistor as determined by the biasing circuit. Initial noise or thermal variations (initial current) produce a feedback voltage from collector to base through the crystal which is in-phase with the initial noise pulse. Thus, as the emitter current increases, the collector current also increases, and additional feedback through L_1 and L_2 further increases the emitter current, until it reaches saturation (or the collector voltage bottoms) and can no longer increase. When the current stops changing, the induced feedback voltage is reduced until there is no longer any voltage fed back into the base-emitter circuit. At this time, the collapsing field around the tank and tickler coils induces a reverse voltage into the base-emitter circuit which causes a decrease in the emitter current, and hence a decrease in the collector current. The decreasing current then induces a reverse voltage into the feedback loop, driving the emitter current to zero or cutoff. At this time a small reverse saturation current (I_{CEO}) flows, representing a loss of efficiency, but having no other effect on circuit operation. The discharge of tank capacitor C through L_1 then causes the voltage applied to the base-emitter circuit to rise from a reverse-bias value through zero to a forward-bias value. Emitter and collector currents flow, and the previous action repeats itself, resulting in sustained oscillations.

While this oscillatory action is going on, piezoelectric action occurs in the crystal; that is, as the feedback voltage is increased, the strain on the crystal is increased with maximum strain (and maximum crystal deformation) occurring at the peak of the


cycle. Upon reversal of the feedback voltage the strain on the crystal is reduced; since the crystal is now changing shape back to its original form, a piezoelectric charge (potential) is produced across the crystal. This charge is opposite to that which produced the deformation of the crystal. For example, if the original charge which caused the deformation was positive, the crystal causes a negative potential to appear across itself when the strain is released. This potential is in the direction of the feedback (decreasing) so that alternate positive and negative charges are induced across the crystal as it vibrates. These potentials add to the feedback voltage; as a result, the crystal enhances the feedback, and the feedback increases the strength of the mechanical vibrations.

Since the feedback and piezoelectric action are regenerative the transistor quickly reaches its saturation and cutoff points. By correctly proportioning the turns and coupling between the tank circuit and the tickler coil, it is easy to obtain the proper amount of feedback, although with the low potentials involved there is no danger of fracturing the crystal as in the vacuum-tube oscillator. The amount of feedback is adjusted to produce maximum stability. The crystal current is not nearly as great as the crystal current in an electron-tube circuit; in fact, the total transistor collector current is usually less (depending on the type of transistor) than the electron-tube crystal current.

Although the collector-emitter capacitance of the transistor is in parallel with the tank circuit, the use of a low L/C ratio (high- C) produces effective capacitance swamping so that variations in the collector supply voltage, which produce a change in this capacitance, have a minimal effect. For good stabilization, a Zener diode placed across the supply provides excellent regulation. By careful design, the short time stability of the semiconductor crystal oscillator can be made as high as 2 or 3 parts in ten million, which is better than the stability of the equivalent electron tube oscillator. The power output is, of course, very small; however, this fact increases the stability since any change of output load or tuning results in a smaller over-all change. Thus, the frequency stability of the circuit is less affected by load changes than that of the electron-tube (triode) circuit. The output may be taken from the emitter or collector, or even the base circuit, by means of either capacitive or inductive coupling.

The circuit operates at the natural or fundamental frequency of the crystal for the series mode; hence, the operating frequency is slightly lower than the tank resonant frequency. It is also possible to operate this circuit using the parallel mode (antiresonant operation) of the crystal by proper choice of circuit parameters. Although the crystal offers a high impedance at the antiresonant frequency, sufficient feedback can be obtained to sustain oscillation in this mode. In this case, the crystal appears as a high-Q inductor which is tuned by the total shunt capacitance (self, stray, and distributed) across it, and the tank is tuned to a higher frequency. This type of operation is particularly applicable to the higher frequencies, where the shunt crystal capacitance is appreciable. For operation in the parallel mode, the frequency stability is slightly degraded and the output is slightly less than the output in the series mode. Both types of operation are in use.

Bias and Stabilization. In practical circuits, bias and stabilization are usually combined. Bias is usually provided by a fixed voltage divider (R_1 and R_B), as shown in the accompanying illustration of a typical tickler coil crystal oscillator. Note that the base in this case is not bypassed for rf, although in some circuits it may be. When it is unbypassed, there is presumed to be a slight amount of degeneration, which enhances the circuit stability.

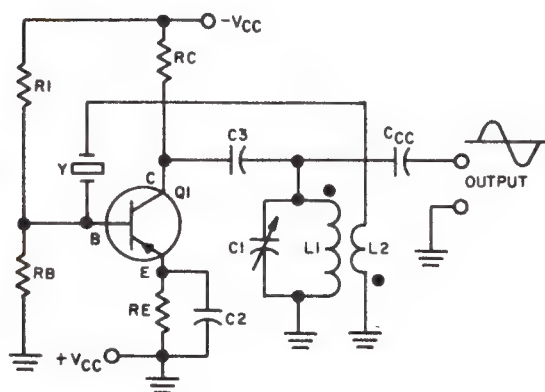

Tickler Coil Tuned Collector Crystal Oscillator

Collector resistor R_C serves two purposes, to drop the collector voltage and to provide resistance stabilization. If the dc losses are serious, the resistor can sometimes be replaced by an r-f choke. Emitter resis-

tor R_E , which is bypassed by capacitor C_2 , provides the major stabilization by emitter swamping action, as explained in the Amplifier Section of this handbook. The tank circuit consists of L_1 tuned by C_1 , with tickler coil L_2 untuned, and is coupled to the collector through C_3 in a shunt-feed arrangement. The crystal is in series with the feedback circuit with the tickler coil polarized so as to produce regenerative feedback. In similar circuits of this type using the tuned base configuration, the crystal is connected directly between base and collector, and the tank between base and ground. In this case, the operation is identical to the operation of the circuit described above; however, the feedback is basically controlled by the capacitance between base and collector, thus making the circuit more suitable for the parallel mode of operation.

Taking the output across the tank through capacitor C_{CC} effectively places the load across the tank and reduces the operating Q, but provides a good waveform because of the smoothing action of the tank circuit. Without the tank circuit, since the oscillations consist essentially of clipped pulses, the waveform would be quite distorted unless the circuit were operated with class A bias. The class of operation is usually class C, with the emitter resistor and capacitor R_E C_2) acting similar to a grid leak in tube oscillators. In the circuit shown, the initial bias is class A for easy starting, with the operating bias being determined by the values of the emitter RC circuit. With large values of capacitance for C_2 fixed bias alone is provided, but as the capacitance is reduced to a small value the self-bias developed across R_E increases.

Failure Analysis.

No Output. In addition to failure of the transistor, no collector voltage or excessive bias can cause a no-output condition. Transistor failure is not very likely under normal conditions, and the transistor should be replaced only after all other checks have been made. Lack of collector voltage can occur because of opening of the series collector resistor or short-circuiting of the tank coupling capacitor, which provides a path to ground through the tank inductor. An open emitter resistor will also cause lack of output. A short-circuited coupling capacitor will place the output load directly across the tank and could change the resonant frequency sufficiently to prevent feedback at the crystal frequency, and stop oscillation.

Reduced Output. Although aging of the crystal may cause a change in the resonant frequency, it is more likely to cause a drop in output as the crystal becomes less active. This condition usually results in a gradual change over a long period of time and is most easily determined by comparison with a known good crystal operating in the same circuit. A change in bias conditions or in the emitter RC network will probably reduce the output because of the amplitude regulating effects of these components. This condition could be caused by an increase in emitter resistance value or by a reduction in capacitance of the emitter bypass capacitor. These conditions are most likely to occur in miniaturized circuits where new component fabrication techniques have not been perfected. If a resistance analysis shows all circuit values normal, there is a possibility that the crystal is dirty and requires cleaning; however, this condition is not very likely to occur in sealed holders, and certainly will not occur in evacuated holders. Do not attempt to clean the crystal yourself. Return it to the crystal laboratory for servicing.

Incorrect or Unstable Frequency. Placement of the equipment so that it is subjected to a change in ambient temperature will cause a change in frequency if the change is not within the range of the temperature characteristic for which the crystal is cut. Likewise, small capacitance changes in the crystal circuit (particularly when the crystal is operated in the parallel resonant mode) will cause slight changes in frequency. Detuning of the tank circuit, if sufficient, may cause the crystal to pop in and out of oscillation with a slight change in frequency. Voltage variations will produce a change in the collector capacitance and cause a slight change in the operating frequency. At very low audio frequencies or at high frequencies near $f_{\max}$, phase shift within the transistor caused by transit time effects may produce instabilities (such trouble is not encountered in properly designed circuits). In the crystal-stabilized circuit (which is not used in the Navy), changes in component values may cause oscillation at undesired frequencies outside the range of the crystal, but in the crystal-controlled circuit they cannot cause this effect because the circuit can oscillate only over a very narrow range about the resonant frequency or at an overtone. This can easily be determined by observing whether the circuit oscillates with the crystal removed. If the crystal is short-circuited, it is possible in the series mode of operation for the circuit to oscillate at the tank frequency, but

not in the parallel mode of operation. Frequency changes can sometimes be traced to a defective crystal, but more often to varying supply voltages. If a crystal oven is used to keep the crystal temperature stabilized, a defective oven may cause the frequency to shift.

COLPITTS CRYSTAL OSCILLATOR (SEMICONDUCTOR)

Application.

The Colpitts crystal oscillator is used mostly at the higher radio frequencies as an extremely stable oscillator in receivers, transmitters, and test equipment. However, it may also be used at low and medium radio frequencies.

Characteristics.

Uses piezoelectric effect of a quartz crystal to control oscillator frequency.

Feedback is provided through a capacitive voltage divider arrangement, which is usually external, but it may be provided through the transistor element capacitances.


Normally does not use a tuned tank circuit adjusted to the crystal fundamental frequency (but may employ a tuned circuit for special applications).

Operates class C if waveform is not important, and class A if good waveform is required.


Circuit Analysis.

General. The Colpitts type crystal oscillator is usually used at the higher radio frequencies where the difficulty of tightly coupling the inductors in the inductive feedback circuits makes their use problematical. Actually, the so-called Colpitts version uses three basic feedback arrangements: (1) the external capacitive voltage divider with the crystal in shunt (or in series) (2) the crystal acting as a high-Q tank inductor similar to that in an ultraudion arrangement (parallel mode operation), and (3) the in-phase capacitive feedback arrangement, which is included in the Colpitts group solely because the feedback is capacitive (some texts may not regard this as a Colpitts, but as a special type of its own). The basic circuits of each type are shown in the accompanying illustration. Part A of the illustration employs the common-emitter configuration, and parts B and C use the common-base configuration. Actually, the circuit of part B can also use the CE configuration, and that of part C can use only the CB or CC arrangements, because the

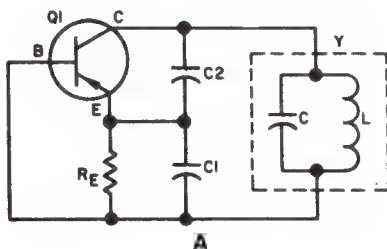
feedback must be between elements of the same phase of polarity. In the case of part C, the circuit is unique with semiconductors, since in electron tubes there is always a polarity inversion between input and output (except when used as cathode followers). The circuit of part B is analogous to the Pierce electron tube crystal oscillator.



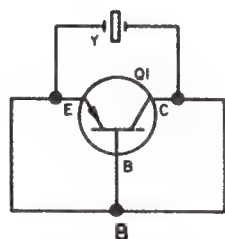External Voltage Divider Arrangement
(Parallel Mode)




Ultraudion Arrangement

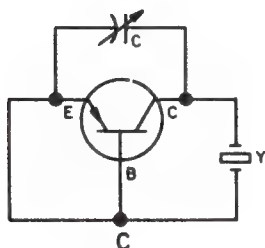

Basic Capacitive Feedback Circuits

For maximum power output, the input and output closely as possible; this requirement accounts to a great extent for the numerous variations in circuitry, since it is usually possible to sue any of the three basic circuit configurations and to ground any element. With the crystal determining the frequency stability of the circuit it is only necessary to arrange the proper polarity of feedback and provide a small amount of excitation to start the crystal oscillating. Although in a few cases the phase relationships within the transistor may require tight coupling to provide oscillation, it is usually easier to obtain stable crystal oscillations than to obtain stable self-excited oscillations, because of the assistance of the piezoelectric effect. The Colpitts semiconductor crystal oscillator, like its electron-tube counterpart, is usually a vigorous oscillator in the high-frequency range. However, the use of a quartz crystal does not extend the maximum frequency of oscillation, although it sometimes does provide better performance in the region between the alpha cutoff frequency and f_{max} . Thus good design makes it mandatory to use a transistor capable of oscillating strongly in the desired radio-frequency region of operation regardless of crystal control. Although there are a number of circuits in use, there is not much evidence at the present state of the art that the Colpitts is much (if any) more stable than the tickler coil crystal oscillator. Its main use is to improve operation at the higher frequencies.

Circuit Operation. A typical common-emitter Colpitts circuits using the external capacitive divider feedback method is shown in the accompanying schematic. Voltage divider bias is used for easy starting and is supplied by R_1 and R_B , with R_E providing emitter swamping resistance for stabilization of the transistor. Feedback is provided from collector to ground. With the base effectively bypassed by C_3 , the capacitive voltage divider consisting of C_1 and C_2 is effectively connected between collector and base for rf. Both feedback divider capacitors are variable to permit adjustment and control of feedback. Capacitor C_1 also serves to bypass rf around emitter swamping resistor R_E . Capacitor C_2 is the primary feedback control, and is usually made variable to facilitate operation with more than one type of transistor and crystal. The crystal is connected between the collector and ground and operates in the parallel mode. The collector is series-fed through the RFC and conventional bypass capacitor C_4 . The output is taken capacitively through C_{cc} from the collector.

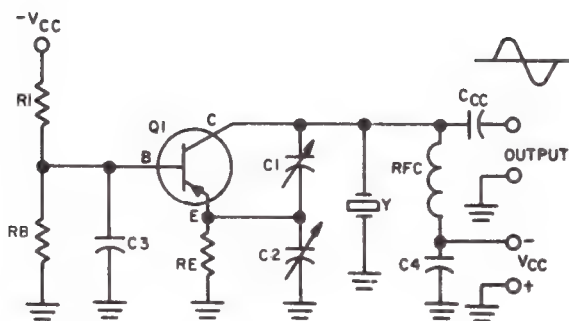


Untuned Colpitts Crystal Oscillator

The operation of the Colpitts type of oscillator basically depends upon the action of the voltage divider consisting of $C1$ and $C2$. Assume that the oscillator is first turned on. With fixed class A bias supplied by bias voltage divider $R1$, R_B , collector current flows, and a voltage appears across the $C1$, $C2$ divider. The voltage appearing across $C1$ is in parallel with emitter resistor R_E . Assume that a noise pulse caused by thermal action in the transistor causes the collector current to increase. A portion of the noise pulse voltage is then fed back through $C2$ to the emitter, causing the collector current to increase further (this is a regenerative action). At the same time, this increase in noise voltage at the collector also appears across crystal Y . Thus, the crystal is slightly strained mechanically by piezoelectric action. When the collector current reaches saturation, no further change in I_C occurs, and the regenerative action ceases. At this time, the electrostatic strain across the crystal begins to reduce as capacitor $C2$ discharges (the heavy current flow from collector to emitter effectively shunts the capacitor). Thus, the emitter to ground voltage is reduced, the forward bias is reduced, and the collector current starts to fall. This action is also regenerative, and the transistor quickly reaches cutoff. As the collector current reduces, the voltage across the crystal approaches that of the supply (becomes more negative), and the crystal is now strained in the opposite direction. As a result, as each cycle of this action continues, the crystal oscillates at its parallel-resonant frequency. Since oscillation of the crystal produces a voltage across it, once started into vibration, the crystal continues to oscillate. Since the crystal is connected in shunt from collector to ground, it effectively

functions as a parallel-resonant tank circuit, and smooths out the pulses of oscillations into approximate sine wave-forms. On the conducting portion of the transistor operating cycle, it is effectively reinforced by the ensuing pulse of collector current, and during the nonconducting portion of the cycle, it supplies what would otherwise be the missing half-cycle of oscillation by flexing in the reverse direction. Emitter resistor R_E and capacitor $C1$ form an amplitude limiting device similar to that of the electron tube grid leak. The output is taken from across the crystal, with C_{cc} acting as a dc blocking and ac coupling capacitor. It is evident that the crystal must be capable of handling the power developed, since if driven too hard it will fracture. However, at the normally low milliwatt outputs obtained with transistors, this is no problem. It does indicate, however, that the transistor crystal oscillator requires additional stages of amplification to produce the same r-f drive as an electron tube crystal oscillator.

A typical Colpitts crystal oscillator of the ultraudion form is shown in the following illustration and may be compared with the basic version. This circuit is analogous to the Pierce type crystal oscillator, and is more easily recognizable because the crystal is connected directly between collector and base. The common-emitter configuration is also used in this version, and feedback is provided directly through the crystal. Voltage divider class A bias is obtained by means of $R1$ and R_B for easy starting, with emitter swamping being provided by R_E , bypassed by $C2$.

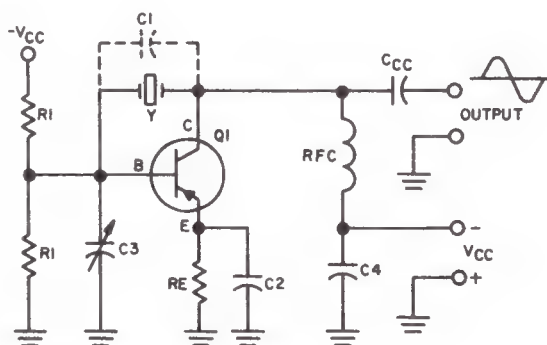


Ultraudion Colpitts Crystal Oscillator

The output is taken capacitively from the collector circuit through C_{cc} . In this instance, C_3 is a variable control which permits adjustment for feedback and transistor variations. Both this circuit and the Pierce electron-tube circuit operate almost identically. The feedback capacitive divider in this case consists of the total shunt capacitance across the crystal (including holder and stray wiring capacitance, plus the internal collector-base capacitance, shown dotted as C_1) and external capacitor C_3 to ground. In this circuit version, the crystal and feedback network appear to be in the base circuit, rather than the collector circuit as in the other version. The difference is that, like the ultraudion electron-tube oscillator, the crystal is considered to be a tank circuit operating in the parallel mode, and since the capacitance of C_1 and C_3 is usually less than that of C_1 and C_2 in the previous circuit version (the emitter-collector capacitances is much larger than the base-collector capacitance), the ultraudion circuit tends to be operable at higher frequencies than the external capacitive-divider circuit. Also, phase shifts within the transistor due to transit time effects are such that they aid in producing the correct feedback polarity.

Now consider one cycle of operation. Assume that crystal Y at rest and the circuit, as illustrated above, is inoperative with no collector voltage applied. At rest, the crystal is unstressed and there is no charge on either plate. When the collector voltage is applied, since the circuit is fixed biased for class A operation by voltage divider R_1 , R_B , collector current flows similarly to that in a conventional amplifier. With the base connected to one plate of the crystal and the collector connected to the other plate, when one plate is negative the other plate will be positive. This is the same condition as when the crystal produces a piezoelectric voltage; it is also the same as the polarity for base-collector operation in the common emitter circuit (base polarity is opposite to collector polarity). Therefore, the instant the collector appears negative at turn-on time, the piezoelectric voltage across the crystal causes the base electrode to be positive; this small positive voltage, in turn, causes a reduction in I_c , producing a decrease in collector current. Thus, the collector voltage (of a PNP transistor) becomes more negative. This action is regenerative, and quickly drives the collector to cutoff. During this

time the crystal is being deformed in the same direction. During cutoff a small I_{CEO} current flows which only affects the efficiency of the circuit. Since the value of I_{CEO} is steady, there is no change in feedback from the collector. Meanwhile, the small charge developed on C_2 by the flow of emitter current through R_E leaks off, reducing the emitter bias and permitting the class A bias to again cause normal current flow. The increase in collector current now causes a reduction in collector voltage, in effect producing a positive swing. The crystal now changes polarity and flexes back toward its original shape. As a result of piezoelectric action, a negative charge now appears on the base electrode. This causes a further swing of collector voltage in the positive direction (this action is also regenerative), and at full current flow the crystal is equally deformed in the opposite direction. At this time the flow of I_c is again steady (corresponds to saturation current flow with self-bias). Since the emitter current flow through R_E produces a bias voltage, C_2 now charges and the emitter bias is added to the fixed bias. Once again the collector current is reduced by the increasing bias, and the cycle repeats. Thus, in flexing back and forth in accordance with the changes in collector voltage, the crystal is caused to oscillate; in turn, it produces an in-phase piezoelectric voltage which enhances circuit action. The crystal oscillates at some frequency between that of series and parallel resonance. Actually, the phase shift of the feedback voltage from collector to base, which is necessary to produce oscillation, is produced by the crystal acting as a high-Q inductor which produces an initial 90-degree shift. An additional phase shift is caused by the base-emitter capacitance, which is sufficient to cause an effective feedback large enough to overcome any of the resistive losses in the circuit. Thus, continuous oscillation under control of the crystal is assumed. Although the basic oscillation consists of distorted pulses of collector current, the effective tank circuit action of the crystal helps smooth out these pulses into approximate sine-wave oscillations. The output is taken through coupling capacitor C_{cc} , and appears as a resistive load in shunt from collector to ground.

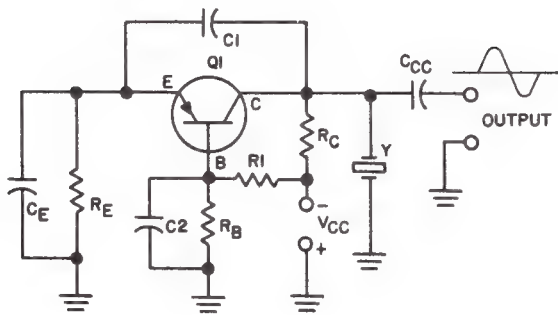The common-base arrangement of the Colpitts crystal oscillator using in-phase capacitive feedback is shown in the following illustration. Voltage divider



Colpitts Common-Base Crystal Oscillator

bias is supplied by R_1 and R_B , and the base resistor is bypassed for rf by C_2 . Emitter resistor R_E , which is bypassed by C_E , provides conventional swamping of the emitter circuit, and R_C provides resistance stabilization in the collector circuit. The crystal is connected between collector and ground, but is effectively connected between the collector and base for rf by means of C_2 . The output is taken capacitively from the collector (across the crystal) through C_{CC} .

Since the emitter and collector in the common-base circuit are of the same polarity (in-phase), feedback is obtained by using C_1 to apply a portion of the collector voltage to the emitter.


Now consider one cycle of operation. Fixed class A bias is supplied by voltage divider R_1 , R_B . When collector voltage is applied, Q_1 conducts as in a conventional amplifier. Assume that a noise pulse occurs in the base circuit, which causes the collector current to increase. The voltage drop across collector resistor R_C appears as a positive-going pulse, which is applied through C_1 to the emitter. This increase in emitter bias is in the forward direction, causing a larger flow of collector current. Thus, a regenerative in-phase feedback exists. The positive-going noise pulse is applied to crystal Y , which is in shunt from collector to ground, causing the crystal to be distorted in one direction by piezoelectric action. When the collector voltage bottoms (becomes almost zero), no further feedback occurs and the crystal flexes in the opposite direction. By piezoelectric action the crystal polarity is now reversed and a negative charge appears at the grounded electrode. Since the base is connected to

ground through C_2 , the base now has a negative voltage applied and thus operates to reduce I_C . As the collector current reduces, the drop across R_C becomes negative-going and approaches the source voltage.

The feedback through capacitor C_1 is also negative and reduces the forward emitter bias, causing a still smaller I_C to flow. This action is also regenerative and continues until cutoff is reached. At this point a small flow of reverse current (I_{CEO}) exists, but it has no effect other than to reduce the over-all efficiency of the circuit. Once the feedback stops, there is no further change in current, and C_E (which was charged negatively during this half-cycle) starts to discharge through emitter resistance R_E . When the emitter voltage drops to a value which again starts I_C flowing, a positive-going voltage is produced across R_C , and a positive voltage is again fed back through C_1 , and the cycle repeats. During this time the crystal is now flexing in the opposite direction and the polarity across it again changes, so that the crystal-induced piezoelectric voltage is in phase with the collector-base voltage. Actually, the crystal acts as a tank circuit, smoothing out the rough pulses of current into approximate sine-wave variations. By appearing as a high-Q inductance, the crystal insures that the proper feedback phase relationship is maintained, and, since it is a low-loss tank, the feedback through C_1 need only be sufficient to supply the small tank losses to sustain oscillation.


By properly proportioning C_E and R_E , the bias can be made to reach the region of class C operation for best efficiency, as in regular gridleak operation, while the fixed class A bias makes certain that starting occurs easily. The output is taken from across the crystal through coupling capacitor C_{CC} . Therefore, the load is in shunt with the crystal and tends to reduce the output somewhat as in the electron-tube Pierce circuit.

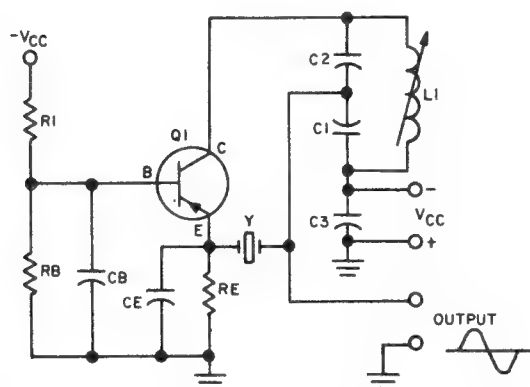Circuit Variations. Because the Colpitts crystal circuit has so many variations, a few representative circuits are shown in the following illustrations to facilitate identification of this type of circuit. Parts are labeled as in previous illustrations where they serve the same function, and the discussion is limited to the basic differences between these circuits and those considered previously.



Tapped Collector Crystal Oscillator


In this circuit version, conventional voltage divider bias and emitter swamping are used for stabilization. The crystal is series-connected between the emitter and the collector by the voltage divider, consisting of C1 and C2, connected across L1. The operation of this circuit is based on a combined matching of impedances and a feedback connection. Connecting the crystal to the emitter through the capacitive voltage divider provides the proper feedback polarity, and the capacitances of C1 and C2 together with L1 form a tuned tank circuit which is resonant to the crystal fundamental (series-resonant) frequency. The input and output impedances of the transistor are matched by the proper capacitance ratios, producing the same effect as though the collector were tapped across L1. The output is taken between the tap and ground, that is, across the crystal. This type of circuit is usually used at the lower r-f frequencies. The use of a tuned tank helps provide a good waveform and permits frequency doubling or the use of an overtone crystal.

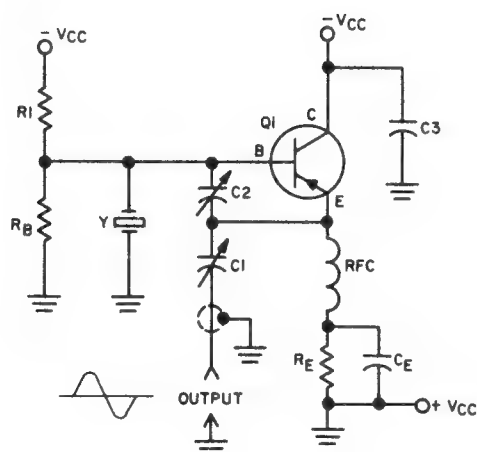

Grounded-Collector Colpitts Crystal Oscillator

A grounded-collector common-emitter version in which the voltage divider and crystal are located in the base circuit shown previously. Conventional voltage divider biasing and emitter swamping are used for stabilization. The collector is grounded for rf by C3. Thus in effect the crystal is connected between base and collector similar to the Pierce grounded-plate electron-tube version. However, the crystal, although isolated from collector voltage, is still subject to the small bias voltage from base to ground. Feedback is provided through capacitive divider C1 and C2, with primary control of feedback being provided by C2. Capacitor C1 is used to tune (match) the output, which is taken between the tap and ground. This type of connection offers a low output impedance suitable for coaxial line matching. The RFC is used to keep the emitter above ground; otherwise, the load or output would be short-circuited through CE. No particular claims are made for this version other than its output matching feature.

The inverse feedback type of crystal oscillator shown in the following illustration, utilizes a conventional Colpitts with an external feedback capacitive voltage divider and with the crystal in the collector circuit. Bias is obtained by a conventional voltage divider, and emitter swamping is used for stabilization. The bias is provided in conjunction with feedback by tapping R_F on L_1 . Thus, dc bias is obtained through R_F and R_B , r-f feedback is obtained through R_F and L_1 . The basic feedback path is through the capacitive divider, C_1 and C_2 , and the secondary feedback path is through L_1 via R_F . Placing the tap at the lower end of L_1 produces regenerative feedback, and placing it at the upper end produces degenerative feedback, because the polarization of the collector is opposite that of the base. Thus, by placement of the tap, the feedback can either enhance oscillation by regenerative action or stabilize operation by degenerative action. The possibility that unwanted resonances of parts in this circuit may tend to cause free-running operation makes this version of dubious value. With the output being taken from the collector, it is more likely that the feedback tap provides better input and output matching to the transistor, similar to the tapped collector circuit previously mentioned.

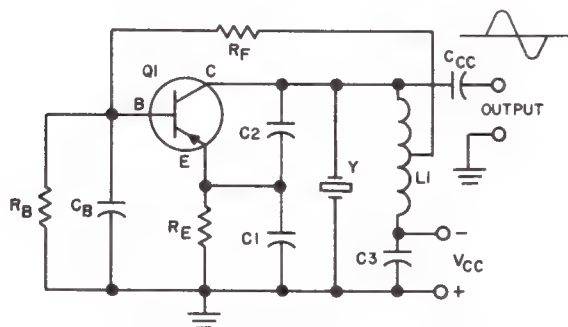

Inverse Feedback Crystal Oscillator

Failure Analysis.

No Output. In tuned circuit oscillators, the loss of output can be due to improper tuning. Also, a defective crystal will prevent operation, in either tuned or untuned circuits. A suspected crystal can easily be checked by the substitution of a crystal known to be good. A simple resistance check will indicate continuity and general parts condition. A defective bias

resistor producing a high bias voltage (in the divider arrangement) can prevent starting, and will be made evident by a resistance or voltage check. An open bias arrangement can prevent operation by causing a lack of bias, or by causing excessive internal bias due to feedback within the transistor. An open r-f choke, collector resistor, or coil will also stop operation. A shorted coil in the tuned circuit can stop oscillation, but the short will not be revealed by a resistance check. This condition is checked (after all other components have been eliminated from suspicion and a crystal known to be good has been substituted) by grid-dipping the tank for resonance. A defective transistor should be suspected only if all other parts check satisfactory and bias and supply voltages are normal.

Reduced Output. A low supply voltage or increased collector resistance can cause a reduction of output. A reduction of bias from class B or C to class A will also result in reduced output. Both of these conditions can be determined by a simple voltage check, preferably with a vacuum-tube voltmeter or a high-resistance volt ohmmeter. Reduced crystal activity, due to aging or semi-fracture, or a dirty crystal can also be a prime cause. In this case, substitution of a crystal known to be good will restore normal operation. A change in the value of the emitter swamping resistor or bypass capacitor can cause excessive bias, and consequent squegging or motorboating due to intermittent blocking of oscillations. In circuits designed for the higher frequencies, changing the lead dress or parts wiring during repair may change the distributed wiring capacitance sufficiently to detune the circuit and cause a reduced output. In the tuned tank versions of this circuit, reduced output can also be caused by a high-resistance tank circuit connection or a shorted turn.

Incorrect Frequency. A defective or dirty crystal can cause an abrupt change from one frequency to another; this can sometimes be corrected by adjusting the tank tuning, if an adjustment is provided. Aging of the crystal can also cause a slow change over a long period of time; this change can sometimes be compensated for by means of a small trimmer capacitor, if the frequency is higher than normal. (Do not add an unauthorized modification to accomplish this. In most circuits a trimmer is included to permit calibration to the exact frequency for which the crystal is ground.) Failure of the collector supply regulation (as well as the bias supply regulation) can cause the effective element capacitance of the transistor to change

and cause slight off-frequency operation. In this case, check the supply voltage with a high-resistance voltmeter and observe whether there are occasional fluctuations of the voltage when the crystal is suddenly removed from its socket and reinserted into its socket or when the load is suddenly removed and replaced. If all components check normal and trouble is still present, the crystal is probably defective.


PART 6-3. TUNED-LINE OSCILLATORS

TUNED-LINE OSCILLATORS

General.

As the frequency of operation extends into the VHF and UHF regions and into the microwaves, it becomes more and more difficult to produce oscillations using conventional electron tubes. At the extremely high frequencies even the best oscillators are not very efficient. The difficulties of high-frequency operation involve the construction of the electron tube. As the frequency increases, the transit time between electrodes must be considered. Also, the tube electrodes have capacitance between each other and ground, and their leads have inductance. At the lower frequencies these capacitances and inductances are negligible as compared with the other lumped circuit components, but at the very high frequencies they become the major part of the circuit, and often must be minimized to extend the upper frequency limit. To minimize lead inductance, electron tubes are debased (no base is used), they use large leads to minimize skin effect, and sometimes have their grids or plates brought out through the envelopes. To reduce interelectrode capacitance, tubes are miniaturized to make their elements smaller (this also reduces their power-handling capability), and special construction in the form of a planar triode or tetrode is used. (The planar type of construction uses a single flat grid (or plate) through which the electron stream passes, instead of grids or plates made up of wires or screens, which are "wrapped" around the emitter as in conventional tube construction.) The original derivation of the planar tube was the well known lighthouse tube (also called *disc seal* tube), which is so named because of its physical resemblance (three or more stepped cylinders) to a lighthouse. These tubes utilize coaxial and

planar elements, or rings, with direct physical connection to the electrodes themselves. There are two forms of oscillator used. One form, which operates in the VHF region, uses a special socket and its operation is similar to that of a conventional LC oscillator. The other, which is used in the UHF region, incorporates a series of coaxial cylinders into which the lighthouse tube fits as an integral part, forming a tuned line coaxial oscillator. Tubes used for low power and receiving purpose are usually provided with conventional pin type sockets, and those used for transmitting are either provided with a special socket and plate cooling fins or are inserted into the cavities or lines to form a compact unit. The construction of a typical tube is illustrated in the accompanying figure.

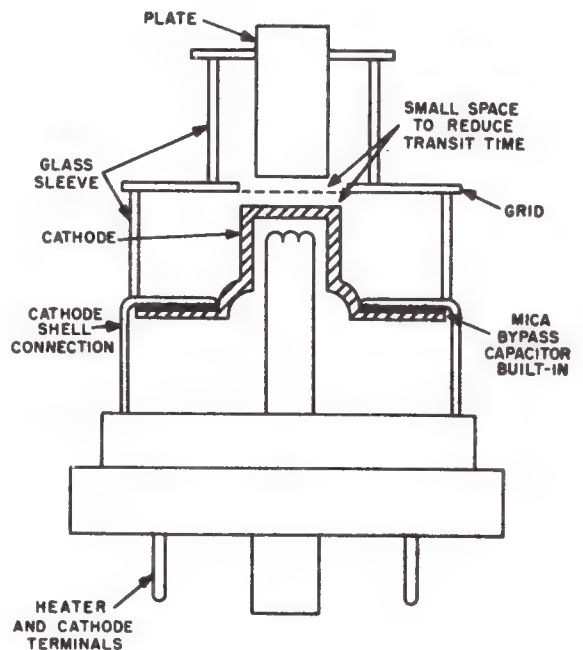

Lighthouse Tube

In addition to the coaxial line oscillators, tuned transmission line, or Lecher line, oscillators are also used. The tuned lines in these oscillators are arranged parallel to each other, instead of being arranged coaxially. At the lower frequencies the lines are used as inductances and are tuned with a shorting capacitor. At the higher frequencies they are tuned with a

shorting bar and operate essentially as a quarter wave transmission line.

The tuned line can be substituted for an LC tank circuit because it possesses the same properties as the tuned tank. When the line is exactly a quarter wavelength long electrically, and is shorted at the far end with the input open, it presents a high impedance at the input and a low impedance at the far end. When it is coupled to a source of energy, a heavy current will flow in the line at the shorted end, but only a small current (or no current) will flow at the open or input end, because of the high input impedance. This effect is exactly the same as that produced by the conventional LC tank; therefore, the quarter-wave line can be substituted in its place.

Use of the transmission line tuned circuit provides a higher Q and lower losses than is possible with conventional lumped inductance and capacitance. The higher Q is obtained because the resistance of the line is low for a given value of reactance, since Q is equal to X_L/R . The low resistance is obtained by using relatively large diameter tubing, since at radio frequencies current flows on the outside of the conductor because of *skin effect*. For UHF applications this loss is made even less by silverplating the outside of the conductor, so that the r-f current flows through a highly conductive path of silver. For single-tube oscillators the concentric type line is frequently used, and for push-pull circuits a balanced two-wire line offers a convenient arrangement (two concentric lines may also be used). The concentric line has the additional advantage that the outer conductor shields the inner conductor and thus reduces unwanted radiation from the tank to a minimum.

An incidental feature of the quarter-wave transmission line tank results from the use of the high-impedance property at the open (input) end and the low-impedance property at the output end to insulate the line as far as rf is concerned. Thus the shorted end of the line may actually be attached to the chassis without affecting the operation. This helps to reduce dielectric losses, which otherwise would be introduced if an actual insulator were used. Unfortunately, this feature cannot be used where dc is applied to the line as in series plate feed arrangements, but it can be used in shunt-feed arrangements.

The tuned lines and circuits discussed in this section are confined to negative grid oscillators; that is, to oscillators where the average grid voltage is always negative, since there are other special oscillators (such

as the Barkhausen-Kurz and Gill-Morrell oscillators) which use positive grid operation to obtain UHF oscillations. This classification is necessary to avoid confusion, as both groups appear to be identical schematically at first glance, since both employ tuned lines. The positive grid voltage is the major identifying feature of the positive grid oscillator and the circuit operation is entirely different from the operation described below.

Because the reactance of the tube interelectrode capacitance and distributed circuit capacitance is small at ultra high frequencies, the circulating (or charging) current in these capacitances is large. It is on the order of many amperes for large power tubes. This high current adds nothing to performance, and may cause damage. Because of skin effect, the current follows the surface of the metal electrodes of the electron tube, and causes localized heating of the seals, sometimes causing cracks and tube failure. Thus, in UHF oscillators the tuned circuit is designed to have a high inductance and the minimum capacitance that will resonate the tank to the operating frequency. Tuned-line tanks provide the required high inductance with a minimum of capacitance. The trend in present day tube manufacturing is to employ ceramics instead of glass as dielectrics, because of their better heat resistance and easy machining properties, in addition to the reduction of inter-electrode capacitances. The push-pull circuit effectively reduces these capacitances to half their normal value since they are in series in push-pull operation. Although an open transmission line has some eddy current and radiation losses, close spacing to less than one hundredth of a wavelength (a few inches) causes the field around one conductor to neutralize the field around the other. Radiation and eddy current losses are thereby minimized, but not as completely as with the shielded coaxial line.

The Q of the quarter-wave short-circuited section of line is much higher than that of the conventional tank circuit because larger diameter conductors can be used than in the conventional coil, making the skin effect less. Specially constructed (planar) tubes extend the transmission line as a part of the tube leads. Thus, the interelectrode capacitances and lead inductances of the tube are all incorporated as a part of the tuned circuit.

Transit time produces two different effects at UHF. (1) it causes the plate current to lag the grid voltage by a small angle, so that the phase difference

between the plate current and plate voltage is greater than 180 degrees. As a result, the power output is decreased and the plate dissipation is increased. (2) The transit time permits an accumulation of electrons on the grid and causes grid current flow, even when the grid is negative. This produces a grid loss which is similar to the loss incurred by shunting the grid with a resistor. At extremely high frequencies this loss is so great that the effect is as though the shunting resistor produced a short circuit between grid and cathode and prevented proper excitation of the tube. The grid loss also results in the development of heat, which can exceed the tube ratings.

Therefore, while tuned lines, together with special tube construction, offer a partial solution to the transit time problem, a different kind of generator other than the simple ultraudion feedback arrangement is required to operate at UHF with reasonable power output. The lighthouse tube provides efficiencies on the order of 48% at 500 MHz to 10% at 2100 MHz for CW operation, and 52% to 35%, respectively, for pulsed emissions. The present day trend is to use klystron generators for UHF, planar tubes for VHF, and either klystron or magnetron generators for microwaves and beyond.

LIGHTHOUSE-TUBE OSCILLATOR

Application.

The lighthouse tube oscillator is used as an r-f source in the UHF range for receivers, test equipment, and low-power oscillators or transmitters. The planar type triode or tetrode is used for transmitters where more than a few watts are needed.

Characteristics.

Use special tube construction to overcome high-frequency limitations.

At frequencies of 300 to 1500 MHz uses external lines, and at frequencies of 1500 to 2500 MHz uses coaxial cylinders, into which the tube is inserted as an integral part.


Tuning is accomplished by means of shorting bars or plungers.

Has low output and low efficiency (10-30%).

Circuit Analysis.

General. The so-called lighthouse tube oscillator is operable over a large range of frequencies, and the frequency of operation basically determines the final form of the oscillator. At frequencies up to about 1500 MHz, the size of the coaxial elements that would be required is so great that external open-wire line or tubing must be used. When the frequency approaches 2500 MHz, however, coaxial elements become small enough for practical use, and the tube itself can be inserted into them to form part of the line. Since the design of the lighthouse tube provided the necessary means of overcoming the difficulty of obtaining oscillations at the high frequencies above 300 MHz, there have been a number of similar designs. Thus, the basic lighthouse tube evolved into the co-planar type of triode and pentode. In this tube the elements are coaxial cylinders, with the outside of the rign forming the electrode contact. Planar tubes using plane rings instead of coaxial cylinders can be used in coaxial lines, or separately with a special socket. The receiving type (or low-power type) has a conventional octal socket using only cathode and heater pins. The transmitting type requires the special socket and is usually equipped with radiation type cooling fins connected to the plate and normally requires forced air cooling. Where coaxial construction is used, the coaxial line itself acts as the heat radiator. Since the basic lighthouse coaxial unit is representative of this type of design, all discussion will be confined to the original type of lighthouse tube. Although now replaced by tubes of planar design, the original lighthouse tube may still be encountered.

Circuit Operation. The construction of a typical self-contained lighthouse tube oscillator is shown in the accompanying illustration. The tuner assembly consists of three concentric tubes, or coaxial lines. The inner tubing is connected to the plate, the center tubing to the control grid, and the outer tubing to the shell or base envelope of the tube. The outer tube is effectively shorted to the cathode for rf by a built-in mica capacitor connected between the metal envelope and the cathode.

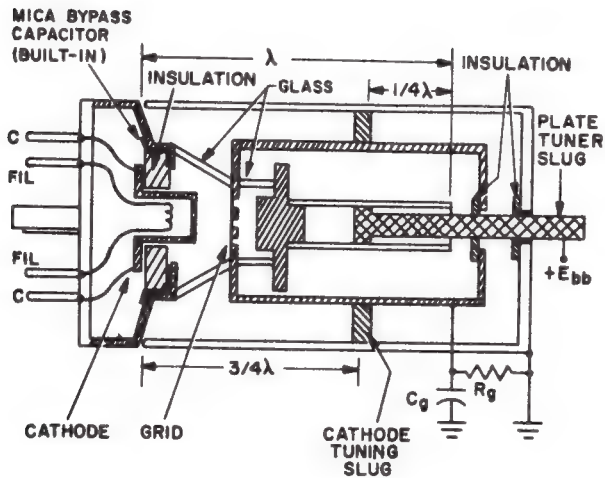


Coaxial Cavity Tuned Oscillator

The cathode (outer) and control grid cylinders form a coaxial cathode line which is effectively short-circuited by a capacitive non-conducting plunger at a point approximately $3/4$ of a wavelength from the point of connection to the tube elements. The position of this plunger is adjusted for the proper amount of feedback. The capacitance between the plunger dielectric and the grid conductor of the coaxial line effectively shunts the rf to the cathode, but does not short-circuit it for dc. The dc path between the cathode and control grid is provided by grid-leak resistor R_g , bypassed by grid capacitor C_g , which produces grid-leak operating bias. A shorting plunger is inserted into the plate line $1/4$ wavelength from the open end ($3/4$ wave from plate end) to tune the plate circuit. Plate voltage is supplied by connecting $B+$ to the plunger. The short circuit provided by the shorting plunger offers a high impedance to rf energy a quarter wavelength away, so that no rfc is needed to isolate the plate supply. Since the grid is located approximately one wavelength from the open end of the line and a high impedance is reflected there by the plate tuning plunger, the grid is also placed at a point of high impedance with respect to plate. Thus the open wavelength-long plate conductor and the shorted three-quarter-wavelength cathode conductor both act as parallel resonant tank circuits. The tuning of the plate circuit determines the operating frequency of the oscillator, and the tuning of the cathode circuit determines the proper amount of

feed-back for stable oscillation. Since there is a certain amount of interaction between the plate and cathode circuits, it is necessary when changing frequency to adjust both plungers for optimum operation.

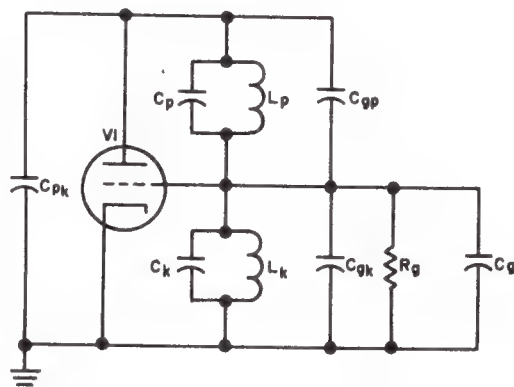Detailed Analysis. The r-f equivalent circuit of the lighthouse tube oscillator is shown in the accompanying illustration.



Lighthouse Equivalent Circuit

The interelectrode capacitance of the lighthouse tube, plus the capacitive effect of the open ends of the grid conductor, is represented in the diagram as C_{pk} . The net reactance of the parallel tuned circuit containing C_k and L_k , shunted by C_{gk} , must be capacitive to ensure that the voltage divider which they form with C_{gp} supplies alternating voltage of the proper polarity to the grid. This means that the frequency of the cathode tank circuit must be lower than the output frequency of the oscillator. The operating frequency of the oscillator is determined primarily by the resonant tank in the plate circuit (C_p , L_p), which is in parallel with C_{gp} , and the effective input capacitance of the voltage divider network; consequently, it is lower than the resonant frequency of the plate tank alone, and slightly higher than the frequency of the cathode tank. To provide the proper feedback to sustain oscillation, it is necessary that the resonant frequency of the cathode tank circuit be less than the resonant frequency of the plate tank circuit. This is accomplished by careful tuning of the lines. Particular care is necessary in adjusting the cathode line; if the line is too short, it appears inductive and

oscillation stops. On the other hand, if the line is too long, the effective feedback divider capacitance is increased, and the amplitude of the feedback voltage becomes too low to sustain oscillation. Consider now one cycle of operation. When the plate voltage is applied, heavy current tends to flow in the plate circuit since the tube is self-biased and the initial bias is zero. The initial rush of current shock-excites both plate-grid and grid-cathode tanks into oscillation. Since the grid-cathode tank ($C_k L_K$) is tuned to a lower frequency than the oscillator output, it appears as a capacitive reactance shunting the grid-cathode interelectrode capacity, C_{gk} . Neglecting the plate tank for the moment, it is seen that C_{gp} will charge due to momentary grid current flow, since C_{gp} and C_{gk} form a capacitive voltage divider between plate and cathode, or ground. Assuming that the charge is in such a direction as to make the grid more positive a momentary and amplified increase in plate current will occur. This action is regenerative. Since the plate tank is tuned to a higher frequency than the r-f output, it appears as an inductive reactance shunting C_{gp} . The result is to produce a negative grid input resistance which overcomes grid circuit losses and permits oscillation to occur. This negative resistance occurs primarily from the tank circuit which, in effect, returns energy to the circuit through its flywheel effect. When the grid pulse reaches its maximum, the plate tank appears as a high inductive impedance across which the plate voltage is dropped. During this time the tank absorbs energy from the circuit. As the grid swings negative plate current is reduced and eventually cut off. During this time the tank is returning energy to the circuit. The feedback is now in an opposite direction to the initial charging current (C_{gp} is discharging), is likewise regenerative, and quickly drives the tube to cutoff. Once oscillatory action is started it continues until the plate voltage is removed, or until the grid tank is detuned too far from resonance to retain the proper phasing. If tuned too high in frequency it appears inductive and the feedback is opposed and oscillation stops. Conversely, if tuned too low in frequency it acts as a heavy capacitive shunt from grid to cathode and also stops oscillation.

Grid bias is provided by grid-leak resistor R_g and capacitor C_g , which are connected between the open (high-impedance) end of the grid line and ground. After a few oscillations are built up, a small charge is put on C_g each time the lower end of the tank circuit swings positive. During the time the grid is not posi-

tive with respect to the cathode part of the charge leaks off through grid leak R_g . The voltage to which the grid capacitor is charged ultimately makes the grid sufficiently negative so that only a small amount of charge is added to the capacitor at the peak of each cycle, and all of this small increase of charge leaks off through R_g during the remaining time of the cycle. Thus the grid is maintained at the proper bias for good operation. If the high negative bias required for proper operation were applied at the time the oscillator was turned on, the tube would be completely cut off and oscillations could not start. It can be seen from the schematic that this circuit is essentially a simple tuned-plate, tuned-grid oscillator with the basic feedback being supplied through the plate-to-grid capacitance.

Failure Analysis.

No Output. Since the unit is of integral construction, loss of output may be caused by failure of the cavity to tune properly, a defective tube, or an open or shorted supply. Where contact fingers are used for the shorting plunger, as in the plate line, poor contact will cause improper tuning and lack of oscillation. Also, poor contact will cause a reduction or complete lack of plate voltage, and produce loss of oscillation. The presence of voltage may be determined by a voltmeter. Poor contacts will be indicated by fluctuations of the plate current as the plunger is tuned, and sometimes by burnt spots on the lines. A defective tube is usually indicated by lack of normal plate current when due to lack of emission, or by abnormal plate current when short-circuited. Because of the inherent solid construction of the coaxial tuner, poor contacts or tube failure are the most common troubles. At radio frequencies any additional resistance in contacts produces losses which are serious in the UHF range. Therefore, effects which are not very noticeable at the lower frequencies can produce complete lack of oscillation at UHF. Since the inner cavities are inaccessible until disassembled, the only practical check is a test for voltage on the heaters and plate, and between grid leak and ground, if accessible. Observation of the plate current while tuning and a check of the voltages should be made first. The unit should then be disassembled and the tube and coaxial tuner checked.

Reduced Output. Reduced output is usually due to low plate voltage or improper tuning. Low plate voltage can be the result of poor contact resistance in

the tuner or a defective supply, which can be easily located by making a voltage test. Improper tuning can be quickly verified by slight readjustment of the controls to see whether the output improves. With normal plate voltage and correct tuning, if the output remains low, either the tube or the grid leak is probably defective.

Incorrect Frequency. Since the frequency is determined by the adjustment of the plate tank, small frequency changes can be corrected by tuning. Plate-voltage and load changes will also affect the frequency to a small extent; these can be checked by changing the load and measuring the supply voltage. Normally the high Q tank afforded by the coaxial cavity results in a highly stable frequency. In cases of high ambient temperature, however, the line and cavity dimensions may change and produce a drift in frequency, depending upon the metal used. For temperature-caused changes, adequate ventilation by means of forced-air cooling is necessary. If the cavities and lines are made from temperature-compensated alloys, the cause of frequency changes will be limited to supply or tube defects.

Instability. Unstable oscillations may be caused by erratic plate supply voltage, lack of regulation, or improper tuning.

LECHER-WIRE OSCILLATOR

Applications.

Lecher-wire oscillators are used in the VHF and UHF regions to generate rf for the receiver oscillators, test equipment, and transmitters.

Characteristics

Uses a pair of lecher wires, or tuned lines, in place of conventional LC tanks.

Frequency of operation is such that use of quarter-wave or half-wave lines are practical.


Has better stability and efficiency than a conventional LC circuit.

Usually used with the planar type of high-frequency tube, but not restricted to any type (can be used with any tube that will oscillate).

Circuit Analysis.

General. The lecher-wire, or transmission-line, oscillator is derived from the lecher wire wavelength measuring principle and the application of transmis-


sion line theory. The lecher-wire principle is shown in the accompanying illustration, in which two parallel wires a few inches apart are capacitively coupled to an r-f source. Assuming that the coupling is loose, the wires are in effect open-circuited. The length of the wires should be at least one full wavelength at frequency of the r-f source. When a shorting bar is series with a current indicator, such as a lamp or r-f ammeter, is placed across the lines, it will be observed that at a point $1/4$ wavelength from the source maximum current is obtained. If the shorting bar is left at that spot and another one is moved along the line, an identical maximum indication (but not the same value) will be obtained at a point $1/2$ wavelength from the first indication ($3/4$ wavelength from the source). This demonstrates that standing waves exist on the line. Such a device can be used to measure the frequency of operation in wavelengths. When the lecher wire is coupled through a single-turn loop to the r-f source, the line is considered closed at both ends; in this case, the first indication will be obtained at the half wavelength point.

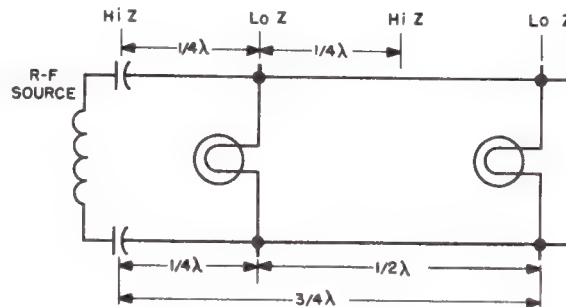


Lecher Line

Transmission line theory predicts that a half-wave line repeats, or reflects, the input conditions at the output.

If a transmission line is open-circuited, it will have maximum impedance at the half-wave points, as shown in the preceding figure. If the transmission line is shorted, it will have the lowest impedance at the half-wave points as shown in the following figure. Conversely, a quarter-wave line (if open) will see a high input impedance (at its source) when shorted at a point a quarter wave from the input end, and if

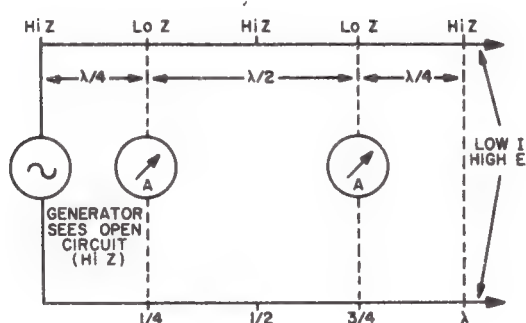


Open-End Line

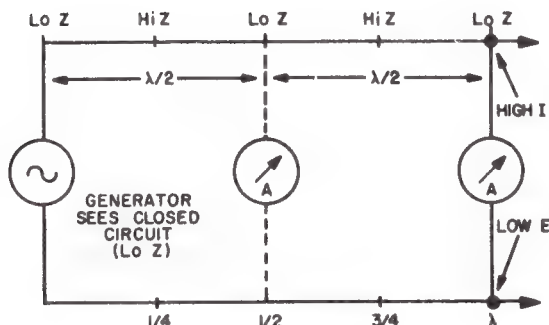

Closed-End Lines

shorted at the input, will have a maximum impedance one quarter wave from the short as shown in the preceding illustrations of open and closed lines.

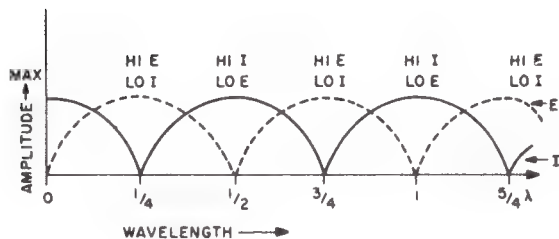
When standing waves exist on the transmission line, the current and voltage are out of phase. That is, at a



Relationships of Standing Waves

point of maximum current, the voltage is at a minimum and, conversely, at the point of maximum voltage, the current is at a minimum as shown in the accompanying illustration. Thus either voltage or current indications may be used in the lecher wire.


If the lecher line is attached to the grid and cathode of an electron tube and ground, and is tuned to a quarter wavelength, the current through the line will be heavy since it is limited only by the resistance in the line at the short; this is the equivalent of a series resonant circuit formed by an LC tank. At the grid and cathode (one quarter wavelength away), the impedance will be high and only a minimum current will flow between cathode and grid. Thus the line simulates a parallel resonant circuit, with a heavy circulating line current and minimum external current as shown in the following illustration.

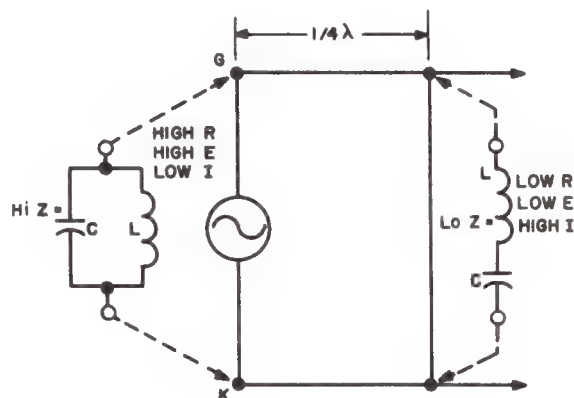

Shorted Line Equivalents

Circuit Operation. When the lecher line is connected between the grid and plate of an electron tube, a simple ultraudion oscillator results, with the line forming the tank connected between grid and plate of the tube, as shown in the following illustration. In the illustration a capacitive shorting bar is employed; since plate voltage is present on the plate bar, it would be applied to the grid if a direct shorting bar were used. At the frequencies used, the capacitor has such a low reactance that it is effectively a short circuit for rf, but it will block dc. Grid-leak bias is obtained through the action of R_g , and the total effective grid-cathode circuit capacitance acts as the grid-leak capacitor. The r-f output can be taken from

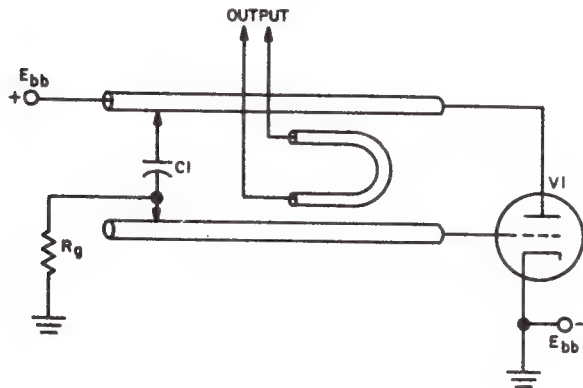the circuit with a hairpin coupling loop or capacitively from the grid or plate bar. Tuning is accomplished by moving the shorting bar along the lecher line. The amplitude is controlled by the grid-leak value and the applied plate voltage, by the spacing




Simple Lecher Line Oscillator

between the bars, and by the tube electrode capacitance. See the ultraudion oscillator circuit discussion in another part of this section for an explanation of the feedback operation of this type of circuit.

Although the simple oscillator just discussed is operable, it has been found advantageous at UHF to utilize circuits which minimize the circuit capacitance. This allows the lecher lines to act more like lumped components, and thereby serve as the controlling factor in the circuit, permitting tube replacement with minimum effect on circuit operation. The tubes may be any type that will operate at the desired frequency of operation. In this circuit all elements are balanced. Since the interelectrode capacitances are in series in a push-pull oscillator, the effective capacitance shunting the circuit is half that for a single tube. (See following illustration.) Thus, the charging current for this amount of capacitance is reduced with a consequent reduction of capacitive circulating currents. As a result, tube seal heating effects and circuit losses are also reduced. Since the tubes operate alternately and the currents are opposite, losses resulting

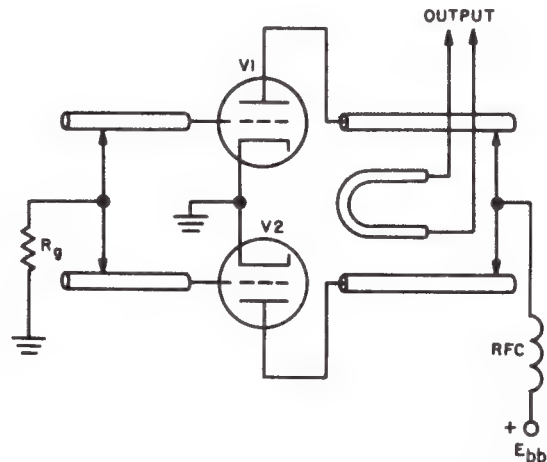
from eddy currents and radiation from the lecher lines are reduced. Such reduction is due to the complete balance in the circuit and the close line spacing which causes the electromagnetic field around one line to almost completely cancel that around the other. Since the same voltages are present on both grid bars and on both plate bars, shorting bars can be used.



Push-Pull Lecher Line Oscillator

For best efficiency and stability at ultra high frequencies, not only the tube losses but also the losses in associated circuits must be kept as low as possible. On the other hand, both the loaded Q and the unloaded Q must be kept high as possible. For this reason, the tuned circuits associated with UHF oscillators use resonant sections of transmission line, rather than coil and capacitor tank combinations.

Since the coaxial line is a form of transmission line, it has properties similar to the open-wire type. At high frequencies it has the further advantage of shielding the line, because the center conductor is entirely surrounded by the shield. As a result, coaxial lines reduce radiation and eddy current losses to an absolute minimum, and for this reason are used extensively. A typical coaxial type of lecher line oscillator is shown in the following illustration.

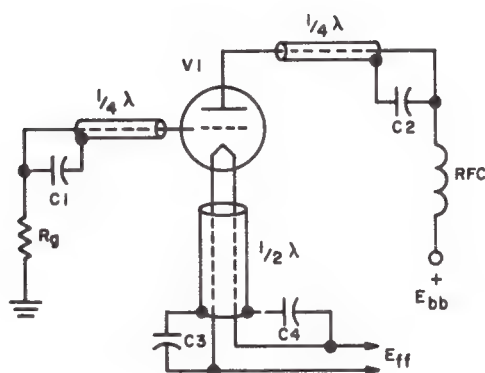

Coaxial Line Oscillator

In this type of oscillator, the grid and plate coaxial lines are shorted by small capacitors, C1 and C2, and have an effective length of one quarter wave each. This oscillator corresponds to a tuned-plate, tuned-grid LC oscillator with series plate feed and grid-leak bias. The filament type of tube shown utilizes the transforming action of a half-wave line section to bypass the filament to ground. At low frequencies the filament would be directly bypassed to ground with a capacitor. At the UHF region, however, this method of bypassing proves ineffective because the filament leads are long enough to offer a large inductive reactance. As a result of the transformer action in the half-wave line, connecting C3 and C4 to the far end of the line provides an effective shunt at the filament *inside the tube*, which ordinarily is inaccessible. Since the length of the line includes the filament leads, the physical length of the external line is slightly shorter than a half-wavelength.

Failure Analysis.

No Output. Lack of supply voltage, a defective tube, an open circuit, or improper tuning can cause loss of output. Resistance and voltage checks will quickly reveal lack of circuit continuity or incorrect voltage conditions. The trouble then may be either in the tube or tuning. If the circuit will not tune and the plate current is excessively high or low, the tube is defective. Lack of contact in the shorting bar is then most probable, since it is possible to have a low dc resistance or continuity indication and a high r-f resistance which will not show on an ohmmeter. The usual troubles in this type of unit are open or high-resistance circuits due to poor solder joints or defec-

tive components. Most line sections are mechanically and electrically of excellent construction. It is possible, however, for silver-plated components to develop a heavy oxide film which effectively open-circuits them at UHF, particularly in areas where corrosive vapors react with the silver. In this case, frequent cleaning is necessary, or gold plating may be required.

Low Output. Low plate supply voltage, together with reduced tube emission, is the primary cause of low output. A check of voltages will detect this type of trouble. Improper tuning can also result in reduced output; it can be eliminated by a slight readjustment of the shorting bars for maximum output. Defective contacts in the shorting bars are usually obvious, causing erratic indications as the bars are moved slightly back and forth. A high-resistance grid leak can also reduce the amplitude of oscillations, but it is easily located by a resistance check. In the open-wire unshielded line, it is also possible for nearby objects to produce capacitive unbalance and mistuning. If this effect is present, the plate meter will show a change in current as the hands or other objects are moved near the tuning controls.

Incorrect Frequency. This type of oscillator is adjustable over a sufficiently broad range that normal plate voltage changes or slight emission changes may be compensated for by tuning. Since the stability is determined by the tuned lines, any large frequency change indicates a defect in the tuning of the lines. This can be caused by poor contact resistance of the shorting bar and by defective shorting capacitors. Reflected load reactance can also affect the circuit operation; this condition is normally indicated by a return of the frequency to original value as the load is adjusted. A lecher line circuit is usually so stable that calibration markings ruled on the line itself can be used to accurately determine the line frequency. Normally, a resistance analysis and voltage checks should quickly reveal the component at fault.

MAGNETRON OSCILLATOR

Applications.

The magnetron oscillator is used in the region of 100 MHz to 30 GHz and beyond, to develop r-f energy. It is used in test equipment, in low-power CW transmitters, in beacons, and particularly in radar equipment, as a source of high-power pulsed r-f energy.

Characteristics.

Utilizes a specially constructed tube with a resonator surrounded by a permanent magnetic field to produce the r-f energy.

Operates with grounded anode.

Is usually operated by a negative pulse applied to the cathode.


Has either coaxial or waveguide output, depending upon the frequency of operation.

Circuit Analysis.

General. There are, generally speaking, two types of magnetrons: the split-anode *negative resistance* (or *dynatron*) type, and the *transit-time* (or *electronic*) type. The negative resistance type uses the principle of negative resistance between the two anodes to produce oscillation, and operates only at frequencies which are low with respect to the transit-time frequency (on the order of 100 MHz to 1000 MHz). The efficiency is low in comparison with the efficiency obtainable with transit-time operation; therefore, it is not very popular, being more or less supplanted by the power type klystron at these frequencies. The frequency of oscillation in this type of magnetron is controlled entirely by the resonator with which it is used, as in conventional LC oscillators. On the other hand, the *transit-time* type of magnetron depends entirely upon the transit time to determine the frequency, with the resonator(s) providing greater efficiency and proper phasing for maximum output. A short treatment of the negative resistance type of magnetron is given below for the sake of completeness, with the remainder of the discussion devoted to transit-time magnetrons, which are in greater use.


Circuit Operation. Before discussing the two types of circuits, it is necessary to establish the fundamentals of operation. The accompanying figure shows

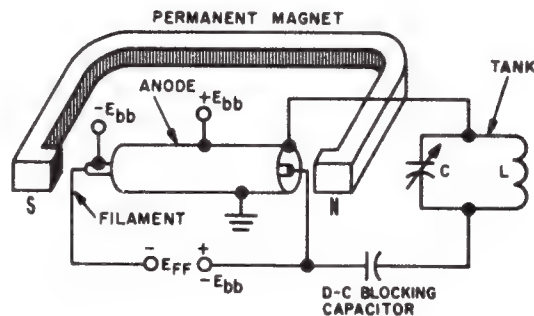a simple magnetron. As can be seen, the tube is a diode with a cylindrical plate surrounding a coaxial



Elementary Magnetron




cathode or filament. A negative voltage is applied to the cathode, in addition to the heater voltage needed for filament emission or heating of the cathode, depending upon whether direct or indirect heating (filament) is used. Because the plate is positive with respect to the cathode, an electrical field exists between cathode and plate (anode); an external dc magnetic field is placed perpendicular to the electric field, and is produced by a strong permanent magnet. See the following illustration. (While an electromagnet could be used and the magnetic field could be alternating, as well, this is done only on the low frequencies for special effects, and will not be discussed further.) In these discussions it is assumed that the magnetic field is produced by a permanent magnet. The tuned tank circuit in which the oscillations take place is connected between the plate and the cathode. This can be a tuned LC circuit, a coaxial cavity, or a special cavity resonator built into the tube.

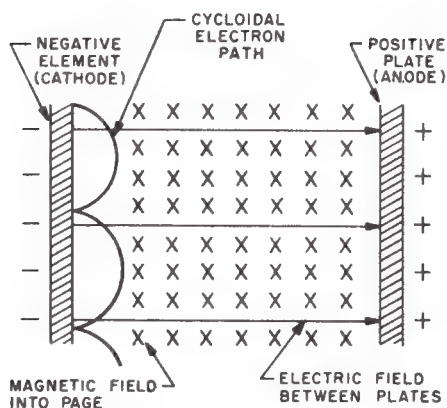

Motion of Electron in Electric and Magnetic Fields

Consider now the effect of the electric field on the electrons emitted from the cathode. In the absence of the permanent magnet field there would be a continuous electron flow in all directions, radially, direct from the cathode to the plate. But with the magnetic field applied, as the electrons are attracted toward the plate they encounter a force (due to the magnetic field) that tends to push them in a direction perpendicular to the forces applied. Since two fields are involved, the plate-to-cathode-voltage induced electric field and the permanent magnet field, and since they are at right angles with respect to each other, the electrons are affected by the vector sum of these forces; with a strong enough field the electrons are deflected in a cycloidal path as shown in the above illustration. Thus they are effectively bent back toward the cathode. The following illustration shows the path followed by a single electron as the external magnetic field is increased. At some low value of field (A in the figure), the electron travels in a slightly curved path, but reaches the anode. At the critical value of field (B in the figure), the electron just grazes the plate and returns to the cathode. When the field exceeds the critical value (C in the figure), the elec-

tron follows a smaller-diameter circular path and returns to the cathode without getting near the plate.

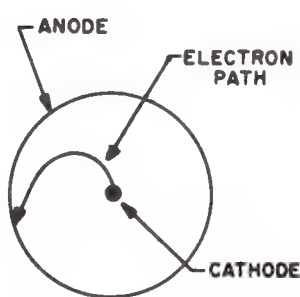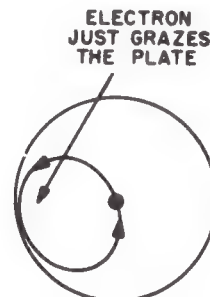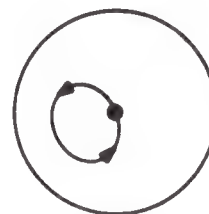A
WEAK FIELDB
CRITICAL FIELDC
STRONG FIELD

Electron Path with Increasing Magnetic Field

The current flow of the magnetron for the previous conditions is shown, perhaps more clearly, by the following graph. With the low value field a constant flow of current occurs between anode and cathode until the critical field value is reached, whereupon the current abruptly ceases and drops off to zero, since the electron can no longer reach the plate. The useful point of operation is where the electron is just prevented from reaching the plate by the critical

field value. Oscillation is then produced by the current induced in the cavity or resonator by the electron movement.


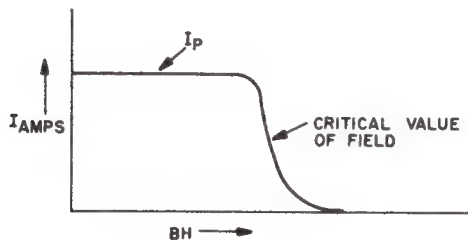


Plate Current vs Field Strength

While the actual electron flow in a magnetron is complicated, it is evident that since an electron is basically a negative charge of electricity, as it approaches an electrode it will change the field distribution around the electrode, inducing a positive charge and causing current flow within or on the electrode by electrostatic induction. As it recedes, a negative change will be induced. If the electron reaches the electrode it will be absorbed, and current will cease. When positive and negative charges are induced in a resonator, current flows alternately back and forth within the resonator, at the frequency to which it is tuned (resonant), and r-f oscillations are thereby produced. This is the simple basic principle by virtue of which the magnetron operates.

Negative Resistance Magnetron. The negative resistance magnetron is a variation of the basic magnetron using a split anode. It is capable of operating at a higher frequency (than the single plate magnetron) and with higher output. Its general construction is similar to the basic magnetron, except that it has a split plate, as shown in the accompanying figure. These half-plates are operated at different potentials by connecting them to opposite ends of a tuned tank circuit (or cavity). When the tank circuit is oscillating, the voltage on one half-plate is increased, while that

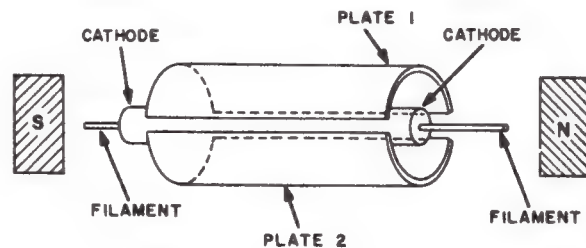on the other half-plate is decreased by an equal amount. This results in a different electron trajectory.



Split-Anode Magnetron

A graph of the plate current versus plate voltage characteristics of one segment of a two-segment magnetron, showing four different values of voltage applied to the other segment, is shown in the accompanying figure. Note that for each voltage there is a negative slope to the curve where the current is reducing as the voltage applied to the segment is increasing. Likewise, a curve of the difference current to the two segments of a split-anode magnetron as a function of the difference in the potential of the two segments when the voltage on one segment is raised as the other segment potential is lowered a like amount shows the same effect, that is, a negative slope. From the earlier discussion on negative resistance oscillators (see contents list under Electronic Oscillators for location), it can be seen that this curve bears a resemblance to the typical lazy "S" type curve that indicates negative resistance. Therefore this tube will produce oscillations of the negative resistance type if a parallel-tuned tank is series connected, either from one segment to the cathode or between the two segments. A schematic showing the tank connected between the two segments is shown in the following figure; this is a typical so-called *push-pull magnetron* circuit (from its resemblance to the push-pull type electron tube circuit.)


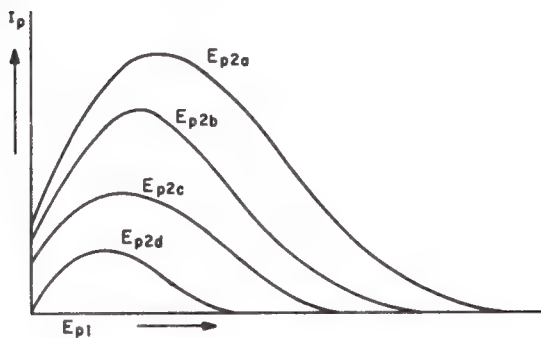


Plate Current vs Plate Voltage Characteristic

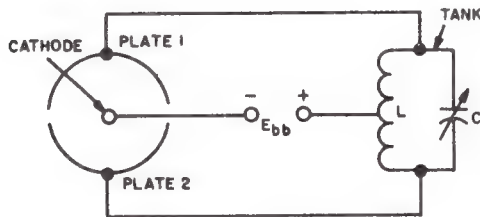
Consider now the effect of the different potential fields between the segments and the cathode. In the quiescent or static condition, since the plate potential is applied equally through the tank coil, as shown in the following illustration, the dc field



Push-Pull Magnetron Circuit

between the cathode and either segment is of equal strength. Once shock-excited (by application of $B+$), a transient oscillation is produced to increase the potential on one segment and decrease the potential on the other segment by a like amount. Thus the field is stronger in one half of the area around the cathode than in the other half. By applying the external permanent magnet field so that it is perpendicular to the cathode, a cycloidal motion is imparted to the single electron in a manner similar to that described in the basic magnetron discussion. The effect of the distorted field, however, is to cause the electron to make a number of revolutions before eventually being attracted to the segment with the lower potential as explained below. This action occurs because after the initial deflection by the field in a particular path of

motion, the electron passes the split between the two plates and enters the electrostatic field set up by the lower-potential plate. Here the magnetic field has a stronger effect on the electron (since the electric field is weaker), and causes it to be deflected with a smaller radius of curvature. As the split is passed again (on the opposite side of the cathode) and the electron once again enters the higher-potential field area, it is again caused to deflect with a change in the radius of curvature. Thus the electron continues to make a series of loops through the magnetic and electric fields until it finally hits the low-potential plate and is absorbed. The following figure shows the effects of different potentials on the motion.

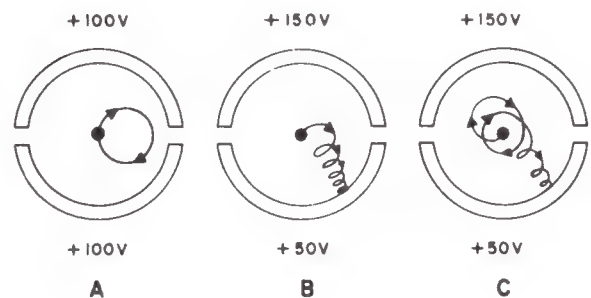


Electron Transit Paths

In part A the fields are equal, with the permanent magnetic field below the critical value. In B and C the field is above the critical value and current flows because of the action just discussed. Two different electron paths are shown for clarity. Actually, it has been found that optimum efficiency is obtained when the electron makes approximately 10 revolutions before contacting the anode. Since oscillation is produced by the negative resistance effect, the tank frequency governs the path of the electron and transit time is maximized. Naturally, this can happen only at the lower frequencies. As the frequency of operation is increased, the transit time eventually becomes the important limiting parameter, and the negative resistance oscillation is ineffective. Since a very concentrated field is required for the negative-resistance magnetron oscillator, the length of the tube plate is limited to a few centimeters for a magnet of reasonable dimensions. In addition, a small-size tube is required to make the magnetron operate efficiently at

UHF. Therefore, the plate size (area) is limited, and produces a serious limitation on the permissible plate heat dissipation. For this reason, heavy-walled plates are necessary to increase the heat radiating properties, and artificial air or water cooling is necessary for high-power operation. These parameters, in effect, are the limitations which restrict its use to the low-frequency end of the UHF spectrum and cause the transit-time magnetron to be in greater demand.

With the electrons traveling in numerous loops, there are bound to be collisions between electrons and bombarding of the filament (or cathode), producing secondary emission and in some cases even destruction of the filament or cathode. This action is cumulative, and sometimes results in filament burn-out before the current can be reduced to a safe value. To minimize this effect, and to prevent unstable operation, the tubes are operated with reduced plate and filament voltage. In some tubes it is possible to use the electron bombardment of the cathode element to provide the heat for emission, once oscillation is started.

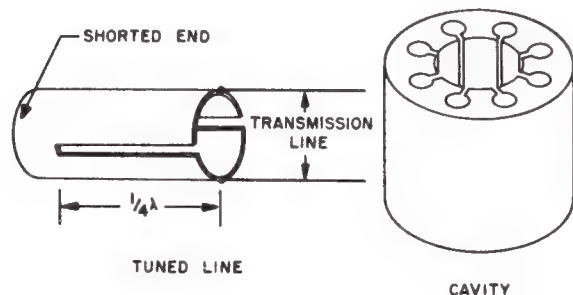Transit Time Magnetron. In this type of magnetron the plate or anode block is usually constructed so that it functions as a tank circuit resonant to a particular frequency. The construction may be that of a simple shorted quarter-wave line resonator, as shown in the accompanying illustration, or as a multi-cavity resonator also illustrated.



Magnetron Tank Circuits

In either case there are no external tank circuits to be tuned, and the output of the magnetron is picked up by a transmission line with coupling loop (or aperture for waveguide) built into the tube. Usually, the anode is composed of more than two segments; as

many as eight or more are often used (while as many as 64 cavities have been used). While this type of magnetron has a reasonably high efficiency (30 to 60 percent) and large output, it is limited in that the frequency of oscillation is fixed by the resonator. Thus it tends to be supplied as a single-frequency unit which usually has provisions for tuning over a limited range (on the order of 1% at 9 GHz), and is operated at a fixed frequency. The average power is limited by the filament emission, and the peak power is limited by the maximum voltage it can safely withstand without damage. Actually, during initial operation the high-power magnetron arcs from plate to cathode, and must be properly adjusted by a process known as *seasoning*, after which it can handle the high voltage properly without damage (within limitations).

New magnetrons require an initial break-in period or seasoning because violent internal arcing occurs when they are first put into operation. Actually, arcing or sparking in small magnetrons, and in high power magnetrons is very common. It occurs with a new tube or after long periods of idleness once a tube has been seasoned. One of the prime causes is the liberation of gas from the tube elements during idle periods. Arcs are also caused by the presence of sharp surfaces in the tube, mode shifting, and by overworking the cathode (drawing excessive current). While the cathode can withstand considerable arcing for short periods of time, if continued excessively it will shorten the useful life of the magnetron and can quickly destroy it. Hence each time the excessive arcing occurs, the tube must be seasoned again until the arcing ceases and the tube is stabilized.

The seasoning procedure is relatively simple. The magnetron voltage is raised from a low value unit until arcing occurs several times a second. The voltage is left at that value until the arcing dies out. Then the voltage is raised further until arcing again occurs, and is left at the value until the arcing again dies out. Whenever the arcing becomes very violent and resembles a continuous arc the applied voltage is excessive and is reduced to permit the magnetron to recover. Once recovered the procedure is again continued. When normal rated voltage is reached and the magnetron remains stable at the rated current value, the seasoning is completed. It is good maintenance practice to season magnetrons left idle either in the equipment, or held as spares, when long periods of non-operating time have accumulated. Follow the

recommended procedures and times for seasoning specified in the equipment technical manuals. The preceding information is general and of an informational nature only.

The outputs of pulsed magnetrons are on the order of megawatts, with an average power of not much more than 1000 to 2000 watts being usable for CW operation (a typical 3-megawatt pulsed radar has a 6-kw average rating). However, as the state of the art changes, these limitations also change; thus where 50 kw was once high power, 5 to 10 megawatts now represents high power.

The construction of transit-time magnetrons is varied; they operate in the VHF, UHF, and SHF regions. Some are not tunable, while others are voltage tunable (anode potential is varied), mechanically tunable by hand or by motor, or are fixed-tuned. They provide power outputs of 50 to 100 milliwatts for receiver operation, and in the megawatt region for high-power radars, with all ranges of in-between powers. They are provided with integral built-in permanent magnets or with external magnets. They are supplied with transmission line outputs or wave-guide outputs, or with transition type coaxial-to-wave-guide outputs. They are of glass-metal or ceramic-metal construction, with advantages claimed for each. Cooling is achieved directly by natural air draft for low powers, by forced air or liquid air-convection, or by heat exchangers for the high-powered types. It is evident, therefore, that the subject of magnetrons covers a large field, with a complexity far beyond the scope of this technical manual. Thus, in the following discussion sufficient detail is provided to insure a basic understanding of the general principles of operation, with the important principles emphasized or expanded as needed. For details on a specific type of magnetron, consult the manufacturer's specifications, and refer to a more comprehensive text for further information.


Detailed Analysis. The magnetron, while capable of generating continuous-wave oscillations, is particularly suited for pulsed power applications, as in radar. That is, the magnetron is capable of producing pulsed powers of more than 1000 times greater than the best c-w output at the same frequency. Basically, there are three factors which produce the favorable conditions for pulsed powers; the magnetron is more efficient at very high levels of power and voltage; an oxide cathode under pulsed operation produces currents over 100 times greater than that obtainable

under dc (non-pulsed or CW) conditions; and finally, by pulsing with small duty cycles, anode heat dissipation is less of a problem, so that greater powers can be handled. On the other hand, a new problem is posed, where the build-up of oscillations from noise to full power must occur reliably for every pulse in a time that may be as short as one-hundredth of a microsecond. Failure of this build-up produces misfiring or mode changing, and often occurs under the proper conditions.

From the preceding discussion it is clearly seen that the understanding of pulsed operation involves new concepts, some entirely different from those in CW operation. Since the magnetron consists basically of an emission system involving electron flow, plus resonators (or cavities) which modify the electron flow, and a means of extracting the r-f output, a discussion of the functioning of each of these items logically leads to a better understanding of the magnetron oscillator.

First consider the emission system, which may be a straight filament, a coiled filament, or an oxide-coated cathode cylinder. Magnetrons using thoriated tungsten or pure tungsten filaments are generally operated at high temperature; because of their ruggedness, these filaments are suitable for c-w type tubes, but consume considerable filament power. The low-temperature, oxide-coated filaments operate best for pulsed-type tubes, producing much larger emissions than the high-temperature type (for a given filament power). However, since they are not as rugged, they are more susceptible to damage from electron bombardment and deterioration effects. The oxide-coated cathode cylinder provides the most practical construction for low-temperature operation; keeping the heater filament independent of the operating circuit avoids any filament inductance effects which might adversely affect the frequency of operation. Another type of operation is also possible with the cathode sleeve, namely, cold-cathode operation. Because of the extremely high secondary emission produced by electron bombardment of the cathode by electrons out of the useful orbit, once started by heated-cathode operation, cold-cathode operation may be obtained by lowering the heater voltage or by removing it entirely. Such operation is commonly used in high-powered magnetrons, operating with extremely high plate voltages and heavy electron bombardment of the cathode.

Since it is desired that the electrons travel in the interspace area between the anode and cathode of the cavity block and thus contribute to the excitation of the various cavities, end shields are placed at the ends of the cathode. These shields, which are of various designs (some may be only small protuberances at the ends of the cathode), minimize the electron leakage paths at the ends of the cathode. These cathode end shields are considered to operate by producing a retarding electrostatic field at the ends of the interspace area. By distorting the equipotential lines at this point in such a way as to produce an inwardly directed force upon the electrons attempting to leak out of the area, they simply urge the electrons toward the center plane of the anode block. While in some cases secondary electrons may also be emitted from the end shields, through bombardment by partially controlled electrons in orbit, the useful electron emission is usually restricted to the cathode alone. An exaggerated illustration of end shields and the retarding field they produce is shown in the following illustration.

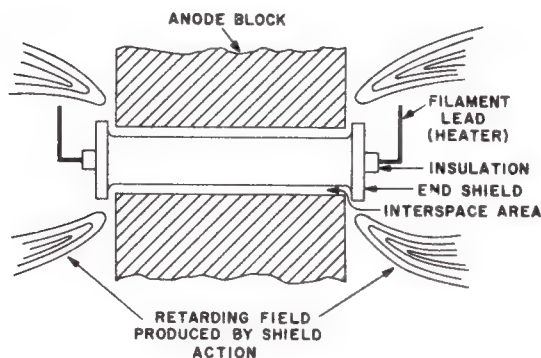


Cathode End Shields

With the cathode emitting a stream of electrons into the interaction space, let us examine the method by which the electrons produce oscillation. A half-section of a typical eight-cavity anode is shown in the following illustration, with the fields and current flow as indicated.

Assume for the initial operation that the cavities have been excited by an r-f field so that each cavity is oscillating. In the capacitive space between the walls of the entrance to the cavity (slot) a charge exists, with one wall negative and the other wall positive. By

construction, the segments are placed 180 degrees apart electrically (pi mode), so that when traveling from one cavity to the other in the interaction space, each cavity is oppositely polarized. Thus the original negative-to-positive charge in cavity 1 is now a positive-to-negative charge in cavity 2, and likewise for the other cavities around the interaction space. A complete cycle of rotation around the anode block is produced in 360 degrees of rotation or some multiple thereof. In the case illustrated, since there are eight cavities (only half are shown) and the phase shift between the cavities is 180 degrees, there is a total of 8 pi radians shift which, when divided by 2 pi (for one full 360° of rotation), gives a number of 4. This arbitrary number is called a *mode* number. As might be surmised, magnetrons can be constructed so that they will operate at a different number of modes for the same frequency.

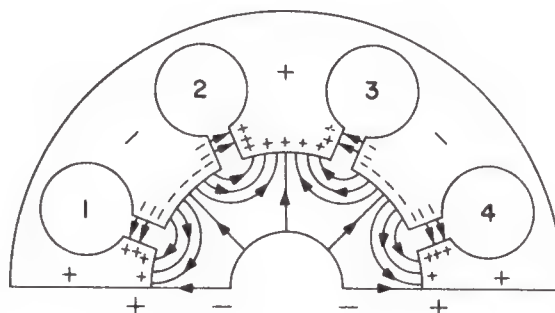

Development of Internal Fields


Examine the illustration and observe the effect of the fields produced. First the r-f field at the entrance to the cavity is strong at the lip but weaker as it extends into the interaction space, as shown by the widely separated lines. Arrows indicate field direction. The straight lines between the anode and cathode represent the dc field produced electrostatically by the anode-to-cathode potential. The dc field is steady except where reinforced or reduced by the changing r-f field. The permanent magnet field is at right angles to it (into the page), and is not shown. Thus two fields are always present in the cavity, and the resulting field affecting the electrons is the vector sum of the two.

Recalling from basic magnetron theory that when an electron approaches an anode it induces a positive

charge, and as it recedes from the anode it induces a negative charge. It is evident that as an electron approaches an anode which is going positive (because of the r-f cavity field), that segment is made more positive, aiding cavity oscillations. If the electron recedes from the anode as it is going negative, oscillations also will be aided. On the other hand, if the electron approaches the anode as it is swinging negative, or recedes as it swings positive, the electron tends to oppose oscillations. If sufficient electrons were so phased, oscillation would stop. Therefore, to sustain oscillation the phasing must be such as to produce more aiding than opposing electrons, or to remove those that oppose the oscillation, retaining only those that aid.


In addition to the r-f fields existing because of cavity resonance, assume that the magnetic field is just slightly greater than the cutoff value. Therefore, if the r-f oscillating field did not exist, or were zero at a point in the interaction space, the electron emitted at the cathode would be returned by the effect of the dc magnetic field. On the other hand, when r-f field is going positive, the electric field is enhanced, and an electron emitted at a point affected by this field would be attracted toward the anode. Because of the effects of the two fields, the electron is forced to travel in a cycloidal path instead of straight, and around the interaction space in a clockwise or counterclockwise direction (depending on the polarity of the magnet). If the distance between the cavity segments is such that the electron traverses the space between adjacent slots in a time equal to one-half cycle of r-f oscillation, when the second slot is reached the electric field will be reversed (the next half-cycle of r-f oscillation is now starting) and will be in an aiding direction. Because of the curved path, however, the *working* electron is traveling in a long path and through a decreasing potential (since the potential through which it falls is less as it approaches the anode). The result is a change in phase of such a nature that by the time the electron approaches the third slot the polarity is opposing and repels the elec-

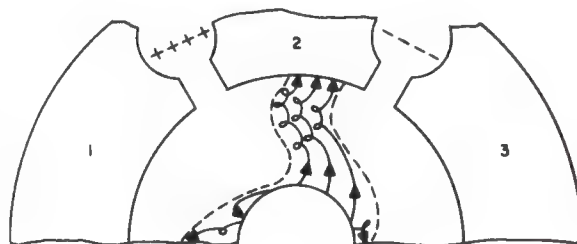tron. Thus the electron is forced to curve back upon itself, and, by the time it is traveling towards the direction from whence it started, the field in segment 2 is again attracting it, and it again curves toward the



Electron Path

anode. Likewise, because of the curved path it enters the number 1 segment field when the field is in a direction that pushes it back toward the number 2 and 3 segments. In this way the working electron follows a series of looped paths between two segments, as shown in the preceding figure until it reaches the anode. During the time it is being attracted by the field, it effectively aids oscillation in that cavity just as if an additional charge were induced into it. Because of the curved path it is in an aiding condition longer than it is in a position where it removes energy from the cavity; therefore, the net result is to enhance the oscillations. Since the distance traversed between segments is effectively 180 degrees, the electron is operating in the pi mode. Thus in an eight-cavity magnetron, four pairs of segments are operating simultaneously, and the effect is the same as that existing in a polyphase motor; that is, an effective traveling field is produced which rotates around the circumference of the interaction space, and oscillation is successively enhanced in each cavity as the field rotates past the slot. The effect is as though a wheel of four spokes were being rotated, as shown in the following figure.

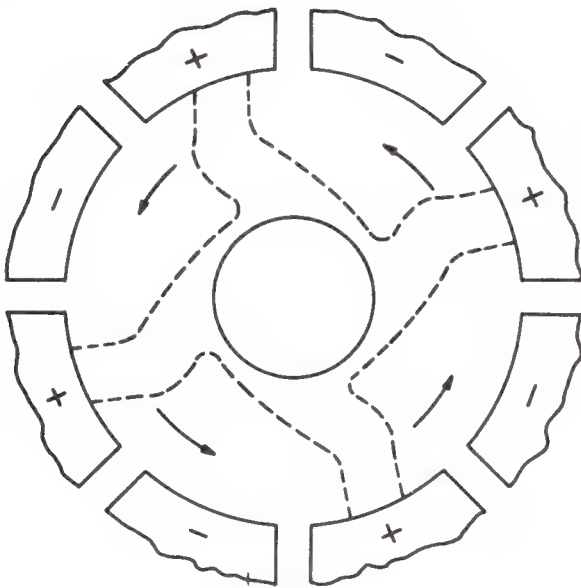

Rotating Electron Field


Conversely, the *non-working* electron is emitted at a time during which the r-f field opposes it and is quickly directed back to the cathode. This is a harmful electron in that it strikes the cathode with considerable force and tends to destroy it. Since the *back radiation* cannot be eliminated, it is used to produce secondary electrons and economize on filament heating.

Since there are electrons emitted from all points on the cathode, there are electrons which start at intermediate points of changing field, and are not attracted or repelled as strongly as the working electron; therefore, their paths are of different orbits. However, since the r-f field varies sinusoidally with time, the result is that the electron emitted before the working electron is retarded until the electron emitted after the working electron catches up. For this reason there is an effective electron density grouping (or bunching) about the working electron, or a *velocity modulation* effect similar to that in the klystron. Thus standard waves similar to those on traveling wave tubes are caused to exist in the inter-action space.

While the r-f field was initially assumed, it is produced by application of the anode voltage or negative cathode driving pulse, which is sufficient to shock-excite the cavities, and with the proper phasing oscil-


lations are built up. This proper phasing is produced through construction and by the proper selection of anode voltages and field strength. Since the phasing of magnetrons is a highly technical subject and of concern only to the designer, it is beyond the scope of this technical manual and will not be discussed.

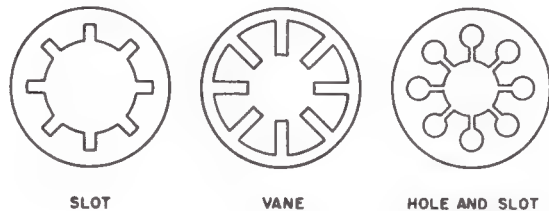Types of Cavities and Modes. There are basically, three different types of cavities used in unstrapped resonant systems; these are the slot, the vane, and the hole-and-slot types of side resonators shown in the following figure.



Types of Resonators

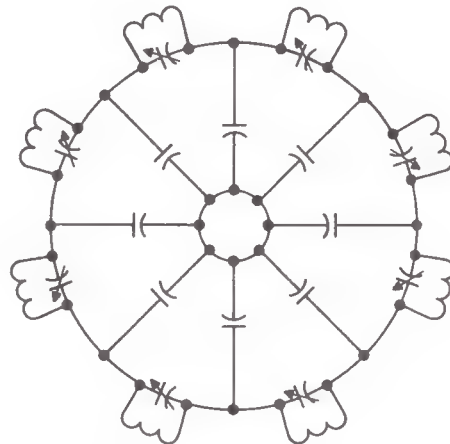
Regardless of the type of resonator used, it is primarily the simple equivalent of a parallel LC tuned circuit, which can be represented schematically by a series of tank, as shown in the following illustration, the interaction space is represented by capacitance between the anode and cathode; inductive effects are neglected for simplicity.



Resonator Equivalent Schematic

While the resonators are shown connected in series, actually each one is independent and is dimensioned and shaped so that all are resonant to the same frequency (identically shaped resonators are used). They are coupled together by the interaction space between the cathode and anode. The spacing of the cavity entrances is approximately a half-wave at the desired frequency of operation (assuming the pi mode of operation). Therefore, the smallest number of cavities that are operable is two (2×180 equals 360 degrees), corresponding to split-plate usage. The maximum number of cavities is limited only by construction since multiplication by two produces the same result (2, 4, 8, 16, 24, and up to 64 as a practical limit).

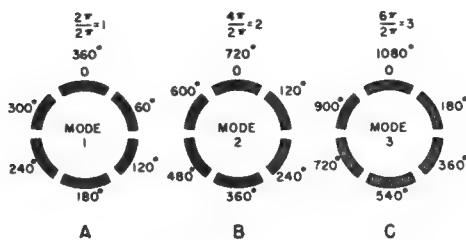Consider now the mode of operation. Assume a basic six-cavity magnetron, as shown in the following illustration; operation is possible in three types of modes, as shown.




Examples of Various Modes

In part A of the figure there is a phasing of 60 degrees between adjacent segments. Therefore, six segments must be traversed before a total phase rotation of 360 degrees (one cycle) is obtained. Since there are 2 Pi radians in 360 degrees by angular measure, this represents a rotation of 2 Pi radians divided by 2 Pi, or mode 1. In part B of the figure the segments are separated 120 degrees, and only one-half as many segments (three segments) need be traversed to produce a complete cycle of operation. When the complete cycle around the magnetron is traversed, a total of 720 degrees of rotation is completed (two complete cycles of operation), or 4 Pi, giving mode 2. In part C of the figure adjacent segments are oppositely polarized, so that only two segments need be traversed to complete a cycle. Therefore, in a complete rotation of the magnetron cavity, 1080 degrees

of rotation is produced, or 6 Pi radians divided by 2 Pi, giving mode 3.


Since a six-cavity magnetron can operate in at least three modes (with either leading or lagging phase, this represents 2×3 modes, or a total of 1 mode for each cavity), there is a frequency for each of these modes at which the output is a maximum. Thus the magnetron generates a series of discrete frequencies arranged symmetrically (in the ideal case) around a center frequency of maximum amplitude for each mode. A typical plot of wavelength variation with mode for typical magnetron is shown in the following graph.

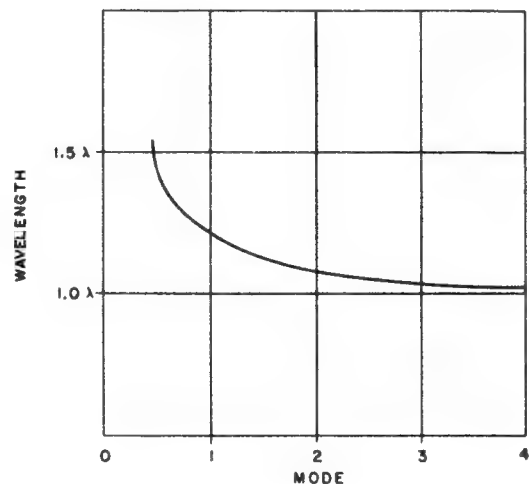

Wavelength vs Mode Variations

The c-w magnetron provides a different output from that of the pulsed magnetron, in that a steady anode voltage is supplied, and the output is mainly concentrated at the mode chosen by the plate voltage and current applied. It still does not consist of a single frequency, however, since the cavity at microwave frequencies can support a number of different types of oscillation. This concept is diametrically opposed to the normal concept of a tuned tank being responsive to only one frequency. It is true, however, because the magnetron consists not of a single cavity, but of a number of cavities, each coupled to the other. As in coupled circuits at the lower frequencies, it is possible to achieve a response curve having a main lobe with numerous side lobes, depending upon the interaction and amount of coupling between the

cavities. This condition is further complicated by the possibility of phased bunching of electrons in the interaction space; thus it can be clearly seen that a single pure frequency output is rather unlikely. In the tunable types of magnetrons, the main spectrum can be shifted to the desired frequency by tuning. In the fixed-tuned magnetron, operation consists mainly of operating at the proper current, which for a pulse of a particular shape produces the desired main lobe at the proper frequency with a minimum of side lobes (other modes). A typical output spectrum for a pulsed magnetron is shown in the accompanying figure.

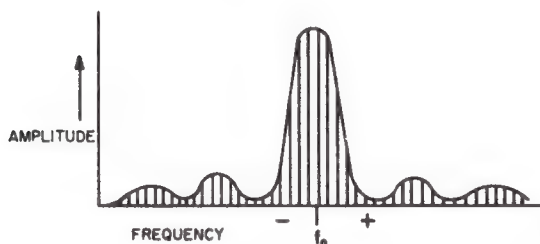


Typical Magnetron Spectrum

The broad spectrum shown is caused mainly by pulsing. Because the pulse is a rectangle with steeply sloping sides, it approximates a square wave with a similar harmonic content. Thus, in effect, many frequencies are induced into the cavities, and all those to which it responds will be present. The shape of the anode pulse is important, since it can cause a distorted output and place the main output energy in an unwanted portion of the spectrum. It should also be understood that this discussion is necessarily general since it concerns actions mostly of interest to the designer. The technician is concerned with making the magnetron perform as designed. He can control only the voltages applied and the currents at which it is operated, plus any cavity tuning which may be possible. Therefore, the preceding discussion of modes and spectrum effects is intended to indicate, in a very limited manner, internal operation effects which are highly complex and beyond the scope of this circuit analysis. The interested reader is referred to standard texts such as the Radiation Laboratory volume on

Microwave Magnetrons, from which much of this material was selected.

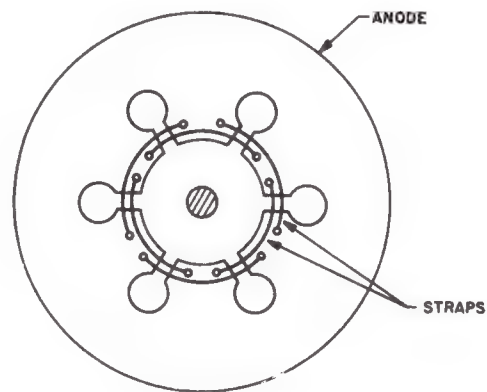Since the unstrapped magnetron presents a number of modes of nearly equal outputs, it has been discarded for the *strapped* type, and for a special type known as the *rising sun* magnetron because of the design of the cavity. Strapping consists of connecting together alternate segments with short, heavy conductors, as shown in the accompanying figure. Thus




Double Ring Strapping

strapping favors mode 3, the Pi mode, and places alternate segments at the same potential (which corresponds to a shift of 2π radians). Operation at mode 2 is impossible, since it would require a shift of $4/3\pi$ radians between alternate segments, and cannot occur with the segments short-circuited. While the straps are essentially simple short circuits, at the frequencies used they have inductance; moreover, since the straps pass near the segments which they connect, they also have capacitance. As a result, the frequency of the mode of operation is slightly altered. At the Pi mode the straps are at the same potentials at the ends, and carry no current (except for a slight capacitive current between them); therefore, the inductance is negligible and the capacitive effect predominates, lowering the basic frequency of the Pi mode. When the magnetron is excited in a different mode, there is a difference in potential between the segments, causing the straps to carry more current between them because of the difference in potentials. Thus both inductive and capacitive

effects operate on the other modes, changing their operating frequency. The result is to further separate the modes and eliminate the possibility of simultaneous operation on two closely spaced modes. Suppression of the unwanted modes increases the over-all efficiency of the magnetron. While it might appear that the symmetry of strapping is essential, this is not so in practice. Actually, by omitting certain straps (usually the ones at the output resonator and adjacent to the input cathode), even greater discrimination is obtained.


The rising sun magnetron design evolved from the fact that symmetry is not required for best results in strapping. The typical design of alternate cavities of the same shape, with adjacent cavities of dissimilar shape, produced the so-called "rising sun" design. Since the sizes of the cavities in the two groups are different, the mode frequencies of this type of magnetron tends to form into two groups as though there were only two resonators. Thus the respective mode frequencies are well separated from the Pi mode, and this unit is suitable for Pi mode operation without the use of strapping. The rising sun design is used at the higher frequencies (above 10 GHz), while strapping with the conventional design is used at the lower frequencies to provide a smaller assembly. A typical rising sun design is shown in the following illustration.

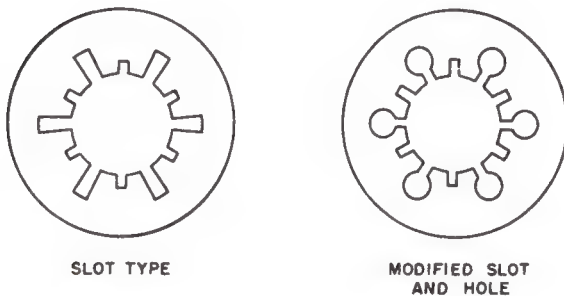

Rising Sun Magnetron


Coupling Methods. F-R energy is usually removed from the magnetron by means of a coupling loop. At frequencies lower than 3 cm the coupling loop is made by bending the inner conductor of a coaxial line into a loop (center-fed coupling) and soldering

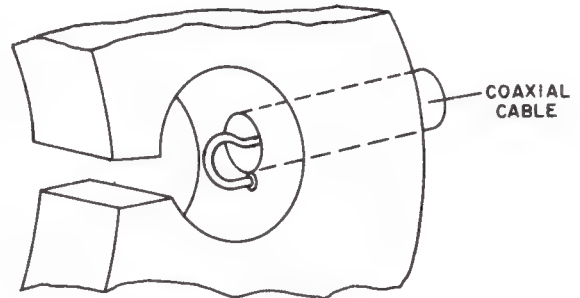the end to the outer conductor, so that the loop projects into the cavity, as shown in the following figure.



Coaxial (center-fed) Coupling Loop

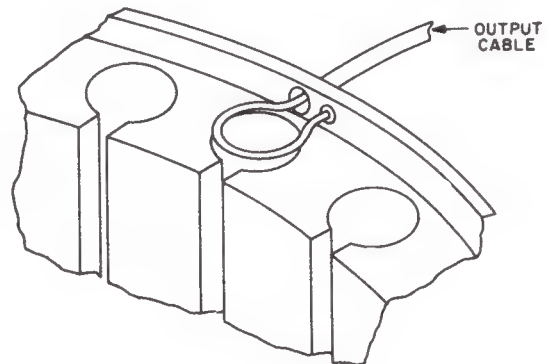At the higher frequencies to obtain sufficient pickup the loop is located at the end of the cavity (halo loop), as shown in the accompanying illustration.





External (halo) Coupling Loop

Other forms of inductive couplings are shown in the following illustration.

In the segment-fed loop it is presumed to intercept the flux passing between cavities, while the strap-fed loop intercepts the energy picked up between the strap and the segment. On the output side, the coaxial line feeds another coax line directly, or it feeds a waveguide through a choke joint, with the vacuum seal at the inner conductor helping to support the

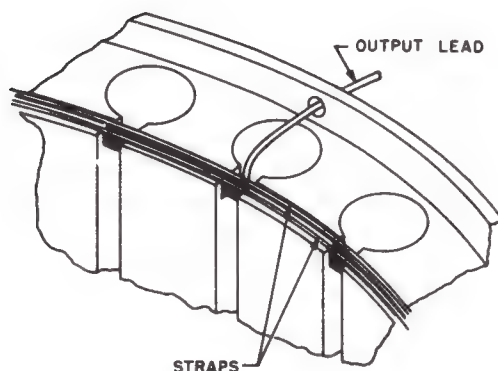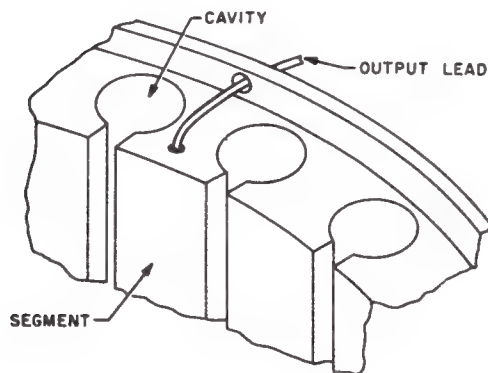line. Direct waveguide connection is usually through a slot in the back of the cavity, with an iris feeding into the waveguide connector through a window.



Segment-Fed Coupling

Strap-Fed Coupling

Tuning. The magnetron is basically fixed-tuned. It is pretuned by adjusting the straps, pressing them in or out to resonate with a test voltage inserted into the cavity from a klystron at the desired operating frequency; the adjustment is made for maximum response on a detector-indicator. Some magnetrons have a flexible plate arranged to move in or out by means of a screw adjustment. Still other magnetrons have pins or rods that screw in or out of the cavities (as in the klystron), and some low-powered types are voltage-tuned. Usually, pretuning is necessary before the magnetron is placed in operation; therefore, some form of mechanical tuning which can be externally performed over a small range tuning which can be externally performed over a small range is used to

adjust it to the desired operating frequency. (Of course, this frequency must be within a specified band of frequencies over which the magnetron is designed to be operable.) Thus in most cases the magnetron output frequency is essentially fixed, with the receiver having its bandpass and frequency automatically centered and maintained in synchronism with the transmitting magnetron.

Failure Analysis.

No Output. Lack of output can be caused by non-oscillation of the magnetron, or by oscillation on an undesired mode which will not couple to the output circuit; it can also be caused by a short circuit or an open circuit. Use of the ammeters and voltmeters supplied with the equipment will usually pinpoint the trouble. A steady high current with low applied anode voltage usually indicates a loss of magnetism which allows the electrons to pass directly from cathode to anode. In this case, remagnetization or replacement of the magnets will generally restore operation. (Sometimes insertion and reinsertion of the small soft iron bar placed between the magnet poles during storage, known as the keeper, a few times will restore the magnet.) An anode-to-cathode short will produce heavy plate current and blow fuses or operate protective circuits immediately after the plate voltage is applied. Such a condition will be indicated by a simple ohmmeter check between the anode and cathode, *with the voltages removed*.

An erratic heavy plate current, usually accompanied by noise and internal flashes within the magnetron (seen through the coupling ports or at visible portions of the glass envelope), particularly in high-power magnetrons, indicates arcing. This is a common occurrence after periods of long idleness or after exceeding the permissible ratings; it can also be caused by land changes or discontinuities in choke or rotating joints, producing excessive r-f reflections. Immediate reduction of plate voltage is imperative to prevent damage to the magnetron or modulator equipment. Then, by following the normal *seasoning* process, the arcing should occur less frequently until the magnetron stabilizes and resumes normal operation.

If there is no output until a number of starting attempts have been made and the output then builds up slowly, this is a possible indication of an open filament. Particularly with extremely high-powered tubes using very high voltages, the phenomenon of

cold cathode operation can occur through the *back bombardment* effect. Checking the filament for continuity *with the plate voltage removed* will quickly determine whether this condition exists.

Since magnetrons are expensive and usually do not plug in as conveniently as common receiving tubes, replacement of the magnetron should be resorted to only after all other checks have been made. Where the current meter indicates zero, it is most probably an open circuit caused by cathode burnout, an open anode or cathode lead, or failure of the modulator or power supply. Checking with the voltmeters provided on the equipment will quickly determine whether the power supply and modulator are normal; if they are, the open must be between these units or within the magnetron. A resistance check for continuity of connections will indicate whether the condition is external to, or within, the magnetron. Do not overlook resetting any overload relays or replacing open fuses in the search.

Reduced Output. Reduction of output below normal is usually more difficult to analyze than lack of output, since the magnetron is very susceptible to variations in the strength of its magnetic field, anode voltage, and load impedance. Such variations cause a loss of output power and efficiency to a large extent, and usually affect the frequency of operation. A shift in the mode of operation can usually be caused by any of the previously mentioned items, and, since the magnetron is normally designed to operate at a particular frequency with maximum output, reduced output may indicate such a condition. Perhaps the best method of trouble shooting is to use a spectrum analyzer such as the echo box, detector, and meter, or by direct observation of the r-f envelope on an oscilloscope. Since the shape of the high-voltage modulator pulse is important, using a portable spectrum analyzer connected via a directional coupler to the magnetron output will save time. Double moding will be indicated by the presence of two or more maximum lobes. A jittering pulse which changes in amplitude or wiggles back and forth is immediately apparent. Changes in load can be made and the effect observed and evaluated. Likewise, the anode voltage can be varied and its effects observed; any frequency instability will be evident. The effect of reduced output will be obvious from local meter indications in the case of c-w magnetron type of operation, but they are not as accurate and are sometimes actually

misleading in pulsed operation. A change in current or voltage will show immediately in the steady voltage type of c-w operation. However, in pulsed operation, where the pulse width and duty cycle govern the average value of the current and voltage, a change in pulse width may compensate for a change in duty cycle (or vice versa); thus the pulsed indications may appear normal, when actually there is a reduction in efficiency and output power. Low power output usually results from a weak magnetron or low modulator output. If the modulator pulse is normal, the trouble lies in the magnetron. A weak magnet will cause a loss of power, by reducing the efficiency of operation, and also a change in the spectrum, which is usually obvious on the oscilloscope. For further information, test, and typical waveforms, refer to *Test Methods and Practices*, NAVSHIPS 0967-000-0130, of the EIMB.

Incorrect Frequency. While magnetron troubles may be divided into three general classifications, namely, wrong frequency, poor spectrum, and low output, they are usually interlinked. For example, a magnetron operating off frequency will most probably show a poor spectrum and produce a lower output, as compared with previously recorded data obtained when the magnetron was known to be operating correctly. In the case of wrong frequency operation for fixed-tuned magnetrons, there are three possible causes. The magnetron may be defective, or frequency pulling or pushing may be present. Frequency pulling may be present because of some fault in the r-f system, such as varying impedance, faulty rotating joints, or be caused by a strong reflection from a nearby object. A change in magnetron frequency due to a change in *load impedance* is known as "pulling". The effect of pulling is greatest at high output powers. The operating point of a magnetron is usually a compromise between high output power and good frequency stability, and is usually chosen for a matched load condition. Magnetron performance is often summed up in what is called the *pulling figure*. This figure is the total change in frequency (usually in MHz) which occurs when the load is adjusted to produce a voltage-standing-wave ratio of 1.5:1, and the phase of the reflection is varied through 360 degrees.

When off-frequency operation occurs and another magnetron is substituted, satisfactory operation of the replacement does not necessarily indicate that the

original magnetron is defective. In some cases a magnetron may be in good condition, but because of individual difference it may be more easily pulled outside the operating band by external conditions (such as a change in load impedance) than another magnetron of the same type number. Blind replacement of the magnetron when off-frequency operation occurs, therefore may result in the discarding of a perfectly good tube. The VSWR of the r-f system should first be checked to determine whether it is high or low. With a low VSWR, normal operation of the r-f system is indicated, and the fault is most likely the magnetron. Sometimes the effects of pulling are not noticed if the frequency is within the operating band, so that occasional off-frequency operation is possible without any visible external indications. Frequency pushing (indicated by waveform distortion) may be present because of improper anode or filament voltage. Magnetron *pushing*, caused by a change in dc anode voltage, is frequently indicated by a poor spectrum shape; this condition results from improper modulator pulse amplitude or shape. The frequency of operation may be slightly altered, or may change from pulse to pulse. Although such operation may be indicated by a changing anode current, a more definite check can be made by use of an oscilloscope.

Magnetron pushing is usually produced by a change of input conditions. The pushing figure is usually expressed in terms of megacycles per second per ampere. In most cases pushing can be neglected for the longer wavelengths where it is slight. It cannot, however, be neglected at the shorter wavelengths. Regardless of the cause of the frequency change, in the case of the tunable magnetron, only a slight adjustment of the tuning control to establish the desired frequency may be all that is required.

When frequencies appear and disappear in the spectrum, the cause is usually arcing, which produces temporary transients. If this condition occurs frequently, seasoning is necessary; there is also the possibility that the magnetron is becoming unstable and approaching the end of its useful life. If it occurs infrequently, operation can be considered normal, but there is the possibility of incipient magnetron failure.

REFLEX KLYSTRON OSCILLATOR

Applications.

The reflex klystron is used as a low-power r-f oscillator in the microwave region (from 1000 MHz to 10,000 MHz) in receivers, test equipment, and low-power transmitters.

Characteristics.

Uses special tube construction to produce r-f feedback and oscillation.

Operates as a positive grid oscillator.

Uses a tuned cavity, either integral (built-in) or external, to determine the basic range of operation.

Uses negative anode (repeller-plate) voltage.

Circuit Analysis.

General. A klystron tube is a specially constructed electron tube using the properties of *transit time* and velocity modulation of the electron beam to produce microwave frequency operation. It can be used as an oscillator or an amplifier. The amplifier employs two or more cavities to produce the proper bunching of electrons, upon which its function and amplifying properties are based. The amplifier type of klystron can produce a large amount of power (up to megawatts) and can be used as an oscillator if proper feedback arrangements are made. However, the reflex klystron offers a simple type of feedback arrangement and performs specifically as a special tube designed for oscillator operation alone. Although the power output of the reflex klystron is limited, it is adequate for receiving and test equipment functions and for low-power transmitters. Where high power is required, it can be achieved by using the reflex klystron as a master oscillator and the conventional amplifier type klystron as a power amplifier. Since microwave radiation is limited to line-of-sight distances, the reflex klystron usually furnishes sufficient power for these relatively short rf transmission paths.

Generally speaking, although the efficiency of the klystron is low as compared with efficiencies obtainable with conventional tubes at the lower frequencies (on the order of 30% as compared with 60%), it is


more efficient than the other types of high-frequency generators in the microwave region. The negative grid tetrode provides approximately the same efficiency at 500 MHz, but its output drops to zero around 1500 MHz; similarly, the lighthouse tube covers a range of from 800 MHz to 2500 or 3000 MHz with comparable efficiencies and then its output drops off; the multicavity klystron, however, is operable up to 10,000 MHz and beyond with efficiencies not less than 10%. In this respect, the reflex klystron offers the lowest efficiency (on the order of 2 or 3 percent) mostly because of its simplicity of construction. For example, the use of more cavities to provide better bunching would give higher efficiency. Actually, the klystron is the only device other than the magnetron (and perhaps the travelling wave tube) which offers practical operation on the microwave frequencies; it is simpler and cheaper than the magnetron (or TWT) and more flexible in its applications, which is the reason for its popular use. Present trends indicate that the reflex klystron will be replaced for high-power operation by the two- or three-cavity klystron, but for simplicity and economy for low-power applications the reflex klystron is more practical.

The klystron has a large power gain than the negative grid tube at the higher frequencies because the tetrode primarily has a smaller cathode area, is limited in the amount of plate voltage that can be applied, and has greater r-f losses. The advantages of the klystron accrue because the cathode is not limited in size but can be made as large as necessary, and, being outside the rf field in the tube, it is unaffected by radio-frequency bombardment or other deleterious effects. Although the negative grid tube has a closely spaced grid and plate (to reduce transit time effects), and distance between the anode and the cathode in the klystron is large (on the order of one inch), permitting larger applied plate voltage before breakdown occurs. Since there is no grid structure in the klystron to heat and cause losses (actually, grids are sometimes used, but are very rugged) and the collector is located outside the r-f field and designed solely to dissipate heat, better efficiency results. The major loss in the klystron is dielectric loss (such as the loss produced by windows in cavities for waveguide couplings), as well as wall absorption. Thus, the r-f gain is limited only by the small r-f input cavity loss and by beam loading of the output cavity. Normally there is no negative feedback to be overcome by virtue of interelectrode couplings, as in the

negative grid tube, since the input and output cavities are isolated. In the case of the reflex klystron, positive feedback is obtained by the use of a repeller electrode so that only one cavity is required.

In the preceding discussion, a number of generalities were made to bring out the inherent differences between negative grid tubes and the klystron. Since the subject of klystrons and their design considerations cover a large field, which is beyond the scope of this text, and since there are so many variations between different products, it is possible that exceptions to some of the generalities can be made. In fact, considering reflex klystrons alone as a small branch of a large family of klystron tubes, there are a number of variations in design from type to type. Therefore, the interested reader is referred to other texts for specific data on a particular type or design, and the generalities made herein should be viewed broadly. The discussion that follows will be restricted to basic principles which can be applied to any type of tube.

The operation of the klystron is predicated upon the development of *velocity modulation* of the electron beam; that is, the velocity of the electron beam is controlled to produce a grouping or bunching of electrons. These bunches of electrons are then passed through grids or cavities to produce oscillations at the desired frequency by direct excitation of the cavities. A basic *klystron* (not reflex type) is shown in the following illustration to establish the fundamental principle of operation. As shown in the figure, a

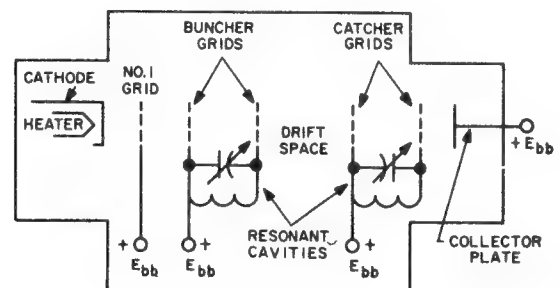

Basic Klystron

heater is used to produce electron emission from a cathode. The electrons from the cathode are attracted to the accelerator grid (No. 1), which is at a positive

potential with respect to the cathode. The accelerator grid may be a flat grid structure or an annular ring (cylinder or sleeve) through which the electrons pass unhindered. Assume that this attraction produces a constant-velocity electron beam, which is further attracted to the next electrode, the buncher grids (or cavity), and then to the next electrode, the catcher grids (or cavity), also at a higher positive potential. If the output from the catcher is fed back to the buncher, and if the proper phase and energy relations are maintained between the buncher and the catcher, the tube will operate as an oscillator. The collector plate, which is also at a positive potential, serves only to collect the electrons which pass the catcher. Successful operation requires that the energy needed for bunching be less than that delivered to the catcher. Amplifying action is obtained because the electrons pass through the buncher in a continuous stream and are effectively grouped so that they pass through the catcher in definite bunches or groups as explained in the following paragraphs.


Bunching is produced by applying an alternating voltage to the buncher grids (produced by excitation of the buncher resonator by the passing electron beam). Assuming that a sine-wave voltage is produced and applied between the buncher grids, it is evident that on the positive alternation the buncher grid nearest the catcher effectively has its positive potential increased, and therefore further accelerates the electron flow. On the negative alternation, the same buncher grid voltage is made less positive and the electron stream is slowed down. Since a continuous stream of electron enters the bunching grids, the number of electrons accelerated by the alternating field between the buncher grids on one half-cycle of operation is equalled almost exactly by the number of electrons decelerated on the negative half-cycle. Therefore, the net energy exchange between the electron stream and the buncher is zero over a complete cycle of alternation, except for the losses that occur in the tuned circuit (cavity) of the buncher.

After passing through the buncher grids, the electrons move through the *drift space* in the tube with velocities which have been determined by their transit through the buncher grids. Since in a conventional klystron the drift space is free of any fields, at some point in this drift space the electrons which were accelerated will catch up with these which were previously decelerated (in a prior passage) to form a bunch. The catcher grids are placed at this point of

bunching (determined by frequency and transit time), to extract r-f energy from the bunched electrons.

At the catcher a different situation exists. Since the electrons are traveling in bunches, spaced so that they enter the catcher field only when the oscillating circuit is in its decelerating half cycle, more energy is delivered to the catcher than is taken from it. The remaining electrons in the beam pass through the grid and travel to the collector plate, where they are absorbed.

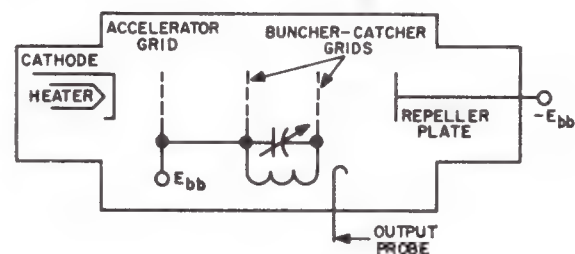In the *reflex klystron*, the catcher grids are replaced by a repeller plate, to which a negative potential is applied, as illustrated in the accompanying figure.




Reflex Klystron

In this type of klystron, the electron beam is also velocity-modulated, and, by proper adjustment of the negative voltage on the repeller plate, the electrons which have passed the bunching field may be made to pass through the resonator again (in the reverse direction) at the proper time to deliver energy to this circuit. Thus, the feedback necessary to produce oscillation is obtained and the tube construction is simplified. Spent electrons are removed from the tube by the positive accelerator grid (when used) or by the grids of the positive buncher cavity. Energy is coupled out of the cavity by means of a one-turn hairpin coupling loop. The operating frequency can be varied over a small range by changing the negative potential applied to the repeller, because this potential determines the transit time of the electrons between their first and second passages through the resonator. Since maximum output depends upon the fact that the electrons must return through the resonator at just the time when they are bunched and at exactly the decelerating half-cycle of oscillating resonator grid voltage, the output is more dependent

than the frequency upon the repeller potential; therefore, the amount of tuning provided by varying the repeller voltage is limited. Usually the volume of the resonator cavity is changed (by mechanical tuning) to make a coarse adjustment of the oscillator frequency, and the repeller voltage is varied over a narrow range to make a fine adjustment of the frequency (electronic tuning) consistent with good output. Since the same grids perform the dual function of bunching and catching in the reflex klystron, they are frequently referred to as the *buncher-catcher grids*. Because of the variation of frequency with accelerating voltage, it is difficult to achieve linear amplitude modulation with a klystron. Frequency modulation may be readily accomplished, however, by introducing a small modulating voltage at the cathode or repeller. The tuned circuit used in the reflex klystron is a cavity resonator, which has a very high Q . Depending upon the tube type, the cavity may be an integral cavity (built into the tube) or an external cavity (clamped around the tube). Several methods are used to tune cavity resonators. Capacitive tuning is provided by mechanical varying the grid gap spacing; inductive tuning is provided by moving screw plugs in or out of the cavity (this changes the volume, making it either smaller and tuned to a higher frequency, or larger and tuned to a lower frequency). In some instances thermal tuning is used by applying heat to grid gap to produce capacitive variations. Several types of output couplings are used, but the coupling loop is the most popular type. Capacitive probe coupling is often used with the external type of cavity because construction difficulties do not readily permit the use of coupling loops with this type of cavity. At frequencies above 10,000 MHz waveguides are employed, and the output is coupled to the waveguide through a window or aperture.

Detailed Analysis. In the practical klystron, the function of the accelerating grid is provided by the cavity, which is maintained at a positive potential sufficiently strong to produce the initial effect of accelerating the electrons to a constant velocity. A focus electrode, in the form of a cylinder connected to the cathode, is also provided to confine and effectively focus the electrons into a narrow beam. Focusing is achieved electrostatically without any external control. Any electrons which travel outside the beam are intercepted and removed, while those within the beam are attracted by the strong positive cavity field and accelerated uniformly. A typical

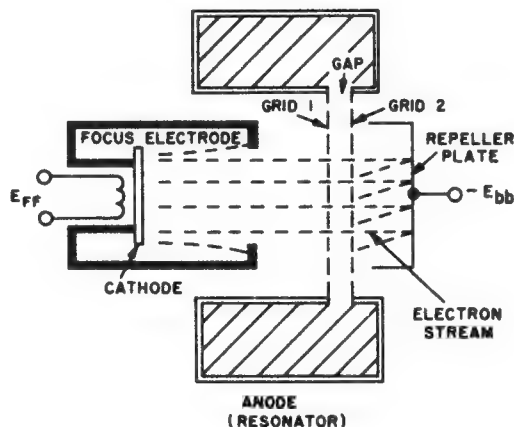
reflex klystron, showing the focusing electrode and the cavity structure, is illustrated in the accompanying figure.



Practical Reflex Klystron

Note the particular shape of the cavity, which has a post-shaped center hole. As a result of this construction, the cavity is very narrow at the point (the gap) where the electrons pass through it. The narrow gap is necessary for proper operation since the transit time through the cavity must be much less than the time for a complete cycle at the frequency of operation. Beyond the center hole the cavity is much larger. The portion of the cavity at the gap where the ends are close together may be considered capacitive in effect, and the remaining portions, where the capacitance is small, may be considered inductive in effect. Consider now the operation of velocity modulation. Since the cavity is developed as a quarter wave coaxial resonator, the input and output ends are at opposite polarities. Also, the current distribution is approximately uniform at the center, where the beam passage takes place. Hence, in the gap a uniform electric field is produced. The passage of the electron beam through this field will distort the field and cause energy to be absorbed from the beam. Thus, the cavity is excited, and it oscillates at a frequency determined by its dimensions. These oscillations produce opposite polarities at the entrance (grid 1) and exit (grid 2) grids, because the sides of the cavity are exactly one quarter wavelength apart at the operating frequency. By virtue of resonance and the use of a high- Q cavity, the r-f oscillations develop a large

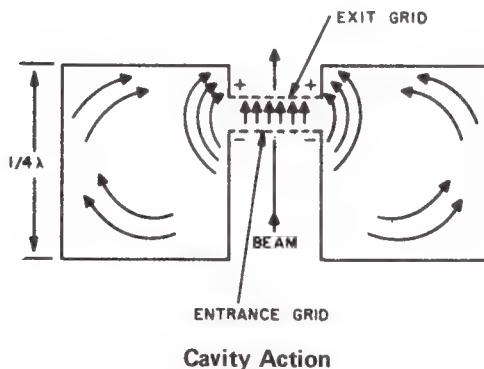
instantaneous voltage, which on the positive alternation places the exit grid at a more positive potential than the entrance grid. As a result, the exit grid is polarized in the proper direction to attract the electron beam and increase the electron beam velocity. See the following illustration for a representation of the cavity action.



On the negative alternation the beam is opposed and effectively slowed down. At and near the change-over points, the ac oscillation voltage is practically zero so that the beam is not affected and it passes through with the initial velocity. The alternate acceleration and deceleration of the beam, together with the ineffective period of no change produces a bunching of the electrons. (In effect, the bunches of electrons occur at a period equal to the frequency of oscillation. Thus, actual density modulation is produced, resulting in an alternating current varying in strength at the frequency of operation, which when absorbed by a resonant cavity will cause rf oscillations.)

Before the electrons with different accelerations are completely bunched, they enter into the repeller-plate field, which is negative and repels the electrons. An electron which was accelerated by the field at the cavity grids will penetrate the electric field at the repeller plate to a greater depth than one which was accelerated less or not at all, and will require a longer time to return to the cavity. Thus, bunching can be achieved by adjustment of the repeller plate voltage to the optimum value. When the voltage is optimized, bunches are formed at the cavity by those electrons

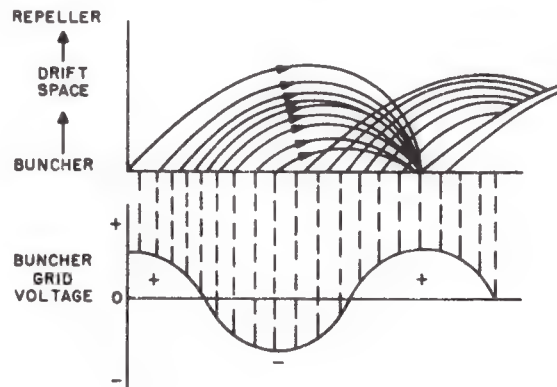which were accelerated meeting those which were not accelerated, but which passed through the gap at a later time, and also by those decelerated electrons which passed through at a still later time. A typical Applegate diagram illustrating the bunching effect is shown in the accompanying figure.




Applegate Diagram

To more clearly understand buncher and catcher operation, we shall review the operation of the two-cavity type of tube. Action is based upon the fact that electrons will give up energy when slowed down, and absorb energy when accelerated. In order for an electron to give up the greatest amount of energy to the catcher, it is necessary that the electron arrive at the center of the catcher at the instant when the electric field at the center of the catcher has its maximum negative (retarding) value. Similarly, in order for a symmetrical group of electrons to deliver as much energy as possible, the center of the group must arrive at the center of the catcher when the catcher field has its maximum negative value. Since the electron at the center of the group is the one that passed the center of the buncher at the instant when the buncher field was changing from negative to positive, the time s/v_0 required by this electron to move through the distance s from the center of the buncher to the center of the catcher, must be equal to the time interval between the zero of the buncher fields and a negative maximum of the catcher field, as shown in the following figure. It is evident from

examination of the illustration that for maximum energy transfer, the catcher field must lag the buncher field by the angle

$$\frac{s}{v_o} \times \frac{2\pi}{T} + 2\pi(\frac{1}{4} - n),$$

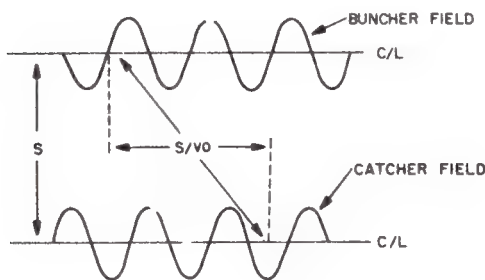where T is the period of the field and n is any integer.




Buncher-Catcher Phase Relationships

Up to this point nothing has been said regarding the means by which the catcher is kept in oscillation. The motion of an electron through a cavity resonator sets up an electromagnetic field within the resonator. In a klystron the electrons pass through the catcher in bunches; therefore, the fields resulting from individual electrons will, for the most part, reinforce each other and thus produce a resultant field of appreciable magnitude. Because the bunches pass through the catcher at time intervals equal to the natural period of oscillation of the catcher, the catcher is set into oscillation. Since the amplitude of oscillation can build up only if the catcher gains energy, the oscillation automatically tends to assume the proper phase relative to the cycle of arrival of electron bunches to result in maximum transfer of energy from the electrons to the catcher. Since the cavity of the reflex klystron acts both as a buncher and a catcher, if an output is to be obtained, the returning electrons must be phased so as to impart energy to the cavity and be absorbed. It is necessary that they approach the cavity when the buncher voltage originally induced is opposing them, or producing deceleration. Therefore, the time taken for a bunch to return to the cavity must be $3/4$ of a cycle of the operating frequency to supply energy by feedback and satisfy the requirements for oscillation. The phasing must be such that


the electrons add energy to the cavity. Therefore, during the first quarter cycle they have not yet returned, and during the second quarter cycle they are in phase opposition (180° apart), but at the $3/4$ cycle they are in phase and will add energy to the cavity. A bunch of electrons which returns to the cavity at a time equal to $3/4$ of a cycle, or any whole number of cycles plus $3/4$ cycle, will supply energy of the proper phase for sustaining oscillations. Thus, oscillations may be obtained at a number of repeller plate voltages for a given frequency setting of the resonator cavity.

Oscillations of maximum amplitude are obtained when the frequency of operation, as determined by the return time of the reflected electrons forming a bunch, coincides with the frequency to which the resonator is tuned. Since only one resonator is used, the tuning of the reflex klystron is relatively simple. Although the frequency of operation for fixed cavity tuning may be varied by changing the repeller voltage, the power output drops off on either side of the cavity frequency because the field of the gap does not provide optimum retardation. The various values of repeller voltage which produce oscillation result in what is known as different *modes* of operation. The most negative repeller voltage for which oscillation results is known as mode 1. Lower values of repeller voltage successively produce the higher modes (2, 3, 4, etc) of operation. A typical output response with repeller voltage variation is illustrated in the following figure.

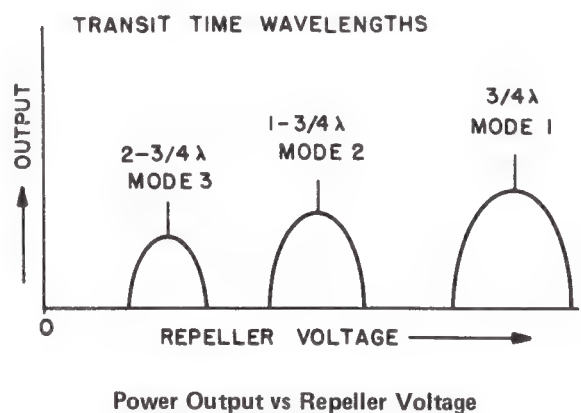

Since the bunching of the electrons for the higher-numbered modes is not so well defined, the net

energy given up by the beam to the resonator field is less, and the output power is smaller, as illustrated. On the other hand, because the bunching is not so well defined, the modes of higher number are tunable over a greater range of frequencies (by adjustment of the repeller voltage). The accompanying illustration of electronic tuning ranges verses modes indicates that for the lower repeller voltages (mode 3) the range of electronic tuning increases but the output decreases.

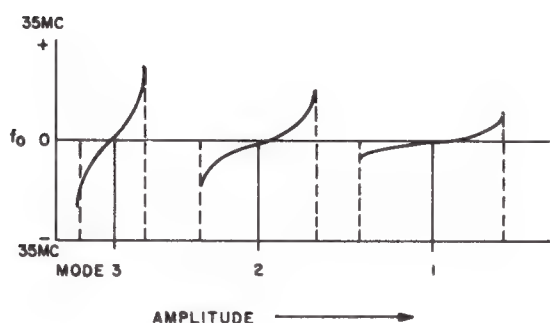

Tuning Ranges vs Modes of Operation

The variation of frequency with changes in the repeller voltage permits the reflex klystron to be used with an automatic-frequency-control circuit, which controls the klystron frequency by lowering (or by increasing) the repeller voltage in the proper direction to compensate for any frequency change. Thus, the circuit can be made self-tuning and provide reasonably good frequency stability, particularly in pulsed operation where voltages and pulse amplitudes change drastically. (See the Special Circuits Section of this handbook for a discussion of the various types of AFC circuits.)

Tuning Methods. The method used for tuning the resonator has an important bearing on the performance of a reflex klystron. Tuning is commonly accomplished by varying the length of the r-f gap, to adjust the capacitive portion of the resonator, although in some tubes the inductive portion is altered. Capacitive tuning requires small motions for large frequency shifts, particularly near the low-frequency end of the tuning range. This extra sensitivity can be either an advantage or a disadvantage depending upon the application. Generally speaking, it creates a problem when temperature compensation

is attempted because there must be considerable reduction of motion by a mechanical linkage between the control knob and the gap itself.

The use of capacitive tuning reduces the range over which reasonable efficiency is obtained. As the frequency is raised by lengthening the gap, the transit angle through the gap increases rapidly because the electrons have farther to go and less time to make the trip. The beam coupling coefficient also drops rapidly at the high frequencies so that the output drops quickly. On the low-frequency side of resonance, a similar drop-off occurs, but it is not so rapid. Since the resonator must incorporate a flexible diaphragm to permit capacitive tuning, problems arise in providing the proper vacuum seal; also, the tube is susceptible to changes caused by strong sound waves impinging on the diaphragm, and to changes in barometric pressure, which cause problems in aeronautical applications.

On the other hand, inductive tuning is usually less sensitive because larger mechanical motions are required to produce the same effect. In radial cavities, screw plugs are used (as many as four to six) for tuning. This method of tuning usually results in a fixed-tuned arrangement because of the mechanical difficulties in providing remote control of a number of plugs. However, since the transit time varies directly with the phase angle, rather than the $3/2$ power as in capacitive tuning, much larger tuning ranges are available with inductive tuning. The largest tuning range (approximately 2 to 1) is provided by a coaxial cavity, but at greatly reduced efficiency (capacitive tuning range is about 0.7 to 1).

Mechanical tuning is usually employed in preference to thermal tuning because of the complexity of the frequency control circuit. Since the thermal motion is usually small, capacitive tuning is practically always used for thermal control. The main drawback of thermal control is thermal inertia, which prevents a rapid response to sudden frequency changes; as a result, overshoot becomes a major problem. In general, thermal tuning is used only for special applications where the simpler types of tuning are inadequate.

Output Coupling. Tubes with integral resonators usually have built-in output circuits that consist basically of a coupling device and an output transmission line. The most common pickup device is an inductive loop formed on the end of a coaxial line

and inserted in a region of the cavity where the magnetic field is high. Aperture coupling, sometimes called *iris* coupling, is also used, but to a lesser extent than the pickup loop. In waveguide applications, the aperture is usually used for simplicity and convenience. For external cavity tubes employing coaxial-line tuners, a capacitive probe is sometimes used.

Failure Analysis.

No Output. Incorrect or no plate voltage can prevent oscillation. An incorrect repeller voltage can usually be re-adjusted (within range of the control) to the proper value, or output frequency may be adjusted by tuning the cavity until the tube operates on some other frequency. Lack of oscillation for all values of repeller voltage and cavity tuning indicates an open circuit, loss of accelerator anode voltage, or a defective tube. With an external cavity klystron, poor electrode contacts can also cause lack of output. A voltage check will quickly indicate whether the potentials are normal. Note: *Although low voltages are used, the cavity is positive while the repeller is negative so both supplies in series provide a possibility of dangerous shock. Observe safety precautions when testing.* A tube with decreasing emission indicates incipient failure by a gradual reduction of plate current, and failure to oscillate at the usual repeller control settings. Such a condition becomes progressively worse over a period of time, and complete failure can be anticipated. Loss of output when automatic frequency control is used can result from failure of the AFC circuits; this type of trouble can be determined by switching to manual and noting whether normal tuning occurs. Since the reflex klystron is an integral unit with only output and supply connections, complete loss of oscillation is usually due to mistuning, loss of supply voltage, or a defective unit.

Reduced Output. In the majority of cases, reduced output is caused by mistuning or lack of proper electrode voltages. Mistuning can usually be corrected by a slight readjustment of the repeller voltage and the cavity tuning unless the tube or supply is defective. There is also a possibility that the output load has changed, requiring a readjustment of the controls. Where stub tuners are employed in the output circuit, reduced output may be caused by improper stub tuning. In either case, a slight readjustment of each of the tuning controls should quickly indicate which is

at fault. Operation on a lower mode due to incorrect supply voltage can be detected by a voltage check; this condition is usually indicated when the controls must be set to a position other than normal for maximum output, or when reduced output is obtained at the optimum adjustment point. If the supply voltages and load are normal, reduced output usually indicates incipient tube failure.

Incorrect Frequency. Slight changes in frequency can usually be corrected by making slight repeller voltage changes and by tuning the cavity. Normally a rough frequency setting is obtained by adjusting the cavity tuning, and a fine frequency setting with optimum output is obtained by adjusting the repeller control. A simple voltage check should indicate whether the repeller and cavity voltages are correct. If the cavity tuning is operable and the repeller voltage is correct, incorrect frequency operation can be caused only by load changes or by a change in the tube cavity mechanism with age. It should be possible to restore the frequency by proper load adjustment. Changes in the mode of operation can be detected by noting whether the tuning range is greater and the output is less. Where AFC circuits are used to maintain the frequency, a shift to manual control will quickly determine whether they are at fault.

Changes in frequency resulting from changes in temperature are usually compensated for by adjustment of the tuning controls; such changes may be caused by localized heating due to improper operation when power type klystrons are used, or by greater than normal ambient temperature changes. When proper operation and normal temperature are restored, the unit should again stabilize at the proper frequency. Unless thermal compensation circuits or devices are provided, it will be necessary to compensate by the use of manual tuning. If continued drift is observed, the tube ratings are probably being exceeded. Where a stable frequency is important, an AFC circuit is usually incorporated. Improper operation of the AFC can be checked by switching to manual operation and observing whether operation is normal.

BACKWARD WAVE (CARCINOTRON) OSCILLATOR

Application.

The carcinotron oscillator is used to supply ultra-high frequency and microwave frequency outputs for transmitting applications.

Characteristics.

Frequency range is from approximately 200 MHz to over 100 GHz.

Output is from a few milliwatts to 150 watts or more.

Efficiency is low, from about 10 to 30 percent.


Output frequency is determined by applied voltage.

An electron gun and magnetic field are used to produce electron bunching.

Circuit Analysis.

General. There are two general types of carciotron in use, the "O" type and the "M" type. The first type uses an electric field to impart kinetic energy to electrons. The kinetic energy of the electron is then extracted by a traveling wave; in the second type, a combination of electric and magnetic fields are used to extract potential energy from the dc field, utilizing electrons as the pivot for this action. Since the O-type is simpler and easier to understand, discussion will be limited to that type. The backward-wave tube is similar to the traveling-wave tube except that basically it is an oscillator rather than an amplifier, and it is the backward component of the traveling wave which produces the action. The typical backward wave oscillator consists of a folded transmission line or waveguide operating in the TE_1 , O mode, constructed so that the waveguide winds back and forth across a center line which produces an axial component of the electric field. The total path length from one end of the tube to the other is on the order of 12 wavelengths, and in a typical tube it will cross the axis about 50 times. An electron beam is directed along the axis through holes in the structure. When this beam has suitable velocity, an interaction occurs between the electron stream traveling from left to right and the backward wave traveling from right to left. This interaction causes energy to be delivered to the backward wave by the electron beam, producing an r-f output.

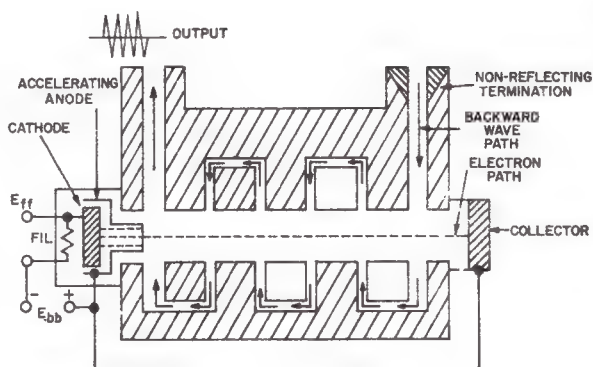Circuit Operation. The schematic of a typical backward oscillator of the folded type is shown in the accompanying illustration.



Folded-Line Backward Wave Oscillator

As can be seen from the illustration, a beam of electrons from an electron gun is directed through a hole in the center of a series of rectangularly folded waveguide sections. The collector electrode is placed at the end opposite the accelerating anode, and a non-reflecting termination is also placed at this end of the waveguide (if it were used as an amplifier this would be the input end). The output is at the electron gun end of the tube. The electron gun is a typical Pierce type, using a filament connected to a cathode and a separate cylindrical accelerating grid or anode. The collector and accelerating anode are connected to a source of positive voltage to attract the electrons from the cathode. Changing this voltage over a ten to one range produces a two to one frequency change which is about the maximum tuning range possible. Backward wave oscillation may also be obtained from a tube using a helix instead of a folded waveguide; in this instance, the circumference of a single turn must be between a quarter and a half wavelength.

Although the Pierce electron gun produces a series of essentially parallel-path electrons, in some tubes there is a tendency for the parallel electrons to be deflected or to stray from the parallel path. This is overcome by adding a solenoid around the envelope of the tube whose axis is in a longitudinal direction.

The focusing field of the solenoid deflects any stray electrons back into the electron stream so that they must travel through the center of the holes in the wave guide. The accelerating anode creates the initial electric field which attracts the electrons from the cathode, while the collector serves to collect the spent electrons after they pass through the waveguide, and return them to the power source. The r-f output is coupled from the waveguide through a probe or an aperture in the end of the waveguide.

Normally, thermal noise produced by current variations in the electron beam produces a noise signal in the waveguide to initiate oscillation. The purpose of the waveguide is to provide a path for the r-f oscillations in proximity to the electron beam, so that interaction can occur between the beam field and the signal field. When a noise signal is generated within the waveguide it is offered a conduction path from the collector back to the cathode end of the tube through which the r-f output current flows. While the electron beam and r-f oscillation (backward wave) signal both travel at the speed of light, and path through the waveguide is longer. Therefore, the backward wave oscillations pass through the waveguide at a much slower speed than the electron, which passes through the center of the waveguide and follows the shorter direct path between cathode and collector. Note that while the electrons flow from left to right, the backward wave travels in the opposite direction from right to left.

When the backward wave oscillation field opposes the field of the electrons passing through the gap at the center of the waveguide, the electrons are decelerated, and are overtaken by other electrons. During the time the beam electrons are decelerated they relinquish kinetic energy to the r-f field which causes them to form in bunches. When the backward oscillation field increases at the gap it enhances the electron field and accelerates the beam electrons, and energy is transferred from the r-f field to the electron beam field. As the oscillating field and electron beam progress in opposite directions through the tube, more bunching occurs. Thus, more beam electrons are available to give up kinetic energy while passing through a decelerating field. Since more time is spent by a beam electron in a decelerating field than in an accelerating field, it gives up more energy to the r-f field than it receives. To ensure the proper phase relationship between the field at the gap and the electron beam, the electron velocity is chosen so that

the total phase difference at the collector end of the tube is approximately one half cycle. Therefore, over most of the length of the tube, the beam electron bunches encounter relatively strong decelerating fields as they cross the gaps. These fields slow down the beam electrons and cause energy to be delivered to the backward wave. If the beam current is sufficiently great self-sustaining oscillations are developed. The amplitude of the backward wave builds up and becomes larger as it progresses from the collector to the gun end of the tube, and passes more and more bunches of beam electrons from which it receives energy. Simultaneously, the beam electron bunching becomes greater as the electrons progress toward the collector. Actually, the backward wave oscillator is a special type of traveling wave tube which characteristically contains a built-in feedback mechanism. In this mechanism, the power generated by a traveling-wave type of interaction is used to supply the signal required at the gun end of the tube to produce bunching of the electron stream.

Failure Analysis.

General. The carcinotron is manufactured as an integral unit and cannot be repaired or altered by the electronic technician. Usually the filament may be observed visually to see if it is illuminated, and the high voltage and beam current may be measured. **WARNING**—be certain to employ all safety precautions since highly dangerous voltages are employed. Always disconnect the power and discharge the circuit with a shorting stick before attaching the voltmeter or ammeter test prods. If normal voltages and currents are obtained but the unit does not oscillate, a higher than normal voltage and beam current may be employed to determine if the tube will oscillate at all. Usually, if normal voltage and current will not produce an output, or produce a much lower than normal output, the tube may be defective. If the tube operates but not on the desired frequency it is possible to increase the frequency by applying higher voltage, or to lower it by reducing the voltage. Such a condition indicates a change in tube characteristics and may be a preliminary indication of incipient failure. Other possibility of trouble could exist; this would be a poor match to the load or a shorting of the load. This possibility can be checked by using a dummy load of the proper value and observing if the output and voltages return to normal.

PART 6-4 BLOCKING AND SHOCK EXCITED

FREE-RUNNING PRF GENERATOR (ELECTRON TUBE)

Application.

The free-running prf generator is a basic blocking oscillator. It produces short-time-duration, large-amplitude pulses for use as timing, synchronizing, or trigger pulses in radar modulators and display indicators.

Characteristics.

Output pulse is a single cycle of oscillation caused by tube conduction at the beginning of each pulse-repetition period.

Pulse-repetition time is determined primarily by the R-C time constant of the grid circuit. The pulse repetition frequency is generally fixed within the range of 200 to 2000 Hz, although the circuit can be arranged to change the R-C time constant and provide for operation at other fixed pulse-repetition frequencies.

Frequency stability is ± 5 percent.


Pulse width and rise time of the output pulse are determined primarily by the transformer characteristics.

Output-pulse polarity is determined by the phasing of the transformer output-tertiary winding. With minor circuit changes, output can also be taken from the cathode circuit.

Circuit Analysis.

General. The free-running blocking oscillator (prf generator) is a special-type oscillator in that the oscillator completes one cycle of operation to produce a pulse and then becomes inactive (blocked) for a considerable period of time, whereupon the cycle of operation to produce a pulse is repeated and the oscillator again becomes inactive. This mode of operation continues, and thus produces a series of output pulses which are of short-time duration, separated by relatively long time intervals.


Circuit Operation. The following circuit schematic illustrates a triode electron tube in a basic free-running blocking oscillator circuit. Transformer T1 provides the necessary coupling between the plate and grid of electron tube V1; terminals 1 and 2 of transformer T1 connect to the plate (primary) winding, terminals 3 and 4 connect to the grid (secondary) winding, and terminals 5 and 6 connect to the output (tertiary) winding. Capacitor C1 and resistor R1 form an R-C circuit to determine the discharge time constant in the grid circuit circuit. The output pulse is taken from the tertiary winding (terminals 5 and 6) of transformer T1.

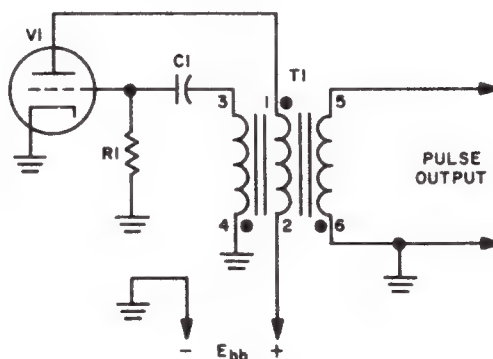

Free-Running PRF Generator

On the circuit schematic, note the placement of small dots near winding terminals 1, 4, and 6 of transformer T1. These dots are used to indicate similar winding polarities. For example, if current flows through the plate windings and terminal 1 is negative, the voltage induced in each of the other windings is such that the dot end is also negative in each winding at the same time; therefore, at this same instant of time, terminals 3 and 5 are positive.

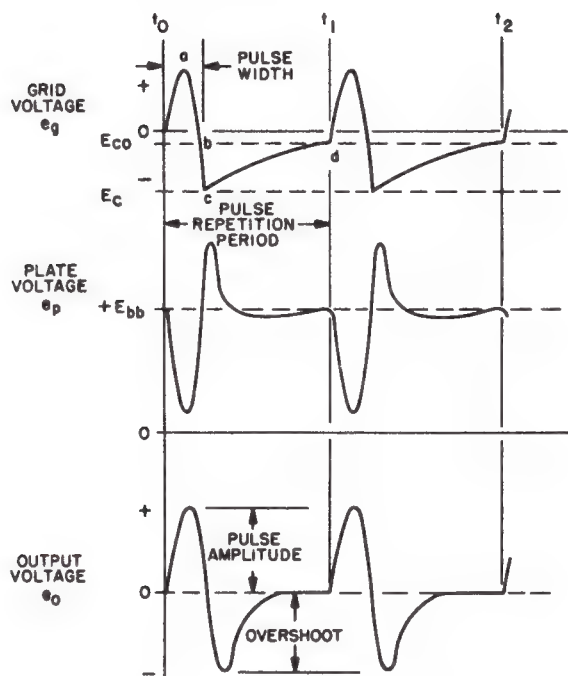For the discussion of circuit operation which follows, refer to the following illustration of the blocking oscillator grid-signal, plate-signal, and output-voltage waveforms.



Theoretical Grid-, Plate-, and Output-Voltage Waveforms

When plate voltage is first applied to the circuit, the grid of V1 is at zero bias and plate current starts to flow through the plate winding (terminals 1 and 2) of transformer T1. A magnetic field is set up about the plate winding and a voltage is induced (through transformer action) in the grid winding (terminals 3 and 4) of transformer T1. Because of the phasing of the plate and grid windings, the voltage produced across the grid winding is impressed on the grid of the tube through coupling capacitor C1 with such polarity as to drive the grid to a positive direction. This results in an increase in the tube plate current, and the action continues with the grid being driven further in the positive direction. When the grid is driven sufficiently positive, the tube begins to draw grid current and capacitor C1 begins to charge. Grid capacitor C1 is charged through the relatively low internal cathode-to-grid resistance of the tube, causing the plate of capacitor C1, which is attached to the grid of V1, to accumulate a surplus of electrons. At this time, however, the plate current has reached its saturation value and the current through the plate

winding of transformer T1 can no longer increase (change); as a result, the voltage induced in the grid winding of the transformer can no longer increase (point *a* on grid-voltage waveform). As a further result, since no induced voltage appears in the grid winding, capacitor C1 starts to discharge through resistor R1 causing the grid potential of V1 to become slightly less positive. This causes the plate current in the plate winding to decrease slightly, accompanied by a decrease in the magnetic field about the plate winding. As the magnetic field begins to collapse, a voltage is induced in the grid winding of a polarity opposite that originally produced; thus, the grid is driven in a negative direction.

As the grid of V1 is driven negative, the plate current continues to decrease and the magnetic field about the plate winding collapses completely. This causes the grid to be driven still further in a negative direction until cutoff is reached (point *b* on waveform) at which time plate current no longer flows through transformer T1.

The highly negative charge existing on capacitor C1 places the grid of V1 below cutoff (point *c* on waveform); then the capacitor slowly discharges through resistor R1 and the grid winding of transformer T1. Since the resistance of the grid winding is low compared to that of the resistor, R1, the resistor is the determining factor in the discharge time of capacitor C1. Furthermore, since the resistance of R1 is large compared to the internal cathode grid resistance of the tube when the grid of V1 is positive, resistor R1 does not affect the charging of capacitor C1.

After an elapsed period of time, as governed by the time constant of R1 and C1, capacitor C1 discharges through resistor R1 to a point near cutoff (point *d* on waveform), where the grid voltage allows the tube to conduct. As plate current once again starts to flow through the plate winding of transformer T1, the entire cycle of operation is repeated.

The changing magnetic field produced about the plate winding of transformer T1 also induces a changing voltage in the tertiary or output winding (terminals 5 and 6). Thus, an output-voltage waveform is produced across the tertiary winding which is similar to the plate-voltage waveform of the blocking oscillator. The pulse output can be of either polarity (with respect to ground) depending upon which terminal of the tertiary winding is grounded. As shown in the

circuit schematic, terminal 6 of T1 is grounded; therefore, the initial output pulse is positive with respect to ground. If desired, limiting or clipping techniques can be applied to the output signal to reduce or eliminate the overshoot (amplitude extreme) in the output waveform. In some instances the desired signal may actually be the overshoot and is used to provide a trigger pulse which is delayed in time by the width of the initial pulse.

The approximate time interval required for the capacitor voltage, E_c , to discharge from maximum to the cutoff value, E_{co} (point *c* to point *d* on the grid-voltage waveform), may be determined by use of the following formula:

$$t \cong 2.30 RC \log \frac{E_c}{E_{co}}$$

Where: t = time interval to discharge to cutoff (seconds)
 E_c = maximum voltage change across capacitor
 E_{co} = negative cutoff value for tube
 R = resistance of grid resistor (megohms)
 C = capacitance of grid-coupling capacitor (μf)

Since the pulse width of the blocking oscillator is usually small compared with the capacitor discharge time, the pulse width may be neglected when approximating the natural operating frequency of the oscillator. The natural operating frequency (Hertz), f_o , can be expressed as the reciprocal of capacitor discharge time; thus, the blocking-oscillator frequency may be approximated using the following formula:

$$f_o \cong \frac{1}{t}$$

Where: t = capacitor discharge time (seconds)

The free-running blocking oscillator, with minor circuit changes, may be synchronized to an external trigger signal by choosing values of $R1$ and $C1$ so that the natural oscillating frequency of the blocking oscillator is slightly lower than the desired frequency. The synchronizing trigger signal, then, must be

slightly above the natural oscillating frequency of the blocking oscillator. Under these conditions, when the tube is held below cutoff, the application of a positive synchronizing pulse will drive the tube into conduction somewhat earlier than the R - C time constant would normally permit. Thus, the oscillator will synchronize its frequency of operation with that of the trigger source and the repetition period of the blocking oscillator will be that of the trigger source.

In a practical blocking-oscillator circuit, resistance $R1$ is usually made up of two resistors: a fixed resistance and a variable resistance connected in series. The variable resistance is then adjusted to provide operation at the desired pulse-repetition frequency. The operating frequency of the blocking oscillator can be changed by switching values of R , C , or both R and C , to alter the time constant. For example, a blocking oscillator designed to operate at 600 pps can be changed to a lower frequency, such as 300 pps, by switching a larger value of R , C , or both, into the circuit to lower the pulse-repetition frequency. Another method of shifting the operating frequency of the blocking oscillator, over a limited range, is to change the quiescent grid voltage of the tube. This method is unaffected by lead resistance, stray capacitance, etc, and is well adapted to remote-control operation.

Important factors affecting the frequency stability of the blocking oscillator are: the stability of grid resistor $R1$ and of capacitor $C1$, the variation or changes in applied filament and plate voltages, and the changes occurring in the electron tube. The circuit is particularly sensitive to changes in filament voltage; a 10 percent decrease in filament voltage may change the oscillator frequency as much as 2 percent, while a 10 percent increase in filament voltage may change the frequency about 1 percent. A change in plate voltage of 10 percent will change the frequency about 1 percent.

Failure Analysis.

No Output. In a nonoscillating condition, negative grid voltage will not be developed; the measured plate voltage at the plate of $V1$ will be below normal because of the steady value of plate current flowing through the plate winding of transformer $T1$ (assuming the plate winding is not open). Capacitor $C1$ and resistor $R1$ directly affect the pulse timing; a shorted capacitor will cause oscillations to cease and prevent development of oscillator grid voltage, and an open

resistor will prevent capacitor discharge. Sustained periodic oscillations of the blocking oscillator depend upon feedback obtained from transformer T1 as well as the action of capacitor C1 and resistor R1. Therefore, any defect in the transformer, such as an open plate or grid winding or a number of shorted turns in either of these windings, will prevent the circuit from operating. A shorted output winding or shorted load impedance may also cause the circuit to stop oscillating, since the tertiary winding is coupled to the plate and grid windings of the transformer. In this case, the impedance reflected to the plate and grid windings may cause excessive losses which will prevent sustained oscillations. Note that if the tertiary winding should open, the circuit will continue to operate; however, no output will be obtained from the tertiary winding.

Incorrect Frequency. The value of oscillator R-C components should be within design tolerance in order to produce the desired operating frequency; where an adjustment is provided, a small change in operating frequency can be compensated for by adjustment of the variable resistance in the grid circuit. It is reasonable to assume that any change in the R-C time constant of the blocking-oscillator grid circuit (change in value of resistance or capacitance, leaky capacitor, etc) will be accompanied by a change in operating frequency. Also, changes in applied filament and plate potentials will affect the operating frequency.

Indiscriminate substitution of tubes in the free-running blocking-oscillator circuit can cause a frequency change because of differences in individual tube characteristics.

Incorrect Pulse Width Or Unstable Output. Capacitor C1 affects the pulse width as well as the R-C discharge time; however, transformer T1 is of greatest influence in determining pulse width and the rise time of the output pulse. The rate of rise of the leading edge of the output pulse depends upon the transformer turns ratio between plate and grid windings and also upon the rate at which current may rise in the windings as determined by their inductance. (A transformer with high step-up ratio and low inductance will produce relatively short-duration pulses.) The pulse width normally obtained is approximately equal to the time of one-half cycle which would be produced at the natural oscillating frequency if the relative large grid-blocking capacitor C1 were not used in the circuit. Thus, a defect in the transformer,

T1, would be likely to cause a change in pulse width accompanied by unstable or erratic output.

The instantaneous blocking-oscillator grid-to-cathode voltage is the difference between the instantaneous charge voltage on the capacitor and the instantaneous negative voltage produced across the grid winding of transformer T1. A rise in capacitor voltage causes the grid voltage to become less positive faster than if the action depended upon transformer voltage alone; thus, the initial pulse is effectively shortened. If either capacitor C1 or resistor R1 should change value, the effect would be more readily noticed as a change of frequency rather than a change of pulse width.

FREE-RUNNING PRF GENERATOR (SEMICONDUCTOR)

Application.

The free-running (prf generator) blocking oscillator is a basic blocking oscillator. It produces short-time-duration, large-amplitude pulses for use as timing, synchronizing, or trigger pulses.

Characteristics.

Output pulse is a single cycle of oscillation caused by transistor (collector element) conduction at the beginning of each pulse-repetition period.

Pulse-repetition time is determined primarily by the R-C time constant in the base-emitter circuit. The pulse-repetition frequency is generally fixed within the range of 200 to 2000 pulses per second.


Pulse width and rise time of the output pulse are determined primarily by the transformer characteristics.

Output-pulse polarity is determined by the phasing of the transformer output-tertiary winding.

Circuit Analysis.

General. The free-running blocking oscillator (prf generator) is a special-type oscillator in that the transistor conducts for a short period to produce a pulse and then becomes cut off (blocked) for a much longer period of time; then the cycle of operation to produce an output pulse is repeated and the oscillator again becomes inactive. This mode of operation continues and thus produces a series of output pulses which are of short-time duration, separated by relatively long time intervals.

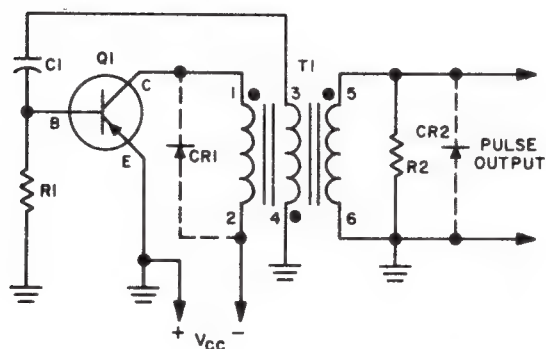Circuit Operation. The following circuit schematic illustrates a PNP transistor in a basic free-running blocking oscillator circuit. (Note the similarity between the blocking oscillator circuit given here and the L-C tickler-Coil oscillator circuit given earlier in this section.)



Free-Running PRF Generator Using PNP Transistor

Transformer T1 provides the necessary regenerative feedback coupling from the collector to the base of transistor Q1; terminals 1 and 2 of transformer T1 connect to the collector (primary) winding, terminals 3 and 4 connect to the base (secondary) winding, and terminals 5 and 6 connect to the output (tertiary) winding. Capacitor C1 and resistor R1 form the R-C circuit which determines the time constant in the base-emitter circuit.

The output pulse is taken from the tertiary winding (terminals 5 and 6) of transformer T1. Damping resistor R2 is connected across the tertiary winding to reduce the amplitude of the back voltage resulting from the collapse of the magnetic field about the transformer after the occurrence of the initial output pulse.


On the circuit schematic, note the placement of small dots near winding terminals 1, 4, and 5 of transformer T1. These dots are used to indicate similar winding polarities. For example, if current flows through the collector winding and terminal 1 is positive, the voltage induced in each of the other wind-

ings is such that the dot end is also positive in each winding at the same time; therefore at this same instant of time, terminals 3 and 6 are negative.

Bias and stabilization techniques employed for a transistor oscillator are essentially the same as those employed for a transistor amplifier. The common-emitter circuit configuration illustrated utilizes a single-battery power source; this source directly produces the required reverse bias voltage in the collector-base circuit. Forward bias for the PNP transistor requires the base to be negative with respect to the emitter. Since the collector is at a negative potential and the emitter is at a positive potential, the two PN junctions within the transistor act as a voltage divider. The junction between collector and base represents a relatively high resistance and develops a large portion of the voltage drop. The junction between emitter and base represents a low resistance and develops a lower voltage drop. The base of the transistor is structurally between the collector and the emitter and assumes a potential which is between the two voltage extremes; therefore, the base can be considered to be less positive than the emitter, or negative with respect to the emitter. Thus, the correct polarity is established to produce a forward bias between the emitter and the base.

The blocking oscillator can be compared to an amplifier with feedback of the proper phase and amplitude to provide regeneration. In the accompanying circuit schematic a common-emitter configuration is shown using a PNP transistor; the regenerative feedback signal must undergo a polarity reversal in passing from the collector to the base. If an NPN transistor is used, the polarity of the supply voltage must be opposite to that given on the schematic in order to maintain forward bias in the base-emitter circuit and reverse bias in the collector-base circuit; however, for either type of transistor the transformer must provide a polarity reversal when feedback is from collector to base.

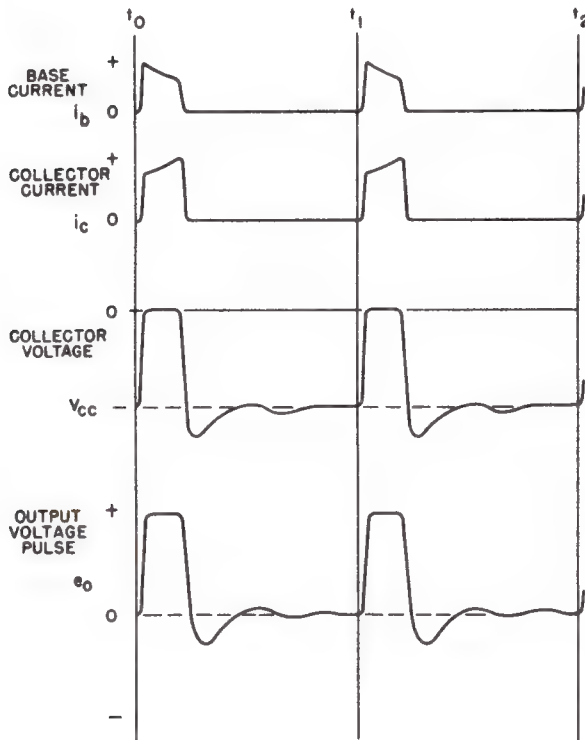For the discussion of circuit operation which follows, refer to the accompanying illustration of the blocking oscillator waveforms.



Theoretical Waveforms for Blocking Oscillator

When dc power is first applied to the circuit, a small amount of collector current, i_c , will start to flow through the collector winding (terminals 1 and 2) of transformer T1. The current flow in the collector winding induces a voltage in the base winding (terminals 3 and 4) which is negative with respect to ground. The induced voltage causes capacitor C1 to charge through the relatively low forward resistance of the base-emitter junction, and the induced voltage appears across the forward resistance to increase the forward bias. The increase in forward bias, in turn, increases the collector current, and regeneration continues rapidly until the transistor becomes saturated. During the essentially flat-top portion of the collector voltage waveform, the collector current, i_c , increases at a slower rate, as determined by the amount of magnetizing current necessary to maintain the voltage drop across the collector winding of transformer T1. Also during this period of time, the base current, i_b , gradually falls off from its peak value as a result of the inability of the transistor to maintain the same

rate of increase in magnetizing current as the transistor approaches saturation; further, at this same time a charge is accumulating on capacitor C1 which subtracts from the voltage supplied by the base winding of transformer T1. At saturation, the collector current, i_c , can no longer continue to increase, and thus becomes a constant value; therefore, there is no longer a voltage induced in the base winding, terminals 3 and 4. As a result, the magnetic field begins to collapse and induces a voltage across the winding which is of opposite polarity to the original voltage. At the same time, capacitor C1 starts to discharge through resistor R1 and the base winding (terminals 3 and 4). The discharge current of capacitor C1 produces a voltage drop across resistor R1 which is of positive polarity at the base of the transistor, thereby driving the base in a positive direction to reduce the forward bias of the base-emitter junction. The reduction in forward bias causes the collector current, i_c , to decay rapidly, which further accelerates the process; thus reverse bias is rapidly achieved at the base-emitter junction. At this time the base and collector currents drop to zero.

Because of the reverse bias, the transistor remains held at cutoff until capacitor C1 discharges through resistor R1 (and transformer T1) to a point where the transistor returns to a forward-biased condition. When the forward-biased condition is reached, conduction begins and another cycle of operation is initiated.


The output pulse width depends principally on the inductance of the transformer, T1. The smaller the inductance, the more rapidly the collector current must increase to maintain magnetizing current, and the faster the collector current will reach saturation. Normally, capacitor C1 has relatively little effect on the pulse width; however, if it is made small enough that it approaches a value where the capacitor charge can change appreciably during the pulse time, there will be a noticeable decrease in pulse duration (width). As the capacitor is made still smaller, the effect will be more pronounced and the pulse duration will be further reduced.

The repetition rate of the free-running blocking oscillator is determined by the time constant of resistor R1 and capacitor C1. Although the resistance of the base winding (terminals 3 and 4) of the pulse transformer also has an effect upon the discharge time constant, the resistance of the winding is low compared to that of resistor R1.

The output pulse is taken from the tertiary winding (terminals 5 and 6) of transformer T1. Damping resistor R2 is connected across the tertiary winding of the transformer to reduce the amplitude of the back voltage (or overshoot) which results from the collapse of the magnetic field about the transformer at the termination of the desired output pulse. If it were not for the damping resistor, the amplitude of the back-voltage pulse could exceed the breakdown voltage of the transistor and cause damage to the transistor. Several modifications can be made to the basic circuit to further reduce the amplitude or to eliminate the undesirable back voltage. One such modification is to connect a clamping diode across the collector winding (terminals 1 and 2) of the transformer as shown on the circuit schematic by the dotted lines connecting diode CR1. Similarly, a clamping diode can be connected across the output winding (terminals 5 and 6) as shown on the circuit schematic by the dotted lines connecting diode CR2, to accomplish the same purpose. In either case, the diode (CR1 or CR2) is connected in the circuit to conduct whenever the back-voltage pulse occurs and to effectively place a short circuit across the associated transformer winding for the duration of the inducted back-voltage pulse; thus it prevents the application of an excessive voltage between the collector and emitter.

The accompanying circuit schematic illustrates a variation of the basic free-running prf generator. In this circuit resistor R1 is returned to the negative terminal of the supply voltage, V_{CC} . Resistor R1 not only limits the base current and establishes the initial condition of forward-bias, but also operates in conjunction with capacitor C1 to determine the operating frequency of the blocking oscillator.

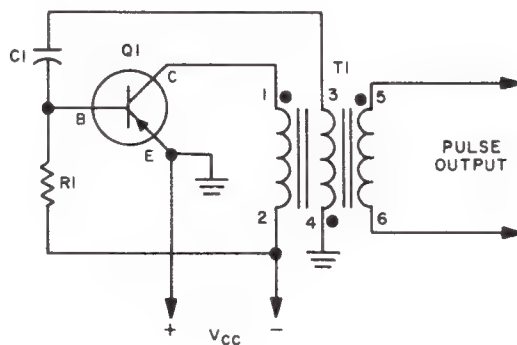The circuit operation is essentially the same as that previously described.



Variation of Basic Free-Running PRF Generator

Failure Analysis.

No Output. Voltage measurements should be made with an electronic voltmeter to determine whether the input voltage is present and whether the correct bias voltages are applied to the collector and base of the transistor. It is possible that the base-emitter junction may change resistance and thereby change the forward bias on the base; such a condition may cause thermal runaway with subsequent damage to the transistor.

Any defect in transformer T1, such as an open collector or base winding or shorted turns in any of the windings, will prevent the circuit from operating properly, since oscillations depend upon regenerative feedback from the transformer. A shorted load impedance, reflected to the collector and base windings, may cause excessive losses which will prevent sustained oscillations. Note that if the output winding

should open, the circuit will continue to operate; however, no output will be obtained from the winding. Furthermore, if damping resistor R2 should open, the induced back-voltage could exceed the voltage breakdown of the collector-emitter junctions and result in damage to the transistor.

A shorted or open capacitor C1 will prevent oscillations, since the regenerative action of the circuit depends upon the charge and discharge of C1. Also, if resistor R1 should open, the base-emitter current path will be broken and thereby prevent transistor operation.

Where the basic oscillator circuit illustrated has been modified to include a clamping diode (CR1 or CR2) across either the collector winding or the output winding, a defective diode with a low front-to-back ratio may cause circuit losses and prevent oscillation. Furthermore, if damping resistor R2 should decrease in value or if the load impedance should drop to an extremely low value, oscillations may not occur because of induced circuit losses.

Reduced Output. The input supply voltage should be measured with an electronic voltmeter to determine whether the input voltage is the correct value. Voltages at the collector and the base of the transistor should also be measured to determine whether they are within tolerances. Where the basic oscillator circuit illustrated has been modified to include a clamping diode across either the collector winding or the output winding, or across each winding, a defective diode with low front-to-back ratio can cause circuit losses which can reduce the output. Moreover, if either clamping resistor R2 or the load impedance should decrease in value, the output amplitude will decrease. Note that if the circuit losses are excessive, the circuit may not oscillate at all.

Incorrect Frequency. The pulse-repetition frequency of the free-running blocking oscillator is determined by the R-C time constant of resistor R1 and capacitor C1; any change in the values of these components will cause a change in operating frequency. Also, any change in the supply voltage will probably affect the pulse-repetition frequency and may affect the amplitude of the output pulse.

PARALLEL-TRIGGERED BLOCKING OSCILLATOR (ELECTRON TUBE)

Application.

The parallel-triggered blocking oscillator is used to produce short-time duration, large-amplitude pulses for use as synchronizing or trigger pulses in radar modulators and display indicators.

Characteristics.

Output pulse is a single cycle of oscillation caused by trigger-amplifier tube conduction which is, in turn, synchronized by a trigger pulse at the beginning of each pulse-repetition period. Some delay is introduced between the time of trigger application to the trigger amplifier and the development of the leading edge of the output pulse.

Pulse repetition time is determined by an external positive-trigger source in conjunction with the R-C time constant of the grid circuit. The pulse-repetition frequency is generally fixed within the range of 200 to 2000 pulses per second.

Trigger amplifier provides isolation and prevents blocking oscillator from reacting on trigger source; also, amplification of trigger pulse sharpens pulse somewhat.

Pulse width and rise time of the output pulse are determined primarily by the transformer characteristics.

Output-pulse polarity is determined by the phasing of the transformer output-tertiary winding. With minor circuit changes, the output can also be taken from the cathode circuit (positive pulse) or from the plate circuit (negative pulse).


Circuit Analysis.

General. The parallel-triggered blocking oscillator is similar to the free-running prf generator except that its pulse-repetition frequency is determined by a positive synchronizing trigger pulse which is applied to a trigger amplifier. The plates of the trigger-amplifier tube and the blocking-oscillator tube are in parallel

and share a common plate winding of the blocking-oscillator transformer. When the trigger amplifier receives a pulse from an external source, it amplifies the pulse and causes current to flow in the plate winding of the transformer; thus, a cycle of oscillation is initiated. Upon completion of the pulse cycle, the circuit becomes inactive until the amplifier receives another trigger pulse. Normal operation of the parallel-triggered blocking oscillator results in the

generation of an output pulse each time a trigger pulse is applied to the trigger amplifier.

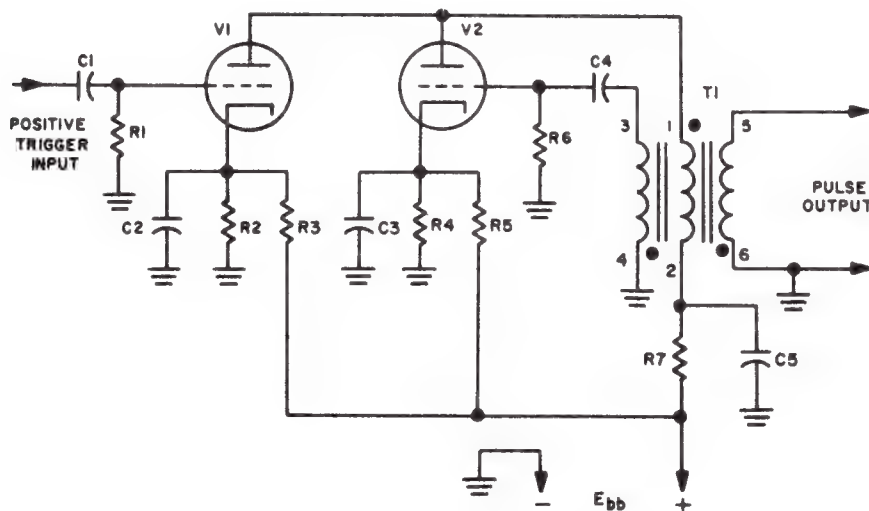Circuit Operation. The following circuit schematic illustrates two triode electron tubes in a parallel-triggered blocking-oscillator circuit; one electron tube is the blocking-oscillator and the other is the trigger amplifier. Although the schematic illustrates two separate triodes, V1 and V2, a twin triode is frequently used in this circuit.




Parallel-Triggered Blocking Oscillator

Transformer T1 provides the necessary coupling (inductive feedback) between plate and grid of electron tube V2; terminals 1 and 2 connect to the plate (primary) winding, which is common to both V1 and V2, terminals 3 and 4 connect to the grid (secondary) winding, and terminals 5 and 6 connect to the output (tertiary) winding. Capacitor C1 couples the input trigger pulse to the grid of V1; resistor R1 is the grid-return resistor for V1. Resistors R2 and R3 form a voltage divider to provide cathode bias for the trigger-amplifier tube, V1; similarly, resistors R4 and R5 provide cathode bias for the blocking-oscillator tube, V2. Capacitors C2 and C3 are the cathode bypass capacitors for V1 and V2, respectively. Capacitor C4 and resistor R6 form an R-C circuit to determine the discharge time constant in the grid circuit of V2. Resistor R7 and capacitor C5 form a plate decoupling network.

The output pulse from the blocking oscillator is taken from the tertiary winding (terminals 5 and 6) of transformer T1.

For the following discussion of circuit operation, refer to the accompanying illustration which shows the input trigger and blocking-oscillator plate-signal, grid-signal, and output-voltage waveforms. Bias voltage for the trigger amplifier, V1, is developed by cathode resistor R2 as a result of the dc current through the series resistance of R2 and R3, connected as a voltage divider between the supply voltage and ground; also, bias is developed for the blocking oscillator, V2, by cathode resistor R4, which is in series with resistor R5 to form a similar voltage divider. The amount of bias developed by resistor R2 is sufficient to hold the grid of V1 near cutoff, whereas the bias developed by resistor R4 places the grid of V2 below cutoff.

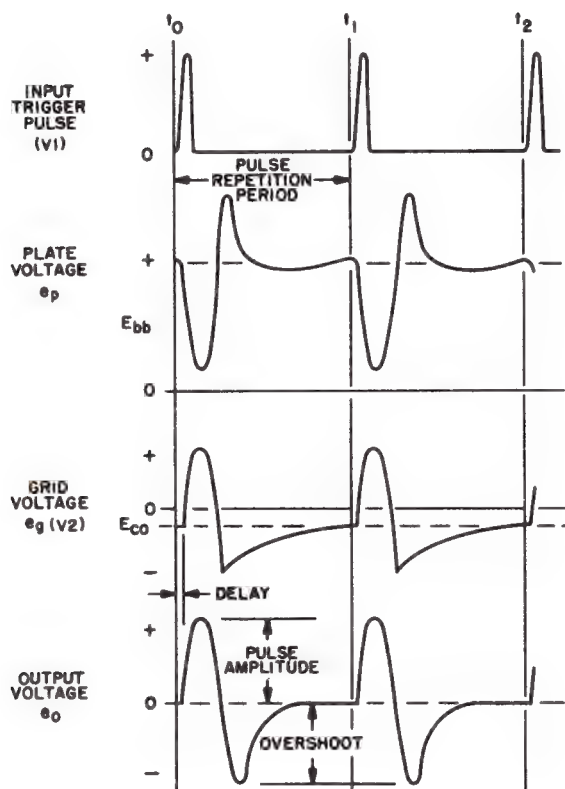

Theoretical Trigger-, Plate-, Grid-, and Output-Voltage Waveforms

To start a single cycle of operation, a positive trigger pulse is applied to the input of trigger amplifier V1 across coupling capacitor C1 and grid-return resistor R1. The trigger pulse developed across resistor R1 is applied to the grid of V1 and amplified by the trigger amplifier. As a result of the positive-going pulse on the grid of V1, the tube conducts and plate current flows through the plate winding (terminals 1 and 2) of the pulse transformer, T1. The voltage at the plates of V1 and V2 starts to drop as the current of the trigger amplifier increases in the plate winding; the increasing current through the plate winding sets up a magnetic field about the winding, and a voltage is induced (through transformer action) in the grid winding (terminals 3 and 4) of transformer T1. Since the trigger pulse is of short duration, the trigger amplifier returns to its initial condition at the end of the trigger pulse, and V1 ceases to conduct because of the cathode bias developed by resistor R2. The

blocking-oscillator action which follows is similar to that which occurs during one cycle of operation for the free-running (prf generator) blocking oscillator.

When trigger-amplifier plate current flows through the plate winding, a grid-signal voltage is produced across the grid winding and is impressed on the grid of V2 through coupling capacitor C4 to drive the grid of V2 in a positive direction. (See grid-voltage waveform.) This causes the blocking-oscillator tube to start to conduct when the positive grid voltage exceeds the value of cathode bias; the regenerative action (feedback) which occurs to complete the cycle of operation is essentially the same as the action previously described for the free-running (prf generator) blocking oscillator. Near the end of the cycle of operation and after the trigger-amplifier tube returns to cutoff, the grid of the blocking oscillator is driven below cutoff as the result of the highly negative charge existing on capacitor C4. (See grid-voltage waveform.) Capacitor C4 slowly discharges through resistor R6 and the grid winding of T1. The time constant of R6 and C4 is chosen so that the grid is held below cutoff for a considerable period of time; thus, the grid gradually approaches the initial value of bias, at which time the circuit is ready to be triggered to initiate another cycle of operation. (The initial value of bias developed across R4 is sufficient to keep the blocking-oscillator tube at or below cutoff.) Under the conditions of operation described above, the blocking oscillator produces an output pulse each time a trigger pulse is applied to the input of the trigger amplifier, V1. The output pulse is delayed slightly, but has the same repetition frequency as the synchronizing trigger pulse.

With minor modification to change the time constant of R6C4, the parallel-triggered blocking oscillator circuit may be used as a pulse-frequency divider to produce output pulses at a submultiple of the trigger-pulse frequency.

The output pulse is taken from the tertiary winding (terminals 5 and 6) of transformer T1 in the same manner as that previously described for the free-running (prf generator) blocking-oscillator circuit.

The parallel-triggered blocking oscillator is relatively insensitive to changes in filament and plate supply voltages. A change in plate voltage of 10 percent may reflect a change as great as 7 percent in pulse amplitude; however, there is little change in pulse width or rise time.

Failure Analysis.

No Output. It is important to establish that the cathode bias voltage developed by each voltage divider (R2, R3, and R4, R5) is correct for the trigger-amplifier and blocking-oscillator tubes, V1 and V2. Since the trigger-amplifier and blocking-oscillator tubes are normally biased at or below cutoff, it is also important to establish that a trigger pulse of correct polarity and amplitude is being supplied to the circuit. When the circuit is in a nonoscillating condition, assuming that the bias voltage is correct for both tubes, the voltage measured at the plates of V1 and V2 will approach the value of the supply voltage, provided that the plate winding of T1 and the decoupling filter (R7 and C5) are not defective. Any defect in the plate or grid windings of transformer T1 is likely to prevent the proper regenerative feedback from occurring; as a result, the circuit will not provide the proper output pulse or may not oscillate at all.

If the tertiary winding of transformer T1 should open, the circuit may still operate but no output will be obtained from the tertiary winding.

Unstable Output. Whenever the output-pulse repetition rate of the blocking oscillator becomes unstable or erratic, the trigger pulse should first be checked to determine whether the fault lies within the trigger-generator circuit. Since the stability of the blocking oscillator is dependent upon the repetition-frequency and pulse-amplitude stability of the trigger source, it is entirely possible that an unstable trigger applied to the trigger amplifier will cause the blocking oscillator to produce output pulses which are synchronized to the faulty trigger. The time constant of R6 and C4 must allow the grid of V2 to return the initial value of bias before the blocking oscillator is triggered; otherwise, the blocking oscillator may not respond reliably to the amplified trigger pulse. Random pulsing of the blocking oscillator can also result if the cathode bias (derived from resistors R4 and R5) is reduced and approaches zero bias. In this case, although the trigger pulse will frequently initiate an operating cycle, the oscillator may attempt to become free-running because of the lack of correct bias. Leakage in capacitor C4 will cause a change in the R-C time constant of the blocking oscillator, and will result in an unstable output which is usually accompanied by a decrease in pulse amplitude.

Low Output. Reduced plate-supply voltage will affect the amplitude (and perhaps the pulse width and

rise time) of the output pulse. Also, if shorted turns should develop in the tertiary winding of T1 or if a decrease in load impedance should occur, the pulse-output amplitude will be reduced not only because of the change in load impedance but also because of the impedance reflected into the plate and grid windings of transformer T1. If the load impedance should fall considerably below the normal value for the circuit, an increase in time delay will occur between the trigger pulse and the start of the output pulse; also, the rise time of the output pulse will increase and will be accompanied by a decrease in pulse amplitude.

SERIES-TRIGGERED BLOCKING OSCILLATOR (ELECTRON TUBE)**Application.**

The series-triggered blocking oscillator is used to produce short-time-duration, large-amplitude pulses for use as synchronizing or trigger pulses in radar modulators and display indicators.

Characteristics.

Output pulse is a single cycle of oscillation caused by tube conduction which is initiated by synchronizing trigger pulse at the beginning of each pulse-repetition period.

Pulse-repetition time is determined by an external positive-trigger source in conjunction with the R-C time constant of the grid circuit. The pulse-repetition frequency is generally fixed within the range of 200 to 2000 pulses per second, although the circuit can be arranged to change the R-C time constant and provide for operation at a submultiple of the trigger-pulse frequency; in this case, the triggered blocking oscillator operates as a pulse frequency divider.

Requires a low-impedance trigger source; there is considerable reaction on the trigger source even if a cathode follower is used for triggering the circuit.

Pulse width and rise time of the output pulse are determined primarily by the transformer characteristics.


Output-pulse polarity is determined by the phasing of the transformer output-tertiary winding. With minor circuit changes, the output can also be taken from the cathode circuit.

Circuit Analysis.

General. The series-triggered blocking oscillator is similar to the free-running prf generator except that

its pulse-repetition frequency is determined by a positive synchronizing trigger pulse. When the oscillator is triggered by a pulse from an external source, it completes one cycle of operation to produce an output pulse and then becomes inactive; the cycle of operation is repeated upon application of another trigger pulse. Normal operation of the series-triggered blocking oscillator results in the generation of an output pulse each time a trigger pulse is applied to the circuit.

Circuit Operation. The following circuit schematic illustrates a triode electron tube in a series-triggered blocking-oscillator circuit. Transformer T1 provides the necessary coupling (inductive feedback) between the plate and grid of electron tube V1; terminals 1 and 2 connect to the plate (primary) winding, terminals 3 and 4 connect to the grid (secondary) winding, and terminals 5 and 6 connect to the output

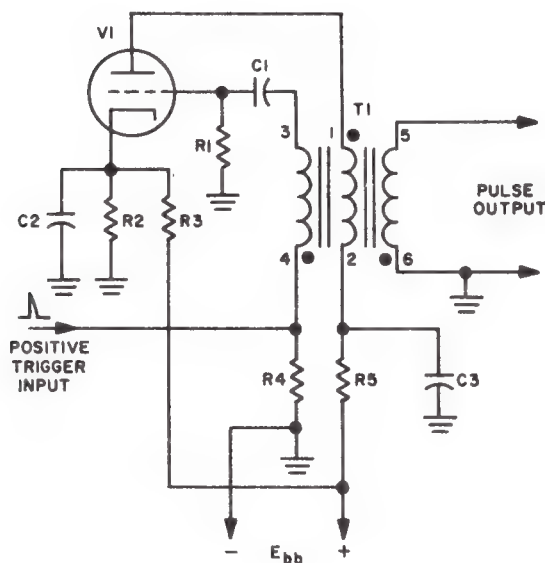


Series-Triggered Blocking Oscillator

(tertiary) winding. Capacitor C1 and resistor R1, in conjunction with R4, form an R-C circuit to determine the discharge time constant in the grid circuit. Resistors R2 and R3 form a voltage divider to provide cathode bias for the tube; the voltage developed across R2 is sufficient to bias the tube at or below cutoff. Capacitor C2 is a cathode bypass capacitor. The synchronizing trigger pulse is applied across resis-

tor R4, which is effectively in series with the grid signal. The value of resistor R4 is generally low; however as indicated previously, this resistance is a part of the total resistance which determines the R-C time constant of the circuit. Resistor R5 and capacitor C3 form a plate decoupling network.

The output pulse from the blocking oscillator is taken from the tertiary winding (terminals 5 and 6 of transformer T1).

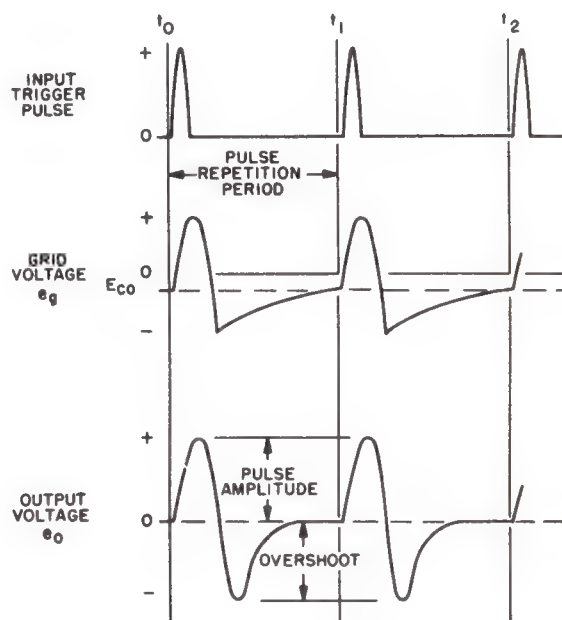For the brief discussion of circuit operation which follows, refer to the accompanying illustration which shows the blocking-oscillator-trigger, grid-signal, and output voltage waveforms.



Theoretical Trigger, Grid-Voltage, and Output-Voltage Waveforms

When voltage is first applied to the circuit, bias voltage for the tube is developed by cathode resistor R2 as a result of the dc current through the series resistance of R2 and R3 connected between the supply voltage and ground. The amount of bias developed is sufficient to hold the grid at or slightly below cutoff; thus, plate current does not flow at this time.

To start a single cycle of operation, a positive trigger pulse is applied across resistor R4. This pulse is applied through the grid winding of transformer T1 and capacitor C1 to the grid of V1, and raises the grid

voltage above cutoff. (The positive-going trigger pulse must be of sufficient amplitude to drive the grid out of the cutoff region to initiate the cycle.) At this time the tube starts to conduct, and the regenerative action which occurs during the cycle of operation is essentially the same as the action previously described for the free-running (prf generator) blocking oscillator. Near the end of the cycle, when the grid is driven below cutoff and plate current no longer flows through the plate winding of T1, the highly negative charge existing on capacitor C1 slowly discharges through resistors R1 and R4 and the grid winding of transformer T1. Since the resistance of the grid winding is low in comparison with the combined resistance of R1 and R4, it has little effect on the discharge time of capacitor C1. Furthermore, the resistance of R4 is low compared to that of R1; therefore, R1 has the predominant effect on the discharge time of capacitor C1.

After an elapsed period of time, as governed by the time constant of R1, R4, and C1, capacitor C1 discharges and allows the grid potential to reach a point near cutoff. When a positive trigger pulse is again applied across resistor R4, another cycle of operation is initiated.

If it were not for the periodic application of the positive trigger pulse to resistor R4, the blocking oscillator would remain cut off because of the value of cathode bias developed across cathode resistor R2. Under these conditions, each time a trigger pulse is applied to the circuit, a complete cycle of the blocking oscillator produces an output pulse which is in synchronism with the trigger pulse and has the same repetition frequency. For synchronization to occur the values of R and C must be chosen so that the natural oscillating frequency of the blocking oscillator, in the absence of cathode bias, is slightly lower than the repetition frequency of the synchronizing trigger pulse.

The operating frequency of the triggered blocking oscillator can be conveniently changed to a sub-multiple of the trigger frequency by switching R-C values to alter the time constant. For example, an additional resistance could be switched into the circuit in series with resistor R1 to increase the R-C time constant. In this case, if the time constant were at least doubled, the oscillator would respond to every other trigger pulse and, therefore, the blocking-oscillator repetition frequency would be one-half that of the trigger source.

The output pulse is taken from the tertiary winding (terminals 5 and 6) of transformer T1 in the same manner as previously described for the free-running (prf generator) blocking-oscillator circuit.

In a practical series-triggered blocking-oscillator circuit, resistor R4 may actually be the cathode resistor for a cathode-follower circuit. In this case, the trigger is applied to the grid of the cathode-follower electron tube, and resistor R4, across which the trigger pulse is developed, represents a low-impedance trigger source to the blocking-oscillator circuit.

The series-triggered blocking oscillator is relatively insensitive to changes in filament and plate-supply voltages, although a change in plate voltage of 10 percent may produce a change as great as 10 percent in pulse amplitude and may be accompanied by some change in pulse width. However, this effect is reduced to some extent by the change in the bias voltage developed across resistor R2 whenever the plate-supply voltage changes.

Failure Analysis.

No Output. Since the oscillator is normally biased to cutoff, it is important that a trigger pulse of the correct polarity and amplitude be supplied to the oscillator circuit. When the circuit is in a nonoscillating condition, assuming that the developed cathode bias is normal, the voltage measured at the plate of V1 will approach the value of the supply voltage, provided that the plate winding of T1 and the decoupling filter (R5 and C3) are not defective. Any defect in the plate or grid windings of transformer T1 is likely to prevent the proper regenerative feedback from occurring; as a result, the circuit will not provide the proper output pulse or may not oscillate at all. If the tertiary winding of transformer T1 should open, the circuit may still operate but no output will be obtained from the tertiary winding.

Unstable Output. Whenever the output-pulse repetition rate of the blocking oscillator becomes unstable or erratic, the trigger pulse should first be checked to determine whether the fault lies within the trigger-generator circuit. Since the stability of the blocking oscillator is dependent upon the repetition-frequency and pulse-amplitude stability of the trigger source, it is entirely possible that an unstable trigger applied to the oscillator will cause the blocking oscillator to produce output pulses which are synchronized to the random triggering. Random pulsing of

the blocking oscillator can also result if the fixed bias (derived from resistors R2 and R3) should be reduced and approach zero bias. In this case, although the trigger pulse will frequently initiate an operating cycle, the oscillator may attempt to become free-running because of the lack of correct bias. Leakage in capacitor C1 will cause a change in the R-C time constant of the blocking oscillator, and will result in an unstable output which is usually accompanied by a decrease in pulse amplitude.

Low Output. Reduced plate-supply voltage will affect the amplitude (and perhaps pulse width) of the output pulse. Also, if shorted turns should develop in the tertiary winding or if a decrease in load impedance should occur, the output will be reduced not only because of the change in load impedance but also because of the impedance reflected into the plate and grid windings of transformer T1.

TRIGGERED BLOCKING OSCILLATOR (SEMICONDUCTOR)

Application.

The basic triggered blocking oscillator is used to produce synchronized, large-amplitude pulses for use as timing, trigger, or control pulses in radar equipment, television sets, and similar electronic switching devices.

Characteristics.

Requires a negative input trigger pulse.

Output pulse is a single cycle of oscillation (positive and negative alternations).

Output-pulse-repetition frequency is determined by the input trigger frequency.

Output-pulse width and rise time are determined primarily by the transformer inductance, capacitance, and resistance characteristics.

Output-pulse polarity is determined by the transformer output (tertiary) winding phasing.


Fixed, Class B (cutoff) bias is employed.

Circuit Analysis.

General. The basic blocking oscillator produces an output pulse each time an input pulse is applied to activate the circuit. Between trigger pulses, the transistor remains cut off (non-conducting), and no output is produced until an input trigger pulse of sufficient amplitude to produce conduction is again applied. The circuit produces one output pulse and then

returns to the inactive (quiescent) state, awaiting the next trigger.

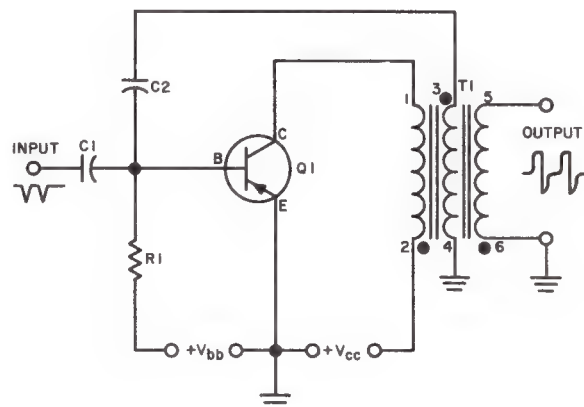Circuit Operation. The accompanying circuit schematic illustrates a basic triggered blocking oscillator using a PNP transistor connected in the common-




Basic Blocking Oscillator

emitter configuration. Transformer T1 provides the regenerative feedback necessary between the collector and the base of transistor Q1 to obtain oscillation. The primary winding (terminals 1 and 2) is connected in series with collector supply V_{CC} and the collector of transistor Q1. The secondary winding (terminals 3 and 4) supplies the feedback voltage, which is applied to the base of transistor Q1 through capacitor C2. Capacitor C2 is also a dc blocking capacitor used to isolate the base from the dc shunting effect of the secondary winding of transformer T1, preventing it from shorting to ground the fixed cutoff bias applied to transistor Q1 through base resistor R1. The negative input trigger is applied through coupling capacitor C1 to the base of transistor Q1, and the output pulse is taken from the tertiary winding (terminals 5 and 6) of transformer T1.

The collector of transistor Q1 is reverse-biased by the negative collector supply, V_{CC} ; the positive base bias supply, V_{BB} , furnishes fixed reverse bias to the base of transistor Q1 through base resistor R1. Thus, in the quiescent state with no input trigger applied, transistor Q1 is completely reverse-biased and cannot conduct. Hence, no output is produced.

When a negative trigger pulse, such as that shown at time t_1 on the accompanying waveform

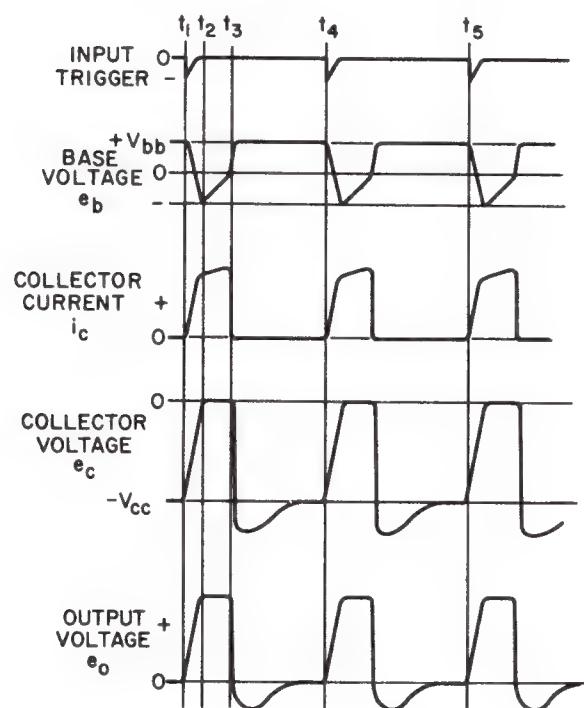illustration, is applied through coupling capacitor C1 to the base of transistor Q1, it forward-biases



Theoretical Waveforms
for Basic Blocking Oscillator

the transistor, causing collector current to flow. The collector current, flowing from the collector supply through the collector (primary) winding of transformer T1 to the transistor, causes a magnetic field to be built up around the collector (primary) winding of the transformer. This increasing magnetic field induces into the base winding of the transformer a voltage of such polarity that the potential on terminals 3 of the winding is negative with respect to ground (terminal 4). This negative potential is applied to the base of transistor Q1 (through capacitor C2), and increases the forward bias on the transistor, causing the collector current to increase further. As the collector current flowing through the collector winding of transformer T1 increases. The magnetic field around the winding increases accordingly, inducing a larger voltage into the base winding of the transformer. The increasing induced voltage is fed back to the base of

transistor Q1, causing the forward bias on the transistor and hence the collector current, to increase still further. Thus, this *regenerative feedback* from the collector to the base of transistor Q1 causes the collector current to continue to increase until the transistor reaches saturation. When transistor Q1 reaches collector-current saturation (time t_2 on the waveform illustration), the collector current flowing through the collector winding of transformer T1 can no longer increase. Therefore, the magnetic field around the collector winding no longer increases; consequently, no feedback voltage is induced into the secondary (base) winding of the transformer. As a result, the voltage across the base winding of transformer T1 decays at a rate determined by the inductance, capacitance, and resistance values of the transformer, causing the negative voltage on the base of transistor Q1 to decrease accordingly. At the same time, the decreasing voltage across the base winding of transformer T1 also induces into the collector winding a voltage of such polarity that it aids (adds to) the collector-supply voltage, effectively increasing the value of the collector-supply voltage. The effectively increased collector-supply voltage raises the saturation point of the transistor; consequently, the collector current increases slightly above the previous saturation value. When the voltage across the base winding of transformer T1 decays to zero (time t_2 on the waveform illustration), no further forward bias is applied through capacitor C2 to the base of transistor Q1, and the transistor ceases to conduct. Since no further forward bias is supplied, the base bias supply resumes control and applied a positive bias voltage through resistor R1 to the base of transistor Q1, reverse-biasing the transistor and holding it below cutoff until the next trigger pulse is applied. Meanwhile, as the transistor decreases in conduction from saturation to cutoff (at time t_3) the collector current flowing through the collector winding of transformer T1 decreases to zero, and the magnetic field around the winding collapses. This collapsing field induces into the collector winding a voltage of such polarity that it tends to keep current flowing in the same direction as the original current flow (that is, the induced voltage aids the collector-supply voltage). The result of adding these voltages is that the voltage on the collector of transistor Q1 momentarily becomes much more negative than the negative collector-supply value. This large negative voltage pulse is called *overshoot* (point

A on the collector-voltage waveform). As the magnetic field around the collector winding of transformer T1 collapses completely, the induced voltage (overshoot) also decreases to zero, and the collector voltage returns to the quiescent value.

Any change of current in the collector winding of transformer T1 also induces a changing voltage into the tertiary, or output, winding of the transformer. The polarity of the output pulse is determined by which terminal of the output winding is grounded. As shown in the circuit schematic, terminal 6 is grounded, and a positive output pulse results (a negative output pulse would be obtained if terminal 5 were grounded instead).

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of multiplier resistance employed on the low-voltage ranges of the standard 20,000 ohms-per-volt meter. Be careful also to observe proper polarity when checking continuity with an ohmmeter, since a forward bias applied through any of the transistor junctions will cause a false low-resistance reading.

No Output. A no-output condition may be caused by an improper input trigger, a lack of supply voltage, or a defective circuit component. First, use an oscilloscope to observe the input trigger voltage waveform. Compare the observed waveform with one shown in the equipment instruction book to be certain that the proper input trigger is applied. Next, use a vacuum-tube voltmeter to measure the supply voltage and eliminate the possibility of a defective power supply. If the correct input trigger is applied and the normal supply voltage is present, further checks must be made to locate the defective component. Use an in-circuit capacitor checker to check capacitors C1 and C2 for opens and leakage, and an ohmmeter to check resistor R1 and transformer T1 for continuity and proper resistance value. If these checks fail to locate a defective component, transistor Q1 is probably at fault.

Low or Distorted Output. Low supply voltage, a defective transistor (Q1), or a defective transformer

(T1) may cause either low-amplitude or distorted output pulses. Measure the supply voltage with a vacuum-tube voltmeter. If the normal value of voltage is measured, the trouble is in the blocking oscillator and not in the power supply.

FAST-RECOVERY BLOCKING OSCILLATOR (ELECTRON TUBE)

Application.

The fast-recovery blocking oscillator produces short-time-duration, large-amplitude pulses for use as timing, synchronizing, or trigger pulses in radar modulators and display indicators.

Characteristics.

Output is a single pulse caused by tube conduction and initiated by a trigger pulse at the beginning of each pulse repetition period.

Pulse repetition frequency is determined by an external trigger source.

Pulse repetition period is much shorter in the fast-recovery blocking oscillator than in other types of blocking oscillators.


Pulse width and rise time are determined primarily by the transformer characteristics.

Output pulse polarity is determined by the phasing of the transformer output (tertiary) winding.

Circuit Analysis.

General. The fast-recovery blocking oscillator is similar to other types of triggered blocking oscillators in that, when triggered, it supplies one output pulse and then becomes inactive. In the normal triggered blocking oscillator, the grid voltage must be allowed to return to a point near cutoff before the circuit is triggered again. This period of time, called *recovery time*, is normally much longer than the pulse width and limits the pulse repetition frequency. The fast-recovery blocking oscillator uses a number of methods to overcome the difficulty of long recovery time.

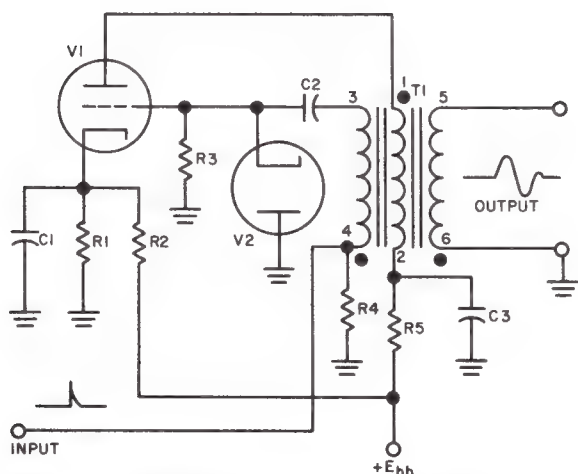Circuit Operation. The accompanying circuit schematic illustrates one type of fast-recovery blocking




Fast-Recovery Blocking Oscillator

oscillator. With the exception of diode V2, it is identical to the series-triggered blocking oscillator discussed previously in this section of the Handbook. Transformer T1 provides the necessary coupling (inductive feedback) between plate and grid of electron tube V1. Terminals 1 and 2 connect to the plate (primary) winding, terminals 3 and 4 connect to the grid (secondary) winding, and terminals 5 and 6 connect to the output (tertiary) winding. Resistors R1 and R2 form a voltage divider which provides cathode bias for triode V1. The voltage developed across cathode resistor R1 biases triode V1 to plate current cutoff. Capacitor C1 is the cathode bypass capacitor for triode V1, and resistor R3 is the grid return resistor. The positive trigger pulse is applied across resistor R4, which has a relatively low value of resistance. Grid capacitor C2 and resistors R3 and R4 normally determine the time constant of the grid circuit. However, when capacitor C2 discharges, diode V2 conducts, shunting grid resistor R3, and the discharge time for the circuit is greatly reduced. Resistor R5 and capacitor C3 form a conventional plate decoupling network. The output from the blocking oscillator is taken from the tertiary winding (terminals 5 and 6) of transformer T1.

The following illustration shows the trigger-, grid-, plate-, and output-voltage waveforms in their proper time relationship. When voltage is first applied to the circuit, dc current flows through voltage divider consisting of resistor R1 and R2. This current flow

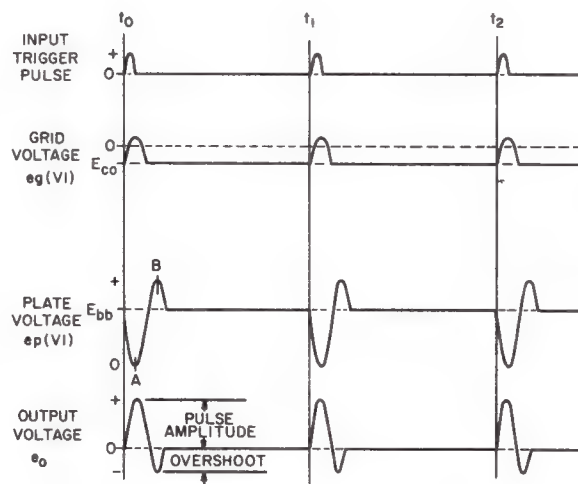develops a bias voltage on the cathode of triode V1 which is sufficient to keep the tube biased to plate-current cutoff. Hence, no current flows in the plate circuit.



Trigger-, Grid-, Plate-, and Output Voltage Waveforms

When a positive trigger pulse is applied to resistor R4, it passes through the grid winding of transformer T1 and is applied to grid capacitor C2. The positive potential on the transformer side of capacitor C2 causes an electron flow from ground through grid resistor R3 to the grid side of the capacitor. This current flow, which eventually charges the capacitor, develops a positive voltage across grid resistor R3 sufficient to raise the bias of triode V1 above cutoff and cause V1 to conduct. As plate current increases and flows through the plate winding terminals 1 and 2) of transformer T1, it produces a magnetic field around the winding. This increasing magnetic field induces a voltage into the grid winding of the transformer. The transformer phasing is such that the induced positive voltage increases the voltage across C2, causes more current to flow through grid resistor R3, increases the charge on grid capacitor C2, and drives the grid of V1 further positive. The increase in positive grid voltage, due to feedback, causes the plate current to increase still further. This *regenerative action* continues. That is a continual increase in grid voltage causes a continual increase in plate current which, in turn, causes a further increase in the grid

(feedback) voltage. Meanwhile, as the plate current rapidly increases toward plate-current saturation, the grid voltage becomes more positive until it reaches zero bias, and grid current flows, charging grid capacitor C2 to its maximum value.

When the plate-current saturation point is reached (point A on the plate-voltage waveform), current flow in the plate winding of transformer T1 no longer increases. Since there is no longer a changing magnetic field around the plate winding of the transformer, no further voltage is induced into the grid winding. Grid capacitor C2 is now fully charged, and since there is no longer a voltage across the grid winding of transformer T1 to sustain this charge, the capacitor begins to discharge. Normally, the capacitor would discharge through grid resistor R3, resistor R4, and the grid winding of the transformer. However, the negatively charged side of grid capacitor C2 is connected to the cathode of diode V2. This negative potential on the cathode of the diode makes it conduct, shunting grid resistor R3. Capacitor C2 now discharges through diode V2, resistor R4, and the grid winding of transformer T1. Since the high resistance of grid resistor R3 is shunted by diode V2 and effectively removed from the circuit, resistor R4 alone determines the discharge time constant of the circuit. Since the value of R4 is low, the time constant is short, and capacitor C2 discharges very quickly. When capacitor C2 discharges, the grid voltage level drops until it reaches the fixed cathode bias (determined by resistors R1 and R2) which keeps the triode biased to cutoff, and plate current ceases.

As plate current stops flowing in the plate winding of transformer T1, the magnetic field around the winding collapses. The collapsing field induces into the plate winding a voltage of a polarity which tends to keep current flowing in the same direction. (That is, the polarity of the induced voltage is series-aiding with that of the plate-supply voltage.) The result of adding these voltages is a momentary increase in plate voltage over and above the plate-supply voltage, called *overshoot* (point B on the plate-voltage waveform). As the magnetic field around transformer T1 decreases in intensity, the induced voltage (overshoot) decreases accordingly, and the plate voltage quickly returns to the normal quiescent value.

Any changes of current in the primary winding of transformer T1 also induce a changing voltage into the tertiary, or output, winding (terminals 5 and 6). The polarity of the output pulse from this winding is

determined by which terminal is connected to ground. As shown in the circuit schematic, terminal 6 is grounded. Therefore, in this case, a positive output pulse results (for a negative output it would be necessary to ground terminal 5 instead).

The fast-recovery blocking oscillator provides one output pulse each time a positive trigger pulse is applied. It is ready again almost immediately to receive another trigger pulse and produce another output pulse. Therefore, it is preferred for circuits operating at fast repetition rates.

Failure Analysis.

No Output. Since the oscillator depends on a positive trigger pulse to initiate operation, it is important to determine whether the input pulse is of the proper polarity and of sufficient amplitude to drive the grid of V1 above cutoff. Use an oscilloscope to observe the input waveform. If the proper trigger pulses are present at the input, use the oscilloscope to observe the signal at the plate of V1. If pulses similar to those shown in the illustration of the plate-voltage waveform are observed, but still no output is obtained, the output (tertiary) winding of transformer T1 is either open or shorted. Use an ohmmeter to check the continuity of this winding; also check for a short to ground (indication of less than 0.1ohm). If no pulses are observed at the plate of V1, either no plate voltage is present or there is a defective feedback circuit or a defective cathode-bias circuit. Measure the voltage on the plate of V1 with a high-resistance voltmeter. If no voltage is measured at this point, a number of other possibilities exist: either an open in the plate winding of transformer T1, an open plate resistor R5, or a shorted bypass capacitor C3. Use an ohmmeter to check these components and isolate the trouble. If the proper voltage is measured at the plate of V1 but no plate pulses are seen on the oscilloscope, the trouble is in either the feedback or bias circuits. Use an ohmmeter to check for an open grid capacitor, C2, or for an open grid winding of transformer T1 to clear the feedback circuits. Then check for proper resistance values of resistors R1, R2, R3, and R4 to clear the bias circuits. If these checks fail to locate the trouble, the tube is probably at fault.

Unstable Output. Since the output stability of the oscillator is dependent upon the input trigger pulse, it is important to be certain that the input trigger is of the proper amplitude and frequency. Use an oscilloscope to observe the input waveform. If the proper

input waveform is observed, the bias circuit or feedback circuit may be faulty. Use an ohmmeter to check capacitor C1 for an open or a short, and to check bias resistors R1 and R2 for proper resistance values. If these checks shown that the bias circuit is not defective, check the feedback circuit with an ohmmeter. First check grid capacitor C2 for a short, and then check resistors R3 and R4 for the proper resistance values. Also use the ohmmeter to check transformer T1 for continuity of the grid and plate windings, for shorts between the windings, and for shorts to ground (less than 1 ohm).

Low Output. Low output may be caused by weak emission in the triode, low plate-supply voltage, or excessive circuit loading. If substituting a good tube for triode V1 does not remedy the trouble, use a high-resistance voltmeter to measure the plate-supply voltage. If this voltage is low, the trouble is in the power supply. If the plate-supply voltage is normal, the transformer is probably defective.

NONSATURATING DIODE-CLAMPED BLOCKING OSCILLATOR (SEMICONDUCTOR)

Application.

The nonsaturating, diode-clamped blocking oscillator is used to produce synchronized, large-amplitude pulses for use as timing or synchronizing pulses in radar, communications, and data-processing equipment.

Characteristics.

Requires a negative input trigger pulse. Output is a single square pulse caused by transistor conduction.

Output-pulse repetition frequency is determined by the input trigger frequency.

Output-pulse width and rise time are determined primarily by the transformer inductance, capacitance, and resistance characteristics.

Output-pulse polarity is determined by the transformer output (tertiary) winding phasing.


Fixed, class B (cutoff) bias is employed.

Circuit Analysis.

General. The nonsaturating, diode-clamped blocking oscillator produces one output pulse each time a trigger pulse is applied to activate the circuit. Between trigger pulses the circuit remains in the inactive (quiescent) state, and no output is produced. The

operation of the nonsaturating, diode-clamped blocking oscillator is similar to that of other types of blocking oscillators except that in this circuit, diode clamping is employed to prevent transistor saturation and to eliminate the normal overshoot which is present in the output of other types of blocking oscillators.

Circuit Operation. The accompanying circuit schematic illustrates a nonsaturating, diode-clamped blocking oscillator using a PNP transistor connected in the common-emitter configuration. Transformer T1 provides the regenerative feedback necessary between the collector and the base of transistor Q1 to obtain oscillation. The primary winding (terminals 1 and 2) is connected in series with the collector supply (made up of V_{CC1} and V_{CC2}) and the collector of transistor Q1. The secondary winding (terminals 3 and 4) is connected from ground to the base of transistor Q1 through dc blocking capacitor C2. This capacitor prevents the base (secondary) winding of the transformer from acting as a dc shunt to ground for the fixed cutoff bias applied to transistor Q1 through base resistor R1. Clamping diodes CR1 and CR2 limit the collector voltage swing, and prevent transistor saturation and overshoot in the output pulse. The negative input trigger is applied through coupling capacitor C1 to the base of transistor Q1, and the output pulse is taken from the tertiary or output winding (terminals 5 and 6) of transformer T1.

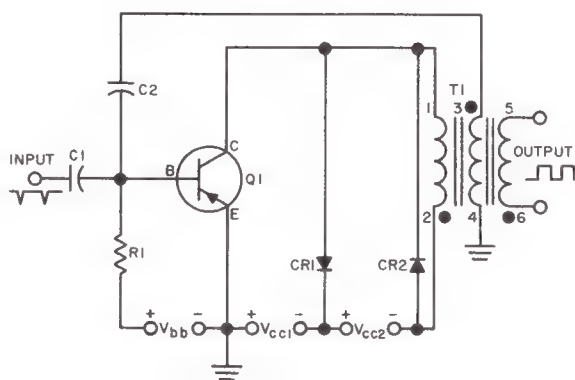


Nonsaturating, Diode-Clamped Blocking Oscillator

The collector of transistor Q1 is reverse-biased by the combined negative voltage of V_{CC1} and V_{CC2} .

The base of transistor Q1 is reverse-biased by the positive voltage applied from the bias supply (V_{BB}) through base resistor R1. Thus, in the quiescent state with no input applied transistor Q1 is completely reverse-biased and cannot conduct. Diode CR1 is reverse-biased by V_{CC2} , which is connected across the diode through the collector (primary) winding of transformer T1, diode CR2 has no bias applied because there is no current flow through the collector winding of transformer T1, and hence no voltage drop occurs it to bias diode CR2. Consequently, neither diode conducts while the circuit is in the quiescent state.

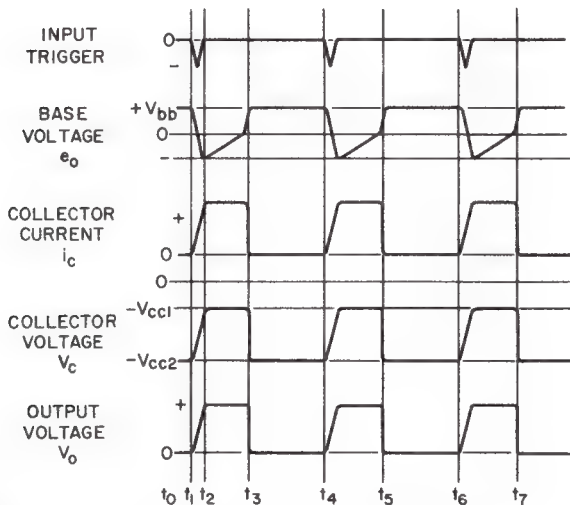When a negative trigger pulse (such as that shown at time t_1 on the accompanying waveform illustration) is applied through coupling capacitor C1 to the base of transistor Q1, it forward-biases the transistor, causing collector current to begin to flow.



**Theoretical Waveforms for Nonsaturating,
Diode-Clamped Blocking Oscillator**

The collector current flowing from V_{CC2} through the collector winding of transformer T1 to the transistor causes a magnetic field to be built up around the collector winding. The increasing magnetic field induces into the base winding of the transformer a voltage of such polarity that the potential on terminal 3 of the winding is negative with respect to ground (terminal 4). This negative potential is applied through capacitor C2 to the base of transistor Q1; it

increases the forward bias on the transistor and causes the collector current to further increase. As the collector current flowing through the primary (collector) winding of transformer T1 increases, the magnetic field around the winding increases accordingly and induces a larger voltage into the base winding of the transformer. This increasing induced voltage is fed back to the base of transistor Q1, increasing the forward bias and causing the collector current to increase still further. Thus, the *regenerative feedback* from the collector to the base of transistor Q1 causes the collector current to continue to increase once the input trigger pulse starts current flowing. As the collector current increases the voltage on the collector of transistor Q1 decreases from the negative (cutoff) value of V_{CC2} to the less negative value of V_{CC1} (time t_2 on the waveform illustration). When the collector voltage becomes less negative than the value of V_{CC1} diode CR1 becomes forward-biased and conducts. Since the forward-biased (conducting) diode has a very low resistance, the voltage drop across it is negligible and the voltage on the collector of transistor Q1 is held equal to the negative value of V_{CC1} . Thus, diode CR1 *clamps* the collector voltage to the negative value of V_{CC1} ; in other words, it prevents the collector voltage from becoming less negative (more positive) than V_{CC1} . Consequently, the collector current flowing through the collector winding of transformer T1, increases, as a result of the regenerative feedback, until the collector voltage drops to the value of V_{CC1} . At this time, diode CR1 begins to conduct and shunts any additional collector current flow around the collector winding of the transformer. Since there is no longer an increasing current flow in the collector winding of transformer T1, the magnetic field around the winding ceases to increase and no further voltage is induced into the base winding. Since no further induced voltage is present, the voltage across the base winding of transformer T1 decays at a rate determined by the inductance, capacitance, and resistance values of the transformer. When the voltage across the base winding of the transformer decays to zero (time t_3 on the waveform illustration), no further forward bias is applied to the base of transistor Q1 and the transistor ceases to conduct. The base bias supply (V_{BB}) again furnishes reverse bias to the base of transistor Q1 to hold the transistor or below cutoff until the next input trigger is applied. Meanwhile, as the collector current flow through the collector winding of transformer T1 decreases to

zero, the magnetic field around the winding collapses; this induces into the collector winding a voltage of such polarity that it tends to keep current flowing in the direction of the original collector current flow. The induced voltage forward-biases diode CR2, and the diode conducts, allowing the induced current to flow through it. Thus, diode CR2 effectively shorts out the voltage induced into the collector winding of transformer T1, and prevents it from having any effect on the remainder of the circuit. Consequently, as the collector current decreases from maximum to zero, the collector voltage increases in the negative direction from the negative value of V_{CC1} to the more negative value of V_{CC2} , and the circuit returns to the quiescent state.

Any change in current in the collector winding of transformer T1 also induces a changing voltage into the tertiary, or output, winding of the transformer. The polarity of this output voltage is determined by grounding the proper terminal of the output winding. As shown in the circuit schematic, terminal 6 is grounded. Therefore, in this case, a positive output pulse results (for a negative output pulse, terminal 5 is grounded instead).

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of multiplier resistance employed on the low-voltage ranges of the standard 20,000-ohms-per-volt meter. Be careful to observe proper polarity when checking continuity with an ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. A no-output condition may be caused by an improper input trigger, a lack of supply voltage, or a defective circuit component. First, use an oscilloscope to observe the input trigger voltage waveform, and compare it with the one shown in the equipment instruction book to determine whether the proper input trigger is applied. Next, use a vacuum-tube voltmeter to measure the supply voltage and eliminate the possibility of a defective power supply. If the proper input trigger is applied and the normal supply voltage is present, further checks must be made to locate the defective circuit component. Use an in-circuit capacitor checker to check capacitors C1 and C2 for open circuits and leakage. Use an ohmmeter to check resistor R1 and transformer T1 for continuity and proper resistance value. Also use the ohmmeter as

a diode tester, to check the forward and reverse resistance of diodes CR1 and CR2.

Low or Distorted Output. Low supply voltage, a defective diode (CR1 or CR2), a defective transistor (Q1) or a faulty transformer (T1) may cause either low-amplitude or distorted output pulses. Measure the supply voltage with a vacuum-tube voltmeter to be certain that the power supply is not at fault. If the normal supply voltage is present, use an ohmmeter or diode tester to check diodes CR1 and CR2 for an adequate front-to-back ratio. If neither diode is defective, the fault is probably in either transistor Q1 or transformer T1.

PULSE-FREQUENCY DIVIDER (ELECTRON TUBE)

Application.

The pulse-frequency divider is used to produce high-amplitude pulses at a submultiple of the input trigger pulse frequency for use as timing or synchronizing pulses in radar and communications equipment.

Characteristics.

Output pulse frequency is a submultiple of the input pulse frequency.

Frequency-division ratio can be adjusted within a small range.

Requires a high-impedance trigger source which produces positive trigger pulses.

Output pulse width and rise time are determined primarily by the transformer characteristics.


Output pulse polarity is determined by the phasing of the transformer output (tertiary) winding.

Circuit Analysis.

General. The operation of the pulse-frequency divider is similar to that of other types of triggered blocking oscillators. However, the pulse-frequency divider is designed so that, instead of producing output pulses at the same frequency as the input pulse frequency, it produces output pulses at a frequency which is only a fraction of the input pulse frequency. In other words, the circuit divides the input pulse frequency down to a lower frequency. The ratio of the input pulse frequency to the output pulse frequency is called the *division ratio*. Although pulse-frequency divider circuits have been designed with

division ratios as high as 100:1, a low division ratio (less than 6:1) gives the best stability. Consequently, most pulse-frequency dividers are designed to operate at low division ratios.

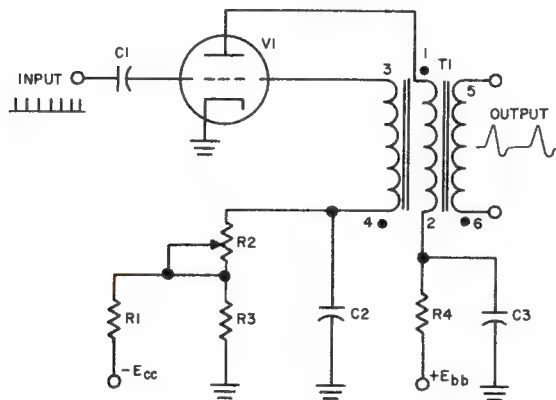Circuit Operation. The accompanying circuit schematic illustrates a pulse-frequency divider with a division ratio that can be adjusted between 2:1 and




Pulse-Frequency Divider

5:1. Transformer T1 provides the coupling (inductive feed-back) between the plate and the grid of triode V1. Terminals 1 and 2 connect to the plate (primary) winding, terminals 3 and 4 connect to the grid (secondary) winding, and terminals 5 and 6 connect to the output (tertiary) winding. The positive trigger pulses are applied through coupling capacitor C1 to the grid of triode V1. Capacitor C2 and resistors R2 and R3 make up the grid R-C circuit. Resistor R2 is variable and allows the time constant of this R-C circuit to be adjusted for the desired division ratio. Resistors R1 and R3 form a voltage-divider network which supplies fixed grid bias voltage for triode V1. Resistor R4 and capacitor C3 form a conventional plate decoupling network.

The following illustration shows the trigger-, grid-, plate-, and output-voltage waveforms in their proper time relationship.

In the quiescent condition (with no trigger pulse applied), V1 is held at plate-current cutoff by the fixed negative bias taken from the voltage divider made up of resistors R1 and R3, and applied through

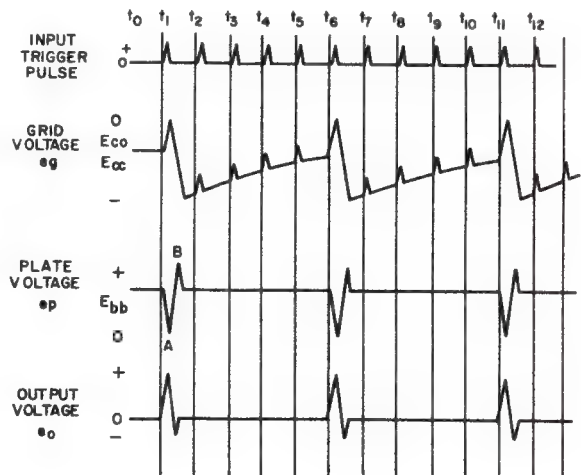grid resistor R2 and the grid winding of transformer T1 to the grid of V1 (time t_0 on the waveform illustration).



Trigger-, Grid-, Plate-, and Output-Voltage Waveforms

When the first positive trigger pulse is applied to the grid of triode V1 through coupling capacitor C1, it drives the grid above cutoff and causes the tube to conduct (time t_1 on the waveform illustration). The increasing plate current flowing through the plate winding (terminals 1 and 2) of transformer T1 produces a magnetic field in the transformer. The changing magnetic field induces a feedback voltage into the grid winding of transformer T1. The transformer phasing the polarity are such that the induced feedback voltage drives the grid of triode V1 more positive, and the plate of capacitor C2 which is connected to the negative end of the grid winding more negative. Thus, the induced feedback voltage causes two things to occur simultaneously: the capacitor charges to a higher potential, and the tube is biased more positive. The increased positive bias causes the plate current of triode V1 to increase further. The increasing plate-current flow through the plate winding of transformer T1 causes the magnetic field in the transformer to increase accordingly, and induces a still larger voltage into the grid winding of


transformer T1. This continuous increase in feedback voltage, grid voltage, and plate current produces a *regenerative-feedback* action which quickly drives the tube toward plate-current saturation. As the grid of triode V1 is driven more and more positive, grid current eventually begins to flow. The flow of grid current through the grid winding of transformer T1 to capacitor C2 causes the capacitor to quickly charge to its maximum negative value.

When plate-current saturation is reached (point A on the plate-voltage waveform), the plate current can no longer increase. Consequently, the magnetic field in transformer T1 no longer increases, and no feedback voltage is now induced into the grid winding. The grid of triode V1 is therefore driven negative by the large negative charge on capacitor C2. This negative grid voltage causes the triode plate current to decrease. As the plate current through the plate winding of transformer T1 decreases, the magnetic field in the transformer decreases accordingly, inducing a feedback voltage of opposite polarity into the grid winding of the transformer. This induced feedback voltage drives the grid of triode V1 further negative, increasing the negative grid bias, and causing plate-current flow through the plate winding of transformer T1 to decrease still further. As previously explained, the regenerative feedback from the plate to the grid of triode V1 produces a continuous cycle which causes the grid to be driven far below cutoff. As plate-current occurs, the plate current ceases to flow, and the magnetic field in the transformer collapses. The collapsing magnetic field induces into the plate winding of transformer T1 a voltage of such polarity that it tends to keep current flowing in the same direction as the original plate-current flow (that is, the induced voltage is series-aiding with the plate-supply voltage). The result of adding these voltages is a momentary increase in plate voltage over and above the plate-supply voltage, called *overshoot* (point B on the plate-voltage waveform). As the magnetic field decreases to zero, the induced voltage (overshoot) decreases accordingly, and the plate voltage returns to the normal, quiescent value.

When plate current ceases, the charge on capacitor C2 is no longer sustained, and the capacitor discharges through resistors R2 and R3 towards the negative fixed-bias value. Since the time constant of

this R-C circuit is very large, capacitor C2 discharges very slowly, and its potential decreases only a small amount by the time the plate pulse and overshoot are completed. The discharge time of the circuit is, in fact, many times longer than the input pulse repetition period. Consequently, the next input trigger pulse (time t_2 on the waveform illustration) occurs while capacitor C2 is still discharging and reducing the bias towards the fixed cutoff bias value. This positive trigger pulse (number 2), when combined with the negative grid voltage remaining on capacitor C2, is not of sufficient amplitude to raise the grid of triode V1 above cutoff. Therefore, trigger pulse number 2 has no effect on the operation of the circuit, and triode V1 remains cut off with capacitor C2 still discharging. The same result occurs during the next three input trigger pulses (times t_3 , t_4 , and t_5 on the waveform illustration). However, when the next input trigger pulse (time t_6 on the waveform illustration) occurs, capacitor C2 is now discharged to nearly the fixed negative bias voltage across resistor R3 (cutoff bias). Therefore, when trigger pulse number 6 is combined with the negative grid voltage remaining on capacitor C2, the resulting pulse is of sufficient amplitude to again drive the grid of triode V1 above cutoff and cause the tube to conduct. Thus, the sixth trigger pulse causes the circuit to begin another cycle of operation. The pulse-frequency divider produces an output pulse as previously explained, and then remains inactive for the next four input trigger pulses. It produces an output pulse for every fifth input pulse. Therefore, the circuit is said to have a division ratio of 5:1.

The division ratio of the pulse-frequency divider is entirely dependent upon the discharge time of capacitor C2, which is determined by the time constant of the grid R-C circuit. Resistor R2 is made variable so that the time constant of the R-C circuit can be adjusted for the desired output frequency. If the value of resistor R2 is decreased, the time constant of the R-C circuit decreases and capacitor C2 discharges more quickly. Thus by proper adjustment of resistor R2, the circuit will operate on every fourth input trigger pulse, giving a division ratio of 4:1. As the value of resistor R2 is decreased still further, the division ratio decreases accordingly. The following illustration shows the trigger- and grid- voltage waveforms for two different frequency-division ratios.

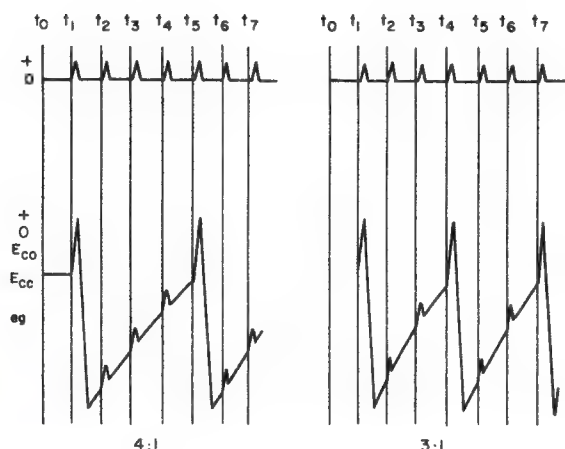

Trigger- and Grid- Voltage Waveforms for
Two Settings of Resistor R2

Failure Analysis.

General. Since the output signal of the pulse-frequency divider is dependent upon the input signal, it is important to be certain that the proper trigger pulses are applied. If the proper input trigger pulses are not applied, the output from the circuit, if present at all, will be unstable or of the wrong frequency. Therefore, the first step in trouble-shooting this circuit is to use an oscilloscope to observe the input waveform, and compare it with the waveform shown in the equipment instruction book to be certain that it is of the proper polarity, amplitude, and frequency.

No Output. In addition to an improper input signal, a no-output condition may be caused by a lack of plate-supply voltage, a fault in the grid circuit, a fault in the plate circuit, a defective tube, or an open output winding of transformer T1. After checking the input signal with an oscilloscope (as explained in the previous paragraph), use the oscilloscope to observe the waveform at the grid of triode V1. If no signal appears at this point, capacitor C1 is open and must be replaced. If the proper grid-voltage waveform is observed, use the oscilloscope to observe the waveform on the plate of triode V1. A proper plate-voltage waveform indicates that the output winding of transformer T1 is defective. If no signal is observed on the plate of triode V1, voltage and resistance checks must be made to isolate the defective com-

ponent. Use a high-resistance voltmeter to measure the plate-supply voltage and determine whether the power supply is at fault. Next, use the voltmeter to measure the voltage on the plate of triode V1. If no plate voltage is present, plate circuit components T1 (primary winding), C3, or R4 are either open or shorted. Use an ohmmeter to check continuity and resistance, and isolate the defective component. If the proper plate voltage is present, either the tube is defective, transformer T1 (secondary winding) is open, resistors R1, R2, or R3 are open, or capacitors C1 or C2 are shorted. Use an ohmmeter to isolate the defective component.

Improper Division Ratio or Unstable Output. An improper input signal, an improper bias-supply voltage, a defective tube, an open or shorted grid circuit, or a defective transformer, T1, may cause either an improper division ratio or an unstable output. After checking the input signal with an oscilloscope (as explained previously), use a high-resistance voltmeter to measure the bias-supply voltage. If the bias-supply voltage is correct, the trouble is in the divider circuit and not in the power supply. Use an ohmmeter to check the grid circuit of the divider for open or shorted components (C1, C2, R1, R2, R3). Triode V1 may also be at fault. Replace the tube with one known to be good, and if this still does not correct the trouble, transformer T1 is probable shorted.

Low Output. A low output may be caused by three conditions: low plate voltage, low tube emission, or excessive circuit loading. Use a high-resistance voltmeter to measure the plate-supply voltage and eliminate the possibility of a faulty power supply. Since defects in capacitor C3 or resistor R4 may also cause low plate voltage, use an ohmmeter to check these components. The low output may also be caused by low emission in triode V1. If replacing the tube with a good one does not correct the trouble, the low output may be caused by excessive circuit loading. Such a condition may be caused by shorted turns in transformer T1.

DISTANCE-MARK DIVIDER (ELECTRON TUBE)

Application.

The distance-mark divider is used to produce short time duration pulses at a submultiple of the input trigger frequency for use as distance marks in radar display indicators.

Characteristics.

Produces output pulses at a submultiple of the input trigger pulse frequency.

Requires a low-impedance trigger source which produces positive trigger pulses.


Output consists of positive pulses taken from the cathode of the tube.

Output pulse width and rise time are determined primarily by the transformer characteristics.

Circuit Analysis.

General. The distance-mark divider is a specific application of the pulse-frequency divider discussed earlier in this section of the Handbook. Like the pulse-frequency divider, the distance-mark divider produces output pulses at a submultiple of the input pulse frequency. That is, it divides the input pulse frequency down to a lower frequency. The ratio of input pulse frequency to output pulse frequency is called the *division ratio* of the circuit. While the division ratio of many pulse-frequency divider circuits is adjustable within a small range, the division ratio of the distance-mark divider is normally fixed (usually 2:1 or 3:1). In this way, the circuit can be designed to give the desired characteristics in the output pulse. Moreover, taking the output from the cathode of the tube also helps to produce the desired output pulse shape and eliminates the overshoot present in other types of blocking oscillators.

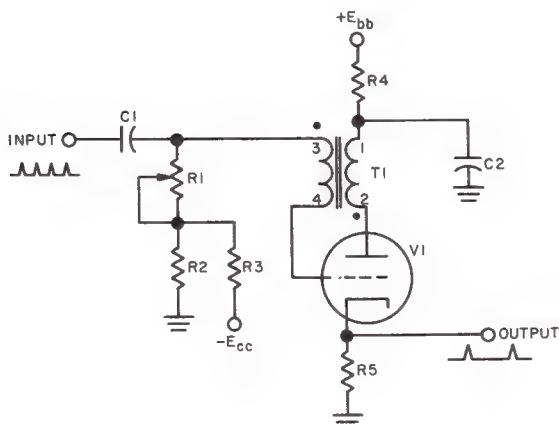
Circuit Operation. The accompanying circuit schematic illustrates a distance-mark divider with a division ratio of 3:1.



Distance-Mark Divider

Transformer T1 provides the coupling (inductive feedback) between the plate and the grid of triode V1. Terminals 1 and 2 connect to the plate (primary) winding, and terminals 3 and 4 connect to the grid (secondary) winding. The input trigger pulses are applied through grid capacitor C1 and the grid winding of transformer T1 to the grid of triode V1. The division ratio of the distance-mark divider is determined by the R-C circuit made up of capacitor C1 and resistors R1 and R2. Resistor R1 is variable and allows the circuit to be adjusted to compensate for variations in component values, supply voltages, and input trigger pulse amplitude. Resistors R2 and R3 form a voltage divider which provides fixed negative grid bias for triode V1. Resistor R4 and capacitor C2 form a conventional plate decoupling network. The output is taken across resistor R5, which is the cathode resistor for triode V1.

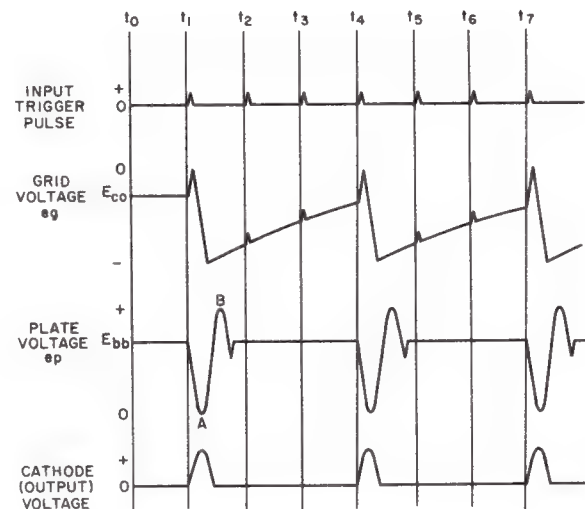The following illustration shows trigger-, grid-, plate and cathode-voltage waveforms in their proper time relationship.



Trigger-, Grid-, Plate-, and Cathode-Voltage Waveforms

In the quiescent condition (with no trigger pulse applied), triode V1 is held at plate-current cutoff by the fixed negative bias taken from the voltage divider made up of resistors R2 and R3, and applied through grid resistor R1 and the grid winding of transformer T1 to the grid of V1 (time t_0 on the waveform illustration).

When the first positive trigger pulse is applied through grid capacitor C1 and the grid winding of transformer T1 to the grid of triode V1, it drives the grid above cutoff and causes the tube to conduct (time t_1 on the waveform illustration). The increasing current flowing through the plate winding of transformer T1 produces a magnetic field in the transformer. The changing magnetic field induces a feedback voltage into the grid winding of transformer T1. The transformer phasing and polarity are such that the induced feedback voltage drives the grid of triode V1 more positive and the plate of capacitor C1 which is connected to the negative end of the grid winding more negative. Thus, the induced feedback voltage causes two things to occur simultaneously: the capacitor charges to a higher potential, and the tube is biased more positive. The increased positive bias causes the plate current of triode V1 to increase further. The increasing plate current flow through the plate winding of transformer T1 causes the magnetic field in the transformer to increase accordingly, and induce a still larger voltage into the grid winding. This continuous increase in feedback voltage, grid voltage, and plate current produces a *regenerative feedback* action which quickly drives the tube toward plate current saturation. As the grid of triode V1 is driven more and positive, grid current eventually begins to flow. The flow of grid current through the grid winding of transformer T1 to capacitor C1 causes the capacitor to quickly charge to its maximum negative value.

When plate-current saturation is reached (point A on the plate-voltage waveform), the plate current can no longer increase. Consequently, the magnetic field in transformer T1 no longer increases, and no feedback voltage is now induced into the grid winding. The grid of triode V1 is therefore driven negative by the large negative charge on capacitor C1. This negative grid voltage, and the positive cathode voltage caused by current flow through cathode resistor R5, cause the triode plate current to decrease. As the plate current through the plate winding of transformer T1 decreases, the magnetic field in the transformer decreases accordingly, inducing a feedback voltage of opposite polarity into the grid winding of the transformer. This induced feedback voltage drives the grid of triode V1 further negative, increasing the negative grid bias, and causing plate-current flow through the plate winding of transformer T1 to decrease still further. As previously explained, the

regenerative feedback from the plate to the grid of triode V1 produces a continuous cycle of operation which causes the grid to be driven far below cutoff. As plate-current cutoff occurs, the plate current ceases to flow and the magnetic field in the transformer collapses. The collapsing field induces a momentary surge of voltage called *overshoot*, into the plate winding of transformer T1 (point B on the plate-voltage waveform). However, since triode V1 is cut off, no current can flow through cathode resistor R5, and the overshoot is not present in the output.

When plate current ceases to flow, the charge on capacitor C1 is no longer sustained, and the capacitor discharges through resistors R1 and R2 toward the fixed negative bias value. The time constant of this R-C circuit is very large, and the discharge time of capacitor C1 is many times longer than the input trigger pulse repetition period. Consequently, the next input trigger pulse (time t_2 on the waveform illustration) occurs while capacitor C1 is still discharging and reducing the bias toward the fixed cutoff bias value. This positive trigger pulse (number 2), when combined with the negative grid voltage remaining on capacitor C1, is not of sufficient amplitude to raise the grid voltage of triode V1 above cutoff. Therefore, trigger pulse number 2 has no effect on the operation of the circuit, and triode V1 remains cut off with capacitor C1 still discharging. The same result occurs during the next input trigger pulse (time t_2 on the waveform illustration). However, when the next input trigger pulse (time t_4 on the waveform illustration) occurs, capacitor C1 is discharged to nearly the fixed negative bias voltage across resistor R2 (cutoff bias). Therefore, when trigger pulse number 4 is combined with the negative grid voltage remaining on capacitor C1, the resulting pulse is of sufficient amplitude to again drive the grid of triode V1 above cutoff and cause the tube to conduct. Thus, the fourth trigger pulse causes the circuit to begin another cycle of operation. The distance-mark divider produces an output pulse as previously explained, and then remains inactive for the next two input trigger pulses. It produces an output pulse for every third input pulse. Therefore, the circuit is said to have a division ratio of 3:1.

The division ratio of the distance-mark divider is entirely dependent upon the discharge time of capacitor C1, which is determined by the time constant of the grid R-C circuit. Thus, the distance-mark divider can be made to produce different division

ratios by using various component values in the grid R-C circuit. Although resistor R1 is variable, and will change the time constant of the circuit somewhat, this range is not normally broad enough to change the division ratio. Normally, resistor R1 is used only to adjust the circuit to compensate for variations in trigger pulse amplitude and supply voltages.

Failure Analysis.

No Output. A no-output condition may be caused by an improper input signal, a lack of plate-supply voltage, a fault in the grid circuit, a fault in the plate circuit, a fault in the cathode circuit, or a defective tube. After checking the input signal with an oscilloscope to be certain that the proper input is applied, use the oscilloscope to observe the waveform at the grid of triode V1. If no signal appears at this point, either capacitor C1 or the grid winding of transformer T1 is open. Use an ohmmeter to make resistance checks and isolate the defective component. If the proper grid-voltage waveform is observed, further voltage and resistance checks must be made to isolate the defective component. Use a high-resistance voltmeter to measure the plate-supply voltage and determine whether the power supply is at fault. Next, measure the voltage on the plate of triode V1. If no plate voltage is present, plate components T1 (primary winding), R4, or C2 are either open or shorted. Use an ohmmeter to check continuity and resistance, and isolate the defective component. If the proper plate voltage is present, either the tube is defective, transformer T1 (secondary winding) is open, or resistors R1, R2, R3, or R5 are open or shorted. Use an ohmmeter to isolate the defective component.

Improper Division Ratio or Unstable Output. An improper input signal, an improper bias-supply voltage, a defective tube, an open or shorted grid circuit, or a defective transformer may cause either an improper division ratio or an unstable output. After checking the input signal with an oscilloscope to be certain that it is of the proper amplitude and frequency, use a high-resistance voltmeter to measure the bias-supply voltage. If the bias-supply voltage is correct, the trouble is in the divider circuit and not in the power supply. Use an ohmmeter to check the grid circuit of the divider for open or shorted components

(C1, R1, R2, R3). Triode V1 may also be at fault. Replace the tube with one known to be good. If this still does not correct the trouble, transformer T1 is probably shorted.

Low Output. A low output is usually caused either by low plate voltage or by low tube emission. Use a high-resistance voltmeter to measure the plate-supply voltage and eliminate the possibility of a faulty power supply. Since defects in capacitor C2 or resistor R4 may also cause low plate voltage, use an ohmmeter to check these components. If these checks fail to locate the trouble, the low output is probably caused by low emission in triode V1.

SHOCK-EXCITED RINGING OSCILLATOR (ELECTRON TUBE)

Application.

The shock-excited ringing oscillator produces a short series of r-f oscillations each time an input gate is applied. The r-f oscillations are normally used as distance marks in radar indicators.

Characteristics.

Requires a high-impedance, negative input gate.

Produces an output only when gated.

R-F output pulse duration is equal to that of the input gate.


Uses a high-Q resonant tank circuit to produce an r-f output.

Output frequency is determined by the tank-circuit inductance and capacitance values.

Circuit Analysis.

General. The shock-excited ringing oscillator uses a parallel-resonant L-C (tank) circuit to produce an r-f output. An electron tube is used as a switch to control (gate) the r-f oscillations. While the basic circuit discussed below serves to illustrate the principles of operation of the shock-excited ringing oscillator, it is not suitable for use in practical circuits. A typical practical circuit is discussed after the basic circuit operation is established.

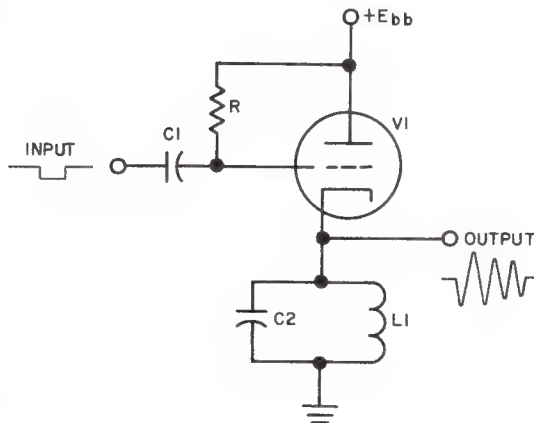Circuit Operation. The accompanying circuit schematic illustrates a basic shock-excited ringing oscillator.




Basic Shock-Excited Ringing Oscillator

In the quiescent state (with no negative gate applied), positive grid bias is applied from the plate supply through grid resistor R1 to the grid of triode V1, and causes the tube to conduct heavily near plate-current saturation. Electron flow is from ground, through inductor L1 and the tube to the plate supply, building up a magnetic field around the inductor. So long as a negative gate is not applied, the circuit remains in this quiescent state (triode V1 conducting heavily and no r-f output).

When a negative input-gate is applied through coupling capacitor C1 to the grid of triode V1, it instantaneously drives the grid below plate-current cutoff, and holds it at cutoff for the duration of the input gate. Plate-current flow through inductor L1 abruptly ceases, and the magnetic field around the inductor collapses. The collapsing magnetic field induces into the inductance a voltage of such polarity that it tends to keep current flowing in the same direction. This is, the induced voltage causes a current to flow from ground toward the cathode of triode V1. The triode, however, is biased below cutoff by the negative gate; therefore, no current will flow through the tube. Consequently, the induced current flows around the tank circuit and charges capacitor C2 negative with respect to ground. When the magnetic field has completely collapsed, no further voltage is induced into inductor L1, and the induced current ceases to flow in the tank circuit. Since there is no longer any induced voltage sustain the charge on capacitor C2, the capacitor discharges back through

inductor L1. The capacitor discharge current flowing through inductor L1 builds up a magnetic field around the inductor which is of opposite polarity from the original magnetic field. When capacitor C2 is full discharged, current flow around the tank circuit again ceases, and the magnetic field around inductor L1 again collapses and induces into the inductance a voltage which tends to keep current flowing in the same direction. This induced voltage causes current to flow around the tank circuit and charges capacitor C2 positive with respect to ground. After the magnetic field completely collapses, the charge on the tank capacitor is no longer sustained, and the capacitor again discharges through inductor L1, once again building up a magnetic field around the inductor in the original direction. This cycle of charge and discharge continues to repeat, producing a *ringing* effect in the tank circuit. That is, the capacitor and inductor charge and discharge alternately, causing the tank circuit to oscillate at a radio-frequency rate. Since the tank circuit has a very high Q (low loss), the r-f oscillations continue for many cycles. Because of the loss in the tank circuit produced by the d-c resistance of the inductor, successive oscillations gradually decrease in amplitude as the energy in the tank circuit is dissipated by this resistance. The resulting output waveform across the tank circuit is a series of damped oscillations, as shown in the following illustration.

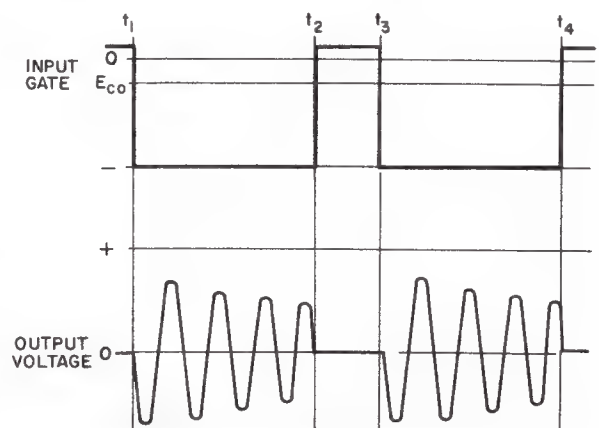

Input Gate and Output-Voltage Waveforms

The damped oscillations continue until the end of the input gate. When the negative input-gate ends, the positive bias supplied by grid resistor R1 resumes control and causes triode V1 to again conduct heavily

near plate-current saturation. When the tube conducts, the heavy plate-current flow through inductor L1 produces a magnetic field around the inductor in one unchanging direction, which effectively shunts the tank circuit and decreases the circuit Q. Consequently, the r-f oscillations are effectively damped out very quickly. The heavy plate current flowing through inductor L1 once again builds up a steady magnetic field around the inductor which effectively prevents any possibility of r-f oscillation, and the circuit remains in the quiescent (no-output) state until the next input gate is applied.

Since triode V1 is cut off while output oscillations are being produced, the frequency of the output oscillations is not affected by the tube. Thus, the output frequency is determined solely by the values of inductance and capacitance in the tank circuit. The duration of the train of r-f output oscillations is determined solely by the length of time triode V1 remains cut off, and is therefore controlled by the duration of the input gate.


The basic shock-excited ringing oscillator just discussed always produced damped oscillations when an input gate is applied. Since these oscillations decrease in amplitude, they are not suitable for many applications, particularly for producing distance marks. The following circuit schematic illustrates a practical type

of shock-excited ringing oscillator which produces r-f oscillations of a constant amplitude when the input gate is applied.

The two-tube shock-excited ringing oscillator shown in the illustration is actually a switched Hartley oscillator (see Section 7 of this Handbook for a detailed discussion of Hartley circuit operation). The circuit consisting of triode V2, capacitor C2, inductor L1, and Resistor R3 is a conventional series-fed Hartley oscillator, consisting of triode V1, capacitor C1, and resistors R1 and R2 is a switching circuit which controls the operation of the Hartley oscillator.

In the quiescent state (with no negative gate applied), no bias is applied to the grid of triode V1 and the tube conducts heavily near plate-current saturation. The electron flow is from ground, through inductor L1, triode V1, and resistor R2 to the plate supply, building up a magnetic field around inductor L1. When triode V1 is conducting, the heavy plate-current flow through inductor L1 produces a steady magnetic field around the tank inductor which effectively shunts the tank circuit and prevents the oscillator from functioning. Consequently, no r-f output oscillations are produced and the circuit remains in this state.

When a negative input-gate is applied to the grid of triode V1 through coupling capacitor C1, it drives the grid far below cutoff. As plate current ceases to flow through tank inductor L1, the magnetic field around it collapses, inducing a voltage into the inductor which tends to keep current flowing in the same direction as the original plate-current flow (that is, from ground thru the inductor to the cathode of triode V1). As in the basic circuit discussed previously, the induced current cannot flow through triode V1 (which is cut off); consequently, it flows around the tank circuit, charging capacitor C2 and initiating a ringing effect. In this practical circuit, however, any potential across the tank is also applied to the grid of oscillator tube V2, and the oscillator section of the circuit functions as a normal Hartley oscillator, producing oscillations of a constant amplitude in the tank circuit. The oscillator portion of this circuit replaces the energy dissipated in the tank coil resistance so that the resulting oscillations are always of constant amplitude. Thus, as long as the negative gate is applied, triode V1 remains cut off, and the oscillator portion of the circuit operates, producing constant-amplitude r-f oscillations.

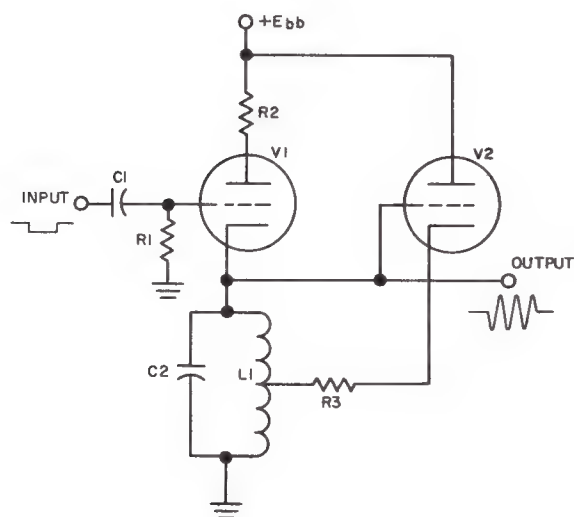

Typical Shock-Excited Ringing Oscillator

The oscillator operates until the end of the negative input gate. When the negative gate ends, the grid bias on triode V1 returns to zero, and the triode again begins to conduct heavily near plate-current saturation. When the tube conducts, the heavy current flow through inductor L1 produces a steady magnetic field around the tank inductor, effectively damping out the r-f oscillations very quickly. Thus the circuit is once again operating in the quiescent state, with triode V1 conducting heavily near saturation, and no r-f output.

The practical shock-excited ringing oscillator produces r-f oscillations of constant amplitude when a negative input gate is applied. As in the basic shock-excited ringing oscillator, the output frequency is determined by the values of inductance and capacitance in the tank circuit, and the duration of the r-f output is determined by the length of the input gate. The output waveform is the same as that shown for the basic circuit, except that all the oscillations are of constant amplitude.

Failure Analysis.

No Output. Failure of the shock-excited ringing oscillator to produce an output when the gate is applied may be caused by a defective switching circuit, by a defective oscillator circuit, or by a lack of plate-supply voltage. To isolate the trouble to one portion of the circuit, temporarily remove triode V1. If continuous output oscillations are now produced, the trouble is in the switching section of the circuit. Use an ohmmeter to check capacitor C1 for a shorted condition, and resistors R1 and R2 for continuity and proper value. If none of these parts are defective, triode V1 is probably shorted. If continuous output oscillations are not produced when triode V1 is temporarily removed, the fault is either in the oscillator section of the circuit or due to a lack of plate-supply voltage. Use a high-resistance voltmeter to check the supply voltage and the plate voltage of triode V2. Proper values of these voltages indicate that the trouble is in the oscillator section of the circuit and not in the power supply. Use an ohmmeter to check capacitor C2 and inductor L1 for a shorted condition, and to check resistor R3 for continuity and proper value. If the trouble still persists, triode V2 is probably at fault.

Continuous R-F Output. Defects in the switching portion of the shock-excited ringing oscillator may cause the circuit to produce output oscillations

whether or not the input gate is present. Use an ohmmeter to check capacitor C1 and resistors R1 and R2 for a shorted or open condition. If none of these parts are defective, triode V1 is probably at fault.

Low Output. Defects in the oscillator portion of the circuit or a low plate-supply voltage may cause either low-amplitude output oscillations or damped (decreasing) output oscillations. First measure the plate-supply voltage with a high-resistance voltmeter to eliminate the possibility of low-supply voltage. If the plate-supply voltage is normal, the trouble is in the oscillator section of the circuit and not in the power supply. (If the output oscillations are damped, triode V2 is probably inoperative and should be replaced with a tube known to be good.) Use an ohmmeter to check inductor L1, capacitor C1, and resistor R3 for continuity of shorts. If no defective parts are found, triode V2 is probably defective.

SHOCK-EXCITED PEAKING OSCILLATOR (ELECTRON TUBE)

Application.

The shock-excited peaking oscillator is used to produce very narrow positive pulses at the beginning of each input gate for use as trigger or synchronizing pulses in radar modulators, display indicators, and other electronic devices.

Characteristics.

Requires a high-impedance, negative input gate.

Produces one very sharp positive pulse at the beginning of each negative input gate.

Produces one relatively broad negative pulse at the end of each negative input gate.


Uses a critically damped tank circuit to produce an output.

Shape of positive output pulse is determined by tank inductance and capacitance values.

Circuit Analysis.

General. The shock-excited peaking oscillator uses a critically damped resonant L-C (tank) circuit to produce a peaked output. An electron tube is used as a switch to control (gate) the tank circuit.

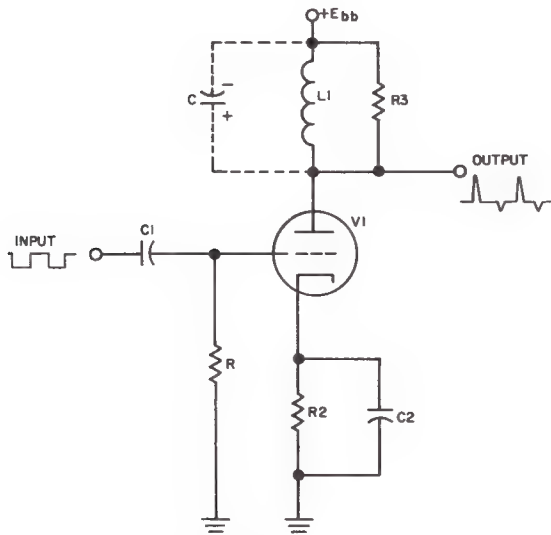
Circuit Operation. The accompanying circuit schematic illustrates a typical shock-excited peaking oscillator.



Shock-Excited Peaking Oscillator

Capacitor C1 and resistor R1 form a conventional R-C input circuit for triode V1, and capacitor C2 and resistor R2 form a conventional cathode bias circuit for the tube. Inductor L1 and its distributed capacitance, C, form a parallel-resonant tank circuit. Since the distributor capacitance is small, the resonant frequency of the tank circuit is very high (approximately 2 mc). This r-f tank is critically damped by resistor R3. That is, the value of resistor R3 is such that it allows the tank circuit to oscillate for only a half cycle after oscillation is started.

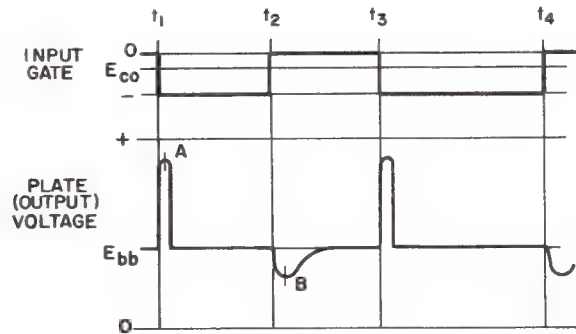The following illustration shows the input-gate and plate-voltage (output) waveform in their proper time relationship.



Input-Gate and Plate-Voltage Waveforms

In the quiescent state (with no negative input-gate applied), no bias is applied to the grid of triode V1, and the tube conducts heavily near plate-current saturation. The plate current is held constant by the cathode bias developed across cathode resistor R2. This constant plate current flowing through inductor L1 builds up a steady magnetic field around the inductance. So long as a negative gate is not applied, the circuit remains in this quiescent state.

When a negative gate is applied through coupling capacitor C1 to the grid of triode V1 (time t_1 on the waveform illustration), it instantaneously drives the grid far below cutoff, and holds it below cutoff for the duration of the input gate. Plate-current flow through inductor L1 abruptly ceases, and the magnetic field around the inductor collapses. The collapsing magnetic field induces into the inductance a voltage of such polarity that it tends to keep current flowing in the same direction as the original plate-current flow. This induced current flowing in

the inductor charges the distributed (tank) capacitance, C , negative on the plate-supply side of the capacitance and positive on the triode side of the capacitance (polarity as shown in schematic). Since the charge time of the capacitance is determined by the resonant frequency of the tank circuit, and the resonant frequency is very high, the capacitance charges very quickly to its maximum value. The potential across the charged capacitance is series-aiding with the plate-supply voltage, and the resultant voltage on the plate of triode V1 momentarily rises above the plate-supply voltage (point A on the plate-voltage waveform). When the magnetic field around the inductor completely collapses, there is no longer any induced voltage to sustain the charge on the distributed (tank) capacitance, the capacitance begins to discharge. Since the dc resistance or resistor R3 is much lower than the impedance of inductor L1 at the resonant frequency, the distributed capacitance discharges very quickly through the resistor, and the triode plate voltage quickly returns to the plate-supply value. Thus, the shock-excited peaking oscillator produces one very sharp positive pulse at the beginning of the negative input gate.

Triode V1 remains cut off, and no further output is produced until the end of the negative input gate. When the input gate ends (time t_2 on the waveform illustration), the grid bias on triode V1 returns to zero, and the triode again begins to conduct heavily near plate-current saturation. As plate current flows through inductor L1, a magnetic field builds up around the inductor. The increasing magnetic field induces into the inductance a voltage of such polarity that it tends to oppose the plate current flowing through the inductor. This induced voltage is series-opposing with the plate-supply voltage, and the resulting voltage on the plate of triode V1 momentarily drops below the plate-supply voltage (point B on the plate-voltage waveform). As the magnetic field around the inductance builds up to its maximum value and ceases to increase, the opposing induced voltage decreases to zero, and the triode plate voltage returns to the plate-supply value. Thus at the end of the negative input gate the shock-excited peaking oscillator produces a negative-going pulse and then returns to the quiescent state, with triode V1 conducting heavily near saturation and a steady unchanging magnetic field built up around inductor L1.

The output from the shock-excited peaking oscillator is a series of alternate positive- and negative-going pulses occurring respectively at the beginning and the

end of the negative input gate. Since the positive output pulses are much sharper, and of greater amplitude, than the negative-going output pulses, the positive pulses are normally the desired portion of the output. The negative-going output pulses are usually eliminated with a clipping or limiting circuit which passes only the desired positive output pulses.

Failure Analysis.

No Output. Failure of the shock-excited peaking oscillator to produce an output when the proper negative input gate is applied may be caused by a defective circuit component, a defective tube, or a lack of plate-supply voltage. After measuring the plate-supply voltage with a high-resistance voltmeter to be certain that the power supply is operating properly, use the voltmeter to measure the voltage on the cathode of triode V1. A lack of cathode voltage indicates that either resistor R2 or capacitor C2 is shorted, or the triode is faulty. If checking resistor R2 and capacitor C2 with an ohmmeter does not reveal a shorted component, triode V1 is probably at fault and should be replaced with a tube known to be good. If the proper voltage is measured on the cathode of triode V1, inductor L1 may be open or shorted, capacitor C1 may be open, or resistor R1 or R3 may be open or shorted. Use an ohmmeter to check these components for continuity, shorts, and proper resistance values. If these checks fail to locate a defective component, triode V1 is probably defective.

Low Output. Output pulses of low amplitude may be caused by low plate-supply voltage, low tube emission, or a defective cathode bias circuit. First, measure the plate-supply voltage with a high-resistance voltmeter to eliminate the possibility of a faulty power supply. If the proper plate-supply voltage is present, use an in-circuit capacitor checker to check cathode capacitor C2 for an open. If this capacitor is open, degenerative action in the cathode bias circuit will cause a low output. If both the plate-supply voltage and capacitor C2 are normal, low emission in triode V1 is probably the cause of the low-output condition. Replace triode V1 with a tube known to be good.

Distorted Output. Defects in the plate circuit of triode V1 may cause a distorted output. Use an ohmmeter to check shunt resistor R3 for continuity and the proper resistance value. If resistor R3 is not defective, inductor L1 is probably at fault.



SECTION 7 MULTIVIBRATORS

PART 7-1. ASTABLE

ASTABLE (FREE-RUNNING) MULTIVIBRATORS

General.

The term *astable multivibrator* refers to a class of multivibrator or relaxation-oscillator circuits that can function in either of two temporarily stable conditions and is capable of rapidly switching from one temporarily stable condition to the other. The astable multivibrator is frequently referred to as a *free-running multivibrator*. It is basically an oscillator consisting of two stages coupled so that the input signal to each stage is taken from the output of the other. One stage conducts while the other is cut off until a point is reached at which the stages reverse their condition; that is, the stage which had been conducting cuts off, and the stage that had been cut off conducts. Thus, the circuit becomes free-running because of the regenerative feedback, and the frequency of operation is determined primarily by its coupling-circuit constants rather than by an external synchronizing pulse.

In electron tube circuits, the frequency of operation can be as low as one-sixtieth of a Hz or as high as 100 kHz; in semiconductor circuits, the frequency of operation ranges from 400 Hz to 200 kHz.

The output of the astable multivibrator is usually nearly rectangular in form. A symmetrical output results when the R-C time constants of the coupling circuits are made equal. Rectangular pulses of almost any desired width (time duration) can be obtained by proportioning the R-C time constants of the coupling circuits with respect to one another; the resulting pulse output is unsymmetrical since the R-C time constants of the coupling circuits are no longer equal.

The operating frequency of the astable multivibrator can be changed by switching values of R or C, or both R and C, in the coupling circuits to alter the time constants. For example, a multivibrator designed to operate at 800 pps can be changed to a lower frequency, such as 400 pps, by simply switching additional capacitors into the circuit in parallel with the existing coupling capacitors to lower the repetition frequency.

The frequency stability of the multivibrator is somewhat better than that of the typical blocking oscillator. However, a disadvantage of the multivibrator is that its output impedance is essentially equal to the plate-load resistance and this resistance must be relatively high in order to obtain good frequency stability. Also, the negative-going waveform is generated at a much lower impedance than the positive-going waveform. Because a changing load will also affect the frequency stability, the output is sometimes fed to a cathode follower, in order to isolate the load from the multivibrator plate circuit. In some instances the desired output from the multivibrator is a differentiated waveform, and this waveform, in turn, is applied to the cathode follower; in this circuit configuration the load will have the least effect upon the multivibrator frequency stability.

BASIC ASTABLE (FREE-RUNNING) MULTIVIBRATOR (ELECTRON TUBE)

Application.

The basic (plate-to-grid coupled) astable multivibrator produces a square-wave output for use as trigger or timing pulses.

Characteristics.

Free-running oscillator; does not require trigger pulse to produce oscillations.

Operating frequency is determined primarily by the R-C time constants in the feedback (plate-to-grid) coupling circuits and by applied voltage.

Frequency stability of 3 percent can be obtained. Input trigger pulses may be applied to the circuit for synchronization to produce a stable output; it may be synchronized at the trigger-pulse frequency or integral submultiples thereof.


Symmetrical square- or rectangular-wave output is produced when the R-C time constants of the grid circuits are equal. Unsymmetrical output is produced when the R-C time constant of one grid circuit is purposely made several times greater than that of the other; for this condition the two tubes are cut off for unequal periods of time.

Output impedance is essentially equal to plate-load impedance.

Circuit Analysis.

General. The free-running plate-to-grid coupled multivibrator is a basic astable multivibrator. The circuit is fundamentally a two-stage R-C coupled amplifier with the output of the second stage coupled to the input of the first stage! Thus the output signal is fed back in the proper phase to reinforce the input signal; as a result, sustained oscillations occur.

Circuit Operation. The following circuit schematic illustrates two triode electron tubes in a basic free-running multivibrator circuit. Electron tubes V1 and V2 are identical-type triode tubes; although the accompanying schematic illustrates two separate triodes, a twin-triode is frequently used in this circuit. Capacitor C1 provides the coupling from the plate of V2 to the grid of V1; capacitor C2 provides the coupling from the plate of V1 to the grid of V2. Resistors R1 and R2 are the grid resistors for V1 and V2, respectively; resistors R3 and R4 are the plate-load resistors for V1 and V2, respectively.

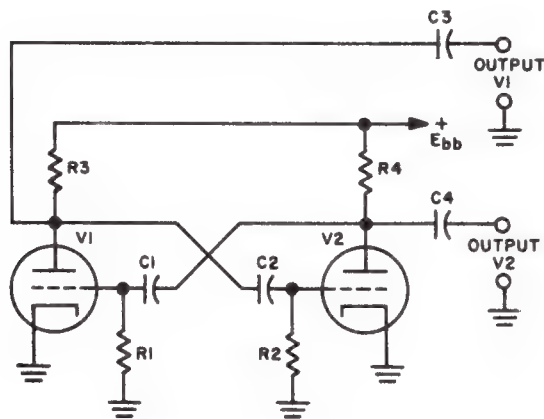

**Triode Plate-to-Grid Coupled
Astable Multivibrator**

Capacitor C1 and resistor R1 form an R-C circuit to determine the discharge time constant in the grid circuit of V1; capacitor C2 and resistor R2 determine the discharge time constant in the grid circuit of V2. Output pulses can be taken from the plate of either or both electron tubes. Capacitors C3 and C4 are the output coupling capacitors for V1 and V2, respectively.


When voltage is first applied to the circuit, the grids of both tubes are at zero bias and plate current

starts to flow through plate-load resistors R3 and R4. Also, capacitors C1 and C2 begin to charge when the applied voltage appears at the plate of each tube. If the constants of both stages of the circuit are alike, the currents through both tubes may at first be nearly equal. In practice, the symmetrical free-running multivibrator component values are held to close tolerances in order to obtain good frequency stability; the value of coupling capacitors C1 and C2 are at least 2 percent tolerance, grid resistors R1 and R2 are 1 percent tolerance, and plate-load resistors R3 and R4 are usually 5 percent tolerance. However, in spite of the close tolerance of the components, there will always be some slight difference in the two currents. This small difference in tube currents will cause a further unbalance, resulting in a regenerative action which rapidly switches the circuit to a condition wherein one tube is conducting maximum current and the other is cut off.

For example, if initially the current through tube V1 should be slightly greater than that through V2, the voltage drop across plate-load resistor R3 will be greater than the drop across resistor R4. This results in a lower plate voltage for V1. This decrease in plate voltage is coupled through coupling capacitor C2 to the grid of V2 as a negative-going instantaneous grid voltage which reduces the plate current of V2. When the current through V2 is decreased, the current through plate-load resistor R4 is also decreased; therefore, the voltage drop across resistor R4 decreases, resulting in a rise in the plate voltage of V2. This increase in plate voltage is coupled through coupling capacitor C1 to the grid of V1 as a positive-going instantaneous grid voltage which increases the plate current of V1. The drop across plate-load resistor R3 increases, the plate voltage of V1 decreases, and as before, the decrease in the plate voltage of V1 is coupled to the grid of V2 as a negative-going voltage. The regenerative switching action just described continues rapidly until V2 is cut off and V1 is at maximum conduction.

In order to cut off plate current in V2, the grid of V2 must be driven negative beyond the cutoff voltage. The negative grid voltage results from a charge on coupling capacitor C2. Since this charge leaks off through grid resistor R2, the grid voltage at V2 does not remain in a negative condition but starts to return to zero as C2 discharges through R2 and the cathode-to-plate conduction resistance of V1. When C2 discharges sufficiently and the grid voltage cutoff point

is reached, plate current once again starts to flow through V2, initiating another switching action similar to the first action described. However, this time as V2 conducts, coupling capacitor C1 discharges through grid resistor R1 to cut off the plate current in V1, and the switching action ends with V1 cut off and V2 at maximum conduction. Here again, the negative charge existing on coupling capacitor C1 must discharge through grid resistor R1 and tube V2 before the grid voltage cut off point is reached and V1 can conduct to initiate another switching action. The switching action repeats continuously with first one tube and then the other tube conducting.

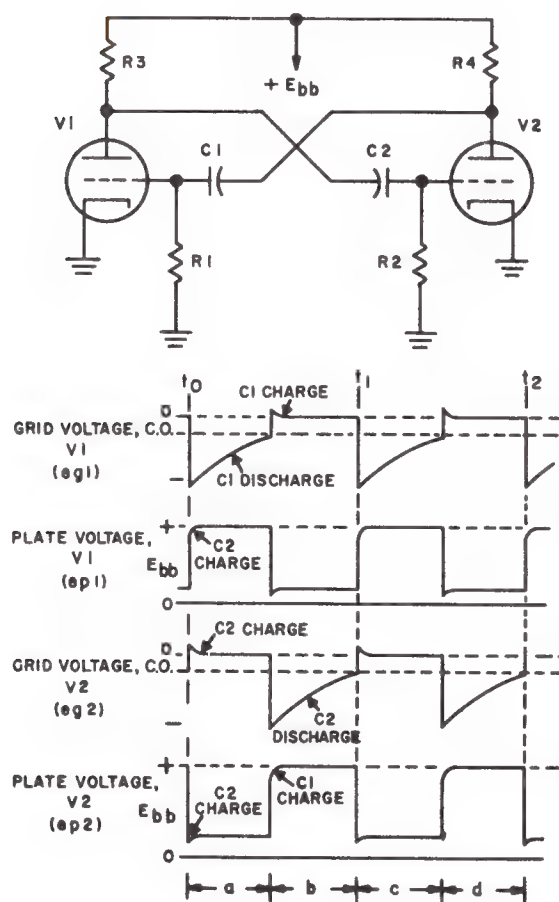

Theoretical Waveforms for a Symmetrical Free-Running Multivibrator

For the following discussion of circuit operation, refer to the accompanying illustration which shows a simplified schematic and waveforms for a symmetrical free-running multivibrator.

At time t_0 (start of time interval *a*) on the waveform illustration, the grid of V1 (e_{g1}) has been driven negative to cut off the tube, and, as a result, the plate voltage of V1 (e_{p1}) has risen rapidly to approach the supply-voltage value (E_{bb}). Coupling capacitor C2 is quickly charged through the low cathode-to-grid internal resistance of V2 and the plate-load resistor, R3. The voltage waveform at the plate of V1 (e_{p1}) is rounded off, and the waveform at the grid of V2 (e_{g2}) has a small positive spike of the same time duration as a result of the charging of coupling capacitor C2. Since at this time the grid of V2 is slightly positive, V2 conducts heavily and the plate voltage of V2 (e_{p2}) drops to a minimum. Note that the plate voltage waveform (e_{p2}) exhibits a small negative spike of the same time duration as the positive spike on the grid waveform (e_{g2}).

While coupling capacitor C2 is being charged, coupling capacitor C1 (previously charged) discharges through grid resistor R1 and through the conduction resistance of V2. Capacitor C1 cannot change its charge immediately; therefore, it produces a negative voltage (e_{g1}) across grid resistor R1, which decays at an exponential rate (toward zero) as capacitor C1 discharges. The rate of discharge is determined primarily by the R-C time constant of R1 and C1. Although the conduction resistance of V2 is included in the discharge path of C1, the resistance is small as compared with the resistance of R1, and can therefore be neglected.

When the negative voltage (e_{g1}) produced across grid resistor R1 decreases near the end of time interval *a* and reaches cutoff, V1 immediately conducts and the plate voltage of V1 (e_{p1}) drops to a minimum; the circuit now switches to the other condition with V2 cut off by the discharge of capacitor C2 through grid resistor R2. This condition is shown on the waveform illustration as the start of time interval *b*. Coupling capacitor C2 discharges through grid resistor R2 and through the conduction resistance of V1. The rate of discharge is determined primarily by the R-C time constant of R2 and C2. (The conduction resistance of V1 is small and can be neglected.)

When the negative voltage (e_{g2}) produced across grid resistor R2 decreases near the end of time interval *b* and reaches cutoff, V2 immediately conducts

and the plate voltage of V2 (e_{p2}) drops to a minimum; the circuit now switches to the other condition with V1 cut off by the discharge of capacitor C1 through grid resistor R1. This condition is shown on the waveform illustration as the termination of interval b at time t_1 .

In the discussion of circuit operation given above, the multivibrator was assumed to be a symmetrical (or balanced) multivibrator; that is, coupling capacitors C1 and C2 are equal, resistors R1 and R2 are equal, and plate-load resistors R3 and R4 are also equal. Therefore, the discharge time constants of R1 and C1 and of R2 and C2 are equal. Also, the time intervals (a , b , c , and d) between the switching actions are equal to one another. To obtain a pulse output which is unsymmetrical (asymmetrical or unbalanced), it is necessary to proportion the time constants in the coupling circuits so that one tube remains cut off for only a short period of time while the other is cut off for a much longer period. For example, if the time constant of R1 and C1 is made short compared to the time constant of R2 and C2, then V1 will be cut off for a short period of time while V2 will be cut off for a longer period. Thus, the time intervals a and c , shown on the waveform illustration will be short while time intervals b and d will be long.

The time interval for either output pulse may be approximated if the voltage change across the coupling capacitor, the R-C time constant of the discharge path, and the cutoff voltage of the tube are known. The approximate time interval, t , for the capacitor to discharge to cutoff may be determined by use of the following formula:

$$t \cong 2.30 RC \log \frac{E_c}{E_{co}}$$


where: t = time interval to discharge to cutoff (seconds)

E_c = maximum voltage change across capacitor

E_{co} = negative cutoff value for tube

R = resistance of grid resistor (megohms)

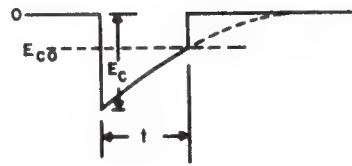C = capacitance of coupling capacitor (μf)



If the grid resistor, R , is returned to a positive voltage source, such as the plate-supply voltage (E_{bb}), the formula becomes:

$$t \cong 2.30 RC \log \frac{E_{bb} + E_c}{E_{bb} + E_o}$$

where: E_{bb} = plate-supply voltage

The natural operating frequency (Hertz) of the oscillator, f_o , may be calculated from the following formula:

$$f_o = \frac{1}{t_1 + t_2}$$

where: t_1 = time interval to discharge to cutoff for V1 grid circuit.

t_2 = time interval to discharge to cutoff for V2 grid circuit.

The free-running multivibrator may be synchronized with a stable external source to force the period of multivibrator action to be exactly the same as the synchronizing source. In this case the multivibrator is called a *driven* multivibrator. Synchronizing signals, when used, are applied to the grid of one multivibrator tube if the impedance of the synchronizing source is high, or to the cathode if the impedance of the source is low. In either case, the frequency of the synchronizing signal must be slightly higher than the natural operating frequency of the multivibrator so

that the synchronizing pulse occurs just prior to the time that normal switching action would occur.

The output of the multivibrator is taken from either or both plate circuits through an output-coupling capacitor (C3 or C4). In cases where it is desired to minimize the effect of a varying load impedance on the multivibrator frequency stability, a cathode follower is used for isolation.

Failure Analysis.

No Output. Assuming that the multivibrator is a free-running type and no synchronizing signal is applied, the applied plate and filament voltages should be measured to determine whether they are within specified values. If either coupling capacitor C1 and C2 should become leaky or shorted, a positive potential will be present on the grid of the associated tube and, as a result, the tube will conduct heavily; the other tube will also conduct heavily, since it will be at zero bias. A similar condition could exist if either coupling capacitor C1 or C2 should open; in this case the feedback necessary to sustain oscillations cannot occur and both tubes will conduct heavily because the grids are at zero bias. If the circuit is in a nonoscillating condition, the voltage at each plate should be measured to determine whether plate-load resistor R3 or R4 is open. If either is open, there will be no plate voltage present on the associated plate; also, the other tube will conduct heavily because of zero bias, and its plate voltage will be low. If either output coupling capacitor (C3 or C4) should become leaky or shorted, the input resistor of the following stage can form a voltage divider which also includes the associated plate-load resistor (R3 or R4). If the input resistor of the following stage is returned to ground or to a negative potential, voltage-divider action may reduce the voltage available at the plate of the multivibrator to the point where oscillations will cease; also, the additional current through the plate-load resistor (R3 or R4) may cause the resistor to burn out.

Incorrect Frequency or Pulse Width. The critical components governing the frequency and pulse width of the multivibrator are those in the coupling circuits. Any change in components governing the R-C discharge time constant will directly affect frequency and pulse width; a change in capacitor C1 or C2 or resistor R1 or R2 will have the greatest effect. A change in the value of plate-load resistor R3 or R4

will affect the amplitude of the output, and it will also have an effect upon the frequency, but not nearly as much as the components mentioned above.

A drift in frequency of the free-running multivibrator will generally occur if the applied plate voltage should change approximately 10 percent from the specified value; also, some frequency drift may occur if the filament voltage should drop below the specified value.

In a practical circuit, where the multivibrator is free-running and is not synchronized from an external source, means should be provided to adjust the applied plate voltage or to adjust the value of resistance in each grid circuit. This provision enables the circuit to be adjusted to the correct frequency and pulse width, and compensates for differences in individual tube characteristics when a tube substitution has been made.

If either output coupling capacitor (C3 or C4) should become leaky or shorted, the voltage-divider action which can occur may reduce the amplitude of the output waveform and cause the multivibrator to operate at a higher frequency, since the grid capacitor (C1 or C2) discharge time is dependent upon the amount of change in capacitor voltage. The operation of the following stage may also be affected by the change in grid-bias voltage resulting from the voltage-divider action.

BASIC ASTABLE (FREE-RUNNING) MULTIVIBRATORS (SEMICONDUCTOR)

Application.

The free-running astable multivibrator circuit is a basic circuit. It is normally used to produce a square-wave output for use as a trigger or timing pulse in electronic equipments; this basic circuit, when modified for application to switching circuitry, is representative of a class of circuits which perform computer logical operations (counting, shift register, and memory circuits), control functions (relay driver circuits), and a variety of similar applications in radar and communications systems.

Characteristics.

Free-running oscillator; does not require a trigger pulse to produce oscillations.

Operating frequency is determined primarily by the time constants in the feedback (collector-to-base) coupling circuits and by the applied voltage.

Symmetrical square-wave or rectangular-wave output is produced when the time constants of the coupling circuits are equal. Unsymmetrical output is produced when the time constant of one coupling circuit is purposely made several times greater than that of the other; for this condition the transistors are cut off or conducting for unequal periods of time.

Output taken from collector of either transistor in common-emitter circuit configuration.


Output impedance is very low when transistor is in conducting (on) state; output impedance is approximately equal to collector load resistance when transistor is in cutoff (off) state.

Circuit Analysis.

General. The free-running collector-coupled multivibrator is a basic astable multivibrator. The circuit is fundamentally a two-stage, R-C-coupled, common-emitter amplifier, with the output of the second stage coupled to the input of the first stage. Since the signal in the collector circuit of a common-emitter amplifier is reversed in phase with respect to the input to the base, a portion of the collector output of each stage is fed to the base electrode of the other stage. Thus, the output signal from each stage is fed back in the proper phase to reinforce the input signal on the base electrode of the other stage; as a result of this regenerative feedback, sustained oscillations occur.

The collector-coupled, common-emitter multivibrator circuit described in the following paragraphs is analogous to the basic plate-to-grid-coupled electron-tube multivibrator circuit described earlier in this section of the handbook.

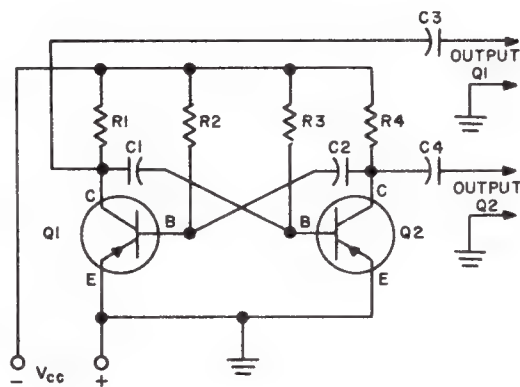Circuit Operation. The following circuit schematic illustrates two transistors in a basic free-running multivibrator circuit.



**Basic Free-Running Astable Multivibrator
Using PNP Transistors**


Transistors Q1 and Q2 are identical PNP transistors used in a common-emitter circuit configuration; either junction or point contact transistors may be used in this circuit. Resistors R1 and R4 are the collector load resistors for Q1 and Q2, respectively; R2 and R3 are the base-biasing resistors for Q1 and Q2, respectively. Capacitor C1 provides the coupling from the collector of Q1 to the base of Q2; capacitor C2 provides the coupling from the collector of Q2 to the base of Q1. Capacitor C1 and resistor R3 form an R-C circuit to determine the discharge time constant for the base of Q2; capacitor C2 and resistor R2 determine the discharge time constant for the base of Q1. Capacitors C3 and C4 are the output coupling capacitors for Q1 and Q2, respectively. An output waveform can be taken from the collector element of either transistor, or output waveforms can be taken from the collector elements of both transistors.

The common-emitter configuration illustrated uses a single-battery power source, V_{CC} . Forward bias for the base of transistor Q1 is obtained through the low-resistance emitter-base junction, which is in series with resistor R2 across the voltage source, V_{CC} ; since the base of Q1 is placed at a negative potential with respect to its emitter, the required forward bias for the PNP transistor is thereby established. In a like manner, forward bias for the base of transistor Q2 is obtained through the emitter-base junction and resistor R3. When voltage is first applied to the multivibrator, the current which flows in each collector load resistor, R1 and R4, is determined by the effective resistance offered by transistors Q1 and Q2 for a given value of base-bias voltage.

The multivibrator circuit shown in the schematic appears to be a balanced (or symmetrical) circuit, since each R-C-coupled stage is identical to the other; however, in spite of the use of close-tolerance components, there will always be minor differences in circuit resistances and in junction resistances within the transistors themselves. (A balanced circuit is assumed here and not necessarily a multivibrator designed for unsymmetrical output.) As a result of this inherent unbalance, the initial collector current (resulting from the forward-bias conditions set up by the emitter-base junction resistances and bias resistors R2 and R3) for each transistor is different, and the immediate effect produced by regenerative action between the coupled stages is that one transistor conducts while the other is cut off. For the purpose of this explanation, assume that initially more collector current flows through transistor Q1 than through transistor Q2; thus, as the collector current of Q1 increases, the voltage at the collector of Q1 decreases with respect to its emitter, or ground. In other words, the collector of Q1 becomes less negative and this, in effect, acts as a positive-going pulse, which is coupled through capacitor C1 to the base of transistor Q2. The positive-going pulse at the base of Q2 makes the base positive with respect to its emitter (ground) and, as a result, Q2 approaches cutoff. The collector current of Q2 decreases because of the reverse-bias action, and the voltage at the collector of Q2 increases, and approaches the supply voltage, $-V_{CC}$. In other words, the collector of Q2 becomes more negative and this, in effect, acts as a negative-going pulse, which is coupled through capacitor C2 to the base of transistor Q1. The negative-going pulse at the base of Q1 places the base negative with respect to its emitter

(ground), and the collector current of Q1 is further increased because of the forward-bias action. This regenerative process continues until Q1 is driven into saturation (as a result of increased forward-bias), and Q2 is cut off (as a result of the reverse-bias conditions).

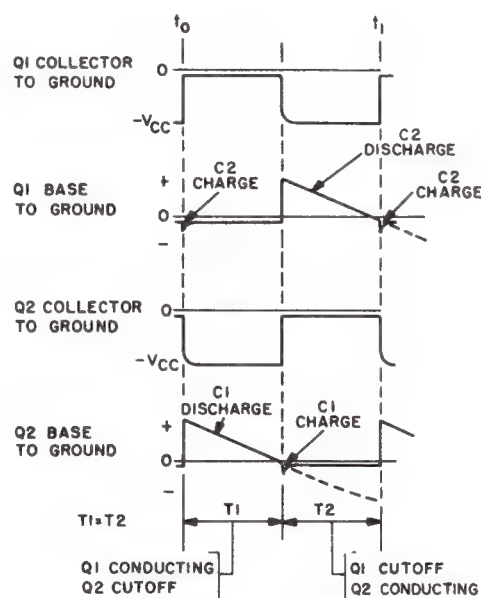For the following discussion of circuit operation, refer to the circuit schematic shown previously, and also to the waveforms shown in the following illustration.



Theoretical Waveforms for a Symmetrical Free-Running Multivibrator (Using PNP Transistors)

Assume that transistor Q1 is conducting and has just reached saturation. When Q1 is at saturation, its collector current no longer increases but rather becomes a constant value (see Q1 collector waveform for period T1); therefore, there is no further change in collector voltage to be coupled through capacitor C1 to the base of transistor Q2. The voltage at the base of Q1 is only a few tenths of a volt negative, and, as a result, capacitor C2 quickly charges (see Q1 base waveform for period T1) through the low resistance of R4 to a potential which is approximately equal to

$-V_{cc}$. Since the collector voltage at Q1 (Q1 is conducting heavily) is at nearly ground potential, capacitor C1 (previously charged) starts discharging (see Q2 base waveform for period T1) at a rate which is equal to the time constant $R3C1$, through transistor Q1, the voltage source, and resistor R3.

As capacitor C1 discharges, the voltage at the base of Q2 becomes less and less positive (negative-going) until a point is reached where reverse bias is no longer applied and Q2 is able to conduct (as shown in the Q2 base waveform at the end of period T1).

When the base of Q2 returns to a forward-bias condition, Q2 begins to conduct and its collector current begins to flow through load resistor R4. As the collector voltage at Q2 drops (see Q2 collector waveform for period T2), a changing (positive-going pulse) voltage is coupled through capacitor C2 to the base of transistor Q1. The voltage at the base of Q1 is only a few tenths of a volt negative, and, as a result of the charge on capacitor C2, reverse bias is applied to the base of Q1. Transistor Q1 is driven to cutoff, and the collector voltage of Q1 rises (see Q1 collector waveform for period T2). This rise, coupled through C1, will drive the base of Q2 further into the forward-bias condition. The voltage at the base of Q2 is only a few tenths of a volt negative, and the collector voltage at Q1 is approximately $-V_{cc}$; as a result, capacitor C1 quickly recharges (see Q2 base waveform for period T2) through the low resistance of R1 to a potential which is approximately equal to $-V_{cc}$. Since the collector voltage at Q2 (Q2 is conducting heavily) is at nearly ground potential (see Q2 collector waveform for period T2), capacitor C2 (previously charged) starts discharging at a rate which is equal to the time constant $R2C2$, through transistor Q2, the voltage source, and resistor R2.

As capacitor C2 discharges (see Q1 base waveform for period T2), the voltage at the base of Q1 becomes less and less positive (negative-going) until a point is


reached where reverse bias is no longer applied, and Q1 is able to conduct.

When the base of Q1 begins to conduct, collector current begins to increase through load resistor R1. As the voltage drops at the collector of Q1 a changing (positive-going pulse) voltage is coupled through capacitor C1 to the base of transistor Q2 to initiate another cycle of operation.

For each half-cycle of operation, whenever a changeover of the multivibrator takes place one of two actions occurs: in one case capacitor C1 recharges through load resistor R1 and the base-emitter junction of Q2 to the value of the supply voltage, V_{cc} , while capacitor C2 discharges through the series circuit consisting of transistor Q2, the voltage source, and resistor R2; in the other case, capacitor C2 recharges through load resistor R4 and the base-emitter junction of Q1 to the value of the supply voltage, V_{cc} , while capacitor C1 discharges through the series circuit consisting of transistor Q1, the voltage source, and resistor R3.

The discharge times of capacitors C1 and C2 are relatively long as compared with their charge times; thus, the capacitor which is charging reaches its final potential long before the other capacitor has completely discharged. This action can be clearly seen if the Q1 and Q2 base waveforms in the illustration are compared for periods T1 and T2.

The waveforms shown in the preceding illustration are for a symmetrical multivibrator, and the output taken from the collector of either transistor is a square wave. The waveforms shown in the following illustration are for an unsymmetrical multivibrator, and the output waveforms have unequal time durations. The general circuit operation is identical with that of the symmetrical multivibrator; however, the on and off times, or charge and discharge times, are different since different R-C values are used.

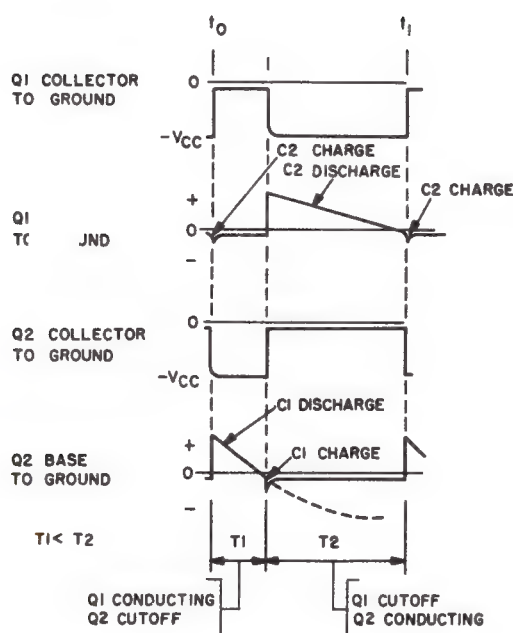

Theoretical Waveforms for an Unsymmetrical Free-Running Multivibrator (Using PNP Transistors)

Failure Analysis.

No Output. An open-circuited, short-circuited, or over-biased condition, as well as a defective transistor, can cause lack of output. The transistor element voltages can be checked against their proper values to determine the defective component. With the circuit in the non-oscillating condition, a check of the voltages at the collector of each transistor will reveal whether load resistor R1 or R4 is open. If either resistor is open, there will be no collector voltage on the associated transistor; also, the other transistor will conduct heavily because of the reduced bias (the circuit is inoperative), and its collector voltage will be low. (In this case the collector resistor can burn out.) If coupling capacitor C1 or C2 is leaky or shorted, the collector resistor of one transistor will be shunted across the base resistor of the other transistor, and the fixed bias on the base of the transistor to which the defective capacitor is connected, will be increased. If the increase in bias is sufficient, the

transistor will be rendered inoperative. (Under certain conditions, an unsymmetrical output can occur.) Also, if coupling capacitor C1 or C2 is open, or if resistor R3 or R4 is open, the circuit will be rendered inoperative, since the R-C circuit resistance will be infinite. If output capacitor C3 or C4 is open, the circuit will operate at a slightly different frequency because of load changes, but no output will be observed.

Incorrect Frequency and Pulse Width. The critical components governing the frequency and pulse width of the multivibrator are those in the coupling circuits. Any change in the components governing the R-C discharge time constant will directly affect the frequency and pulse width. A change in value of coupling capacitor C1 or C2 or in the base resistance R2 or R3 will have the greatest effect. Although a change in the value of collector resistor R1 or R4 will affect the frequency and pulse width, it will have a greater effect on the output amplitude of the waveform.

A 10 percent variation in the collector voltage may cause some frequency drift. However, in practical circuits where the multivibrator is unsynchronized and free-running, adjustments are usually provided to adjust the collector voltage or the base resistance (usually the latter). In this manner the circuit can be set to the correct frequency and pulse width, and can be compensated for the difference in transistor characteristics when a replacement is made.

If output coupling capacitor C3 or C4 is leaky or shorted, the voltage divider action which can occur through the base resistance of the next stage may reduce the amplitude of the output waveform and cause the multivibrator to operate at a higher frequency. This is true because the discharge time in the base circuit is dependent on the amount of change in the voltage applied to the capacitor. Another effect can be a change in the operation of the following stage caused by the bias voltage resulting from this voltage divider action.

If this following stage employs a PNP transistor, the forward bias on the transistor will be increased, with a resultant increase in collector current. The excessive collector current may cause burnout of the collector resistor or the transistor, depending on the ratings of those parts. If the stage employs an NPN transistor the bias will be reversed and cutoff may occur.

PENTODE ELECTRON-COUPLED ASTABLE MULTIVIBRATOR

Application.

The pentode electron-coupled astable multivibrator produces a square-wave output for use as trigger or timing pulses.

Characteristics.

Essentially the same characteristics as the basic astable multivibrator discussed earlier in this section with following exceptions:

Operating frequency is determined primarily by the R-C time constants in the feedback (screen-to-grid) coupling circuits and by the applied screen voltage.

Changes in load have minimum effect upon multivibrator frequency because load is isolated from pentode screen (multivibrator plate) circuit by electron-stream coupling and suppressor-grid action of tube.

Circuit Analysis.


General. The pentode electron-coupled multivibrator is basically a free-running (triode) plate-to-grid-coupled multivibrator using the screen grids of sharp cutoff, pentode-type tubes as plates for the multivibrator switching function. The circuit is fundamentally a two-stage R-C amplifier with the output (screen grid) of the second stage coupled to the input of the first stage. The screen grid of each tube functions in the oscillator circuit as though it were the plate of a triode. Thus, the output signal from the screen grid is fed back in the proper phase to reinforce the input signal; as a result, sustained oscillations occur. The output, taken from the plate-load resistor, is coupled to the multivibrator oscillatory circuit through the electron stream of the pentode tube.

Circuit Operation. The following circuit schematic illustrates two pentode electron tubes in a basic free-running multivibrator circuit. Electron tubes V1 or V2 are identical sharp cutoff, pentode-type tubes. Capacitor C1 provides the coupling from the screen grid of V2 to the grid of V1; capacitor C2 provides the coupling from the screen grid of V1 to the grid of V2. Resistors R1 and R2 are the grid resistors for V1 and V2, respectively; resistors R3 and R4 are the screen resistors for V1 and V2. Resistors R5 and R6 are the plate-load resistors for V1 and V2,

respectively. Resistor R7 is a series voltage-dropping resistor which is common to both screen-grid circuits.

Capacitor C1 and resistor R1 form an R-C circuit to determine the discharge time constant in the grid circuit of V1; capacitor C2 and resistor R2 determine the discharge time constant in the grid circuit of V2.

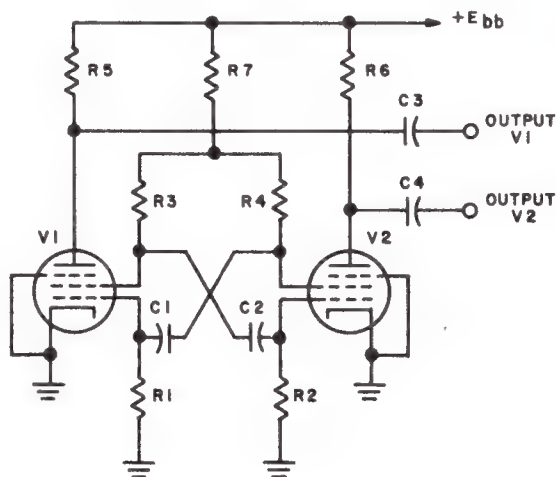Output pulses can be taken from the plate of either or both electron tubes. Capacitors C3 and C4 are the output coupling capacitors for V1 and V2, respectively.



Pentode Electron-Coupled Astable Multivibrator

The switching action of the electron-coupled multivibrator is similar to that of the triode plate-to-grid-coupled multivibrator circuit, previously described in this section.

When voltage is first applied to the circuit, the grids of both tubes are at zero bias and both plate and screen currents start to flow; the plate currents pass through plate-load resistors R5 and R6, and the screen currents pass through resistors R3 and R4 and through the common voltage-dropping resistor, R7. Also, capacitors C1 and C2 begin to charge when the applied voltage appears at the screen of each tube. The currents through both tubes may be equal at first; however, in spite of the close tolerances of the components in the control-grid and screen-grid circuits, there will always be some slight difference in the total currents of the tubes. The difference in screen-grid currents will cause a further unbalance, resulting in a regenerative action which rapidly

switches the circuit to a condition wherein one tube is conducting maximum screen and plate currents and the other is cut off.

For example, if initially the total plate and screen current through tube V1 should be slightly greater than that through V2, the voltage drop across screen resistor R3 will be greater than the drop across screen resistor R4. This results in a lower screen voltage for V1. This decrease in screen voltage is applied through coupling capacitor C2 to the grid of V2 as a negative-going instantaneous grid voltage which reduces the plate and screen currents of V2. When the screen current of V2 is decreased, the current through screen resistor R4 (and resistor R7) is also decreased; therefore, the voltage drop across resistor R4 decreases, resulting in a rise in the screen voltage of V2. This increase in screen voltage is fed through coupling capacitor C1 to the grid of V1 as a positive-going instantaneous grid voltage which increases the screen current of V1. The voltage drop across screen resistor R3 increases as the screen current increases, the screen voltage of V1 decreases, and, as before, the decrease in the screen voltage of V1 is applied to the grid of V2 as a negative-going voltage. Note that as the screen current of V1 increases the screen current of V2 decreases. Since the screen currents of V1 and V2 flow through dropping resistor R7, the voltage (with respect to ground) at the junction of resistors R3, R4, and R7 remains essentially constant throughout the entire period of oscillation.

The regenerative switching action just described for the screen-grid to control-grid coupling of the pentode multivibrator circuit continues rapidly until V1 is cut off and V1 is at maximum conduction. In order to cut off plate and screen current in V2, the grid of V2 must be driven negative beyond the cutoff voltage. The negative grid voltage results from a charge on coupling capacitor C2. Since this charge leaks off through grid resistor R2, the grid voltage of V2 does not remain in a negative condition but starts to return to zero as C2 discharges through resistor R2 and the conduction resistance (cathode to screen grid) of V1. When capacitor C2 discharges sufficiently and the grid voltage cutoff point is reached, the plate and screen currents once again start to flow through V2, initiating another switching action similar to the first action described. However, this time as V2 conducts, coupling capacitor C1 discharges through grid resistor R1 to cut off the plate and screen currents in

V1, and the switching action ends with V1 cut off and V2 at maximum conduction. Here again, the charge existing on coupling capacitor C1 must discharge through grid resistor R1 and tube V2 before the grid voltage cutoff point is reached and V1 can conduct to initiate another switching action.

In a sharp cutoff pentode tube, as long as the plate voltage is greater than the applied screen voltage, the plate current in the tube depends largely upon the screen voltage rather than upon the value of the applied plate voltage. The screen grid is made positive with respect to the cathode and therefore attracts electrons from the cathode; however, most of the electrons attracted by the screen pass on through the screen grid and reach the plate. It is this flow of electrons to the plate that couples the multivibrator action to the plate circuit, from which the output waveform is obtained. The term *electron coupled* refers to this method of coupling within the tube.

The fact that plate current is largely independent of applied plate voltage makes it possible to produce the desired output waveform in the plate circuit since the positive potential existing on the screen will control the number of electrons arriving at the plate. Furthermore, the plate and screen currents are controlled by the action of the control grid; therefore, when the tube is at maximum conduction and plate current flows through the plate-load resistor, the voltage drop across the plate-load resistor is also maximum and the plate voltage of the tube is minimum. When the tube is cut off, the plate voltage is at maximum. Thus, the voltage at the plate of the tube is determined by the coupling of the electron stream to the plate circuit, and this, in turn, is governed by the switching action of the multivibrator oscillatory circuit (control and screen grids). The suppressor grid acts to shield the screen from the plate and prevents changes in loading from affecting the oscillatory circuit; therefore, the frequency of the multivibrator is reasonably independent of changes in output loading.

Like the triode plate-to-grid-coupled multivibrator, described previously in this section, the proportioning of the R-C time constants of the coupling circuits (R1C1 and R2C2) determine whether the output waveform will be symmetrical or unsymmetrical.

The output waveform is taken from either or both plate circuits and coupled to the load through an output-coupling capacitor (C3 or C4).

Failure Analysis.

No Output. Assuming that the multivibrator is a free-running type and no synchronizing signal is applied, the plate, screen, and filament voltages should be measured to determine whether they are within specified values. If either coupling capacitor C1 or C2 should become leaky or shorted, a positive potential will be present on the grid of the associated tube, and, as a result, the tube will conduct continuously; the other tube will also conduct, since it will be at zero bias. A similar condition could exist if either coupling capacitor C1 or C2 should open; in this case, the feedback necessary to sustain oscillations cannot occur, and both tubes will conduct continuously because the grids are at zero bias. If this circuit is in a nonoscillating condition, the voltage at each screen grid should be measured to determine whether screen resistor R3 or R4 is open. If either is open, there will be no screen voltage present on the associated screen grid, and the tube will be cut off; also, the other tube will conduct continuously because of zero bias, and its plate and screen voltages will be low. Furthermore, if resistor R7 should open, there will be no voltage at either screen grid, and both tubes will be cut off.

Note that, if a plate load resistor (R5 or R6) should open, the multivibrator oscillatory circuit (control and screen grids) may function normally, but no output waveform will be obtained from the tube associated with the open plate-load resistor.

Incorrect Frequency or Pulse Width. The critical components governing the frequency and pulse width of the multivibrator are those in the coupling circuits. Any change in components governing the R-C discharge time constant will directly affect frequency and pulse width; a change in capacitor C1 or C2 or resistor R1 or R2 will have the greatest effect. A change in the value of screen resistor R3 or R4 or dropping resistor R7 will also have an effect upon the frequency and pulse width, but not nearly as much as the coupling components mentioned above.

In a practical circuit, where the multivibrator is free-running and is not synchronized from an external source, means may be provided to adjust the applied screen voltage or to adjust the value of resistance in each control-grid circuit. This provision enables the circuit to be adjusted to the correct frequency and pulse width and compensates for differences in individual tube characteristics when a tube substitution has been made.

Reduced Output. A reduction in output amplitude is generally caused by a defective tube; however, it can also be caused by a decrease in the applied plate voltage or an increase in the resistance of the associated plate-load resistor (R5 or R6). A similar condition can also result from a change in the value of the applied screen voltage; however, in this case the multivibrator frequency will probably be affected before a noticeable change in output occurs.

If either output coupling capacitor (C3 or C4) should become leaky or shorted, the input resistor of the following stage can form a voltage divider which also includes the associated plate-load resistor (R5 or R6). If the input resistor of the following stage is returned to ground or to a negative potential, voltage-divider action may reduce the voltage available at the plate of the multivibrator and reduce the amplitude of the output waveform; also, the additional current through the plate-load resistor (R5 or R6) may cause the resistor to burn out. Furthermore, the operation of the following stage may also be affected by the change in grid-bias voltage resulting from the voltage-divider action.

TRIODE CATHODE-COUPLED ASTABLE MULTIVIBRATOR**Application.**

The triode cathode-coupled astable multivibrator produces a square- or rectangular-wave output for use as trigger or timing pulses.

Characteristics.

Free-running oscillator; does not require trigger pulse to produce oscillations.

Operating frequency is determined primarily by the R-C time constant in the grid circuit and by the applied voltage.

Frequency stability is rather poor when unsynchronized; however, stability is good when synchronized by an external timing pulse.

Circuit may be synchronized at the timing-pulse frequency or integral submultiples thereof.


Either a symmetrical square- or rectangular-wave output or an unsymmetrical output may be produced by changing circuit constants for voltages.

Output impedance is essentially equal to plate-load impedance.

Circuit Analysis.

General. The triode cathode-coupled astable multivibrator is functionally similar to the basic Triode Plate-to-Grid-Coupled Astable Multivibrator discussed at the beginning of this section of the handbook. R-C coupling is provided from the plate of V1 to the grid of V2, as in the basic plate-to-grid-coupled circuit, but in this instance the coupling from V2 to V2 is direct, being affected in the cathode circuit through a common cathode resistor; the R-C coupling (in the basic circuit) from the plate of V2 to the grid of V1, is therefore, omitted. A variation of this cathode-coupled circuit uses separate cathode bias resistors, with V2 coupled to V1 through a capacitor rather than directly. Output signals can be taken from the plate of either or both electron tubes, as in the basic plate-to-grid-coupled circuit configuration.


Circuit Operation. The following circuit schematic illustrates two triode electron tubes in a basic cathode-coupled astable (free-running) multivibrator circuit employing direct coupling in the cathode circuit. Electron tubes V1 and V2 are identical-type triode tubes; although the schematic illustrates separate triodes, a twin-triode is frequently used in this circuit. Capacitor C1 provides the coupling from the plate of V1 to the grid of V2. Resistors R1 and R2 are the grid resistors of V1 and V2, respectively; resistors R3 and R4 are the plate-load resistors of V1 and V2, respectively. Resistor R5 is the common cathode-coupling and bias resistor coupling V2 to V1.

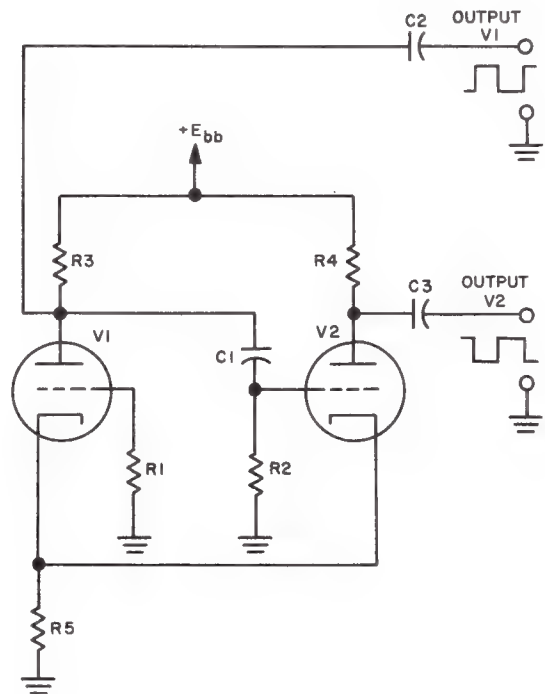

**Triode Cathode-Coupled Astable Multivibrator
(Direct Coupling)**

Capacitors C2 and C3 are the output coupling capacitors for V1 and V2, respectively.


Capacitor C1 and resistor R2 form an R-C circuit establishing the time constant in the grid circuit of V2. The initial charge path for capacitor C1 is from its left side through V1 plate-load resistor R3 and the plate supply voltage to ground, then through cathode resistor R5 and the low (approximately 1K) cathode-to-grid conduction resistance of V2 to the right side of C1, as illustrated by the solid-line path in part A of the following simplified schematic diagram. When the conduction through V2 decreases, and the grid of V2 no longer draws current, the charge path for C1 is completed through grid resistor R2, as illustrated by the dotted-line path in the same diagram. For all practical purposes, C1 charges completely during the time that V2 conducts; the amount of charge via R2 is negligible. Part B of the diagram shows the discharge path for capacitor C1 to be through grid resistor R2, common cathode resistor R5, and the low cathode-to-plate conduction resistance of V1. The time constant of the charge path and the cutoff voltage level of V1 determine the length of time that V1 is cutoff; the time constant of the discharge path and the cutoff voltage level of V2 determine the length of time that V2 is cutoff.

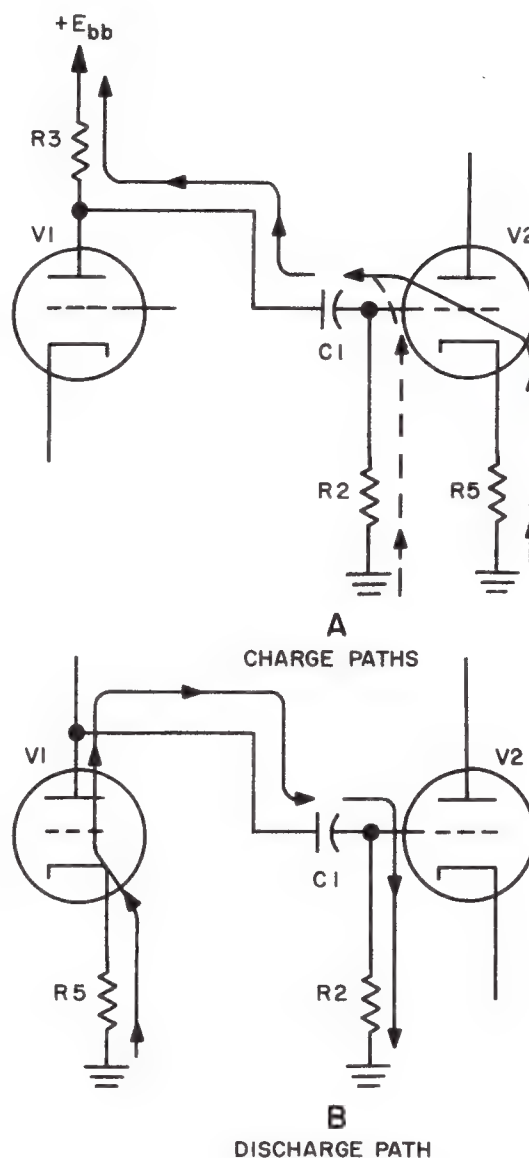

Charge and Discharge Paths for Capacitor C1

If the time constants for the charge and discharge of C_1 are equal, a symmetrical square-wave output is produced by the circuit; by making the charge and discharge R-C time constants different, the circuit produces an asymmetrical, or unsymmetrical, rectangular-wave output. Although the conduction resistance of V_1 and the resistance of cathode resistor R_5 are in the discharge path, their resistance value is small as compared with that of R_2 , and are, therefore, neglected in the discharge path time-constant calculations.

For the following discussion of circuit operation, refer to the preceding illustrations in addition to the following illustration which shows the theoretical waveforms for a symmetrical triode cathode-coupled astable multivibrator employing direct coupling between the cathodes. When voltage is first applied, the grids of both tubes are at zero bias and plate current begins to flow through plate-load resistors R_3 and R_4 . When voltage is applied to the plate of V_1 , capacitor C_1 begins to charge along the path previously outlined. As C_1 charges, the grid of V_2 becomes positive. Since there is no coupling capacitor from the plate of V_2 to the grid of V_1 , the voltage at the plate of V_2 has no effect on the conduction of V_1 . The plate current of V_2 flowing through cathode resistor R_5 makes the voltage at the top of the resistor positive with respect to ground. This voltage is a bias voltage of sufficient amplitude to cut off conduction of V_1 and still permit V_2 to conduct, since at this time the grid of V_1 is at ground (zero volts) and the grid of V_2 is at a positive potential. Thus, the initial conditions for circuit operation are established; that is, V_2 is conducting and V_1 is cut off.

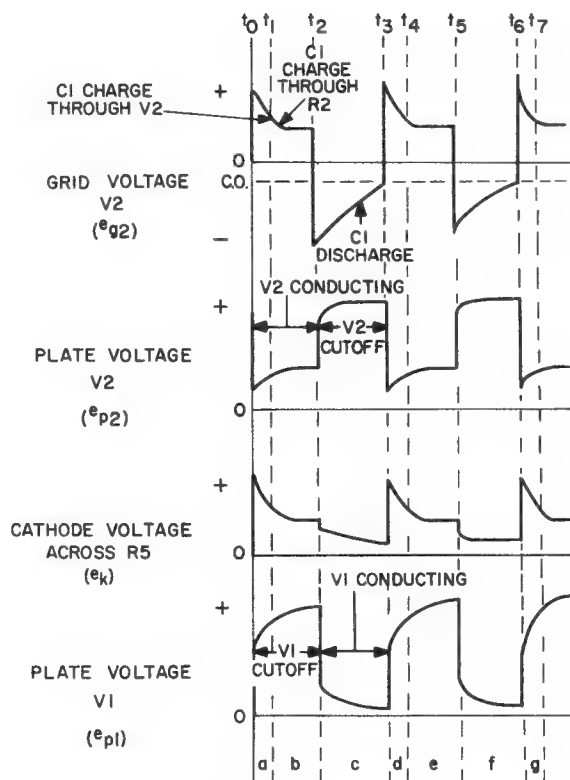

Theoretical Waveforms for Symmetrical Cathode-Coupled Astable Multivibrator (Direct Coupling)

The foregoing multivibrator action is summarized at time t_0 (start of time interval a) on the waveform

illustration. Note that the grid of V2 (e_{g2}) is driven positive, causing heavy conduction through this tube. At the same instant, the plate voltage of V2 (e_{p2}) decreases (is negative-going) as a result of plate current through plate-load resistor R4. Also, the same plate current, flowing through common cathode resistor R5, produces a positive voltage (e_k) which provides a bias sufficient to cut off V1 and cause the plate voltage (e_{p1}) of this tube to approach B+. The positive-going voltage at the plate of V1 is instantaneously coupled through capacitor C1 to the grid of V2, driving this grid still further positive. All of the action described is instantaneous and cumulative, so that the high positive potential on the grid of V2 causes this tube to conduct heavily, while V1 is cut off.

With V1 cut off, its plate voltage is at B+, and capacitor C1 charges toward this value. The waveform at the plate of V1 (e_{p1}) is rounded off, and the waveform at the grid of V2 (e_{g2}) has a small positive spike of the same time duration as a result of the charging of capacitor C1. Since at this time V2 is conducting, its plate voltage (e_{p2}) drops. Note that the plate-voltage waveform has a small negative spike of the same time duration as the positive spike on the grid waveform.

As capacitor C1 charges, electrons are accumulated on its right side; this accumulation of electrons is a negative charge which acts in opposition to the positive potential on the grid of V2, in effect causing this potential to decrease from its most positive excursion. This is illustrated during time interval *a* (between t_0 and t_1), where the rapid charging of C1 is represented by the steep portion of the V2 grid voltage (e_{g2}) waveform. Note that during the rapid charge time of C1 the positive voltage on the grid of V2 decreases until, at t_1 , it is equal to the voltage (e_k) across common cathode resistor R5. At this instant the grid of V2 ceases to draw current. However, C1 continues to charge, but at slower rate through grid resistor R2, which is much larger in value than the total resistance in the "fast" charge path. This change in the R-C time constants of the charging paths of C1 accounts for the abrupt change in the voltage waveforms at t_1 .

During time interval *b* (from t_1 to t_2), capacitor C1 continues to charge slowly and the grid voltage of V2 decreases slowly; this causes a reduction in the plate current of V2, which results in a decreasing volt-


age drop across common cathode resistor R5. This action continues until the voltage drop across resistor R5 decreases to the level where tube V1 is no longer held below cutoff. In other words, since the bias on tube V1 is determined by the cathode voltage (e_k), V1 remains cut off so long as the cathode voltage is positive with respect to ground by more than the cutoff voltage (bias) of V1. When the cathode voltage drops to the level of the V1 cutoff voltage, as at t_2 on the cathode voltage (e_k) waveform, V1 conducts and rapidly cuts off V2 because the large negative-going signal at its plate is coupled through capacitor C1 to the grid of V2. Thus, the first switching action occurs; that is, V2 is cutoff and V1 is conducting.

When tube V1 is conducting, capacitor C1 discharges through grid resistor R2, common cathode resistor R5, and the plate resistance of V1. The grid voltage of V2 approaches cutoff as capacitor C1 discharges; this is illustrated by the V2 grid voltage (e_{g2}) waveform during time interval *c* (between t_2 and t_3). At t_3 the grid voltage of V2 just reaches the cutoff level, permitting this tube to conduct. When the plate current of V2 increases, the voltage across common cathode resistor R5 (waveform e_k) also increases (goes positive); this increases the bias on V1 and thereby reduces the conduction of V1. The decreasing plate current of V1 produces a positive-going signal across its plate-load resistor, R3, which, in turn, is coupled through capacitor C1 to the grid of V2, causing this grid to become highly positive. In addition to increasing the plate current of V2, the positive grid voltage again causes grid current flow and charges capacitor C1. Thus, the second switching action occurs and the cycle is now complete as the initial conditions once again are reached; that is, V2 is conducting and V1 is cutoff.

In the preceding discussion the multivibrator was considered to be a symmetrical type; that is, the periods for conduction and cutoff of the tubes are equal. An asymmetrical, or unbalanced, output can be obtained by having V2 cutoff for a longer period than V1. Adjusting the value of the cathode resistance will permit this to happen, since it is the bias voltage developed across the common cathode resistor that determines when V1 begins conduction. In this case, the combined time intervals of *a* and *b* will be less than time interval *c*.


Another configuration of a triode cathode-coupled astable multivibrator is the circuit shown in the

following schematic diagram. This circuit is identical to the basic common-cathode-resistor-coupled circuit just discussed, except that the feedback from V2 to V1 now is by capacitive coupling through C4 between the two cathodes. Although the same switching action occurs between the two tubes and the cutoff time of V2 is still determined by the discharging of capacitor C1 through grid resistor R2, the cutoff time of V1 in this instance is determined by the charging of capacitor C4 through its cathode resistor, R5. (Note that this circuit differs from the basic common-cathode-resistor-coupled multivibrator in that, in addition to capacitive coupling between cathodes, separate cathode resistors are used.)

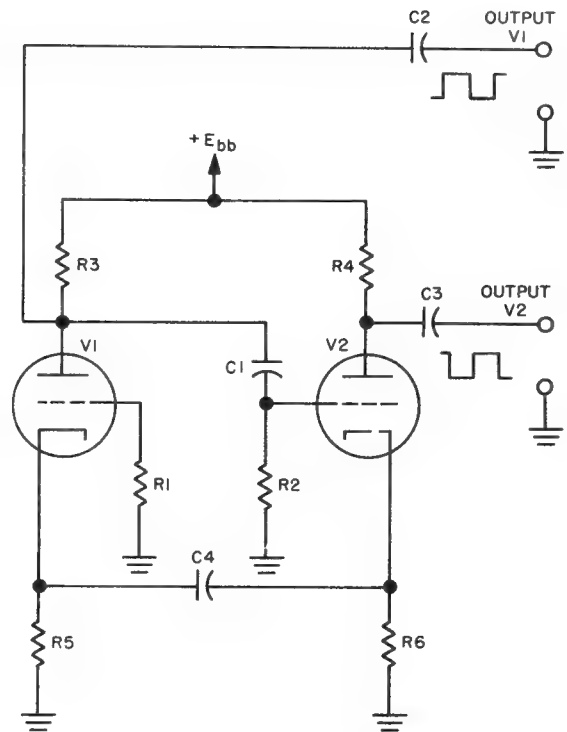


**Triode Cathode-Coupled Astable
Multivibrator (Capacitive Coupling)**


The charge and discharge paths for capacitors C1 and C4 are depicted in the following illustration. Note that capacitor C1 (parts A and B of the illustration) the paths are the same as in the direct-coupled circuit just discussed, except that the cathode resistor through which capacitor C1 now charges initially is R6. The charge path for capacitor C4 (part C of the illustration) is from its right side through the low cathode-to-plate conduction resistance of V2, plate-load resistor R4, and the plate-supply voltage to ground, then through V1 cathode resistor R5 to its left side. Part D of the illustration shows the discharge path for capacitor C4 to be from its left side through the low cathode-to-plate conduction resistance of V1, plate-load resistor R3, and the plate-supply voltage to ground, then through V2 cathode resistor R6 to its right side.

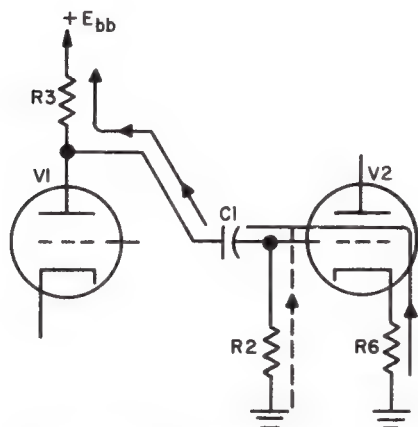


A. CAPACITOR C1 CHARGE PATHS

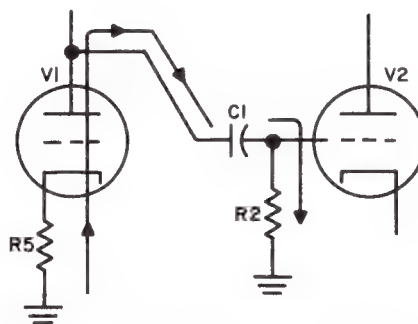

B. CAPACITOR C1 DISCHARGE PATH

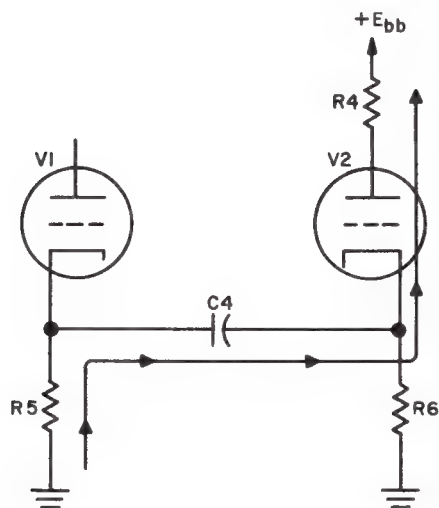

C. CAPACITOR C4 CHARGE PATH

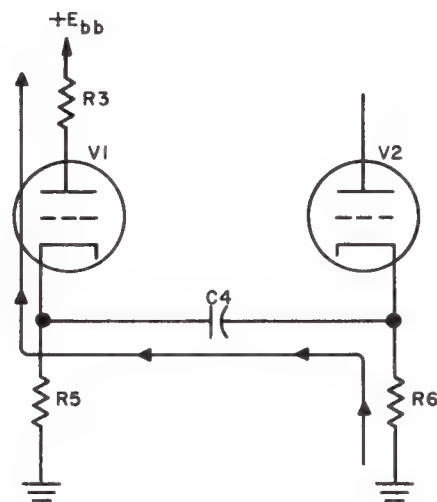

D. CAPACITOR C4 DISCHARGE PATH

Charge and Discharge Paths for Capacitors C1 and C4
of Capacitive-Coupled Multivibrator

The free-running frequency of the output signal is determined primarily by the values of R-C time constants R2-C1 in the grid of V2 and R5-C4 in the cathode circuit, and by the value of the applied voltage. The symmetry of the square-wave output signals depends upon the degree of balance between the two tubes and their associated circuit components.

Consider now the operation of the astable multivibrator being discussed. When voltage is first applied to the circuit, the grids of both tubes are at zero bias, and plate current begins to flow through plate-load resistors R3 and R4. Also, capacitor C1 begins to charge by drawing grid current through resistor R2 and tube V2, making the grid of this tube positive. The plate current of V2 flowing through cathode resistor R6 makes the voltage at the top of the resistor more positive with respect to ground. This positive voltage swing is coupled through capacitor C4 to the cathode of V1, where it acts as a bias voltage to hold V1 cutoff. At this instant, capacitor C4 begins charging through resistor R5 toward the positive voltage at the top of resistor R6. The positive voltage at the top of R5 holds V1 cut off until C4 reaches the approximate potential across R6. At this time, the decrease in current through R5 decreases the bias on V1 and allows it to conduct, thereby causing the multivibrator switching action. That is, conduction of V1 causes the voltage at the V1 plate to decrease, and this negative-going voltage is coupled through capacitor C1 to the grid of V2, where it drives the grid negative and cuts off V2.

When V2 is cutoff, capacitor C1 discharges through R2, R5, and V1. Also, the voltage on the cathode of V2 decreases (becomes less positive); this negative going voltage is coupled through capacitor C4 to the cathode of V1. Since V1 is already conducting the negative-going signal merely aids its conduction. However, the plate current of V1 flowing through cathode resistor R5 produces a positive voltage at the top of this resistor. Capacitor C4 now discharges through V1, plate-load resistor R3, and cathode resistor R6. As capacitor C4 discharges, the voltage at the top of resistor R6 decreases (becomes less positive) because of the accumulation of electrons on the right side of capacitor C4. When the combination of the voltage on the grid of V2 (becoming less negative as capacitor C1 discharges through resistor R2) and the voltage on its cathode (becoming less positive as capacitor C4 discharges through resis-

tor R6) decreases sufficiently, V2 again conducts. The switching action repeats continuously with first one tube and then the other tube conducting.

The output of the multivibrator is taken from either or both plate circuits through output coupling capacitor C2 or C3. In cases where it is desired to minimize the effect of varying load impedance on the frequency stability of the multivibrator, a cathode follower is used for stability.

The triode cathode-coupled astable multivibrator, like the plate-to-grid-coupled type, may be synchronized with a stable external source to force the period of the multivibrator action to be exactly the same as that of the synchronizing source. The frequency of the synchronizing signal must be slightly higher than the natural operating frequency of the multivibrator so that the synchronizing pulse occurs just prior to the time that normal switching action would occur.

Failure Analysis.

No Output. Assuming that the multivibrator is a free-running type and no synchronizing signals are applied, the plate and filament voltages should be measured to determine whether they are within the specified values. If coupling capacitor C1 should become leaky or shorted, a positive potential will be present on the grid of V2 and, as a result, tube V2 will conduct heavily; V1 will remain cutoff because of the high positive potential (bias) on its cathode as a result of the heavy conduction of V2. If the circuit does not oscillate, measure the voltage at each plate to determine whether plate-load resistor R3 or R4 is open. If either resistor is open, there will be no voltage on the associated plate; also, the other tube will conduct heavily and, as a result of the heavy conduction, its plate voltage will be low.

In the common-cathode-resistor-coupled circuit configuration, if cathode resistor R5 were to open there would be no output because neither tube would conduct, and the plate voltage of both tubes would be at B+. In the capacitive-coupled-cathode circuit configuration, if cathode resistor R5 or R6 were to open only the associated tube (V1 or V2, respectively) would not conduct. If coupling capacitor C4 were to open there would be no feedback from V2 to V1, and thus no output from the multivibrator.

Reduced Output. A reduction in the output amplitude is generally caused by a defective tube; however, it can also be caused by a decrease in the applied

plate voltage or an increase in the resistance of the associated plate-load resistor, R3 or R4. If either output coupling capacitor, C2 or C3, should become leaky or shorted, the input resistor of the following stage can form a voltage divider which also includes the associated plate-load resistor, R3 or R4. If the input resistor of the following stage is returned to ground or to a negative potential, voltage-divider action may reduce the voltage available at the plate of the multivibrator and reduce the amplitude of the output waveform; also, the additional current through the plate-load resistor, R3 or R4, may cause the resistor to burn out. Furthermore, the operation of the following stage may also be affected by the change in grid-bias voltage resulting from the voltage-divider action.

Incorrect Frequency or Pulse Width. The critical components governing the frequency and pulse width of the multivibrator are those in the coupling circuits. Any change in the components governing the grid or cathode R-C time constants will directly affect the frequency and pulse width; a change in the R-C combinations of R2-C1 or R5-C4 will have the greatest effect. A change in the value of plate-load resistor R3 or R4 will affect the amplitude of the output; it will also have an effect on the frequency, but not nearly so much as the components mentioned above.

If the plate-supply voltage, $+E_{bb}$, should change approximately 10 percent from the specified value, a drift in frequency will generally occur; some frequency drift may also occur if the filament voltage should drop below the specified value.

In a practical circuit, where the multivibrator is free-running and not synchronized from an external source, a variable resistor may be provided to adjust the applied plate voltage or to adjust the value of resistance in each grid circuit. This provision enables the multivibrator to be adjusted to the correct frequency and pulse width, and permits adjustment to compensate for differences in individual tube characteristics when a tube substitution is made.

If either output coupling capacitor (C2 or C3) should become leaky or shorted, the voltage-divider action which can occur may reduce the amplitude of the output waveform and cause the multivibrator to operate at a higher frequency, since the grid capacitor (C1) discharge time is dependent upon the amount of change in capacitor voltage.

PART 7-2. BISTABLE

BISTABLE (START-STOP) MULTIVIBRATORS General.

The term *bistable multivibrator* refers to one class of multivibrator or relaxation oscillator circuits that can function in either of two stable states and is capable of switching rapidly from one stable state to the other upon the application of a trigger pulse. In the strict sense of the word, the bistable multivibrator is not an oscillator; rather, it is a circuit having two conditions of stable (bistable) equilibrium and requiring two input triggers to complete a single cycle. The operation of the bistable multivibrator is dependent upon the timing-control action involved in the transfer of conduction from one tube to the other, initiated by an input trigger pulse of proper polarity and sufficient amplitude. Because there is a sudden reversal (or "flopping") from one stable state to the other, the bistable multivibrator is frequently referred to as a *flip-flop* circuit.

The bistable multivibrator produces an output pulse, more commonly called a "gate", having fast rise and fall times and extreme flatness on top. To generate this type of waveform the circuit requires one trigger pulse for turn-on (start) and another trigger pulse for turn-off (stop), thus generating a "step" function for each input trigger. When the trigger pulses are of constant frequency and are applied at long time intervals (low frequency), the gates generated are wide. On the other hand, when the trigger pulses are of constant frequency and are applied at short time intervals (high frequency), the gates generated are narrow. In all cases, however, two input trigger pulses are required to complete one cycle of operation, resulting in an output gate frequency one-half that of the input trigger frequency.

Although the turn-on and turn-off input trigger pulses (which can be applied from different sources as well) can be of either positive or negative polarity, a negative trigger is preferred. A reason for this requirement is that if a tube is biased far beyond cutoff, a high-amplitude positive pulse is required to drive the tube from cut off into conduction. On the other hand, a low-amplitude negative pulse will immediately cut off conduction of a tube. In addition, the circuit used to generate a low-amplitude pulse requires less power.

When a transistor is operating in the saturation region, a phenomenon known as *minority carrier storage* occurs. Because the collector-base voltage is limited in its excursion by the resistance in the collector circuit, the collector cannot accept all of the minority carriers injected by the emitter, and, as a result, an excess of minority carriers is built up in the base region. In a PNP transistor that is in a state of saturation, an excess of holes is built up in the base; before the transistor can be turned off, this excess must be removed. Thus, the turn-off operation is a function of the amount of minority carrier storage. Minority carrier storage is one limiting factor in the switching speed of the multivibrator; other factors that limit the switching speed are the operating level of the transistors, collector capacitance, and external circuit elements.

Minority carrier storage can be prevented by limiting the excursion of the collector voltage of a switching stage to an area outside the saturation region of the transistor. In this case, the collector current is not limited by the collector circuit resistance, but rather by the maximum current limitation of the transistor. This is the basis of operation of the "nonsaturating multivibrator"; this circuit is discussed in detail later in this section, as are several other semiconductor bistable multivibrator circuits and bistable multivibrator triggering techniques.

The rectangular-gate output of the bistable multivibrator can be either positive or negative in polarity. Each gate is formed by the combination of positive and negative step functions produced by turning the multivibrator on and off. The negative-going step is inherently faster than the positive-going step. When connecting other circuits to the bistable multivibrator output, precautions should be taken so as to prevent the shunting capacitance from causing undesirable effects on the rise and fall times of the step function.

BASIC FLIP-FLOP (ECCLES-JORDAN) MULTIVIBRATOR (ELECTRON TUBE)

Application.

The basic flip-flop (Eccles-Jordan) multivibrator produces a square- or rectangular-wave output for use as gating or timing signals, or for on-off switching operations in binary counter circuits.

Characteristics.

Circuit assumes one of two stable states: one tube normally conducting with the other tube normally cut off, and vice versa.

Requires two input triggers to complete one cycle of operation; the circuit assumes a stable state upon completion of each half-cycle of operation.

For a constant-frequency input, the output frequency is one-half that of the input trigger frequency.

Input triggers can be either positive or negative; positive trigger affects normally cut-off tube, and negative trigger affects normally conducting tube.

Symmetrical triggering occurs when the same trigger pulse is applied simultaneously; unsymmetrical triggering occurs when triggers are applied separately.

Symmetrical or unsymmetrical output gate depends on timing sequence of input trigger pulses; input triggers from different sources (turn-on and turn-off triggers) produce unsymmetrical gate output.

Plate-to-grid feedback coupling is direct (through resistors), with bypass capacitors used to speed up switching from one stable state to the other.


Circuit can be made to assume the same stable state whenever voltages are applied by incorporating a definite imbalance within the circuit or by using a manually controlled "reset" signal.

Tubes can be grid-biased by connecting to negative supply, or cathode-biased by connecting cathodes through voltage divider to positive supply.

Circuit Analysis.

General. The basic flip-flop (Eccles-Jordan) Multivibrator is capable of producing a square- or rectangular-wave output pulse (gate) in response to two input triggers. This type of multivibrator has two stable (bistable) states — one tube is normally conducting while the other tube is normally held cut off — and will function for only one-half cycle upon the application of an input trigger. Feedback from the plate of one tube to the grid of the other is direct through a coupling resistor bypassed with a capacitor, whose function is to reduce or eliminate the effects of tube interelectrode capacitance. Because two input triggers (turn-on and turn-off) are required to complete one cycle of operation, the output-gate frequency of the bistable multivibrator is one-half the input trigger frequency. The output gate length is determined by the time interval of the turn-on and turn-off input trigger. Output signals can be taken from the plate of either or both electron tubes.

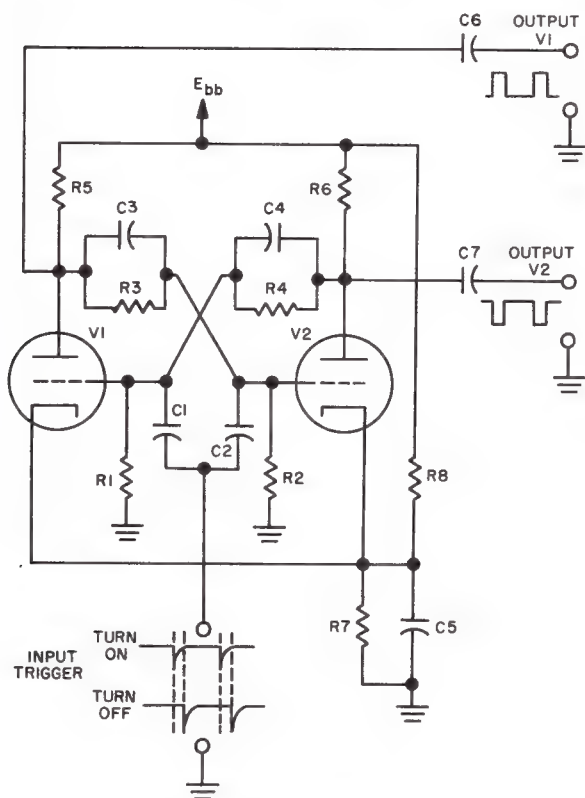Circuit Operation. The accompanying circuit schematic illustrates two triode electron tubes in the basic




Basic Flip-Flop Multivibrator

multivibrator circuit. Electron tubes V1 and V2 are identical-type triode tubes; although the accompanying schematic illustrates two separate triodes, a twin-triode is frequently used in this circuit. Resistors R1 and R2 are the grid resistors for V1 and V2, respectively. Resistor R3 provides the direct coupling from the plate of V1 to the grid of V2, and resistor R4 provides the direct coupling from the plate of V2 to the grid of V1. Feedback resistors R3 and R4 are bypassed with capacitors C3 and C4, respectively. These capacitors permit faster switching action from one tube to the other by reducing the effects of tube interelectrode capacitance. Resistors R5 and R6 are the plate-load resistors for V1 and V2, respectively. Capacitors C1 and C2 are the input-trigger coupling capacitors for V1 and V2, respectively; they provide symmetrical triggering. Capacitors C6 and C7 are the

output-gate coupling capacitors for V1 and V2, respectively. Operating bias for this bistable multivibrator, which is cathode-biased, is determined by the combination of the cathode and respective grid circuit voltage dividers. The cathode circuit voltage divider consists of common cathode resistor R7, bypassed with capacitor C5, and resistor R8; the voltage divider for the grid circuit of V1 consists of resistors R1, R4, and R6, and the voltage divider for the grid circuit of V2 consists of resistors R2, R3, and R5.

Consider now the operation of the basic flip-flop multivibrator by referring to the preceding circuit illustration and the following illustration of the idealized theoretical waveforms. Also, in order to more fully analyze the timing sequence, assume that the circuit under consideration is for a radar application wherein it is desirable to have the gate length controlled by the display circuit. Thus, the radar sweep circuit provides the turn-off trigger to return the multivibrator to its initial stable state.

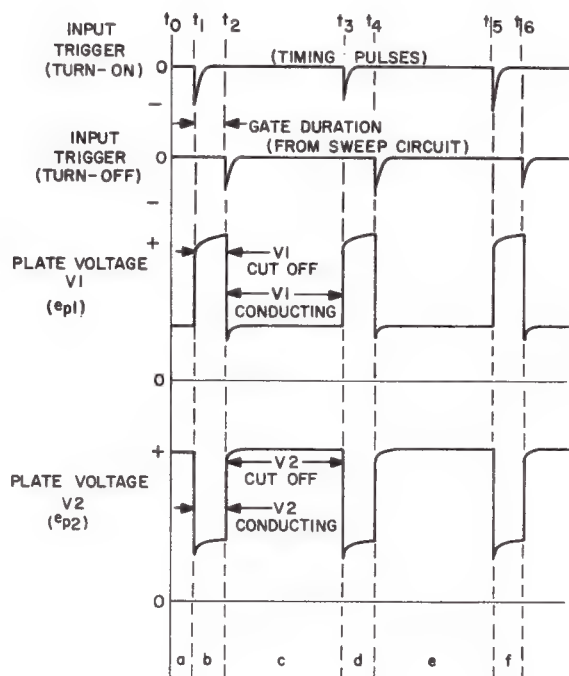

Theoretical Waveforms for Basic Flip-Flop Multivibrator

When voltage is first applied to the circuit, there is a slight conduction through both tubes. Because of the inherent imbalance of the circuit, however, one tube will conduct slightly more than the other. For example, if initially the current through V1 should be slightly greater than that through V2, the voltage drop across plate-load resistor R5 will be greater than the drop across plate-load resistor R6. This results in a lower plate voltage for V1, which is applied through resistor R3 to the grid of V2, thus causing the voltage at this grid to become more negative and reduce the current through V2. When the plate current through V2 is reduced, the current through plate-load resistor R6 likewise is reduced; therefore, the voltage drop across resistor R6 decreases, resulting in a rise in the plate voltage of V2. The positive-going plate voltage of V2 is applied through resistor R4 to the grid of V1, making this grid more positive. The regenerative action just described continues rapidly until V2 is cut off and V1 is at maximum conduction. Thus, the circuit is in one of its two stable states of equilibrium, as represented by time interval *a* on the waveform illustration. Note that the output at the plate of V1 is at its most negative excursion (V1 is conducting) while the output at the plate of V2 is positive (V2 is cut off). Since there is no internal R-C time constant timing circuit to drive the nonconducting tube out of cutoff, the circuit remains in this stable condition until an input trigger pulse is applied.

Assume now that a negative trigger pulse of sufficient amplitude is applied simultaneously to both grids through input capacitors C1 and C2. This trigger pulse, which is the turn-on input trigger from the radar timing circuits, is applied at t_1 as illustrated on the waveform diagram. Because V2 is already cut off, the input trigger has little effect on this tube; however, the same negative trigger pulse drives the grid of V1 below cutoff, causing this normally conducting tube to decrease conduction. As soon as V1 reduces conduction, its plate voltage rises toward the plate-supply voltage, $+E_{bb}$. The positive-going signal at the plate of V1 is now coupled through resistor R3 and applied to the grid of V2, driving V2 into conduction. Thus, at instant t_1 a switching action occurs; V2 now conducts heavily, as indicated by the waveform at its plate, and V1 is cutoff. The multivibrator remains in this condition, which is its second stable state as de-

picted by time interval *b*, until another trigger is applied.

When the desired gate duration is attained, the negative turn-off trigger from the radar sweep circuits is applied (at t_2) and the gate is terminated. The negative-going turn-off trigger cuts off conduction of V2 and causes a switching action that returns the multivibrator to its original stable state, in which V1 is conducting and V2 is cut off. The circuit remains in this condition (time interval *c*) until another negative trigger from the radar timing circuits is applied at t_3 .

Close examination of the waveform illustration reveals that the length of the output gates is determined by the time interval between the turn-on and turn-off triggers. If the frequency of the turn-off trigger is made lower, the time interval between the triggers will increase; hence, the gate length will likewise increase. Conversely, the gate length will decrease if the turn-off trigger frequency is increased. Thus, the bistable multivibrator provides a positive or negative gate output in response to a timing (turn-on) input trigger pulse, with the gate being terminated by a turn-off trigger pulse. If a single constant-frequency trigger is used for both the turn-on and turn-off functions, the circuit will produce a symmetrical square-wave output having a frequency one-half that of the input-trigger frequency.

In the symmetrical-input bistable multivibrator being considered, positive input trigger pulses of sufficient amplitude can also be used to initiate the switching action between tubes V1 and V2. When the positive trigger pulse is applied simultaneously to the grids of the tubes, there will be no effect on the operation of the conducting tube. However, the plate current of the cut-off tube will be increased, causing its plate voltage to fall. The fall in plate voltage, when coupled to the grid of the conducting tube, drives this tube into cutoff.

Although it is true that either negative or positive input trigger pulses can cause the switching action to occur, triggering with negative pulses is preferred. For example, if the cut-off tube is biased with a high negative potential, a high-amplitude positive pulse is required to drive the tube into conduction, and only the most positive portion of the pulse has any effect. On the other hand, a low-amplitude negative pulse applied to the conducting tube immediately drives

this tube into cutoff, causing an instantaneous switching action.

Failure Analysis.

No Output. The input trigger should be checked with an oscilloscope to determine whether it is being applied to the circuit and whether it is of the proper polarity and amplitude. Lack of an input trigger at the grid of V1 or V2 can be due to an open coupling capacitor, C1 or C2, or to failure of the external input-trigger source.

Failure of the plate voltage supply, $+E_{bb}$, will disrupt the operation of the circuit, as will an open cathode circuit. With tubes (or a single twin-triode tube) installed in the circuit, the filament and plate voltages should be measured, as well as the bias voltage developed across the cathode resistance, to determine whether the applied voltages are within tolerance and whether plate-load resistor R5 or R6 and cathode-bias resistor R7 or R8 is open. If coupling resistor R3 or R4 is open there will be no feedback signal to cause the multivibrator switching action. If bypass capacitor C3 or C4 is open feedback will still occur, but the interelectrode capacitance of the tube may cause undesirable effects on the wavefront of the feedback signal. An open output coupling capacitor, C6 or C7, will prevent the output-gate signal from reaching the following stage.

Reduced Output. A reduction in output is generally caused by a defective tube; however, it can also be caused by a decrease in the applied plate voltage or an increase in the resistance of the associated plate-load resistor, R5 or R6. A leaky or shorted output coupling capacitor, C6 or C7, will form a voltage divider with the input resistor of the following stage. If the input resistor of this following stage is returned to ground or to a negative supply, the voltage at the plate of both V1 and V2 will be reduced, and the operation of the following stage will be upset by the change in voltage applied to its grid. Also, the additional current through plate-load resistor R5 or R6 may cause the resistor to burn out.

Incorrect Frequency or Gate Width. The basic flip-flop multivibrator has no components governing the frequency or width of its output-gate signal; these are both governed by the input triggers applied to the circuit. Therefore, any change in the output-gate frequency or width is a result of improper operation of the turn-on and/or turn-off trigger generating circuits.

BASIC FLIP-FLOP MULTIVIBRATOR (SEMICONDUCTOR)

Application.

The basic flip-flop multivibrator produces a square-or rectangular-wave output for use as gating or timing signals in radar sets. It is also used in switching-circuit applications, and for computer logic operations which include counting, shift-registers, clock pulses, and memory circuitry. This circuit is often used for relay-control functions, and for a variety of similar applications in radar and communications systems.

Characteristics.

Circuit assumes one of two stable states: one transistor normally conducts while the other transistor is cut off, and vice versa.

Requires two input triggers to complete one cycle of operation; the circuit assumes a stable state upon completion of each half-cycle of operation.

For a constant-frequency input, the output frequency is one-half that of the input trigger frequency.

Input trigger can be either positive or negative (positive trigger may be applied to base of conducting transistor, and negative trigger may be applied to base of cut-off transistor in common-emitter circuit configuration).

Symmetrical triggering occurs when the same trigger pulse is applied simultaneously; unsymmetrical triggering occurs when triggers are applied separately.

Symmetrical or unsymmetrical output gate depends on timing sequence of input trigger pulses; input triggers from different sources (turn-on and turn-off triggers) produce unsymmetrical output gate.

Collector-to-base feedback coupling is direct (through resistors), with bypass capacitors used to speed up switching from one stable state to the other.

Circuit can be made to assume the same initial stable state whenever voltages are applied by incorporating a definite imbalance within the circuit, or by using a manually controlled "reset" signal.

Output is taken from collector of either transistor in common-emitter circuit configuration.


Output impedance is low when transistor is in conducting (on) state; output impedance is approximately equal to collector load resistance when transistor is in cutoff (off) state.

Circuit Analysis.

General. The basic flip-flop multivibrator is capable of producing a square- or rectangular-wave output pulse (gate) in response to two input triggers. This type of multivibrator has two stable (bistable) states — one transistor is normally conducting while the other transistor is normally held cut off — each one functions for only one-half cycle when triggered. Feedback from the collector of one transistor to the base of the other is direct through a coupling resistor bypassed by a capacitor. The capacity shunts the high-frequency components of the pulse from collector to base around the coupling resistor so that the rapid change taking place at one collector is coupled,

with minimum attenuation, to the base of the other transistor. Because two input triggers (turn-on and turn-off) are required to complete one cycle of operation, the output gate frequency of the flip-flop multivibrator is one-half the input trigger frequency. The output gate length is determined by the time interval between the turn-on and turn-off triggers. Output signals are taken from the collector of either or both transistors in the common emitter circuit configuration.

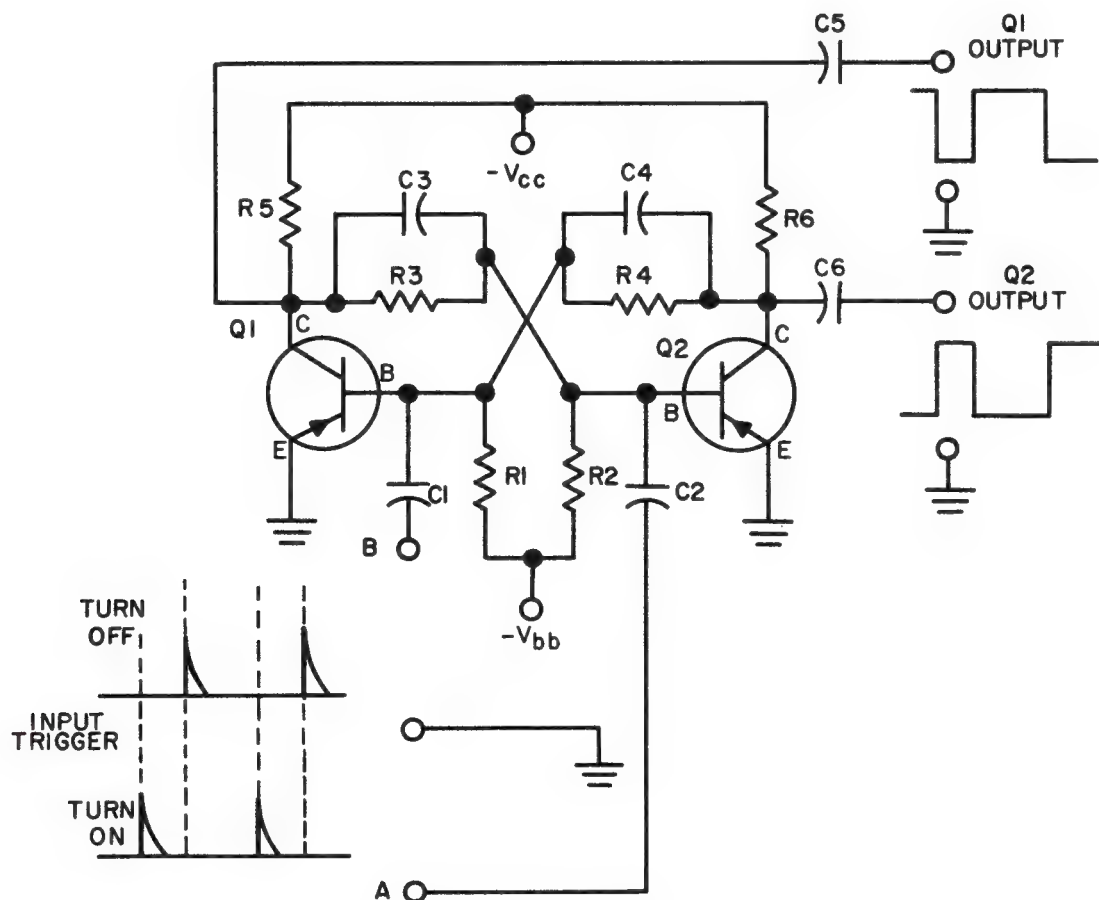Circuit Operation. The accompanying circuit schematic illustrates two transistors in a basic flip-flop multivibrator circuit. Transistors Q1 and Q2 are



Basic Flip-Flop Multivibrator Using PNP Transistors

identical PNP transistors used in a common-emitter circuit configuration; either junction or point-contact transistors may be used in this circuit. Resistors R1 and R2 are the base-biasing resistors for Q1 and Q2, respectively. Resistor R3 provides the direct coupling from the collector of Q1 to the base of Q2, and resistor R4 provides the direct coupling from the collector of Q2 to the base of Q1. Feedback resistors R3 and R4 are bypassed with capacitors C3 and C4, respectively; these capacitors permit faster switching action from one transistor to the other. Resistors R5 and R6 are the collector-load and output resistors for Q1 and Q2, respectively. Capacitors C1 and C2 are the input trigger coupling capacitors for Q1 and Q2, respectively; they provide unsymmetrical triggering. Capacitors C5 and C6 are the output-gate coupling capacitors for Q1 and Q2, respectively. An output waveform can be taken from the collector element of either transistor, or output waveforms can be taken from the collector elements of both transistors simultaneously.

Fixed bias for the PNP transistors of this flip-flop multivibrator is obtained from two separate d-c voltage sources via voltage-divider networks. Resistors R1, R4, and R6 form one voltage divider between the positive d-c ($+V_{BB}$) and negative d-c ($-V_{CC}$) supply voltages. The resistor values are selected so that the voltage at the top of R1 is negative with respect to the grounded P-type emitter of Q1; thus, the emitter of Q1 is forward biased with respect to the N-type base. Another voltage divider, consisting of resistors R2, R3, and R5 between the positive and negative supply voltages, forward biases the emitter of Q2 in the same manner. That is, the voltage at the top of R2 (at the N-type base of Q2) is negative with respect to the P-type emitter of Q2. Because of the voltage-divider action, the voltage at the collector of each transistor is more negative than the voltage at its base; thus, the collector-base junction of each PNP transistor is reverse biased.


When voltage is first applied to the circuit, the current which flows in each collector load resistor (R5 and R6) is determined by the effective resistance offered by transistors Q1 and Q2 for a given value of base-bias voltage. Although the multivibrator shown in the schematic appears to be a balanced circuit, and in spite of the use of close-tolerance components, there is always minor differences in internal resistance within the transistors. As a result of this inherent imbalance, the initial collector current (resulting from

the forward-bias conditions set up by the emitter-base junction resistances and bias resistors R1 and R2) for each transistor is different, and the immediate effect produced by regenerative action between the coupled stages is that one transistor conducts while the other is cut off.

For the purpose of this explanation, assume initially that more collector current flows through transistor Q1 than through transistor Q2; thus, as the collector current of Q1 increases, the negative voltage at the collector of Q1 decreases with respect to its emitter, or ground. Thus, the collector of Q1 becomes less negative and this, in effect, acts as a positive-going pulse, which is directly coupled through resistor R3 to the base of transistor Q2. The positive-going pulse at the base of Q2 makes the base positive with respect to the emitter (ground) and, as a result, Q2 is reverse-biased and approaches cutoff. The collector current of Q2 decreases because of the reverse-bias action between its base and emitter, and the voltage at the collector of Q2 increases, rising towards the value of the supply voltage. In other words, as the collector of Q2 becomes more negative a negative-going pulse is developed across R6, which is directly coupled through resistor R4 to the base of transistor Q1. The negative-going pulse at the base of Q1 makes the base negative with respect to its emitter (ground), and increase the forward bias on the base, causing the collector current of Q1 to further increase. This regenerative process continues until Q1 is driven into saturation (as a result of the increased forward-bias), and Q2 is cut off (as a result of the increased reverse-bias). Thus, with the initial application of dc power, one transistor is turned on while the other is cut off, and each transistor is then held in this particular state of operation by the feedback from the other transistor until the off-trigger arrives.

For the following discussion of basic flip-flop multivibrator circuit operation, refer to the preceding circuit schematic and the following illustration of the idealized theoretical waveforms. Assume that transistor Q1 has been initially turned on and is conducting heavily in a saturated state, while transistor Q2 remains cut off. Thus, the circuit is resting in one of its two stable states of equilibrium as discussed above. The initial turn-on period is represented by time interval a on the waveform illustration, while the steady state conducting condition of Q1 is represented by time interval b . Therefore, the output at the collector of Q1 is at its most positive excursion,

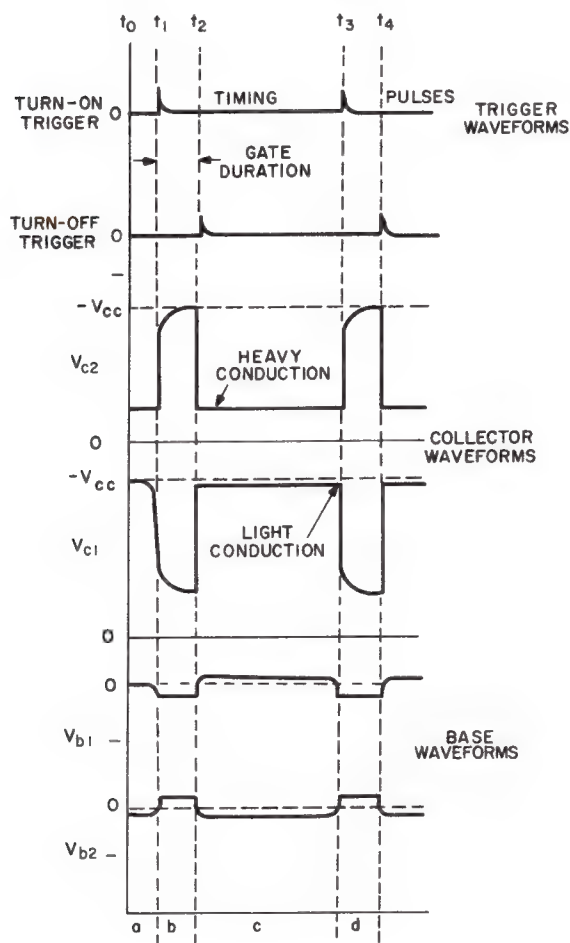while the output at the collector of Q2 is at its most negative excursion (Q2 is cutoff). Since there is no internal time constant circuit provided to permit the nonconducting transistor to be automatically raised above cutoff (the fixed bias network ensures that it is held below cutoff), the circuit remains in this stable condition until a positive off-trigger is applied Q1.



Theoretical Waveforms for Basic Flip-Flop Multivibrator (Using PNP Transistors)

At time t_2 , the positive turn-off trigger is applied to terminal B, and the base of Q1 is instantaneously driven below cutoff. Collector current flow through Q1 reduces, and heavy collector current flow through Q2 develops a positive-going output voltage across R6, which is also applied, through R4 and C4 to re-

verse bias the base of Q1. This additional reverse-bias quickly causes Q1 collector current to cease, and the collector voltage rises quickly towards the supply value producing a negative-going output through C5. At the same time, this negative-going collector voltage is fed back through R3 and C3 to the base of Q2 as a forward bias. This continuous feedback action of reverse bias on Q1 and forward bias on Q2 continues until the collector voltage on Q2 bottoms, or saturation is reached. The circuit now rests in its second stable state, (during time interval c) with Q1 nonconducting while Q2 conducts heavily. The switching action is speeded up by capacitors C3 and C4 which allow the instantaneous changes to be immediately applied to the associated base element to produce the steep leading and trailing edges of the waveform. The circuit remains in this condition (time interval c) until another turn-on trigger of positive polarity is applied to terminal A.

At time t_3 , the positive turn-on trigger is applied to C2 and the base of Q2 which is forward biased and heavily conducting. The instantaneous positive bias produced by the input signal cancels the existing forward bias and reverse-biases Q2, stopping collector current flow. As the collector current of Q2 ceases, the collector voltage of Q2 rises towards that of the supply and produces a negative-going output signal. Meanwhile, this negative output voltage is also fed back to the base of Q1 through feedback resistor R4 which is bypassed by C4. The instantaneous negative swing through C4 quickly drives the base of Q1 in a forward-biased direction, and causes Q1 to conduct. As Q1 conducts, an output voltage of positive-going polarity is developed across R5, and is fed back through R3, bypassed by C3, to the base of Q2 driving it still further towards cutoff. Thus Q2 is held cut off, while Q1 once again conducts heavily near saturation. This is the starting condition and the other stable operating point (time interval d on the waveform).

Close examination of the waveform illustration reveals that the length of the output gates is determined by the time interval between the turn-on and turn-off triggers. If the frequency of the turn-off trigger is made lower, the time interval between the triggers will increase; hence, the gate length will decrease if the turn-off trigger frequency is increased. Thus, the bistable multivibrator provides a positive or negative output gate in response to a timing input (turn-on) trigger pulse, with the gate being terminated by a

turn-off trigger pulse. If a *single* constant-frequency trigger is used for both the turn-on and turn-off functions, the circuit produces a *symmetrical* square wave output, with a frequency one-half that of the trigger frequency. A single pulse can be used for triggering because either the leading or the trailing edge of the trigger can be used. When conducting, and the leading edge is applied, a positive trigger operates to reverse bias the conducting transistor while the feedback causes the nonconducting transistor to be turned on. Conversely, if the trailing edge of the trigger pulse is applied to the nonconducting transistor, it produces a forward-biased condition and starts the transistor conducting, while feedback from the transistor produces a reverse bias to stop the first transistor from operating. This action is true as long as the trigger is a sharp pulse of short duration. If of long duration, an unsymmetrical output will be produced.

In the symmetrical-input bistable multivibrator under discussion, negative trigger pulses of sufficient amplitude can also be used to initiate the switching action between transistors Q1 and Q2. When the negative pulse is applied simultaneously to the base of the transistors, there will be no effect on the operation of the conducting tube. However, the collector current on the cut-off transistor will be increased, causing the collector voltage to decrease. The decrease in collector voltage when coupled to the grid of the nonconducting transistor drives this transistor into full conduction. In turn, feedback through this newly turned on transistor biases off the originally conducting transistor.

Although it is true that either negative or positive input trigger pulses can cause the switching action to occur, triggering with positive pulses is preferred. For example, if the cut-off transistor is biased with a highly positive potential, a high-amplitude negative pulse is required to drive it into conduction, and only the most negative portion of the pulse has any effect. On the other hand, a low amplitude positive pulse applied to the conducting transistor immediately drives this transistor into cutoff, causing a relatively instantaneous switching action.

Failure Analysis.

No Output. The input trigger should be checked with an oscilloscope to determine whether it is being applied to the circuit, and whether it is of the proper amplitude and polarity. Lack of an input trigger at

the base of Q1 or Q2 can be due to an open coupling capacitor, C1 or C2, or to failure of the external input-trigger source. If the input signal does not appear on the base side of the capacitor use an in-circuit capacitance checker to check C1 or C2 for proper capacitance or an open circuit.

Failure of the base bias or collector bias supply will disrupt operation of the circuit as would an open feedback circuit. Use a voltmeter to check the base bias, collector, and supply voltages. Normal voltage indications on these elements also indicates that neither R1 nor R2 is open and, likewise, R3 and R4 also. If either C3 or C4 is shorted, the circuit will still operate as a direct-coupled unit and operation will be somewhat slowed up, but an output will still be obtained. If normal signals appear on the collectors but not at the output, coupling capacitor C5 or C6 is probably open. Use an in-circuit capacitance checker to verify the capacitance value and to check for an open or shorted condition.

Reduced Output. A reduction of output is usually caused by low collector voltage, improper bias, or defective transistor. A change in the resistance of the associated collector load resistor R5 or R6 will also affect the output amplitude. Check the resistance with an ohmmeter. A leaky or shorted output coupling capacitor, C5 or C6, will form a voltage divider with the input resistor of the following stage. If the input resistor of the following stage is returned to ground or to a bias supply, the collector voltage on either Q1 or Q2 will be changed and operation of the following stage will be upset by the change in voltage on its grid. In addition, this may possibly cause additional collector current flow through collector resistor R5 or R6 and may cause the resistor to burn out.

Incorrect Frequency or Gate Width. The basic flip-flop multivibrator has no parts governing the frequency or width of the output gate signal; these are both governed by the input triggers applied to the circuit. Therefore, any change in the output-gate frequency or width is a direct result of improper operation of the turn-on and/or turn-off trigger generating circuits.

PENTODE FLIP-FLOP (ECCLES-JORDAN) MULTIVIBRATOR

Application.

Same application as basic flip-flop (Eccles-Jordan) multivibrator (electron tube).

Characteristics.


Same characteristics as basic flip-flop (Eccles-Jordan) multivibrator (electron tube), except it uses plate-to-suppressor grid feedback coupling instead of plate-to-grid feedback coupling.

Circuit Analysis.

General. The pentode Eccles-Jordan (flip-flop) multivibrator is capable of producing a square- or rectangular-wave output pulse (gate) in response to two input triggers. The circuit has two stable (bistable) states — one tube is normally conducting while the other tube is normally held cutoff. Like the triode Eccles-Jordan multivibrator, discussed earlier in this Section of the Handbook, the circuit operation is controlled by the application of an input trigger pulse which causes the conduction to switch from one tube to the other. Thus, the multivibrator will function for only one-half cycle upon the application of each input trigger. Feedback from the plate of one tube to the suppressor grid of the other is direct through a coupling resistor bypassed with a capacitor, whose function is to reduce or eliminate the effects of tube interelectrode capacitance.

The feedback connection to the opposite suppressor grid, instead of the control grid, frees the control grid for application of the trigger pulses. Because two input triggers (turn-on and turn-off) are required to complete one cycle of operation, the output-gate frequency of the bistable multivibrator is one-half the input trigger frequency. The output gate length is determined by the time interval of the turn-off input triggers. Output signals can be taken from the plate of either or both electron tubes.

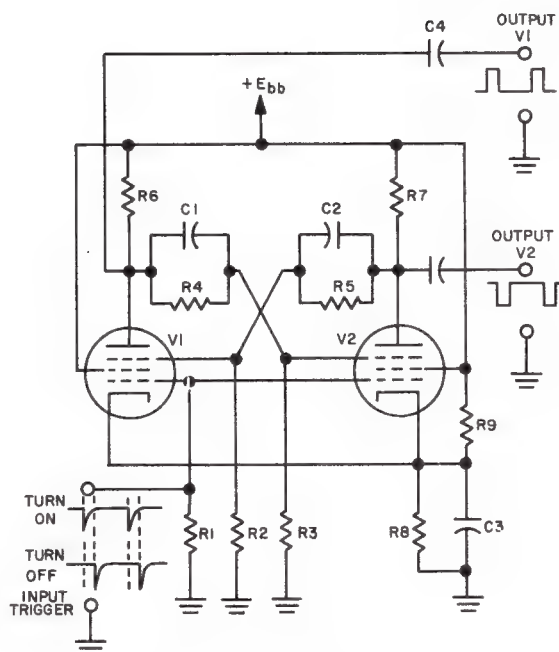Circuit Operation. The accompanying circuit schematic illustrates two pentode electron tubes in an Eccles-Jordan bistable multivibrator configuration.




**Pentode Eccles-Jordan (Flip-Flop)
Multivibrator**

Electron tubes V1 and V2 are identical sharp cutoff pentode-type tubes. Resistor R1 is a common grid resistor for both tubes. Resistors R2 and R3 are the suppressor grid resistors for V1 and V2, respectively. Resistor R4 provides direct-coupled feedback from the plate of V1 to the suppressor grid of V2; resistor R5 provides direct-coupled feedback from the plate of V2 to the suppressor grid of V1. Feedback resistors R4 and R5 are bypassed with capacitors C1 and C2, respectively. These capacitors permit faster

switching action from one tube to the other by reducing the effect of tube interelectrode capacitances. Resistors R6 and R7 are the plate-load resistors for V1 and V2, respectively; the screen grids are tied directly to the supply voltage, $+E_{bb}$. Suppressor grid voltage for V1 is obtained from a voltage divider consisting of resistors R2, R5, and R7; suppressor grid voltage for V2 is obtained from a voltage divider consisting of resistors R3, R4, and R6. Capacitors C4 and C5 are the output coupling capacitors for V1 and V2, respectively. Operating bias for this bistable multivibrator, which is cathode-biased, is obtained from a voltage divider consisting of common cathode resistor R8, bypassed with capacitor C3, and resistor R9. A comparison of the pentode and triode Eccles-Jordan multivibrator circuits reveals their similarities and differences.

Consider now the operation of the pentode Eccles-Jordan multivibrator by referring to the preceding circuit illustration. Since the output-gate waveforms of the pentode circuit are similar to those of the triode Eccles-Jordan multivibrator presented earlier in this Section of the Handbook, reference to the triode circuit waveforms can be made for this pentode circuit as well. The waveforms are reproduced in the following figure for convenience.

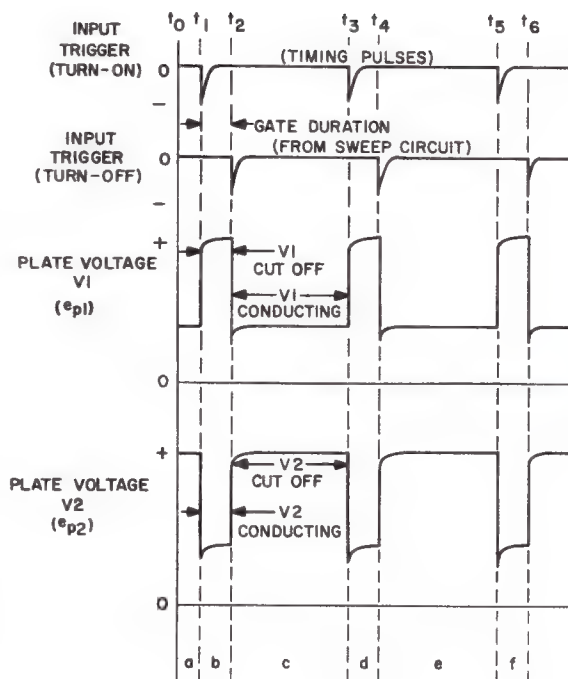

Theoretical Waveforms for Pentode Eccles-Jordan (Flip-Flop) Multivibrator

When voltage is first applied to the circuit, there is a slight conduction through both tubes. However, because of the inherent imbalance of the circuit, one tube will conduct slightly more than the other. For example, if initially the current through V1 should be slightly greater than that through V2, the voltage drop across plate-load resistor R6 will be greater than the drop across plate-load resistor R7. This results in a lower plate voltage for V1, which is applied through resistor R4 to the suppressor grid of V2. The negative-going signal on the V2 suppressor grid reduces the plate current of this tube, thus reducing the current through plate-load resistor R7 and causing a voltage rise at the plate of V2. This positive-going voltage is coupled through resistor R5 to the suppressor grid of V1, further increasing the plate current of V1. Suppressor grid current flows at a slight positive suppressor grid voltage, but decreases at a high positive suppressor grid voltage, such as when the positive-going signal is applied from the plate of V2. The plate current of V1 increases further, and a regenerative action occurs instantaneously to drive V1 into heavy conduction and V2 into cutoff. Thus, the multivibrator is in one of its stable states, as depicted during time interval *a* in the waveform illustration referenced previously. Since there is no internal R-C time constant timing circuit to drive the nonconducting tube out of cutoff, the circuit remains in this stable state until a timing pulse is applied to the control grids to cause the switching action.

Assume now that a negative trigger pulse of sufficient amplitude is applied simultaneously to both control grids. The trigger pulse, applied at t_1 , has little effect on the operation of V2 since this tube is already cut off. However, the same negative trigger drives the grid of V1 below cutoff, causing this tube to reduce conduction. As soon as V1 reduces conduction, its plate voltage rises toward the plate supply voltage, $+E_{bb}$. The positive-going signal at the plate of V1 is now coupled through resistor R4 and applied to the suppressor of V2 driving V2 into conduction. Thus, at instant t_1 a switching action occurs, with the result that V2 now becomes the conducting tube and V1 is cut off. Thus, the circuit is in the second of its two stable states, as depicted during time interval *b*. The multivibrator remains in the condition wherein V2 is conducting and V1 is cut off until the next negative trigger pulse is applied to cause another switching action.

When the desired gate duration is attained, the negative turn-off trigger is applied (at t_2) and the gate is terminated. The negative-going turn-off trigger cuts off conduction of V2 and causes a switching action that returns the multivibrator to its original stable state wherein V1 is conducting and V2 is cut off. The circuit remains in this condition (time interval *c*) until another negative trigger from the timing circuits, the turn-on trigger, is applied at t_3 .

As in the triode Eccles-Jordan multivibrator, the length of the output gates of the pentode configuration is determined by the time interval between the turn-on and turn-off triggers. The gate length will increase if the turn-off trigger frequency is decreased; conversely, the gate length will decrease if the turn-off trigger frequency is increased. If a single constant frequency trigger is used for both the turn-on and turn-off functions, the circuit will produce a symmetrical square-wave output having a frequency one-half that of the input-trigger frequency.

Although positive trigger pulses could be used to "drive" the pentode Eccles-Jordan bistable multivibrator, negative trigger pulses are preferred; a small-amplitude negative pulse when applied to the conducting tube will immediately drive this tube into cutoff to cause an instantaneous switching action. The output of the multivibrator is taken from either or both plate circuits through an output coupling capacitor (C4 or C5). A cathode follower should be used couple the positive gate output to a circuit that requires grid current, since the multivibrator may occasionally fail.

Failure Analysis.

No Output. The input trigger should be checked with an oscilloscope to determine whether it is being applied to the circuit and whether it is of the proper polarity and amplitude. Lack of an input trigger at the grid of V1 or V2 can be due to failure of the external input-trigger source or to the coupling from the trigger source to the multivibrator.

Failure of the supply-voltage source, $+E_{bb}$, will disrupt the operation of the circuit, as will an open cathode circuit. With tubes installed in the circuit, the filament, plate, screen grid, and suppressor grid voltages should be measured, as well as the bias voltage developed across the cathode resistance, to determine whether the applied voltages are within tolerance and whether any of the respective electrode resistors are

open (resistors R2 through R9). If coupling resistor R4 or R5 is open, there will be no feedback signal to affect the multivibrator switching action; in addition, the dc operating potential from the associated suppressor grid will be removed. If bypass capacitor C1 or C2 is open, feedback will still occur, but the inter-electrode capacitance of the tube may cause undesirable effects on the wavefront of the feedback signal. An open output coupling capacitor, C6 or C7, will prevent the output-gate signal from reaching the following stage.

Reduced Output. A reduction in output is generally caused by a defective tube; however, it can also be caused by a decrease in the applied voltage or an increase in the resistance of the associated plate-load resistor, R6 or R7. A leaky or shorted output coupling capacitor, C4 or C5, will form a voltage divider with the input resistor of the following stage. If the input resistor of this following stage is returned to ground or to a negative supply, the voltage at the plate, screen grid, and suppressor grid of both V1 and V2 will be reduced, and the operation of the following stage will be upset by the change in voltage applied to its grid. Also, the additional current through the resistors associated with the electrodes mentioned previously may cause the resistors to burn out.

Incorrect Frequency and Gate Width. The pentode Eccles-Jordan (flip-flop) multivibrator has no components governing the frequency or width of its output-gate signals; these are both governed by the input triggers applied to the circuit. Therefore, any change in the output-gate frequency or width is a result of improper operation of the turn-on and-or turn-off trigger generating circuits.

DIRECT COUPLED (OR BINARY) MULTIVIBRATOR (SEMICONDUCTOR)

Application.

The direct-coupled (or binary) multivibrator produces a square or rectangular output waveform primarily for use in computer circuit and switching operations such as computer logic, counting and shift register operations, clock pulse generation and memory circuit.

Because of its simplicity is also serves a variety of similar applications in radar and electronic equipments.

Characteristics.

Usually employs self bias.

Provides two outputs (one is the inverse of the other).

Requires a turn-off or reset trigger to change state.

Requires a minimum number of parts.


Operates at low levels (10-15 millivolt input controls 200-300 millivolt output).

Circuit Analysis.

General. The dc coupled or binary (count-by-two circuit) multivibrator offers design simplicity and a minimum of parts which leads to its frequent use in logic circuitry. It is basically, a bistable multivibrator with two states of stable operation. In the on-state, one transistor continuously conducts while the other remains cut off. In the off-state, the previously conducting transistor is cut off and the previously non-conducting transistor is switched on. The change of state is accomplished only by a separate trigger. There is no R-C timing network to permit automatic charge or discharge to control the switching rate. Design is usually such that the conducting transistor operates in a saturated condition. Thus the base voltage is higher than the emitter and the collector voltages, and all element voltages are low in value with only a fraction of a volt difference between them. Consequently, the conducting transistor has a low value of dissipation, and the output is also low. As a result, the dc multivibrator usually requires a stage of external amplification if other transistors are to be driven by it. When operated as a saturated flip-flop it requires a higher turn-off power than that of the non-saturating type (discussed later in this section of the Handbook). Since no emitter resistors are used, the circuit is somewhat sensitive to temperature changes above 60 degrees Centigrade.

Circuit Operation. The following schematic illustrates a basic dc flip-flop. Note that only two resistors (R1 and R2) are used, which serve both as collector resistors and as feedback resistors, and

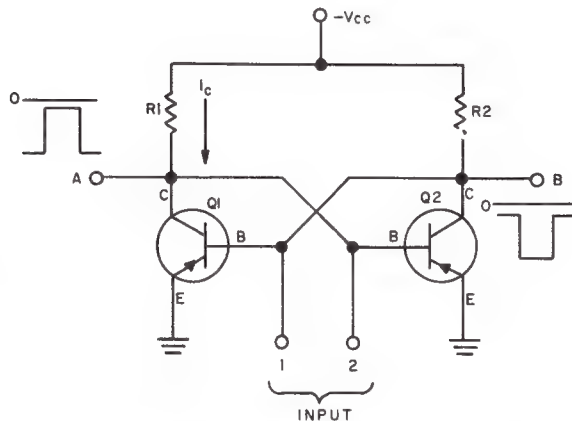
across which the output is developed. For simplicity, the control trigger circuitry is not shown.



Basic PNP Direct-Coupled (Binary) Flip Flop

Initially a forward bias is applied to both transistors by connecting the base of Q1 and Q2 to R2, and R1, respectively (the negative supply voltage through the resistor places a forward negative bias on the transistor). In the absence of a trigger pulse both transistors tend to conduct. However, the first one to establish a flow of collector current produces a positive-going collector swing which is applied to bias the opposite transistor below cutoff. Because of the inherent slight difference in base resistance between similar transistors, one transistor will always conduct more heavily than the other. Assume for the sake of discussion that Q1 is conducting and Q2 is driven to cutoff. Since this circuit operates at collector saturation, a heavy current flows from the supply through resistor R1, and transistor Q1 to ground. The flow of i_c as shown on the schematic produces a positive voltage drop across R1. This positive-going voltage is fed back directly to the base of Q2 as a reverse bias which immediately stops conduction through Q2. The heavy flow of i_c drops the collector voltage of Q1 to almost zero (it is saturated). Meanwhile, since Q2 stops conducting its collector voltage rises to nearly the full negative supply value. Since the base of Q1 is connected to the collector end of R2, this negative-going feedback voltage is applied to the base of Q1 as a large forward bias. The base voltage on Q1 is now higher than that of the collector, and since the emit-

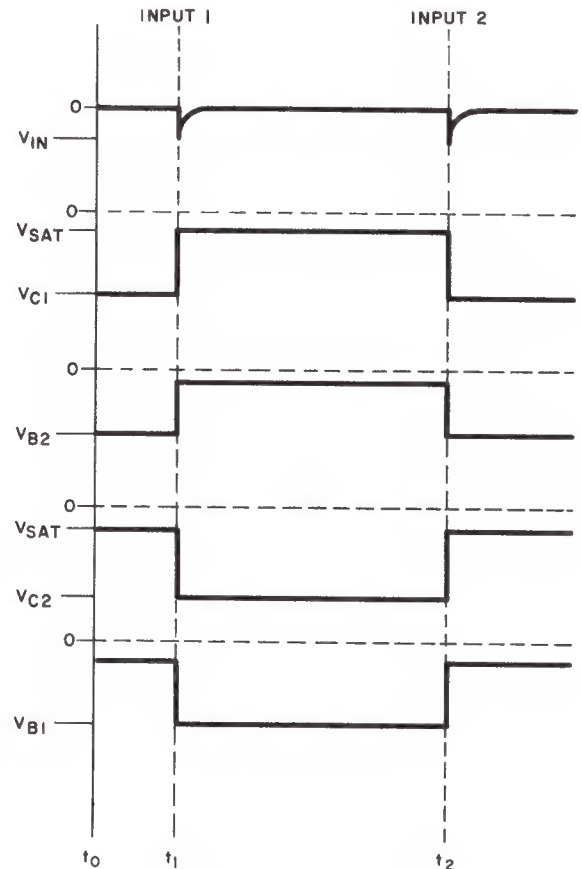ter is grounded and effectively at zero potential, the base voltage is also higher than the emitter. Thus the base voltage is the dominating voltage which holds Q1 conducting until a turn-off trigger arrives. The circuit is now operating between intervals t_1 and t_2 as shown on the following waveform illustration.




Typical Waveforms

At time t_2 the turn-off trigger arrives, and a negative input pulse is applied via input 2. Consequently, the negative input on the base drives Q2 in a forward direction (the small saturation voltage fed from the collector of Q1 is easily overcome by the negative input pulse), and Q2 conducts. Immediately, current flow through R2 causes a positive swinging voltage to be applied to the base of Q1, stopping conduction through R1. As conduction ceases through R1 the collector voltage of Q1 rises towards the full negative supply value, and feeds back an increasing negative

voltage to the base of Q2. Thus, Q2 is quickly switched into conduction while Q1 is turned-off. At time T_2 the second stable state is accomplished, and now the circuit awaits another turn-off trigger at time t_3 . This is merely a repeat of the sequence of operation at time t_1 . Namely, a negative trigger is applied to input 1 which drives the base of Q1 in a forward direction, causes collector current flow through R1 and feeds back a positive-going voltage to the base of Q2 causing it to stop conducting. Instantaneously, the collector voltage of Q2 rises towards the negative supply value, and drives the base of Q1 into heavy conduction. The circuit is now resting in the initial state, with Q1 conducting heavily and Q2 cut off.

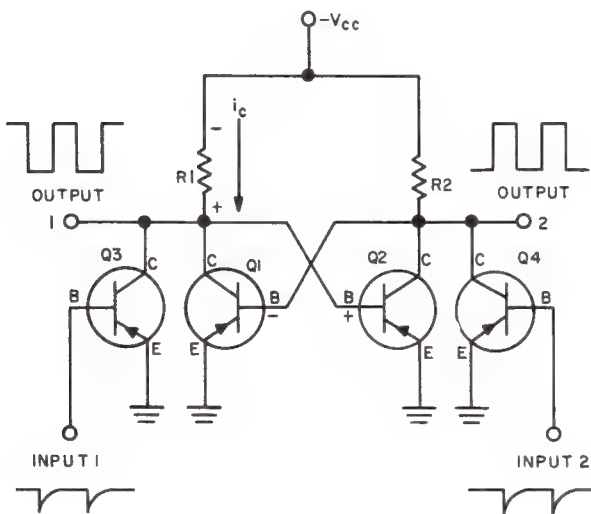The circuit schematic of a practical binary multivibrator is shown in the following illustration, with control circuitry. Except for the operation of transistors Q3 and Q4, circuit operation is identical and corresponding parts are labelled identically so that the previous discussion applies.



Typical PNP Binary Multivibrator

Transistor Q3 and Q4 merely act as switches, when a negative trigger is applied to their base they conduct, and when no trigger is present they are held nonconducting. The control transistor connected to the conducting multivibrator transistor is held at cutoff by the low saturation voltage of the collector to which it is connected, while the other is held cutoff

by the high reverse bias at the non-conducting collector. Since their emitters are connected directly to ground, when triggered, they develop a shut-off pulse which stops the conducting transistor from operating and causes the switching. For example, assume Q1 heavily conducting, with its base held negative by the feedback from R2. Q4 is resting reverse biased awaiting the control trigger. When the negative control trigger (input 2) arrives, the base of Q4 is driven negative and this forward bias causes the transistor to conduct through R2. Flow of collector current in Q4 develops a positive swinging pulse across R2 and drives the base of Q1 positive to cutoff. Thus Q1 is stopped from conducting. Transistor Q3 operates similarly, assuming Q2 conducting and Q1 cut off, the negative input to Q3 (input 1) causes collector conduction and produces a positive pulse across R1, thereby driving Q2 base positive to cutoff, and switching Q1 into conduction by the feedback developed as the collector of Q2 rises towards the negative supply at cutoff.

Failure Analysis.

Partial or No Output. A no-output condition can only be caused by a lack of bias voltage because of a blown fuse or defect in the supply, or because both transistors Q1 and Q2 or load resistors R1 and R2 are defective. If either Q1 or Q2 is operable and either R1 or R2 is not open, a single unswitched output will be obtained, since the circuit has two states of operation. First check the supply voltage with a high resistance voltmeter to ascertain that a blown fuse or defective power supply is not at fault. Then check the collector voltage to ground. Transistors Q1 and Q3 will show either a high negative voltage or practically zero voltage depending on whether or not Q1 is conducting, while Q2 and Q4 will produce exactly the opposite indication under normal operation. If both Q1 and Q2 indicate either a low voltage or a high voltage, one or both of the transistors is at fault. Use an in circuit transistor checker to locate the defective one. In the absence of a transistor checker use an ohmmeter, and check the forward and reverse resistance of the emitter and collector junctions with the bias removed. The forward resistance should be considerably lower than the reverse resistance. Replace any defective transistors with known good ones. Since control transistors Q3 and Q4 shunt the multivibrator transistors, if defective, the output will also be shunted to ground. If inoperative, there will still be a single output and the stage will not change state.

If they are simultaneously shorted, there will be no output and both Q1 and Q2 collector voltage will be almost zero. If only one is shorted there still will remain a single output which cannot be switched by application of an input trigger.

Reduced Output. A reduced output is usually caused by low collector voltage, improper bias, or a defective transistor. Any change in the resistance of collector load resistors R1 or R2 will also affect the output amplitude. Use a high resistance voltmeter to check the supply and collector voltages, and measure the resistance of R1 and R2 with an ohmmeter. If the voltages are normal and both R1 and R2 are of proper value the transistor must be at fault. Check the beta of both transistors with an in-circuit checker to determine which has a loss of gain, or use an oscilloscope to locate the low output waveform and associated transistor.

Incorrect Frequency or Gate Width. The direct-coupled multivibrator has no parts governing the internal frequency or width of the output gate signal; these are solely controlled by the input triggers applied to the circuit. Therefore, any change in output gate frequency or width can only be a direct result of improper operation of the turn-on or turn-off trigger generating circuits, not the multivibrator.

SQUARING MULTIVIBRATOR (SEMICONDUCTOR)

Application.

The squaring multivibrator, also known as the Schmitt trigger or emitter-coupled bistable multivibrator, is primarily used to supply a square or rectangular output when triggered by a sine-wave, sawtooth, or other irregularly shaped waveforms.

Characteristics.

May be self or fixed biased.

Has two stable (bistable) states of operation (one transistor conducts while the other is cut off, and vice versa).

Provides a symmetrical output gate regardless of input waveform.


Collector to base feedback provides one switching path, while common emitter coupling feedback provides the other switching path.

Use common emitter configuration.

Circuit Analysis.

General. The Schmitt circuit differs from the conventional bistable multivibrator circuit in that one of the coupling (feedback) networks is replaced by a common emitter resistor (the equivalent of cathode coupling in the electron tube). The additional regenerative feedback developed by the common emitter-feedback coupling arrangement provides quicker action and straighter leading and trailing edges on the output waveform than in other multivibrators. Because of the relatively instantaneous switching action of this arrangement, the waveform of the input trigger has no effect on the output so that essentially square-wave output signals are always produced.

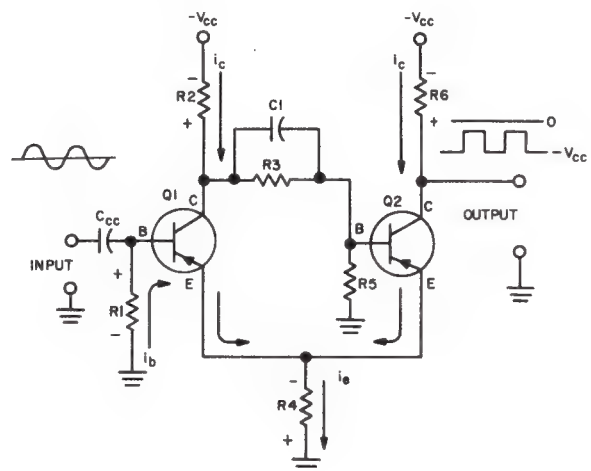Circuit Operation. The schematic of a typical Schmitt type squaring circuit is shown in the following illustration.



PNP Squaring Multivibrator


Transistor Q2 is the initially conducting transistor, which is supplied with forward base bias by resistor network R2, R3, and R5 connected as a voltage divider between the negative voltage supply and ground. Capacitor C_{cc} and base resistor R1 form a conventional R-C input coupling circuit. Resistor R4 is the feedback (coupling) resistor which is common

to both emitters, and R6 is the collector resistor of Q2 across which the output waveform is developed. Capacitor C3 bypasses feedback resistor R3 to help speed up switching action.

Initially, transistor Q2 conducts heavily because of the large forward bias supplied by the voltage divider consisting of collector resistor R2, feedback resistor R3, and base resistor R5, series-connected between the negative supply and ground. A reverse collector bias is applied Q1 through R2, and a reverse emitter-bias is developed across the common emitter resistor R4 by Q2 current flow. Base current flow through R1 is also in a direction which produces a reverse base on Q1, so that Q1 cannot conduct until triggered. Thus, Q1 remains cutoff, while Q2 conducts. With Q2 conducting, a positive-going output voltage is developed across collector resistor R6 which lowers the effective collector voltage of Q2 to almost zero. No output coupling capacitor is shown since the circuit may be direct coupled to the following driver stage, if desired.

Assume now a sine-wave input signal is applied to C_{cc} . During the positive half-cycle of operation the positive input voltage applied across R1 keeps Q1 reverse-biased so that it cannot conduct. Since in this condition the output is developing a positive signal similar to that through initial conduction, as explained previously, it is evident that the input and output are in phase. When the input signal swings negative during the opposite half-cycle of operation, a negative voltage appears across R1 as C_{cc} discharges. The case of Q1 is thereby driven negative and forward biased, starting collector current flow through R2. The direction of electron flow is such that the collector end of R2 becomes positive (as marked on the schematic), and this instantaneous positive swing is coupled through C1 to the base of Q2, appearing as a positive reverse bias which instantly stops current flow through Q2. The reduction of collector current flow through R6 produces a voltage of opposite polarity to that shown on the schematic, that is a

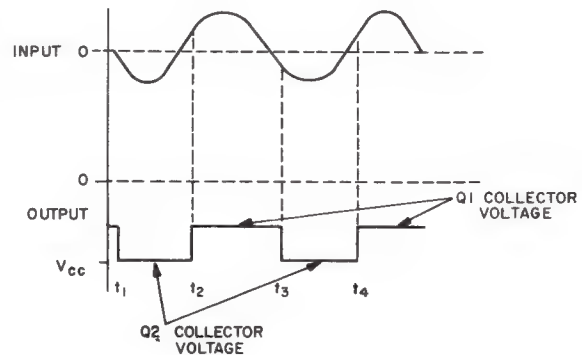negative output voltage, as the collector of Q2 rises towards the supply voltage (time t_1 to t_2 on the following waveform illustration).



Typical Input and Output Waveforms

Although R3 connects the collector of Q1 to the base of Q2, and any voltage appearing on the collector of Q1 will also eventually appear on Q2 base, a speed up of this action is obtained by bypassing R3 with capacitor C1. Thus, the high frequency components of the collector signal are not slowed up by the resistance of R3 so that switching action is faster than without C1.

Consider now the effect of the common coupling resistor (R4) in the emitter circuit. Initially the heavy current through Q2 produced a negative drop across R4, as marked on the schematic. This negative emitter bias which is degenerative, because no bypass capacitor is employed, also tends to prevent Q2 current flow. However, the base bias of Q2 is much larger and the degenerative emitter voltage produced across R4 has little effect on Q2 collector current flow. However, Q1 is already at cutoff, and this additional negative emitter bias ensures that it remains so

until sufficient base input is applied (on the next half-cycle) to overcome this reverse bias.

With the collector current flow of Q2 reducing, the degenerative voltage developed across R4 also reduces, which is the same as applying an increasing positive voltage between emitter and ground. Thus, while the base of Q1 is driven in a forward-biased direction by the input signal, a regenerative feedback is developed in the emitter circuit by the reduction of Q2 current flow. Consequently, transistor Q1 is quickly driven into heavy conduction near saturation. The resulting instantaneous positive swing developed across R2 is instantly applied through C1 to the base of Q2, and quickly drives Q2 to cutoff. The circuit now rests in its second stable state (interval t_1 to t_2) until another trigger arrives to drive Q2 into conduction and cut off Q1.

When the input signal again swings in a positive direction (time interval t_2), the positive voltage appearing across R1 causes a reverse bias to be applied Q1 base and reduce collector current flow through R2; this produces a negative swinging voltage across R2, which is applied to the base of Q2 through capacitor C1. The negative swing forward-biases Q2 and starts it conducting, and develops a positive-going voltage swing across R6 to provide an in-phase output voltage. Simultaneously, the increased negative emitter (reverse) bias developed across feedback resistor R4 further stops conduction in Q1. This regenerative feedback action quickly drives Q2 to collector saturation and Q1 to cutoff, whereupon the rising negative collector voltage of Q1 applied to the base of Q2 through C1 and R3 holds Q2 strongly conducting despite the degenerative emitter voltage developed across R4 (time interval t_2 to t_3). This is the initial order of conduction and the transistor awaits the next trigger (at time t_3) to turn off Q2 and turn on Q1. Because of the extreme regenerative action of the emitter-coupled circuit, once started, the switching action is quickly accomplished, and the shape of the input trigger has no effect in determining the output waveform. Cutoff and turn-on is sharp and the sides of the waveform are steep. The width of the output waveform like the other bistable multivibrators is controlled by the difference in time between the off

and on pulses. When symmetrical and equal a true square wave is produced.

Failure Analysis.

Constant or No Output. Lack of supply voltage, an open common emitter resistor, or defective transistors are about the only three items which can cause a no output condition, since at least one steady output can always be obtained if any voltage is present. Check the supply voltage with a high resistance voltmeter to make certain that a blown fuse or defective supply are not at fault. Since R4 connects both transistors to ground and they are reverse collector biased, no conduction will occur if R4 is open, and a steady negative output will be obtained. A zero emitter to ground voltage reading will indicate that R4 should be replaced. If a steady positive, or near zero but constant voltage is obtained, Q1 is probably defective. On the other hand if Q2 is shorted the same indication would occur. Likewise, if Q2 is open a steady negative output voltage would be obtained through R6. It is evident that it is rather difficult because of the feedback and direct connections in this type of circuit to obtain a specific indication which conclusively points to only one cause of trouble. Therefore, a simple voltage check plus a resistance analysis of the few parts involved should quickly locate the defective component. If the voltage and resistance are correct but an unswitchable steady output is still obtained, check that an input trigger is being received on both sides of coupling capacitor C_{cc} , using an oscilloscope.

Reduced Output. A reduced output can occur because of low supply voltages, improper bias voltage, or defective transistors. Check the supply and bias voltage with a high resistance voltmeter. Use an incircuit transistor checker, or check for a low forward-resistance and a high reverseresistance with an ohmmeter.

Incorrect Pulse Width or Frequency. Like the other bistable multivibrators, an effect on frequency or pulse width is controlled by the time difference between the on- and off-triggers. Thus any faulty operation of this type is due solely to defects in the trigger generating circuits and not the multivibrator.

SATURATING MULTIVIBRATOR (SEMICONDUCTOR)

Application.

The saturating multivibrator is used to supply a rectangular gate, or trigger, in radar and control applications, and in the logic switching circuits of computers and similar devices.

Characteristics.

Usually uses fixed bias.

Provides two outputs simultaneously, one the inverse of the other. Requires a turn-on or turn-off trigger to change state.

Has two (bistable) stable states (one transistor conducts while the other remains cut off and vice versa).


Output power is considerable lower than that of the nonsaturating type.

Operating speed is slower than the non-saturating multivibrator.

Circuit Analysis.

General. In the saturating multivibrator, the emitter and collector voltages are lower than the base voltage and there is only a few tenths of a volt difference between them. Consequently, it takes more driving power in this saturating circuit, as compared with the nonsaturating circuit, to drive the stage out of saturation (a larger trigger is required). The output voltage is also less. Thus, while a certain amount of stability may be imparted by saturated operation the gain and speed suffer. The gain is limited by the low saturation voltages, and the speed by the amount of time required to obtain hold dispersion (the extremely heavy saturation current injects extra holes in the base, which require a finite recovery time to remove them). As a result, the saturated circuit is used where its simplicity makes it more economically feasible than the non-saturating type.

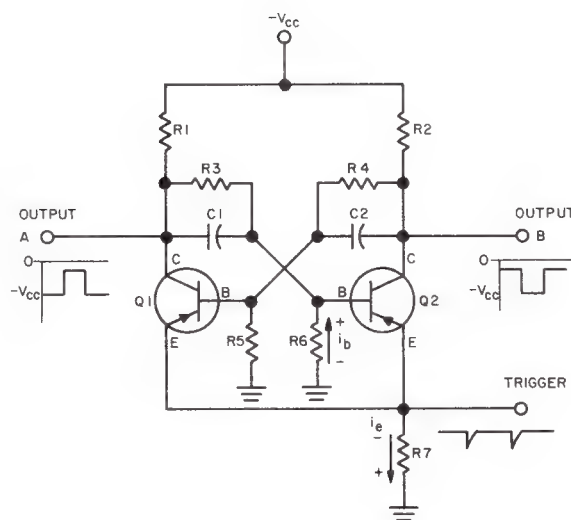Circuit Operation. The schematic of a typical saturated multivibrator is shown in the accompanying illustration.




Saturated PNP Multivibrator

Fixed bias is applied by a voltage divider arrangement, consisting of R1, R3, and R6 for transistor Q2, and R2, R4, and R5 for Q1, connected between the negative supply and ground. Feedback resistors R3 and R4 are bypassed by capacitors C1 and C2, respectively, to speed up response. An output is taken from each collector, and the input trigger is applied across emitter resistor R7, which is common to both transistors. This circuit arrangement is that of the conventional bistable multivibrator arranged for common emitter triggering.

In the quiescent condition, with no trigger applied, both transistors conduct immediately when the supply voltage is applied, since they are both forward biased through voltage dividers to the negative supply. Although the circuit is symmetrical, that is, the collector, feedback, and base resistors are all of equal values to minimize any unbalance, there still exists a

slight difference in base resistance between transistors of the same types. Thus, one transistor always tends to conduct more heavily than does its counterpart, and through feedback from the collector to the opposite base drives the associated transistor to cutoff, and itself to full conduction. Assume for the sake of discussion the normally-on transistor is Q1, while Q2 is the normally-off transistor. From time t_0 to t_1 (as shown on the following waveform illustration) the initial conduction is established as previously explained, so that a time t_1 transistor Q1 is conducting while Q2 is cutoff. Since the turn-off input trigger at this time is stopping Q2 there is no effect and the circuit rests in its initially-on state until time t_2 .

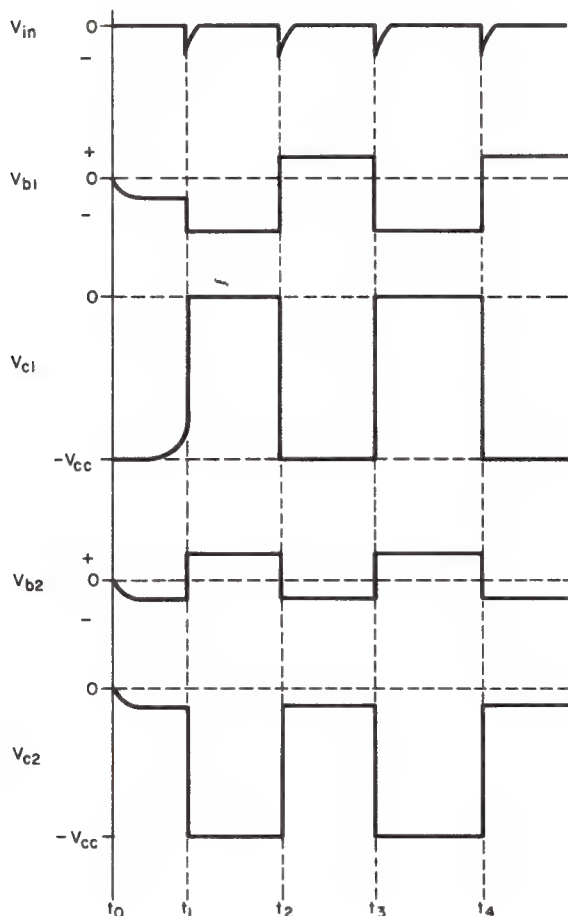

Typical Waveforms

During the interval from t_1 to t_2 a continuous positive (reverse) bias exists at the base of Q2 due to base current flow from ground through R6, producing a voltage drop of the polarity shown on the schematic (this current is actually produced by reverse collector current I_{ceo}). Thus, with reverse base bias and a reverse collector bias, Q2 remains cut off until the next turn-on trigger arrives. Since no collector current flows through R2 the collector of Q2 rises towards the value of the negative supply voltage and drives Q1 base in a forward-biased direction, causing heavy conduction through Q1. The heavy collector current drops the voltage across R1 to almost zero, and a positive-going output is produced at A, while a negative output from Q2 is produced at terminal B. Once saturated, the collector voltage of Q1 is less than the base voltage fed back from Q2. With high current but low voltage, the power dissipation of the transistor is well within ratings (one advantage of saturated operation is the low collector dissipation involved). The heavy emitter current flow through the common, emitter-coupling resistor R7 places a large degenerative voltage on the emitter of Q2 which effectively reverse-biases Q2. Thus Q2 is held in its off-state, regardless of whether or not the off period is long enough for C1 to discharge. The only effect on operation that C1 has is that of speeding up the switching operation by shunting the high frequency transients around R3 to help speed up turn-on, or turn-off, switching action.

When the negative trigger is applied at t_2 the emitter of Q1 is driven negative, which is the same as driving the base positive to reverse bias the transistor. Since transistor Q2 is already reverse-biased, this trigger has no effect on Q2, only on Q1. Consequently, the collector and emitter current of Q1 is reduced. This reduction of collector current produces a negative-swinging voltage across collector resistor R1, and through C1 to the base of Q2. The instantaneous negative swing applied to the base of Q2 drives Q2 in a forward-biased direction, and causes collector current flow through collector resistor R2. The voltage drop across R2 produced by the increasing collector current reduces the collector voltage, effectively producing a positive-swinging voltage at the collector, which is fed back through capacitor C2 to the base of Q1. The positive-swinging voltage drives the base of Q1 instantaneously in a reverse-biased direction and causes a further drop in collector current. The

regenerative feedback action continues smoothly and quickly until Q2 is driven into collector saturation (collector voltage bottoms), while Q1 is cut off. While this regenerative feedback and switching action occurs, a degenerative voltage is developed across common resistor R7 in the emitter circuits of both transistors. Although this degenerative emitter voltage normally is of such polarity as to oppose the increase of current, it is not of as great an amplitude as the feedback voltage developed across R5 which is driving Q1 to cutoff, or the feedback voltage developed across R1 which is driving Q2 into conduction. It does, however, aid in obtaining collector current cut off on Q1 since the transistor is already being driven in that direction, and eventually reaching saturation. Because the heavy collector saturation current of Q1 produces extra holes in the base of Q1, transistor Q1 does not stop conduction immediately when its base voltage is driven positive and base current flow is stopped. But instead, the collector current continues to flow for a finite interval, even though there is no forward bias on Q1, until the holes are removed from the base of Q1 and cut-off prevails. With no collector current flow, the collector of Q1 rises in a negative direction towards the full supply voltage, and a negative output is produced at terminal A. Meanwhile, as Q2 conducts heavily saturated, the collector current is almost zero, and a positive output voltage is produced at terminal B by the voltage drop across collector resistor R2 of Q2. Conditions are now exactly opposite the original state and Q2 rests in the on-state (interval t_2 to t_3), while Q1 rests in the cutoff state awaiting a negative turn-on trigger at time t_3 .

When the turn-on trigger arrives at time t_3 , the emitter of Q1 and Q2 is driven negative. Since Q1 is already in a non-conducting state the trigger cannot further stop conduction so it has no effect on the operation of Q1. However, the trigger does drive Q2 in a reverse-biased direction (a negative emitter trigger has the same effect as a positive base trigger), and causes a reduction of collector current flow through R12. Immediately a negative-swinging voltage is developed across R2 and applied through C1 to the base of Q1, which drives Q1 in a forward direction towards saturation. The increasing collector current flow through R1, again produces a positive-swinging collector voltage which is applied through C1 to the base of Q2, further driving Q2 in a reverse biased direction and further reducing collector current flow.

This regenerative switching action is smooth, continuous and relatively fast so that except for a slight delay caused by hole storage, as explained previously for the opposite condition of conduction in Q1, the switching is considered to be almost instantaneous. When Q1 reaches saturation and Q2 is completely cutoff, minimize hole storage time and produce speedy operation, even as high as 20 MHz. Thus, the tendency is to use saturated circuitry generally for its simplicity and economy. Non-saturated circuits are usually only used when output power requirements call for more power than can be produced with saturated circuits.

Failure Analysis.

General. When making voltage checks use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low voltage ranges. Be careful also to observe proper polarity when checking continuity with an ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

Partial or Steady Output. Failure of one half of the circuit to operate will produce a partial output in the form of a steady single polarity output. Failure of the supply voltage, or emitter resistor R7, are about the only two possibilities of obtaining no output at all. Because of the feedback connections it becomes rather difficult to isolate the trouble by symptom along. It is quicker to make a voltage check and determine if the supply voltage is present, and that no fuse or power supply is at fault. Then use an ohmmeter to the stage again rests in the original conducting state awaiting a turn-on trigger for Q2 to change operation (interval t_3 to t_4). Meanwhile, a positive output is developed across R2 and applied output terminal B, while a negative output is developed across R1 and applied to terminal A.

Practically all the non-clamped multivibrators are of the saturated type, since clamping the waveform to operate within the normal operating region of the transistor when use as an amplifier is necessary. As long as the base drive is allowed to draw collector current until the transistor collector voltage bottoms, saturation will always occur. Therefore a produce the unchanging steady current represented by the flat top of the output pulse there must be no further change of collector current. In the simple multivibrator this is achieved by collector current saturation, and in the

more complicated types of multivibrators by clamping diodes. At the time transistors were first discovered and applied to this type of circuit, hole storage time effects caused a serious limitation in the speed of operation at which practical multivibrators could be made to operate. At the present state of the art, however, special switching transistors have been developed which check for continuity and proper resistance values to locate the defective part.

If either collector resistor R1 or R2 is open, no collector voltage will appear on the associated transistor, Q1 or Q2, respectively, and the bias voltage divider will be open. Therefore, the other transistor will be effectively cutoff biased by the floating base, and the normal reverse collector bias. With no conduction, a single negative output will be produced while the other output will be zero due to the open collector circuit. In the event emitter resistor R7 which is common to both transistors opens, there will be no flow of current through either transistor, but a negative output will appear at both output terminals since the transistors will, in effect, operate as if both were biased to cutoff. Thus, both collector voltages will rise to the full value of the supply. Therefore, if either transistor fails, or both fail, a negative output will be produced.

Normal voltage indications on the base and collector elements of the transistors usually indicates that any associated series resistors have continuity and proper value. However, it is just as easy to check the resistance of each resistor with an ohmmeter because of the few parts involved. Since it is important to check that the proper polarity and amplitude of input trigger exists and that it is present, use an oscilloscope to observe the waveforms. When the waveforms are improper or missing it locates the general area of the trouble, which must then be further localized by voltage and resistance checks.

Reduced Output. A reduced output is usually caused by low collector voltage, improper bias, or a defective transistor. A change in the associated collector load resistor, R1 or R2, will also affect the output amplitude. Use an oscilloscope to observe the waveforms and determine where the reduced amplitude exists. Then check for proper bias and collector voltage in that portion of the circuit, and make certain that the collector resistance is normal. If normal voltages are present and the collector resistance is within tolerance, and a low output amplitude still exists, it must be because of reduced transistor current.

Incorrect Frequency or Gate Width. Since the multi-vibrator has no parts which govern the frequency or width of the output signal, these are both governed by the input triggers' applied to the circuit. Hence, any change in these parameters must be the direct result of improper operation of the turn-on or turn-off trigger generating circuits.

NONSATURATING MULTIVIBRATOR (SEMI-CONDUCTOR)

Application.

The nonsaturating multivibrator is used to supply a rectangular gate or trigger in radar and control equipments, and in the logic switching circuits of computers and similar devices. Particularly where a large power output is required.

Characteristics.

Usually uses fixed bias.

Provides two simultaneous outputs, one is the inverse of the other.

Requires a turn-on or a turn-off trigger to change state.

Has two stable operating states (bistable).

Output frequency is one-half that of the trigger frequency.

Output power is greater than that of the saturating type.


Operating speed is faster than the saturating multivibrator.

Uses clamping diodes to prevent saturation effects.

Circuit Analysis.

General. The nonsaturating multivibrator uses clamping diodes to stop collector saturation, and steering diodes to make certain the proper trigger is received, thus avoiding false triggering. In the circuit discussed below breakdown diodes are also used to prevent forward biasing of the collector which would cause saturation. Consequently, the transistors operate in the normal operating region (over the linear portion of their transfer curve). Basically the circuit is that of a conventional emitter-coupled bistable multivibrator, with the steering, clamping, and breakdown diodes added.

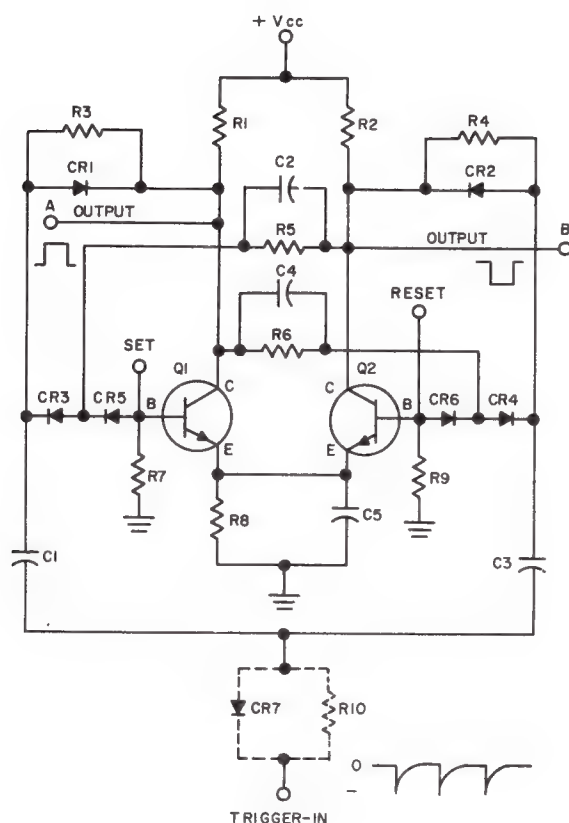Circuit Operation. The schematic of a typical nonsaturating multivibrator is shown in the accompanying illustration.



NPN Nonsaturating Multivibrator


Resistors R1 and R2 are the collector resistors of Q1 and Q2, respectively. The collector to base feedback networks are C2 and R5, and C4 and R6, with the common coupling-emitter resistor R8, bypassed by C5 to prevent degeneration. Resistors R7 and R9 are the base return resistors. The clamping diodes are CR1 and CR2 which shunt R3 and R4. Diodes CR3 and CR4 are the respective steering diodes of Q1 and Q2. Breakdown diodes CR5 and CR6 are saturation limiters which prevent the collector voltage of Q1 and Q2 from being forward biased when conducting. Input triggering pulses are injected at input terminal I (connected for parallel triggering), while terminals A and B are the output terminals from which the square wave output is taken. Transistor Q2 is considered to be the normally-on transistor, while Q1 is normally-off. When the negative input trigger is applied to the

base of Q2, these conditions are reversed and Q2 is turned off, while Q1 is turned on. When the next negative trigger is applied to the base of Q1, the circuit reverts back to the initial state of operation, with Q1 off, and Q2 on.

In the absence of an input signal, both transistors initially conduct. Although the multivibrator circuit is symmetrical (corresponding resistors have the same value), there is always a slight difference in collector resistivity between transistors of the same type, so that one transistor will conduct more heavily than the other. In turn, the heavier-conducting transistor produces a feedback voltage which cuts off the light-conducting transistor. Assume for the sake of discussion that Q1 is initially in the off-condition while Q2 is in the on-condition.

In the quiescent condition, then, Q1 is effectively at cutoff, or at its lowest limit of conduction held by a negative, reverse-bias feedback voltage from the collector of Q2 via R-C network R5, C2 (NPN transistors require a negative bias voltage for cutoff). With no collector current flowing through R1, the collector of Q1 is at a high positive voltage near the supply value (reverse-biased collector), and both steering diode CR3 and clamping diode CR1 are held in a reverse-biased condition. At the same time, the negative feedback voltage produced by collector current flow through R2, and applies through C2 and R5 holds breakdown diode CR5 in a forward-biased condition but cuts off the base of Q1. In a similar manner, the emitter bias developed across R8 and C5 holds the emitter-base junction of Q1 in a reverse-biased condition preventing conduction. Meanwhile, a positive feedback voltage from the collector of Q1 is applied via C4 and R6 to the base of Q2 through breakdown diode CR6. Because of the high reverse voltage (collector of Q1 is near supply level), breakdown diode CR6 conducts in a reverse direction and maintains a constant forward bias on Q2, which causes heavy current flow but not collector saturation. The heavy collector current flow through collector resistor R2 develops a negative-going voltage which is applied to terminal B as an output, simultaneously with the positive output from terminal A. As Q2 collector current increases, the voltage drop across R2 increases also, the collector voltage of Q2 reduces becoming less positive. Since steering diode CR4 is connected to the collector of Q2 through R4, when the collector voltage drops lower than the positive feedback voltage developed across R1 (which is

applied through R6 to the anode of diode CR4) the diode becomes forward-biased and conducts, and as the collector voltage drops further CR2 eventually conducts. The collector of Q2 is now connected through the two diodes to the cathode of breakdown diode CR6 and the junction of R6. As long as the breakdown diode maintains a constant potential between the base and collector of Q2, the collector voltage cannot fall lower than the base voltage. Therefore, the collector cannot be forward biased and saturation cannot occur. Although the collector current may still increase if additional base current drive is supplied, the collector potential remains constant at the fixed minimum value. The operating range of Q2 (and later Q1) then, is from the minimum value of collector voltage to almost the full supply voltage at cutoff. The stage is now in its initial conducting or on-state with Q2 conducting and Q1 off, and rests in this condition until a turn-off trigger is received.

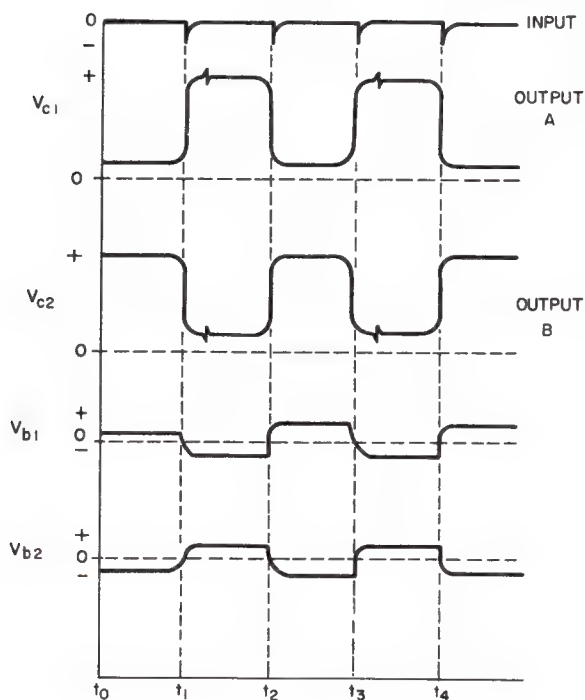

Multivibrator Waveforms

At time t_1 in the preceding waveform illustration, a negative trigger is applied to steering diode CR4, but since it is already conducting the trigger has

no effect and the stage rests in the initially-on condition (interval t_1 to t_2). At time t_2 , the next negative trigger is applied through C1 to the cathode of diode CR3 and simultaneously to CR4 via C3. Since Q1 is nonconducting and the base is already negative, no effect is felt on Q1. However, when the negative pulse passes through CR4 and CR6 and appears on the base of Q2 it instantly partially reverse-biases the conducting transistor and causes a reduction in Q2 collector current flow through R2. As the collector current decreases, the drop across R2 is reduced and collector voltage becomes more positive. This positive-going voltage is applied as feedback through C2 and R5, causing breakdown diode CR5 to conduct in a reverse direction, and driving the base of Q1 in a forward-biased direction. Collector current now flows through R1 and produces a negative-going voltage which is applied through feedback network C4 and R6 to the base of Q2 through breakdown diode CR6. Thus Q2 is driven further in a reverse-biased direction, and a larger turn-on voltage is fed back again to the base of Q1 by the increasing collector current flow through R1. The regenerative feedback continues smoothly and rapidly until Q1 is fully conducting while Q2 is turned-off. The circuit now rests in its second stable state (interval t_2 to t_3) until triggered off again at time t_3 . When Q1 conducts, diodes CR3 and CR1 are activated similarly to diodes CR2 and CR4 in the discussion of Q2 operation, so that CR5, CR3, and CR1 continue to conduct, while a negative output pulse is produced at terminal A. With Q2 held at cutoff by feedback from Q1, a positive square-wave output pulse is obtained at terminal B as the collector voltage of Q2 rises toward the full supply value. In this instance, the emitter bias developed across R8 by conduction of Q1 keeps Q2 emitter reverse-biased, while breakdown diode CR5 maintains a constant difference in potential between the base and collector of Q1. Thus, while additional current may be drawn through Q1 if the base current drive increases, the collector voltage remains steady at its minimum clamped potential. If additional current is required, it is supplied through the shunt diode circuit from the cut-off side of the circuit via R2, and R5. Since any additional base current supplied at this time would cause only a small increase of collector current this shunting action will not appreciably reduce the output voltage developed across R2. But what is more important, is that additional collector current through R1 cannot occur and drop the collector of

Q1 to zero and cause saturation. At time t_4 , the next negative trigger is applied through C1, and CR3, and CR5, to the base of Q1, reducing the flow of collector current because of the reverse bias it applies subsequently, the previously discussed cycle of feedback through C4 and R6 occurs, driving the base of Q2 into conduction, and produces additional feedback through C2 and R5 to drive the base of Q1 in the off-direction. Thus time t_4 corresponds to the initial trigger at t_1 which was previously considered ineffective, since Q2 was already assumed to be turned on.

When a positive trigger pulse is applied through C1 or C3, it reverse-biases the steering diodes and cannot reach a triggering point in the circuit. After the pulse ceases, the positive charge on the capacitor is quickly discharged through either CR1 or CR2. Any similar effect produced by the trailing edge of a negative trigger is also eliminated in this fashion providing a fast recovery time. Diodes CR7 and resistor R10, shown in dotted lines in the schematic, are trigger shaping devices to allow speedy triggering, they are not necessarily a part of the multivibrator. Resistor R10 is used to slow up any positive trigger so that false triggering cannot occur. Diode CR7 acts as a gate for negative triggers and shunts them around R10 to avoid any attenuation, while forcing any positive excursions to travel through R10. Feedback capacitors C2 and C4 function only to pass the high frequency component of the switching transients from collector to base without attenuation. Thus the switching action is speeded up, and the output waveform has steep leading and trailing edges rather than sloping sides produced by slow switching action.

Although clamping and steering diodes provide improved operation, it is possible to design nonsaturating multivibrators using the standard saturated multivibrator circuit with different values of component parts. In this case, parts values are chosen so that saturation does not occur. It is also of interest to note that, while the saturated circuits use heavy currents at very low voltages the dissipation is less than that involved in the nonsaturating circuit, which uses near-saturation currents at higher voltages with a consequent increase in average collector dissipation. Therefore, the nonsaturating circuit usually requires transistors with higher ratings.

Failure Analysis.

General. While making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low voltage ranges. Be careful also to observe the proper polarity when checking continuity with an ohmmeter, since a forward bias through any of the transistor junction will cause a false low-resistance reading.

Partial or No Output. It is necessary that the proper polarity and amplitude trigger be applied before the circuit will switch from one state to another. However, it will rest in one stable state and produce a single output if unable to respond to a trigger, or if disabled. Use an oscilloscope to determine that the proper trigger is applied, and then check the element voltages to determine if the circuit is otherwise normal. Check the supply voltage first to make certain the fault is not in a blown fuse or defective power supply. With the normal voltages present and a proper trigger at the input, if switching will not occur check steering diodes CR3 and CR4 to see if they pass the pulse. If not, replace the defective diode with a known good one. Should emitter resistor R8 which is common to both Q1 and Q2 open, neither will function but a dual positive output will be obtained from terminals A and B since they will rise to the full value of the supply voltage. Failure of breakdown diodes CR5 and CR6 will allow saturation to occur, but will not prevent obtaining an output. When the collector voltage is found to be lower than the base voltage the associated breakdown diode is inoperative and should be replaced with one known to be good.

Low Output. Low collector voltage, improper bias, failure of the breakdown diodes, or the transistors themselves can cause a low output. If emitter bypass capacitor C5 is open, degeneration will cause a reduction of output. Use an in-circuit capacitance checker for this test. A change in the associated collector load resistors, R1 or R2, will also effect the output amplitude. Use an oscilloscope to observe the output waveform and determine where the reduced amplitude exists. Then check for the proper bias and collector voltage in that portion of the circuit. If normal voltage is present and the collector resistor is within tolerance, but low output amplitude still exists it must be caused by reduced collector current.

Incorrect Frequency or Gate Width. Since the multivibrator has no parts which govern the frequency or width of the output signal, these are both governed by the input triggers applied to the circuit. Hence, any change in these parameters must be the direct result of improper operation of the turn-on or turn-on or turn-off trigger generating circuits.

RELAY CONTROL MULTIVIBRATOR (SEMICONDUCTOR)

Application

The relay control multivibrator is used in computers and electronic switching circuits to control a relay or similar electromechanical device where the ratio of the on-off currents is 10 or more.

Characteristics.

Usually uses fixed bias.

Requires a turn-on and a turn-off trigger to change state.

Has two stable states (bistable).

Operates at a frequency of one half the trigger pulse frequency.

Is a saturating type of multivibrator.

Uses steering diodes for stability.

Inductive kickback from the relay coil is prevented by a diode clipper.


Operating speed is limited by the relay operating speed.

Circuit Analysis.

General. In the relay control multivibrator, one transistor is used to operate the relay, with a pull-in to drop-out current ratio of approximately 15 to 1. A rectangular output is simultaneously obtained from the other transistor; a positive output is obtained with the relay closed, and a negative output with the relay open. Steering diodes are provided to prevent false triggering and a protective diode is placed across the relay operating coil to prevent inductive operating transients from affecting the transistor to which the relay is connected.

Circuit Operation. The schematic of a typical relay control multivibrator is shown in the following illustration. As can be seen from the schematic, relay K1 is operated by transistor Q1, while Q2 provides a rectangular output voltage. The negative input trigger is applied through attenuating resistors R9 or R10

and capacitors C3 or C4 to turn off the conducting transistor. Resistor R4 is the collector resistor for Q2, while the relay coil of K1 functions similarly for Q1. The feedback network for Q1 consists of C2 and R3, while Q2 is held in conduction by a voltage divider arrangement of R1 and R2 together with bias resistor R7. Diode CR2 prevents the collector voltage swing of Q1 across relay coil K1 from supplying the feedback to operate Q2. Resistors R6 and R7 are the base bias resistors. Note that fixed bias is supplied from a separate base bias source, and that two different collector supplies are used, with that of Q1 (V_{cc1}) being the lowest.

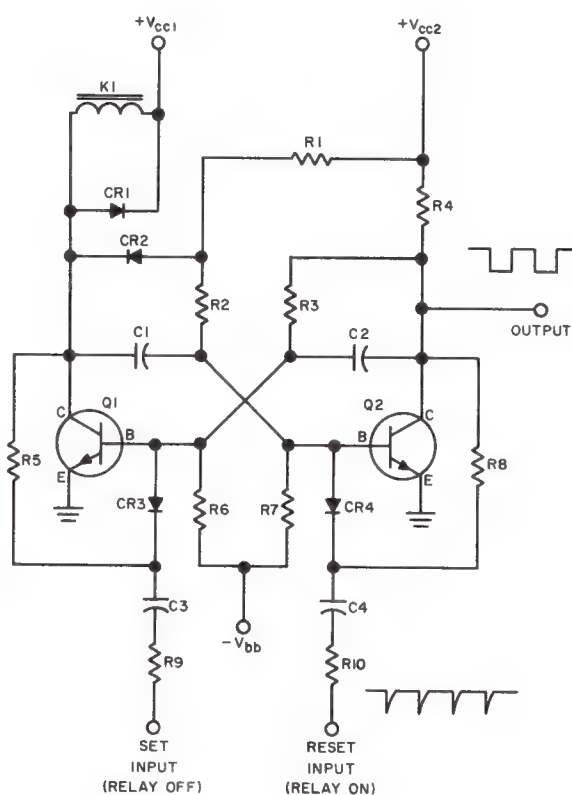

NPN Relay Control Multivibrator

Normally, transistor Q2 is the conducting transistor while Q1 is cut off. Initially both transistors will conduct, but with bias voltage divider R1, R2, and R7 connected between the high positive voltage of V_{cc2} and negative base bias supply V_{bb} , a positive (forward) bias exists on Q2 base. Therefore, Q2 conducts heavily and develops a negative-going voltage

across collector resistor R4, which is fed back through C2 and R3 to the base of Q1, driving it into cutoff. As the voltage across K1 coil rises to the supply value of V_{cc1} , diode CR2 is reverse biased and prevents any feedback from the collector of Q1 to the base of Q2. The negative feedback voltage on Q1 base holds NPN transistor Q1 in a non-conducting condition with only a small reverse-collector current flow through K1 relay coil. At this time, any voltage drop across K1 places a positive bias on protective diode CR1 to keep it reverse-biased and nonconducting. As long as the cathode of diode CR2 remains at the positive level of V_{cc1} , and as long as the voltage drop across R1 keeps the anode lower than the cathode voltage, CR2 also remains in a non-conducting condition.

When a negative trigger is applied to the reset input terminal through R10 and C4, the base of Q2 is momentarily driven negative by the conduction of steering diode CR4, and causes Q2 to stop conducting. Thus, as the forward bias on Q2 is reduced by the input trigger, the collector current voltage drop across R4 reduces (becomes positive-going).

The feedback of the positive-swinging collector voltage through C2 and R3 to the base of Q1 produces a forward bias which causes Q1 collector current to increase. The flow of Q1 collector current through the relay coil of K1 is of a polarity which keeps CR1 reverse-biased. CR2 also remains reverse biased, until the collector potential of Q1 drops below the anode potential applied through R1 and R2. As Q2 collector current decreases and Q1 collector current increases the base of Q1 is further driven towards saturation by the feedback from R4. Eventually, relay K1 pulls in, and transistor Q1 is in saturation, while transistor Q2 is cut off. At this time a positive voltage is developed at the output terminal of Q2 as the collector voltage of Q2 rises to the supply value of V_{cc2} . At saturation the collector voltage of Q1 is less than the base voltage (only a few tenths of a volt) and CR2 is forward-biased. Electron current flow from ground through Q1 and CR2 to R1, and voltage supply V_{cc2} produces a negative reverse bias voltage which is fed back through R2 to Q2 base to hold Q2 in a nonconducting state. This is the second stable state, with Q1 on and Q2 off.

When a negative trigger is applied through R9 and C3 from the set-input of Q1, steering diode CR3 temporarily conducts and produces a momentary reverse bias on the base of Q1, causing Q1 collector current

to reduce. The reducing collector current allows the voltage on the cathode of CR2 to rise in a positive direction towards supply voltage V_{cc1} and eventually reverse-biases the diode. The positive voltage fed back to the base of Q2 through R1 and R2 now causes Q2 to again conduct. Thus Q2 quickly reaches the initial stable conducting state with Q1 cut off by the negative feedback through C2 and R3. When the collector current flowing through relay coil of K1 is reduced to zero, the inductive field about the coil collapses and causes CR1 to momentarily conduct when a negative transient appears on the cathode. The negative inductive kick is thereby effectively clipped off, protecting Q1 from the inductive surge voltage.

Steering diodes CR3 and CR4 will now allow a positive trigger pulse to appear on the base of either Q1 or Q2, thus false triggering is prevented. Resistors R9 and R10 are not always required, in fact, they are really not a part of the multivibrator. They are used to provide a high impedance input instead of the approximate 300 ohm impedance offered by the coupling capacitors alone. These resistors also prolong the discharge time of the trigger, ensuring that the switching action occurs before the trigger is removed. With the steering diode cathodes connected back to their associated collector through R5 and R8, the conducting transistor maintains the diode in an almost forward biased condition (in saturation the collector is almost the same value as the base voltage — within tenths of a volt). Thus the large trigger pulse instantly turns the diode on and triggers the conducting transistor off. If a negative trigger pulse was accidentally applied to the nonconducting transistor, the large collector to base reverse bias would prevent the diode from being forward biased, and the trigger would be ineffective.

Since the output voltage is in-phase with the closing of the relay it may be used to signal the position of the relay or to trigger an associated circuit. The prime purpose of this multivibrator circuit, however, is to control the relay. Since the relay is a mechanical device, it operates at slower speeds than the electronic circuit; thus the relay operating speed determines the maximum switching speed.

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of shunting resistance employed on the low voltage ranges. Be careful to observe proper polarity when

checking continuity with an ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output or Partial Output. Total loss of output could only result from lack of supply voltage, since an output will be produced even if both transistors are inoperative. Although the relay will not operate if Q1 is defective or has a defective circuit part, a positive voltage equal to the V_{cc2} supply will still be obtained from Q2, if inoperative, or a negative output if operable. Use an oscilloscope to determine that the proper input trigger exists and passes through the correct steering diode (an open diode can prevent triggering). Then measure the supply voltage and check the collector voltage on both transistors. With the correct collector bias supply voltage and base bias voltage present, the collector of the conducting transistor should measure very low (a few tenths of a volt), while the cut off transistor will have a high collector voltage almost the same as that of the supply voltage. If both collector voltages are low, either relay coil K1 or collector resistor R4 is open, or the transistor(s) are shorted. Check the resistance of R4 and K1 coil.

Where an output is obtained but no switching occurs, in addition to defective steering diodes, either R9, R10, C3 or C4 can be open. Hence the necessity to use the oscilloscope to determine if the input trigger appears at the transistor base terminal. The circuit will operate without feedback capacitors C1 and C2 but will be somewhat slowed down, and will most probably cause sloping leading and trailing edges on the output waveform at high switching speeds.

Erratic Operation. Since the circuit is controlled by an external trigger it is important to observe the trigger with an oscilloscope to be certain that the trigger itself is not erratic. If the trigger appears normal in shape and amplitude, check operation of the steering diodes and the resistance of R5 and R8. If the resistance of R5 or R8 increases with age, or they become open, the biasing of the steering diodes and the discharge time of R9, C3 or R10, C4 will be changed. Such condition might also be caused by defective transistors. Check the resistors with an ohmmeter, and the diodes and transistors with an in-circuit checker, if possible.

Incorrect Frequency or Gate Width. Since the multivibrator has no parts which govern the frequency or width of the output signal, these are both governed by the input triggers applied to the circuit. Hence, any change in these parameters must be the direct

result of improper operation of the turn-on or turn-off trigger generating circuits.

Low Output. Low collector voltage, improper bias, or defective transistors can cause a low output voltage. A change in collector resistor R4 will also affect the output amplitude. Use an oscilloscope to check the output waveform and determine where the reduced amplitude exists. Then check for the proper bias and collector voltages in that portion of the circuit. If normal voltages are present and the collector resistor is within tolerance, but low output amplitude still exists, it can only be because of reduced collector current.

PART 7-3. MONOSTABLE

MONOSTABLE (ONE-SHOT) MULTIVIBRATORS

General.

The term *monostable multivibrator* refers to one class of multivibrator or relaxation oscillator circuits that function in a stable condition until the application of a trigger pulse. At this time the circuit switches rapidly and goes through one complete cycle of operation, after which it reverts to its original stable condition, in which it remains until the application of another trigger pulse. The monostable (or *one-shot*) multivibrator is essentially a two-stage resistance-capacitance-coupled amplifier, and not an oscillator in the strict sense of the word, with one stage normally cut off and the other stage normally conducting. The one shot multivibrator operates in much the same manner as the free-running, or astable, type discussed earlier in this Section of the Handbook, except that this circuit requires an input trigger to initiate the multivibrator action and produce the output signal.

The monostable multivibrator produces a square- or rectangular-wave output pulse, more commonly called a "gate", having fast rise and fall times and extreme flatness on top; the pulse is produced only in response to an input trigger. The output frequency is determined by the frequency of the input trigger, and the duration of the gate length is determined by the circuit design. The one-shot multivibrator can be used at pulse-repetition rates from zero to maximum which is determined by the gate length and the R-C time constant of the circuit. A nominal range of gate time duration is from 30 to 2500 microseconds,

which will accommodate trigger pulses in the range of 200 to 2000 pps.

In applications requiring different gate lengths, the gate-determining components can be switched in value to produce the desired gate length. Also, the monostable multivibrator may supply both positive and negative gates to as many as four branches. A precaution is that the positive-gate output should not be applied to a circuit requiring grid current as the multivibrator may occasionally fail; the use of a cathode follower or buffer circuit will eliminate this disadvantage. Because the monostable multivibrator is not well suited for controlling the gate length with a turn-off trigger pulse, a bistable multivibrator should be used when this type of control is desired.

Although the output from the monostable multivibrator is sometimes differentiated to provide a pulse either at the leading edge or the trailing edge of the gate waveform, in most cases only the leading edge of the waveform must be extremely fast; the trailing edge is usually not used for critical timing applications. A negative-going leading edge is used whenever possible since such a gate can be obtained rather easily from any tube electrode except the cathode. In addition, a negative gate at the plate of a multivibrator tube will always be generated at a lower impedance than a positive gate at the same plate.

TRIODE PLATE-TO-GRID-COUPLED MONOSTABLE MULTIVIBRATOR

Application.

The triode plate-to-grid-coupled monostable multivibrator produces a square-wave or rectangular-wave output for use as gating or timing signals.

Characteristics.

Circuit assumes a stable state in which one tube normally conducts and the other tube is normally cut off.

Requires an input trigger to cause circuit operation; circuit returns to stable state upon completion of one cycle of operation.

Input trigger can be either negative or positive; negative trigger affects tube that is normally conducting, and positive trigger affects tube that is normally cut off.

Produces square-wave or rectangular-wave output gates for both positive and negative polarity in response to an input trigger.


Output gate length is determined by R-C time constant in grid circuit and by the applied voltage; output frequency is determined by input trigger frequency.

Circuit Analysis.

General. The triode plate-to-grid-coupled monostable multivibrator is a two-stage resistance-capacitance-coupled amplifier capable of producing a square-wave or rectangular-wave output pulse (gate) in response to an input trigger. The monostable multivibrator has only one stable state, in which one tube normally conducts while the other tube is normally cut off, and will function for only one complete cycle upon the application of the input trigger. To achieve the stable condition, the grid of the normally conducting tube is usually returned to B+, while the grid of the tube that is normally cut off is returned to ground or to a negative voltage source. Feedback from the plate of one tube to grid of the opposite tube is through R-C coupling. Because the monostable multivibrator operates for only one cycle in response to an input-trigger pulse, the output frequency of this circuit is dependent upon the input trigger frequency; the output gate length is determined by the R-C time constant of the plate-to-grid feedback network and the applied voltage. Output signals can be taken from the plate of either or both electron tubes.


Circuit Operation. The following circuit schematic illustrates two triode electron tubes in a plate-to-grid-coupled monostable multivibrator configuration. Electron tubes V1 and V2 are identical-type triode tubes; although the accompanying schematic illustrates two separate triodes, a twin-triode is frequently used in this circuit. Capacitor C1 provides coupling from the plate of V2 to the grid of V1, and capacitor C2 provides coupling from the plate of V1 to the grid of V2. Resistor R1 returns the grid of V1 to the negative voltage (bias) supply, -Ecc, and resistor R2 returns the grid of V2 to the positive voltage supply, +Ebb. Resistors R3 and R4 are the plate-load resistors for V1 and V2, respectively. Capacitors C3 and C4 are the output coupling capacitors for V1 and V2, respectively. The tube that

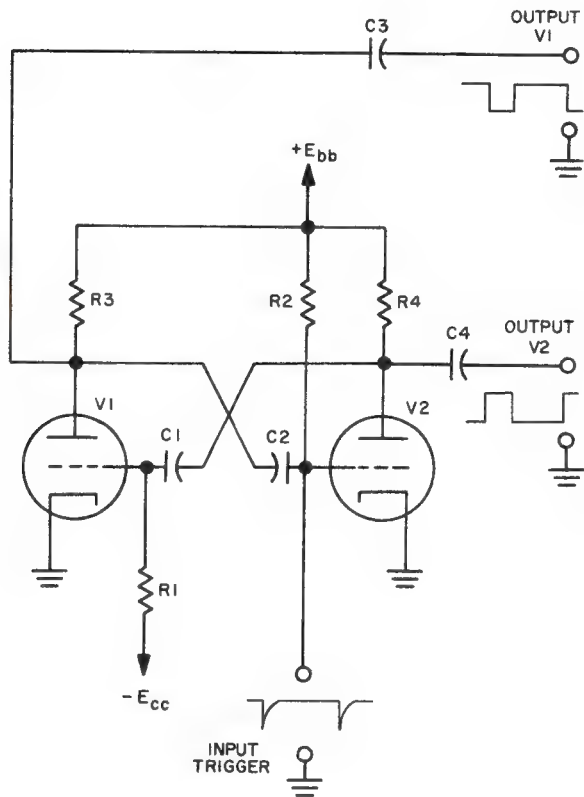is normally cut off is V1, and the tube that is normally conducting is V2.



**Triode Plate-to-Grid-Coupled
Monostable Multivibrator**


The following simplified schematic diagram illustrates the charge and discharge paths for feedback capacitor C2. The cutoff time of V2 is determined by the discharge of capacitor C2 through resistor R2 toward the positive voltage supply, +Ebb. Although the conduction resistance of V1 is included in the discharge path of C2, it is small as compared with the resistance of R2, and can therefore be neglected. The cutoff time of V1 is determined by the period of the input trigger pulse. If the R2-C2 time constant is made exactly one-half the period of the trigger pulse, the multivibrator produces a symmetrical square-wave output; if the R2-C2 time constant is made longer or shorter than one-half the trigger pulse period, an asymmetrical rectangular-wave output is produced.

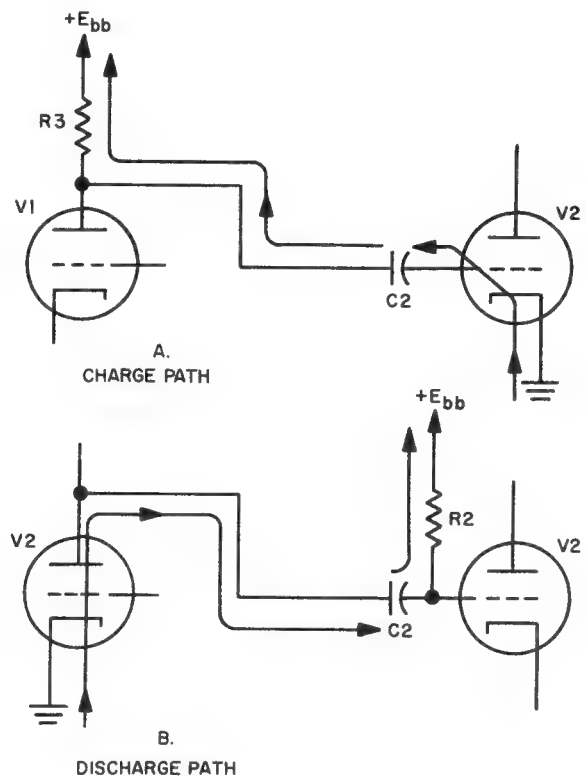

Charge and Discharge Paths for Capacitor C2

Consider now the operation of the triode plate-to-grid-coupled monostable multivibrator by referring to the preceding circuit illustrations and the following illustration to the idealized theoretical waveforms. When voltage is first applied, V2 goes into conduction and V1 cuts off. This action results from the fact that the grid of V2 is returned through resistor R2 to a positive voltage, while the grid of V1 is returned through resistor R1 to a negative voltage. Thus, at time t_0 (start of time interval a) on the waveform illustration, the grid voltage of V2 (eg_2) is slightly positive, causing conduction through V2, and a decrease in its plate voltage (ep_2). The negative-going voltage at the plate of V2 is coupled through capacitor C1 to the grid of V1, thus aiding in cutting off this tube (waveform eg_1). Also, at t_0 , coupling capacitor C2 charges through the low cathode-to-grid internal resistance of V2 (approximately 1K) and the V1 plate-load resistor, R3. The voltage at the plate of

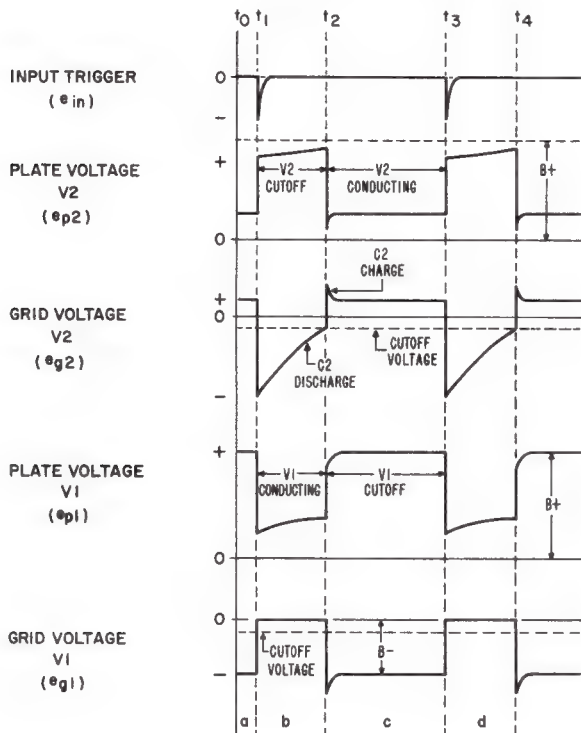V1 is represented by the ep_1 waveform. At t_0 , then, the plate-to-grid-coupled monostable multivibrator assumes its stable state, in which V2 normally conducts and V1 is normally cut off; the circuit remains in this condition until a trigger pulse is applied.



Theoretical Waveforms for Triode Plate-to-Grid Coupled Monostable Multivibrator

Assume now that a negative trigger pulse of sufficient amplitude to cut off the tube is applied directly to the grid of V2. The effect of this trigger pulse (e_{in} , applied at t_1) is to drive V2 into cutoff. As a result of the decreased conduction through V2, the plate voltage of V2 (ep_2) rises toward the supply voltage, and the positive-going signal is coupled through capacitor C1 to the grid of V1, thus raising the grid voltage (eg_1) above cutoff and driving V1 into conduction. The plate voltage of V1 (ep_1) decreases, and the negative-going signal is coupled through capacitor C2 to the grid of V2 to drive V2 further into cutoff. Thus, at t_1 a switching action

occurs and the multivibrator is in a "temporary" stable state in which V1 conducts and V2 is cutoff.

During this temporary stable state (time interval b), capacitor C2 discharges through resistor R2 toward the potential of the positive voltage supply. This causes the grid voltage of V2 (eg_2) to rise toward the potential of the positive voltage supply until the point is reached where the grid voltage of V2 can no longer hold the tube cut off. At that instant, t_2 , V2 once again conducts and the negative-going signal at its plate is coupled through capacitor C1 to the grid of V1 which again cuts off V1. The voltage waveform at the plate of V1 (ep_1) is rounded off, and the waveform at the grid of V2 (eg_2) has a small positive spike of the same time duration as a result of the charging of coupling capacitor C2 when V2 again conducts. The plate voltage waveform of V2 (ep_2) has a small negative spike at the same time duration as the positive spike on the V2 grid voltage waveform (eg_2). Hence, at t_2 , the multivibrator reverts to its original stable condition, in which V2 conducts and V1 is cut off; the circuit remains in this condition (time interval c) until another negative trigger pulse is applied at t_3 .

Close examination of the waveforms reveals that the monostable multivibrator goes through one complete cycle of operation for each input trigger pulse. Also, the time of application of the trigger pulse determines when V1 is driven into conduction, and the R-C time constant of R2-C2 and the applied voltage determines when V2 is driven into conduction. Thus, the monostable multivibrator output frequency is determined by the input trigger frequency, and the output gate width is determined by the discharging of capacitor C2 through resistor R2 toward the potential of the positive voltage supply.

A negative trigger pulse applied to the grid of the normally conducting tube, as was done in this case, is not the only method by which the multivibrator circuit can be triggered. A negative trigger pulse applied directly to the plate of V1 and coupled through capacitor C2 to the grid of V2 serves the same purpose. A positive trigger pulse applied directly to the plate of V2 or to the grid of V1 will also trigger the circuit. In some practical-circuit applications, a positive trigger is applied to the grid of a "trigger-inverter" stage whose plate is connected in parallel with the plate of V1; the inverted trigger is then coupled through capacitor C2 to the grid of V2 as a negative trigger pulse. In any event, a cycle of

multivibrator operation is initiated by driving the normally conducting tube into cutoff, or by driving the tube that is normally cut off into conduction.

Failure Analysis.

No Output. The input trigger should be checked with an oscilloscope to determine whether it is being applied to the circuit and whether it is of the proper polarity and amplitude. Lack of an input trigger at the grid of V2 can be due to failure of the external input-trigger source.

Failure of the positive voltage supply, +Ebb, will disrupt the operation of the circuit, as will an open cathode circuit. With tubes (or a single twin-triode tube) installed in the circuit, the filament and plate voltages should be measured, as well as the grid bias voltage, to determine whether the applied voltages are within tolerance and whether plate-load resistor R3 or R4 or grid-bias resistor R1 or R2 is open. If coupling capacitor C1 or C2 opens, there will be no feedback signal to effect the multivibrator switching action. An open output coupling capacitor, C3 or C4, will prevent the output-gate signal from reaching the following stage.

Reduced Output. A reduction in output is generally caused by a defective tube; however, it can also be caused by a decrease in the applied plate voltage or an increase in the resistance of the associated plate-load resistor, R3 or R4. A leaky or shorted output coupling capacitor, C3 or C4, will form a voltage divider with the input resistor of the following stage. In this input resistor is returned to ground or to a negative voltage supply, the voltage at the plate of both V1 and V2 will be reduced, and the operation of the following stage will be upset by the change in voltage applied to its grid. Also, the additional current through plate-load resistor R3 or R4 may cause the resistor to burn out.

Incorrect Frequency or Gate Width. The plate-to-grid-coupled monostable multivibrator has no components governing the frequency of its output-gate signal; this frequency is governed by the input trigger applied to the circuit. Therefore, any change in the output-gate frequency is a result of improper operation of the trigger generating circuits. A change in the output-gate width, however, will result if there is a change in the value of either resistor R2, capacitor C2, or the applied voltage. A change in the resistance or capacitance of the R2-C2 timing control circuit will have the greatest effect on the gate width;

changes in the applied voltage will affect the gate width to a lesser degree.

TRIODE COMMON-CATHODE-RESISTOR-COUPLED MONOSTABLE MULTIVIBRATOR

Application.

The triode common-cathode-resistor-coupled monostable multivibrator produces a square-wave or rectangular-wave output for use as gating or timing signals.

Characteristics.

Circuit assumes a stable state, in which one tube normally conducts and the other tube is normally cut off.

Requires an input trigger to cause circuit operation; circuit returns to stable state upon completion of one cycle of operation.

Input trigger can be either negative or positive; negative trigger affects tube that is normally conducting, and positive trigger affects tube that is normally cut off.

Produces square-wave or rectangular-wave output gates of both positive and negative polarity in response to an input trigger.


Output gate length is determined by R-C time constant in grid circuit and by the applied voltage; output frequency is determined by input trigger frequency.

Circuit Analysis.

General. The triode common-cathode-resistor-coupled monostable multivibrator is functionally similar to the Triode Plate-to-Grid-Coupled Monostable Multivibrator discussed previously in this Section of the Handbook. The circuit has only one stable state, in which one tube normally conducts while the other tube is normally cut off, and will function for only one complete cycle upon the application of an input trigger pulse. To achieve the stable condition, the grid of the normally conducting tube is usually returned to its cathode or to B+ while the grid of the tube that is normally cut off is returned to ground or to a negative voltage (bias) supply. R-C coupling is provided from the plate of V1 to the grid of V2, but the coupling from V2 to V1 is effected across a common cathode resistor. Because the monostable multivibrator operates for only one


cycle in response to an input trigger pulse, the output frequency of this circuit is dependent upon the input trigger time constant of the grid circuit and by the applied voltage. Output signals can be taken from the plate of either or both electron tubes.

Circuit Operation. The following circuit schematic illustrates two triode electron tubes in a common-cathode-resistor-coupled monostable multivibrator configuration. Electron tubes V1 and V2 are identical-type triode tubes; although the accompanying schematic illustrates two separate triodes, a twin-triode is frequently used in this circuit. Capacitor C1 is the input coupling capacitor for application of a positive trigger to the grid of V1. Capacitor C2 provides coupling from the plate of V1 to the grid of V2. Resistor R1 returns the grid of V1 to ground, and resistor R2 returns the grid of V2 to the common cathode connection. Resistors R3 and R4 are the plate-load resistors for V1 and V2, respectively. Resistor R5 is the common cathode bias and coupling resistor for coupling from V2 to V1. Capacitors C3 and C4 are the output coupling capacitors for V1 and V2, respectively. The tube that is normally cut off is V1, and the tube that is normally conducting is V2.

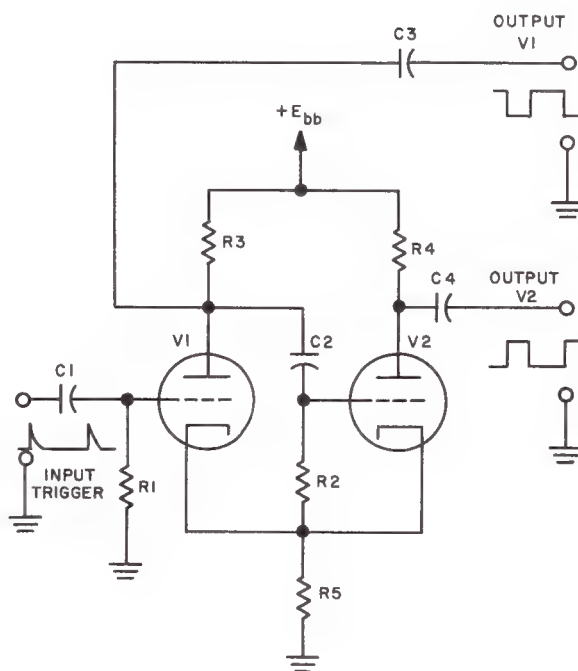


Triode Common-Cathode-Resistor-Coupled
Monostable Multivibrator

The following simplified schematic diagram illustrates the charge and discharge paths for capacitor C2. The cut-off time of V2 is determined by the discharge of capacitor C2 through resistor R2. Although the conduction resistance of V1 is included in the discharge path of C2, it is frequency; the output gate length is determined by the R-C small as compared with the resistance of R2, and can therefore be neglected. The cutoff time of V1 is determined by the period of the input trigger pulse. If the R2-C2 time constant is made exactly one-half the period of the trigger pulse, the multivibrator produces a symmetrical square-wave output; if the R2-C2 time constant is made longer or shorter than one-half the trigger pulse period, an asymmetrical rectangular-wave output is produced.

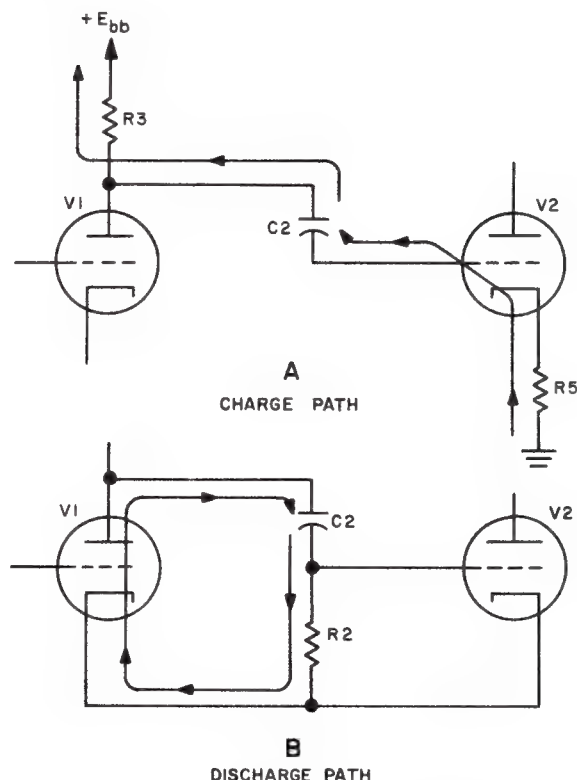

Charge and Discharge Paths for Capacitor C2

Consider now the operation of the triode common-cathode-resistor-coupled monostable multivibrator by referring to the preceding circuit illustrations and the following illustration of the idealized theoretical waveforms. When voltage is first applied, V2 goes into conduction and V1 cuts off. This action results from the fact that the grid of V2 is returned through resistor R2 to the cathode, initially placing this grid at the same potential as the cathode, and thus allowing V2 to conduct heavily. The plate current flow of V2 through common cathode resistor R5 makes the voltage at the top of the resistor positive with respect to ground, producing a bias voltage of sufficient amplitude to hold V1 cut off (since its grid is returned to ground through resistor R1), and still permit V2 to conduct. Thus, at time t_0 (start of time interval *a*) on the waveform illustration, the grid voltage of V2 (e_{g2}) is slightly positive, causing conduction through V2; as a result, the plate voltage (e_{p2}) of V2 decreases because of plate current flow through plate-load resistor R4. Also, as a result of V2 plate current, there is a positive voltage (e_k) developed across common cathode resistor R5, which provides the bias to cut off V1. The positive-going voltage at the plate of V1 (e_{p1}) is coupled through capacitor C2 to the grid of V2, driving the grid further positive. Also, at t_0 , coupling capacitor C2 charges through the low cathode-to-grid internal resistance of V2 (approximately 1K) and the plate-load resistor, R3, of V1. At t_0 , then the common-cathode-resistor-coupled monostable multivibrator assumes its stable state, in which V2 normally conducts and V1 is normally cut off; the circuit remains in this condition until a trigger pulse is applied.

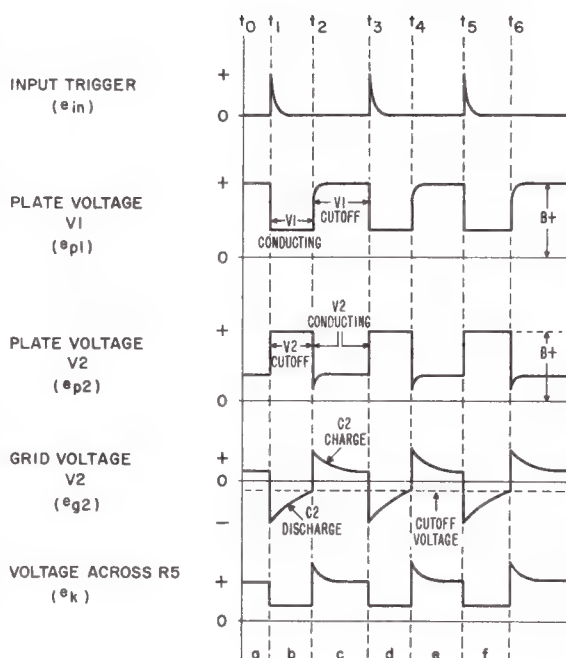

Theoretical Waveforms for Triode Common-Cathode-Resistor-Coupled Monostable Multivibrator

Assume now that a positive trigger pulse of sufficient amplitude to cause the tube to conduct is applied to the grid of V1 through coupling capacitor C1. The effect of this trigger pulse (e_{in} , applied at t_1) is to drive V1 into conduction, thus causing an increase in current through V1 and a decrease in the

plate voltage (ep_1) of V1. This negative-going voltage is applied instantaneously through capacitor C2 to the grid of V2, driving the grid voltage of V2 (eg_2) below cutoff. When the V2 plate current ceases, the voltage drop (ek) across cathode resistor R5 decreases to the level where it decreases the bias on V1, permitting this tube to conduct more heavily. Thus, at t_1 , a switching action occurs and the multivibrator is in a "temporary" stable state, in which V1 conducts and V2 is cut off.

During this temporary stable state (time interval *b*), capacitor C2 begins to discharge, causing the grid voltage of V2 (eg_2) to become less negative. The discharge path of C2 is downward through grid resistor R2 and then upward through the low cathode-to-plate conduction resistance of V1. At this time V1 alone is conducting; its plate current is limited by its own cathode bias, which is not sufficient to cut off V1. As the voltage (eg_2) on the grid of V2 becomes less negative, because of the discharging of capacitor C2, it soon reaches the point, at t_2 , where it is no longer of sufficient amplitude to hold V2 in cutoff. Consequently, V2 once again conducts, and the flow of V2 plate current through common cathode resistor R5 increases the voltage drop (ek) across this resistor, again increasing the bias of V1 and reducing the flow of plate current through V1. As the conduction through V1 decreases, the plate voltage (ep_1) of V1 rises toward the potential of the positive voltage supply, +Ebb. The positive-going signal at the plate of V1 is coupled through capacitor C2 to the grid of V2, driving this grid positive (waveform eg_2 , at t_2). Thus, capacitor C2 stops discharging and again begins charging. The voltage waveform at the grid of V2 (eg_2) has a small positive spike of the same time duration, as a result of the charging of coupling capacitor C2 when V2 again conducts. The plate voltage waveform of V2 (ep_2) has a small negative spike, and the voltage waveform across common cathode resistor R5 (ek) has a small positive spike of the same time duration as the positive spike on the V2 grid voltage waveform (eg_2). Hence, at t_2 , the multivibrator reverts to its original stable condition in which V2 conducts and V1 is cut off; the circuit remains in this condition (time interval *c*) until another positive trigger pulse is applied at t_3 .

Close examination of the waveforms reveals that the monostable multivibrator goes through one complete cycle of operation for each input trigger pulse. Also, the time of application of the trigger pulse

determines when V1 is driven into conduction, and the R-C time constant of R2-C2 and the applied voltage determine when V2 is driven into conduction. Thus, the monostable multivibrator output frequency is determined by the input trigger frequency, and the output gate width is determined by the discharging of capacitor C2 through resistor R2 toward the potential of the positive voltage supply.

A positive trigger pulse applied to the grid of the tube that is normally cutoff, as was done in this case, is not the only method by which the multivibrator circuit can be triggered. A negative trigger pulse applied directly to the cathode of V1 or applied to the grid of V2 and coupled to the cathode of V1 through the cathod-follower action of R5 serves the same purpose. In some practical-circuit applications, a positive trigger is applied to the grid of a "trigger-inverter" stage whose plate is connected in parallel with the plate of V1; the inverted trigger is then coupled through capacitor C2 to the grid of V2 as a negative trigger pulse. In any event, a cycle of multivibrator operation is initiated by driving the normally conducting tube into cutoff, or by driving the tube that is normally cut off into conduction.

Failure Analysis.

No Output. The input trigger should be checked with an oscilloscope to determine whether it is being applied to the circuit and whether it is of the proper polarity and amplitude. Lack of an input trigger at the grid of V1 can be due to an open coupling capacitor, C1, or to failure of the external input-trigger source.

Failure of the positive voltage supply, +Ebb, will disrupt the operation of the circuit, as will an open cathode circuit. With tubes (or a single twin-triode tube) installed in the circuit, the filament and plate voltages should be measured, as well as the bias voltage developed across the cathode resistance, to determine whether the applied voltages are within tolerance and whether plate-load resistor R3 or R4 or cathode bias resistor R5 is open. If coupling capacitor C2 opens, there will be no feedback signal to effect the multivibrator switching action. An open output coupling capacitor, C3 or C4, will prevent the output-gate signal from reaching the following stage.

Reduced Output. A reduction in output is generally caused by a defective tube; however, it can also be caused by a decrease in the applied voltage or an increase in the resistance of the associated plate-load

resistor, R3 or R4. A leaky or shorted output coupling capacitor, C3 or C4, will form a voltage divider with the input resistor of the following stage. If the input resistor of this following stage is returned to ground or to a negative voltage supply, the voltage at the plate of both V1 and V2 will be reduced, and the operation of this following stage will be upset by the change in voltage applied to its grid. Also, the additional current through plate-load resistor R3 or R4 may cause the resistor to burn out.

Incorrect Frequency or Gate Width. The common-cathode-resistor-coupled monostable multivibrator has no components governing the frequency of its output-gate signal; this frequency is governed by the input trigger applied to the circuit. Therefore, any change in the output-gate frequency is a result of improper operation of the trigger-generating circuits. A change in the output-gate width, however, will result if there is a change in the value of either resistor R2, capacitor C2, or the applied voltage. A change in the resistance or capacitance of the R2-C2 timing control circuit will have the greatest effect on the gate width; changes in the applied voltage will affect the gate width to a lesser degree.

BASIC ONE-SHOT TRANSISTOR MULTIVIBRATOR

Application.

The basic one-shot transistor multivibrator is used to provide a delay function for compatible logic circuits, or is used as gate in computers, electronic control or communication equipment.

Characteristics.


- Usually uses fixed bias.
- Requires an on-trigger, but will automatically turn itself off.
- Operates at the same repetition frequency as that of the trigger.
- Has one stable state (monostable).
- Is a saturating type of multivibrator.

Circuit Analysis.

General. The basic one-shot multivibrator is a triggered circuit, which requires a trigger pulse to initiate action. Once the trigger pulse initiates the action, the circuit automatically completes one full cycle of operation. Either the stable state of cutoff or

saturation is used. Normally, one transistor is operated saturated while the other is at cutoff. When the circuit is triggered by an external pulse, the operating point is moved from the initial stable region to the other stable (operating) region. The time constant of the circuit elements determines how long the circuit will remain in the stable (operating) region. At the end of the time constant, the operating point then moves back to the original stable region.

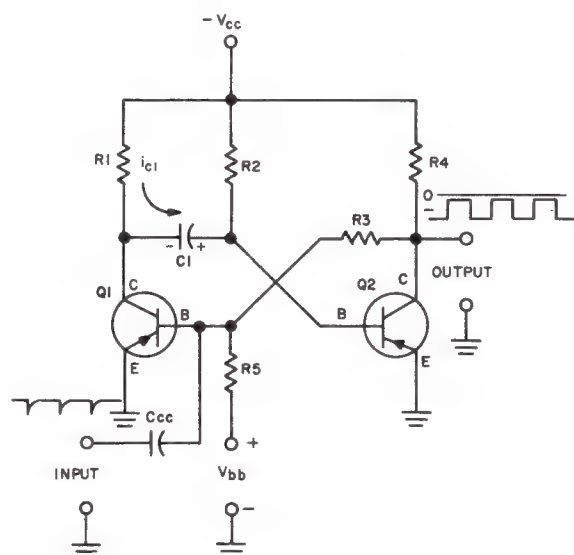Circuit Operation. The schematic of a typical basic monostable (one-shot) multivibrator is shown in the accompanying illustration.



Basic PNP One-Shot Multivibrator


Fixed forward bias is applied to the base of Q2 by resistor R2, while the voltage divider consisting of R4, R3, and R5 form a fixed bias divider between the base bias supply and the collector supply and ground. Thus Q1 is biased slightly positive, and is cut off by this reverse-bias. Resistor R4 also is the collector resistor for Q2, and R1 serves a similar function for Q1. Resistor R3 serves as the collector-to-base feedback resistor for Q1, while C1 is the feedback capacitor for Q2. Both emitters are grounded and a cross-connected, grounded-emitter circuit is used. The input is applied through coupling capacitor Ccc, while the output is taken directly from the collector of Q2.

If desired, the output load could also be capacitively coupled.

In the quiescent condition, transistor Q2 conducts heavily while transistor Q1 is cut off. This action occurs initially because of the large negative forward bias placed on the base of Q2 by resistor R2, which is connected back to the negative supply. Thus an application of power Q2 quickly saturates, and develops a positive-swinging output across R4, which is fed back to the base of Q1 through resistor R3, holding the transistor at cut off. During the on-period of Q2, feedback capacitor C1 is charged positively, through R1 and the low base-emitter saturation resistance of Q2. The low saturation resistance of Q2 base-emitter junction acts as a switch, connecting R1 and C1 in series with the negative supply source and ground.

When the negative trigger is applied to Q1 base through coupling capacitor Ccc (time t_1 in the following waveform illustration), transistor Q1 is driven into conduction by this forward bias. The flow of Q1 collector current through R1 reduces the effective collector voltage and produces a positive-swinging voltage across R4, which is applied through feedback capacitor C1 as a positive reverse bias to cut off Q2. As the collector current of Q2 reduces, the voltage across collector resistor R4 rises toward that of the negative collector supply, and an increasing forward-bias is fed back to the base of Q1 through feedback resistor R3. Thus Q2 is cut off and Q1 is turned on. Operation is now reversed and the output from Q2 is a negative voltage. Since C1 is positively charged, when disconnected from ground by Q2 being driven into cut off, the capacitor holds the base of Q2 highly positive (reverse-biased) while it discharges. The discharge path is through the low collector-to-emitter saturation resistance of Q1, and ground on one side, and through R2 to the negative supply on the other side. The discharge is shown by the typical RC discharge curve on the trailing edge of the V_{b2} waveform (time t_1 to t_2) in the waveform illustration. Q2 remains nonconducting until the base voltage drops to zero and the base of Q2 goes slightly negative at time t_2 . Q2 immediately starts to conduct, and the flow of collector current through R4 produces a positive-swinging voltage, which is applied through feedback resistor R3 to drive Q1 in a reverse-biased direction and stop conduction through Q1. This action occurs quickly, and a positive square wave now appears at the output of Q2. The quiescent state of

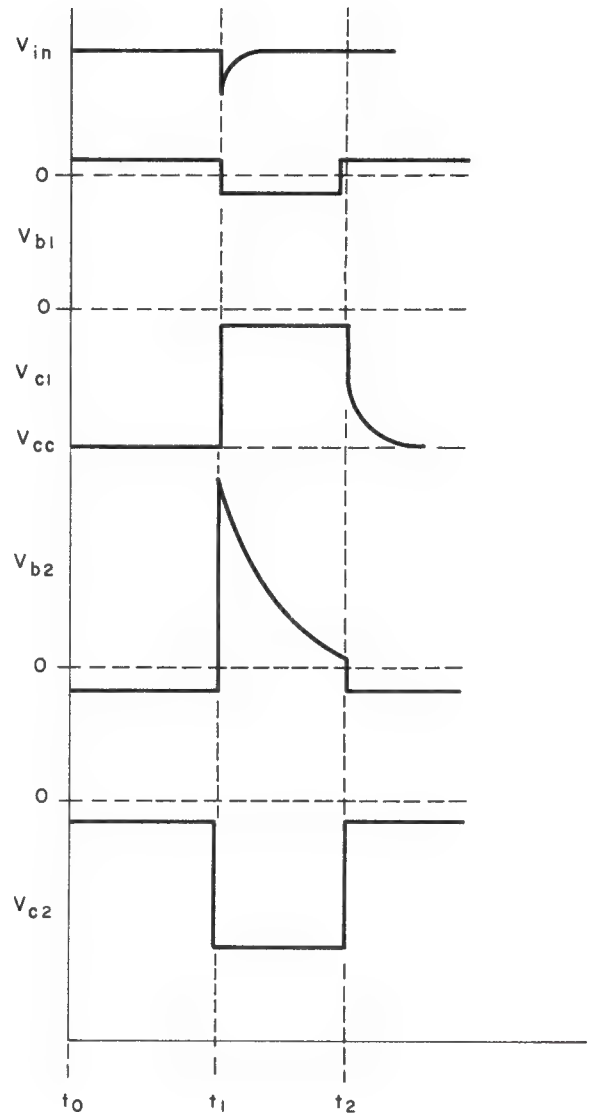operation continues until the next trigger (time t_2), whereupon the switching action described above is again repeated.



Monostable Multivibrator Waveforms

Failure Analysis.

General. When making voltage checks, use a vacuum-tube voltmeter to avoid the low values of

shunting resistance employed on the low voltage ranges. Be careful to observe proper polarity when checking continuity with an ohmmeter, since a forward bias through any of the transistor junctions will cause a false low-resistance reading.

No Output. Lack of supply voltage, an open collector resistor, R4, or a defective transistor can cause a no-output indication. Measure the supply and collector voltages with a high resistance voltmeter, if the supply voltage is normal but the collector voltage is low or zero, either R4 is open or Q2 is shorted. Checking the resistance of R4 with an ohmmeter will determine if Q2 needs replacement.

Continuous Output. If bias resistor R2 increases with age or opens, the base of Q2 will tend to float in a zero-biased condition. The collector of Q2 will rise to the supply value, and a continuous output with no switching action will occur. The same indication will also occur if R3 is open, since Q1 will be biased beyond cut off and the trigger will not be large enough to initiate action. At the very best, an attempt to switch may be noticed, with the circuit reverting back to the cut off condition when the trigger ceases. Such action is best observed with an oscilloscope. Should R5 open, a negative (forward-bias) will be placed on Q1, and both Q1 and Q2 will conduct with a continuous positive output from Q2. On the other hand if Q1 is stopped from conducting by a short across R5, Q2 will continue to operate alone, also producing a continuous positive output. Because of the few resistors in the circuit a quick check with an ohmmeter will determine if they are satisfactory. Should C1 be open circuited, no feedback can be applied from the collector of Q1 to the base of Q2 and switching will not occur, again Q2 will rest in a conducting position with a positive output near zero. If C1 becomes short circuited, R1 and R2 will be paralleled and a higher forward bias will be applied. Q2 base, holding it in conduction and preventing operation. Use an in-circuit capacitance checker to check the capacity of C1. If the resistors are satisfactory, together with C1, then Q1 must be defective if a continuous output still occurs.

Low Output. Low collector voltage, improper bias, or defective transistors can cause a low output voltage. A change in collector resistor R4 will also affect the output amplitude. Use an oscilloscope to check the output waveform and determine where the reduced amplitude exists. Then check for the proper bias and collector voltages in that portion of the cir-

cuit. If normal voltages are present and the collector resistor is within tolerance, but a low output amplitude still exists, it can only be because of reduced collector current.

Incorrect Frequency. Since the multivibrator has no parts which govern the frequency of operation, it is governed by the applied input trigger. Hence any change in frequency must be the result of improper operation of the turn-on trigger generating circuits.

Incorrect Pulse Width. While the frequency is governed by the input trigger, the length of time the circuit operates before flipping back to the initial stable condition is determined by the circuit time-constant governed by the charge and discharge of C1 through R2, and also R1. Thus if the value of C1 changes or that of R1 or R2 changes, or if the saturation resistance of transistor Q2 changes appreciably, a different pulse width may be expected. Observation of the output pulse on an oscilloscope will show any change in width. Measure the value of C1 with an in-circuit capacitance checker, and check the resistance of R1 and R2. If these parts appear satisfactory replace Q2 with a known good transistor. Any delays in switching are the result of minority carrier injection into the base at saturation, which requires a finite discharge time until the circuit can be triggered. Should a noticeable delay in switching occur after the circuit has been operating properly, check all parts values.

PHANTASTRON MULTIVIBRATOR

Application.

The phantastron multivibrator is used to generate a rectangular-wave output having extreme linearity and accuracy, for use as gating or timing signals.

Characteristics.

Operation is similar to that of a monostable multivibrator.

Pulse width or delay varies linearly with the applied control voltage.

Requires an electron tube of the pentode or pentagrid type.

Circuit operation turn-on is by application of negative trigger to the plate, or positive trigger to the suppressor, of a pentode or the additional control grid of a pentagrid tube; turn-off is automatic by internally generated waveform.

Output can be taken from the cathode, screen, or plate, and may be either positive or negative, as selected.


Provides either a low-impedance or high-impedance output, as determined by output connections.

Circuit Analysis.

General. The phantatron circuit is considered to be a relaxation oscillator similar to the multivibrator in operation; the screen-coupled and cathode-coupled phantatron circuits are analogous to the plate-to-grid-coupled and cathode-coupled monostable multivibrators, respectively. A difference in the operation of the circuits is that the monostable multivibrator derives its timing from an exponential waveform developed by an R-C network, whereas the phantatron uses a basic Miller-type sweep generator to produce a linear timing waveform. The phantatron is usually turned on by the application of a gating or trigger pulse, and is turned off automatically by an internally generated waveform. Both a positive and a negative rectangular-wave output with well-defined leading edges may be obtained from the phantatron, depending on the output connections.

For a thorough analysis of Miller circuit operation, and the operation of the screen-coupled, and fast-recovery pentode phantatron circuits, refer to the discussion of time delay circuits in the Special Circuits Section of this Handbook.

Circuit Operation. The following schematic illustrates a pentagrid tube (type 6SA7 or equivalent) in a cathode-coupled phantatron multivibrator configuration. Although the schematic illustrates a pentagrid tube, a sharp-cutoff pentode, such as the 6AS6 or its electrically equivalent premium-type miniature 5725 or subminiature 5636, could be used as well, provided that the necessary circuit modifications are incorporated as illustrated and described in the Special Circuits Section of this Handbook.

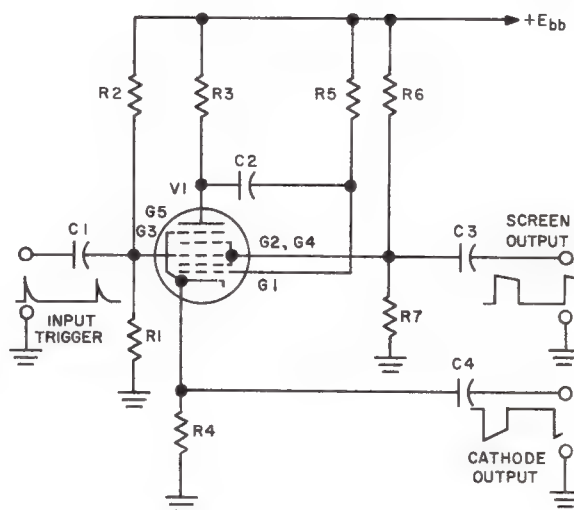

Pentagrid Phantatron Multivibrator


The functions of the electrodes of the pentagrid tube used in this circuit are as follows: Grid 1, which is the control grid, controls the total tube (cathode) current. Grids 2 and 4, connected internally, act as the screen grid. The cathode, the control grid (grid 1), and the screen grid (grids 2 and 4) correspond to the normally conducting tube of the cathode-coupled monostable multivibrator. (For analysis of Triode Common-Cathode-Resistor-Coupled Monostable Multivibrator operation, refer to the applicable discussion given earlier in this Section of the Handbook.) Grid 3, which is additional control grid, controls the division between screen and plate current; a negative voltage on this grid reduces plate current and increases screen current; a positive voltage has the opposite effect. Also, grid 3 has the effect of changing the cathode current, since some of the

electrons returned toward the cathode by its action pass through the screen grid and reduce the space charge near the cathode, thereby causing the increase of screen current to be less than the corresponding decrease in plate current. Grid 5, connected internally to the cathode, is suppressor grid. The cathode, the additional control grid (grid 3), and the plate correspond to the normally cutoff tube of the cathode-coupled monostable multivibrator.

The circuit components of the pentagrid-tube phantastron multivibrator serve the following functions: Resistors R1 and R2 form a voltage divider from the positive voltage supply (+E_{bb}) to ground, setting the bias level of grid 3 and thereby initially holding plate current cut off. Resistor R3 is the plate-load resistor. The cathode-bias resistor, R4, also serves as the cathode-load resistor. Resistors R6 and R7 form a voltage divider from the positive voltage supply (+E_{bb}) to ground, setting the operating voltage level of the screen grid. Resistor R5 returns the control grid to the positive voltage supply, setting the bias level that initially permits the screen grid to conduct heavily. Operation of the circuit occurs at the rate determined by the discharge of feedback capacitor C2 through resistor R5; in some circuits this grid-return resistor, which usually has a value exceeding 1 megohm, is made variable to set the maximum delay or pulse width of the output gate. Capacitor C2 also provides feedback from plate to grid to allow rapid response to any changes in the plate voltage. Capacitor C1 couples the input trigger to grid 3; this trigger initiates (or turns on) the phantastron action. Capacitors C3 and C4 are the output coupling capacitors for the screen grid and cathode, respectively; a positive gate is obtained from the screen grid, and a negative gate from the cathode. If desired, a linear sawtooth waveform can be obtained from the plate of the phantastron circuit.

The following simplified schematic diagram shows the charge and discharge paths for capacitor C2. The charge path (part A of the illustration) is from ground through cathode resistor R4, the low cathode-to-grid conduction resistance of V1, to the right side of the capacitor, and then from the left side of the capacitor through plate-load resistor R3 and the positive voltage supply back to ground. This path causes capacitor C2 to charge at an exponential rate during the time that plate current is cut off and the tube is drawing heavy screen current and only slight control grid current. The discharge path (part B of the illus-


tration) for capacitor C2 is from its right side through grid-bias resistor R5 and the positive voltage supply (+E_{bb}) to ground, and then from ground through cathode resistor R4 and the low cathode-to-plate conduction resistance of V1 to the left side of the capacitor. This path causes capacitor C2 to discharge at a linear rate during the time that screen current is low (near cutoff) and the tube is drawing heavy plate current. The linear discharge of capacitor C2 results from the Miller effect of tube V1, producing a much longer discharge circuit than could be obtained from R5-C2 alone. That is, although the discharge rate of capacitor C2 is determined by the time constant of R5-C2, the discharge capacitance is not the value of C2 alone, but is effectively the value of C2 times the quantity unity plus the gain of V1 ($1 + A$), which is the Miller effect.

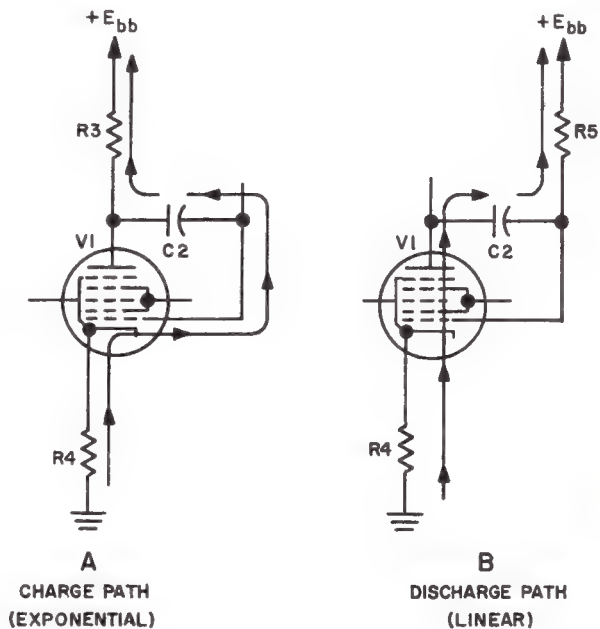

Charge and Discharge Paths for Capacitor C2

The operation of the phantastron multivibrator can be more easily understood by referring to the preceding circuit illustrations and the accompanying waveform illustration during the following discussion. When voltage is first applied, the plate section of the tube is in cutoff and there is heavy screen grid current. The conduction of screen current

is a result of the operating voltage on this electrode, as determined by voltage divider resistor R6 and R7. The voltage is sufficiently positive to attract electrons emitted by the cathode as a result of the positive bias on the control grid (positive voltage return to B+ through resistor R5); this permits the flow of cathode current at this time. In addition to permitting heavy screen current, the positive control grid draws current and charges capacitor C2 through the path described previously. The total screen and control grid current through cathode-bias resistor R4 produces a voltage drop across this resistor. Comparison of the e_k and e_{g3} waveforms reveals that the positive potential at the top of resistor R4 is now greater than the positive potential at grid 3, which is obtained from the action of voltage divider resistors R1 and R2. A bias voltage is therefore established between grid 3 and the cathode; this bias is sufficient to cut off plate current, while having no effect on screen or control grid current. Because there is no plate current, the plate potential is maximum positive (at B+), as depicted by the e_p voltage waveform during time interval *a*. Notice, also, during time interval *a*, that the screen voltage ($e_{g2,4}$) is at a minimum as a result of heavy screen current, the cathode voltage (e_k) is positive, and the control grid voltage (e_{g1}) is positive because the positive-going signal at the plate is fed back through capacitor C2. This, then, is the stable state of the phantatron multivibrator; the circuit remains in this condition (heavy screen current and plate current cut off) until a positive trigger pulse is applied to grid 3 at t_1 .

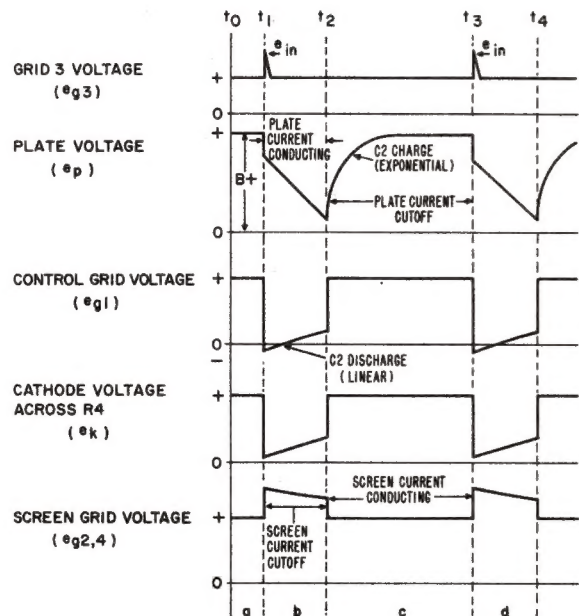

Theoretical Waveforms for Pentagrid
Phantatron Multivibrator

When the positive trigger (e_{in}) is applied through capacitor C1 to grid 3, it overcomes the bias on this grid and permits plate current to flow. This current, in turn, causes an immediate drop in the plate voltage developed across plate-load resistor R3. The

negative-going signal at the plate is coupled through capacitor C2 to the control grid, where it drives the grid sufficiently negative to reduce the total cathode current. Since the total cathode current is reduced, the screen current is also reduced; thus a positive-going voltage is produced at the screen grid. Through cathode-follower action, the negative-going signal at the control grid is coupled to the cathode, where it reduces the bias between the cathode and grid 3. With a decrease in this bias voltage there is an increase in plate current, resulting in a further drop in plate voltage. The action just described is cumulative and instantaneous, so that when the positive trigger is applied to grid 3 at t_1 , there is an immediate increase in plate current and a sharp fall in plate voltage, a decrease in screen current and a sharp increase in screen voltage, a decrease in total cathode current and sharp decrease in cathode voltage, and the control grid is driven negative. All of the voltage relationships are depicted at t_1 on the waveform illustration.

The fact that the plate current increases while the cathode current decreases is possible because the screen current is now decreasing. Therefore, the rise in plate current results from the fact that the plate draws current which had previously gone to the screen grid. That is, the bias between the cathode and grid 3 is decreasing, which is a regenerative action, causing the plate current to increase. Simultaneously, the bias between the cathode and control grid is increasing, which is a degenerative action, causing the total tube current (and screen grid current) to decrease. The screen grid current is only reduced—not cut off completely; if it were cut off completely, the plate current would also be cut off and circuit would not function. Hence, there must be a point where the regenerative and degenerative effects are equal and the current stabilizes for an instant. This is the instant (at t_1 , when the sharp drop in plate voltage ceases) at which capacitor C2 begins its linear discharge action.

As capacitor C2 discharges during time interval b , it loses electrons from its right side, in effect making this side of the capacitor (and the control grid as well) more positive to reduce the bias between the control grid and the cathode. The reduction in control grid bias permits a heavier flow of plate current through the tube, which gradually raises the voltage drop across cathode-bias resistor R4 (ek waveform) and lowers the plate voltage (ep waveform), as illustrated during time intervals b . The rate of change

in tube current is governed by the discharge rate of capacitor C2 through resistor R5. Thus, in discharging, the control grid side of capacitor C2 gradually becomes more positive, causing an increase in plate current that produces a constant decrease in plate voltage. The positive voltage increment on the control grid is always slightly greater than the negative-going plate signal it produces; therefore, the the grid potential gradually rises and the plate potential gradually drops, as depicted by the respective grid (eg₁) and plate (ep) waveforms during time interval b .

An important characteristic of this circuit is the extreme linearity of the rate of change in the plate voltage and grid voltage during time interval b . The positive-going grid increases tube conduction, thereby decreasing the internal resistance of the tube. A decreasing resistance in series with a capacitor results in a linear voltage discharge of the capacitor, instead of the exponential discharge obtained when a fixed value of resistance is in series with a capacitor. The phantastron plate voltage during time interval b is, therefore, a linear downward-sloping voltage, and the grid voltage is a linear upward-sloping voltage.

The action described during time interval b continues until the plate voltage becomes so low (only a few volts) that the tube can no longer amplify the changes in plate voltage. At this instant, t_2 , capacitor C2 stops discharging and the control grid is rapidly driven positive, causing the tube current to increase at a very fast rate. The rapid rise of current through cathode-bias resistor R4 produces a high positive potential on the cathode, which, in relation to the positive potential at grid 3, is a bias sufficient to cut off plate current. Since the total tube current is increasing at this instant, the additional current must flow in the screen grid circuit. The action now occurring is regenerative; as the plate voltage goes positive because of plate-current cutoff, the control grid goes positive and causes an increase in tube current, which produces a higher voltage drop across resistor R4 to increase the bias on grid 3 and further cut off plate current. Thus, the phantastron multivibrator has returned to its original stable state of plate current cutoff and maximum screen grid current, as illustrated during time interval c , until the next trigger pulses at t_3 again causes a cycle of phantastron action. Before the phantastron is ready for the next cycle of operation, however, capacitor C2 must

charge through the relatively long exponential R-C time constant circuit of R3-C2. Because of the relatively slow recharging of C2, a long period must pass after completion of the phantastron gate before the application of the next trigger pulse. The long charge time of C2 is depicted on the plate voltage (ep) waveform during time interval c.

As mentioned previously, when the phantastron is triggered (turned on) there is a sudden drop in the screen current. This produces on the screen grid a positive-going voltage with a steep leading edge (eg₂₁₄ waveform). As the tube current gradually increases, producing the linear drop in plate voltage, the screen current increases in the same manner, but by a much smaller amount. The screen waveform will therefore decrease linearly by a small amount until the point of plate-current cutoff (described previously) is reached. At the instant of plate-current cutoff, the screen current increases sharply, causing a sharp drop in screen voltage, as depicted by the trailing edge of the eg₂₁₄ voltage waveform; this is the positive-gate output waveform coupled through capacitor C3 to the screen output terminals. The resultant negative-gate output, ek, taken across cathode resistor R4, is coupled through capacitor C4 to the cathode output terminals. This negative-gate waveform also has steep leading and trailing edges, with the flat portion falling off in amplitude at a linear rate.

From the circuit action just described, it is evident that changing the value of the applied voltage will determine the point, and the time, at which the plate voltage "bottoms", with respect to the time of application of the input trigger. Changing the value of either feedback capacitor C2 or grid resistor R5 will also affect the pulse width by controlling the rate of discharge of capacitor C2. For example, increasing the value of either resistor R5 or capacitor C2 will increase their R-C time constant, thereby causing capacitor C2 to discharge more slowly and increase the width of the delay gate. A decrease in the value of either resistor R5 or capacitor C2 will have the opposite effect on the width of the delay gate. In some phantastron circuits the grid resistor, R5 in this case, is made variable so as to control the maximum width of the delay gate.

Variations of the phantastron multivibrator include separate diodes for input trigger application and clamping the plate voltage at a predetermined level, and a cathode follower in the charging circuit of

feedback capacitor C2. The diode in the input trigger circuit acts as a trigger injector and also as a disconnecting diode to effectively isolate the trigger circuit after the phantastron action has started. The "plate-voltage catching", or clamping, diode establishes the maximum level of plate voltage, and since the turnoff level is fixed, effectively controls the time during which the phantastron produces the linear delay gate. The cathode follower is added to reduce the time required for recharging the feedback capacitor, C2 in this case, between gates; the plate circuit of the pentagrid tube merely raises the grid voltage of the cathode follower, and conduction through this tube charges the capacitor at a much faster rate than through the normal plate-load-resistor charge path. The latter type of circuit is known as a "fast-recovery phantastron". All the variations in phantastron circuitry mentioned in this paragraph are described in more detail in the Special Circuits Section of this Handbook.

Failure Analysis.

No Output. The input trigger should be checked with an oscilloscope to determine whether it is being applied to the circuitry and whether it is of the proper polarity and amplitude. Lack of an input trigger at the additional control grid (grid 3) can be due to an open input coupling capacitor, C1, or to failure of the external input-trigger source. It is also possible for excessive bias to make the circuit inoperative because the input trigger amplitude is not sufficient to overcome the bias and initiate the phantastron action. Such a condition is indicated when an input trigger can be seen with an oscilloscope on grid 3 of the pentagrid tube and voltage appears on all tube elements, but either the control grid or cathode voltage is higher than normal. This is most likely to occur when a negative voltage source is used with a common bleeder network to obtain the bias (as in a screen-coupled circuit). Since this cathode-coupled pentagrid circuit develops its own bias, an excessive current drain or short-circuit condition would be needed to increase the bias to the non-operating point.

Failure of the positive voltage supply, +Ebb, will disrupt the operation of the circuit, as will an open cathode circuit. With a tube installed in the circuit, the filament, plate, screen, and grid 3 voltages should be measured, as well as the bias voltage developed across the cathode resistance, to determine whether

the applied voltages are within tolerance and whether an associated electrode resistor is open. If feedback capacitor C2 is open, there will be no feedback signal to promote the phantastron action. An open output coupling capacitor, C3 or C4, will prevent the output-gate signal from reaching the following stage.

Reduced Output. A reduction in output is generally caused by a defective tube; however, a low screen gate output can also be caused by a decrease in applied voltage or a change in resistance value in the screen circuit. Low cathode gate output indicates low cathode current, which is the sum of all tube element currents, and thus may be caused by any one of numerous conditions (decreased tube conductance, reduce plate or screen voltage, etc). Usually, a voltage check will locate the defective circuit and component. A leaky or shorted output coupling capacitor, C3 or C4, will form a voltage divider with the input resistor of the next stage. If the input resistor of this next stage is returned to ground or to a negative supply, the voltage at the screen grid or cathode will be reduced, and the operation of the stage will upset by the change in voltage applied to its grid.

Distorted or Unstable Output. Distortion is indicated by a nonlinear waveform or an inaccurate time delay. Linearity and accuracy of the output gate

waveform development is the basic property of this circuit, with the controlling elements being the applied d-c control voltage and the R-C time constant in the feedback circuit. Control voltage trouble may occur when the circuit uses a separate external control voltage from a separate power supply, since power supply fluctuations can easily change the operating level and, therefore, the gate duration. A change of time constant due to changes in circuit values or to feedback capacitor failure or leakage will change the rate of operation and hence the gate length; this should be most noticeable for the longer gate lengths. False triggering due to pickup of noise or stray pulses in the control cabling (on remote units) may affect both the turn-on and turn-off of the gate. This instability, or jitter, can also be caused by power supply fluctuations. An oscilloscope waveform check at each electrode is usually the best method of checking for the cause of the jitter, which can then be traced to its source.

Incorrect Frequency. The phantastron multivibrator has no components governing the frequency of its output gate signal; this frequency is governed by the input trigger applied to the circuit. Therefore, any change in the output gate frequency is a result of improper operation of the trigger generating circuits.